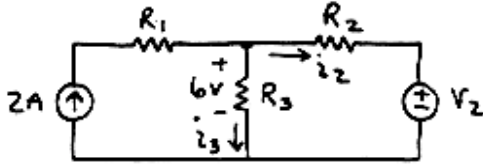


### Chapter 3 – Resistive Circuits

#### Exercises

Ex 3.3-1



$$i_3 = \frac{6V}{R_3} = \frac{6V}{2\Omega} = 3A$$

from KCL at top node


$$i_2 = 2 - i_3 = 2 - 3 = -1A$$

KVL around 2nd loop :  $-6 + R_2 i_2 + v_2 = 0 \Rightarrow v_2 = 6 - (1)(-1) = 7V$

Ex 3.3-2  $-18 + 0 - 12 - v_a = 0 \Rightarrow v_a = -30V$

Ex 3.3-3  $-v_a - 10 + 4v_a - 8 = 0 \Rightarrow v_a = \frac{18}{3} = 6V$

Ex 3.4-1

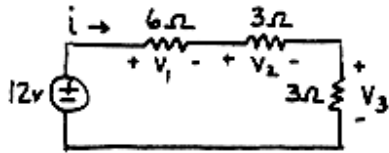


from voltage divider

$$v_3 = 12 \left( \frac{3}{3+9} \right) = 3V \therefore i = \frac{v_3}{3} = 1A$$

$$\left. \begin{aligned} \text{now } P_{6\Omega} &= i^2(6) = (1)^2(6) = 6W \\ P_{3\Omega_1} &= i^2(3) = (1)^2(3) = 3W \\ P_{3\Omega_2} &= i^2(3) = (1)^2(3) = 3W \end{aligned} \right\} P_{6\Omega} + P_{3\Omega_1} + P_{3\Omega_2} = 12W \text{ absorbed}$$

$$P_{\text{source}} = v_i = (12V)(1A) = 12W \text{ supplied}$$

Ex 3.4-2

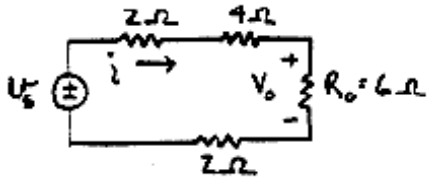

if  $P_0 = 6W$  and  $R_0 = 6\Omega \Rightarrow i^2 = \frac{P_0}{R_0} = \frac{6}{6} = 1$  or  $i = 1A$

$\therefore v_0 = iR_0 = (1)(6) = 6V$


from KVL:  $-v_s + i(2+4+6+2) = 0 \Rightarrow v_s = 14i = 14V$

Ex 3.4-3 from voltage divider  $\Rightarrow v_m = \frac{25}{25+75} 8 = 2V$

Ex 3.4-4 from voltage divider  $\Rightarrow v_m = \frac{25}{25+75} (-8) = -2V$

**Ex. 3.5-1**

Equiv. Ckt.

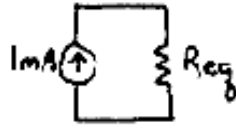

$$\frac{1}{R_{eq}} = \frac{1}{1} + \frac{1}{1} + \frac{1}{1} + \frac{1}{1}$$

$$R_{eq} = \underline{1/4 \text{ k}\Omega}$$

$$i \text{ in each } R = \frac{1}{4}(1\text{mA}) = \underline{\frac{1}{4}\text{mA}}$$

**Ex 3.5-2** from current divider  $\Rightarrow i_m = \frac{10}{10+40}(-5) = -2 \text{ A}$

**Ex 3.6-1**  $R_p = \frac{(4)(2)}{4+2} = \frac{8}{6} = \underline{\frac{4}{3}\Omega}$

$\therefore V = R_p (3\text{A}) = \frac{4}{3}(3) = \underline{4\text{V}}$

ProblemsSection 3-3 Kirchoff's Laws

**P3.3-1** KVL:  $v_1 + 2 - 3 - 6 - 8 + 4 = 0$  (outside loop)

$$\underline{v_1 = +11 \text{ V}}$$

KVL:  $v_2 + 2 - 3 - 6 = 0$  (right mesh)

$$\underline{v_2 = 7 \text{ V}}$$

KVL:  $3 + 2 - i_3 = 0$  (top node)

$$\underline{i_3 = 5 \text{ A}}$$

**P3.3-2** KVL:  $-v_1 + 2 + 4 + 5 = 0$  (outside loop)

$$\underline{v_1 = 11 \text{ V}}$$

KCL:  $-1 + 3 + i_4 = 0$  (top, left node)

$$\underline{i_4 = -2 \text{ A}}$$

KCL:  $1 + i_3 - 3 = 0$  (bottom, left node)

$$\underline{i_3 = 2 \text{ A}}$$

KCL:  $-i_4 + 2 + i_2 = 0$  (top, right node)

$$-(-2) + 2 + i_2 = 0 \Rightarrow \underline{i_2 = -4 \text{ A}}$$

**P3.3-3**

KVL :  $-12 - R_2(3) + v = 0$  (outside loop)

$$v = 12 + 3R_2 \text{ or } R_2 = \frac{v-12}{3}$$

KCL  $i + \frac{12}{R_1} - 3 = 0$  (top node)

$$i = 3 - \frac{12}{R_1} \text{ or } R_1 = \frac{12}{3-i}$$

$$v = 12 + 3(3) = \underline{21 \text{ V}}$$

(a)  $i = 3 - \frac{12}{6} = \underline{1 \text{ A}}$

(b)  $R_2 = \frac{2-12}{3} = -\frac{10}{3} \Omega$ ;  $R_1 = \frac{12}{3-1.5} = \underline{8 \Omega}$

(c)  $24 = -12 i$ , because 12 and  $i$  adhere to the passive convention.


$$\therefore \underline{i = -2 \text{ A}} \text{ and } R_1 = \frac{12}{3+2} = \underline{2.4 \Omega}$$

$9 = 3v$ , because 3 and  $v$  do not adhere to the passive convention

$$\therefore \underline{v = 3} \text{ and } R_2 = \frac{3-12}{3} = \underline{-3 \Omega}$$

The situations described in (b) and (c) cannot occur if  $R_1$  and  $R_2$  are required to be nonnegative.

**P3.3-4**

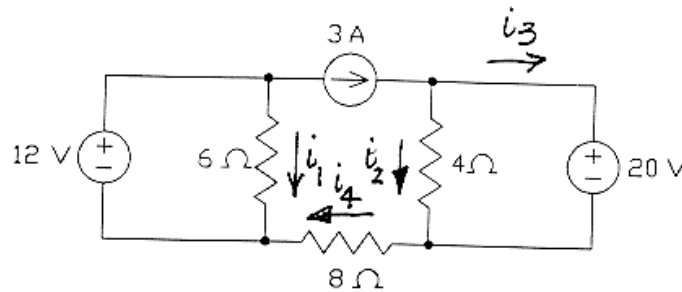

$$i_1 = \frac{12}{6} = 2 \text{ A}$$

$$i_2 = \frac{20}{4} = 5 \text{ A}$$

$$i_3 = 3 - i_2 = -2 \text{ A}$$


$$i_4 = i_2 + i_3 = 3 \text{ A}$$

Power absorbed by the  $4 \Omega$  resistor =  $4 \cdot i_2^2 = \underline{100 \text{ W}}$

Power absorbed by the  $6 \Omega$  resistor =  $6 \cdot i_1^2 = \underline{24 \text{ W}}$

Power absorbed by the  $8 \Omega$  resistor =  $8 \cdot i_4^2 = \underline{72 \text{ W}}$

**P3.3-5**

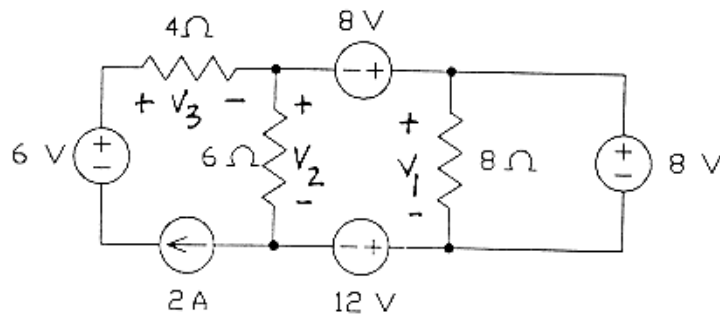

$$v_1 = 8 \text{ V}$$

$$v_2 = -8 + 8 + 12 = 12 \text{ V}$$


$$v_3 = 2 \cdot 4 = 8 \text{ V}$$

$$4 \Omega : P = \frac{v_3^2}{4} = \underline{16 \text{ W}}$$


$$6 \Omega : P = \frac{v_2^2}{6} = \underline{24 \text{ W}}$$

$$8 \Omega : P = \frac{v_1^2}{8} = \underline{8 \text{ W}}$$


**P3.3-6**

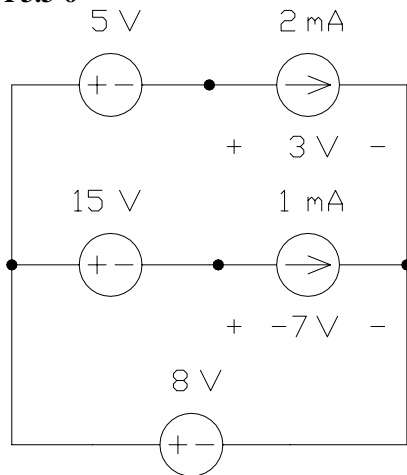

**P3.3-7**

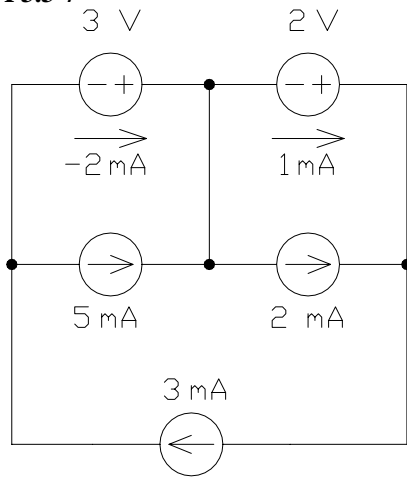

**P3.3-8**

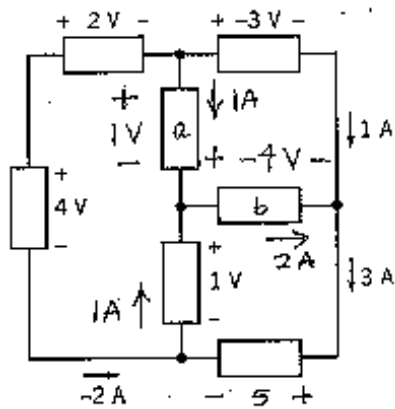


$$P_a = (1V)(1A) = \underline{+1 \text{ Wabsorbed}}$$

$$P_b = (-4V)(2A) = \underline{-8 \text{ Wabsorbed}}$$

$$= \underline{-8 \text{ Wabsorbed}}$$

**P3.3-9**

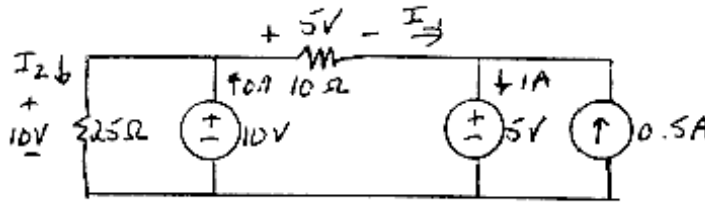

$$I_1 = \frac{5V}{10\Omega} = 0.5 \text{ A}$$

$$I_2 = \frac{10V}{25\Omega} = 0.4 \text{ A}$$

$$P_{10V} = (-10)(0.9) = -9W_{\text{absorbed}} = \underline{9W_{\text{delivered}}}$$

$$P_{5V} = (5)(1) = \underline{5W_{\text{absorbed}}}$$


$$P_{0.5A} = (-5)(0.5) = -2.5W_{\text{absorbed}} = \underline{2.5W_{\text{delivered}}}$$

$$P_{10\Omega} = (5)(0.5) = \underline{2.5W_{\text{absorbed}}}$$

$$P_{25\Omega} = (10)(0.4) = \underline{4W_{\text{absorbed}}}$$

$$\Sigma P_{\text{absorbed}} = \underline{0W} \quad \text{energy balance}$$

**P3.3-10**

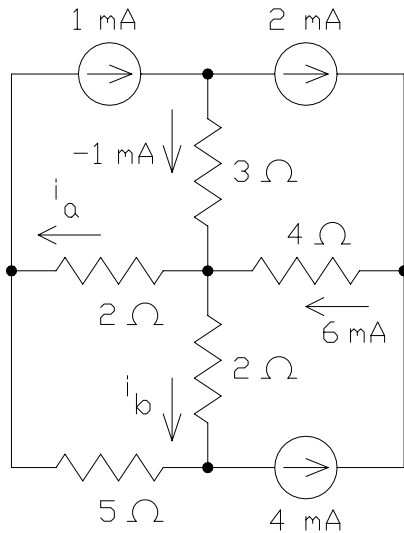

$$i_a + i_b = 6 - 1 = 5 \text{ mA} = 0.005 \text{ A}$$

$$-2i_a + 2i_b - 5(i_a - 0.001) = 0$$

Solving yields:

$$i_a = 0.00167 = 1.67 \text{ mA}$$

$$i_b = 0.005 - i_a = 0.00333 = 3.33 \text{ mA}$$

**Section 3-4 A Single-Loop Circuit – The Voltage Divider**

**P3.4-1**  $V_1 = \frac{6}{6+3+5+4} 12 = \frac{6}{18} 12 = \underline{4 \text{ V}}$

$$V_2 = \frac{3}{18} 12 = \underline{2V}; \quad V_3 = \frac{5}{18} 12 = \underline{\frac{10}{3} \text{ V}}$$

$$V_4 = \frac{4}{18} 12 = \underline{\frac{8}{3} \text{ V}}$$


**P3.4-2**

(a)  $R = 6 + 3 + 2 + 4 = \underline{15\Omega}$

(b)  $i = \frac{28}{R} = \frac{28}{15} = \underline{1.867 \text{ A}}$

(c)  $P = 28 \cdot i \quad (28 \text{ and } i \text{ do not adhere to the passive convention.})$   
 $= 28(1.867) = \underline{52.27 \text{ W}}$

P3.4-3

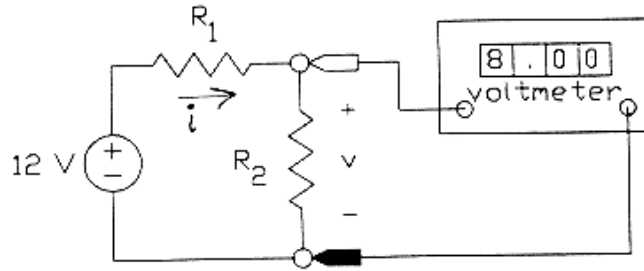


$$iR_2 = v = 8 \text{ V}$$

$$12 = iR_1 + v = iR_1 + 8$$

$$\Rightarrow 4 = iR_1$$

- (a)  $i = \frac{8}{R_2} = \frac{8}{100}$ ;  $R_1 = \frac{4}{i} = \frac{4 \cdot 100}{8} = \underline{50\Omega}$
- (b)  $i = \frac{4}{R_1} = \frac{4}{100}$ ;  $R_2 = \frac{8}{i} = \frac{8 \cdot 100}{4} = \underline{200\Omega}$
- (c)  $1.2 = 12 i \Rightarrow i = 0.1 \text{ A}$ ;  $R_1 = \frac{4}{i} = \underline{40\Omega}$
- $$R_2 = \frac{8}{i} = \underline{80\Omega}$$

P3.4-4

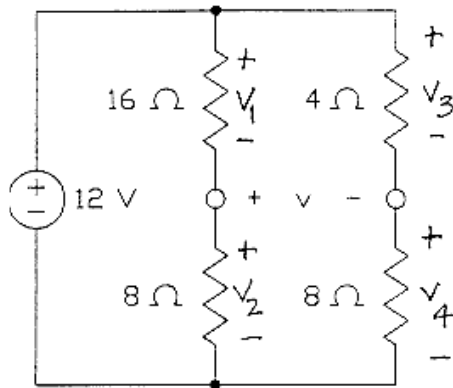

Voltage division

$$v_1 = \frac{16}{16+8} 12 = 8 \text{ V}$$

$$v_3 = \frac{4}{4+8} 12 = 4 \text{ V}$$

KVL:  $v_3 - v - v_1 = 0$

$$\underline{v = -4 \text{ V}}$$

P3.4-5

using voltage divider:  $v_0 = \left( \frac{100}{100+2R} \right) v_s$

with  $v_s = 20 \text{ V}$  and  $v_0 = 9 \text{ V}$ ,  $R = 61\Omega$

with  $v_s = 28 \text{ V}$  and  $v_0 = 13 \text{ V}$ ,  $R = 58\Omega$

$$\left. \begin{array}{l} \text{with } v_s = 20 \text{ V and } v_0 = 9 \text{ V, } R = 61\Omega \\ \text{with } v_s = 28 \text{ V and } v_0 = 13 \text{ V, } R = 58\Omega \end{array} \right\} \underline{R = 60\Omega}$$

Section 3-5 Parallel Resistors and Current Division

**P3.5-1**

$$i_1 = \frac{\frac{1}{6}}{\frac{1}{6} + \frac{1}{3} + \frac{1}{2} + 1} \quad 4 = \frac{1}{1+2+3+6} \quad 4 = \frac{1}{3} \text{ A}$$

$$i_2 = \frac{\frac{1}{3}}{\frac{1}{6} + \frac{1}{3} + \frac{1}{2} + 1} \quad 4 = \frac{2}{3} \text{ A}; \quad i_3 = \frac{\frac{1}{2}}{\frac{1}{6} + \frac{1}{3} + \frac{1}{2} + 1} \quad 4 = 1 \text{ A}$$

$$i_4 = \frac{1}{\frac{1}{6} + \frac{1}{3} + \frac{1}{2} + 1} \quad 4 = 2 \text{ A}$$

**P3.5-2**

(a)  $\frac{1}{R} = \frac{1}{6} + \frac{1}{12} + \frac{1}{4} = \frac{1}{2} \Rightarrow R = 2$

(b)  $v = 6 \cdot 2 = 12 \text{ V}$

(c)  $P = 6 \cdot 12 = 72 \text{ W}$

**P3.5-3**

$$i = \frac{8}{R_1} \text{ or } R_1 = \frac{8}{i}$$

$$8 = R_2(2-i) \Rightarrow i = 2 - \frac{8}{R_2} \text{ or } R_2 = \frac{8}{2-i}$$

(a)  $i = 2 - \frac{8}{12} = \frac{4}{3} \text{ A}; R_1 = \frac{8}{4/3} = 6\Omega$


(b)  $i = \frac{8}{12} = \frac{2}{3} \text{ A}; R_2 = \frac{8}{2 - 2/3} = 6\Omega$

(c)  $R_1 = R_2$  will cause  $i = \frac{1}{2} \cdot 2 = 1 \text{ A}$ . The current in both  $R_1$  and  $R_2$  will be 1 A.

$$2 \cdot \frac{R_1 R_2}{R_1 + R_2} = 8; \text{ when } R_1 = R_2 \quad 2 \cdot \frac{1}{2} R_1 = 8 \Rightarrow R_1 = 8$$

$$\therefore R_1 = R_2 = 8\Omega$$

**P3.5-4**

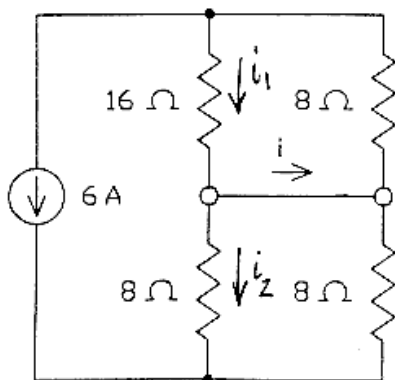

Current division:

$$i_1 = \frac{8}{16+8}(-6) = -2 \text{ A}$$

$$i_2 = \frac{8}{8+8}(-6) = -3 \text{ A}$$

$$i = i_1 - i_2 = +1 \text{ A}$$

**P3.5-5** current division:  $i_2 = \left( \frac{R_1}{R_1 + R_2} \right) i_s$  and Ohm's Law:  $v_o = i_2 R_2$  yields


$$i_s = \left( \frac{v_o}{R_2} \right) \left( \frac{R_1 + R_2}{R_1} \right)$$

plugging in  $R_1 = 4\Omega$ ,  $v_o = 9\text{ V}$  gives  $i_s = 3.15\text{ A}$

and  $R_1 = 6\Omega$ ,  $v_o = 13\text{ V}$  gives  $i_s = 3.47\text{ A}$

So any  $\underline{3.15\text{ A} \leq i_s \leq 3.47\text{ A}}$  keeps  $9\text{ V} \leq V_o < 13\text{ V}$ .

**P3.5-6**

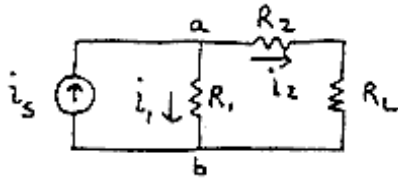

$$\text{now } i_2 = \frac{v_{ab}}{R_2 + R_L} = \frac{40}{10 + 30} = 1\text{ A}$$

$$\text{from KCL: } i_1 = i_s - i_2 = 2 - 1 = 1\text{ A}$$

$$\therefore R_1 = \frac{V_{ab}}{i_1} = \frac{40\text{ V}}{1\text{ A}} = \underline{40\Omega}$$

### Section 3-7 Circuit Analysis

**P3.7-1**

$$(a) \quad R = 16 + \frac{48 \cdot 24}{48 + 24} = \underline{32\Omega}$$

$$(b) \quad v = \frac{32 \cdot 32}{8 + \frac{32 \cdot 32}{32 + 32}} \cdot 24 = \underline{16\text{ V}}; \quad i = \frac{16}{32} = \underline{\frac{1}{2}\text{ A}}$$


$$(c) \quad i_2 = \frac{48}{48 + 24} \cdot \frac{1}{2} = \underline{\frac{1}{3}\text{ A}}$$

**P3.7-2**

$$(a) \quad R_1 = 4 + \frac{3 \cdot 6}{3 + 6} = \underline{6\Omega}$$

$$(b) \quad \frac{1}{R_p} = \frac{1}{12} + \frac{1}{6} + \frac{1}{6} \Rightarrow R_p = \underline{2.4\Omega}$$
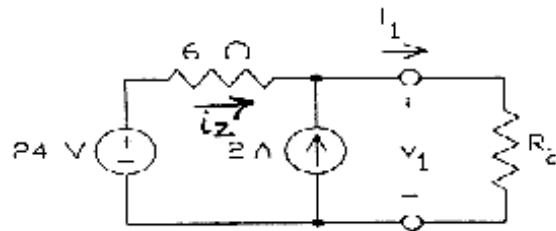
$$R_2 = 8 + R_p = \underline{10.4\Omega}$$



$$(c) \quad \begin{aligned} i_2 + 2 &= i_1 \\ -24 + 6i_2 + R_2 i_1 &= 0 \\ -24 + 6(i_1 - 2) + 10.4i_1 &= 0 \end{aligned}$$


$$i_1 = \frac{36}{16.4} = \underline{2.2\text{ A}} \quad v_1 = i_1 R_2 = 2.2(10.4) = \underline{22.88\text{ V}}$$







(d) 
$$i_2 = \frac{\frac{1}{6}}{\frac{1}{6} + \frac{1}{6} + \frac{1}{12}} \cdot 2.2 = \underline{0.878 \text{ A}}, \quad v_2 = (0.878)(6) = \underline{5.3 \text{ V}}$$


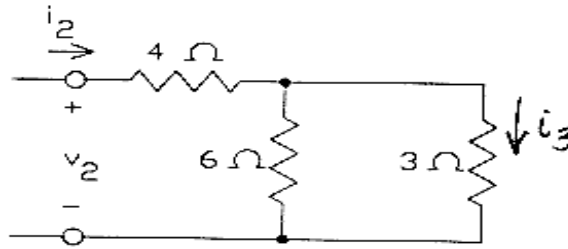
(e) 
$$i_3 = \frac{6}{3+6} i_2 = 0.585 \text{ A}$$
  

$$P = 3i_3^2 = \underline{1.03 \text{ W}}$$



**P3.7-3**

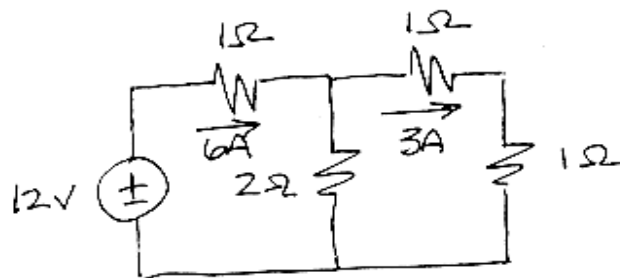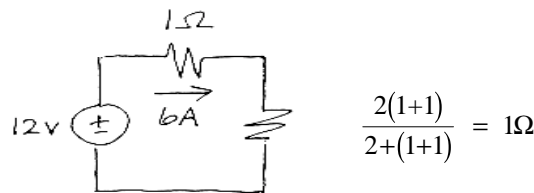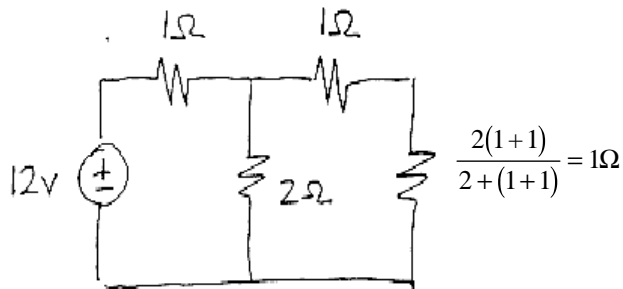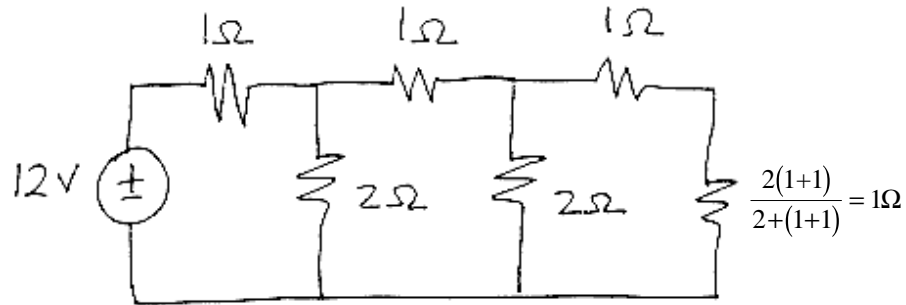

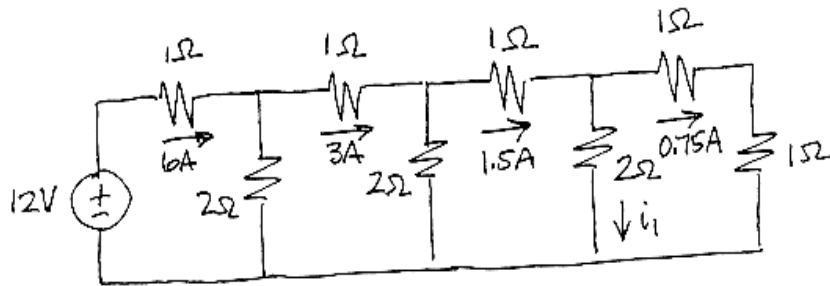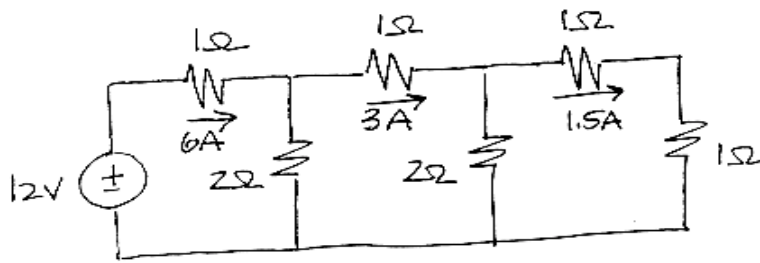


$$i_1 = \frac{1}{2}(1.5) = \underline{\underline{\frac{3}{4} \text{ A}}}$$

**P 3.7-4**


(a)  $\frac{1}{R_2} = \frac{1}{24} + \frac{1}{12} + \frac{1}{8} \Rightarrow R_2 = 4\Omega$  and  $R_1 = \frac{(10+8) \cdot 9}{(10+8)+9} = 6\Omega$

(b)

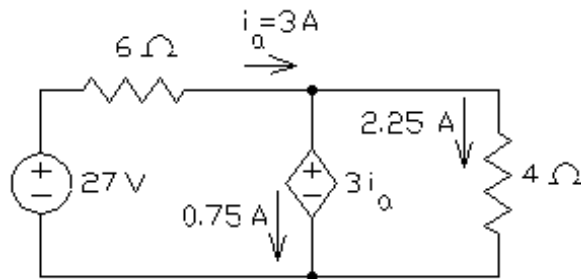


First, apply KVL to the left mesh to get  $-27 + 6i_a + 3i_a = 0 \Rightarrow i_a = 3 \text{ A}$ . Next, apply KVL to the right mesh to get  $4i_b - 3i_a = 0 \Rightarrow i_b = 2.25 \text{ A}$ .

(c)

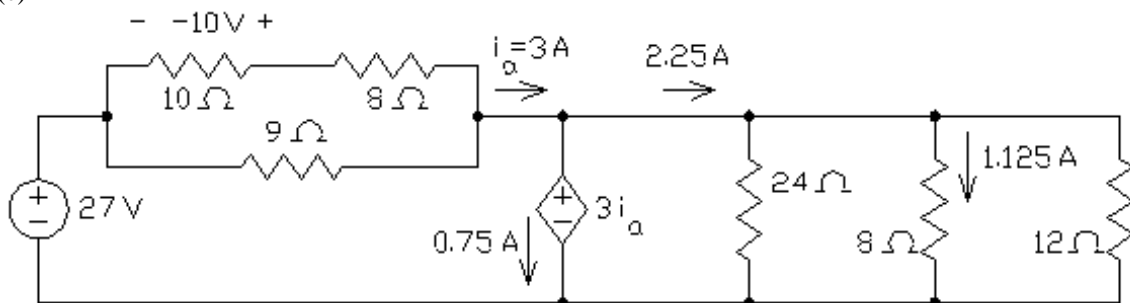


$$i_2 = \frac{\frac{1}{8}}{\frac{1}{24} + \frac{1}{8} + \frac{1}{12}} 2.25 = 1.125 \text{ A} \quad \text{and} \quad v_1 = -(10) \left[ \frac{9}{(10+8)+9} 3 \right] = -10 \text{ V}$$

**P3.7-5**

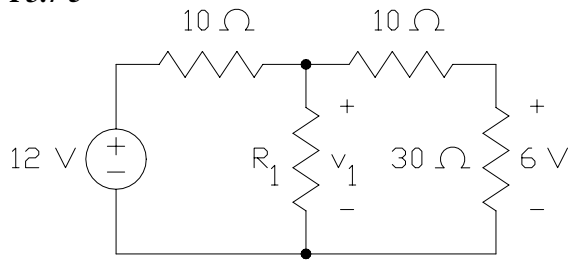
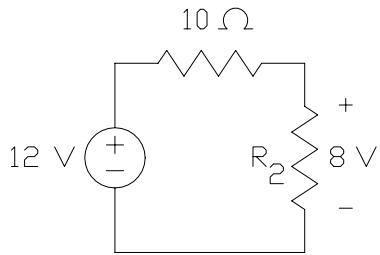
$$\frac{30}{10+30} v_1 = 6 \Rightarrow v_1 = 8 \text{ V}$$




$$\frac{R_2}{R_2+10} 12 = 8 \Rightarrow R_2 = 20 \Omega$$

$$20 = \frac{R_1(10+30)}{R_1+(10+30)} \Rightarrow R_1 = 40 \Omega$$


*Alternate values that can be used to change the numbers in this problem:*

meter reading, V	Right-most resistor, Ω	$R_1, \Omega$
6	30	40
4	30	10
4	20	15
4.8	20	30

**P3.7-6**

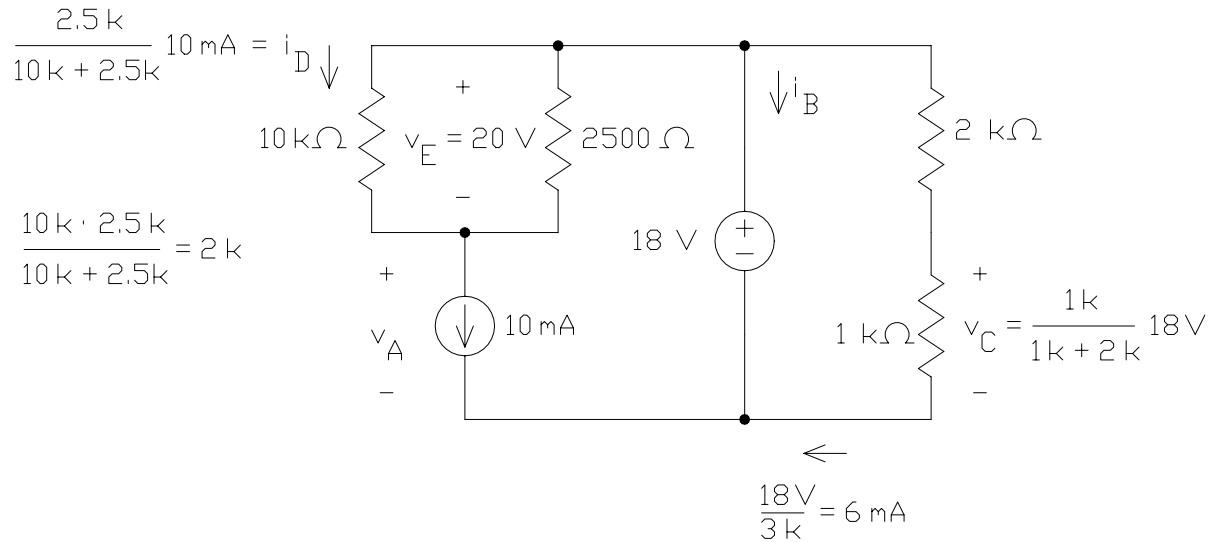


**P 3.7-7**

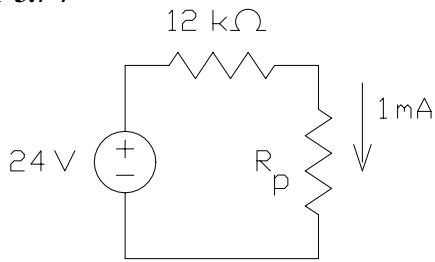

$$1 \times 10^{-3} = \frac{24}{12 \times 10^3 + R_p} \Rightarrow R_p = 12 \times 10^3 = 12 \text{ k}\Omega$$

$$12 \times 10^3 = R_p = \frac{(21 \times 10^3) R}{(21 \times 10^3) + R} \Rightarrow R = 28 \text{ k}\Omega$$

**P3.7 ^**

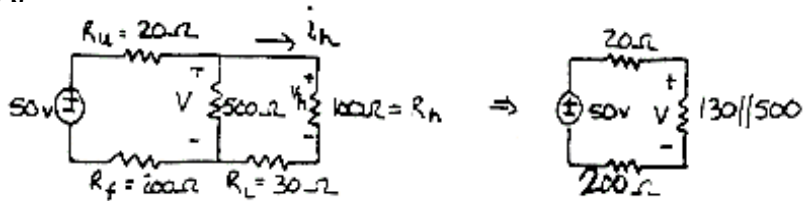




(Note:  $R_h = 100\Omega$ )




$$\text{Voltage divider} \Rightarrow v = 50 \left( \frac{130 \parallel 500}{130 \parallel 500 + 200 + 20} \right) = 15.963 \text{ V}$$

$$\therefore v_h = v \left( \frac{100}{100 + 30} \right) = (15.963) \left( \frac{10}{13} \right) = 12.279 \text{ V}$$

$$\therefore i_h = \frac{v_h}{100} = 122.79 \text{ A}$$


**P 3.7-9**

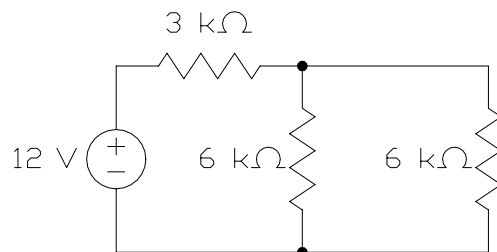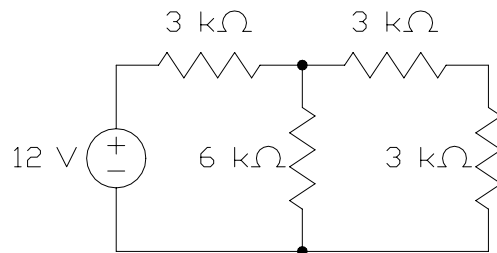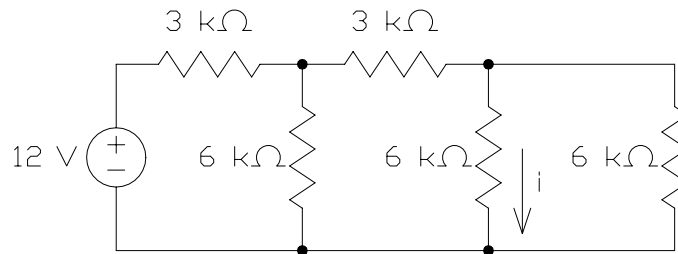

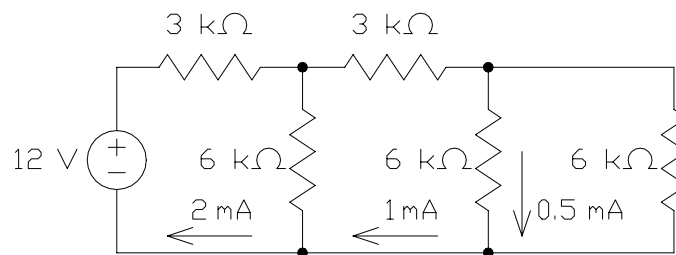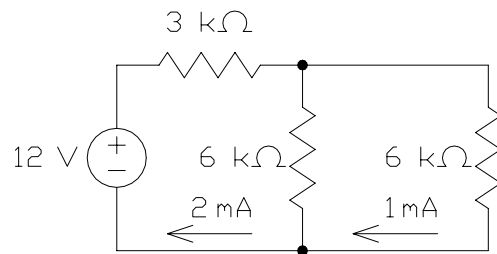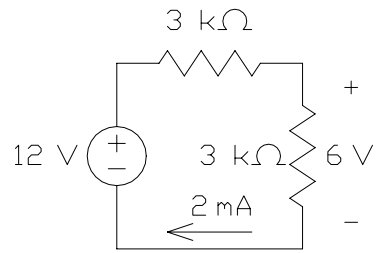

**P3.7-10**

reduce ckt.

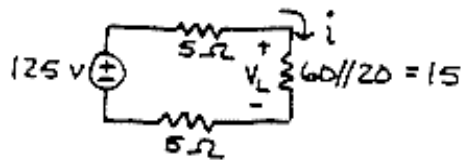


$$i = \frac{125\text{V}}{25\Omega} = 5\text{ A}$$


$$\therefore v_L = 15i = 15(5) = 75\text{ V}$$

$$\therefore P_L = \frac{v_L^2}{R_L} = \frac{(75)^2}{20} = \underline{281.25\text{ W}}$$

P 3.7-11

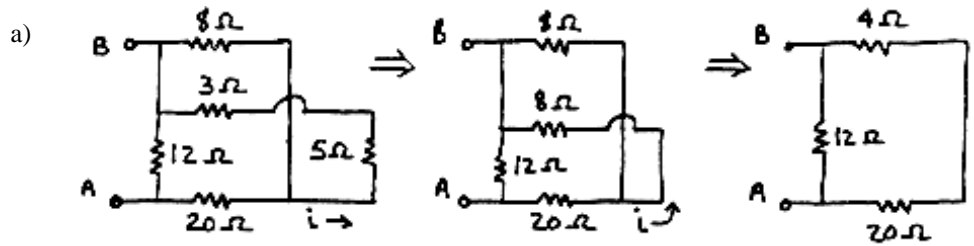
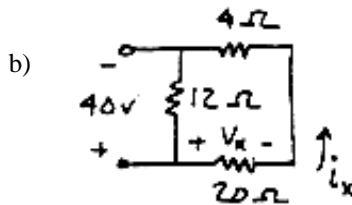
$$R_{eq} = 24 \parallel 12 = \frac{(24)(12)}{24 + 12} = \underline{8\Omega}$$




from voltage divider


$$v_x = 40 \left( \frac{20}{20+4} \right) = 100/3 \text{ V} \quad \therefore i_x = \frac{100/3}{20} = \underline{\frac{5}{3} \text{ A}}$$

from current divider  $i = i_x \left( \frac{8}{8+8} \right) = \underline{\frac{5}{6} \text{ A}}$


P3.7-12

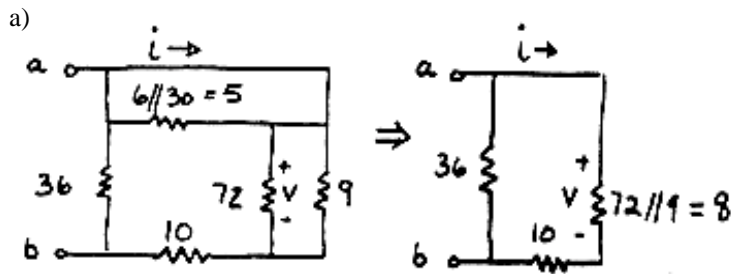
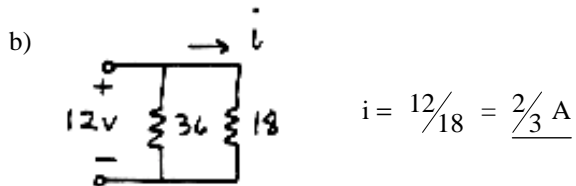
$$R_{eq} = 36 \parallel 18 = \frac{(36)(18)}{36 + 18} = \underline{12\Omega}$$



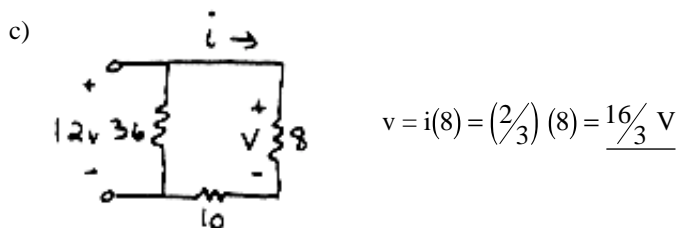
$$i = \frac{12}{18} = \underline{\frac{2}{3} \text{ A}}$$



$$v = i(8) = \left( \frac{2}{3} \right) (8) = \underline{\frac{16}{3} \text{ V}}$$

P3.7-13

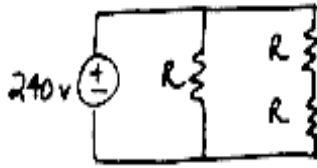


$$R_{eq} = \frac{2R(R)}{2R+R} = \frac{2}{3}R$$

$$P_{\text{deliv. to ckt}} = \frac{v^2}{R_{eq}} = \frac{240^2}{\frac{2}{3}R} = 1920 \text{ W}$$

Thus  $R=45\Omega$

P3.7-14

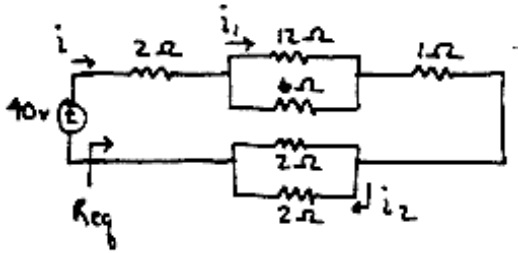

$$R_{eq} = 2 + 1 + (6 \parallel 12) + (2 \parallel 2)$$


$$= 3 + 4 + 1 = \underline{8\Omega}$$

$$\therefore i = \frac{40}{R_{eq}} = \frac{40}{8} = \underline{5 \text{ A}}$$

$$\text{from current divider } i_1 = i \left( \frac{6}{6+12} \right) = (5) \left( \frac{1}{3} \right) = \underline{\frac{5}{3} \text{ A}}$$

$$i_2 = i \left( \frac{2}{2+2} \right) = (5) \left( \frac{1}{2} \right) = \underline{\frac{5}{2} \text{ A}}$$

P3.7-15

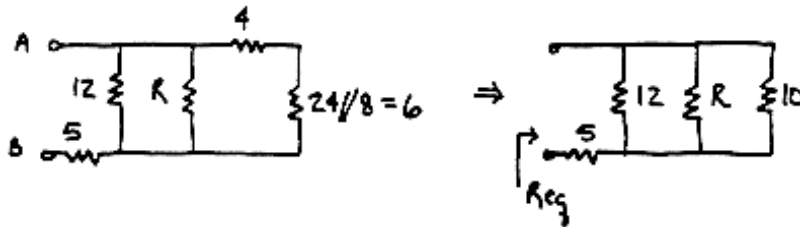


$$R_{eq} = 5 + \frac{1}{\frac{1}{12} + \frac{1}{R} + \frac{1}{10}} = 9; \text{ solving for } R \text{ yields } \underline{R = 15\Omega}$$

P3.7-16

R in parallel with  $R = \frac{R}{2}$ , R series with  $R = 2R$


$$\frac{R}{2} \parallel 2R = \frac{\left(\frac{R}{2}\right)(2R)}{\frac{R}{2} + 2R} = \frac{2}{5}R \leftarrow \text{same for both sides}$$
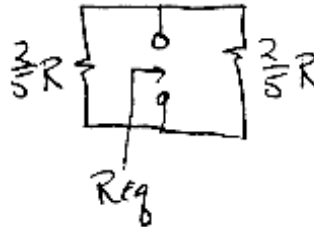
$$R_{eq} = \frac{\left(\frac{2}{5}R\right)\left(\frac{2}{5}R\right)}{\frac{2}{5}R + \frac{2}{5}R} = \frac{R}{5} \text{ but } R_{eq} = 20\Omega, \therefore \underline{R = 100\Omega}$$



## Verification Problems

### VP 3-1

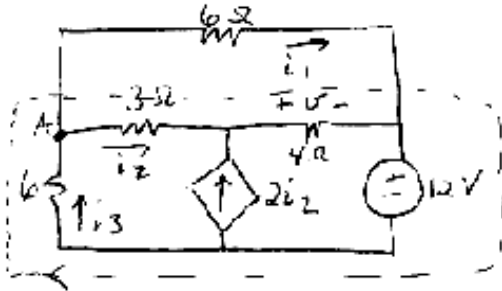


$$\begin{aligned} \text{KCL @ A: } i_3 &= i_1 + i_2 \\ -1.167 &= -0.833 + (-0.333) \\ -1.167 &= -1.166 \quad \text{OK} \end{aligned}$$

$$\begin{aligned} \text{KVL around dotted loop} \\ 6i_3 + 3i_2 + v + 12 &= 0 \\ \text{yields } v &= -4.0 \text{ V} \quad \underline{\text{not } v = -2.0 \text{ V}} \end{aligned}$$
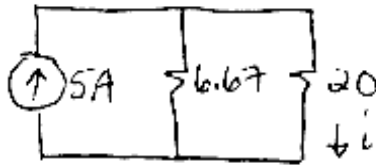
### VP 3-2

reduce circuit  $5 + 5 = 10$  in parallel with  $20\Omega$  gives  $6.67\Omega$



by current division;


$$i = \left( \frac{6.67}{20 + 6.67} \right) 5 = \underline{1.25 \text{ A}}$$

$\therefore$  Reported value was correct.

### VP 3-3

$$v_0 = \left( \frac{320}{320 + 650 + 230} \right) (24) = \underline{6.4 \text{ V}} \quad \therefore \text{Reported value was incorrect.}$$

### VP 3-4

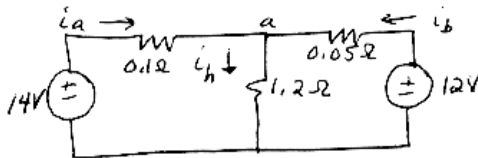

$$\text{KVL left loop: } -14 + 0.1i_a + 1.2i_h = 0$$

$$\text{KVL right loop: } -12 + 0.05i_b + 1.2i_h = 0$$

KCL @ a:  $i_a + i_b = i_h$  ← This alone shows the reported results were incorrect.


Solving the three above equations yields:

$$\underline{i_a = 16.8 \text{ A}} \quad \underline{i_h = 10.3 \text{ A}} \quad \therefore \text{Reported values were incorrect.}$$

$$\underline{i_b = -6.49 \text{ A}}$$



**VP3-5**

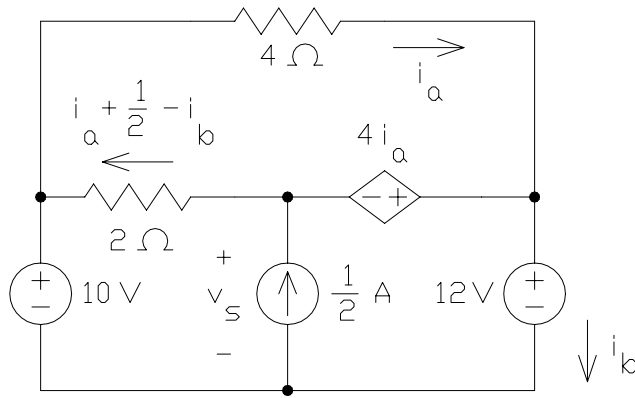


Top mesh:  $0 = 4 i_a + 4 i_a + 2 \left( i_a + \frac{1}{2} - i_b \right) = 10(-0.5) + 1 - 2(-2)$

Lower left mesh:  $v_s = 10 + 2 \left( i_a + 0.5 - i_b \right) = 10 + 2(2) = 14 \text{ V}$

Lower right mesh:  $v_s + 4 i_a = 12 \Rightarrow v_s = 12 - 4(-0.5) = 14 \text{ V}$

The KVL equations are satisfied so the analysis is correct.

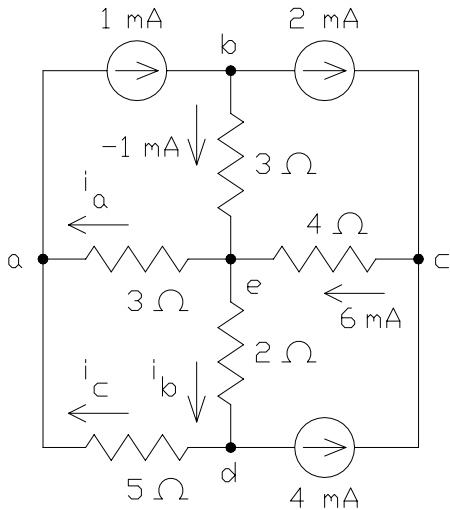**VP 3-6** Apply KCL at nodes b and c to get:



KCL equations:

Node e:  $-1 + 6 = 0.5 + 4.5$


Node a:  $0.5 + i_c = -1 \Rightarrow i_c = -1.5 \text{ mA}$

Node d:  $i_c + 4 = 4.5 \Rightarrow i_c = 0.5 \text{ mA}$

That's a contradiction. The given values of  $i_a$  and  $i_b$  are not correct.

## Design Problems

### DP 3-1

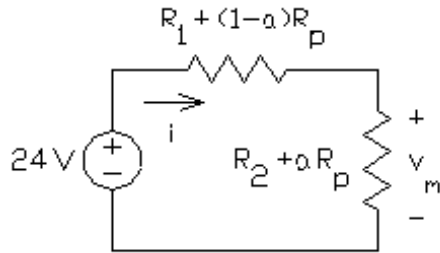

Using voltage division:

$$v_m = \frac{R_2 + aR_p}{R_1 + (1-a)R_p + R_2 + aR_p} 24 = \frac{R_2 + aR_p}{R_1 + R_2 + R_p} 24$$

$$v_m = 8 \text{ V when } a = 0 \Rightarrow$$

$$\frac{R_2}{R_1 + R_2 + R_p} = \frac{1}{3}$$

$$v_m = 12 \text{ V when } a = 1 \Rightarrow$$

$$\frac{R_2 + R_p}{R_1 + R_2 + R_p} = \frac{1}{2}$$

The specification on the power of the voltage source indicates

$$\frac{24^2}{R_1 + R_2 + R_p} \leq \frac{1}{2} \Rightarrow R_1 + R_2 + R_p \geq 1152 \Omega$$

Try  $R_p = 2000 \Omega$ . Substituting into the equations obtained above using voltage division gives  $3R_2 = R_1 + R_2 = 2000$  and  $2(R_2 + 2000) = R_1 + R_2 + 2000$ . Solving these equations gives  $R_1 = 6000 \Omega$  and  $R_2 = 2000 \Omega$ .

With these resistance values, the voltage source supplies 48 mW while  $R_1$ ,  $R_2$  and  $R_p$  dissipate 12 mW, 4 mW and 8 mW respectively. Therefore the design is complete.

**DP 3-2**

Try  $R_2 = \infty$ . That is,  $R_2$  is an open circuit. From KVL, 8 V will appear across  $R_1$ . Using voltage

division,  $\frac{200}{R_1 + 200} 12 = 4 \Rightarrow R_1 = 400 \Omega$ . The power required to be dissipated by  $R_1$

is  $\frac{8^2}{400} = 0.16 \text{ W} < \frac{1}{8} \text{ W}$ . To reduce the voltage across any one resistor, let's implement  $R_1$  as the series

combination of two  $200 \Omega$  resistors. The power required to be dissipated by each of these resistors is

$$\frac{4^2}{200} = 0.08 \text{ W} < \frac{1}{8} \text{ W}.$$

Now let's check the voltage:

$$11.88 \frac{190}{190 + 420} < v_0 < 12.12 \frac{210}{210 + 380}$$

$$3.700 < v_0 < 4.314$$

$$4 - 7.5\% < v_0 < 4 + 7.85\%$$

Hence,  $v_o = 4 \text{ V} \pm 8\%$  and the design is complete.


**DP 3-3**

$$v_{ab} \cong 200\text{mV}$$

$$v = \frac{10}{10 + R} 120V_{ab} = \frac{10}{10 + R} (120) \quad (.2)$$

$$\text{let } v = 16 = \frac{240}{10 + R} \Rightarrow \underline{R = 5\Omega}$$

$$\therefore P = \frac{16^2}{10} = \underline{25.6\text{W}}$$

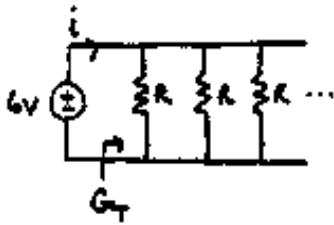**DP 3-4**

$$i = G_T v = \frac{N}{R} v$$

$$\text{where } G_T = \sum_{n=1}^N \frac{1}{R_n} = N \left( \frac{1}{R} \right)$$

$$\therefore N = \frac{iR}{v} = \frac{(9)(12)}{6} = \underline{18 \text{ bulbs}}$$