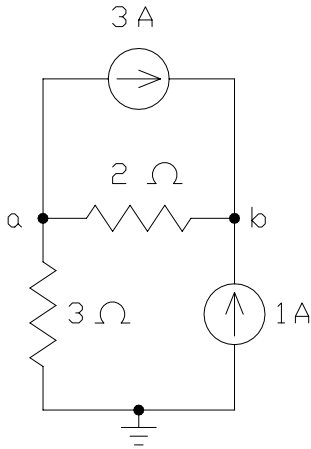


## Chapter 4 – Methods of Analysis of Resistive Circuits

### Exercises

#### Ex 4.3-1




$$\text{KCL at a: } \frac{v_a}{3} + \frac{v_a - v_b}{2} + 3 = 0 \Rightarrow 5v_a - 3v_b = -18$$

$$\text{KCL at b: } \frac{v_b - v_a}{2} - 3 - 1 = 0 \Rightarrow v_b - v_a = 8$$

Solving these equations gives:

$$v_a = 3 \text{ V and } v_b = 11 \text{ V}$$

#### Ex 4.3-2

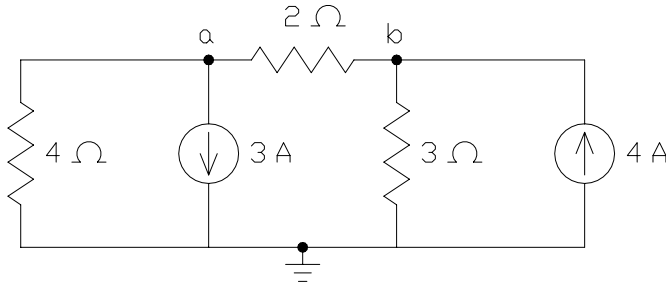

KCL at a:

$$\frac{v_a}{4} + \frac{v_a - v_b}{2} + 3 = 0 \Rightarrow 3v_a - 2v_b = -12$$

KCL at b:

$$\frac{v_b}{3} - \frac{v_a - v_b}{2} - 4 = 0 \Rightarrow -3v_a + 5v_b = 24$$

Solving:

$$v_a = -4/3 \text{ V and } v_b = 4 \text{ V}$$

$$\text{Ex. 4.4-1 } 2 + \frac{v_b + 10}{20} + \frac{v_b}{30} = 5 \Rightarrow v_b = 30 \text{ V and } v_a = 40 \text{ V}$$

$$\text{Ex. 4.4-2 } \frac{(v_b + 8) - (-12)}{10} + \frac{v_b}{40} = 3 \Rightarrow v_b = 8 \text{ V and } v_a = 16 \text{ V}$$

**Ex 4.5-1** Apply KCL at node a to express  $i_a$  as a function of the node voltages. Substitute the result into


$v_b = 4 i_a$  and solve for  $v_b$ .

$$v_b = 4 \left( \frac{9 + v_b}{12} \right) \Rightarrow v_b = 4.5 \text{ V}$$

**Ex. 4.5-2** : The controlling voltage of the dependent source is a node voltage so it is already expressed as a function of the node voltages. Apply KCL at node a.

$$\frac{v_a - 6}{20} + \frac{v_a - 4v_a}{15} = 0 \Rightarrow v_a = -2 \text{ V}$$

**Ex. 4.6-1**

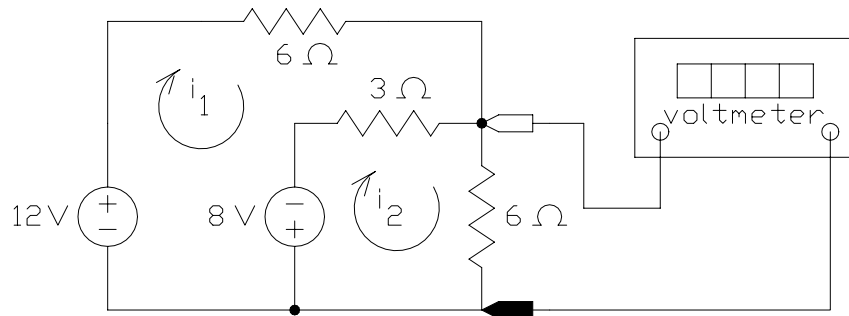

Mesh equations:

$$-12 + 6i_1 + 3(i_1 - i_2) - 8 = 0 \Rightarrow 9i_1 - 3i_2 = 20$$


$$8 - 3(i_1 - i_2) + 6i_2 = 0 \Rightarrow -3i_1 + 9i_2 = -8$$

Solving these equations gives:

$$i_1 = \frac{13}{6} \text{ A and } i_2 = -\frac{1}{6} \text{ A}$$

The voltage measured by the meter is  $6i_2 = -1 \text{ V}$ .


**Ex 4.7-1**

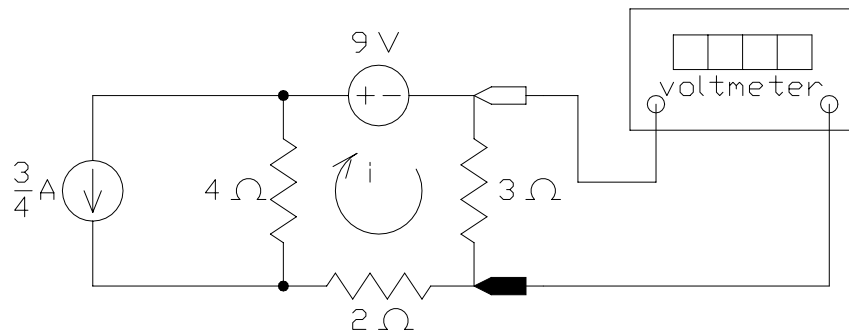

$$\text{Mesh equation: } 9 + 3i + 2i + 4\left(i + \frac{3}{4}\right) = 0 \Rightarrow (3 + 2 + 4)i = -9 - 3 \Rightarrow i = \frac{-12}{9} \text{ A}$$


The voltmeter measures  $3i = -4 \text{ V}$

**Ex 4.7-2**

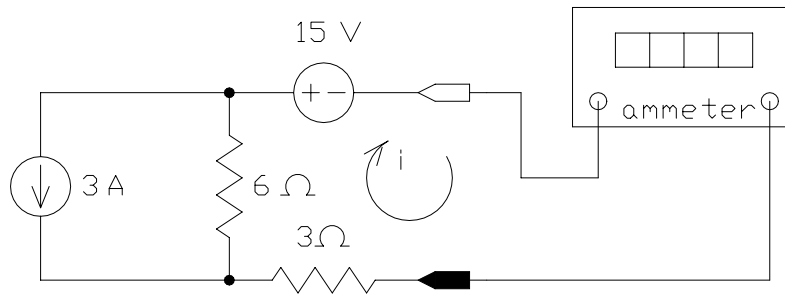

Mesh equation:  $15 + 3i + 6(i + 3) = 0 \Rightarrow (3 + 6)i = -15 - 6(3) \Rightarrow i = \frac{-33}{9} = -6\frac{2}{3} \text{ A}$

**Ex 4.7-3**

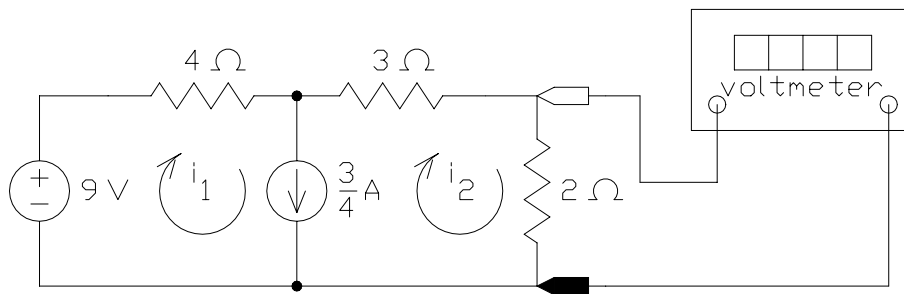


Express the current source current in terms of the mesh currents:  $\frac{3}{4} = i_1 - i_2 \Rightarrow i_1 = \frac{3}{4} + i_2$ .

Apply KVL to the supermesh:  $-9 + 4i_1 + 3i_2 + 2i_2 = 0 \Rightarrow 4\left(\frac{3}{4} + i_2\right) + 5i_2 = 9 \Rightarrow 9i_2 = 6$

so  $i_2 = \frac{2}{3} \text{ A}$  and the voltmeter reading is  $2i_2 = \frac{4}{3} \text{ V}$

**Ex 4.7-4**

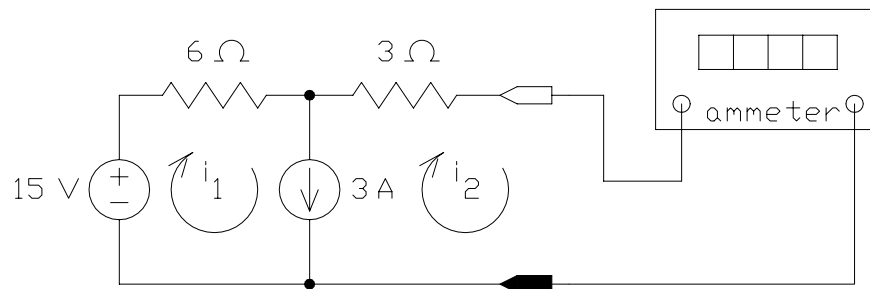


Express the current source current in terms of the mesh currents:  $3 = i_1 - i_2 \Rightarrow i_1 = 3 + i_2$ .

Apply KVL to the supermesh:  $-15 + 6i_1 + 3i_2 = 0 \Rightarrow 6(3 + i_2) + 3i_2 = 15 \Rightarrow 9i_2 = -3$

Finally,  $i_2 = -\frac{1}{3} \text{ A}$  is the current measured by the ammeter.

Ex. 4.7-5

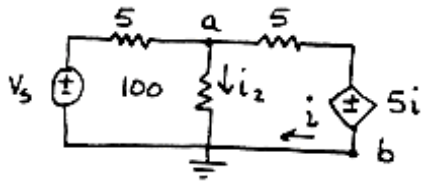

$$v_{ab} = 5i + 5i = 10i$$

$$\therefore P_{\text{motor}} = (v_{ab})i = 10i^2 = 150$$


$$\Rightarrow i = \sqrt{15} \text{ A}$$

$$\therefore v_{ab} = (10)(\sqrt{15}) \text{ V}$$

$$\Rightarrow i_2 = \frac{v_{ab}}{100} = \frac{\sqrt{15}}{10} \text{ A}$$

KCL at a:  $\frac{(v_{ab} - v_s)}{5} + i_2 + i = 0 \Rightarrow v_s = \frac{31\sqrt{15}}{2} = 60.03 \text{ V}$

Ex. 4.7-6

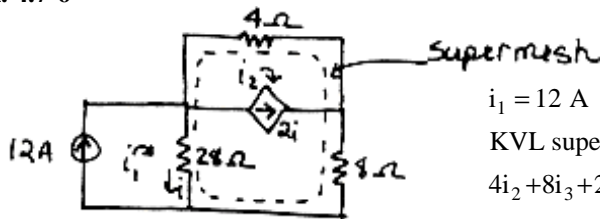

$$i_1 = 12 \text{ A} \quad (1)$$

KVL supermesh:

$$4i_2 + 8i_3 + 28(i_3 - 12) = 0 \quad (2)$$


$$\text{also: } 2i = i_3 - i_2 \quad (3)$$

Solving (1)  $\rightarrow$  (3) yields  $i_3 = 9 \text{ A}$   
 $\therefore i = 12 - 9 = 3 \text{ A}$

Ex. 4.8-1

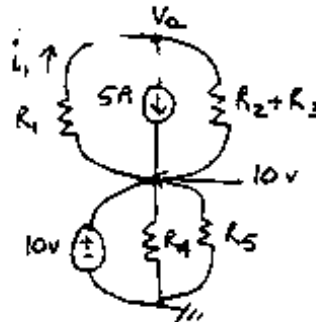- (a) Nodal analysis since the other node is known ( $= v_s$ ); thus only need one node equation at a.
- (b) Nodal analysis since when the circuit is redrawn (shown below), only one node equation at  $v_a$  is required


Mesh analysis would require 4 mesh currents  $\Rightarrow$  4 unknowns.



## Problems

### Section 4-3 Node Voltage Analysis of Circuits with Current Sources


#### P4.3-1

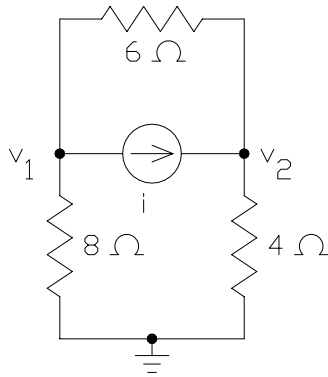

KCL at node 1:

$$0 = \frac{v_1}{8} + \frac{v_1 - v_2}{6} + i = \frac{-4}{8} + \frac{-4 - 2}{6} + i = -1.5 + i \Rightarrow i = 1.5 \text{ A}$$

#### P 4.3-2

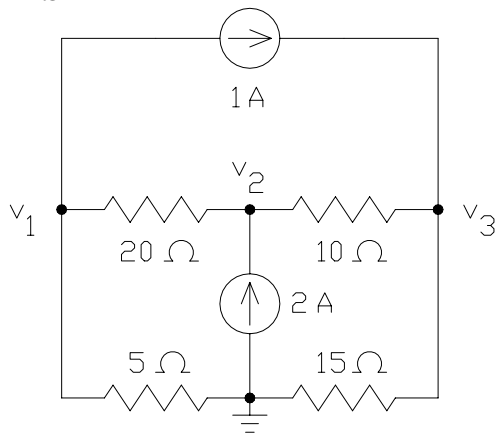

KCL at node 1:

$$\frac{v_1 - v_2}{20} + \frac{v_1}{5} + 1 = 0 \Rightarrow 5v_1 - v_2 = -20$$

KCL at node 2:


$$\frac{v_1 - v_2}{20} + 2 = \frac{v_2 - v_3}{10} \Rightarrow -v_1 + 3v_2 - 2v_3 = 40$$

KCL at node 3:

$$\frac{v_2 - v_3}{10} + 1 = \frac{v_3}{15} \Rightarrow -3v_2 + 5v_3 = 30$$

Solving gives  $v_1 = 2 \text{ V}$ ,  $v_2 = 30 \text{ V}$  and  $v_3 = 24 \text{ V}$ .

#### P 4.3-3

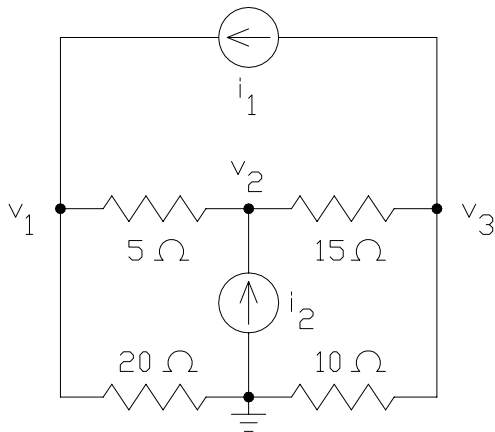

KCL at node 1:

$$\frac{v_1 - v_2}{5} + \frac{v_1}{20} = i_1 \Rightarrow i_1 = \frac{4 - 15}{5} + \frac{4}{20} = -2 \text{ A}$$

KCL at node 2:

$$\frac{v_1 - v_2}{5} + i_2 = \frac{v_2 - v_3}{15} \Rightarrow i_2 = -\left(\frac{4 - 15}{5}\right) + \frac{15 - 18}{15} = 2 \text{ A}$$

**P4.3-4**

$$-.003 + \frac{v_1}{R_1} + \frac{v_1 - v_2}{500} = 0$$

$$-\frac{v_1 - v_2}{500} + \frac{v_2}{R_2} - .005 = 0$$


When

$$v_1 = 1 \text{ and } v_2 = 2$$

$$-.003 + \frac{1}{R_1} + \frac{-1}{500} = 0 \Rightarrow R_1 = \frac{1}{.003 + \frac{1}{500}} = \underline{200\Omega}$$

$$-\frac{-1}{500} + \frac{2}{R_2} - .005 = 0 \Rightarrow R_2 = \frac{2}{.005 - \frac{1}{500}} = \underline{667\Omega}$$

**P 4.3-5**

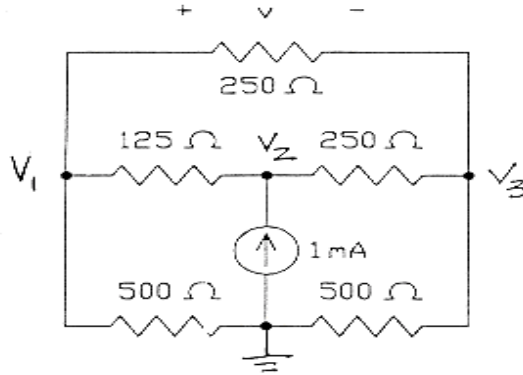

$$\frac{v_1}{500} + \frac{v_1 - v_2}{125} + \frac{v_1 - v_3}{250} = 0$$

$$-\frac{v_1 - v_2}{125} - .001 + \frac{v_2 - v_3}{250} = 0$$

$$-\frac{v_2 - v_3}{250} - \frac{v_1 - v_3}{250} + \frac{v_3}{500} = 0$$

$$\Rightarrow v_1 = 0.261 \text{ V}$$

$$v_2 = 0.337 \text{ V}$$

$$v_3 = 0.239 \text{ V}$$

$$\text{Finally, } v = v_1 - v_3 = \underline{0.022 \text{ V}}$$

**Section 4-4 Node Voltage Analysis of Circuits with Current and Voltage Sources**

**P4.4-1**

$$\frac{v_a - 10}{100} + \frac{v_a}{100} + \frac{v_a - 2}{100} = 0 \Rightarrow 3v_a = 12$$

$$\Rightarrow \underline{v_a = 4 \text{ V}}$$

**P4.4-2**

$$-.003 + \frac{v_a + 8}{500} + \frac{v_a}{500} - .005 = 0$$


$$\therefore \underline{v_a = -2 \text{ V}}$$

**P4.4-3**

$$\frac{v_a - 10}{100} + \frac{v_a}{100} + \frac{v_a - 8}{100} - .03 = 0$$

$$\therefore \underline{v_a = 7 \text{ V}}$$

**P4.4-4**

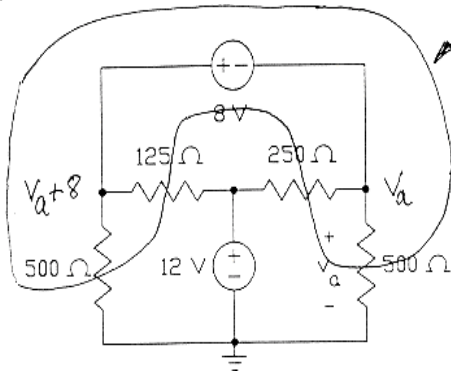

$$\frac{v_a+8}{500} + \frac{(v_a+8)-12}{125} + \frac{v_a-12}{250} + \frac{v_a}{500} = 0$$


$$\therefore v_a = 4 \text{ V}$$

**P4.4-5**

$$-\frac{10-6}{100} + \frac{6}{R_3} + \frac{6-4}{100} = 0 \Rightarrow R_3 = 300 \Omega$$

**P4.4-6**

a)

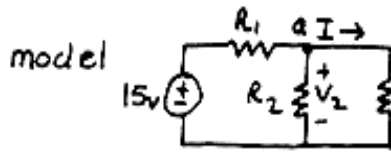

need to keep  $v_2$  across  $R_2$  as  $4.8 \leq v_2 \leq 5.4$

$I = .3$  or  $.1 \text{ A}$  depending on whether activated or not

↑	↑
display is active	not active

$$\text{KCL at a: } \frac{v_2-15}{R_1} + \frac{v_2}{R_2} + I = 0$$

$$\Rightarrow v_2' = 4.8 \text{ V } (I' = .3 \text{ A}) \quad \& \quad v_2'' = 5.4 \text{ V } (I'' = .1 \text{ A})$$

assumed that maximum  $I$  results in minimum  $v_2$  and Visa-Versa

Now plug in  $v_2'$  &  $v_2''$  into KCL eqn. to generate 2 eqns and then solve for

$$R_1 \ \& \ R_2 \Rightarrow R_1 = 7.89 \ \Omega, \ R_2 = 4.83 \ \Omega$$


b)  $I_{R_{1\max}} = \frac{15-4.8}{7.89} = 1.292 \text{ A} \Rightarrow P_{R_{1\max}} = (1.292)^2(7.89) = 13.17 \text{ W}$

$$I_{R_{2\max}} = \frac{5.4}{4.83} = 1.118 \text{ A} \Rightarrow P_{R_{2\max}} = \frac{(5.4)^2}{4.83} = 6.03 \text{ W}$$

$$I_{15\text{V}\max} = 1.292 \text{ A}$$

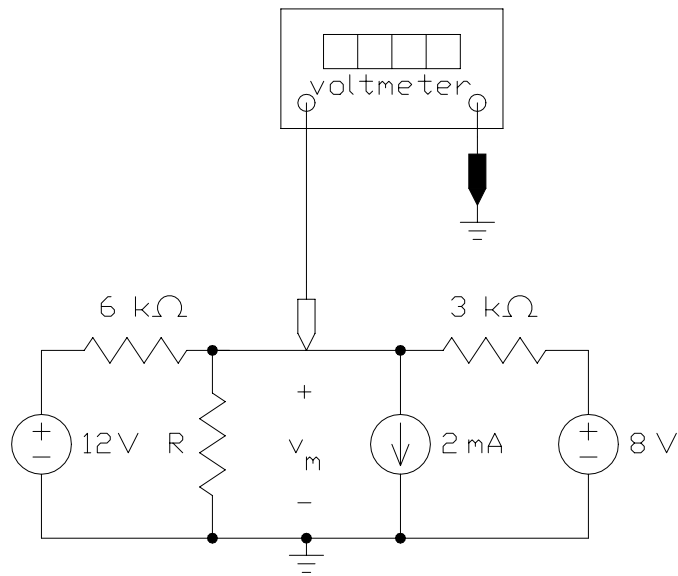c) No; if the supply voltage (15V) were to rise or drop, the voltage at the display would drop below 4.8V or rise above 5.4V. The power dissipated in the resistors is excessive. Most of the power from the supply is dissipated in the resistors, not the display.

**P4.4-7** Label the voltage measured by the meter. Notice that this is a node voltage.



Write a node equation at the node at which the node voltage is measured.


$$-\left(\frac{12 - v_m}{6\text{k}\Omega}\right) + \frac{v_m}{R} + 2\text{mA} + \frac{v_m - 8}{3\text{k}\Omega} = 0$$

That is

$$\left(3 + \frac{6\text{k}\Omega}{R}\right)v_m = 16 \Rightarrow R = \frac{6\text{k}\Omega}{\frac{16}{v_m} - 3}$$

- (a) The voltage measured by the meter will be 4 volts when  $R = 6\text{k}\Omega$ .  
 (b) The voltage measured by the meter will be 2 volts when  $R = 1.2\text{k}\Omega$ .

**P4.4-8**

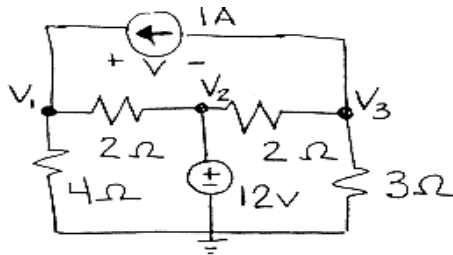

$$v = v_1 - v_3$$

$$v_2 = 12\text{V}$$

$$\text{KCL at } v_1: \frac{v_1}{4} + \frac{v_1 - v_2}{2} - 1 = 0$$

$$\text{KCL at } v_3: \frac{v_3}{3} + \frac{v_3 - v_2}{2} + 1 = 0$$

$$\text{Solving for } v_1 \text{ \& } v_3: v_1 = 9.33\text{V}$$

$$v_3 = 6\text{V}$$

$$v = 9.33 - 6 = \underline{3.33\text{V}}$$



## Section 4-5 Node Voltage Analysis with Dependent Sources

**P4.5-1**

$$v_a = 9 - v_b - \frac{9 - v_b}{100} + (.02)(9 - v_b) + \frac{v_b}{200} = 0$$

$$\therefore \underline{v_b = +18 \text{ V}; v_a = -9 \text{ V}}$$

**P4.5-2**

$$-.002 + \frac{v_a}{10,000} + \frac{v_a - 4000 \left( \frac{v_a}{10,000} \right)}{6000} = 0$$

$$-.002 + \frac{v_a}{10,000} + \frac{.6v_a}{6000} = 0 \Rightarrow \underline{v_a = 10 \text{ V}}$$

**P4.5-3**

$$\frac{v_a - 6}{1000} + \frac{v_a}{2000} + \frac{v_a - 4v_a}{3000} = 0 \Rightarrow v_a = 12 \text{ V}$$


$$i_b = \frac{v_a - 4v_a}{3000} = \underline{-12 \text{ mA}}$$

**P4.5-4**

$$i_a = \frac{2 - v_b}{4000}$$

$$-\frac{2 - v_b}{4000} + \frac{v_b}{2000} - 5 \left( \frac{2 - v_b}{4000} \right) = 0 \Rightarrow \underline{v_b = 1.5 \text{ V}}$$

**P 4.5-5**

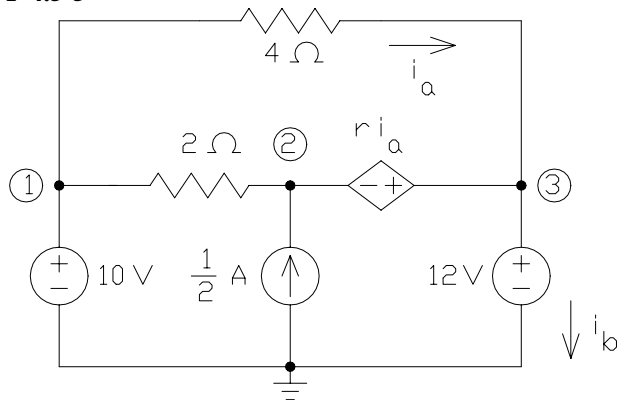


Apply KCL to the supernode of the CCVS to get

$$\frac{12 - 10}{4} + \frac{14 - 10}{2} - \frac{1}{2} + i_b = 0 \Rightarrow i_b = -2 \text{ A}$$

Next

$$\left. \begin{aligned} i_a &= \frac{10 - 12}{4} = -\frac{1}{2} \\ r i_a &= 12 - 14 \end{aligned} \right\} \Rightarrow r = \frac{-2}{-\frac{1}{2}} = 4 \frac{\text{V}}{\text{A}}$$

**P4.5-6**

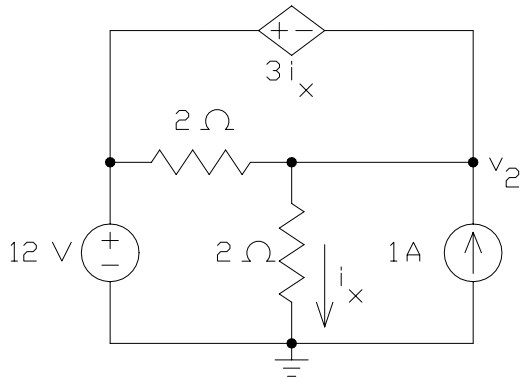

First, express the controlling current of the CCVS in


terms of the node voltages:  $i_x = \frac{v_2}{2}$

Next, express the controlled voltage in terms of the node voltages:

$$12 - v_2 = 3i_x = 3 \frac{v_2}{2} \Rightarrow v_2 = \frac{24}{5} \text{ V}$$

so  $i_x = 12/5 \text{ A} = 2.4 \text{ A}$ .

**P4.5-7**

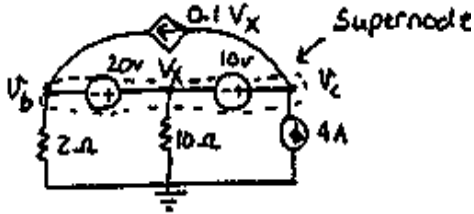


KCL:  $\frac{v_b}{2} + \frac{v_x}{10} + 4 = 0$  (1)

also  $v_b = v_x - 20$  (2)

(1) & (2) yields  $v_x = 10 \text{ V}$

**Section 4-6 Mesh Current Analysis with Independent Voltage Sources**

**P 4.6-1**

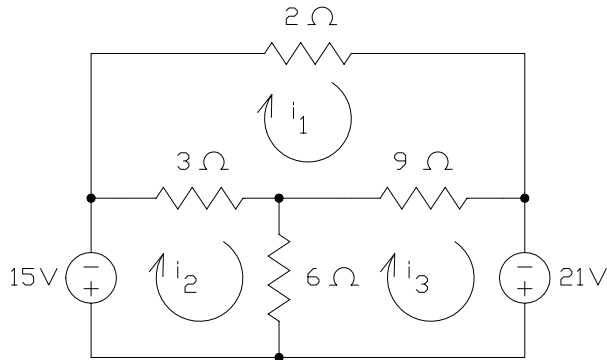

$$2i_1 + 9(i_1 - i_3) + 3(i_1 - i_2) = 0$$

$$15 - 3(i_1 - i_2) + 6(i_2 - i_3) = 0$$

$$-6(i_2 - i_3) - 9(i_1 - i_3) - 21 = 0$$

or

$$14i_1 - 3i_2 - 9i_3 = 0$$


$$-3i_1 + 9i_2 - 6i_3 = -15$$

$$-9i_1 - 6i_2 + 15i_3 = 21$$

so

$$i_1 = 3 \text{ A}, i_2 = 2 \text{ A} \text{ and } i_3 = 4 \text{ A}.$$

**P 4.6-2**

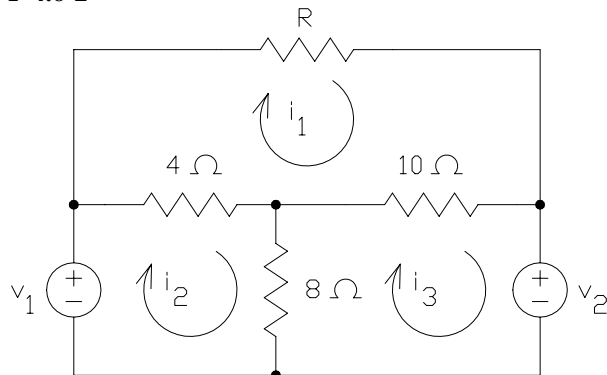

Top mesh:

$$4(2 - 4) + R(2) + 10(2 - 4) = 0$$

so  $R = 12 \Omega$ .

Bottom, left mesh:

$$8(4 - 3) + 10(4 - 2) + v_2 = 0$$


so  $v_2 = -28 \text{ V}$ .

Bottom right mesh

$$-v_1 + 4(3 - 2) + 8(3 - 4) = 0$$


so  $v_1 = -4 \text{ V}$ .

P4.6-3

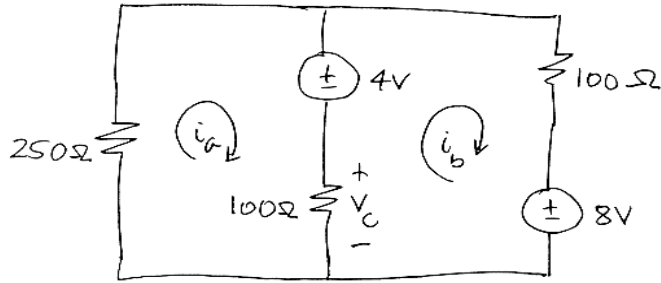


$$\begin{aligned} \text{loop a} \quad & 250 i_a + 4 + 100 (i_a - i_b) = 0 \\ & 350 i_a - 100 i_b = -4 \\ \text{loop b} \quad & -100(i_a - i_b) - 4 + 100 i_b + 8 = 0 \\ & -100 i_a + 200 i_b = -4 \\ & \underline{i_a = -20 \text{ mA} , i_b = -30 \text{ mA}} \end{aligned}$$

P4.6-4

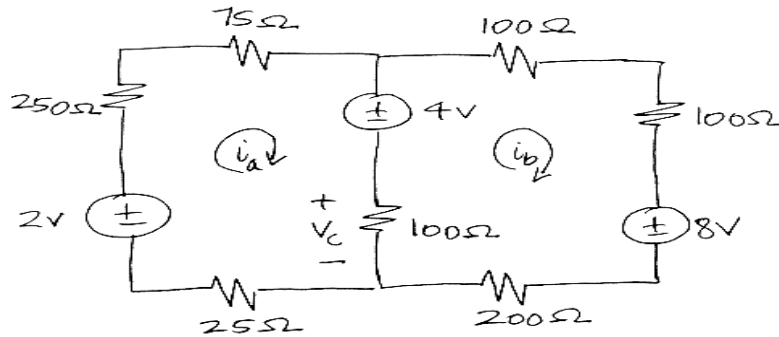

$$\begin{aligned} \text{loop 1} \quad & 25 i_a - 2 + 250 i_a + 75 i_a + 4 + 100 (i_a - i_b) = 0 \\ & 450 i_a - 100 i_b = -2 \\ \text{loop 2} \quad & -100(i_a - i_b) - 4 + 100 i_b + 100 i_b + 8 + 200 i_b = 0 \\ & -100 i_a + 500 i_b = -4 \\ & \underline{i_a = -6.5 \text{ mA} , i_b = -9.3 \text{ mA}} \end{aligned}$$

P4.6-5

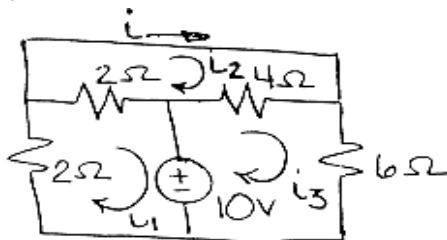


$$\begin{aligned} \text{KVL1:} \quad & 2i_1 + 2(i_1 - i_2) + 10 = 0 \\ \text{KVL2:} \quad & 2(i_2 - i_1) + 4(i_2 - i_3) = 0 \\ \text{KVL3:} \quad & -10 + 4(i_3 - i_2) + 6i_3 = 0 \\ & i = i_2 \Rightarrow \underline{i = -0.294 \text{ A}} \end{aligned}$$

Section 4-7 Mesh Current Analysis with Voltage and Current Sources


(a) Independent Sources

P4.7-1

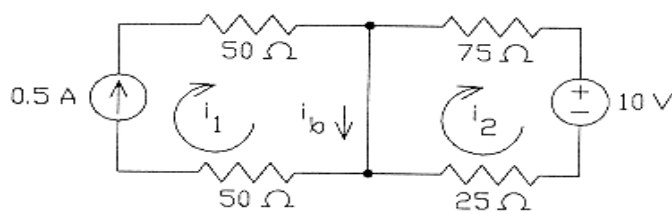


$$\begin{aligned} \text{loop 1 } i_1 &= \frac{1}{2} \text{ A} \\ \text{loop 2 } 75 i_2 + 10 + 25 i_2 &= 0 \Rightarrow i_2 = -0.1 \text{ A} \\ i_b &= i_1 - i_2 = \underline{0.6 \text{ A}} \end{aligned}$$

P4.7-2

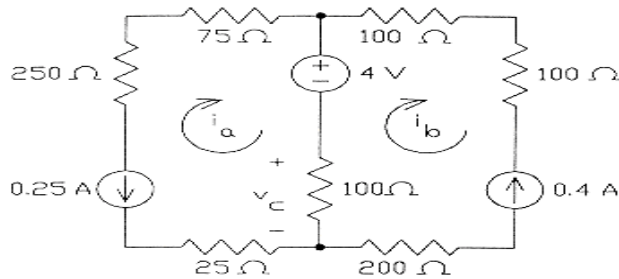

$$\begin{aligned} \text{loop a } i_a &= -0.25 \text{ A} \\ \text{loop b } i_b &= -0.4 \text{ A} \\ v_c &= 100(i_a - i_b) = 100(0.15) = \underline{15 \text{ V}} \end{aligned}$$

P4.7-3

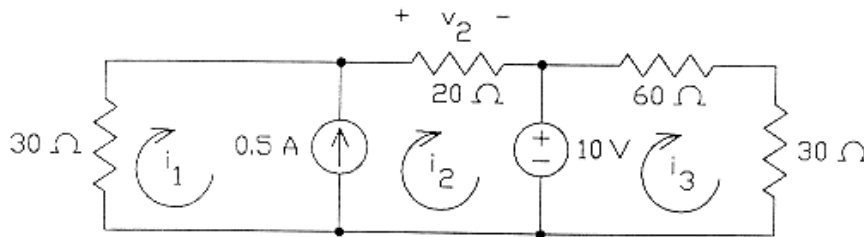


$$\text{loop 1 } i_1 - i_2 = -0.5 \Rightarrow i_1 = i_2 - 0.5$$

$$\begin{aligned} \text{loop 1,2 } 30 i_1 + 20 i_2 + 10 &= 0 \\ 30(i_2 - 0.5) + 20 i_2 &= -10 \\ 50 i_2 - 15 &= -10 \\ i_2 &= \frac{5}{50} = .1 \text{ A} \\ i_1 &= -0.4 \text{ A} \\ v_2 &= 20 i_2 = \underline{2 \text{ V}} \end{aligned}$$

P4.7-4

$$\begin{aligned} i_b &= i_a - 0.02 \\ 250 i_a + 100(i_a - 0.02) + 9 &= 0 \\ \therefore i_a &= -0.02 \text{ A} = -20 \text{ mA} \\ v_c &= 100(i_a - 0.02) = \underline{-4 \text{ V}} \end{aligned}$$

P4.7-5

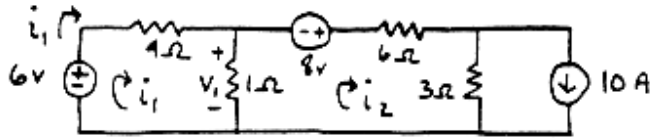


$$\text{KVL mesh } i_1 : -6 + 4i_1 + (i_1 - i_2) = 0 \Rightarrow -6 + 5i_1 - i_2 = 0 \quad (1)$$

$$\text{KVL mesh } i_2 : (i_2 - i_1) - 8 + 6i_2 + 3(i_2 - 10) = 0 \Rightarrow -38 - i_1 + 10i_2 = 0 \quad (2)$$

Solving (1) & (2) simultaneously yields  $i_1 = 2 \text{ A}$  and  $i_2 = 4 \text{ A}$ .  $\therefore v_1 = 1(i_1 - i_2) = -2 \text{ V}$

P4.7-6

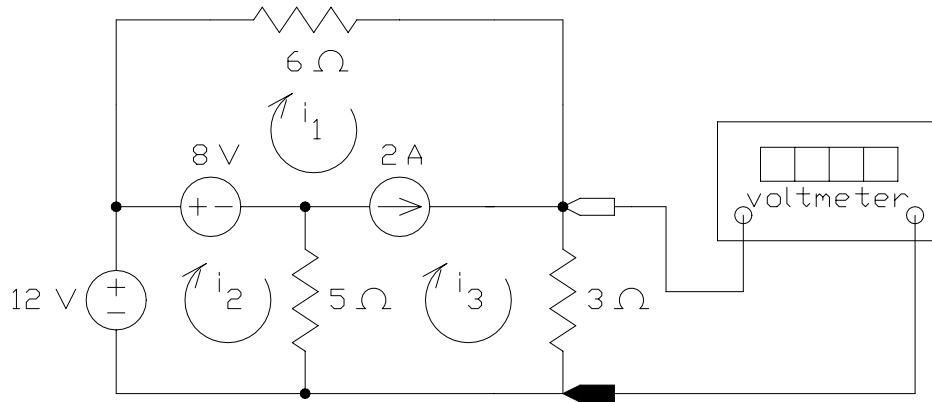

Express the current source current in terms of the mesh currents:

$$i_3 - i_1 = 2 \Rightarrow i_1 = i_3 - 2$$

$$\text{Supermesh: } 6i_1 + 3i_3 - 5(i_2 - i_3) - 8 = 0 \Rightarrow 6i_1 - 5i_2 + 8i_3 = 8$$


$$\text{Lower, left mesh: } -12 + 8 + 5(i_2 - i_3) = 0 \Rightarrow 5i_2 = 4 + 5i_3$$

Eliminating  $i_1$  and  $i_2$  from the supermesh equation:

$$6(i_3 - 2) - (4 + 5i_3) + 8i_3 = 8 \Rightarrow 9i_3 = 24$$

$$\text{The voltage measured by the meter is: } 3i_3 = 3 \frac{24}{9} = 8 \text{ V}$$


**P4.7-7**

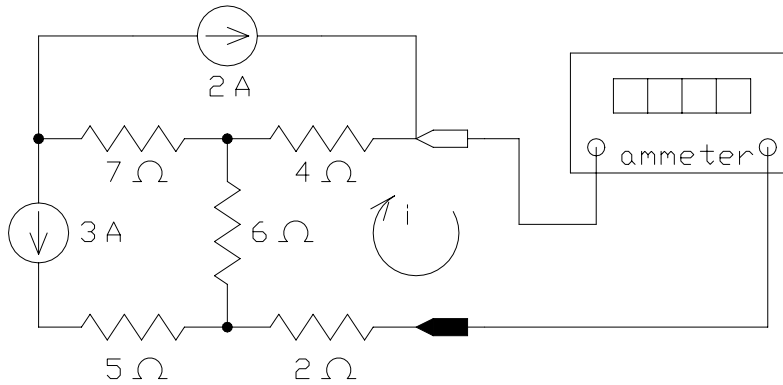

Mesh equation for right mesh:

$$4(i-2) + 2i + 6(i+3) = 0 \Rightarrow 12i - 8 + 18 = 0 \Rightarrow i = \frac{10}{12} \text{ A}$$

**P4.7-8**

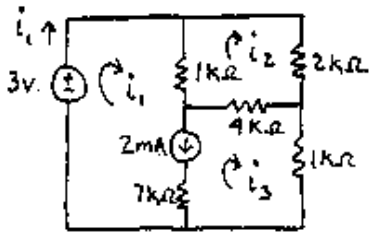

KVL around mesh  $i_1$  &  $i_3$  combined

$$-3 + (i_1 - i_2) + 4(i_3 - i_2) + i_3 = 0$$

yields  $3 - i_1 + 5i_2 - 5i_3 = 0$  (1)

KVL around mesh  $i_2$

$$i_2 - i_1 + 2i_2 + 4(i_2 - i_3) = 0$$

yields  $i_1 - 7i_2 + 4i_3 = 0$  (2)


also  $i_1 - i_3 = 2$  (3)

Solving (1), (2), & (3) simultaneously yields  $i_1 = 3 \text{ mA}$

**Section 4-7 Mesh Current Analysis with Voltage and Current Sources**

**b) Independent and Dependent Sources**

**P4.7-9**

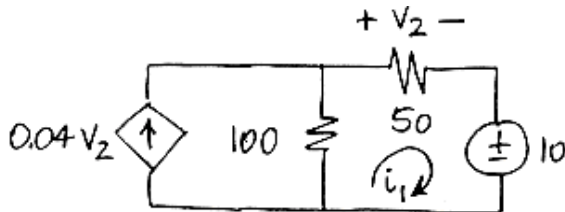

$$v_2 = 50i_1$$

$$-100(0.04(50i_1) - i_1) + 50i_1 + 10 = 0 \Rightarrow i_1 = 0.2 \text{ A}$$

$$v_2 = 50i_1 = 10 \text{ V}$$

**P4.7-10**

$$i_b = 4i_b - i_a \Rightarrow i_b = \frac{1}{3} i_a$$

$$-100\left(\frac{1}{3}i_a\right) + 200i_a + 8 = 0 \Rightarrow i_a = -0.048 \text{ A}$$

**P4.7-11**

$$i_b = .06 - i_a$$

$$-100(0.06 - i_a) + 50(0.06 - i_a) + 250i_a = 0$$

$$\therefore i_a = 10 \text{ mA}$$

$$v_o = 50i_b = 50(0.06 - 0.1) = \underline{2.5 \text{ V}}$$


**P4.7-12**

$$v_b = 100(.006 - i_a)$$

$$-100(.006 - i_a) + 3[100(.006 - i_a)] + 250i_a = 0$$

$$\therefore i_a = \underline{-24 \text{ mA}}$$

**P4.7-13**

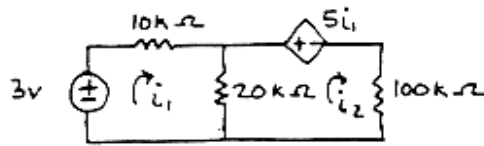

$$\text{KVLi}_1: -3 + 10i_1 + 20(i_1 - i_2) = 0 \Rightarrow \underline{30i_1 - 20i_2 = 3} \quad (1)$$

$$\text{KVLi}_2: 5i_1 + 100i_2 + 20(i_2 - i_1) = 0 \Rightarrow \underline{i_1 = 8i_2} \quad (2)$$

$$\text{Solving (1) \& (2) simultaneously} \Rightarrow i_1 = \frac{6}{55} \text{ mA}, i_2 = \frac{3}{220} \text{ mA}$$

$$\therefore P_{\text{deliv. to } 5i_1 \text{ and } 100k\Omega} = (5i_1)(i_2) + 100(i_2)^2$$

$$= 5\left(\frac{6}{55}\right)\left(\frac{3}{220}\right) + 100\left(\frac{3}{220}\right)^2 = 0.026 \text{ mA}$$

$$= 2.6 \times 10^{-5} \text{ W}$$

$$\therefore \text{Energy in 24 hr.} = Pt = (2.6 \times 10^{-5})(24 \text{ hr})\left(\frac{3600 \text{ s}}{\text{hr}}\right)$$

$$= \underline{2.25 \text{ J}}$$


**P4.7-14 (a)**

$$v_o = -gR_L v \text{ and } v = \frac{R_2}{R_1 + R_2} v_i \Rightarrow \frac{v_o}{v_i} = -g \frac{R_L R_2}{R_1 + R_2}$$

**(b)**

$$\text{So have } \frac{v_o}{v_i} = -g \frac{(5 \times 10^3)(10^3)}{1.1 \times 10^3} = -170 \Rightarrow \underline{g = 0.0374 \text{ S}}$$

**P4.7-15**

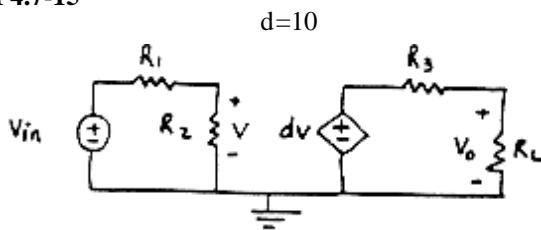

$$\text{from voltage divider } v = v_{in} \frac{R_2}{R_1 + R_2}$$


$$\text{from voltage divider } v_o = dv \frac{R_L}{R_L + R_3}$$

$$= (10)v_{in} \frac{R_2}{R_1 + R_2} \cdot \frac{R_L}{R_L + R_3}$$

$$\therefore \frac{v_o}{v_{in}} = \frac{10R_L R_2}{(R_L + R_3)(R_1 + R_2)}$$

## Section 4-8 Node Voltage Method and Mesh Current Method Compared

### P4.8.1

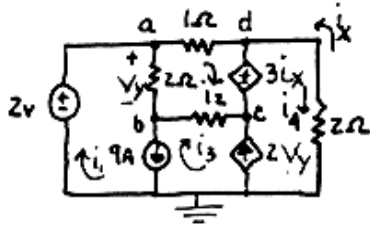

a) Mesh Analysis

Combine loop 1, 3, & 4 into supermesh

$$\Rightarrow -2 + (i_1 - i_2)2 + (i_3 - i_2) - 3i_x + 2i_4 = 0 \quad (1)$$

$$\text{loop } i_2: -2i_1 + 4i_2 - i_3 + 3i_x = 0 \quad (2)$$

$$\text{also: } i_1 - i_3 = 9 \quad (3)$$

$$i_4 - i_3 = 2v_y \quad (4)$$

$$2(i_1 - i_2) = v_y \quad (5)$$

and  $v_c = -2i_x - 3i_x$  (6) Solving (1)–(7) simultaneously yields

$$i_4 = -i_x \quad (7) \quad i_x = -1 \text{ A}, \underline{v_c = 5 \text{ V}}$$

b) Nodal Analysis

$$v_a = 2 \text{ V}$$

$$\text{KCL at b: } 9 + \frac{v_b - v_c}{1} + \frac{v_b - 2}{2} = 0 \Rightarrow 3v_b - 2v_c = -16 \quad (1)$$

form super node around nodes c & d, then KCL yields

$$\frac{v_d - 2}{1} + \frac{v_d}{2} - 2v_y + \frac{v_c - v_b}{1} = 0$$

with  $v_y = 2 - v_b$  and multiplying above through by 2 yields

$$2v_b + 2v_c + 3v_d = 12 \quad (2)$$

$$\text{also: } v_d - v_c = 3i_x = 3\left(-\frac{v_d}{2}\right) \Rightarrow v_c + 2.5v_d = 0 \quad (3)$$

Solving (1)–(3) yields

$$\underline{v_c = 5 \text{ V}} \text{ and } v_d = 2 \text{ V} \Rightarrow \underline{i_x = -\frac{v_d}{2} = -1 \text{ A}}$$




PSpice Problems

SP 4-1 Spice deck corresponding to Problem SP 4-1

```
V1 1 0 dc 6
R2 1 2 3
I3 0 2 dc 1
V4 3 2 dc 3
R5 3 0 6
R6 3 1
.END
```

NODE	VOLTAGE	NODE	VOLTAGE
( 1 )	6.0000	( 2 )	4.0000
( 3 )	7.0000		

VOLTAGE SOURCE	CURRENTS
NAME	CURRENT
V1	-1.667E-01
V4	-1.667E+00

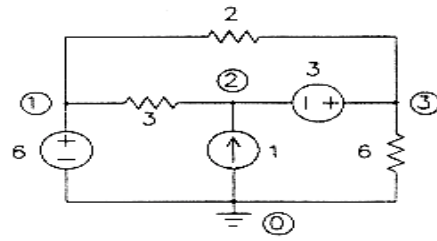


SP 4-2 Spice Deck Corresponding to Problem SP 4-2

```
VI 1 0 dc 40
R2 1 2 220
R3 2 0 150
R4 2 3 330
R5 3 0 75
R6 1 3 100
.END
```

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
( 1 )	40.0000	( 2 )	16.3950	( 3 )	17.0570


VOLTAGE SOURCE	CURRENTS
NAME	CURRENT
V1	-3.367E-01

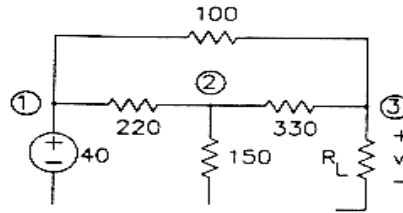

SP 4-3 Spice Deck corresponding to Problem SP 4-3


```
V1 1 0 dc 5
R3 2 0 2K
R4 2 3 6K
R5 3 0 3K
.END
```

V=0.588V

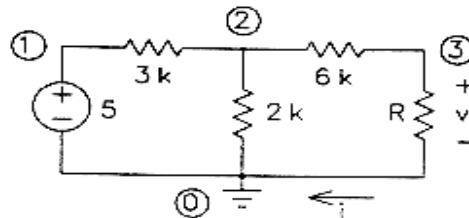

SP 4-4 Spice deck corresponding to Problem SP 4-4
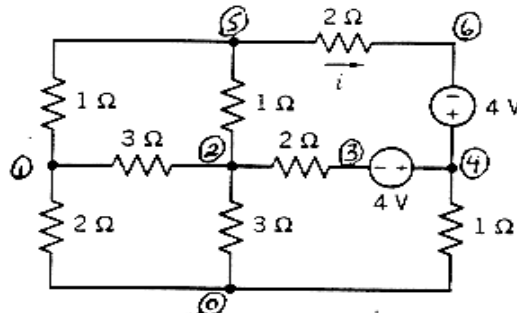
```
R1 1 0 2
R2 1 2 3
R3 1 5 1
R4 2 0 3
R5 2 3 2
R6 2 5 1
V7 4 3 4
R8 4 0 1
V9 4 6 4
R10 5 6 2
.END
```



NODE	VOLTAGE	NODE	VOLATAGE	NODE	VOLTAGE
( 1 )	-1.2332	( 2 )	-1.6364	( 3 )	-2.8379
( 4 )	1.1621	( 5 )	-1.7154	( 6 )	-2.8379

VOLTAGE SOURCE	CURRENTS
NAME	CURRENT
V7	-6.008E-0.1
V9	-5.613E-0.1


SP 4-5

Input File:

```

R1      0      5      6000
R2      1      6      3000
R3      1      2      2000
R4      3      4      2000
R5      4      5      8000
V1      2      3      dc 16
V2      6      4      dc 8
I1      5      4      dc 1m
Vsc1    1      0      0
H1      3      6      Vsc1 4

```

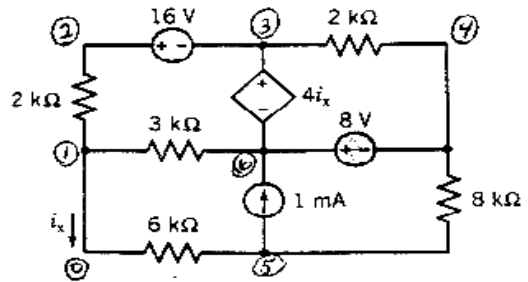

```

.dc V1 16 16 1
.print dc I(Vsc1)
.end

```

Output:

```

V1      I(Vsc1)
1.600E+1 1.684E-03

```


SP 4-6

Input File:

```

R1      0      1      1
R2      3      4      7
R3      4      10     5
R4      10     7      3
R5      6      7      4
R6      10     9      2
R7      7      8      6
V1      9      11     dc 6
V2      2      1      dc 10
Vsc1    2      3      0
Vsc2    11     0      0
Vsc3    5      6      0
H1      1      10     Vsc2 4
F1      8      9      Vsc1 2
E1      4      5      7 8 3

```

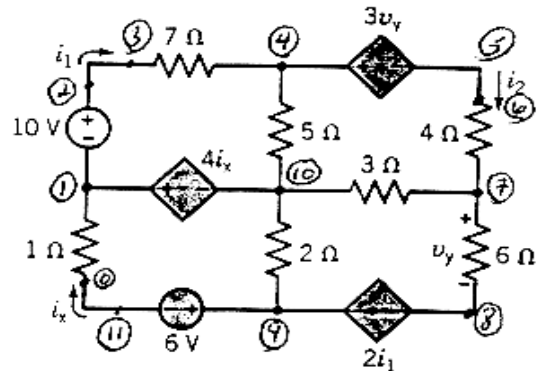

```

.dc V1 6 6 1
.print dc I Vsc2
.end


```

Output:

```
V1          I(Vsc2)
6.000+E00 -6.706E-01
```

SP 4-7 Spice deck corresponding to Problem SP 4-7
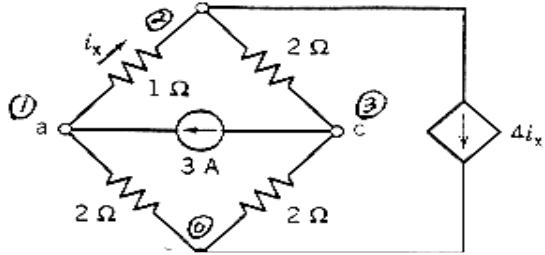
```
R1      1 0 2
R2      4 2 1
VSC3    1 4 0
F3      2 0 VSC3  4
R4      2 3 2
R5      3 0 2
I6      3 1 DC    3
.END
```




NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
( 1 )	8.6667	( 2 )	10.0000	( 3 )	2.0000
( 4 )	8.6667				

VOLTAGE SOURCE NAME	CURRENTS CURRENT
VSC3	-1.333E+00

## Verification Problems

### VP 4-1

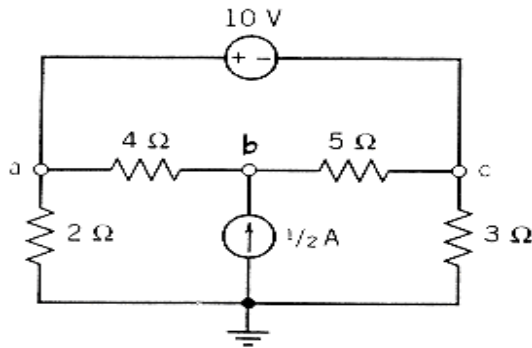


Apply KCL at node b

$$\frac{v_b - v_a}{4} - \frac{1}{2} + \frac{v_b - v_c}{5} = 0$$

$$-\frac{4.8 - 5.2}{4} - \frac{1}{2} + \frac{-4.8 - 3.0}{5} \neq 0$$

The given voltages do not satisfy the KCL equation at node b. They are not correct.

### VP 4-2

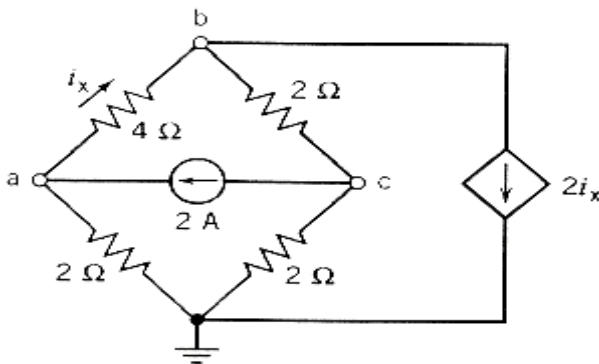

Apply KCL at node a:

$$-\left(\frac{v_b + v_a}{4}\right) - 2 + \frac{v_a}{2} = 0$$

$$-\left(\frac{20 - 4}{4}\right) - 2 + \frac{4}{2} = -4 \neq 0$$

The given voltages do not satisfy the KCL equation at node a. They are not correct.


### VP 4-3

Writing a node equation:

$$-\left(\frac{12 - 7.5}{R_1}\right) + \frac{7.5}{R_3} + \frac{7.5 - 6}{R_2} = 0$$

so
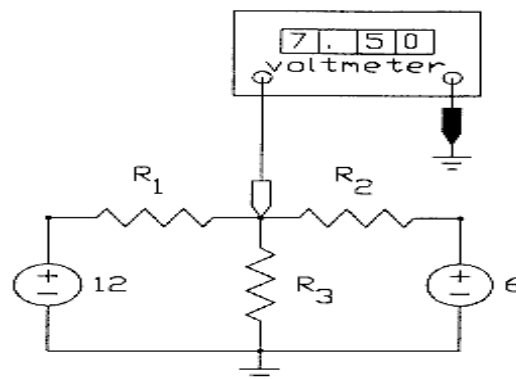
$$-\frac{4.5}{R_1} + \frac{7.5}{R_3} + \frac{1.5}{R_2} = 0$$




There are only three cases to consider. Suppose  $R_1 = 5\text{k}\Omega$  and  $R_2 = 10\text{k}\Omega$ . Then

$$-\frac{4.5}{R_1} + \frac{7.5}{R_3} + \frac{1.5}{R_2} = -0.9 + 0.75 + 0.15 = 0$$

This choice of resistance values corresponds to branch currents that satisfy KCL. Therefore, it is indeed possible that two of the resistance are  $10\text{k}\Omega$  and the other resistance is  $5\text{k}\Omega$ . The  $5\text{k}\Omega$  is  $R_3$ .

**VP 4-4**

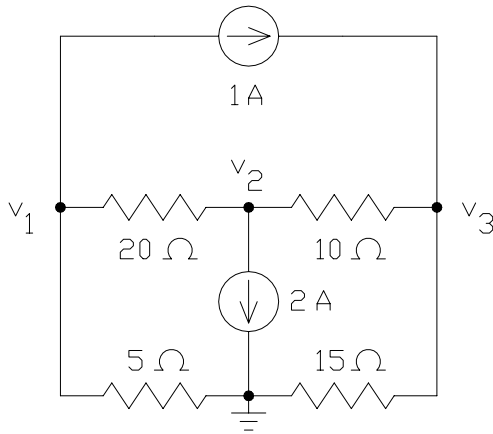

KCL at node 1:

$$0 = \frac{v_1 - v_2}{20} + \frac{v_1}{5} + 1 = \frac{-8 - (-20)}{20} + \frac{-8}{5} + 1$$


KCL at node 2:

$$\frac{-8 - (-20)}{20} = 2 + \frac{-20 - (-6)}{10} \Rightarrow \frac{12}{20} = \frac{6}{10}$$

KCL at node 3:  $\frac{-20 - (-6)}{10} + 1 = \frac{-6}{15} \Rightarrow \frac{-4}{10} = \frac{-6}{15}$

KCL is satisfied at all of the nodes so the computer analysis is correct.

**VP 4-5**

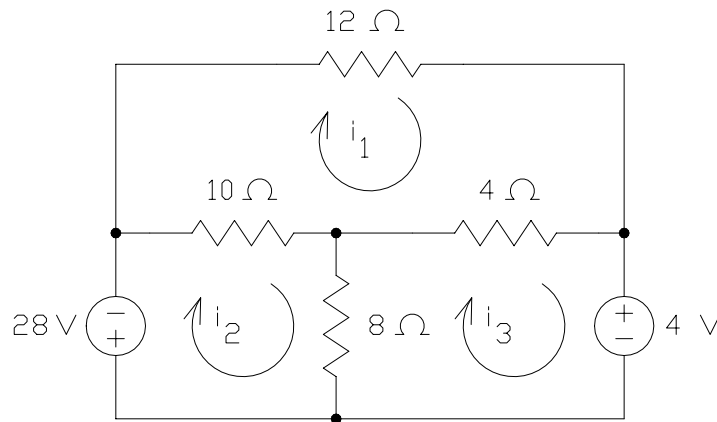

Top mesh:  $10(2 - 4) + 12(2) + 4(2 - 3) = 0$

Bottom right mesh  $8(3 - 4) + 4(3 - 2) + 4 = 0$


Bottom, left mesh:  $28 + 10(4 - 2) + 8(4 - 3) \neq 0$  (Perhaps the polarity of the 28 V source was entered incorrectly.)

KVL is not satisfied for the bottom, left mesh so the computer analysis is not correct.

## Design Problems

### DP 4-1

Simplify to

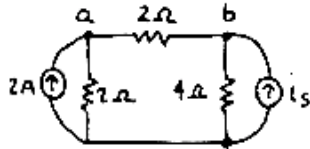

$$\text{KCL at node a: } v_a \left( \frac{1}{2} + \frac{1}{2} \right) - \frac{1}{2} v_b - 2 = 0 \quad (1)$$


$$\text{at node b: } -\frac{1}{2} v_a + \left( \frac{1}{2} + \frac{1}{4} \right) v_b - i_s = 0 \quad (2)$$

$$\text{now } v_{ba} = 3 = v_b - v_a \Rightarrow v_b = 3 + v_a \quad (3)$$

Plugging (3) into (1) yields:  $v_a = 7 \text{ V}$  &  $v_b = 10 \text{ V}$

thus from (2) get:  $i_s = 4 \text{ A}$

### DP 4-2

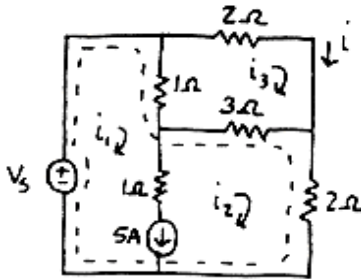

$$i_3 = i = 3 \text{ A}$$

$$\text{Supermesh: } -v_s + 1(i_1 - i_3) + 3(i_2 - i_3) + 2i_2 = 0$$

$$-v_s + i_1 + 5i_2 = 12 \quad (1)$$

$$\text{mesh 3: } 1(i_3 - i_1) + 2i_3 + 3(i_3 - i_2) = 0$$


$$i_1 + 3i_2 = 18 \quad (2)$$

$$\text{also } i_1 - i_2 = 5 \quad (3)$$

Combining (2) & (3) yields  $i_2 = 3.25 \text{ A}$ ,  $i_1 = 8.25 \text{ A}$

from (1)  $v_s = 12.5 \text{ V}$

### DP 4-3

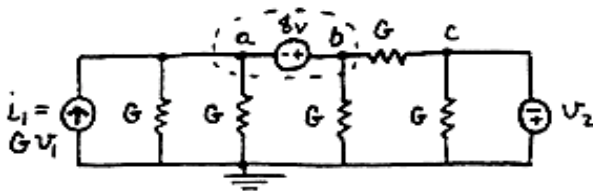

$$G = .5 \text{ S}$$

$$i_1 = Gv_1$$

$$v_c = -v_2$$

$$\text{Supernode: } v_a(G + G) + v_b(G + G) - Gv_c = i_1 \quad (1)$$

$$\text{also: } v_b - v_a = 8 \quad (2)$$

$$\text{Combining (1) \& (2) yields } v_a + (8 + v_a) + 5v_2 = 5v_1$$


$$2v_a = 5v_1 - 5v_2 - 8$$

$$\Rightarrow v_a = \frac{.5v_1 - .5v_2 - 8}{2} = 0$$

$$\therefore .5v_1 - .5v_2 = 8$$

so let  $v_2 = 2 \text{ V}$  and  $v_1 = 18 \text{ V}$  (one solution)

DP 4-4

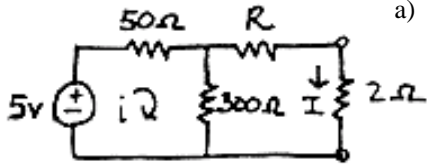

a) KVL left mesh :  $-5 + 50i + 300(i - I) = 0$  (1)

right mesh :  $(R+2)I + 300(I - i) = 0$  (2)

Solving (1) & (2) for I  $\Rightarrow I = \frac{150}{1570 + 35R}$  (3)

Desire  $50\text{mA} \leq I \leq 75\text{mA}$

so if  $R = 100$ , then  $I = 29.59 \text{ mA} \Rightarrow$  lamp will not light


b) from (3) note that as  $R \downarrow I \uparrow$ , so try  $R = 50 \Omega \Rightarrow I = 45 \text{ mA}$  (won't light)

try  $R = 25\Omega \Rightarrow I = 61 \text{ mA} \Rightarrow$  will light


Now check if  $R \pm 10\%$  will light and not burn out

$$\left. \begin{array}{l} -10\% \rightarrow 22.5\Omega \rightarrow I = 63.63 \text{ mA} \\ +10\% \rightarrow 27.5\Omega \rightarrow I = 59.23 \text{ mA} \end{array} \right\} \begin{array}{l} \text{lamp will} \\ \text{stay on} \end{array}$$

DP 4-5

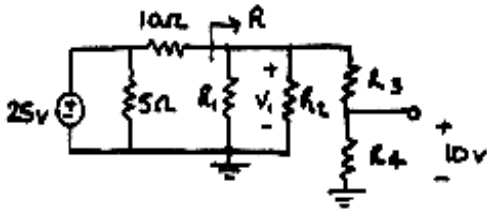

$$R = R_1 // R_2 // (R_3 + R_4)$$

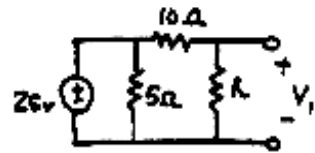

$$v_1 = 25 \frac{R}{10 + R}$$


Using voltage divider

$$10 = \frac{R_4}{R_3 + R_4} v_1 = \frac{R_4}{R_3 + R_4} \frac{(R_1 // R_2 // (R_3 + R_4))}{10 + (R_1 // R_2 // (R_3 + R_4))} 25$$

one solution: choose  $R_1 = R_2 = 25\Omega \rightarrow 10 = \frac{R_4}{20} \frac{(12.5 // 20)}{10 + (12.5 // 20)} 25 \Rightarrow R_4 = 18.4\Omega$

&  $R_3 + R_4 = 20 \Rightarrow R_3 = 1.6\Omega$

DP 4-6

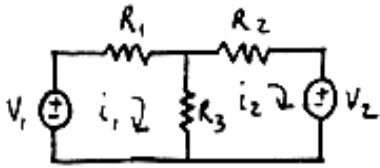

$$\text{mesh } i_1: (R_1 + R_3) i_1 - R_3 i_2 - v_1 = 0 \quad (1)$$

$$\text{mesh } i_2: -R_3 i_1 + (R_2 + R_3) i_2 + v_2 = 0 \quad (2)$$

$$\text{from (1) \& (2) get: } i_1 = \frac{\begin{bmatrix} v_1 & -R_3 \\ -v_2 & (R_2 + R_3) \end{bmatrix}}{\Delta} \quad i_2 = \frac{\begin{bmatrix} (R_1 + R_3) & v_1 \\ -R_3 & -v_2 \end{bmatrix}}{\Delta}$$

$$\text{where } \Delta = (R_1 + R_3)(R_2 + R_3) - R_3^2$$

Now if  $R_1 = R_2 = R_3 = 1K$  where  $K$  represents 1000

$$\text{then } \Delta = 4 - 1 = 3K^2$$


$$\text{so we have } i_1 = \frac{[2v_1 - v_2] K}{3K^2}, \quad i_2 = \frac{[-2v_2 + v_1] K}{3K^2}$$

$$\Rightarrow i = i_1 - i_2 = \frac{v_1 + v_2}{3K}$$

$$\text{if } v_1 = v_2 = 1 \text{ V} \Rightarrow i = \frac{2}{3} \text{ mA} \quad \text{okay}$$

$$\text{if } v_1 = v_2 = 2 \text{ V} \Rightarrow i = \frac{4}{3} \text{ mA} \quad \text{okay}$$

DP 4-7

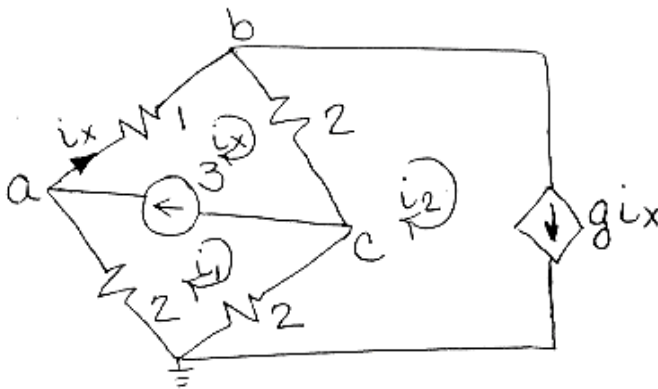

$$v_a - v_c = \frac{20}{3}$$

$$i_x - i_1 = 3$$

$$v_a = -2i_1$$

$$i_2 = g i_x$$

$$v_c = 2i_1 - 2i_2$$

$$i_x + 2i_x - 2i_2 + 2i_1 - 2i_2 + 2i_1 = 0$$

$$\text{Substituting solve for } g: \underline{g=4}$$