

Chapter 5 Circuit Theorems

Exercises

Ex 5.3-1 $R = 10 \Omega$ and $i_s = 1.2 \text{ A}$.

Ex 5.3-2 $R = 10 \Omega$ and $i_s = -1.2 \text{ A}$.

Ex 5.3-3 $R = 8 \Omega$ and $v_s = 24 \text{ V}$.





Ex 5.3-4 $R = 8 \Omega$ and $v_s = -24 \text{ V}$.

Ex 5.4-1 $v_m = \frac{20}{10+20+20}15 + 20\left(-\frac{10}{10+(20+20)}2\right) = 6 + 20\left(-\frac{2}{5}\right) = -2 \text{ V}$


Ex 5.4-2 $i_m = \frac{25}{3+2} - \frac{3}{2+3}5 = 5 - 3 = 2 \text{ A}$

Ex 5.4-3 $v_m = 3\left(\frac{3}{3+(3+3)}5\right) - \frac{3}{3+(3+3)}18 = 5 - 6 = -1 \text{ A}$

Ex 5.5-1

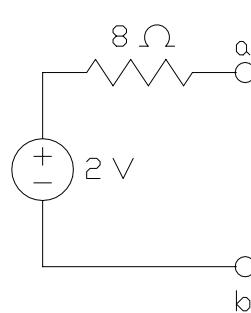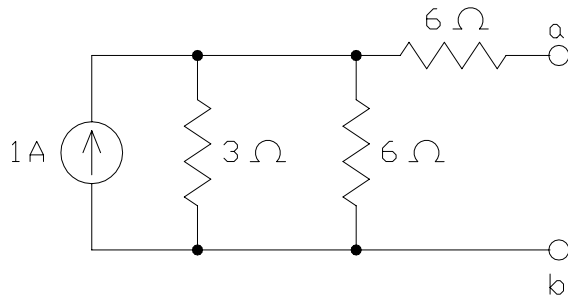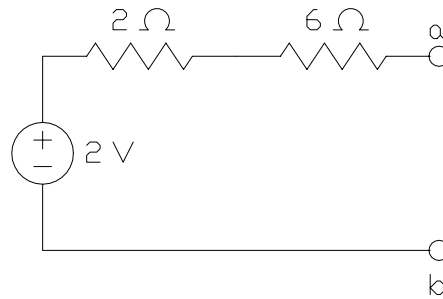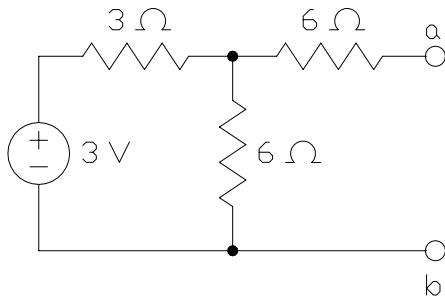


Ex 5.5-2

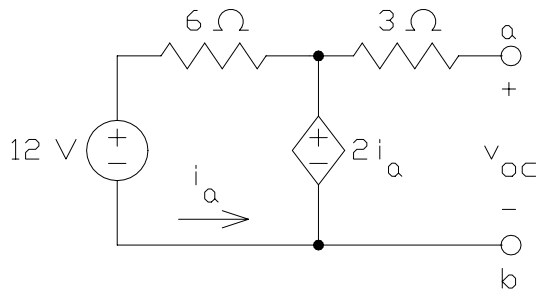

$$i_a = \frac{2i_a - 12}{6} \Rightarrow i_a = -3 \text{ A}$$

$$v_{oc} = 2i_a = -6 \text{ V}$$

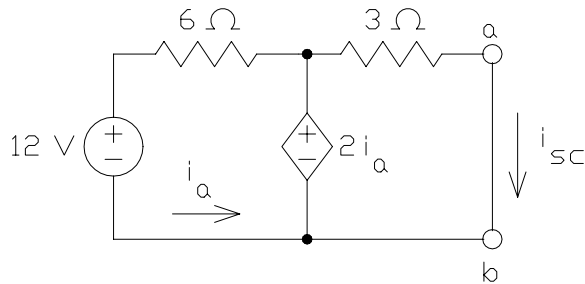


$$12 + 6i_a = 2i_a \Rightarrow i_a = -3 \text{ A}$$

$$3i_{sc} = 2i_a \Rightarrow i_{sc} = \frac{2}{3}(-3) = -2 \text{ A}$$

$$R_t = \frac{-6}{-2} = 3 \Omega$$

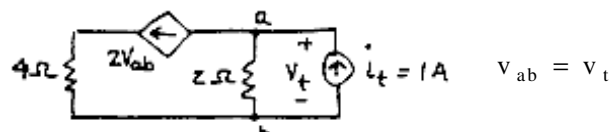
Ex. 5.5-3 No independent sources $\therefore v_{oc} = i_{sc} = 0 \Rightarrow$ apply 1A test source







$$\text{KCL at a: } 2v_t + \frac{v_t}{2} - 1 = 0 \Rightarrow v_t = \frac{2}{5} \text{ V}$$

$$\therefore R_T = \frac{v_t}{i_t} = \frac{2}{5} \Omega$$


Thev. equiv. ckt

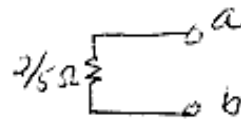


Ex 5.6-1

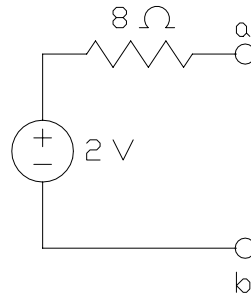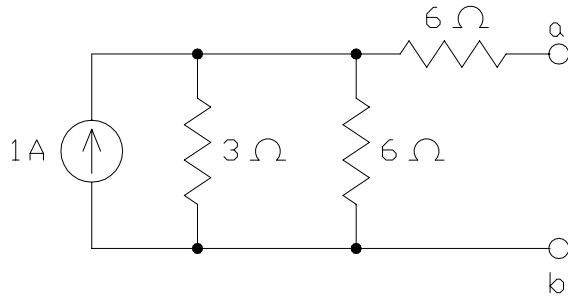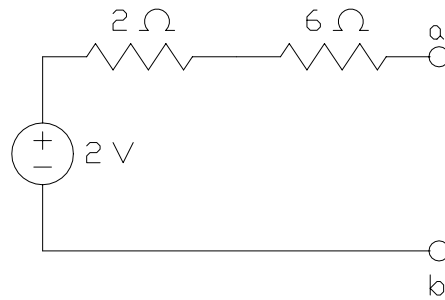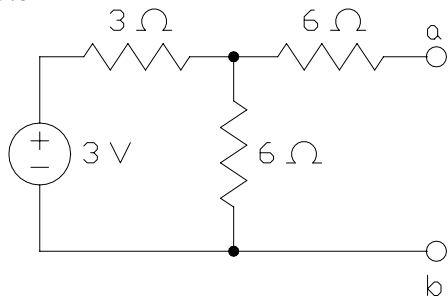

Finally:

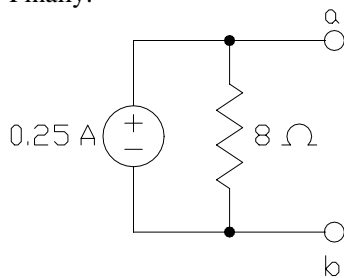


Ex 5.6-2

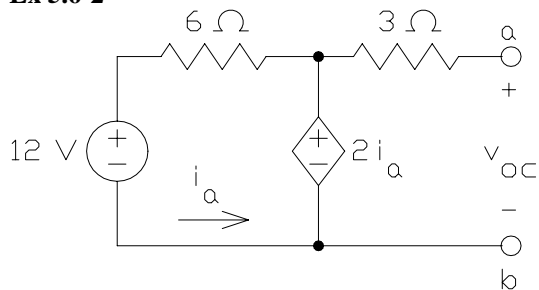

$$i_a = \frac{2i_a - 12}{6} \Rightarrow i_a = -3 \text{ A}$$

$$v_{oc} = 2i_a = -6 \text{ V}$$

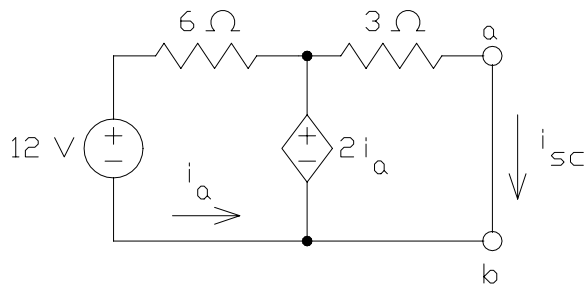


$$12 + 6i_a = 2i_a \Rightarrow i_a = -3 \text{ A}$$

$$3i_{sc} = 2i_a \Rightarrow i_{sc} = \frac{2}{3}(-3) = -2 \text{ A}$$

$$R_t = \frac{-6}{-2} = 3 \Omega$$


Ex. 5.6-3

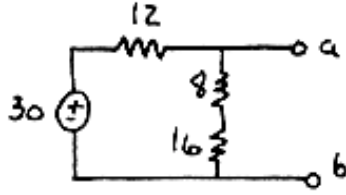

$$R_T = \frac{12 \times 24}{12 + 24} = \frac{12 \times 24}{36} = 8\Omega$$


$$v_{oc} = \frac{24}{12 + 24} \cdot 30 = 20V$$

So we have

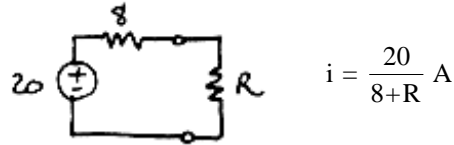

$$i = \frac{20}{8 + R} \text{ A}$$


Ex. 5.7-1 Find v_{oc}

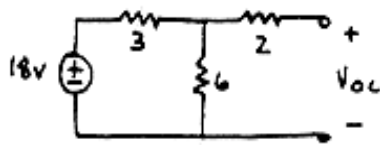


From voltage divider

$$v_{oc} = 18V \left(\frac{6}{6+3} \right) = 12V$$

Find R_T (short 18V source)

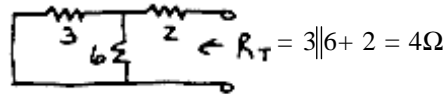


\therefore Thev. equiv. ckt \Rightarrow

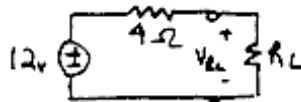

For max power to $R_L \Rightarrow R_L = R_T = 4\Omega \quad \therefore P_{\max_{R_L}} = \frac{(v_{RL})^2}{R_L} = \frac{(6)^2}{4} = 9W$

Ex. 5.7-2 Find i_{sc}

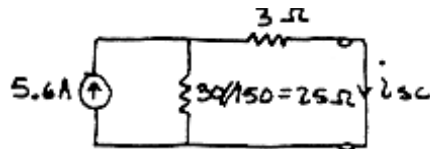

From current divider

$$i_{sc} = 5.6A \left(\frac{25}{25+3} \right)$$


$$\underline{i_{sc} = 5A}$$

Find R_T (open 5.6A source)



$$R_T = 25 + 3 = \underline{28\Omega}$$

\therefore Norton equiv. ckt \Rightarrow

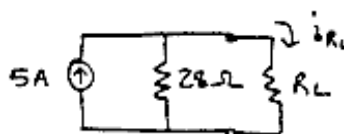

For max power $R_L = R_T = 28\Omega \quad \therefore P_{L_{\max}} = (i_{R_L})^2 R_L = (5/2)^2 (28) = \underline{175W}$

Ex. 5.7-3




$$P_{L_{\max}} = \frac{(V_{L_{\max}})^2}{R_L} = \frac{\left[10V\left(\frac{5}{5+R_t}\right)\right]^2}{R_L}$$

Now for V_L to be maximized, R_t must be minimized

\therefore choose $R_t = 1\Omega$

$$\therefore P_{L_{\max}} = \frac{\left[10\left(\frac{5}{6}\right)\right]^2}{5} = \underline{13.9W}$$

Ex. 5.7-4

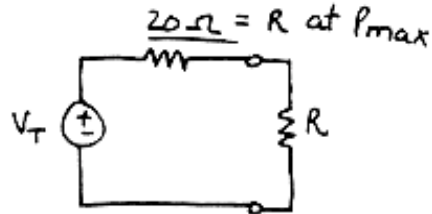

$$P_{\max} = 5 = \left(\frac{V_T}{40}\right)^2 20 = \frac{V_T^2}{80}$$







$$V_T = \sqrt{400} = \underline{20V}$$

PROBLEMS

Section 5-3: Source Transformations

P5.3-1


(a)

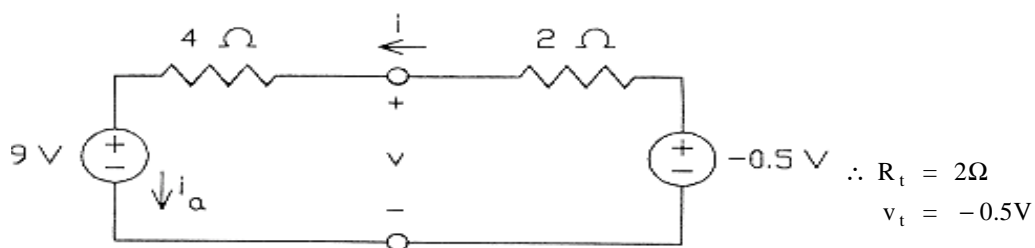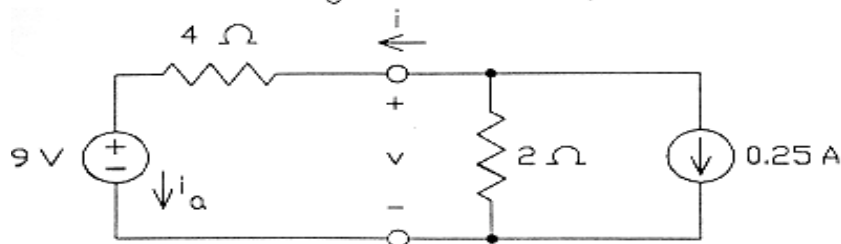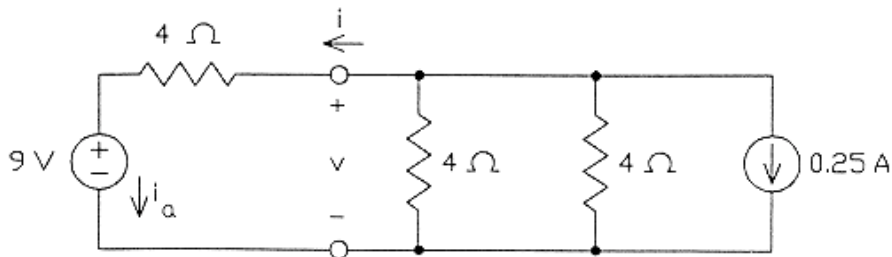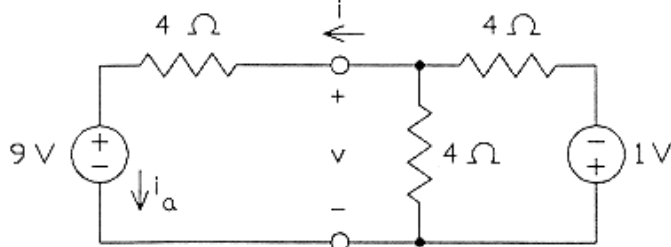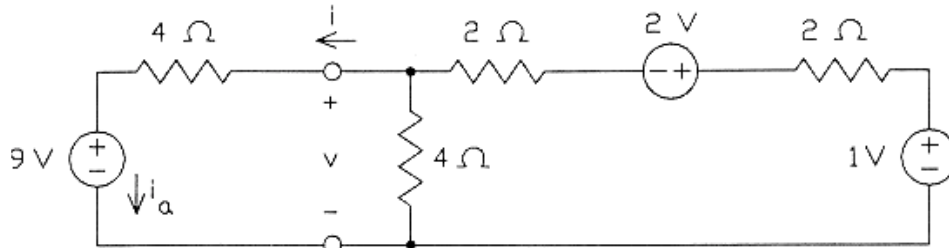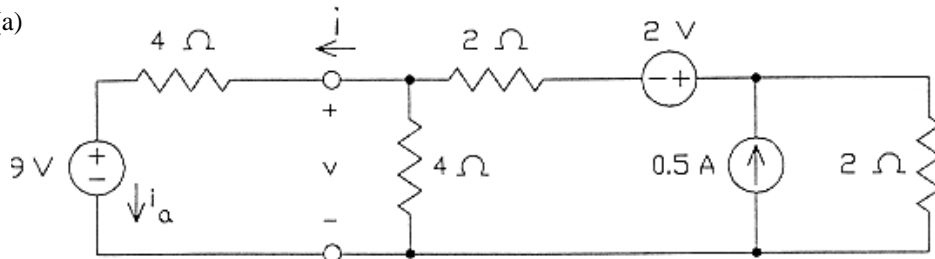

(b) $-9 - 4i - 2i + (-0.5) = 0$
 $i = \frac{-9 + (-0.5)}{4 + 2} = -1.58A$
 $v = 9 + 4i = 9 + 4(-1.58) = 2.67V$


(c) $i_a = i = -1.58A$

P5.3-2

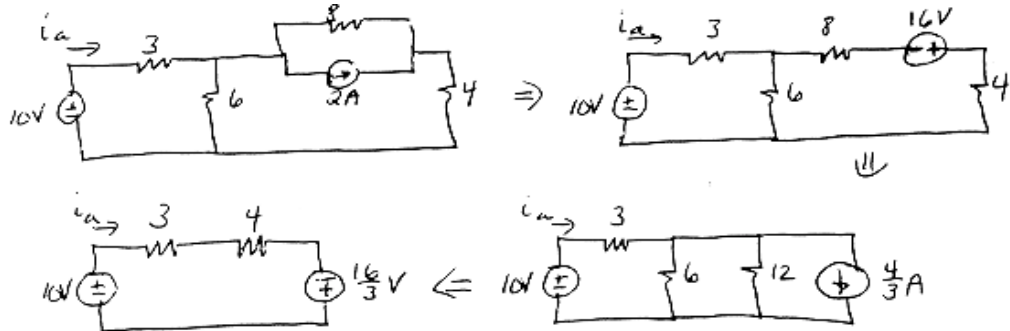


KVL: $-10 + 3i_a + 4i_a - \frac{16}{3} = 0 \quad \therefore i_a = 2.19A$

P5.3-3

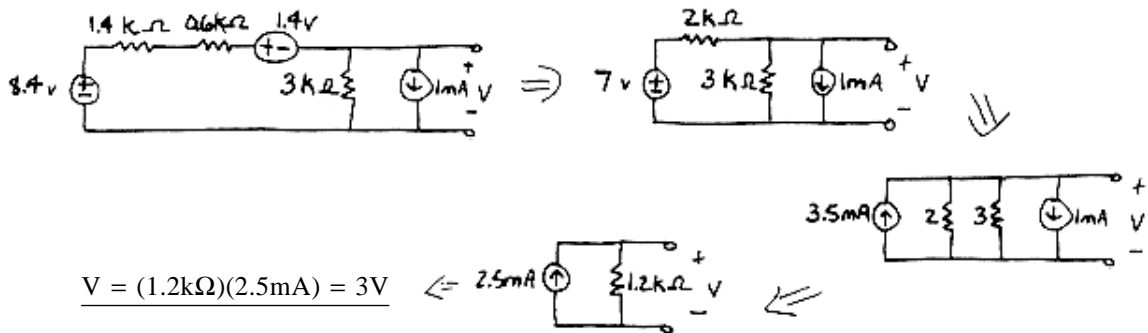


$V = (1.2k\Omega)(2.5mA) = 3V$

P5.3-4

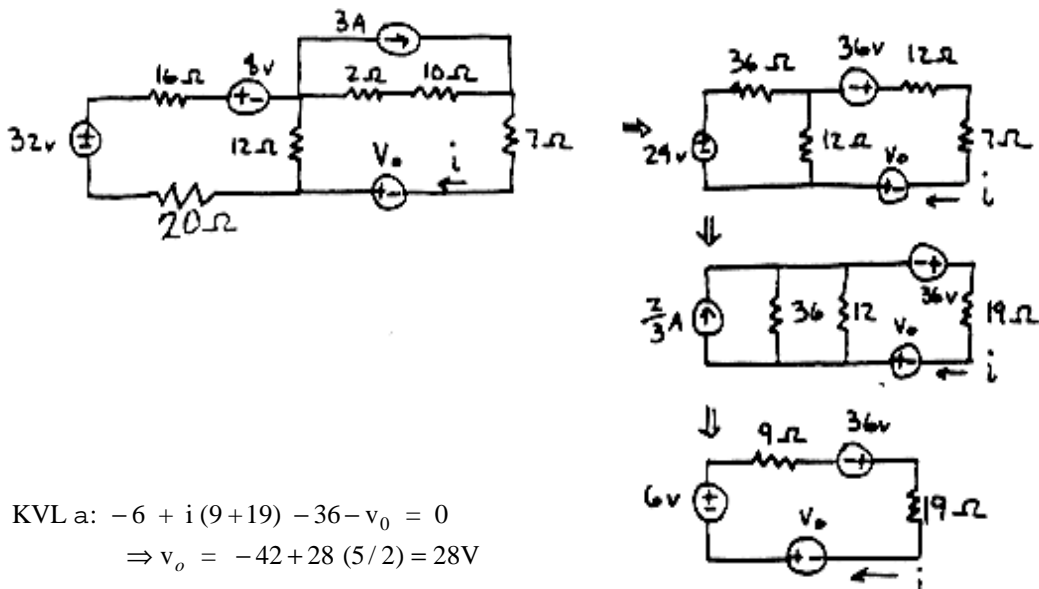

KVL a: $-6 + i(9 + 19) - 36 - v_o = 0$
 $\Rightarrow v_o = -42 + 28(5/2) = 28V$


P5.3-5

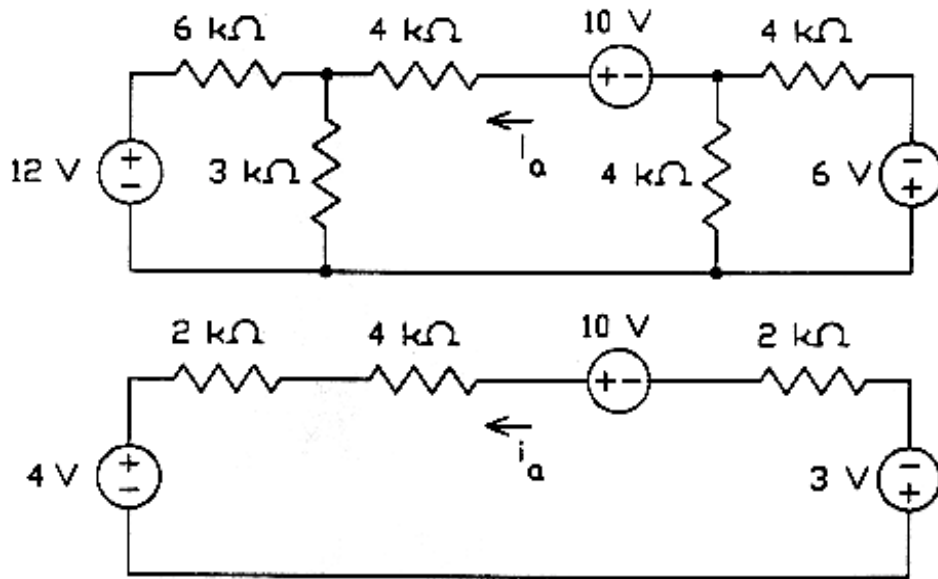

$$-4 - 2000i_a - 4000i_a + 10 - 2000i_a - 3 = 0$$

$$\therefore i_a = 375 \mu\text{A}$$

P5.3-6

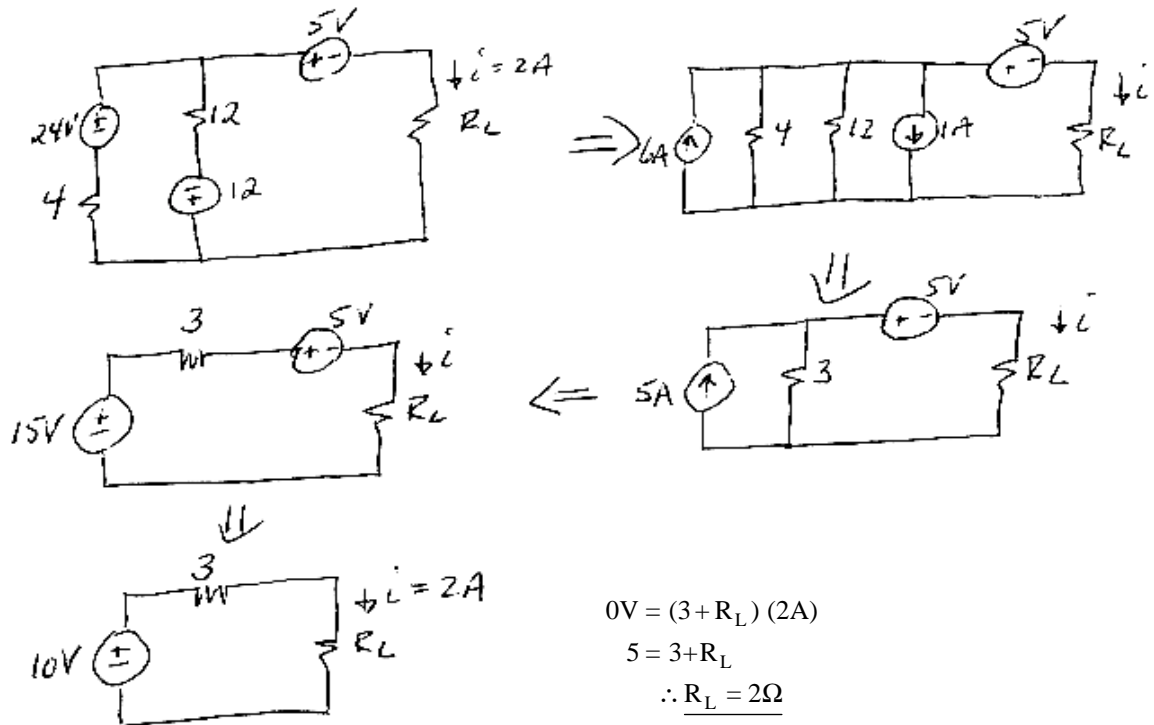




$$0V = (3 + R_L)(2A)$$

$$5 = 3 + R_L$$

$$\therefore R_L = 2\Omega$$

Section 5-4 Superposition

P5.4-1

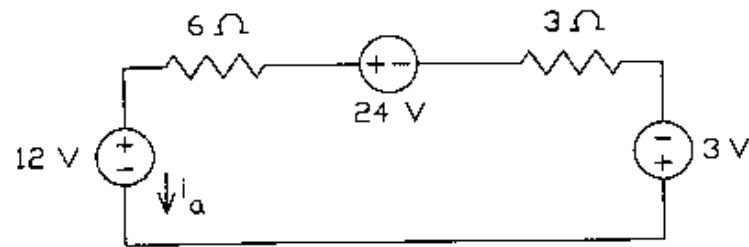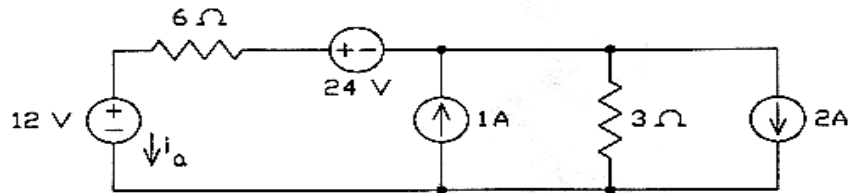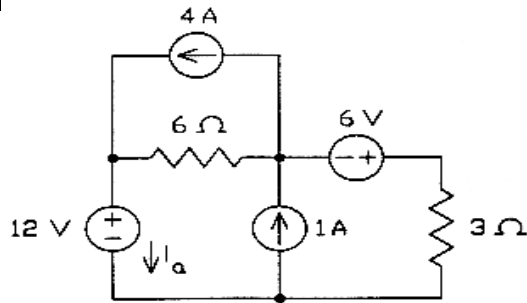

$$-12 - 6i_a + 24 - 3i_a - 3 = 0 \Rightarrow i_a = 1 \text{ A}$$


P5.4-2 Consider 6A source only (open 9A source)



From current divider:

$$v_1 / 20 = 6 \left[\frac{15}{15 + 30} \right] \Rightarrow v_1 = 40 \text{ V}$$

Consider 9A source only (open 6A source)

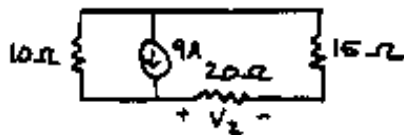


Current divider

$$v_2 / 20 = 9 \left[\frac{10}{10 + 35} \right] \Rightarrow v_2 = 40 \text{ V}$$

$$\therefore v = v_1 + v_2 = 40 + 40 = 80 \text{ V}$$

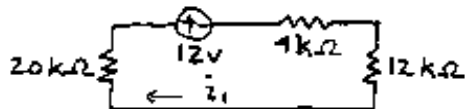
P5.4-3 Consider 12V source only (open both current sources)



$$\text{KVL a: } 20i_1 + 12 + 4i_1 + 12i_1 = 0$$

$$\Rightarrow i_1 = -1/3 \text{ mA}$$

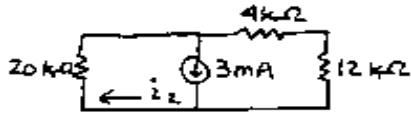
Consider 12mA source only (short 12V and open 6mA sources)



From current divider

$$i_2 = 3 \left[\frac{16}{16+20} \right] = \underline{\underline{\frac{4}{3} \text{ mA}}}$$

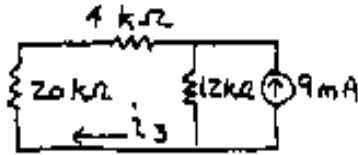Consider 9mA source only (short 12V and open 12mA sources)




From current divider

$$i_3 = -9 \left[\frac{12}{24+12} \right] = \underline{\underline{-3 \text{ mA}}}$$

$$\therefore i = i_1 + i_2 + i_3 = -1/3 + 4/3 - 3 = \underline{\underline{-2 \text{ mA}}}$$

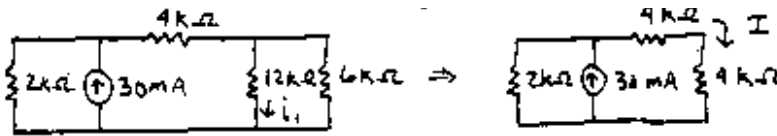P5.4-4 Consider 30mA source only (open 15mA and short 60V sources)




$$\text{Current divider} \Rightarrow I = 30 \left(\frac{2}{2+8} \right) = 6 \text{ mA}$$

$$\therefore i_1 = I \left(\frac{6}{6+12} \right) = \underline{\underline{2 \text{ mA}}}$$

Consider 15mA source only (open 30mA source and short 60V source)

Continued

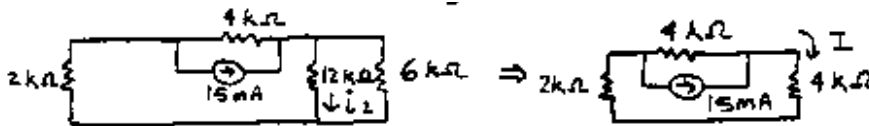

$$\text{Current divider} \Rightarrow I = 15 \left(\frac{4}{4+6} \right) = 6 \text{ mA}$$

$$\therefore i_2 = I \left(\frac{6}{6+12} \right) = \underline{\underline{2 \text{ mA}}}$$

Consider 15V source only (open both current sources)




From current divider

$$i_3 = -2.5 \left(\frac{6/6}{6/6+12} \right) = -10 \left(\frac{3}{3+12} \right) = \underline{\underline{-5 \text{ mA}}}$$

$$\therefore i = i_1 + i_2 + i_3 = 2 + 2 - 5 = \underline{\underline{3.5 \text{ mA}}}$$

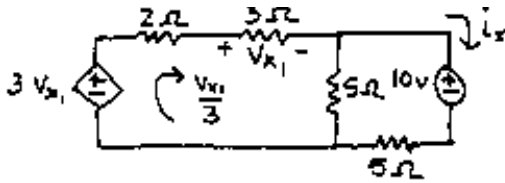P5.4-5 Consider 10V source only (open 4A source)



KVL 1st mesh a:


$$-3v_{x_1} + 5\left(\frac{v_{x_1}}{3}\right) + 5\left(\frac{v_{x_1}}{3} - i_x\right) = 0$$

$$\Rightarrow \underline{v_{x_1} = 15i_x} \quad (1)$$

KVL 2nd mesh a: $5(i_x - v_{x_1}/3) + 10 + 5i_x = 0$ (2)

Solving (1) and (2) simultaneously $\Rightarrow \underline{v_{x_1} = 10V}$

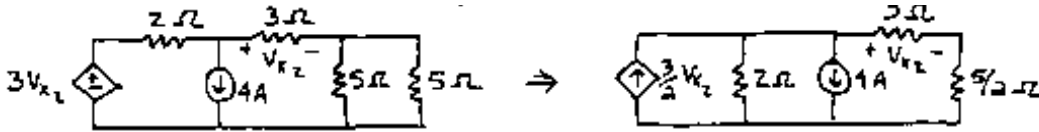
Consider 4A source only (short 10V source)



Using current divider: $\frac{v_{x_2}}{3} = (3/2v_{x_2} - 4)\left(\frac{2}{2+3+5/2}\right) \Rightarrow \underline{v_{x_2} = 16V}$

$\therefore \underline{v_x = v_{x_1} + v_{x_2} = 10 + 16 = 26V}$

P5.4-6

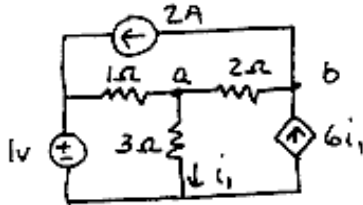

KCL at b: $i + 6i_1 - 2 = 0$


$\Rightarrow i_1 = 1/3 - 1/6 i$ (1)

KVL around left lower mesh:

$1(i_1 + i) + 3i_1 - 1 = 0$ (2)

Plugging (1) into (2) $\Rightarrow \underline{i = -1A}$


P5.4-7 Consider v_2 source only

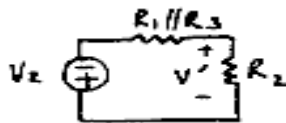

Voltage divider: $v' = -v_2 \left[\frac{R_2}{R_2 + R_1 \parallel R_3} \right]$

$v' = -v_2 \left[\frac{R_2(R_1 + R_3)}{R_1 R_2 + R_1 R_3 + R_2 R_3} \right]$

Consider v_1 source only

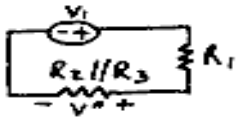

Voltage divider $v'' = v_1 \left[\frac{R_2 \parallel R_3}{R_2 \parallel R_3 + R_1} \right]$

$v'' = v_1 \left[\frac{R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} \right]$

Consider i_1 source only




$v''' = 0$ since no current flows through R_2, R_3 and R_1





$\therefore \underline{v = v' + v'' + v'''} = \frac{v_1 R_2 R_3 - v_2 (R_2 (R_1 + R_3))}{R_1 R_2 + R_1 R_3 + R_2 R_3}$

Section 5-5: Thévenin's Theorem


Ex 5.5-1

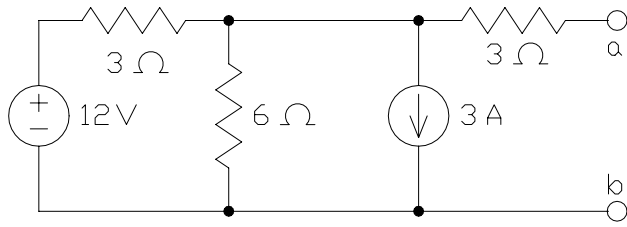


(a)

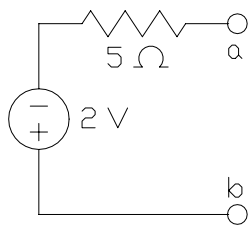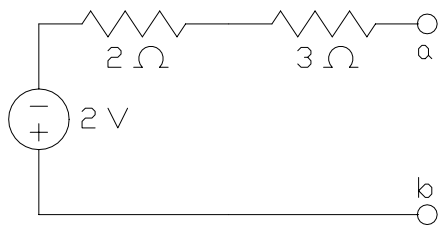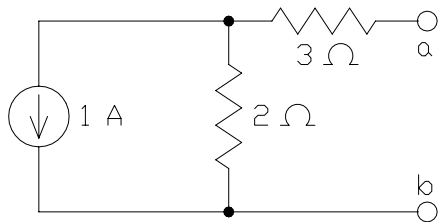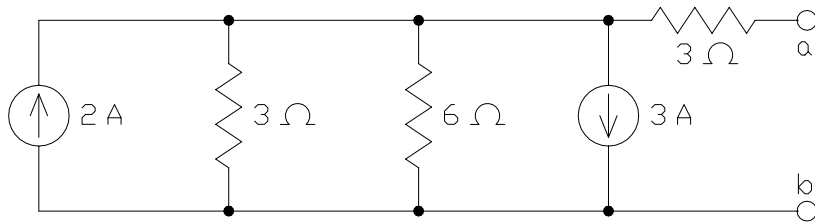


P5.5-2 Use source transformations

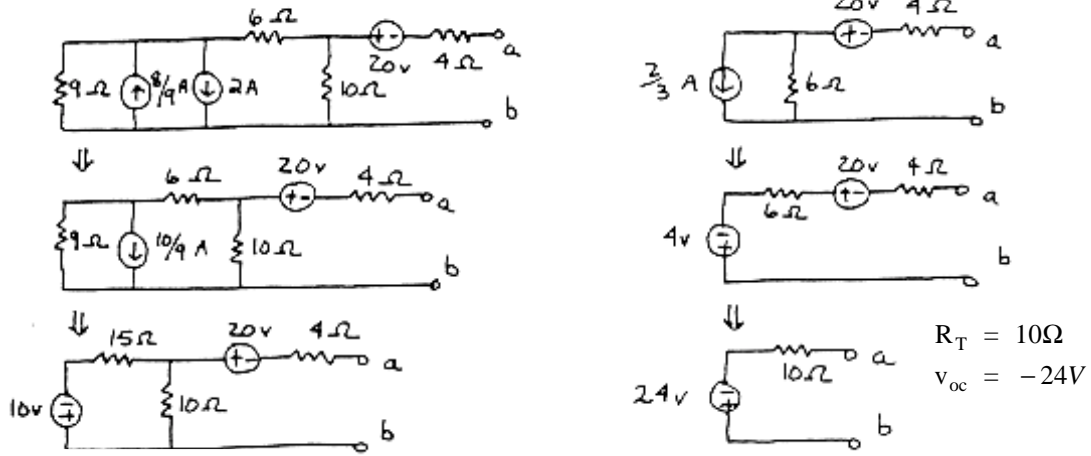

P5.5-3 Use source transformations

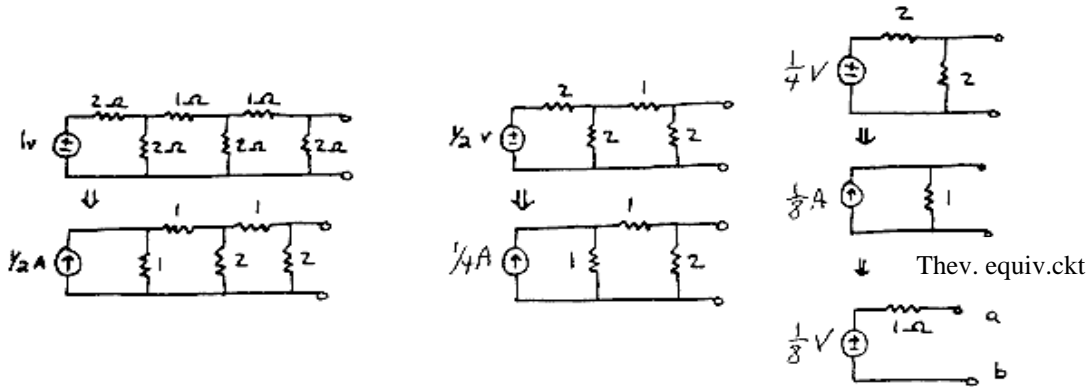


P5.5-4 Find R_T :

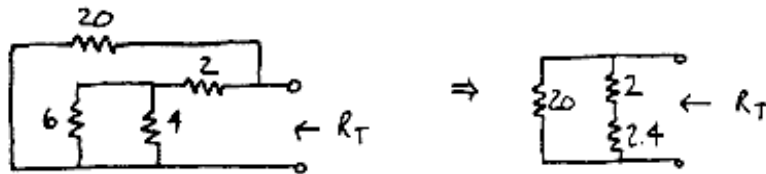

$$R_T = \frac{20(2+2.4)}{20+2+2.4} = \underline{3.61\Omega}$$

Continued

Find v_T :

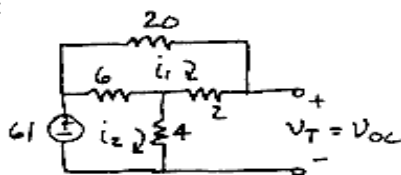

$$v_T = 2i_1 + 4i_2$$


$$\text{mesh } i_1: 28i_1 - 6i_2 = 0 \quad (1)$$

$$\text{mesh } i_2: -6i_1 + 10i_2 - 61 = 0 \quad (2)$$

Solving (1) & (2) yields: $i_1 = 1.5A$, $i_2 = 7A$

$$\therefore v_T = 3 + 28 = \underline{31V}$$


P5.5-5 Find v_{oc}

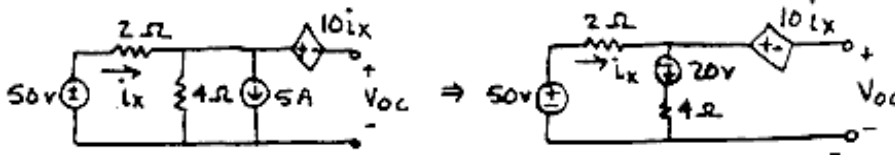

KVL around 1st mesh a: $-50 + 2i_x - 20 + 4i_x = 0 \Rightarrow i_x = 70/6 \text{ A}$

KVL around 2nd mesh a: $-4i_x + 20 + 10i_x + v_{oc} = 0$
 $\Rightarrow v_{oc} = -90 \text{ V}$

Find i_{sc}

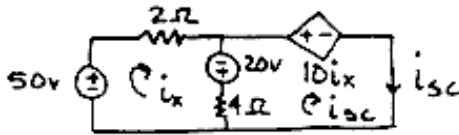


KVL i_x mesh a: $-50 + 2i_x - 20 + 4(i_x - i_{sc}) = 0$
 $6i_x - 4i_{sc} - 70 = 0$ (1)

KVL i_{sc} mesh a: $4(i_{sc} - i_x) + 20 + 10i_x = 0$
 $6i_x + 4i_{sc} + 20 = 0$ (2)


Solving (1) and (2) simultaneously $\Rightarrow i_{sc} = -45/4 \text{ A}$

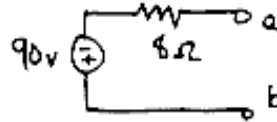$\therefore R_T = \frac{v_{oc}}{i_{sc}} = 8\Omega$ Thev. equiv.ckt :



P5.5-6

For v_{oc} :

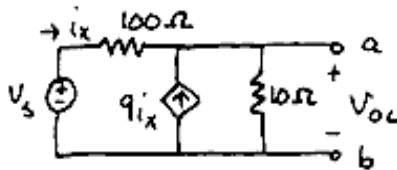


$i_x = \frac{v_s - v_{oc}}{100}$

KCL at terminal a:

$\frac{1}{100}(v_{oc} - v_s) - 9\left[\frac{1}{100}(v_s - v_{oc})\right] + \frac{1}{10}v_{oc} = 0$
 $\Rightarrow v_{oc} = \frac{1}{2}v_s$

Use current source at a-b to find R_T :

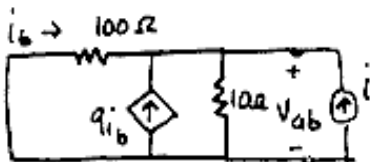


$i_b = -\frac{v_{ab}}{100}$


KCL: $\frac{1}{100}v_{ab} - 9\left[\frac{1}{100}(-v_{ab})\right] + \frac{1}{10}v_{ab} - i = 0$

$\Rightarrow i = \frac{1}{5}v_{ab} \therefore R_T = \frac{v_{ab}}{i} = 5\Omega$

So Thev. equiv.

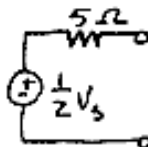


P5.5-7

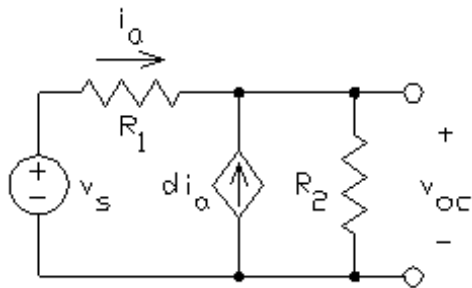

$$v_s + R_1 i_a + (d+1)R_2 i_a = 0$$


$$i_a = \frac{v_s}{R_1 + (d+1)R_2}$$
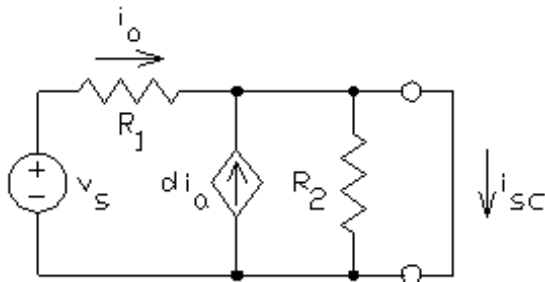
$$v_{oc} = \frac{(d+1)R_2 v_s}{R_1 + (d+1)R_2}$$



$$i_a = \frac{v_s}{R_1}$$
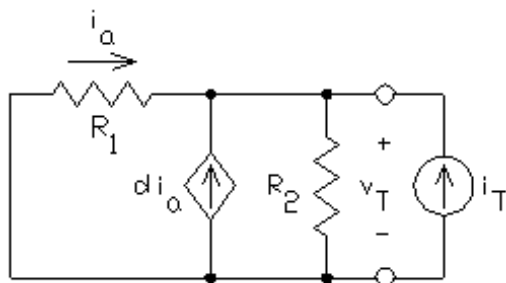
$$i_{sc} = (d+1)i_a = \frac{(d+1)v_s}{R_1}$$



$$-i_a - d i_a + \frac{v_T}{R_2} - i_T = 0$$

$$R_1 i_a = -v_T$$

$$i_T = (d+1) \frac{v_T}{R_1} + \frac{v_T}{R_2} = \frac{R_2(d+1) + R_1}{R_1 R_2} v_T$$

$$R_t = \frac{v_T}{i_T} = \frac{R_1 R_2}{R_1 + (d+1)R_2}$$

(b) Let $R_1 = R_2 = 1 \text{ k}\Omega$. Then


$$625 \Omega = R_t = \frac{1000}{d+2} \Rightarrow d = \frac{1000}{625} - 2 = -0.4 \text{ A/A}$$

and

$$5 = \frac{(d+1)v_s}{d+2} \Rightarrow v_s = \frac{-0.4+2}{-0.4+1} 5 = 13.33 \text{ V}$$

P5.5-8

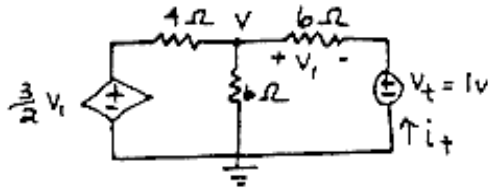Since no independent sources $v_{oc} = i_{sc} = 0 \therefore$ apply test source




$$V = v_1 + v_t$$

KCL at V: $\frac{(V - \frac{3}{2}v_t)}{4} + \frac{V}{6} + \frac{v_1}{6} = 0$ & with $V = v_1 + 1$ so $v_1 = -2A$

now $i_t = -\frac{v_1}{6} = \frac{1}{3}A \therefore R_T = \frac{v_t}{i_t} = \frac{1}{\frac{1}{3}} = 3\Omega$

P5.5-9

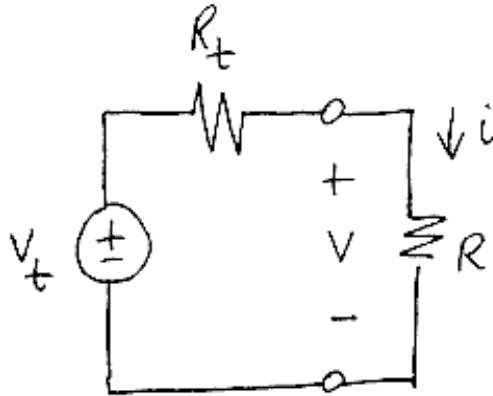

$$V = \frac{R}{R+R_t} v_t$$


$$6 = \frac{2000}{2000+R_t} v_t \quad (\text{line 1})$$

$$2 = \frac{4000}{4000+R_t} v_t \quad (\text{line 2})$$

$$\therefore \underline{v_t = 1.2V} \quad \text{and} \quad \underline{R_t = -1600\Omega}$$

When $R = 8000$, $V = \frac{8000}{8000-1600} 1.2 = \underline{1.5V}$

P5.5-10

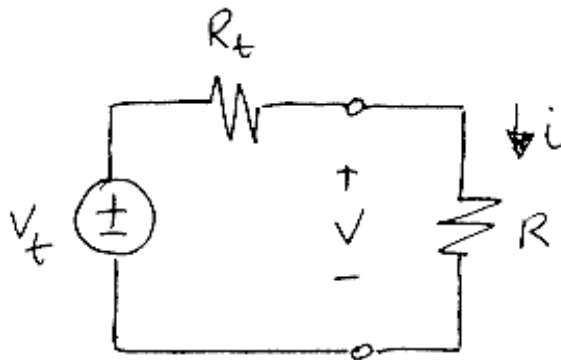

$$i = \frac{v_t}{R+R_t}$$

$$0.004 = \frac{v_t}{2000+R_t} \quad (1)$$

$$0.003 = \frac{v_t}{4000+R_t} \quad (2)$$

so $\underline{v_t = 24V}$ and $\underline{R_t = 4000\Omega}$

(a) $0.002 = \frac{24}{R+4000} \Rightarrow \underline{R = 8000\Omega}$


(b) when $R = 0$ then $i = \frac{24}{4000} = \underline{6 \text{ mA}}$

P5.5-11


From the graph, when $v_{ab} = v = 0 \Rightarrow i = i_{sc} = 20 \text{ mA}$
 when $i = 0 \Rightarrow v = v_{oc} = -3 \text{ V}$

$$\therefore R_T = \frac{v_{oc}}{i_{sc}} = \frac{-3 \text{ V}}{20 \text{ mA}} = -15 \text{ k}\Omega = -150 \Omega$$

Thev. equiv. ckt \Rightarrow

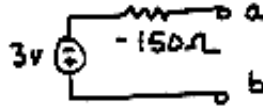


P5.5-12

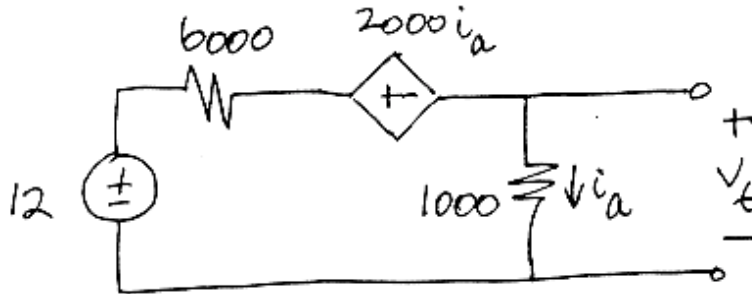

$$-12 + 6000i_a + 2000i_a + 1000i_a = 0$$

$$i_a = 4/3000 \text{ A}$$

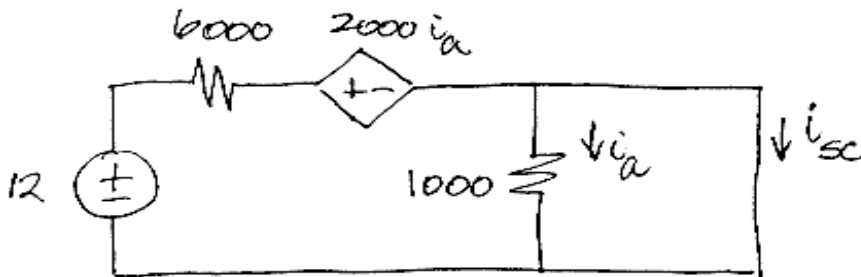
$$v_t = 1000 i_a = \frac{4}{3} \text{ V}$$



$$i_a = \frac{0}{1000} = 0$$

$$-12 + 6000i_{sc} = 0 \Rightarrow i_{sc} = 2 \text{ mA}$$
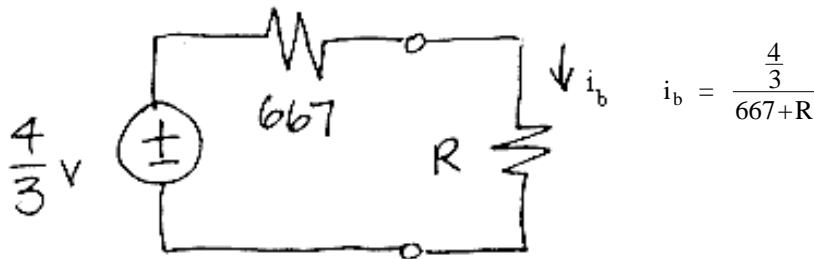
$$R_t = \frac{v_t}{i_{sc}} = \frac{\frac{4}{3}}{.002} = 667 \Omega$$




$$i_b = \frac{\frac{4}{3}}{667 + R}$$

$$\therefore i_b = 0.002 \text{ requires } R = \frac{\frac{4}{3}}{0.002} - 667 = 0$$

P5.5-13


- 1) disconnect R_L
open circuit a - b

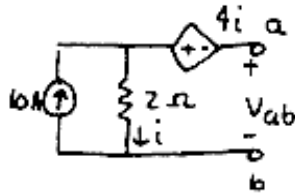

$$\text{KVL: } -v_{ab} - 4i + 2i = 0, \quad i = 10A$$

$$\Rightarrow v_T = v_{ab} = -2i = \underline{-20V}$$

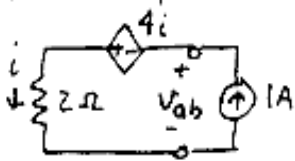- 2) set independent source = 0 and place 1A source at a - b




$$\text{KVL: } -v_{ab} - 4i + 2i = 0, \quad i = 1A$$

$$\Rightarrow v_{ab} = -2A$$

$$\therefore R_T = v_{ab}/1A = \underline{-2\Omega}$$

- 3)

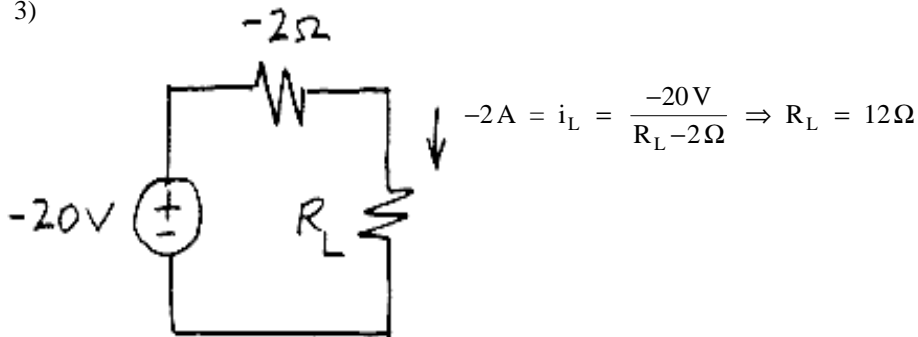


P5.5-14


When the terminals of the boxes are open-circuited, no current flows in Box A, but the resistor in Box B dissipates 1 watt. Box B is therefore warmer than Box A. If you short the terminals of each box, the resistor in Box A will draw 1 amp and dissipate 1 watt. The resistor in Box B will be shorted, draw no current, and dissipate no power. Then Box A will warm up and Box B will cool off.

P5.5-15

Redraw ckt as:

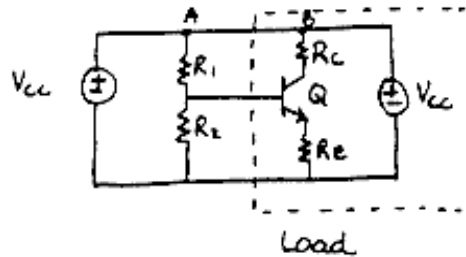

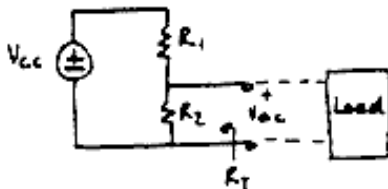
Since points A & B are at same potential, virtually no current exists between A-B \therefore open ckt.



Find R_T : kill v_{cc} source $\Rightarrow R_T = R_1 \parallel R_2 = R_1 R_2 / (R_1 + R_2)$

Find v_{oc} : voltage divider $v_{oc} = v_{cc} \left(\frac{R_2}{R_1 + R_2} \right)$

can replace above ckt as :

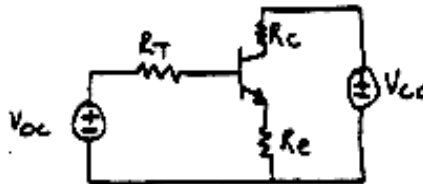


where $v_{oc} = v_{cc} \left(\frac{R_2}{R_1 + R_2} \right)$

$$R_T = \frac{R_2 R_1}{R_2 + R_1}$$

P5.5-16

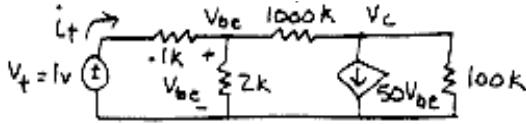(a) Since there are no independent sources, apply test source



$$\begin{aligned} \text{KCL at } v_{be} : & -i_t + \frac{1}{2}v_{be} + (v_{be} - v_c)/1000 = 0 \\ \downarrow & -1000i_t + 501v_{be} - v_c = 0 \end{aligned} \quad (1)$$


$$\begin{aligned} \text{KCL at } v_c : & (v_c - v_{be})/1000 + 50v_{be} + v_c/100 = 0 \\ \downarrow & 11v_c + 50000v_{be} = 0 \end{aligned} \quad (2)$$

$$\text{also } (1 - v_{be})/.1 = i_t \quad (3)$$

Solving (1), (2), & (3) simultaneously yields $i_t = 3.35 \text{ mA}$

$$\therefore R_{IN} = \frac{v_t}{i_t} = \frac{1 \text{ V}}{3.35 \text{ mA}} = .299 \text{ k}\Omega = 299 \Omega$$

(b) Apply test source

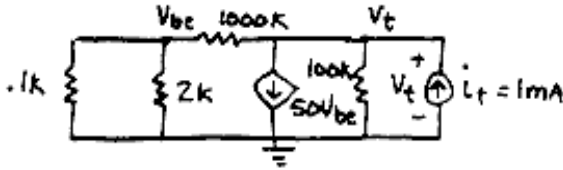

$$\begin{aligned} \text{KCL at } v_{be} : & v_{be}/.1 + v_{be}/2 + (v_{be} - v_t)/1000 = 0 \\ \downarrow & 10501v_{be} = v_t \end{aligned} \quad (1)$$

$$\begin{aligned} \text{KCL at } v_t : & (v_t - v_{be})/1000 + 50v_{be} + v_t/100 - 1 = 0 \\ \downarrow & 11v_t + 49999v_{be} - 1000 = 0 \end{aligned} \quad (2)$$

Solving (1) & (2) yields : $v_t = 63.5 \text{ V}$

$$\therefore R_{out} = v_t/i_t = 63.5 \text{ V}/1 \text{ mA} = 63.5 \text{ k}\Omega$$

P5.5-17


When $0 < V < V_p$, it works as a pure resistor

$$\text{so } R = V_p/I_p \quad V_{oc} = 0$$




When $V_p < V < V_m$, it is linear but shows negative resistance characteristic

$$\begin{aligned} \Rightarrow V_{oc} &= V_{oc}|_{I=0} = V_1 \\ R &= \frac{V_{oc}}{I_{sc}} = -\frac{V_1}{I_1} \end{aligned}$$

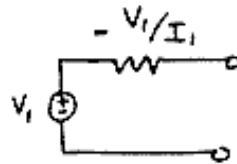


When $V_m < V < V_f$, it is linear

$$\begin{aligned} \text{so } V_{oc} &= V_{oc}|_{I=0} = V_2 \\ R &= \frac{V_{oc}}{I_{sc}} = \frac{V_f - V_2}{I_p} \end{aligned}$$

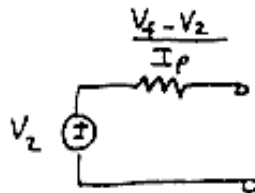


Section 5-6: Norton's Theorem


P5.6-1

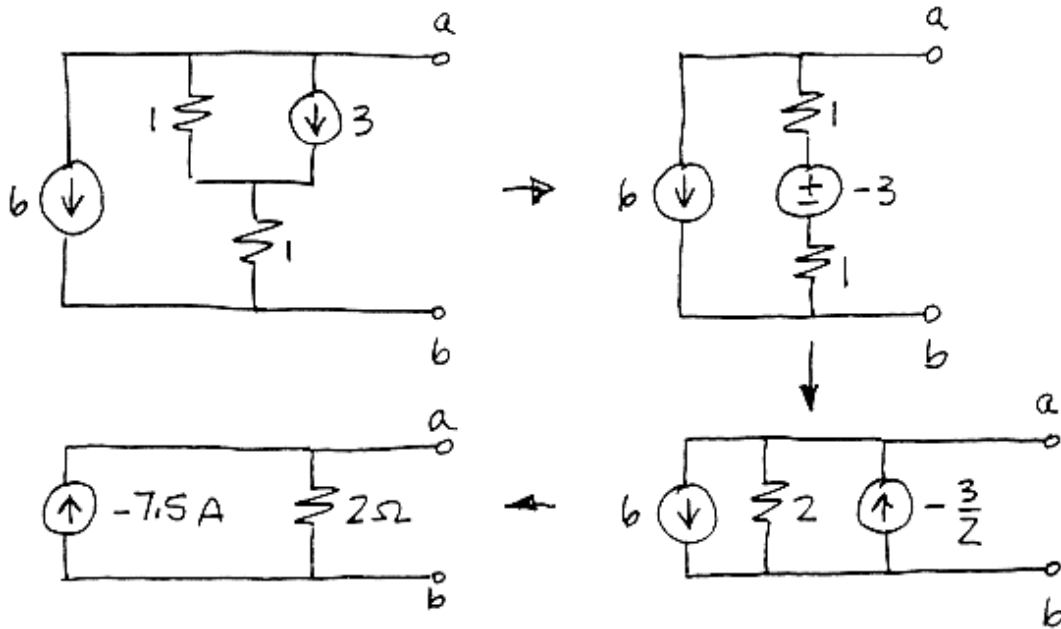

P5.6-2

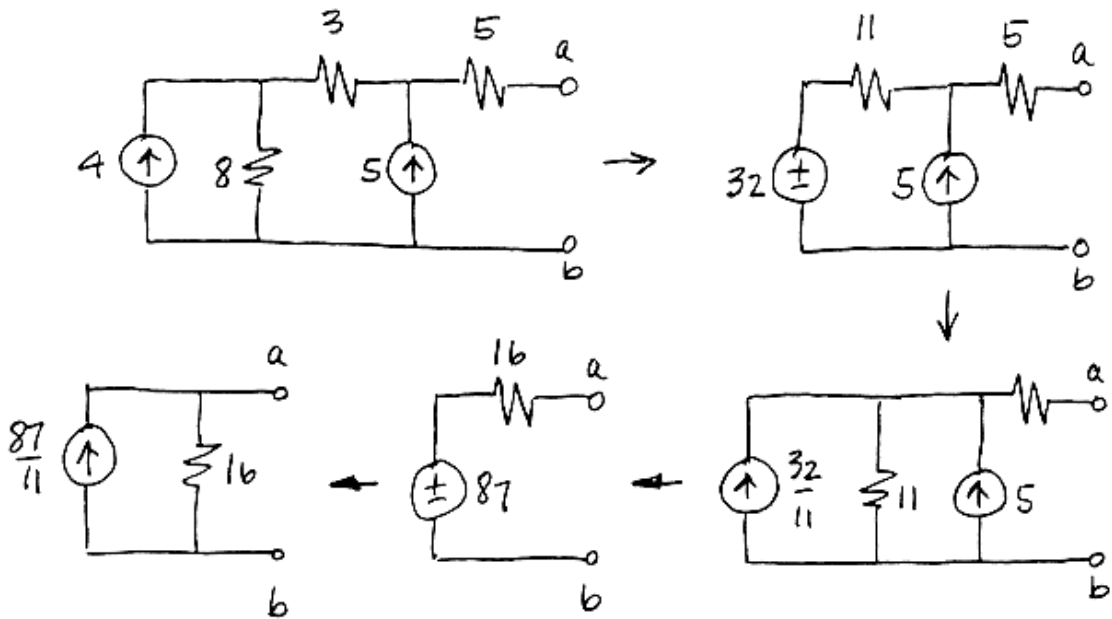

P5.6-3 Find v_{oc}

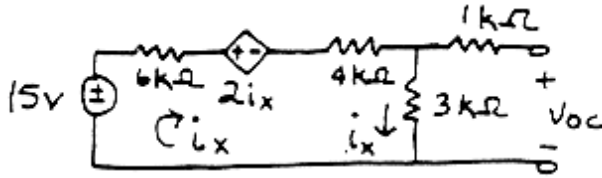


$$\text{KVL a: } -15 + i_x(6+4) + 2i_x + 3i_x = 0$$

$$\Rightarrow i_x = 1\text{mA}$$

$$\therefore v_{oc} = 3i_x = 3\text{V}$$

Find i_{sc}

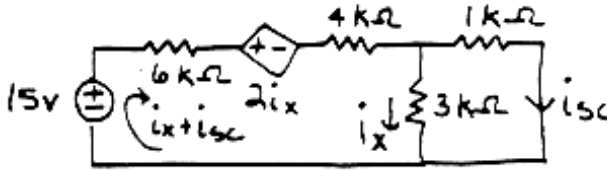

$$\text{KVL a: } -15 + 2i_x + 10(i_x + i_{sc}) + 3i_x = 0$$


$$\Rightarrow -15 + 15i_x + 10i_{sc} = 0 \quad (1)$$

$$\text{KVL a: } -3i_x + i_{sc} = 0 \quad (2)$$

Solving (1) & (2) simultaneously yields: $i_{sc} = 1\text{mA}$


$$\therefore R_T = \frac{v_{oc}}{i_{sc}} = \frac{3}{1} = 3\text{k}\Omega$$

Norton equiv. ckt.

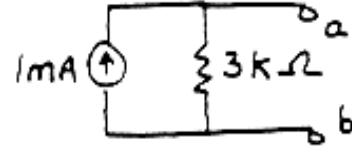

P5.6-4

Find v_{oc}

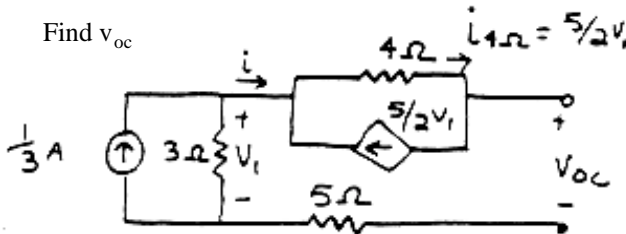


by inspection $i = 0$

$$\text{from left mesh: } v_1 = 3(1/3) = 1\text{V}$$

$$\text{from KVL a: } -v_1 + 4i_{4\Omega} + v_{oc} = 0$$

$$\Rightarrow v_{oc} = v_1 - 4(5/2v_1) = -9\text{V}$$

Find i_{sc}

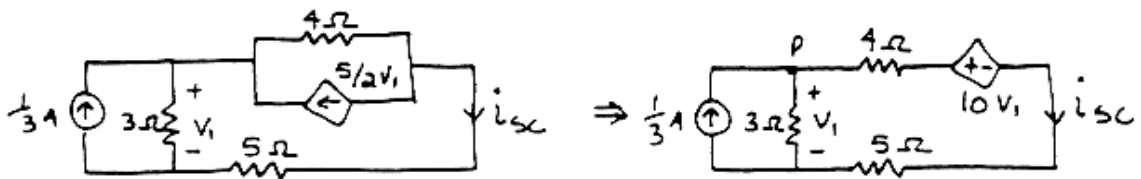


$$\text{from KVL a: } -v_1 + 4i_{sc} + 10v_1 + 5i_{sc} = 0$$

$$\Rightarrow 9v_1 + 9i_{sc} = 0 \quad (1)$$

$$\text{from KCL at P: } -\frac{1}{3} + \frac{v_1}{3} + i_{sc} = 0 \quad (2) \quad (1) \text{ \& \ } (2) \text{ yields}$$



$$\therefore R_T = \frac{v_{oc}}{i_{sc}} = \frac{-9}{1/2} = -18\Omega$$

$$\text{Norton equiv. ckt: } i_{sc} = \frac{1}{2}\text{A}$$

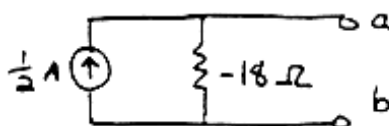

Section 5-7: Maximum Power Transfer


P5.7-1

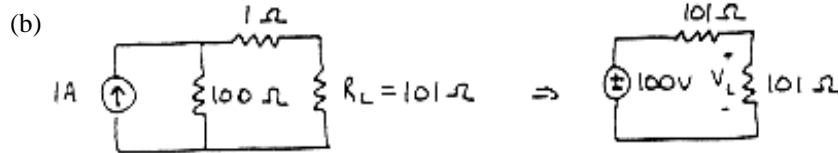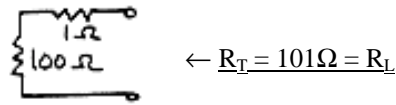

$$P_{\max} = v_L^2 / 101 = (50)^2 / 101 = 24.75 \text{ W}$$

P5.7-2

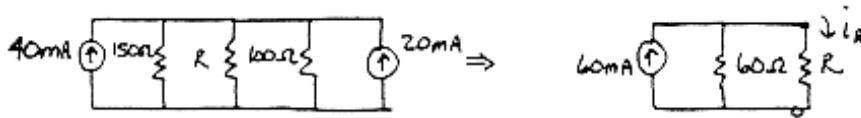
(a) Use source transformations to reduce ckt.



Norton equiv. where $R_T = 60\Omega$ \therefore want $R_L = 60\Omega$

(b) $P_{\max} = i_R^2 (R) = (30)^2 (60) = 54,000 \mu \text{ W} = 54 \text{ mW}$

P5.7-3

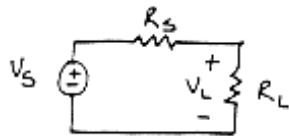


$$V_L = V_S \left[\frac{R_L}{R_S + R_L} \right]$$

$$\therefore P_L = \frac{V_L^2}{R_L} = \frac{V_S^2 R_L}{(R_S + R_L)^2}$$

By inspection, P_L is max when you vary R_S to get the smallest denominator. \therefore set $R_S = 0$

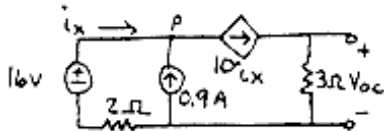
P5.7-4 Find R_T using $R_T = v_{oc} / i_{sc}$. First find v_{oc} :



KCL at P: $-i_x - 0.9 + 10i_x = 0 \Rightarrow i_x = 0.1 \text{ A}$

$\therefore v_{oc} = 3(10i_x) = 3 \text{ V}$

Find i_{sc}

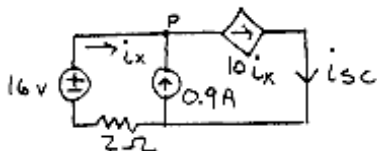


KCL at P: $-i_x - 0.9 + 10i_x = 0 \Rightarrow i_x = 0.1 \text{ A}$


$\therefore i_{sc} = 10i_x = 1 \text{ A}$

$P_{L_{\max}} = \frac{V_L^2}{R_L} = \frac{(1.5)^2}{3} = 0.75 \text{ W}$

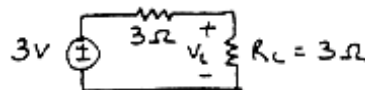$\therefore R_T = v_{oc} / i_{sc} = 3\Omega = R_L$ for max power



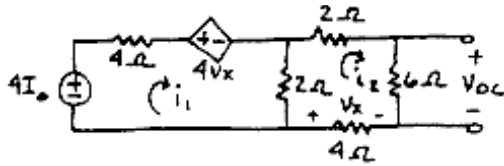P5.7-5 (a) For max power $R_L = R_T$. First find v_{oc} :



$$\text{KVL } a_1: -4I_0 + 4i_1 - 4v_x + 2(i_1 - i_2) = 0$$

$$\Rightarrow 6i_1 - 2i_2 + 4v_x - 4I_0 = 0 \quad (1)$$

$$\text{KVL } a_2: 2i_2 + 6i_2 - v_x + 2(i_2 - i_1) = 0$$


$$\Rightarrow -2i_1 + 10i_2 - v_x = 0 \quad (2)$$

$$\text{also } v_x = 4i_2 \quad (3)$$

$$\text{and } v_{oc} = 6i_2 \quad (4)$$

Solving (1), (2), (3), & (4) yields $v_{oc} = I_0$

Find i_{sc}

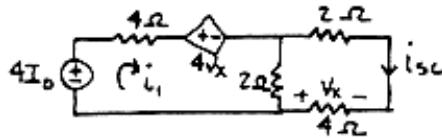

$$\text{KVL } a_1: -4I_0 + 4i_1 + 4v_x + 2(i_1 - i_{sc}) = 0$$

$$\Rightarrow 6i_1 - 2i_{sc} + 4v_x - 4I_0 = 0 \quad (1)$$

$$\text{KVL } a_x: 2i_{sc} + 4i_{sc} + 2(i_{sc} - i_1) = 0$$

$$\Rightarrow -2i_1 + 8i_{sc} = 0 \quad (2)$$

$$\text{also } v_x = -4i_{sc} \quad (3)$$

Solving (1), (2), & (3) yields $i_{sc} = \frac{2}{3} I_0$ $\therefore R_T = \frac{v_{oc}}{i_{sc}} = \frac{3}{2} \Omega = R_L$


$$(b) P_{L_{max}} = 54 \text{ W} = \frac{(v_{oc}/2)^2}{R_L} = I_0^2/6$$

$$\Rightarrow I_0 = 18 \text{ A}$$

P5.7-6

$$P_{max} = v_T^2/4R_T$$

Find $R_T \Rightarrow$ kill i source

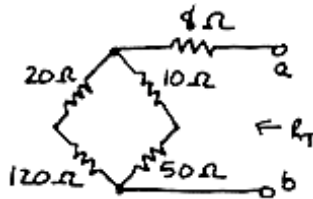

$$R_T = 8 + (20 + 120) \parallel (10 + 50)$$

$$= 50 \Omega$$

find v_{oc} :


$$i_{10\Omega} = \frac{120 + 50}{120 + 50 + 20 + 10} 20 \text{ A}$$

$$= 17 \text{ A}$$

$$\therefore v_{10\Omega} = 10(17) = 170 \text{ V}$$


$$v_{50\Omega} = 50(17 - 20) = -150 \text{ V} \Rightarrow v_{oc} = v_{10\Omega} + v_{50\Omega} = 170 - 150 = 20 \text{ V}$$
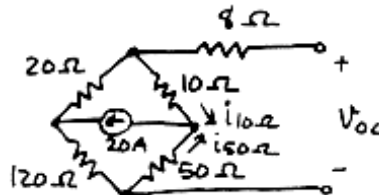
$$\therefore P_{max} = \frac{20^2}{4} = 2 \text{ W}$$



PSpice Problems

SP 5-1

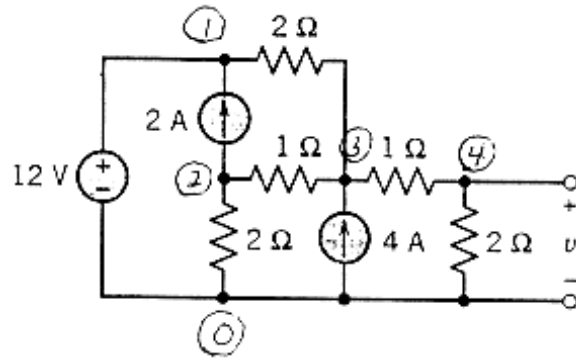


Input file

```
V1 1 0 dc 12
I2 2 1 dc 2
R3 2 0 2
R4 2 3 1
R5 1 3 2
R6 3 4 1
I7 0 3 dc 4
R8 4 0 2
.dc V1 12 12 1
.print dc V(4)
.END
```

result $V(4) = v = 4.952E+00V$

SP 5-2

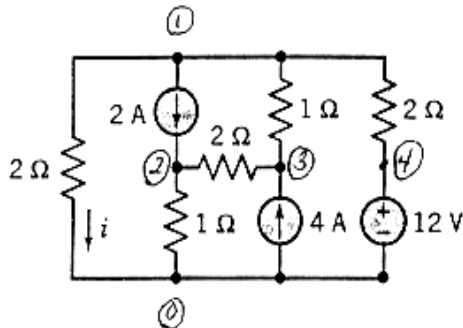


Input file

```
R1 1 0 2
I2 1 2 dc 2
R3 2 0 1
R4 2 3 2
R5 1 3 1
I6 0 3 dc 4
R7 1 4 2
V8 4 0 dc 12
.dc V8 12 12 1
.print dc I(R1)
.END
```

result

$i = I(R1) = 3.000E+00A$

SP 5-3

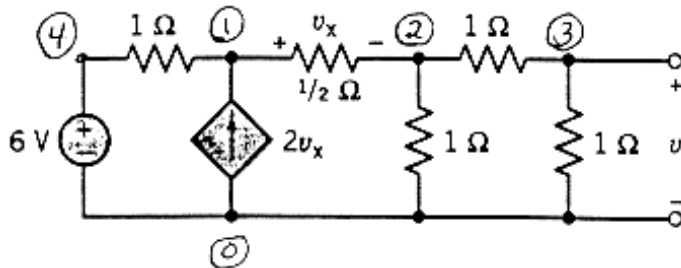


result

$v = v(3) = 1.714E+00V$

Input file

```
V1 4 0 dc 6
G2 0 1 1 2 2
R3 1 2 500m
R4 1 4 1
R5 2 0 1
R6 2 3 1
R7 3 0 1
.dc V1 6 6 1
.print dc V(3)
.END
```



SP 5.4

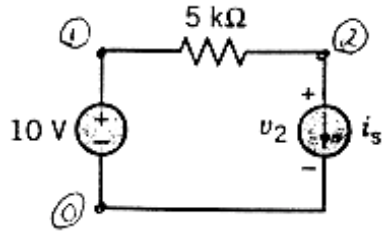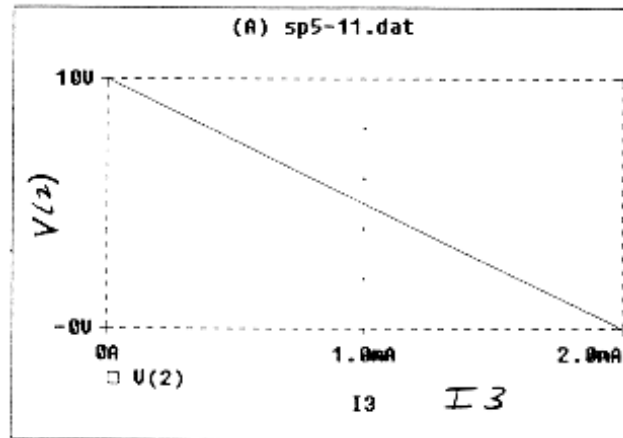


Input file

```
V1 1 0 dc 10
R2 1 2 5k
I3 2 0 dc 1m
.dc I3 0 2e-3 0.2e-3
.probe V(2)
.end
```

Probe result



SP 5-5

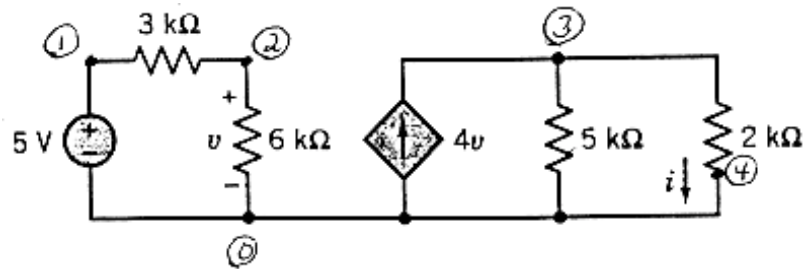


Input file

```
V1 1 0 dc 5
R1 1 2 3k
R2 2 0 6k
G4 0 3 2 0 4
R3 3 0 5k
R4 3 0 2k
.dc V1 5 5 1
.print dc I(R4)
.end
```

result $i = I(R4) = 9.524E+00A$

SP 5-6

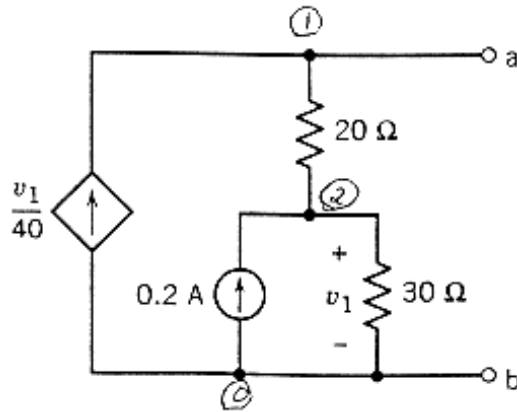

Input file

```
G1 0 1 2 0 25m
R2 1 2 2 20
I3 0 2 dc 0.2
R4 2 0 30
.tf V(1) I3
.end
```

result

answer: $V_1 = V_{oc} = V_T = 36V$

| NODE | VOLTAGE | NODE | VOLTAGE |
|-------|----------------|-------|---------|
| (1) | <u>36.0000</u> | (2) | 24.0000 |

$R_{TH} = \text{OUTPUT RESISTANCE AT } V(1) = 2.000E+02\Omega$



Verification Problems

VP 5-1 Evaluating data

Case 1: $R_L = 0\Omega$; $i = I_{sc} = 97.2\text{mA} = \frac{V_{oc}}{R_t}$ (1)

Case 2: $R_L = 500\Omega$; $i = 43.8\text{mA} = \frac{V_{oc}}{R_t + 500}$ (2)

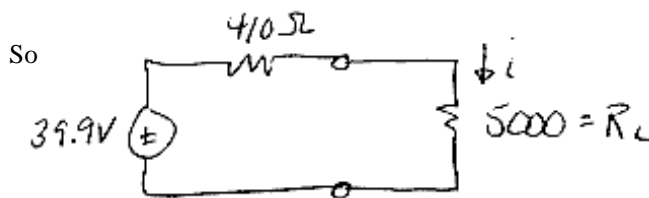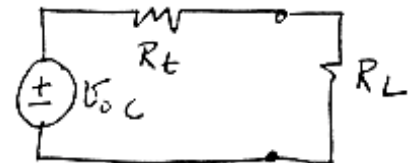Solving 1+2 yields $R_t = 410\Omega$, $v_{oc} = 39.9\text{V}$



When $R_L = 5000\Omega$

$$i = \frac{V_{oc}}{R_t + R_L} = 7.37\text{mA}$$

not 16.5mA as recorded \therefore the data is inconsistent.


VP 5-2

$V_{oc} = 12 \text{ V}$ (line 1 of the table)

$I_{sc} = 3 \text{ mA}$ (line 3 of the table)

so

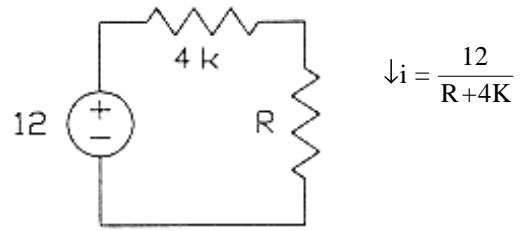$R_{TH} = V_{oc} / I_{sc} = 4 \text{ k}\Omega$



Hence the circuit can be simplified as shown above right. (Check:

$$\frac{12}{10\text{k}\Omega + 4\text{k}\Omega} = 0.857 \text{ mA}$$


as shown in line 2 of the table.)

When $i = 1 \text{ mA}$ is required

$$1\text{mA} = \frac{12}{R + 4\text{k}\Omega} \Rightarrow R = \frac{12}{1\text{mA}} - 4\text{k}\Omega = 8\text{k}\Omega$$

I agree with my lab partner's claim that $R = 8000$ causes $i = 1 \text{ mA}$.

VP 5-3

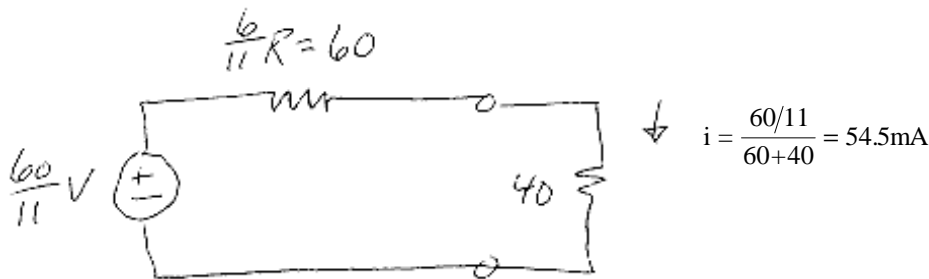

The measurement is consistent with the prelab calculations.

Design Problems

DP 5-1 The equation of representing the straight line in Figure DP 5-1b is $v = -R_t i + v_{oc}$. That is, the slope of the line is equal to -1 times the Thevenin resistance and the "v - intercept" is equal to the open circuit voltage. Therefore: $R_t = -\frac{0-5}{0.008-0} = 625 \Omega$ and $v_{oc} = 5 \text{ V}$.

Try $R_1 = R_2 = 1 \text{ k}\Omega$. ($R_1 \parallel R_2$ must be smaller than $R_t = 625 \Omega$.) Then

$$5 = \frac{R_2}{R_1 + R_2} v_s = \frac{1}{2} v_s \Rightarrow v_s = 10 \text{ V}$$

and

$$625 = R_3 + \frac{R_1 R_2}{R_1 + R_2} = R_3 + 500 \Rightarrow R_3 = 125 \Omega$$

Now v_s , R_1 , R_2 and R_3 have all been specified so the design is complete.

DP 5-2 The equation of representing the straight line in Figure DP 5-2b is $v = -R_t i + v_{oc}$. That is, the slope of the line is equal to -1 times the Thevenin resistance and the "v - intercept" is equal to the open circuit voltage. Therefore: $R_t = -\frac{0-(-3)}{-0.006-0} = 500 \Omega$ and $v_{oc} = -3 \text{ V}$.

From the circuit we calculate

$$R_t = \frac{R_3 (R_1 + R_2)}{R_1 + R_2 + R_3} \text{ and } v_{oc} = -\frac{R_1 R_3}{R_1 + R_2 + R_3} i_s$$

so

$$500 \Omega = \frac{R_3 (R_1 + R_2)}{R_1 + R_2 + R_3} \text{ and } 3 \text{ V} = -\frac{R_1 R_3}{R_1 + R_2 + R_3} i_s$$

Try $R_3 = 1 \text{ k}\Omega$ and $R_1 + R_2 = 1 \text{ k}\Omega$. Then $R_t = 500 \Omega$ and

$$-3 = -\frac{1000 R_1}{2000} i_s = \frac{R_1}{2} i_s \Rightarrow 6 = R_1 i_s$$

This equation can be satisfied by taking $R_1 = 600 \Omega$ and $i_s = 10 \text{ mA}$. Finally, $R_2 = 1 \text{ k}\Omega - 400 \Omega = 600 \Omega$. Now i_s , R_1 , R_2 and R_3 have all been specified so the design is complete.

DP 5-3 The slope of the graph is positive so the Thevenin resistance is negative. This would require

$$R_3 + \frac{R_1 R_2}{R_1 + R_2} < 0, \text{ which is not possible since } R_1, R_2 \text{ and } R_3 \text{ will all be non-negative.}$$

Is it not possible to specify values of v_s , R_1 , R_2 and R_3 that cause the current i and the voltage v in Figure DP 5-3a to satisfy the relationship described by the graph in Figure DP 5-3b.

DP 5-4 The equation of representing the straight line in Figure DP 5-4b is $v = -R_t i + v_{oc}$. That is, the slope of the line is equal to the Thevenin impedance and the "v - intercept" is equal to the open circuit voltage. Therefore: $R_t = -\frac{-5-0}{0-0.008} = -625 \Omega$ and $v_{oc} = -5$ V.

$$R_t = -\frac{-5-0}{0-0.008} = -625 \Omega \text{ and } v_{oc} = -5 \text{ V.}$$

The open circuit voltage, v_{oc} , the short circuit current, i_{sc} , and the Thevenin resistance, R_t , of this circuit are given by

$$v_{oc} = \frac{R_2 (d+1)}{R_1 + (d+1)R_2} v_s,$$

$$i_{sc} = \frac{(d+1)}{R_1} v_s$$

and

$$R_t = \frac{R_1 R_2}{R_1 + (d+1)R_2}$$

Let $R_1 = R_2 = 1 \text{ k}\Omega$. Then

$$-625 \Omega = R_t = \frac{1000}{d+2} \Rightarrow d = \frac{1000}{-625} - 2 = -3.6 \text{ A/A}$$


and

$$-5 = \frac{(d+1)v_s}{d+2} \Rightarrow v_s = \frac{-3.6+2}{-3.6+1}(-5) = -3.077 \text{ V}$$

Now v_s , R_1 , R_2 and d have all been specified so the design is complete.

DP 5-5 a) Find Thev. equiv.

v_{oc} :

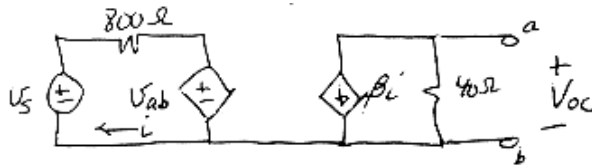


$$-v_s + 800 i + v_{ab} = 0 \quad (1)$$

$$v_{ab} = v_{oc} \quad (2)$$

$$v_{oc} = -(\beta i) \quad (3)$$

Solving eqs. (1) - (3) yields $v_{oc} = v_s / \left(1 - \frac{20}{\beta}\right)$

I_{sc} :

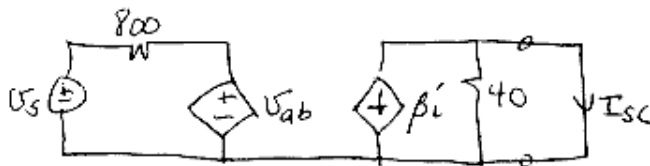


$$I_{sc} = -\beta i \quad (4)$$

$$v_{ab} = 0 \quad (5)$$

$$v_s = 800i \quad (6)$$

Solving eqs. (4) - (6) yields $I_{sc} = -\beta v_s / 800$

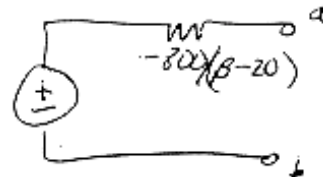so $R_t = \frac{v_{oc}}{I_{sc}} = \frac{-800}{\beta - 20}$ and Thev. equiv. $\frac{v_s}{\left(1 - \frac{20}{\beta}\right)}$



b) $R_t = R_L = 400 = \frac{-800}{\beta - 20} \Rightarrow \underline{\beta = 18}$

c) Max power to R_L , largest v_{oc} , largest v_s , smallest R_t

$$P_L = \frac{(V_L)^2}{R_L} \quad (7)$$

$$\text{and } V_L = \frac{400}{R_{total}} v_{oc} \quad (8)$$

with

$$R_{total} = \frac{-800}{\beta - 20} + 400 \text{ (a) yields } \underline{\beta = \pm 18}$$

d) delivering large amounts of power could melt antenna.

DP 5-6 Max power to load : $R_L = R_t = 50\Omega$

But split power equally ($R_{L1} = R_{L2} = 50\Omega$)



$$\frac{(R+50)(R+50)}{R+50+R+50} = 50 \Rightarrow \text{yields } \underline{R=50\Omega}$$