

## Chapter 5 Circuit Theorems

### Exercises

**Ex 5.3-1**  $R = 10 \Omega$  and  $i_s = 1.2 \text{ A}$ .

**Ex 5.3-2**  $R = 10 \Omega$  and  $i_s = -1.2 \text{ A}$ .

**Ex 5.3-3**  $R = 8 \Omega$  and  $v_s = 24 \text{ V}$ .





**Ex 5.3-4**  $R = 8 \Omega$  and  $v_s = -24 \text{ V}$ .

**Ex 5.4-1**  $v_m = \frac{20}{10+20+20}15 + 20\left(-\frac{10}{10+(20+20)}2\right) = 6 + 20\left(-\frac{2}{5}\right) = -2 \text{ V}$


**Ex 5.4-2**  $i_m = \frac{25}{3+2} - \frac{3}{2+3}5 = 5 - 3 = 2 \text{ A}$

**Ex 5.4-3**  $v_m = 3\left(\frac{3}{3+(3+3)}5\right) - \frac{3}{3+(3+3)}18 = 5 - 6 = -1 \text{ A}$

**Ex 5.5-1**

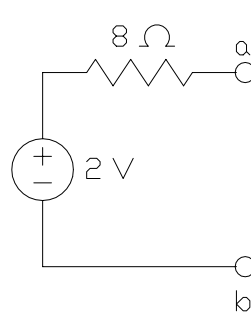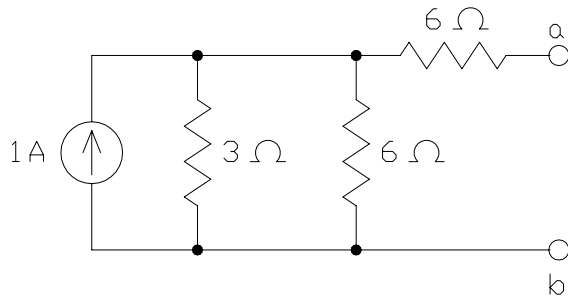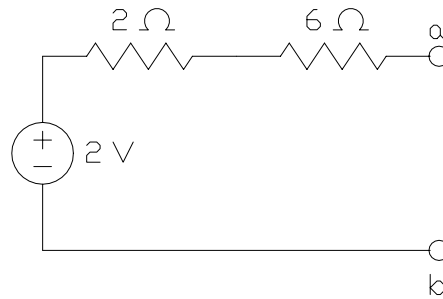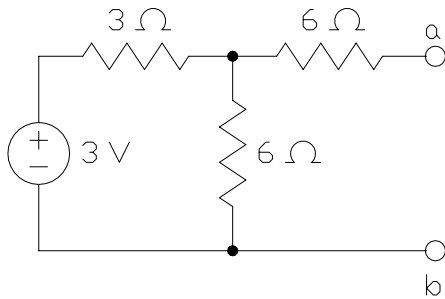


**Ex 5.5-2**

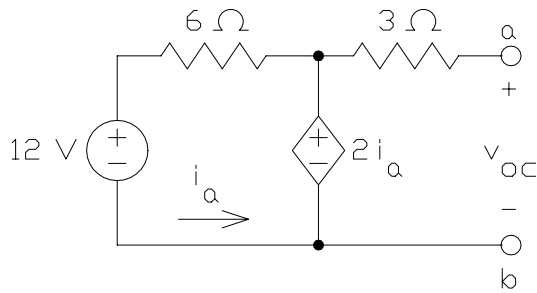

$$i_a = \frac{2i_a - 12}{6} \Rightarrow i_a = -3 \text{ A}$$

$$v_{oc} = 2i_a = -6 \text{ V}$$

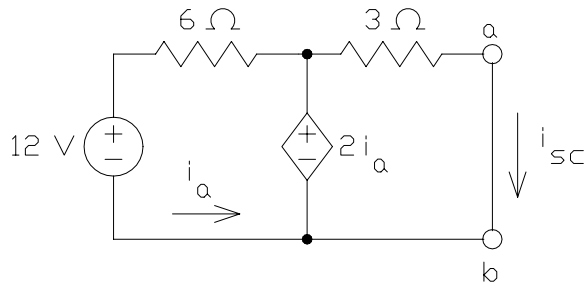


$$12 + 6i_a = 2i_a \Rightarrow i_a = -3 \text{ A}$$

$$3i_{sc} = 2i_a \Rightarrow i_{sc} = \frac{2}{3}(-3) = -2 \text{ A}$$

$$R_t = \frac{-6}{-2} = 3 \Omega$$

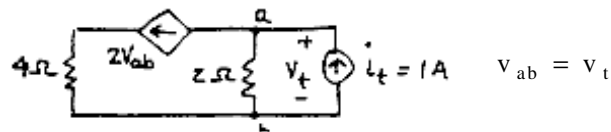
**Ex. 5.5-3** No independent sources  $\therefore v_{oc} = i_{sc} = 0 \Rightarrow$  apply 1A test source







$$\text{KCL at a: } 2v_t + \frac{v_t}{2} - 1 = 0 \Rightarrow v_t = \frac{2}{5} \text{ V}$$

$$\therefore R_T = \frac{v_t}{i_t} = \frac{2}{5} \Omega$$


Thev. equiv. ckt

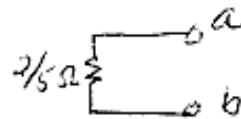


**Ex 5.6-1**

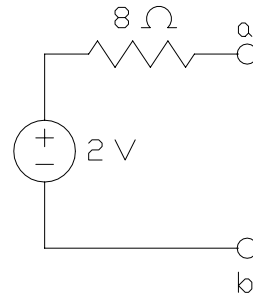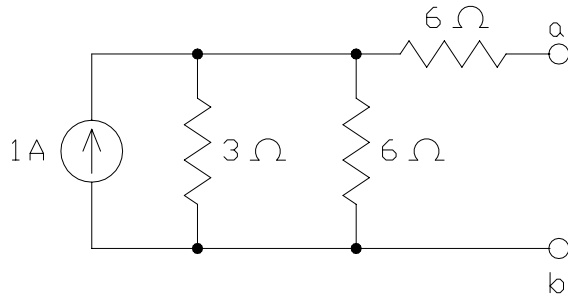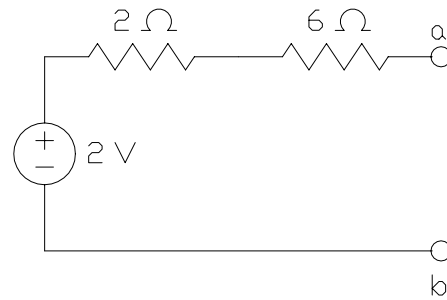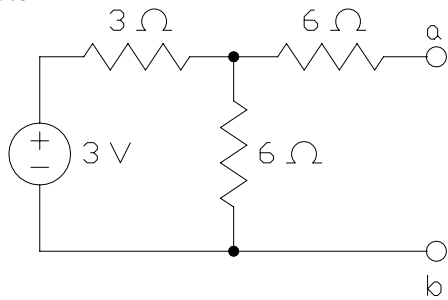

Finally:

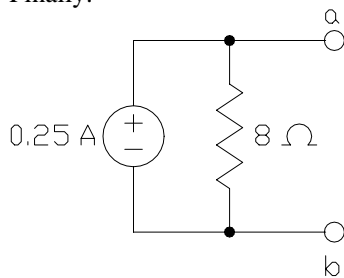


**Ex 5.6-2**

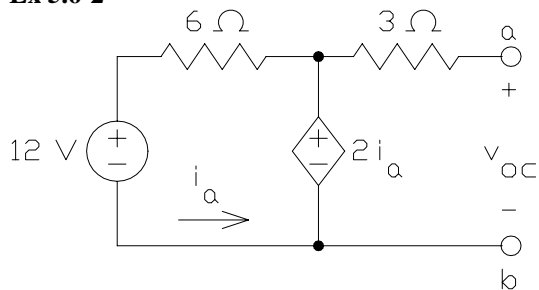

$$i_a = \frac{2i_a - 12}{6} \Rightarrow i_a = -3 \text{ A}$$

$$v_{oc} = 2i_a = -6 \text{ V}$$

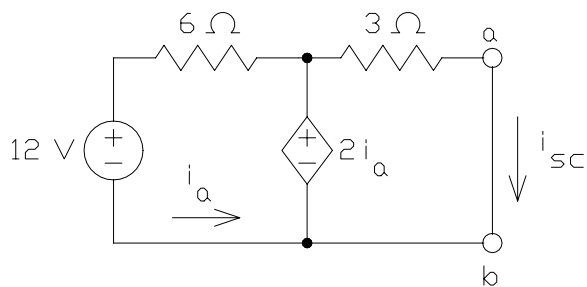


$$12 + 6i_a = 2i_a \Rightarrow i_a = -3 \text{ A}$$

$$3i_{sc} = 2i_a \Rightarrow i_{sc} = \frac{2}{3}(-3) = -2 \text{ A}$$

$$R_t = \frac{-6}{-2} = 3 \Omega$$


Ex. 5.6-3

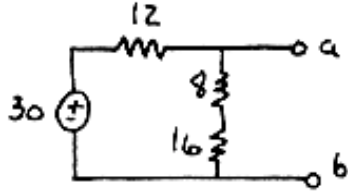

$$R_T = \frac{12 \times 24}{12 + 24} = \frac{12 \times 24}{36} = 8\Omega$$


$$v_{oc} = \frac{24}{12 + 24} \cdot 30 = 20V$$

So we have

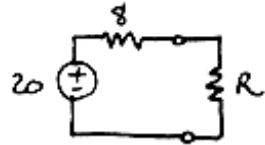

$$i = \frac{20}{8 + R} \text{ A}$$


Ex. 5.7-1 Find  $v_{oc}$

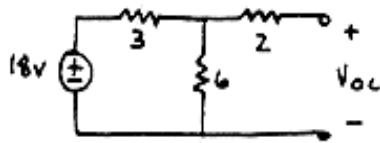


From voltage divider

$$v_{oc} = 18V \left( \frac{6}{6+3} \right) = 12V$$

Find  $R_T$  (short 18V source)

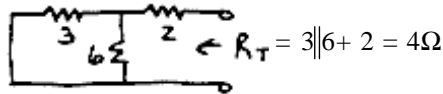


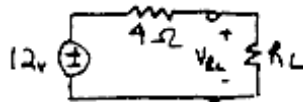$\therefore$  Thev. equiv. ckt  $\Rightarrow$



For max power to  $R_L \Rightarrow R_L = R_T = 4\Omega \quad \therefore P_{\max_{R_L}} = \frac{(v_{RL})^2}{R_L} = \frac{(6)^2}{4} = 9W$

Ex. 5.7-2 Find  $i_{sc}$

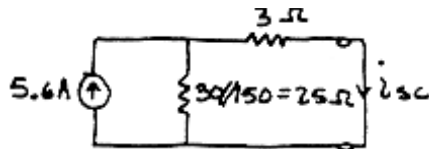

From current divider

$$i_{sc} = 5.6A \left( \frac{25}{25+3} \right)$$


$$i_{sc} = 5A$$

Find  $R_T$  (open 5.6A source)




$$R_T = 25 + 3 = 28\Omega$$

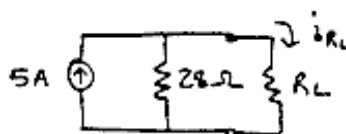$\therefore$  Norton equiv. ckt  $\Rightarrow$



For max power  $R_L = R_T = 28\Omega \quad \therefore P_{L_{\max}} = (i_{R_L})^2 R_L = (5/2)^2 (28) = 175W$

Ex. 5.7-3

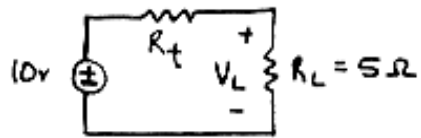


$$P_{L_{\max}} = \frac{(V_{L_{\max}})^2}{R_L} = \frac{\left[10V \left(\frac{5}{5+R_t}\right)\right]^2}{R_L}$$

Now for  $V_L$  to be maximized,  $R_t$  must be minimized

∴ choose  $R_t = 1\Omega$

$$\therefore P_{L_{\max}} = \frac{\left[10\left(\frac{5}{6}\right)\right]^2}{5} = \underline{13.9W}$$

Ex. 5.7-4

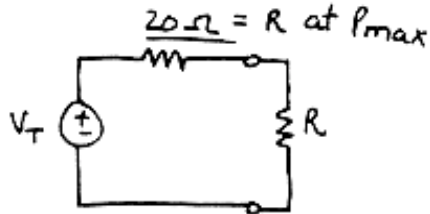

$$P_{\max} = 5 = \left(\frac{V_T}{40}\right)^2 20 = \frac{V_T^2}{80}$$







$$V_T = \sqrt{400} = \underline{20V}$$

PROBLEMS

Section 5-3: Source Transformations

P5.3-1


(a)

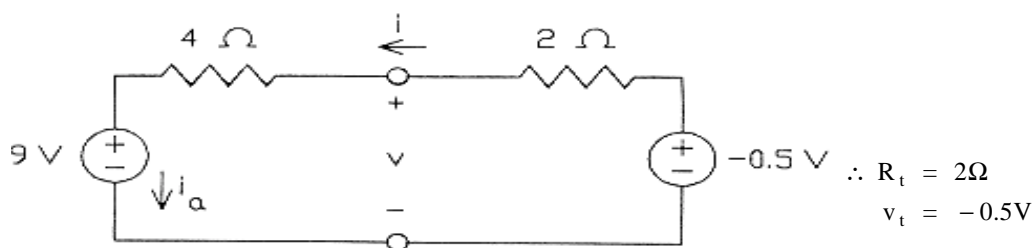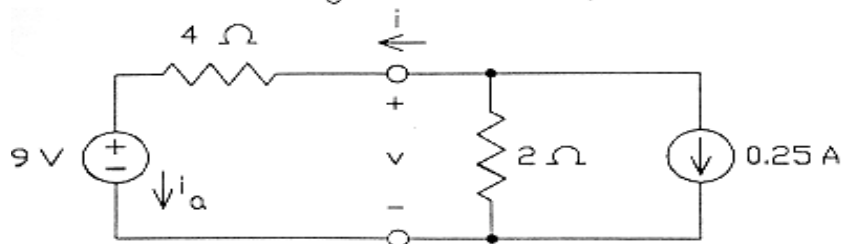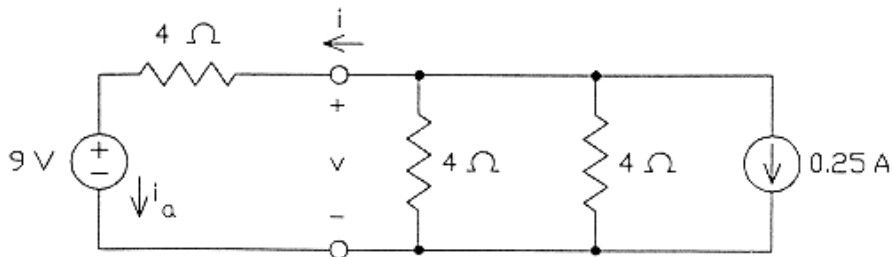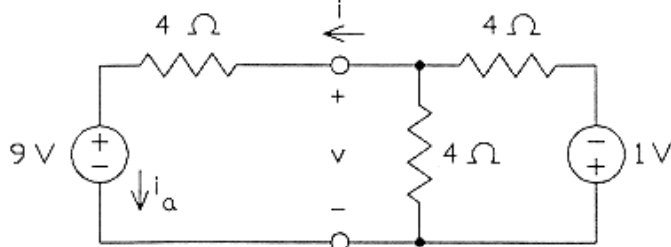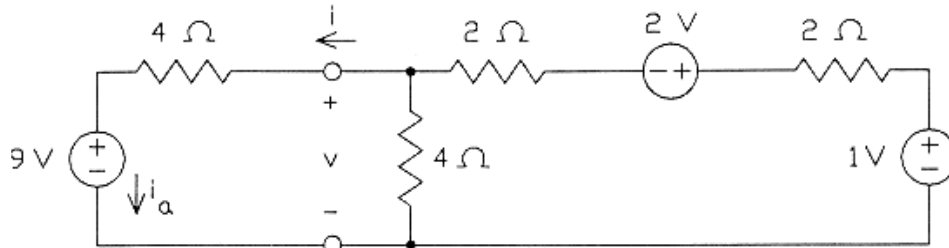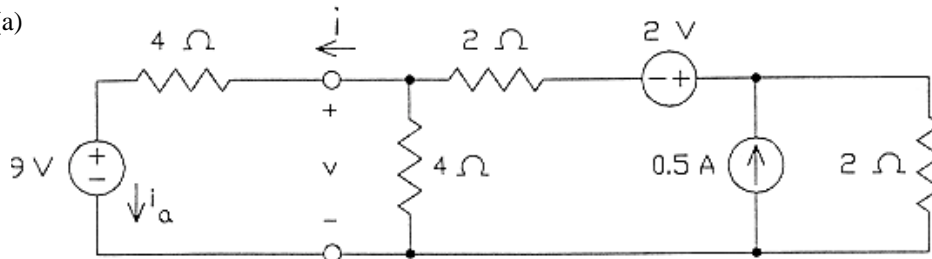

(b)  $-9 - 4i - 2i + (-0.5) = 0$   
 $i = \frac{-9 + (-0.5)}{4 + 2} = -1.58A$   
 $v = 9 + 4i = 9 + 4(-1.58) = 2.67V$


(c)  $i_a = i = -1.58A$

**P5.3-2**

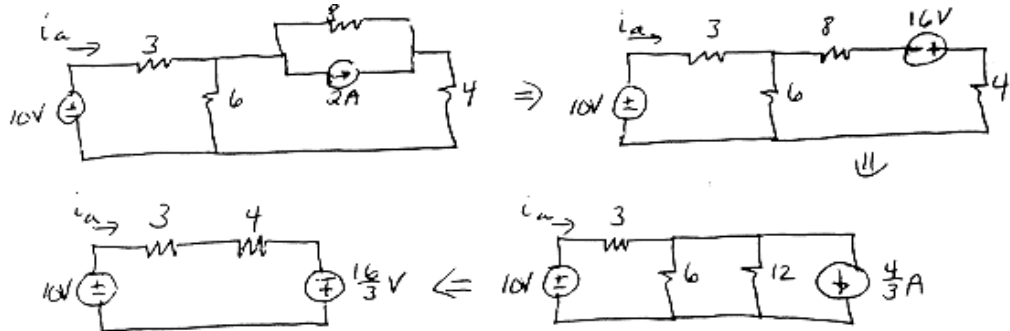


KVL:  $-10 + 3i_a + 4i_a - \frac{16}{3} = 0 \quad \therefore i_a = 2.19A$

**P5.3-3**

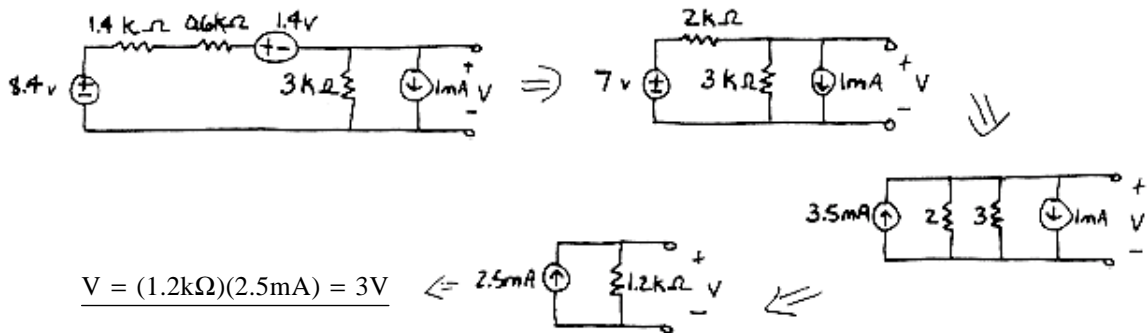


$V = (1.2k\Omega)(2.5mA) = 3V$

**P5.3-4**

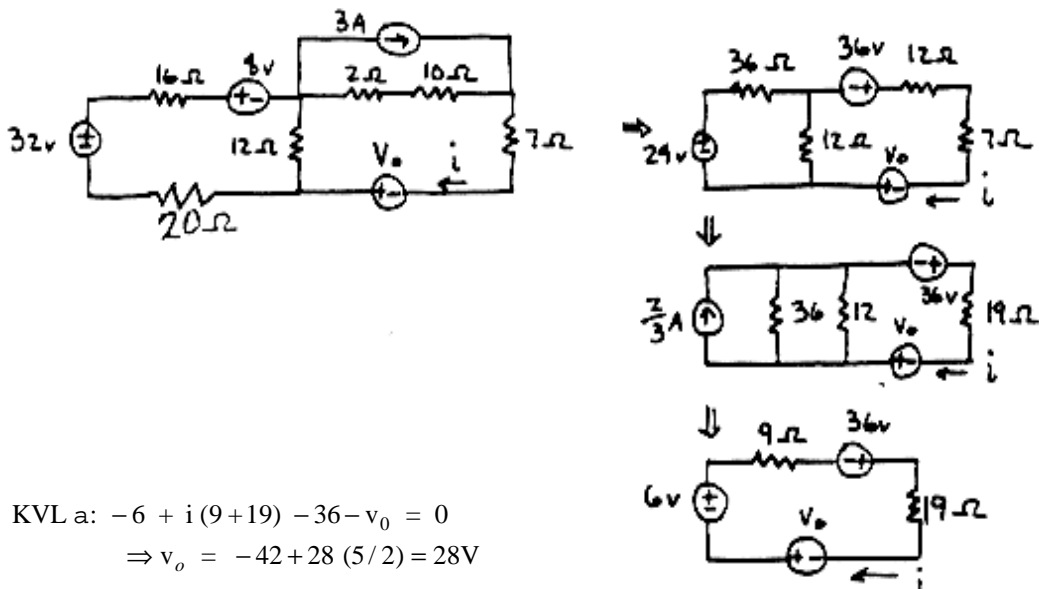

KVL a:  $-6 + i(9 + 19) - 36 - v_o = 0$   
 $\Rightarrow v_o = -42 + 28(5/2) = 28V$


P5.3-5

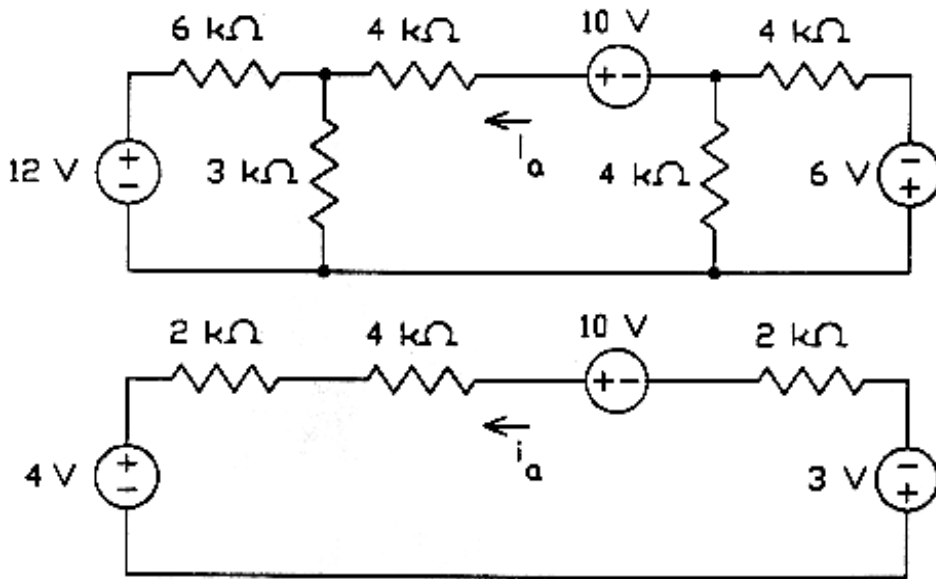

$$-4 - 2000i_a - 4000i_a + 10 - 2000i_a - 3 = 0$$

$$\therefore i_a = 375 \mu\text{A}$$

P5.3-6

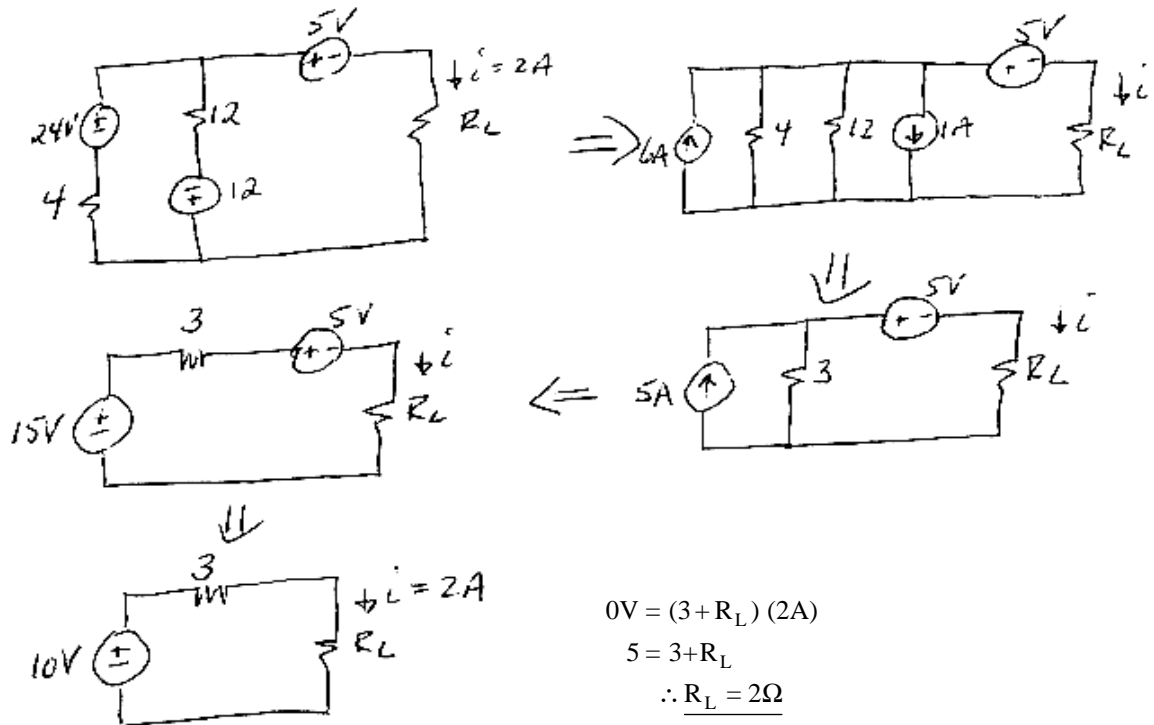

$$0V = (3 + R_L)(2A)$$




$$5 = 3 + R_L$$

$$\therefore R_L = 2\Omega$$



Section 5-4 Superposition

P5.4-1

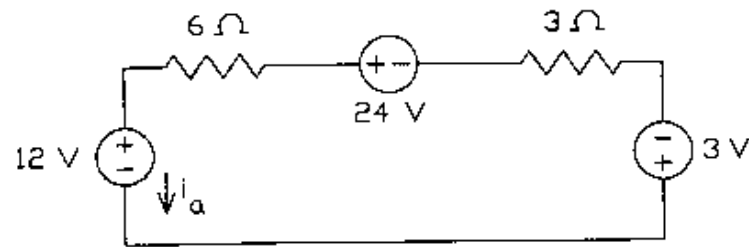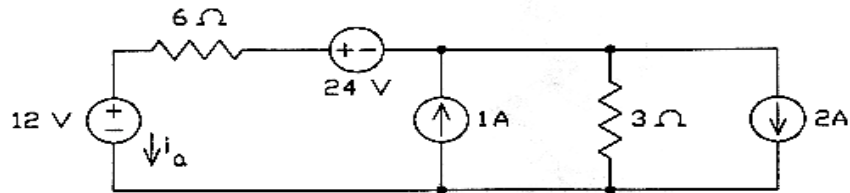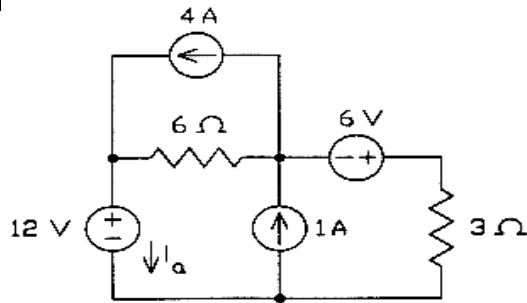

$$-12 - 6i_a + 24 - 3i_a - 3 = 0 \Rightarrow i_a = 1 \text{ A}$$


P5.4-2 Consider 6A source only (open 9A source)



From current divider:

$$v_1 / 20 = 6 \left[ \frac{15}{15 + 30} \right] \Rightarrow \underline{v_1 = 40V}$$

Consider 9A source only (open 6A source)

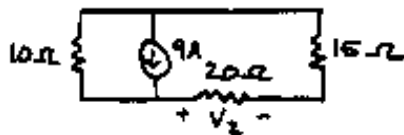


Current divider

$$v_2 / 20 = 9 \left[ \frac{10}{10 + 35} \right] \Rightarrow \underline{v_2 = 40V}$$

$$\therefore v = v_1 + v_2 = 40 + 40 = \underline{80V}$$

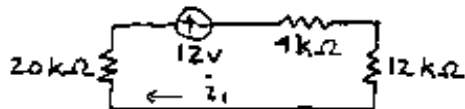
P5.4-3 Consider 12V source only (open both current sources)



$$\text{KVL a: } 20i_1 + 12 + 4i_1 + 12i_1 = 0$$

$$\Rightarrow \underline{i_1 = -1/3 \text{ mA}}$$

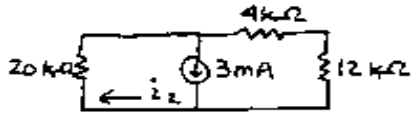
Consider 12mA source only (short 12V and open 6mA sources)



From current divider

$$i_2 = 3 \left[ \frac{16}{16+20} \right] = \underline{\underline{\frac{4}{3} \text{ mA}}}$$

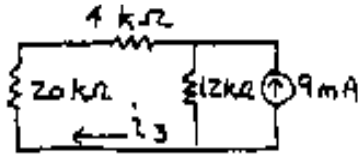Consider 9mA source only (short 12V and open 12mA sources)




From current divider

$$i_3 = -9 \left[ \frac{12}{24+12} \right] = \underline{\underline{-3 \text{ mA}}}$$

$$\therefore i = i_1 + i_2 + i_3 = -1/3 + 4/3 - 3 = \underline{\underline{-2 \text{ mA}}}$$

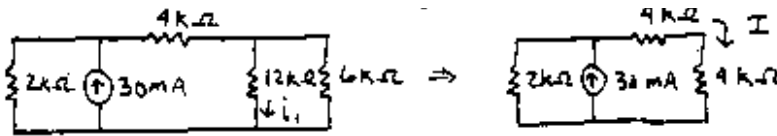P5.4-4 Consider 30mA source only (open 15mA and short 60V sources)




$$\text{Current divider} \Rightarrow I = 30 \left( \frac{2}{2+8} \right) = 6 \text{ mA}$$

$$\therefore i_1 = I \left( \frac{6}{6+12} \right) = \underline{\underline{2 \text{ mA}}}$$

Consider 15mA source only (open 30mA source and short 60V source)

Continued

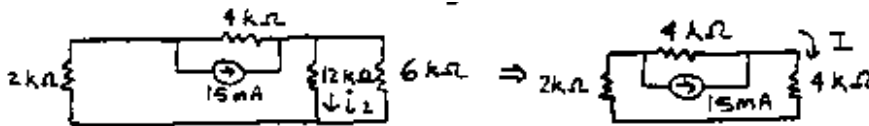

$$\text{Current divider} \Rightarrow I = 15 \left( \frac{4}{4+6} \right) = 6 \text{ mA}$$

$$\therefore i_2 = I \left( \frac{6}{6+12} \right) = \underline{\underline{2 \text{ mA}}}$$

Consider 15V source only (open both current sources)




From current divider

$$i_3 = -2.5 \left( \frac{6/6}{6/6+12} \right) = -10 \left( \frac{3}{3+12} \right) = \underline{\underline{-5 \text{ mA}}}$$

$$\therefore i = i_1 + i_2 + i_3 = 2 + 2 - 5 = \underline{\underline{3.5 \text{ mA}}}$$

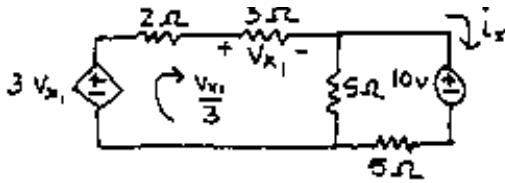P5.4-5 Consider 10V source only (open 4A source)



KVL 1st mesh a:


$$-3v_{x_1} + 5\left(\frac{v_{x_1}}{3}\right) + 5\left(\frac{v_{x_1}}{3} - i_x\right) = 0$$

$$\Rightarrow \underline{v_{x_1} = 15i_x} \quad (1)$$

KVL 2nd mesh a:  $5(i_x - v_{x_1}/3) + 10 + 5i_x = 0$  (2)

Solving (1) and (2) simultaneously  $\Rightarrow \underline{v_{x_1} = 10V}$

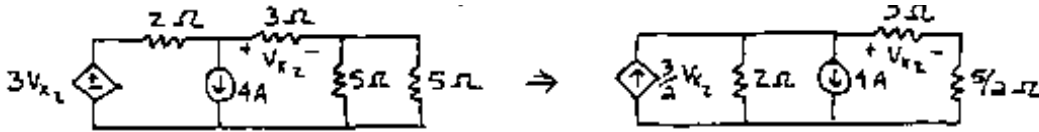
Consider 4A source only (short 10V source)



Using current divider:  $\frac{v_{x_2}}{3} = (3/2v_{x_2} - 4)\left(\frac{2}{2+3+5/2}\right) \Rightarrow \underline{v_{x_2} = 16V}$

$\therefore \underline{v_x = v_{x_1} + v_{x_2} = 10 + 16 = 26V}$

P5.4-6

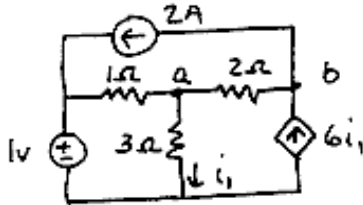

KCL at b:  $i + 6i_1 - 2 = 0$


$\Rightarrow i_1 = 1/3 - 1/6 i$  (1)

KVL around left lower mesh:

$1(i_1 + i) + 3i_1 - 1 = 0$  (2)

Plugging (1) into (2)  $\Rightarrow \underline{i = -1A}$


P5.4-7 Consider  $v_2$  source only

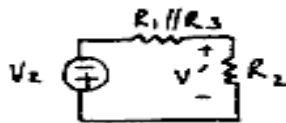

Voltage divider:  $v' = -v_2 \left[ \frac{R_2}{R_2 + R_1 \parallel R_3} \right]$

$v' = -v_2 \left[ \frac{R_2(R_1 + R_3)}{R_1 R_2 + R_1 R_3 + R_2 R_3} \right]$

Consider  $v_1$  source only

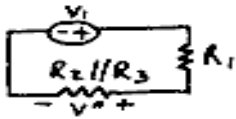

Voltage divider  $v'' = v_1 \left[ \frac{R_2 \parallel R_3}{R_2 \parallel R_3 + R_1} \right]$

$v'' = v_1 \left[ \frac{R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} \right]$

Consider  $i_1$  source only




$v''' = 0$  since no current flows through  $R_2, R_3$  and  $R_1$





$\therefore \underline{v = v' + v'' + v'''} = \frac{v_1 R_2 R_3 - v_2 (R_2 (R_1 + R_3))}{R_1 R_2 + R_1 R_3 + R_2 R_3}$

Section 5-5: Thévenin's Theorem


Ex 5.5-1

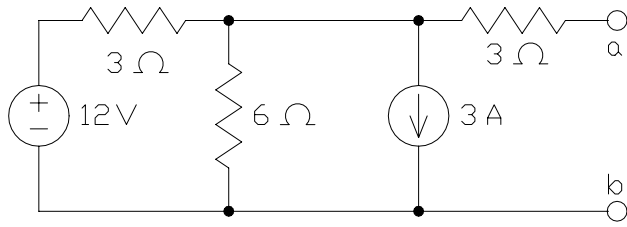


(a)

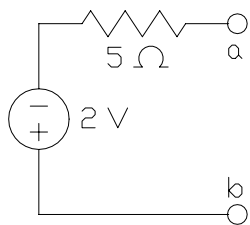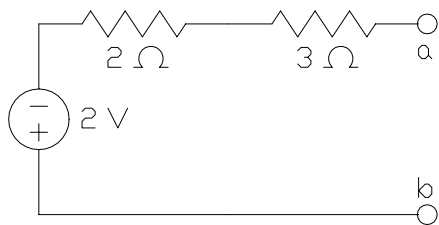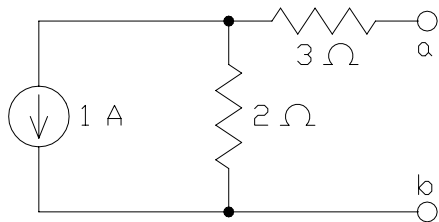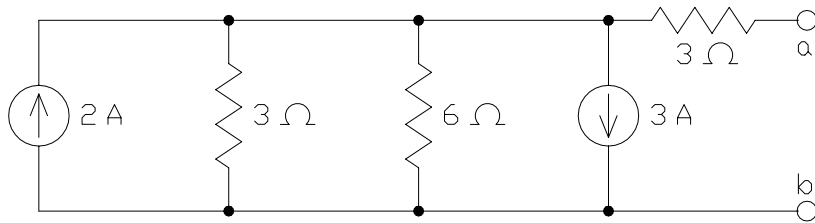


P5.5-2 Use source transformations

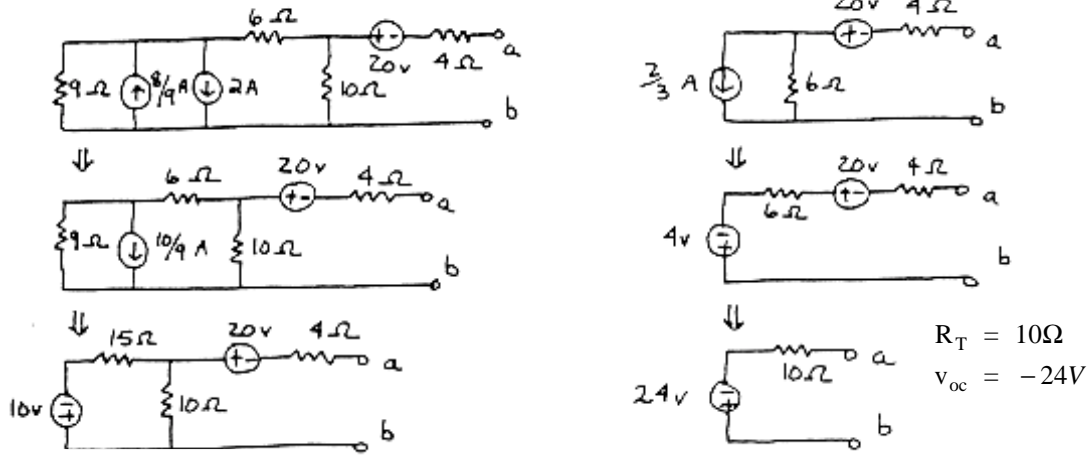

P5.5-3 Use source transformations

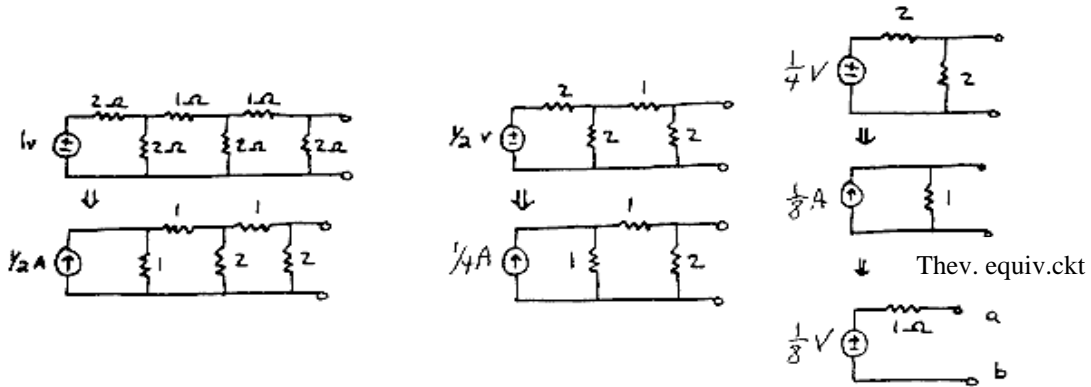


P5.5-4 Find  $R_T$ :

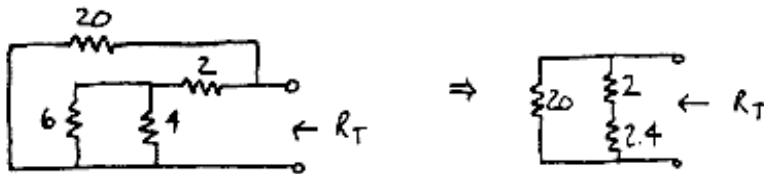

$$R_T = \frac{20(2+2.4)}{20+2+2.4} = \underline{3.61\Omega}$$

Continued

Find  $v_T$ :

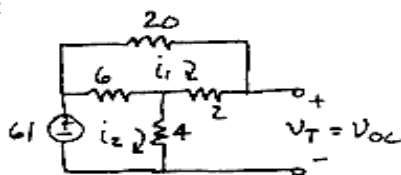

$$v_T = 2i_1 + 4i_2$$


$$\text{mesh } i_1: 28i_1 - 6i_2 = 0 \quad (1)$$

$$\text{mesh } i_2: -6i_1 + 10i_2 - 61 = 0 \quad (2)$$

Solving (1) & (2) yields:  $i_1 = 1.5A$ ,  $i_2 = 7A$

$$\therefore v_T = 3 + 28 = \underline{31V}$$


P5.5-5 Find  $v_{oc}$

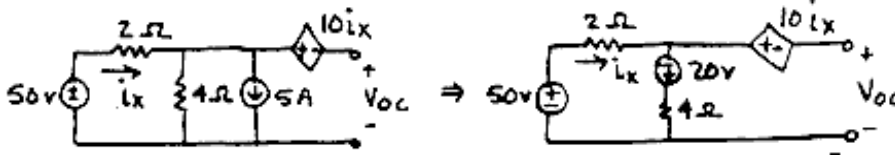

KVL around 1st mesh a:  $-50 + 2i_x - 20 + 4i_x = 0 \Rightarrow i_x = 70/6 \text{ A}$

KVL around 2nd mesh a:  $-4i_x + 20 + 10i_x + v_{oc} = 0$   
 $\Rightarrow v_{oc} = -90 \text{ V}$

Find  $i_{sc}$

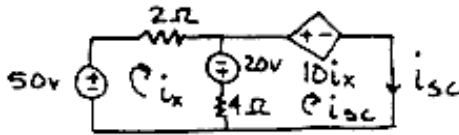


KVL  $i_x$  mesh a:  $-50 + 2i_x - 20 + 4(i_x - i_{sc}) = 0$   
 $6i_x - 4i_{sc} - 70 = 0$  (1)

KVL  $i_{sc}$  mesh a:  $4(i_{sc} - i_x) + 20 + 10i_x = 0$   
 $6i_x + 4i_{sc} + 20 = 0$  (2)


Solving (1) and (2) simultaneously  $\Rightarrow i_{sc} = -45/4 \text{ A}$

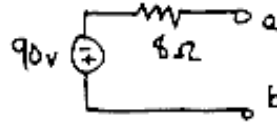$\therefore R_T = \frac{v_{oc}}{i_{sc}} = 8\Omega$  Thev. equiv.ckt :



P5.5-6

For  $v_{oc}$ :

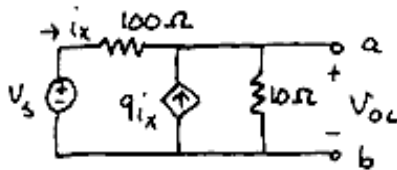


$i_x = \frac{v_s - v_{oc}}{100}$

KCL at terminal a:

$\frac{1}{100}(v_{oc} - v_s) - 9\left[\frac{1}{100}(v_s - v_{oc})\right] + \frac{1}{10}v_{oc} = 0$   
 $\Rightarrow v_{oc} = \frac{1}{2}v_s$

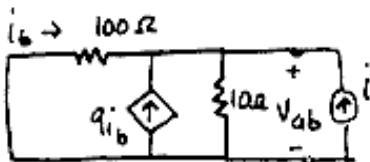Use current source at a-b to find  $R_T$ :




$i_b = -\frac{v_{ab}}{100}$


KCL:  $\frac{1}{100}v_{ab} - 9\left[\frac{1}{100}(-v_{ab})\right] + \frac{1}{10}v_{ab} - i = 0$

$\Rightarrow i = \frac{1}{5}v_{ab} \therefore R_T = \frac{v_{ab}}{i} = 5\Omega$

So Thev. equiv.

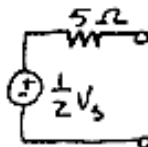


P5.5-7

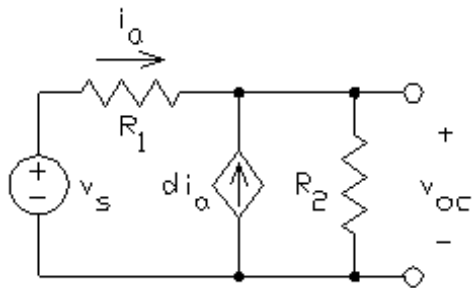

$$v_s + R_1 i_a + (d+1)R_2 i_a = 0$$


$$i_a = \frac{v_s}{R_1 + (d+1)R_2}$$
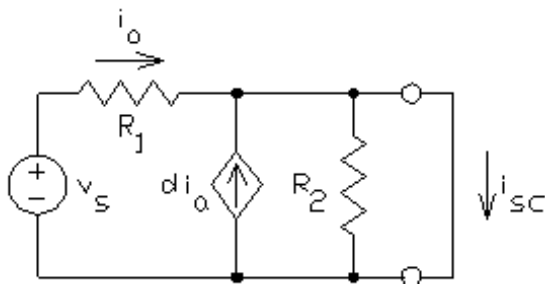
$$v_{oc} = \frac{(d+1)R_2 v_s}{R_1 + (d+1)R_2}$$



$$i_a = \frac{v_s}{R_1}$$
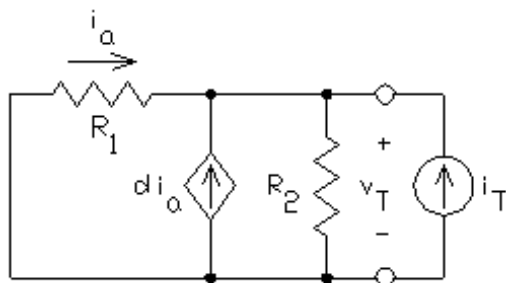
$$i_{sc} = (d+1)i_a = \frac{(d+1)v_s}{R_1}$$



$$-i_a - d i_a + \frac{v_T}{R_2} - i_T = 0$$

$$R_1 i_a = -v_T$$

$$i_T = (d+1) \frac{v_T}{R_1} + \frac{v_T}{R_2} = \frac{R_2(d+1) + R_1}{R_1 R_2} v_T$$

$$R_t = \frac{v_T}{i_T} = \frac{R_1 R_2}{R_1 + (d+1)R_2}$$

(b) Let  $R_1 = R_2 = 1 \text{ k}\Omega$ . Then


$$625 \Omega = R_t = \frac{1000}{d+2} \Rightarrow d = \frac{1000}{625} - 2 = -0.4 \text{ A/A}$$

and

$$5 = \frac{(d+1)v_s}{d+2} \Rightarrow v_s = \frac{-0.4+2}{-0.4+1} 5 = 13.33 \text{ V}$$

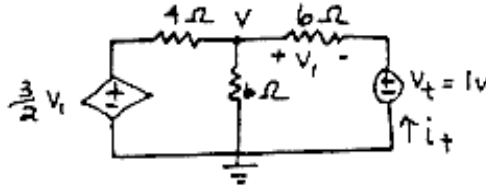**P5.5-8**

Since no independent sources  $v_{oc} = i_{sc} = 0 \therefore$  apply test source




$$V = v_1 + v_t$$

KCL at V:  $\frac{(V - \frac{3}{2}v_1)}{4} + \frac{V}{6} + \frac{v_1}{6} = 0$  & with  $V = v_1 + 1$  so  $v_1 = -2A$

now  $i_t = -\frac{v_1}{6} = \frac{1}{3}A \therefore R_T = \frac{v_t}{i_t} = \frac{1}{\frac{1}{3}} = 3\Omega$

**P5.5-9**

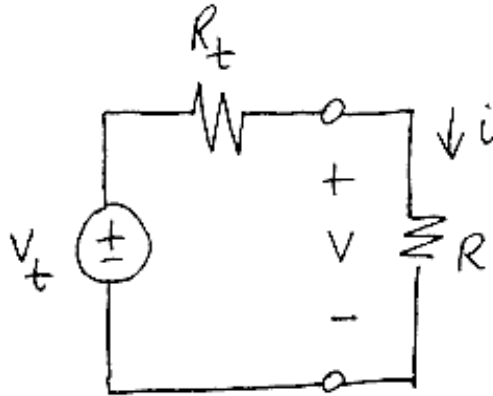

$$V = \frac{R}{R+R_t} v_t$$


$$6 = \frac{2000}{2000+R_t} v_t \quad (\text{line 1})$$

$$2 = \frac{4000}{4000+R_t} v_t \quad (\text{line 2})$$

$$\therefore \underline{v_t = 1.2V} \quad \text{and} \quad \underline{R_t = -1600\Omega}$$

When  $R = 8000$ ,  $V = \frac{8000}{8000-1600} 1.2 = \underline{1.5V}$

**P5.5-10**

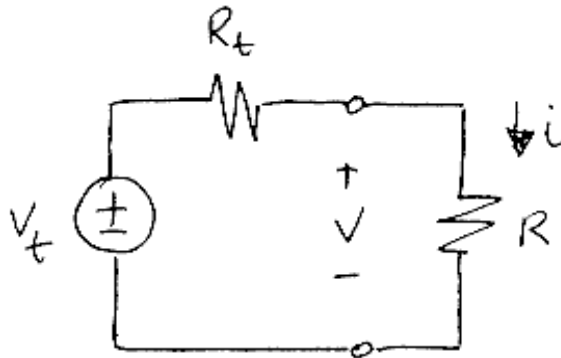

$$i = \frac{v_t}{R+R_t}$$

$$0.004 = \frac{v_t}{2000+R_t} \quad (1)$$

$$0.003 = \frac{v_t}{4000+R_t} \quad (2)$$

so  $\underline{v_t = 24V}$  and  $\underline{R_t = 4000\Omega}$

(a)  $0.002 = \frac{24}{R+4000} \Rightarrow \underline{R = 8000\Omega}$

(b) when  $R = 0$  then  $i = \frac{24}{4000} = \underline{6 \text{ mA}}$




P5.5-11


From the graph, when  $v_{ab} = v = 0 \Rightarrow i = i_{sc} = 20 \text{ mA}$   
 when  $i = 0 \Rightarrow v = v_{oc} = -3 \text{ V}$

$$\therefore R_T = \frac{v_{oc}}{i_{sc}} = \frac{-3 \text{ V}}{20 \text{ mA}} = -15 \text{ k}\Omega = -150 \Omega$$

Thev. equiv. ckt  $\Rightarrow$

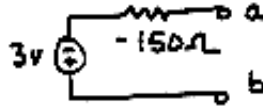


P5.5-12

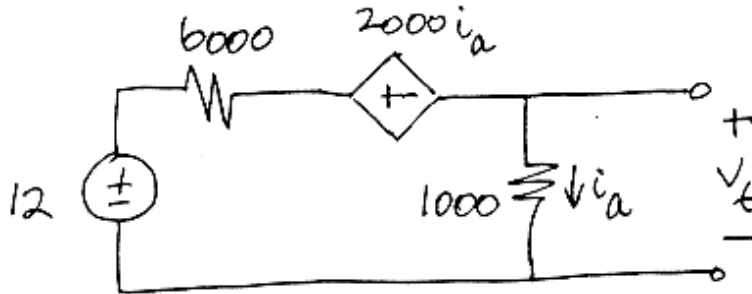

$$-12 + 6000i_a + 2000i_a + 1000i_a = 0$$

$$i_a = 4/3000 \text{ A}$$

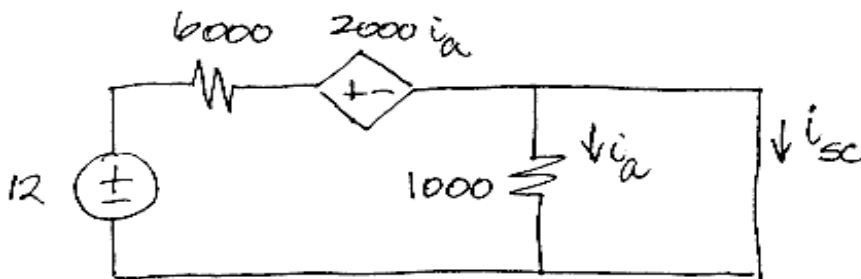
$$v_t = 1000 i_a = \frac{4}{3} \text{ V}$$



$$i_a = \frac{0}{1000} = 0$$

$$-12 + 6000i_{sc} = 0 \Rightarrow i_{sc} = 2 \text{ mA}$$
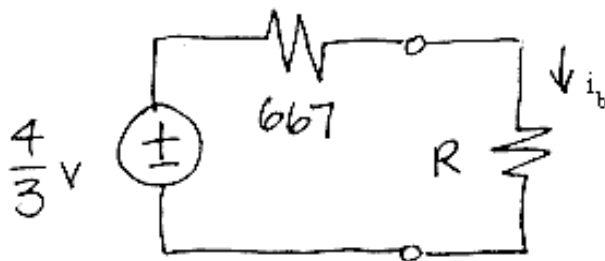
$$R_t = \frac{v_t}{i_{sc}} = \frac{\frac{4}{3}}{.002} = 667 \Omega$$




$$i_b = \frac{\frac{4}{3}}{667 + R}$$

$$\therefore i_b = 0.002 \text{ requires } R = \frac{\frac{4}{3}}{0.002} - 667 = 0$$

**P5.5-13**

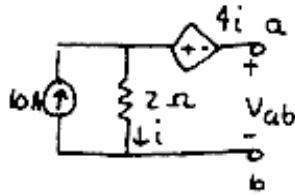
- 1) disconnect  $R_L$   
open circuit a - b



$$\text{KVL: } -v_{ab} - 4i + 2i = 0, \quad i = 10A$$

$$\Rightarrow v_T = v_{ab} = -2i = \underline{-20V}$$

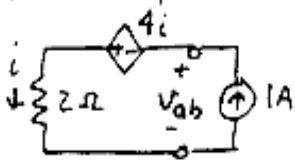- 2) set independent source = 0 and place 1A source at a - b




$$\text{KVL: } -v_{ab} - 4i + 2i = 0, \quad i = 1A$$

$$\Rightarrow v_{ab} = -2A$$

$$\therefore R_T = v_{ab}/1A = \underline{-2\Omega}$$

- 3)

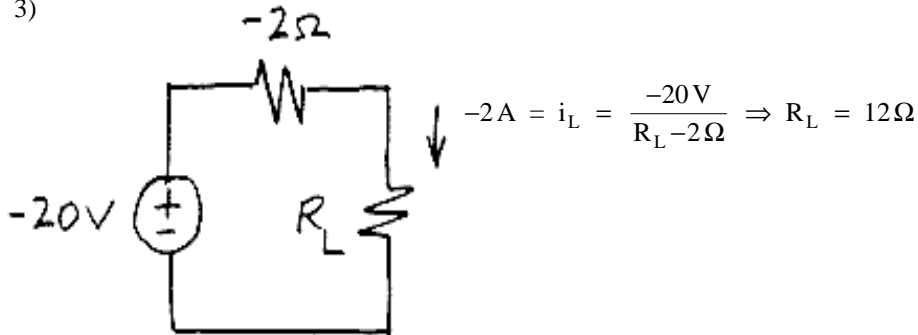


**P5.5-14**


When the terminals of the boxes are open-circuited, no current flows in Box A, but the resistor in Box B dissipates 1 watt. Box B is therefore warmer than Box A. If you short the terminals of each box, the resistor in Box A will draw 1 amp and dissipate 1 watt. The resistor in Box B will be shorted, draw no current, and dissipate no power. Then Box A will warm up and Box B will cool off.

**P5.5-15**

Redraw ckt as:

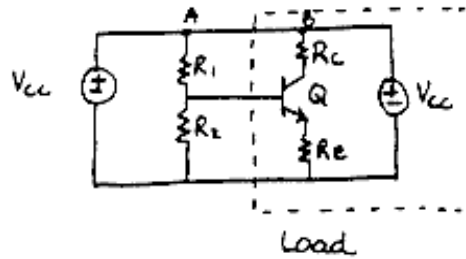

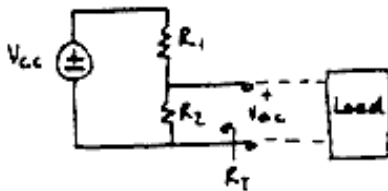
Since points A & B are at same potential, virtually no current exists between A-B  $\therefore$  open ckt.



Find  $R_T$ : kill  $v_{cc}$  source  $\Rightarrow R_T = R_1 \parallel R_2 = R_1 R_2 / (R_1 + R_2)$

Find  $v_{oc}$ : voltage divider  $v_{oc} = v_{cc} \left( \frac{R_2}{R_1 + R_2} \right)$

can replace above ckt as :

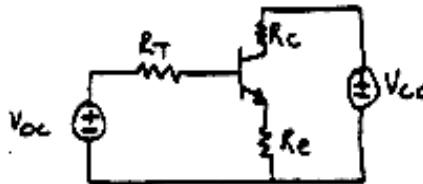


where  $v_{oc} = v_{cc} \left( \frac{R_2}{R_1 + R_2} \right)$

$$R_T = \frac{R_2 R_1}{R_2 + R_1}$$

**P5.5-16**

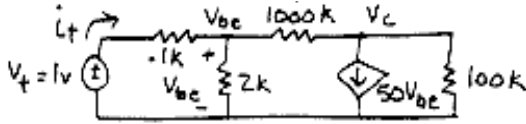(a) Since there are no independent sources, apply test source



$$\begin{aligned} \text{KCL at } v_{be} : & -i_t + \frac{1}{2}v_{be} + (v_{be} - v_c)/1000 = 0 \\ \downarrow & -1000i_t + 501v_{be} - v_c = 0 \end{aligned} \quad (1)$$


$$\begin{aligned} \text{KCL at } v_c : & (v_c - v_{be})/1000 + 50v_{be} + v_c/100 = 0 \\ \downarrow & 11v_c + 50000v_{be} = 0 \end{aligned} \quad (2)$$

$$\text{also } (1 - v_{be})/.1 = i_t \quad (3)$$

Solving (1), (2), & (3) simultaneously yields  $i_t = 3.35 \text{ mA}$

$$\therefore R_{IN} = \frac{v_t}{i_t} = \frac{1 \text{ V}}{3.35 \text{ mA}} = .299 \text{ k}\Omega = 299 \Omega$$

(b) Apply test source

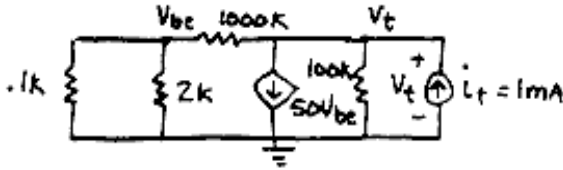

$$\begin{aligned} \text{KCL at } v_{be} : & v_{be}/.1 + v_{be}/2 + (v_{be} - v_t)/1000 = 0 \\ \downarrow & 10501v_{be} = v_t \end{aligned} \quad (1)$$

$$\begin{aligned} \text{KCL at } v_t : & (v_t - v_{be})/1000 + 50v_{be} + v_t/100 - 1 = 0 \\ \downarrow & 11v_t + 49999v_{be} - 1000 = 0 \end{aligned} \quad (2)$$

Solving (1) & (2) yields :  $v_t = 63.5 \text{ V}$

$$\therefore R_{out} = v_t/i_t = 63.5 \text{ V}/1 \text{ mA} = 63.5 \text{ k}\Omega$$

**P5.5-17**


When  $0 < V < V_p$ , it works as a pure resistor

$$\text{so } R = V_p/I_p \quad V_{oc} = 0$$



When  $V_p < V < V_m$ , it is linear but shows negative resistance characteristic

$$\begin{aligned} \Rightarrow V_{oc} &= V_{oc}|_{I=0} = V_1 \\ R &= \frac{V_{oc}}{I_{sc}} = -\frac{V_1}{I_1} \end{aligned}$$

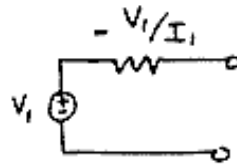

When  $V_m < V < V_f$ , it is linear

$$\begin{aligned} \text{so } V_{oc} &= V_{oc}|_{I=0} = V_2 \\ R &= \frac{V_{oc}}{I_{sc}} = \frac{V_f - V_2}{I_p} \end{aligned}$$

