
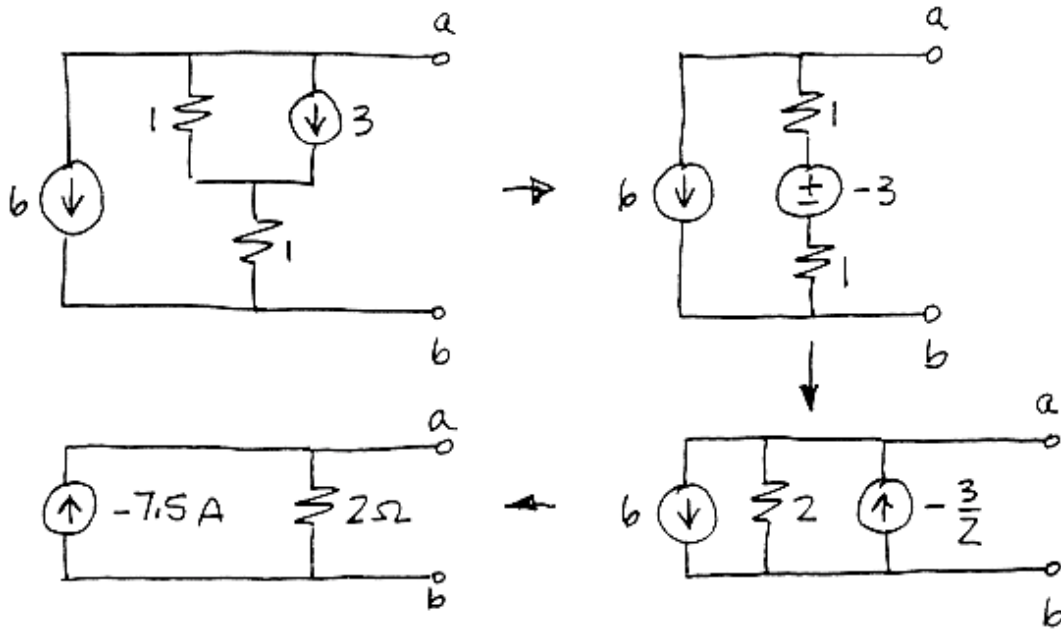


Section 5-6: Norton's Theorem


P5.6-1

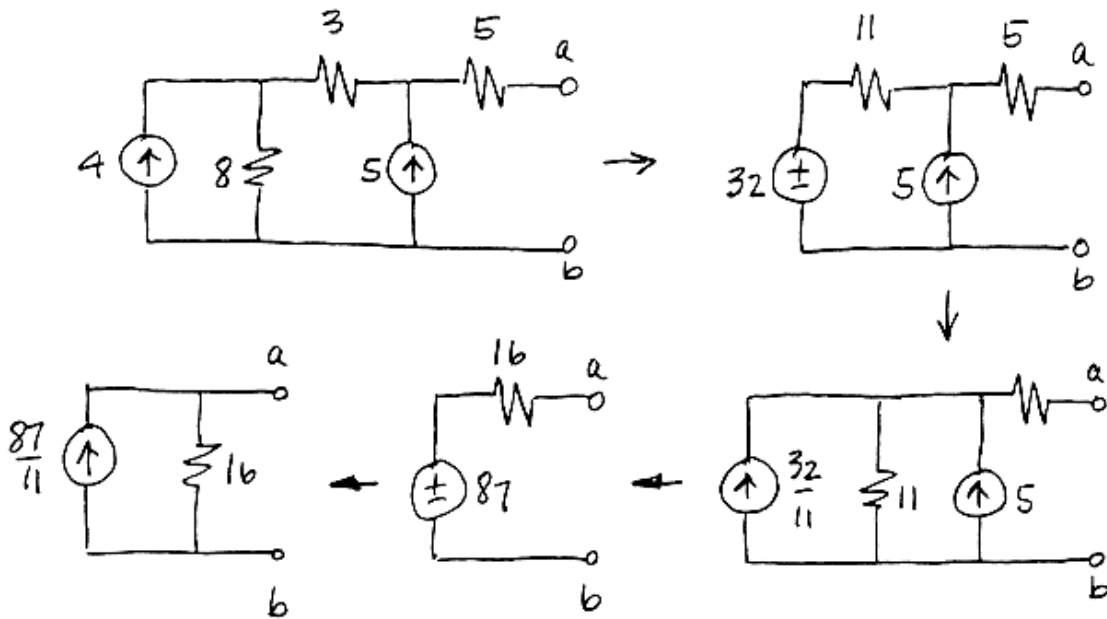

P5.6-2



P5.6-3 Find v_{oc}

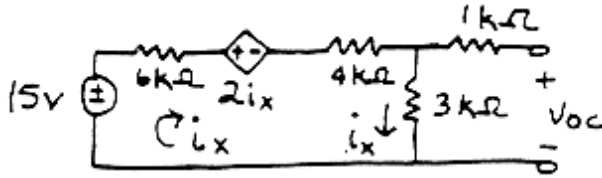


$$\text{KVL a: } -15 + i_x(6+4) + 2i_x + 3i_x = 0$$

$$\Rightarrow i_x = 1\text{mA}$$

$$\therefore v_{oc} = 3i_x = 3\text{V}$$

Find i_{sc}

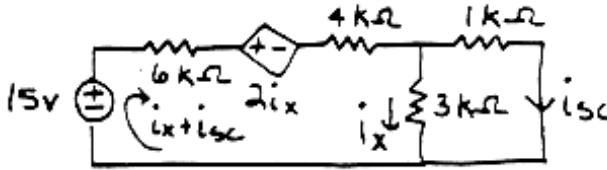

$$\text{KVL a: } -15 + 2i_x + 10(i_x + i_{sc}) + 3i_x = 0$$


$$\Rightarrow -15 + 15i_x + 10i_{sc} = 0 \quad (1)$$

$$\text{KVL a: } -3i_x + i_{sc} = 0 \quad (2)$$

Solving (1) & (2) simultaneously yields: $i_{sc} = 1\text{mA}$


$$\therefore R_T = \frac{v_{oc}}{i_{sc}} = \frac{3}{1} = 3\text{k}\Omega$$

Norton equiv. ckt.

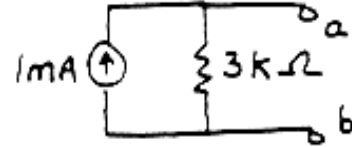

P5.6-4

Find v_{oc}

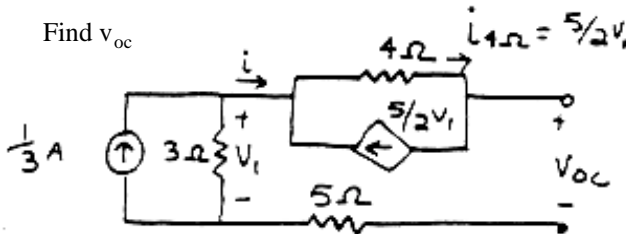


by inspection $i = 0$

$$\text{from left mesh: } v_1 = 3(1/3) = 1\text{V}$$

$$\text{from KVL a: } -v_1 + 4i_{4\Omega} + v_{oc} = 0$$

$$\Rightarrow v_{oc} = v_1 - 4(5/2v_1) = -9\text{V}$$

Find i_{sc}

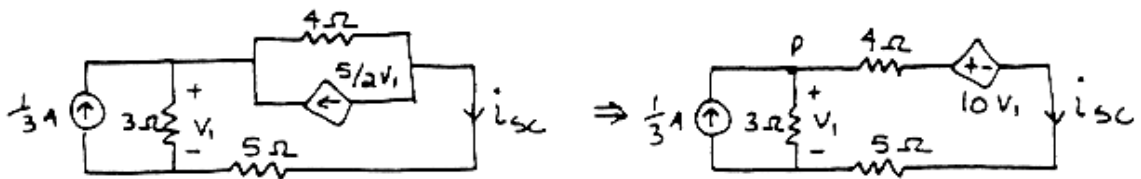


$$\text{from KVL a: } -v_1 + 4i_{sc} + 10v_1 + 5i_{sc} = 0$$

$$\Rightarrow 9v_1 + 9i_{sc} = 0 \quad (1)$$

$$\text{from KCL at P: } -\frac{1}{3} + \frac{v_1}{3} + i_{sc} = 0 \quad (2) \quad (1) \text{ \& \ } (2) \text{ yields}$$



$$\therefore R_T = \frac{v_{oc}}{i_{sc}} = \frac{-9}{1/2} = -18\Omega$$

$$\text{Norton equiv. ckt: } i_{sc} = \frac{1}{2}\text{A}$$

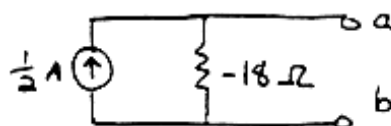

Section 5-7: Maximum Power Transfer


P5.7-1

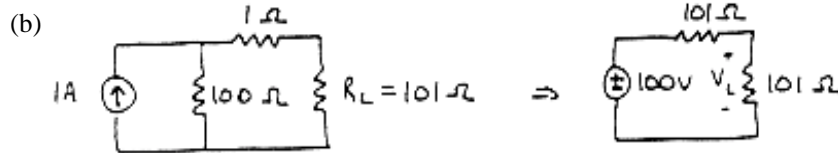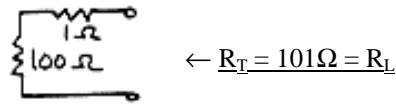

$$P_{\max} = v_L^2 / 101 = (50)^2 / 101 = 24.75 \text{ W}$$

P5.7-2

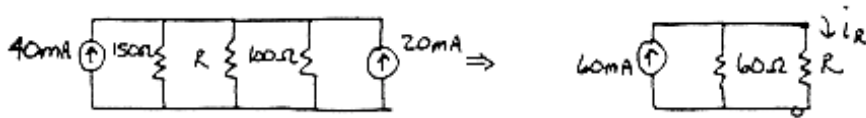
(a) Use source transformations to reduce ckt.



Norton equiv. where $R_T = 60\Omega$ \therefore want $R_L = 60\Omega$

(b) $P_{\max} = i_R^2 (R) = (30)^2 (60) = 54,000 \mu \text{ W} = 54 \text{ mW}$

P5.7-3

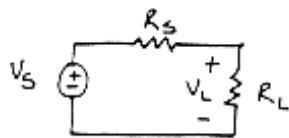


$$V_L = V_S \left[\frac{R_L}{R_S + R_L} \right]$$

$$\therefore P_L = \frac{V_L^2}{R_L} = \frac{V_S^2 R_L}{(R_S + R_L)^2}$$

By inspection, P_L is max when you vary R_S to get the smallest denominator. \therefore set $R_S = 0$

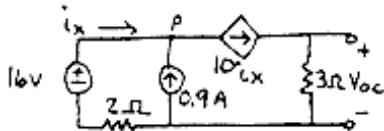
P5.7-4 Find R_T using $R_T = v_{oc} / i_{sc}$. First find v_{oc} :



KCL at P: $-i_x - 0.9 + 10i_x = 0 \Rightarrow i_x = 0.1 \text{ A}$

$\therefore v_{oc} = 3(10i_x) = 3 \text{ V}$

Find i_{sc}

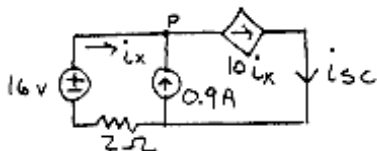


KCL at P: $-i_x - 0.9 + 10i_x = 0 \Rightarrow i_x = 0.1 \text{ A}$


$\therefore i_{sc} = 10i_x = 1 \text{ A}$

$P_{L_{\max}} = \frac{V_L^2}{R_L} = \frac{(1.5)^2}{3} = 0.75 \text{ W}$

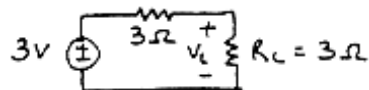$\therefore R_T = v_{oc} / i_{sc} = 3\Omega = R_L$ for max power



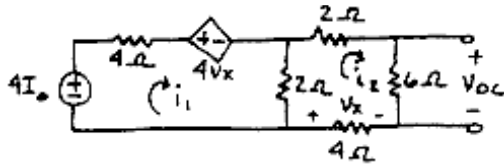P5.7-5 (a) For max power $R_L = R_T$. First find v_{oc} :



$$\text{KVL } a_1: -4I_0 + 4i_1 - 4v_x + 2(i_1 - i_2) = 0$$

$$\Rightarrow 6i_1 - 2i_2 + 4v_x - 4I_0 = 0 \quad (1)$$

$$\text{KVL } a_2: 2i_2 + 6i_2 - v_x + 2(i_2 - i_1) = 0$$


$$\Rightarrow -2i_1 + 10i_2 - v_x = 0 \quad (2)$$

$$\text{also } v_x = 4i_2 \quad (3)$$

$$\text{and } v_{oc} = 6i_2 \quad (4)$$

Solving (1), (2), (3), & (4) yields $v_{oc} = I_0$

Find i_{sc}

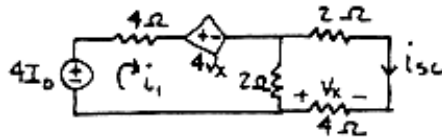

$$\text{KVL } a_1: -4I_0 + 4i_1 + 4v_x + 2(i_1 - i_{sc}) = 0$$

$$\Rightarrow 6i_1 - 2i_{sc} + 4v_x - 4I_0 = 0 \quad (1)$$

$$\text{KVL } a_x: 2i_{sc} + 4i_{sc} + 2(i_{sc} - i_1) = 0$$

$$\Rightarrow -2i_1 + 8i_{sc} = 0 \quad (2)$$

$$\text{also } v_x = -4i_{sc} \quad (3)$$

Solving (1), (2), & (3) yields $i_{sc} = \frac{2}{3} I_0$ $\therefore R_T = \frac{v_{oc}}{i_{sc}} = \frac{3}{2} \Omega = R_L$


$$(b) P_{L_{max}} = 54 \text{ W} = \frac{(v_{oc}/2)^2}{R_L} = I_0^2/6$$

$$\Rightarrow I_0 = 18 \text{ A}$$

P5.7-6

$$P_{max} = v_T^2/4R_T$$

Find $R_T \Rightarrow$ kill i source

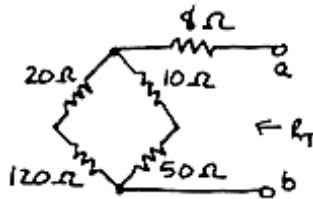

$$R_T = 8 + (20 + 120) \parallel (10 + 50)$$

$$= 50 \Omega$$

find v_{oc} :


$$i_{10\Omega} = \frac{120 + 50}{120 + 50 + 20 + 10} 20 \text{ A}$$

$$= 17 \text{ A}$$

$$\therefore v_{10\Omega} = 10(17) = 170 \text{ V}$$


$$v_{50\Omega} = 50(17 - 20) = -150 \text{ V} \Rightarrow v_{oc} = v_{10\Omega} + v_{50\Omega} = 170 - 150 = 20 \text{ V}$$
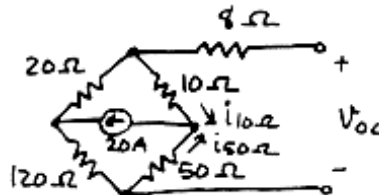
$$\therefore P_{max} = \frac{20^2}{4} = 2 \text{ W}$$



PSpice Problems

SP 5-1

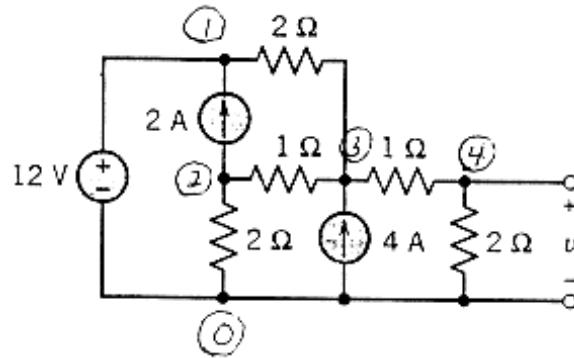


Input file

```
V1 1 0 dc 12
I2 2 1 dc 2
R3 2 0 2
R4 2 3 1
R5 1 3 2
R6 3 4 1
R7 0 3 dc 4
R8 4 0 2
.dc V1 12 12 1
.print dc V(4)
.END
```

result $V(4) = v = 4.952E+00V$

SP 5-2

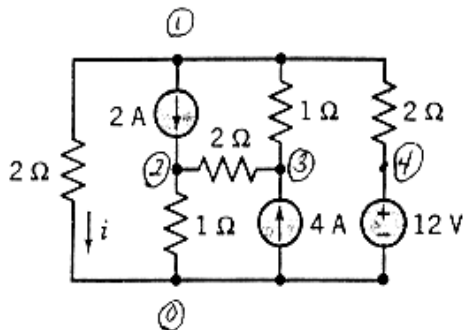


Input file

```
R1 1 0 2
I2 1 2 dc 2
R3 2 0 1
R4 2 3 2
R5 1 3 1
I6 0 3 dc 4
R7 1 4 2
V8 4 0 dc 12
.dc V8 12 12 1
.print dc I(R1)
.END
```

result

$i = I(R1) = 3.000E+00A$

SP 5-3

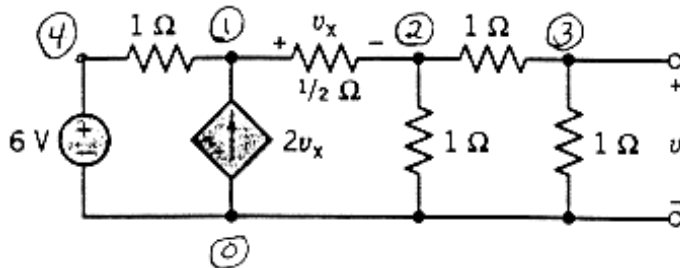


result

$v = v(3) = 1.714E+00V$

Input file

```
V1 4 0 dc 6
G2 0 1 1 2
R3 1 2 500m
R4 1 4 1
R5 2 0 1
R6 2 3 1
R7 3 0 1
.dc V1 6 6 1
.print dc V(3)
.END
```


SP 5.4

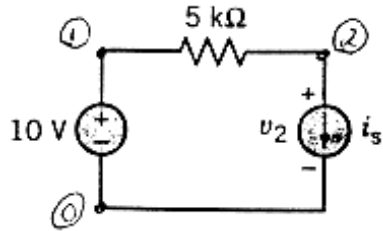


Input file

```
V1 1 0 dc 10
R2 1 2 5k
I3 2 0 dc 1m
.dc I3 0 2e-3 0.2e-3
.probe V(2)
.end
```

Probe result

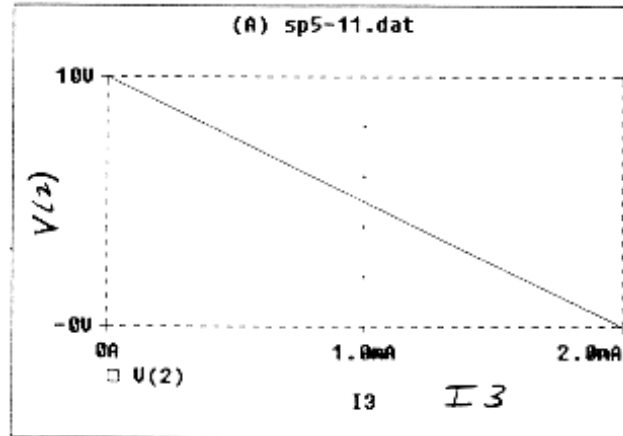

SP 5-5

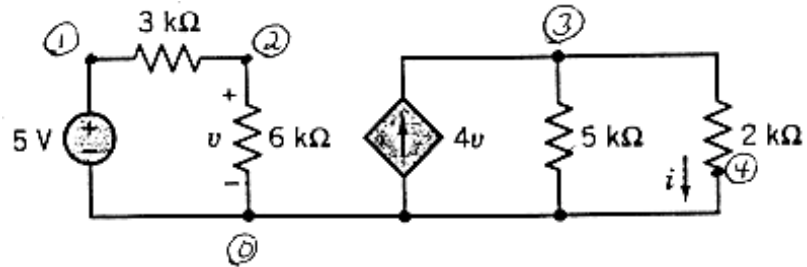


Input file

```
V1 1 0 dc 5
R1 1 2 3k
R2 2 0 6k
G4 0 3 2 0 4
R3 3 0 5k
R4 3 0 2k
.dc V1 5 5 1
.print dc I(R4)
.end
```

result $i = I(R4) = 9.524E+00A$

SP 5-6

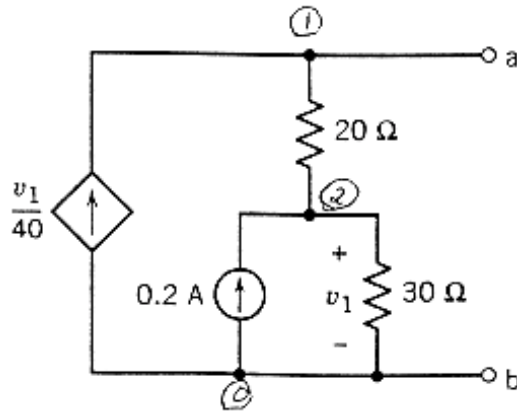

Input file

```
G1 0 1 2 0 25m
R2 1 2 2 20
I3 0 2 dc 0.2
R4 2 0 30
.tf V(1) I3
.end
```

result

answer: $V_1 = V_{oc} = V_T = 36V$

| NODE | VOLTAGE | NODE | VOLTAGE |
|-------|----------------|-------|---------|
| (1) | <u>36.0000</u> | (2) | 24.0000 |

$R_{TH} = \text{OUTPUT RESISTANCE AT } V(1) = 2.000E+02\Omega$



Verification Problems

VP 5-1 Evaluating data

Case 1: $R_L = 0\Omega$; $i = I_{sc} = 97.2\text{mA} = \frac{V_{oc}}{R_t}$ (1)

Case 2: $R_L = 500\Omega$; $i = 43.8\text{mA} = \frac{V_{oc}}{R_t + 500}$ (2)

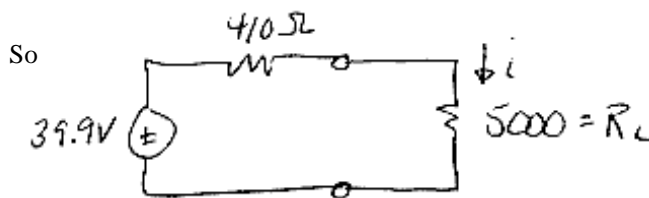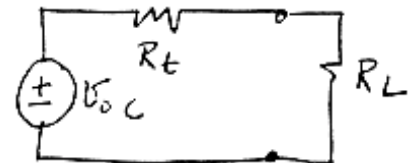Solving 1+2 yields $R_t = 410\Omega$, $v_{oc} = 39.9\text{V}$



When $R_L = 5000\Omega$

$$i = \frac{V_{oc}}{R_t + R_L} = 7.37\text{mA}$$

not 16.5mA as recorded \therefore the data is inconsistent.


VP 5-2

$V_{oc} = 12 \text{ V}$ (line 1 of the table)

$I_{sc} = 3 \text{ mA}$ (line 3 of the table)

so

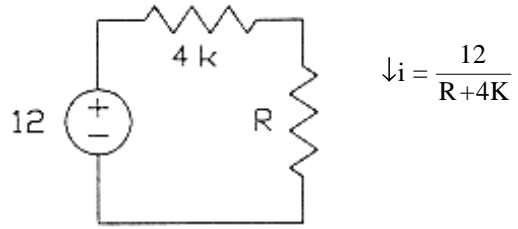$R_{TH} = V_{oc} / I_{sc} = 4 \text{ k}\Omega$



Hence the circuit can be simplified as shown above right. (Check:

$$\frac{12}{10K\Omega+4K\Omega} = 0.857 \text{ mA}$$

as shown in line 2 of the table.)

When $i = 1 \text{ mA}$ is required

$$1\text{mA} = \frac{12}{R+4\text{k}\Omega} \Rightarrow R = \frac{12}{1\text{mA}} - 4\text{k}\Omega = 8\text{k}\Omega$$

I agree with my lab partner's claim that $R = 8000$ causes $i = 1 \text{ mA}$.

VP 5-3



The measurement is consistent with the prelab calculations.

Design Problems

DP 5-1 The equation of representing the straight line in Figure DP 5-1b is $v = -R_t i + v_{oc}$. That is, the slope of the line is equal to -1 times the Thevenin resistance and the "v - intercept" is equal to the open circuit voltage. Therefore: $R_t = -\frac{0-5}{0.008-0} = 625 \Omega$ and $v_{oc} = 5 \text{ V}$.

Try $R_1 = R_2 = 1 \text{ k}\Omega$. ($R_1 \parallel R_2$ must be smaller than $R_t = 625 \Omega$.) Then

$$5 = \frac{R_2}{R_1 + R_2} v_s = \frac{1}{2} v_s \Rightarrow v_s = 10 \text{ V}$$

and

$$625 = R_3 + \frac{R_1 R_2}{R_1 + R_2} = R_3 + 500 \Rightarrow R_3 = 125 \Omega$$

Now v_s , R_1 , R_2 and R_3 have all been specified so the design is complete.

DP 5-2 The equation of representing the straight line in Figure DP 5-2b is $v = -R_t i + v_{oc}$. That is, the slope of the line is equal to -1 times the Thevenin resistance and the "v - intercept" is equal to the open circuit voltage. Therefore: $R_t = -\frac{0-(-3)}{-0.006-0} = 500 \Omega$ and $v_{oc} = -3 \text{ V}$.

From the circuit we calculate

$$R_t = \frac{R_3 (R_1 + R_2)}{R_1 + R_2 + R_3} \text{ and } v_{oc} = -\frac{R_1 R_3}{R_1 + R_2 + R_3} i_s$$

so

$$500 \Omega = \frac{R_3 (R_1 + R_2)}{R_1 + R_2 + R_3} \text{ and } 3 \text{ V} = -\frac{R_1 R_3}{R_1 + R_2 + R_3} i_s$$

Try $R_3 = 1 \text{ k}\Omega$ and $R_1 + R_2 = 1 \text{ k}\Omega$. Then $R_t = 500 \Omega$ and

$$-3 = -\frac{1000 R_1}{2000} i_s = \frac{R_1}{2} i_s \Rightarrow 6 = R_1 i_s$$

This equation can be satisfied by taking $R_1 = 600 \Omega$ and $i_s = 10 \text{ mA}$. Finally, $R_2 = 1 \text{ k}\Omega - 400 \Omega = 600 \Omega$. Now i_s , R_1 , R_2 and R_3 have all been specified so the design is complete.

DP 5-3 The slope of the graph is positive so the Thevenin resistance is negative. This would require

$$R_3 + \frac{R_1 R_2}{R_1 + R_2} < 0, \text{ which is not possible since } R_1, R_2 \text{ and } R_3 \text{ will all be non-negative.}$$

Is it not possible to specify values of v_s , R_1 , R_2 and R_3 that cause the current i and the voltage v in Figure DP 5-3a to satisfy the relationship described by the graph in Figure DP 5-3b.

DP 5-4 The equation of representing the straight line in Figure DP 5-4b is $v = -R_t i + v_{oc}$. That is, the slope of the line is equal to the Thevenin impedance and the "v - intercept" is equal to the open circuit voltage. Therefore: $R_t = -\frac{-5-0}{0-0.008} = -625 \Omega$ and $v_{oc} = -5$ V.

$$R_t = -\frac{-5-0}{0-0.008} = -625 \Omega \text{ and } v_{oc} = -5 \text{ V.}$$

The open circuit voltage, v_{oc} , the short circuit current, i_{sc} , and the Thevenin resistance, R_t , of this circuit are given by

$$v_{oc} = \frac{R_2 (d+1)}{R_1 + (d+1)R_2} v_s,$$

$$i_{sc} = \frac{(d+1)}{R_1} v_s$$

and

$$R_t = \frac{R_1 R_2}{R_1 + (d+1)R_2}$$

Let $R_1 = R_2 = 1 \text{ k}\Omega$. Then

$$-625 \Omega = R_t = \frac{1000}{d+2} \Rightarrow d = \frac{1000}{-625} - 2 = -3.6 \text{ A/A}$$


and

$$-5 = \frac{(d+1)v_s}{d+2} \Rightarrow v_s = \frac{-3.6+2}{-3.6+1}(-5) = -3.077 \text{ V}$$

Now v_s , R_1 , R_2 and d have all been specified so the design is complete.

DP 5-5 a) Find Thev. equiv.

v_{oc} :

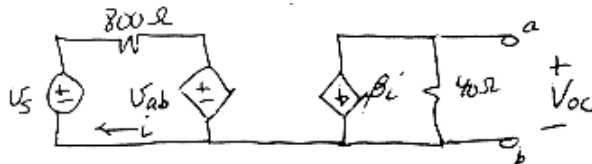


$$-v_s + 800 i + v_{ab} = 0 \quad (1)$$

$$v_{ab} = v_{oc} \quad (2)$$

$$v_{oc} = -(\beta i) \quad (3)$$

Solving eqs. (1) - (3) yields $v_{oc} = v_s / \left(1 - \frac{20}{\beta}\right)$

I_{sc} :

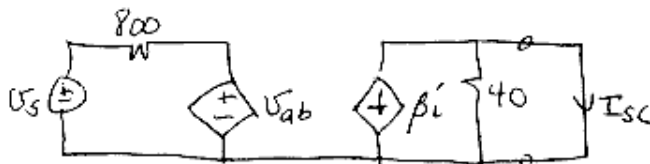


$$I_{sc} = -\beta i \quad (4)$$

$$v_{ab} = 0 \quad (5)$$

$$v_s = 800i \quad (6)$$

Solving eqs. (4) - (6) yields $I_{sc} = -\beta v_s / 800$

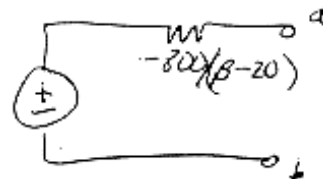so $R_t = \frac{v_{oc}}{I_{sc}} = \frac{-800}{\beta - 20}$ and Thev. equiv. $\frac{v_s}{\left(1 - \frac{20}{\beta}\right)}$



b) $R_t = R_L = 400 = \frac{-800}{\beta - 20} \Rightarrow \underline{\beta = 18}$

c) Max power to R_L , largest v_{oc} , largest v_s , smallest R_t

$$P_L = \frac{(V_L)^2}{R_L} \quad (7)$$

$$\text{and } V_L = \frac{400}{R_{total}} v_{oc} \quad (8)$$

with

$$R_{total} = \frac{-800}{\beta - 20} + 400 \text{ (a) yields } \underline{\beta = \pm 18}$$

d) delivering large amounts of power could melt antenna.

DP 5-6 Max power to load : $R_L = R_t = 50\Omega$

But split power equally ($R_{L1} = R_{L2} = 50\Omega$)



$$\frac{(R+50)(R+50)}{R+50+R+50} = 50 \Rightarrow \text{yields } \underline{R=50\Omega}$$