


Chapter 6: The Operational Amplifier

Exercises


Ex. 6.4-1

$$\frac{v_s}{R_1} + \frac{v_s - v_0}{R_2} + 0 = 0$$

$$\frac{v_0}{v_s} = 1 + \frac{R_2}{R_1}$$

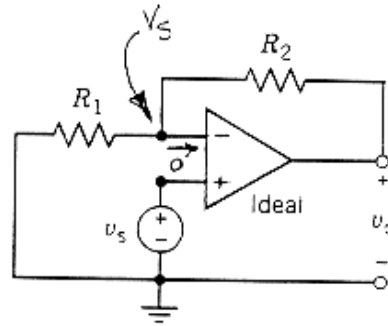

Ex. 6.4-2

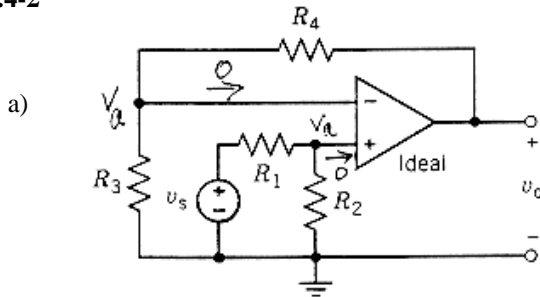


$$v_a = \frac{R_2}{R_1 + R_2} v_s$$

$$\frac{v_a}{R_3} + \frac{v_a - v_0}{R_4} + 0 = 0$$

$$\frac{v_0}{v_a} = 1 + \frac{R_4}{R_3} \Rightarrow \frac{v_0}{v_s} = \left(\frac{R_2}{R_1 + R_2} \right) \left(1 + \frac{R_4}{R_3} \right)$$

b) When $R_2 \gg R_1$ then $\frac{R_2}{R_1 + R_2} \approx \frac{R_2}{R_2} = 1$ and $\frac{v_0}{v_s} \approx 1 + \frac{R_4}{R_3}$


Ex. 6.5-1

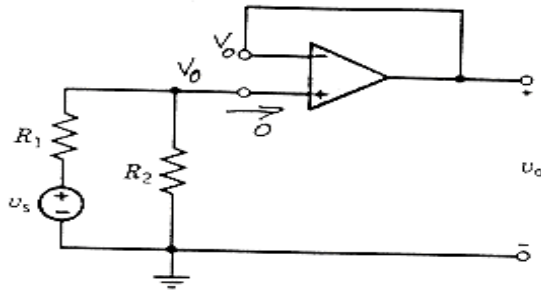

$$\frac{v_0}{R_2} + \frac{v_0 - v_s}{R_1} + 0 = 0$$

$$\frac{v_0}{v_s} = \frac{R_2}{R_1 + R_2}$$

Ex. 6.6-1

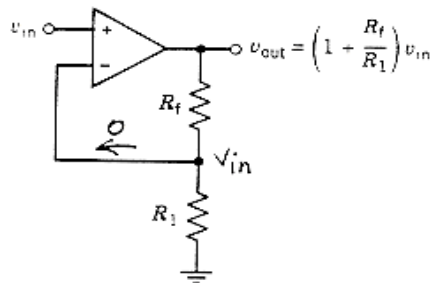

$$\frac{v_{in} - v_{out}}{R_f} + \frac{v_{in}}{R_1} + 0 = 0 \Rightarrow v_{out} = \left(1 + \frac{R_f}{R_1} \right) v_{in}$$

when $R_f = 100\text{k}\Omega$ and $R_1 = 25\text{k}\Omega$ then

$$\frac{v_{out}}{v_{in}} = \left(1 + \frac{100 \cdot 10^3}{25 \cdot 10^3} \right) = 5$$

(b) Noninverting amplifier


Ex. 6.7-1

Analysis of the circuit in Section 6.7 showed that output offset voltage = $6 v_{os} + (50 \cdot 10^3) i_{b1}$

For a $\mu\text{A}741$ opamp, $|v_{os}| \leq 1\text{mV}$ and $|i_{b1}| \leq 80\text{nA}$ so

$$|\text{output offset voltage}| = |6 v_{os} + (50 \cdot 10^3) i_{b1}| \leq 6(10^{-3}) + (50 \cdot 10^3)(80 \cdot 10^{-9}) = 10\text{mV}$$

Ex. 6.7-2

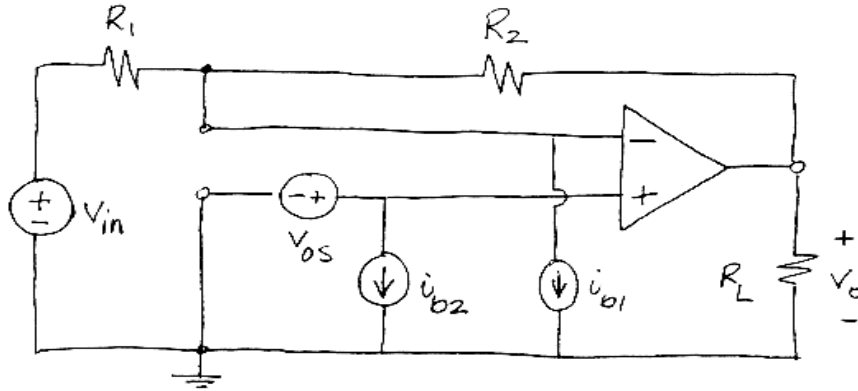

$$v_0 = -\frac{R_2}{R_1} v_{in} + \left(1 + \frac{R_2}{R_1}\right) v_{os} + R_2 i_{b1}$$

When $R_2 = 10\text{k}\Omega$, $R_1 = 2\text{k}\Omega$, $|v_{os}| \leq 5\text{mV}$ and $|i_{b1}| \leq 500\text{nA}$ then
 output offset voltage $\leq 6(5 \cdot 10^{-3}) + (10 \cdot 10^3)(500 \cdot 10^{-9}) \leq 35 \cdot 10^{-3} = 35\text{mV}$


Ex. 6.7-3

Analysis of this circuit in Section 6.7 showed that output offset voltage $= 6v_{os} + (50 \times 10^3)i_{b1}$

For a typical OPA101AM, $v_{os} = 0.1\text{mV}$ and $i_b = 0.012\text{nA}$ so

$$\begin{aligned} |\text{output offset voltage}| &\leq 6[0.1 \times 10^{-3}] + (50 \times 10^3)[0.012 \times 10^{-9}] \\ &\leq 0.6 \times 10^{-3} + 0.6 \times 10^{-6} \approx 0.6 \times 10^{-3} \\ &\leq 0.6\text{mV} \end{aligned}$$

Ex. 6.7-4

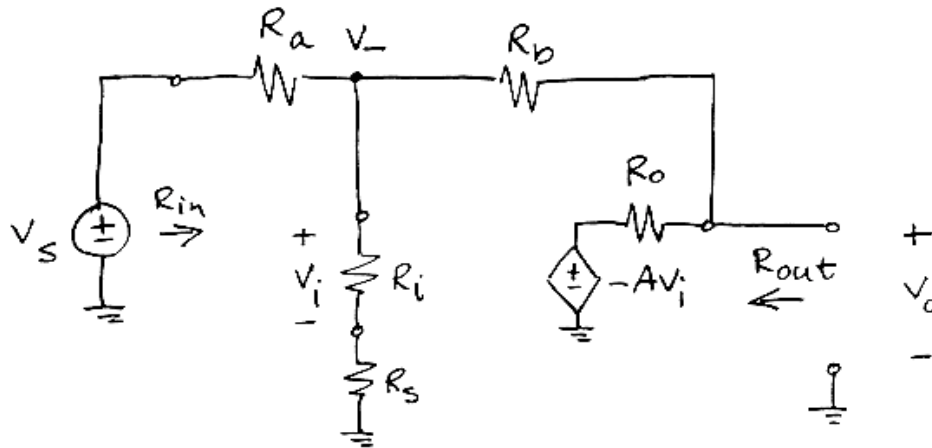

$$\frac{V_- - V_s}{R_a} + \frac{V_- - V_0}{R_b} + \frac{V_-}{R_i + R_s} = 0$$

$$\frac{V_0 - \left(-A \frac{R_i}{R_i + R_s} V_-\right)}{R_0} + \frac{V_0 - V_-}{R_b} = 0$$

After some algebra

$$A_v = \frac{V_0}{V_s} = \frac{R_0(R_i + R_s) + A R_i R_f}{(R_f + R_0)(R_i + R_s) + R_a(R_f + R_0 + R_i + R_s) - A R_i R_a}$$

For the given values, $A_v = -2.00006$

Ex. 6.8-1

```
Spice deck
V1      1 0      200mV
V2      2 0      125mV
V3      3 0      250mV
R1      1 5      50k
R2      2 5      25k
R3      5 4      100k
XOA1    5 0 4    IDEAL_OP_AMP
R4      4 6      25k
R5      3 6      10k
R6      6 7      50k
R7      7 0      100k
XOA2    6 0 7    IDEAL_OP_AMP
```

```
.SUBCKT IDEAL_OP_AMP 1 2 3
E 3 0 1 2 -1G
.ENDS IDEAL_OP_AMP
.END
```

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(1)	.2000	(2)	.1250	(3)	.2500
(4)	-.9000	(5)	900.0E-12	(6)	-550.0E-12
(7)	.5500				

Ex. 6.8-2

```
Spice deck
V1      1 0      200mV
V2      2 0      125mV
V3      3 0      250mV
R1      1 5      25k
R2      2 5      50k
R3      5 4      100k
XOA1    5 0 4    TL501_OP_AMP
R4      4 6      25k
R5      3 6      10k
R6      6 7      50k
R7      7 0      100k
XOA2    6 0 7    TL501_OP_AMP
```

```
.SUBCKT TL501_OP_AMP 1 2 5
IB1     1 0      .0175nA
IB2     2 0      .0425nA
VOS     3 2      .59mV
RI      1 3      1MEG
E       4 0 1 3  -105000
RO      4 5      250
.ENDS TL501_OP_AMP
.END
```

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(1)	.2000	(2)	.1250	(3)	.2500
(4)	-.8958	(5)	598.6E-06	(6)	584.8E-06
(7)	.5463	(XOA1.3)	590.0E-06	(XOA1.4)	-.9070
(XOA2.3)	590.0E-06	(XOA2.4)	.5504		

Ex. 6.8-3

```

Spice deck
V1 1 0 200mV
V2 2 0 125mV
V3 3 0 250mV
R1 1 5 5k
R2 2 5 2.5k
R3 5 4 10k
XOA1 5 0 4 UA741_OP_AMP
R4 4 6 2.5k
R5 3 6 1k
R6 6 7 5k
R7 7 0 10k
XOA2 6 0 7 UA741_OP_AMP

```

```

SUBCKT UA741_OP_AMP 1 2 5
IB1 1 0 70nA
IB2 2 0 90nA
VOS 3 2 1mV
RI 1 3 2MEG
E 4 0 1 3 -200000
RO 4 5 75
.ENDS UA741_OP_AMP
.END


```

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(1)	.2000	(2)	.1250	(3)	.2500
(4)	-.8958	(5)	.0010	(6)	997.2E-06
(7)	.5429	(XOA1.3)	.0010	(XOA1.4)	-.9258
(XOA2.3)	.0010	(XOA2.4)	.5551		

Problems

Section 6-4: The Ideal Operational Amplifier

P6.4-1

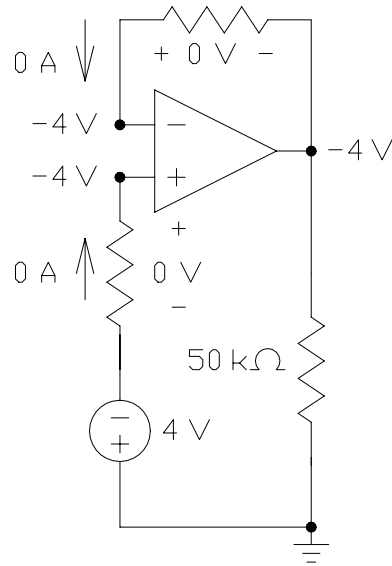

P6.4-2

KVL a1:

$$-12 + 3000i + 0 + 2000i = 0$$

$$\Rightarrow i = \frac{12}{5000} = 2.4\text{mA}$$


$$i_0 = i = 2.4\text{mA}$$

$$i_1 = i = 2.4\text{mA}$$

$$v_a = -i_1(1000) + 0$$

$$= -2.4\text{V}$$
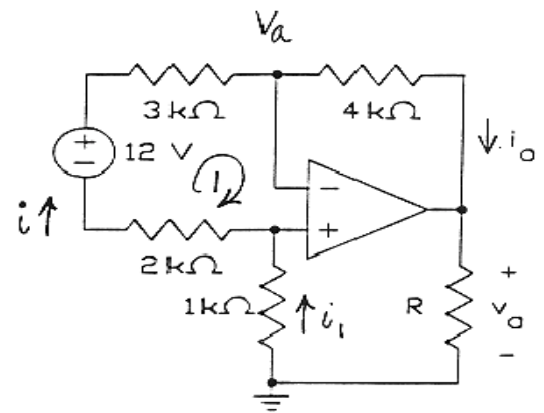
$$v_0 = v_a - i_0(4000) = -2.4 - (2.4 \times 10^{-3})(4000) = -12\text{V}$$




P6.4-3

$$v_a = -2\text{V}$$


$$\frac{v_0 - (-2)}{8000} + \frac{12 - (-2)}{4000} = 0$$

$$\Rightarrow v_0 = -30\text{V}$$
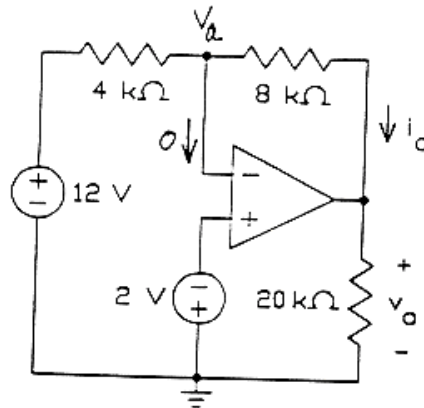
$$i_0 = \frac{-2 - v_0}{8000} = 3.5\text{mA}$$



P6.4-4

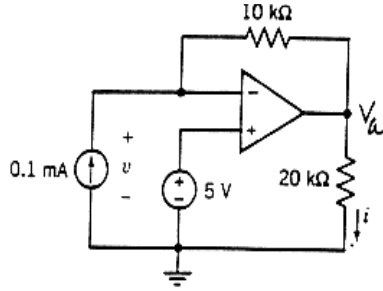

$$v = 5 \text{ V}$$

$$-\left(\frac{v_a - 5}{10000}\right) - 0.1 \times 10^{-3} - 0 = 0$$

$$\Rightarrow v_a = 4 \text{ V}$$


$$i = \frac{v_a}{20000} = \frac{1}{5} \text{ mA}$$

P6.4-5


$$-\left(\frac{v_0 - 0}{3000}\right) - \left(\frac{12 - 0}{4000}\right) - 2 \cdot 10^{-3} = 0$$

$$\Rightarrow v_0 = -15 \text{ V}$$

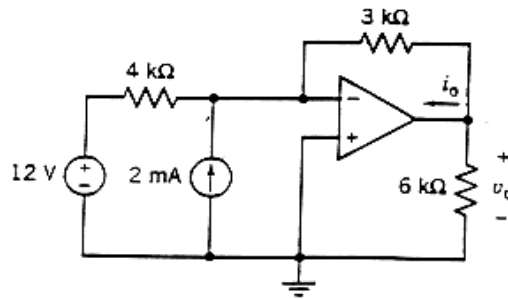
$$i_0 + \frac{v_0}{6000} + \frac{v_0}{3000} = 0 \Rightarrow i_0 = 7.5 \text{ mA}$$



P6.4-6

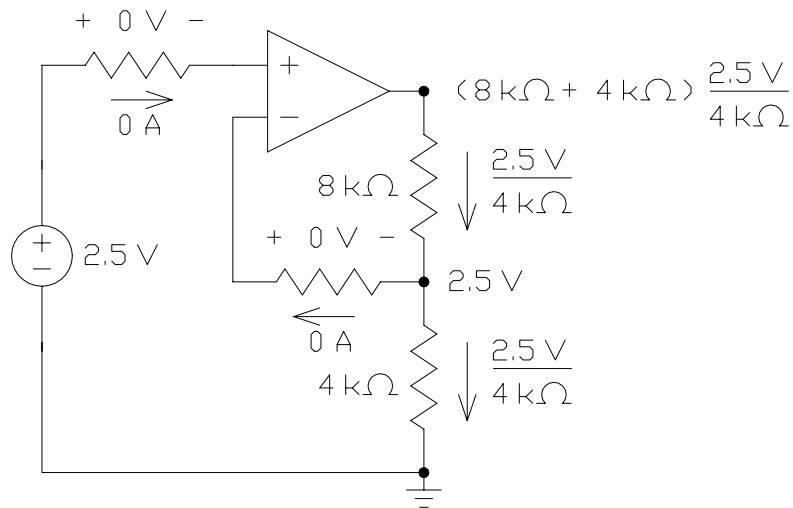

P6.4-7

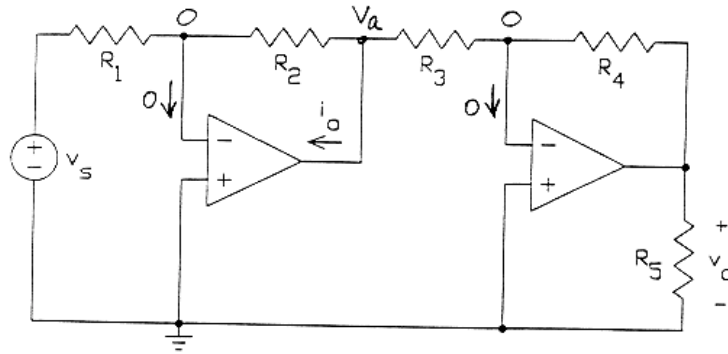


$$-\left(\frac{v_s - 0}{R_1}\right) - \left(\frac{v_a - 0}{R_2}\right) + 0 = 0 \Rightarrow v_a = -\frac{R_2}{R_1} v_s$$

$$i_0 = \frac{0 - v_a}{R_2} + \frac{0 - v_a}{R_3} = \frac{R_2 + R_3}{R_2 R_3} v_a = -\left(\frac{R_2 + R_3}{R_1 R_3}\right) v_s$$

$$-\left(\frac{v_0 - 0}{R_4}\right) - \left(\frac{v_a - 0}{R_3}\right) + 0 = 0 \Rightarrow v_0 = -\frac{R_4}{R_3} v_a = \frac{R_2 R_4}{R_1 R_3} v_s$$


P6.4-8

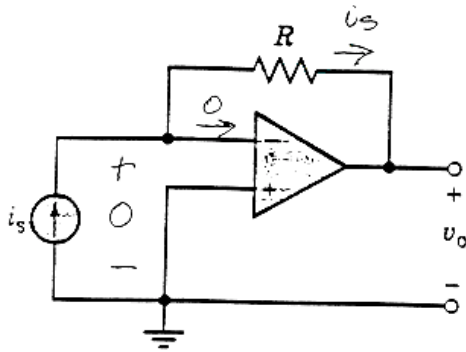

$$v_0 = 0 - R i_s$$

$$\therefore \frac{v_0}{i_s} = -R$$

P6.4-9

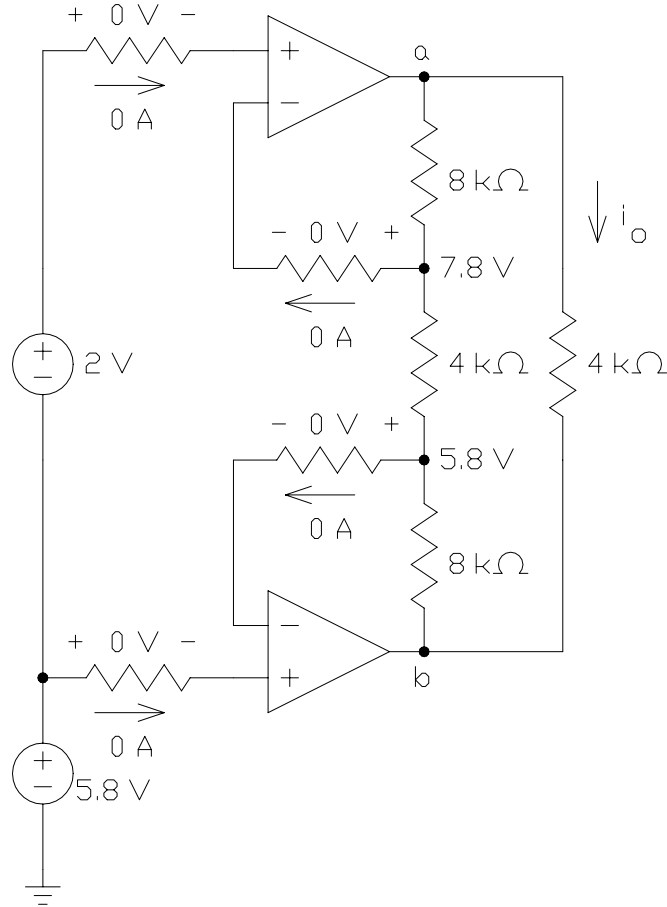

P 6.4-10


KCL at node a: $\frac{v_a - (-18)}{4000} + \frac{v_a}{8000} + 0 = 0 \Rightarrow v_a = -12 \text{ V}$

The node voltages at the input nodes of ideal op amps are equal so $v_b = v_a$.

Voltage division: $v_o = \frac{8000}{4000 + 8000} v_b = -8 \text{ V}$

Section 6-5: Nodal Analysis of Circuits Containing Ideal Operational Amplifiers

P6.5-1

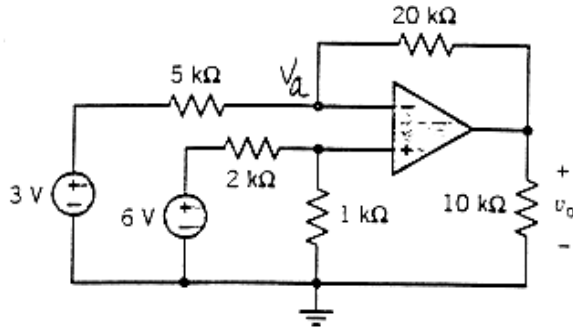

$$v_a = \frac{1000}{2000+1000}6 = 2 \text{ V}$$

$$-\left(\frac{v_o-2}{20000}\right) - \left(\frac{3-2}{5000}\right) = 0$$

$$\Rightarrow v_o = -2 \text{ V}$$

P6.5-2

KCL at node b: $\frac{v_b-2}{20e3} + \frac{v_b}{40e3} + \frac{v_b+5}{40e3} = 0 \Rightarrow v_b = -\frac{1}{4} \text{ V}$

$v_e = v_b = -\frac{1}{4} \text{ V}$ because the node voltages at the input nodes of an ideal op amp are equal


KCL at node e: $\frac{v_e}{1000} + \frac{v_d+v_e}{40e3} = 0 \Rightarrow v_d = 10v_e = -\frac{10}{4} \text{ V}$

P6.5-3


$$0 = \frac{v_a-12}{6000} + \frac{v_a}{6000} + \frac{v_a-0}{6000} \Rightarrow v_a = 4 \text{ V}$$

$$-\left(\frac{v_a-0}{6000}\right) + 0 + \left(\frac{0-v_0}{6000}\right) = 0 \Rightarrow v_0 = -v_a = -4 \text{ V}$$
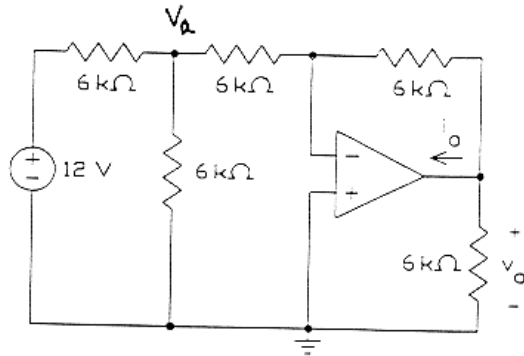
$$i_0 - \left(\frac{0-v_0}{6000}\right) + \frac{v_0}{6000} = 0 \Rightarrow i_0 = -\frac{v_0}{3000} = 1.33 \text{ mA}$$



P6.5-4

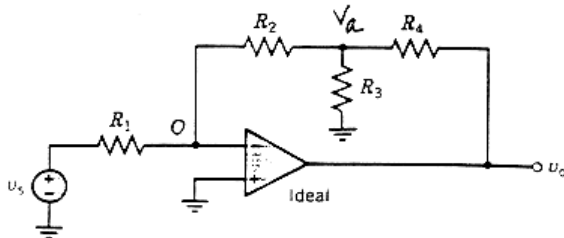

$$-\left(\frac{v_a-0}{R_2}\right) - \left(\frac{v_s-0}{R_1}\right) = 0$$


$$\Rightarrow v_a = -\frac{R_2}{R_1} v_s$$

$$\frac{v_a-v_0}{R_4} + \frac{v_a}{R_3} + \frac{v_a-0}{R_2} = 0 \Rightarrow v_0 = R_4 \left(\frac{1}{R_4} + \frac{1}{R_3} + \frac{1}{R_2} \right) v_a = \frac{R_2 R_3 + R_2 R_4 + R_3 R_4}{R_2 R_3} v_a$$

$$= -\frac{R_2 R_3 + R_2 R_4 + R_3 R_4}{R_1 R_3} v_s$$

Plug in values \Rightarrow yields $\frac{v_0}{v_s} = -200$

P6.5-5

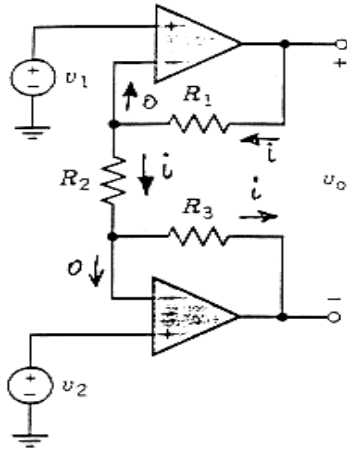

$$i = \frac{v_1 - v_2}{R_2}$$

$$v_0 = (R_1 + R_2 + R_3)i$$

$$= \frac{R_1 + R_2 + R_3}{R_2}(v_1 - v_2)$$


P6.5-6

$$\frac{v_1 - v_a}{R_1} + \frac{v_1 - v_2}{R_7} + 0 = 0 \Rightarrow v_a = \left(1 + \frac{R_1}{R_7}\right)v_1 - \frac{R_1}{R_7}v_2$$

$$\frac{v_2 - v_b}{R_2} - \frac{v_1 - v_2}{R_7} + 0 = 0 \Rightarrow v_b = \left(1 + \frac{R_2}{R_7}\right)v_2 - \frac{R_2}{R_7}v_1$$

$$-\left(\frac{v_b - v_c}{R_4}\right) + \frac{v_c - 0}{R_6} + 0 = 0 \Rightarrow v_c = \frac{R_6}{R_4 + R_6}v_b$$
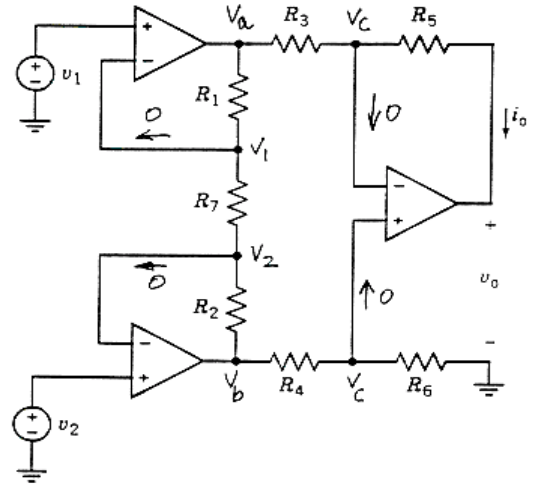
$$-\left(\frac{v_a - v_c}{R_3}\right) + \left(\frac{v_c - v_0}{R_5}\right) + 0 = 0 \Rightarrow v_0 = -\frac{R_5}{R_3}v_a + \left(1 + \frac{R_5}{R_3}\right)v_c$$



$$v_0 = \left[\frac{R_5 R_1 + R_6 (R_3 + R_5)}{R_3 R_7} \left(1 + \frac{R_2}{R_7}\right)\right] v_2 - \left[\frac{R_5}{R_3} \left(1 + \frac{R_1}{R_7}\right) + \frac{R_6 (R_3 + R_5) R_2}{R_3 (R_4 + R_6) R_7}\right] v_1$$

$$i_0 = \frac{v_c - v_0}{R_5} = \dots$$

P6.5-7

$$\text{KCL at node b: } \frac{v_a}{20e3} + \frac{v_c}{25e3} = 0 \Rightarrow v_c = -\frac{5}{4}v_a$$

$$\text{KCL at node a: } \frac{v_a - (-12)}{40e3} + \frac{v_a}{10e3} + \frac{v_a + 0}{20e3} + \frac{v_a - \left(-\frac{5}{4}v_a\right)}{10e3} = 0 \Rightarrow v_a = -\frac{3}{4} \text{ V}$$

$$\text{so } v_c = -\frac{5}{4}v_a = -\frac{15}{16}$$

P6.5-8

$$-\left(\frac{v_a - 0}{10000}\right) + 0 - \left(\frac{(v_a + 6) - 0}{30000}\right) = 0$$

$$\Rightarrow v_a = -1.5 \text{ V}$$

$$\frac{v_a - 0}{10000} + \frac{v_a + 6 - 0}{30000} + \frac{v_a - v_b}{30000} + \frac{(v_a + 6) - 0}{10000} = 0$$

$$\Rightarrow 3v_a + v_a + 6 + v_a - v_b + 3[(v_a + 6) - v_b] = 0$$


$$\Rightarrow v_b = 2v_a + 6 = 3 \text{ V}$$

$$\frac{v_b}{10000} + \frac{v_b - v_0}{30000} - \left(\frac{v_a - v_b}{30000}\right) - \left(\frac{(v_a + 6) - v_b}{10000}\right) = 0$$

$$\Rightarrow 3v_b + (v_b - v_0) - (v_a - v_b) - 3[(v_a + 6) - v_b] = 0$$

$$\Rightarrow v_0 = 8v_b - 4v_a - 18 = \underline{12 \text{ V}}$$
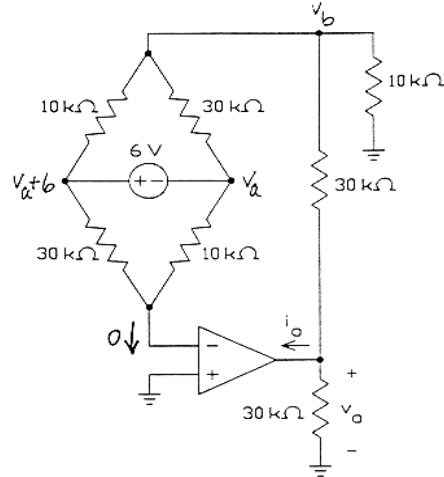
$$i_0 + \frac{v_0}{30000} + \frac{v_0 - v_b}{30000} = 0 \Rightarrow i_0 = -0.7 \text{ mA}$$



P6.5-9


$$-i_0(10000) - i_0(20000) + 5 = 0$$

$$i_0 = \frac{1}{6} \text{ mA}$$

$$v_a = 10000 i_0 = \frac{10}{6} \text{ V}$$

$$\frac{v_a}{10000} + \frac{v_a - v_0}{20000} = 0$$

$$\Rightarrow v_0 = 3v_a = 5 \text{ V}$$

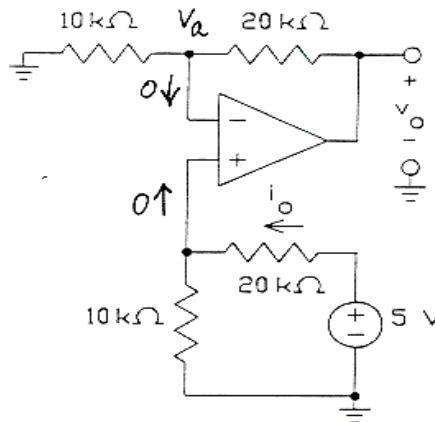

P6.5-10

KCL at node b: $\frac{v_b + 12}{40e3} + \frac{v_b}{20e3} = 0 \Rightarrow v_b = -4 \text{ V}$

$v_c = v_b = -4 \text{ V}$ because the node voltages at the input nodes of an ideal op amp are equal.


$v_d = v_c + 0 \cdot 10e3 = -4 \text{ V}$ because the currents into the inputs of an ideal op amp are zero.

KCL at node g: $-\left(\frac{v_f - v_g}{20e3}\right) + \frac{v_g}{40e3} = 0 \Rightarrow v_g = \frac{2}{3}v_f$

KCL at node d: $\frac{v_d - v_f}{20e3} + \frac{v_d - \frac{2}{3}v_f}{20e3} = 0 \Rightarrow v_f = \frac{6}{5}v_d = -\frac{24}{5} \text{ V}$ so $v_g = \frac{2}{3}v_f = -\frac{15}{5} \text{ V}$.

$v_c = v_g = -\frac{16}{5} \text{ V}$ because the node voltages at the input nodes of an ideal op amp are equal

P6.5-11

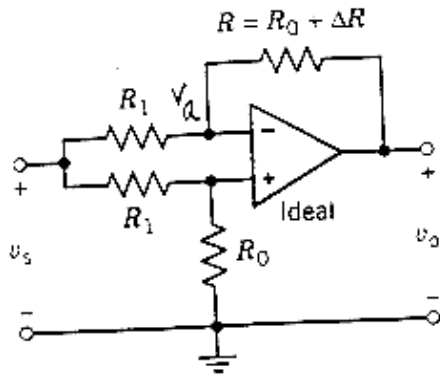

$$v_a = \frac{R_0}{R_1 + R_0} v_s$$

$$\frac{v_a - v_s}{R_1} + \frac{v_a - v_o}{R_0 + \Delta R} = 0$$

$$\frac{R_0 + \Delta R}{R_1} (v_a - v_s) + v_a = v_o$$


$$v_o = \left[\left(\frac{R_0 + \Delta R}{R_1} + 1 \right) \frac{R_0}{R_1 + R_0} - \frac{R_0 + \Delta R}{R_1} \right] v_s$$

$$= -\frac{\Delta R}{R_1 + R_0} v_s$$

$$= \left(-v_s \frac{R_0}{R_1 + R_0} \right) \frac{\Delta R}{R_0}$$


Section 6-6: Design Using Operational Amplifier

P6.6-1

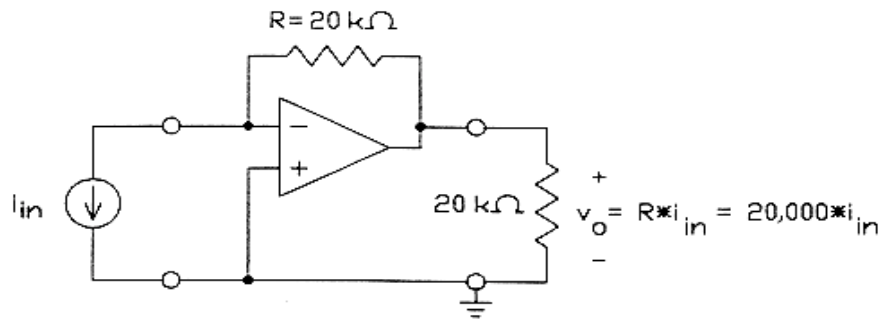


$$v_o = R * i_{in} = 20,000 * i_{in}$$

P6.6-2

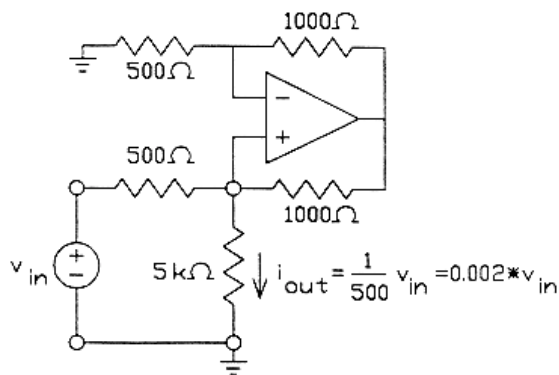


$$i_{out} = \frac{1}{500} v_{in} = 0.002 * v_{in}$$


P6.6-3

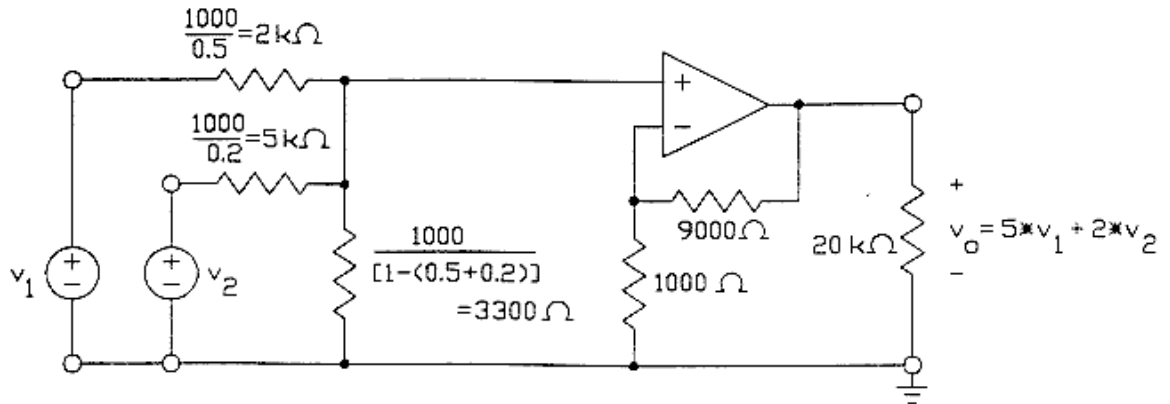


P6.6-4

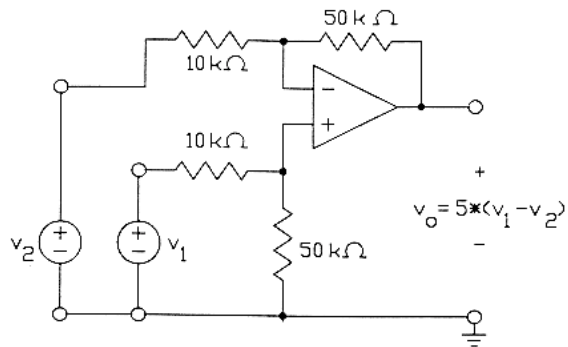


P6.6-5

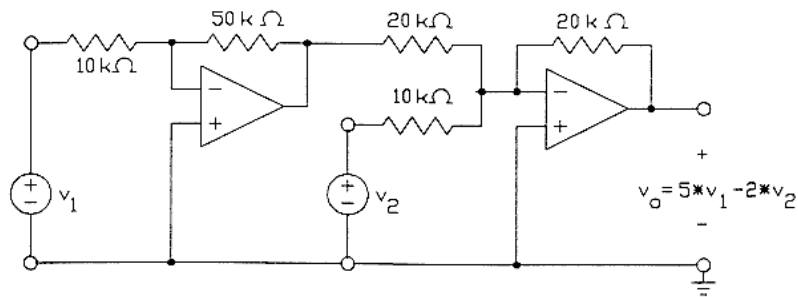

P6.6-6

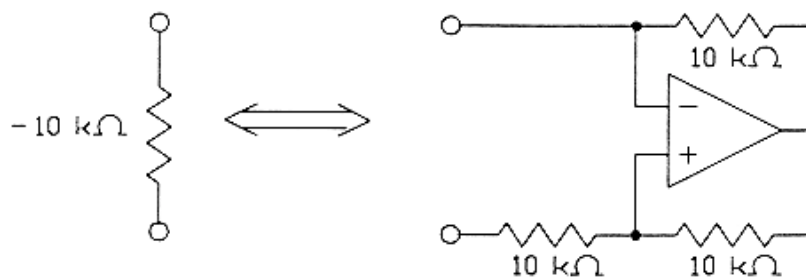

P6.6-7

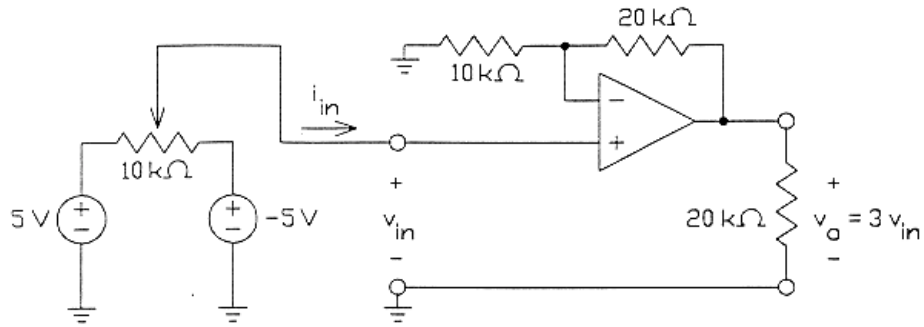


P6.6-8

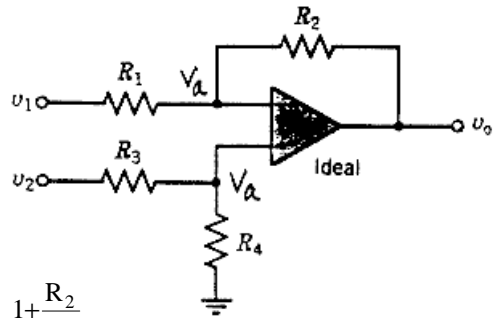(a)
$$v_a = \frac{R_4}{R_3 + R_4} v_2$$

$$\frac{v_a - v_1}{R_1} + \frac{v_a - v_0}{R_2} = 0$$

$$\Rightarrow v_0 = \left(\frac{R_2 + 1}{R_1} \right) v_a - \frac{R_2}{R_1} v_1$$



$$= \left(\frac{R_2 + 1}{R_1} \right) \frac{R_4}{R_3 + R_4} v_2 - \frac{R_2}{R_1} v_1 = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{R_3}{R_4}} v_2 - \frac{R_2}{R_1} v_1$$

(b)
$$11 = \frac{R_2}{R_1} \text{ and } 4 = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{R_3}{R_4}} = \frac{12}{1 + \frac{R_3}{R_4}} \Rightarrow \frac{R_3}{R_4} = 2$$

For example:


$$R_1 = 10\text{k}\Omega, R_2 = 110\text{k}\Omega, R_3 = 20\text{k}\Omega \text{ \& } R_4 = 10\text{k}\Omega$$

P6.6-9



We know this ckt yields $v_0 = -\frac{R}{R_1}v_1$

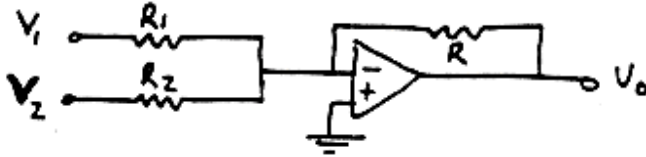
so consider adding another input lead into the negative terminal



with $v_i \approx 0$, KCL at negative input yields

$$-v_1/R_1 - v_2/R_2 = v_0/R \Rightarrow v_0 = -\frac{R}{R_1}v_1 - \frac{R}{R_2}v_2$$

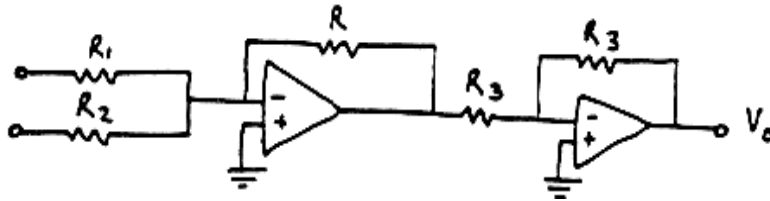Since need to invert the answer, add an inverter to the output,






Let $R_3 = 10\text{k}\Omega$

Now $\frac{R}{R_1} = 6$ and $\frac{R}{R_2} = 2 \therefore$ let $R = 60\text{ k}\Omega$

$R_1 = 10\text{k}\Omega$ and $R_2 = 30\text{k}\Omega$

P6.6-10

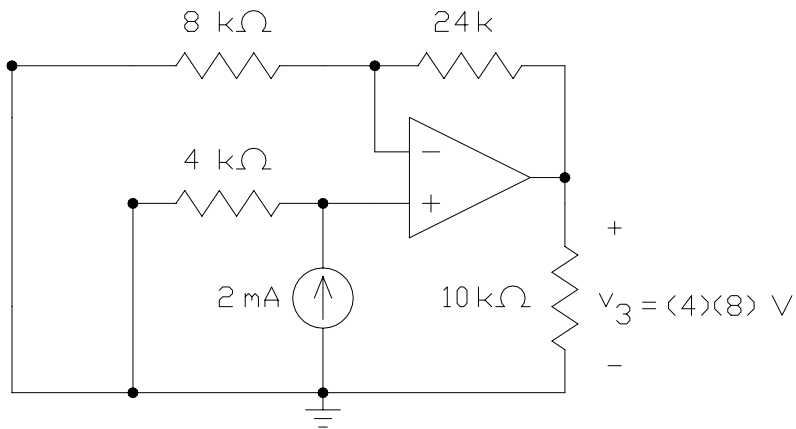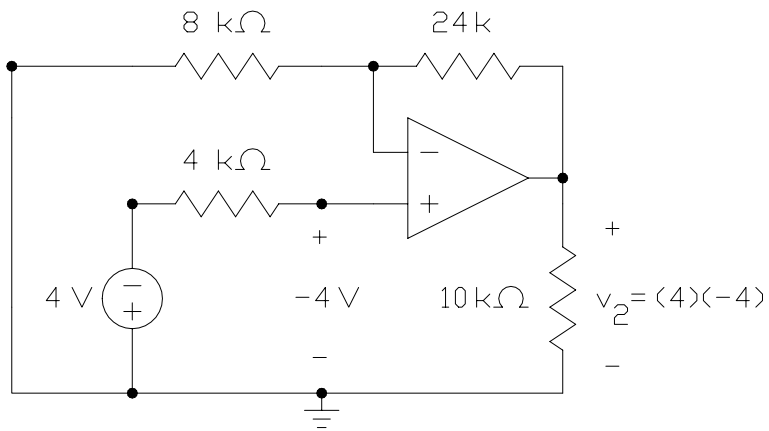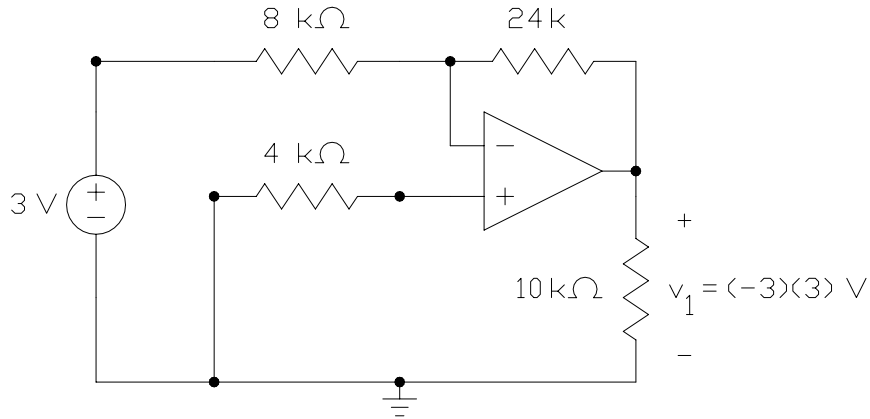


Using superposition, $v_o = v_1 + v_2 + v_3 = -9 - 16 + 32 = 7 \text{ V}$

P6.6-11

R_1	6	12	24	$6 \parallel 12$	$6 \parallel 24$	$12 \parallel 12$	$12 \parallel 24$	$6 \parallel 12 \parallel 12$	$6 \parallel 12 \parallel 24$	$12 \parallel 12 \parallel 24$
R_2	$12 \parallel 12 \parallel 24$	$6 \parallel 12 \parallel 24$	$6 \parallel 12 \parallel 12$	$12 \parallel 24$	$12 \parallel 12$	$6 \parallel 24$	$6 \parallel 12$	24	12	6
$-v_o/v_s$	0.8	0.286	0.125	2	1.25	0.8	0.5	8	3.5	1.25

P6.6-12

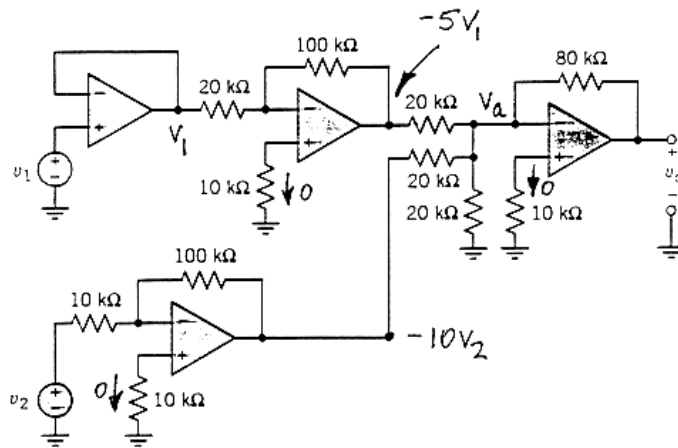

$$\frac{v_a - (-5v_1)}{20\text{k}\Omega} + \frac{v_a - (-10v_2)}{20\text{k}\Omega} + \frac{v_a}{20\text{k}\Omega} + \frac{v_a - v_0}{80\text{k}\Omega} = 0$$

$$4(v_a + 5v_1) + 4(v_a + 10v_2) + 4v_a + v_a - v_0 = 0$$

$$v_a = 0(10\text{k}\Omega) = 0$$

$$v_0 = 20v_1 + 40v_2$$

P 6.6-13

$$v_c = -(3v_a + 1)$$

$$v_o = -(3v_b + 2v_c + 2) = -(3v_b - 2(3v_a + 1) + 2) = -3v_b + 6v_a$$

P6.6-14


- (a) $2R \parallel 2R = R$
 R in series with $R = 2R$
 \vdots
 $R_{eq} = R$

$$\underline{I = \frac{V_R}{R}}, \quad I_1 = \frac{V_R}{R} \left(\frac{2R}{4R} \right) = \frac{V_R}{2R}$$

$$I_2 = \frac{V_R}{2R} \left(\frac{2R}{4R} \right) = \frac{V_R}{2^2 R}$$

$$\vdots$$

$$I_n = \frac{V_R}{2^n R}$$

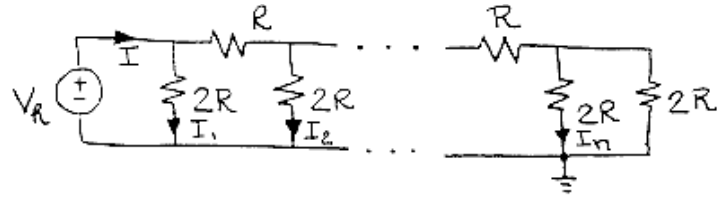

(b) $\frac{V_0}{R_f} = b_1 I_1 + b_2 I_2 + \dots + b_n I_n$

$$V_0 = R_f \left[b_1 \frac{V_R}{2R} + b_2 \frac{V_R}{2^2 R} + \dots + b_n \frac{V_R}{2^n R} \right] = \frac{R_f V_R}{R} \left[b_1 2^{-1} + b_2 2^{-2} + \dots + b_n 2^{-n} \right]$$

(c) $I^+ + I^- = \frac{V_R}{2R} + \frac{V_R}{2^2 R} + \dots + \frac{V_R}{2^n R}$

$$= \frac{V_R}{R} \left[2^{-1} + 2^{-2} + \dots + 2^{-n} \right]$$


$$= \frac{V_R}{R} \left[1 - 2^{-n} \right]$$

(d)

$-V_0$	b1	b2	b3	b4
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	0	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1

Section 6-7: Characteristics of the Practical Operational Amplifier


P6.7-1

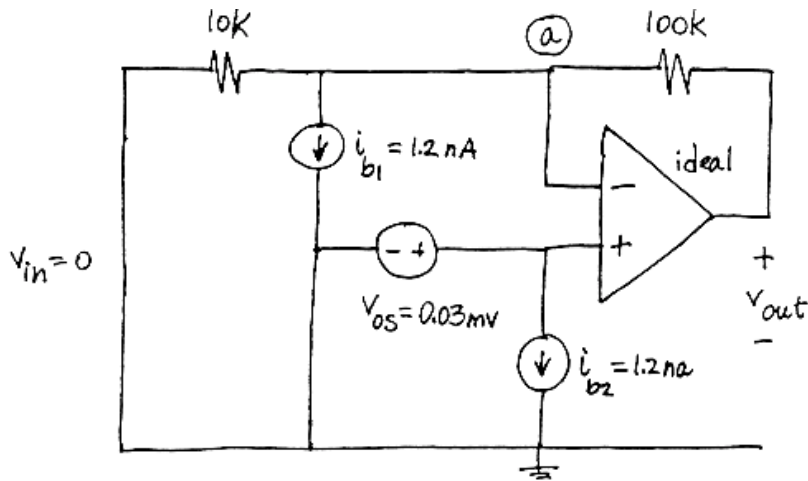

The node equation at node a is $\frac{V_{out} - V_{os}}{100k} = \frac{V_{os}}{10k} + i_{b1}$

$$\begin{aligned} \text{so } V_{out} &= \left(1 + \frac{100k\Omega}{10k\Omega}\right) V_{os} + 100k\Omega \cdot i_{b1} = 11V_{os} + 100k\Omega \cdot i_{b1} \\ &= 11(0.03mV) + 100k\Omega(1.2nA) \\ &= \underline{0.45mV} \end{aligned}$$


P6.7-2

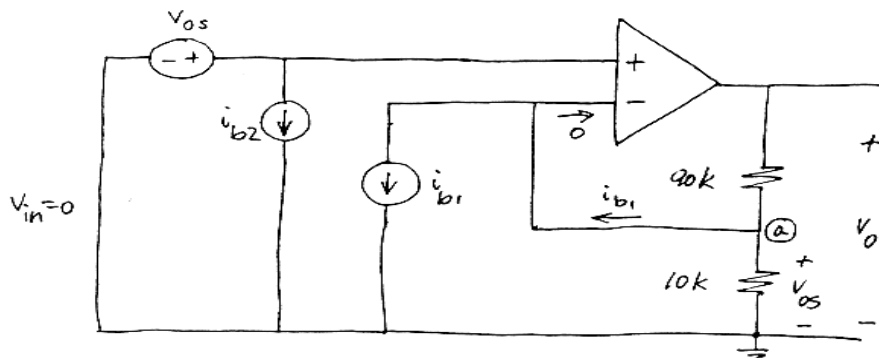

The node equation at node a is

$$\begin{aligned} \frac{V_{os}}{10k} + i_{b1} &= \frac{V_0 - V_{os}}{90k\Omega} \\ \text{so } V_0 &= \left(1 + \frac{90k\Omega}{10k\Omega}\right) V_{os} + 90k\Omega i_{b1} = 10V_{os} + 90k\Omega i_{b1} \\ &= 10(5mV) + 90k\Omega(0.05nA) \\ &= 50.0045mV \approx \underline{50mV} \end{aligned}$$

P6.7-3

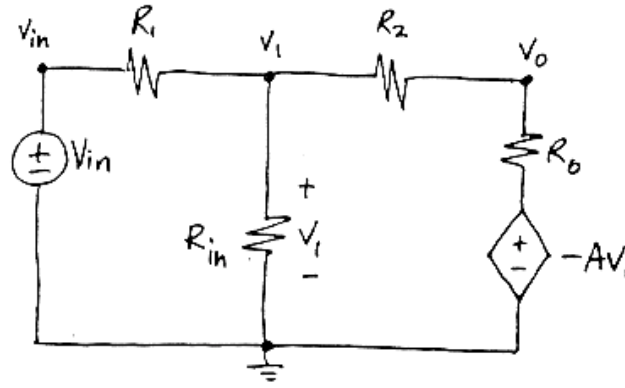

$$\left. \begin{aligned} \frac{v_1 - v_{in}}{R_1} + \frac{v_1}{R_{in}} + \frac{v_1 - v_0}{R_2} &= 0 \\ \frac{v_0 + Av_1}{R_0} + \frac{v_0 - v_1}{R_2} &= 0 \end{aligned} \right\} \Rightarrow \frac{v_0}{v_{in}} = \frac{R_{in}(R_0 - AR_2)}{(R_1 + R_{in})(R_0 + R_2) + R_1 R_{in}(1 + A)}$$


P6.7-4

a) $\frac{v_0}{v_{in}} = -\frac{R_2}{R_1} = -\frac{49\text{k}\Omega}{5.1\text{k}\Omega} = -9.6078$

b) $\frac{v_0}{v_{in}} = \frac{2\text{M}\Omega(75 - (200,000)(50\text{k}\Omega))}{(5\text{k}\Omega + 2\text{M}\Omega)(75 + 50\text{k}\Omega) + (5\text{k}\Omega)(2\text{M}\Omega)(1 + 200,000)}$
 $= -9.9995$

c) $\frac{v_0}{v_{in}} = \frac{2\text{M}\Omega(75 - (200,000)(49\text{k}\Omega))}{(5.1\text{k}\Omega + 2\text{M}\Omega)(75 + 49\text{k}\Omega) + (5.1\text{k}\Omega)(2\text{M}\Omega)(1 + 200,000)}$
 $= -9.6073$

P6.7-5

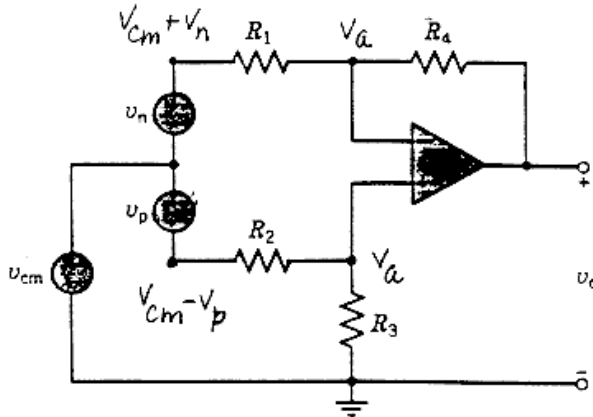

$$v_a = \frac{R_3}{R_2 + R_3}(v_{cm} - v_p)$$

$$\frac{v_a - v_0}{R_4} + \frac{v_a - (v_{cm} + v_n)}{R_1} = 0$$

$$v_0 = -\frac{R_4}{R_1}(v_{cm} + v_n) + \frac{R_4 + R_1}{R_1}v_a$$

$$= -\frac{R_4}{R_1}(v_{cm} + v_n) + \frac{(R_4 + R_1)R_3}{R_1(R_2 + R_3)}(v_{cm} - v_p)$$


when $\frac{R_4}{R_1} = \frac{R_3}{R_2}$ then $\frac{(R_4 + R_1)R_3}{R_1(R_2 + R_3)} = \frac{\frac{R_4 + 1}{R_1} \times R_3}{\frac{R_3 + 1}{R_2}} = \frac{R_4}{R_1}$

so

$$v_0 = -\frac{R_4}{R_1}(v_{cm} + v_n) + \frac{R_4}{R_1}(v_{cm} - v_p) = -\frac{R_4}{R_1}(v_n + v_p)$$


P6.7-6

(a)

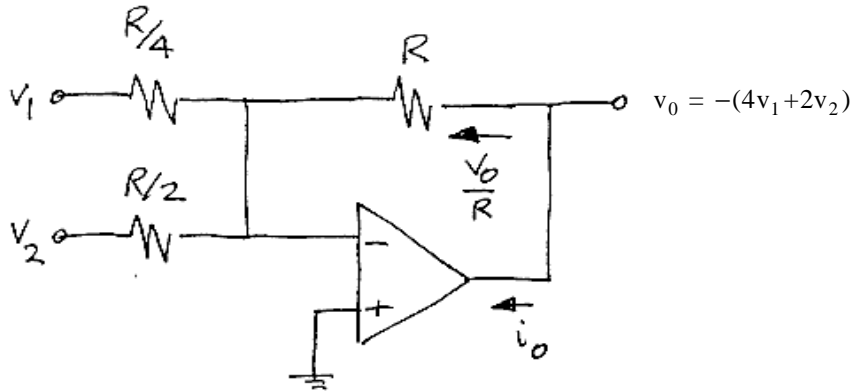

$$|i_0| \leq \frac{4|v_1| + 2|v_2|}{R} \leq \frac{6}{R} < i_{\text{sat}} \quad \text{so } R > \frac{6}{i_{\text{sat}}} = \frac{6}{2 \times 10^{-3}} = 3 \text{ k}\Omega \text{ is required}$$

(b)

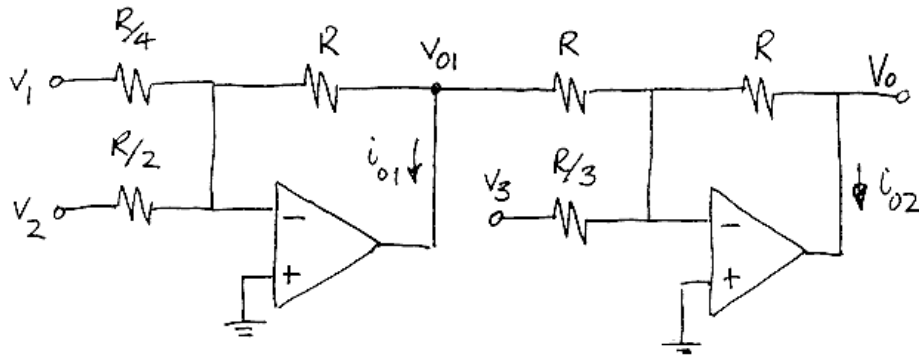

$$v_{01} = -(4v_1 + 2v_2); \quad v_0 = -(v_{01} + 3v_3) = 4v_1 + 2v_2 - 3v_3$$

$$i_{01} = -\frac{v_{01}}{R} - \frac{v_{01}}{R} = -\frac{2v_{01}}{R}$$

$$|i_{01}| \leq \frac{2}{R}(4|v_1| + 2|v_2|) \leq \frac{12}{R} \leq i_{\text{sat}}$$

$$\text{so } R \geq \frac{12}{i_{\text{sat}}} = \frac{12}{2 \cdot 10^{-3}} = 6 \text{ k}\Omega$$

Also


$$i_{02} = -\frac{v_0}{R} = -\frac{4v_1 + 2v_2 - 3v_3}{R}$$

$$|i_{02}| \leq \frac{4|v_1| + 2|v_2| + 3|v_3|}{R} \leq \frac{9}{R} < i_{\text{sat}}$$

$$\text{so } R \geq \frac{9}{i_{\text{sat}}} = \frac{9}{2 \cdot 10^{-3}} = 4.5 \text{ k}\Omega$$

$\therefore R \geq 6 \text{ k}\Omega$ satisfies both constraints.

P6.7-7

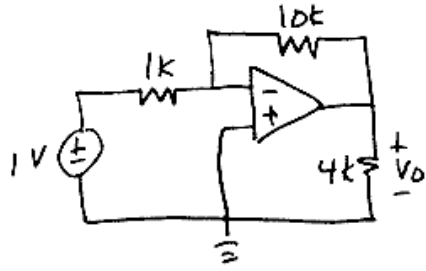


(a) Ideal op amp, KCL

$$\frac{1}{1\text{k}\Omega} + \frac{v_0}{10\text{k}\Omega} = 0$$

$$\underline{v_0 = -10\text{ V}}$$

b) Finite gain op amp

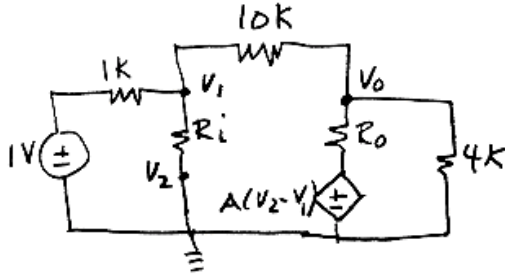

$$A = 10^4, R_i = 200\text{k}\Omega, R_o = 5\text{k}\Omega$$

$$\text{KCL @ } v_1: \frac{1-v_1}{1\text{k}} + \frac{v_0-v_1}{10\text{k}\Omega} - \frac{v_1}{R_i} = 0$$

$$\text{KCL @ } v_0: \frac{v_1-v_0}{10\text{k}\Omega} + \frac{A(v_2-v_1)-v_0}{R_o} - \frac{v_0}{4\text{k}\Omega} = 0$$

$$\text{Solving yields } \underline{v_0 = -10.03\text{ V}}$$



PSpice Problems

SP 6-1

From the PROBE plot shown below

$$v_0 \approx 1 \text{ V when } v_s \approx 0.1 \text{ V}$$

$$\text{Then } i_0 = \frac{v_0}{2000} \approx 0.5 \text{ mA}$$

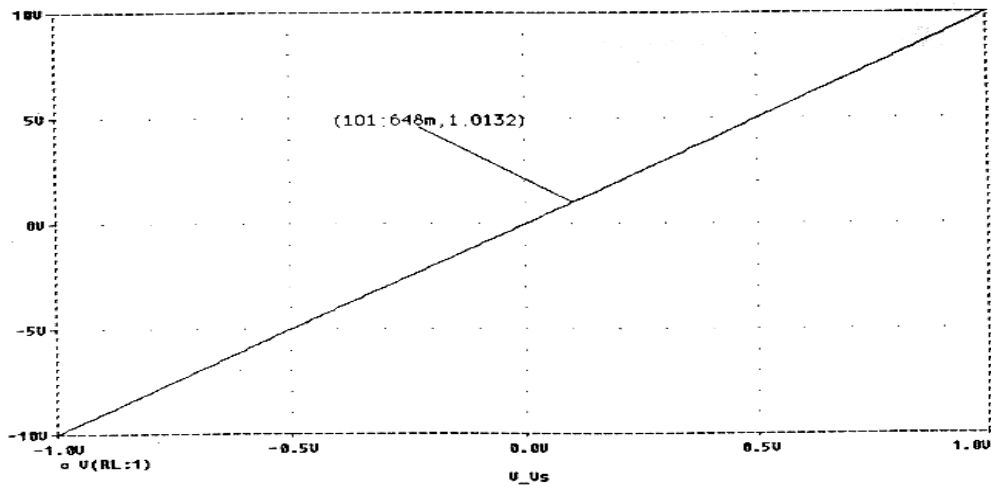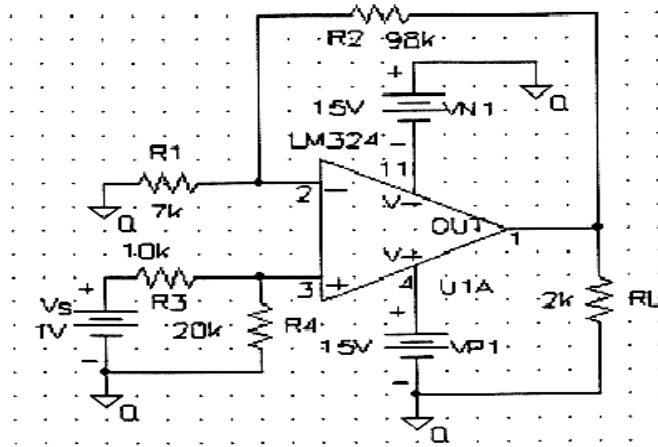


SP 6-2

These PROBE plots indicates that


$$v_0 = -8.0024 \text{ V and}$$

$$i_0 = -2.0006 \text{ mA}$$

Notice that a model of the LM324 op amp was used instead of an ideal op amp

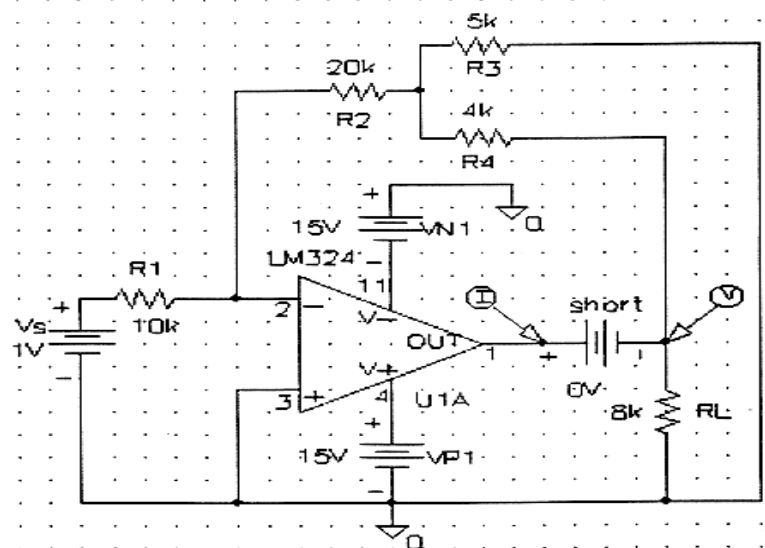

SP 6-2 (continued)

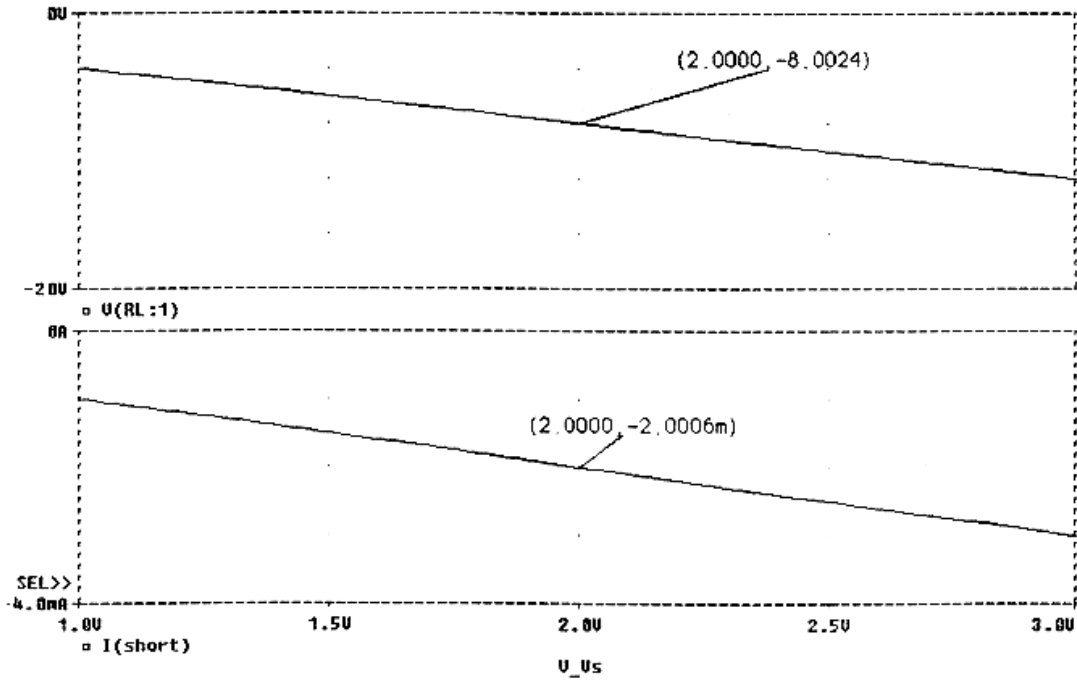


SP 6-3 Spice deck corresponding to SP 6-3

```
R1 1 0 10K
R2 1 5 30K
R3 1 2 10K
R4 1 3 30K
R5 2 4 30K
R6 3 4 10K
VS 2 3 DC 6
RI 4 0 10MEG
XOA1 4 0 5 IDEAL
R7 5 0 30K
```

```
.SUBCKT IDEAL 1 2 3
E 3 0 1 2 -1G
.ENDS IDEAL
.END
```

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(1)	3.0000	(2)	4.5000	(3)	-1.5000
(4)	-12.00E-09	(5)	12.0000		

VOLTAGE SOURCE NAME	CURRENTS
VS	-3.000E-04

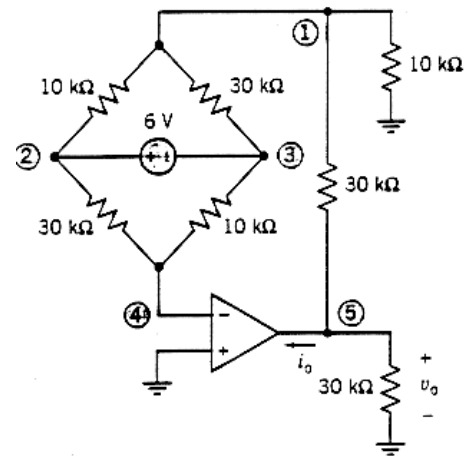


SP 6-4 Spice deck corresponding to Problem SP 6-4(a)

```
V1 1 0 DC .02
R1 1 2 2K
R2 2 0 50K
R3 2 3 10K
R4 3 4 10K
R5 4 0 2K
X0A 1 4 2 3 IDEAL
```

```
.SUBCKT IDEAL 1 2 3
E 3 0 1 2 -1G
.ENDS IDEAL
.END
```

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(1)	.0200	(2)	.5000	(3)	3.0000
(4)	.5000				

```
VOLTAGE SOURCE CURRENTS
NAME          CURRENTS
VS            2.400E-04
```

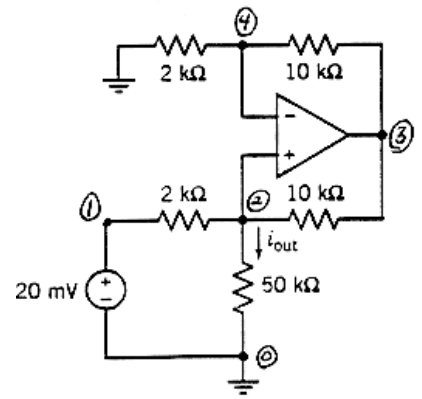

SP 6-4b Spice deck corresponding to Problem SP 6-4(b)

```
VS 1 0 DC .02
R1 1 2 2K
R2 2 0 50K
R3 2 3 10K
R4 3 4 10K
R5 4 0 2K
X0A 1 4 2 3 UA741
```

```
.SUBCKT UA741 1 2 5
IB1 1 0 70nA
IB2 2 0 90nA
VOS 3 2 1mV
RI 1 3 2MEG
E 4 0 1 3 -200000
RO 4 5 75
.ENDS UA741
.END
```


NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(1)	.0200	(2)	.5285	(3)	3.1777
(4)	.5295	(X0A1.3)	.5295	(X0A1.4)	3.2174

```
VOLTAGE SOURCE CURRENTS
NAME          CURRENT
VS            2.543E-04
X0A1.VOS     -8.044E-12
```

SP 6-5 Spice deck corresponding to Problem SP 6-5(a)

```
V1 1 0 DC .02
R1 1 2 2K
R2 2 3 5K
R3 2 0 3.33K
V2 3 0 DC .01
X0A 1 5 2 4 IDEAL
R4 4 5 9K
R5 5 0 1K
```
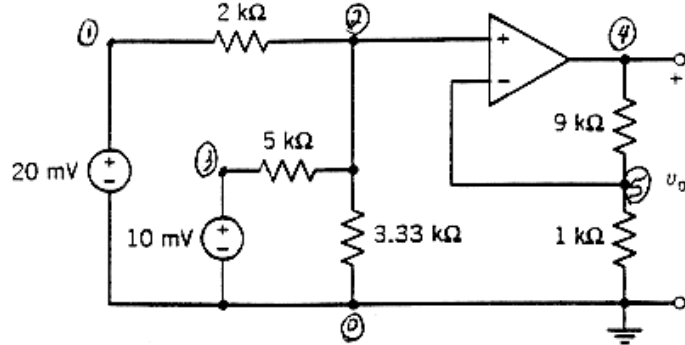
```
.SUBCKT IDEAL 1 2 3
E 3 0 1 2 -1G
.ENDS IDEAL
.END
```



NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(1)	.0200	(2)	.0120	(3)	.0100
(4)	.1200	(5)	.0120		

```
VOLTAGE SOURCE CURRENTS
NAME          CURRENTS
V1            -4.002E-06
V2            3.993E-07
```

SP 6-5 Spice deck corresponding to Problem SP 6-5(b)



```
V1 1 0 DC .02
R1 1 2 2K
R2 2 3 5K
R3 2 0 3.33K
V2 3 0 DC .01
X0A 1 5 2 4 UA741
R4 4 5 9K
R5 5 0 1K
```

```
.SUBCKT UA741 1 2 5
IB1 1 0 70nA
IB2 2 0 90nA
VOS 3 2 1mV
RI 1 3 2MEG
E 4 0 1 3 -200000
RO 4 5 75
.ENDS UA741
.END
```



NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(1)	.0200	(2)	.0119	(3)	.0100
(4)	.1297	(5)	.0129	(X0A1.3)	.0129
(X0A1.4)	.1307				

```
VOLTAGE SOURCE CURRENTS
NAME          CURRENT
V1            -4.047E-06
V2            3.813E-07
X0A1.VOS     -3.267E-13
```



SP 6-6

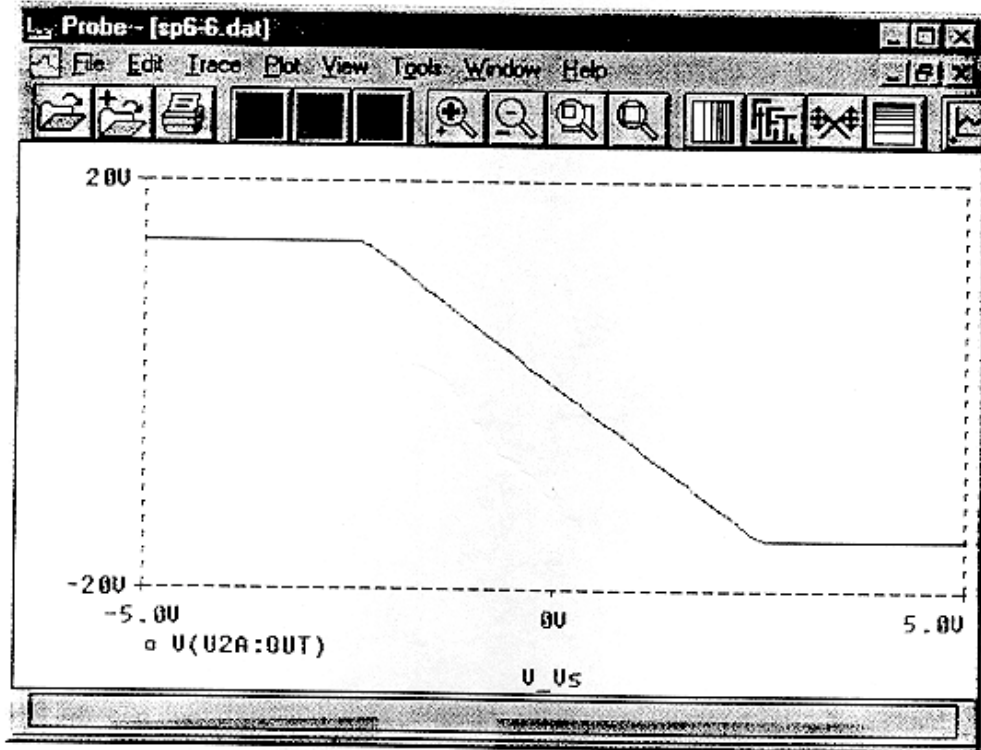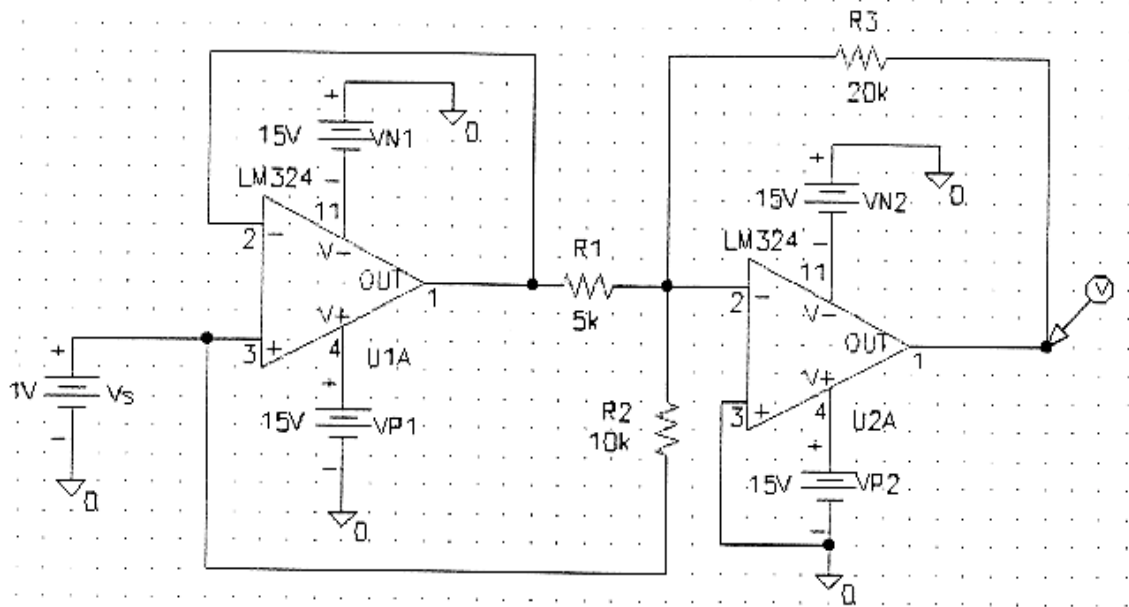

SP 6-7

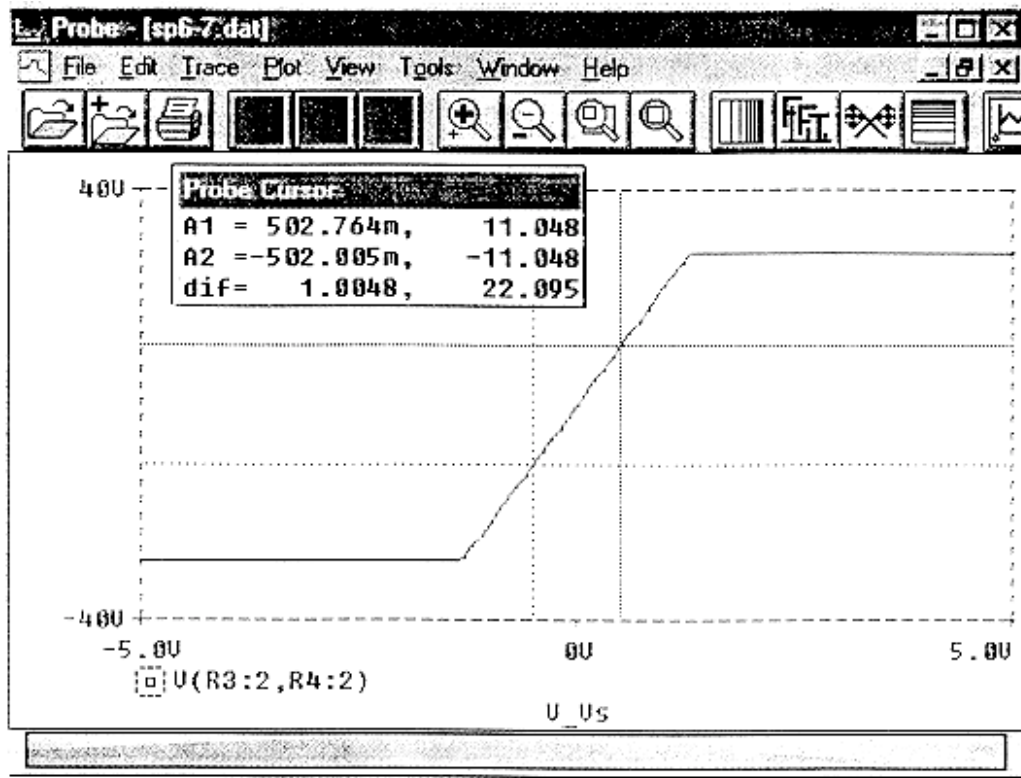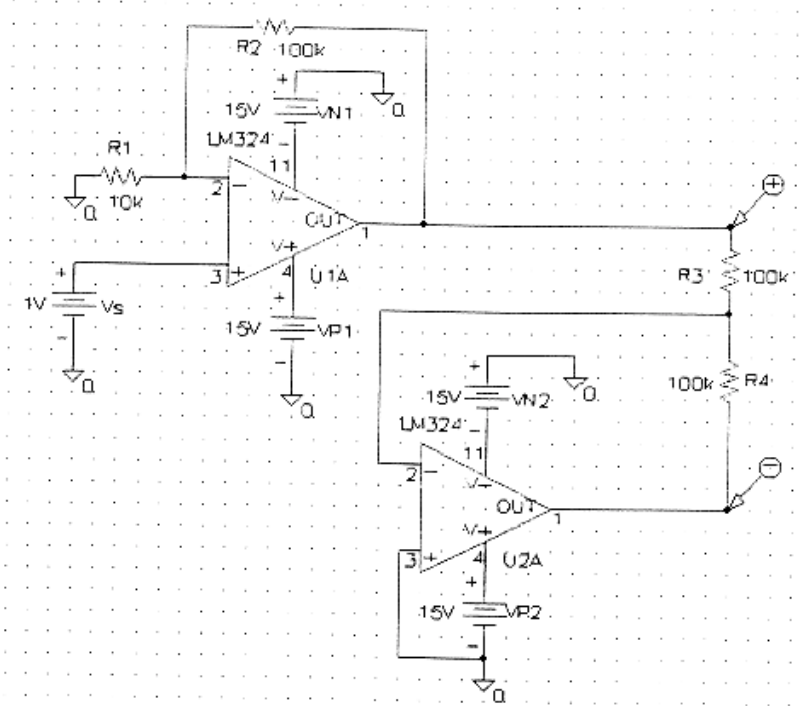


SP 6-8

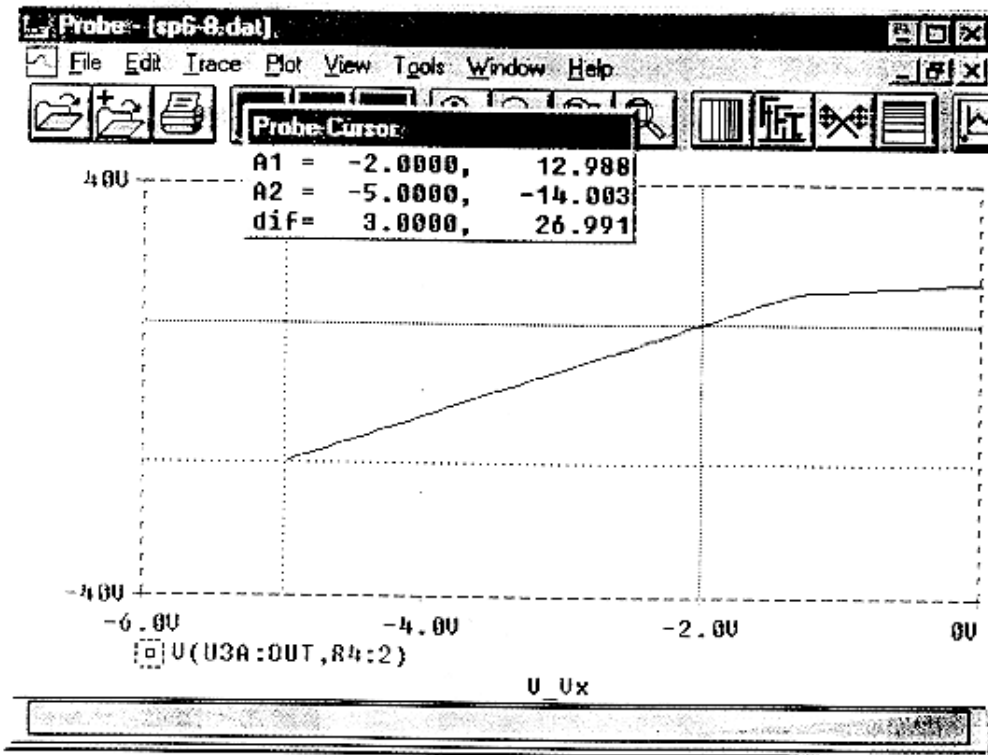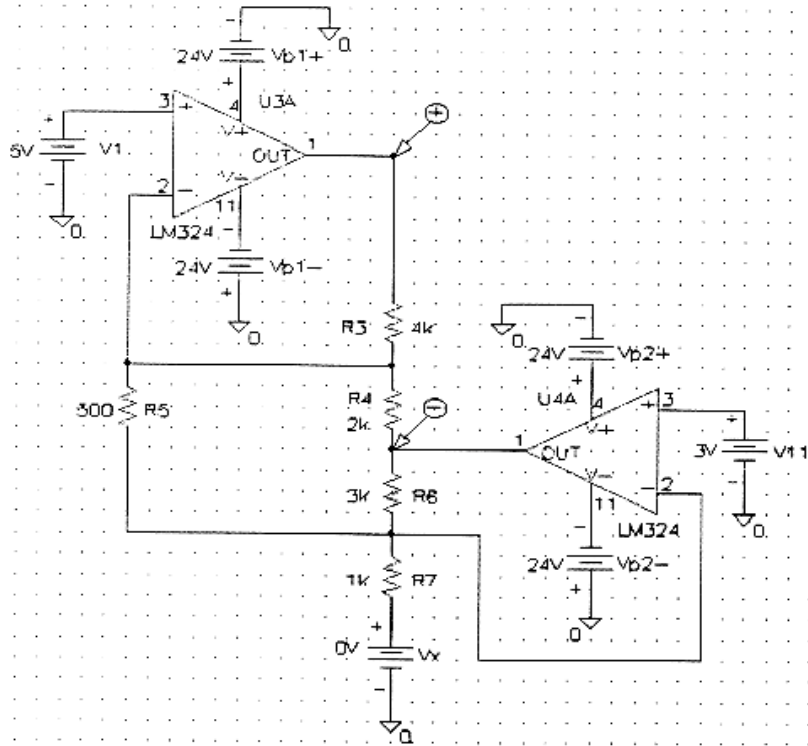

Verification Problems

VP 6-1

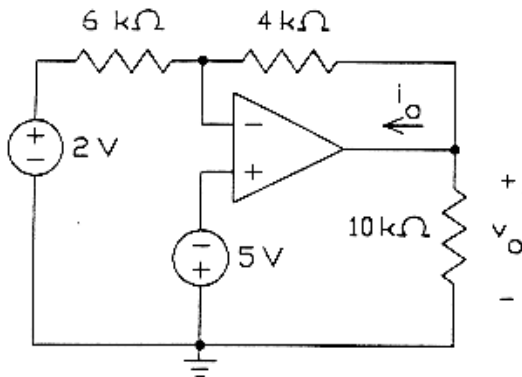

Apply KCL at the output node of the op amp to get


$$i_o + \frac{v_o}{10,000} + \frac{v_o - (-5)}{4000} = 0$$

or, when $v_o = 7$ V and $i_o = -1$ mA,

$$-10^{-3} + \frac{7}{10,000} + \frac{12}{4000} = 2.7 \times 10^{-3} \neq 0$$

KCL is not satisfied, so the analysis cannot be correct.

VP 6-2

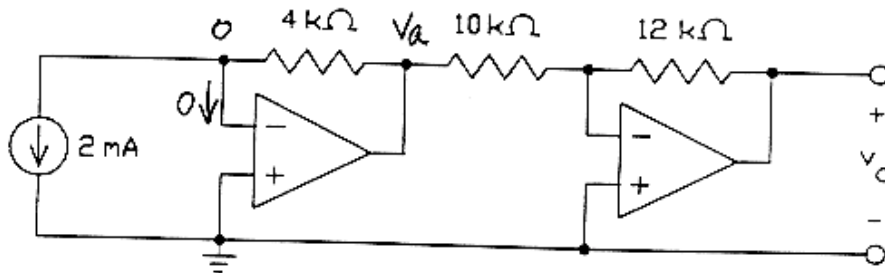

$$v_a = (4 \times 10^3)(2 \times 10^{-3}) = 8 \text{ V}$$

$$v_o = -\frac{12 \times 10^3}{10 \times 10^3} v_a = -1.2(8) = -9.6 \text{ V}$$

So $v_o = -9.6$ V instead of 9.6 V.

VP 6-3

When $v_o = -12$ V, the current in the $4 \text{ k}\Omega$ resistor is

$$i = \frac{-12 - 2}{4000} = -3.5 \text{ mA}$$


Then

$$i = \frac{2 - v_a}{2000}$$

or

$$2 - v_a = 2000(-3.5 \cdot 10^{-3})$$

$$v_a = 2 + 2(3.5) = 9 \text{ V}$$

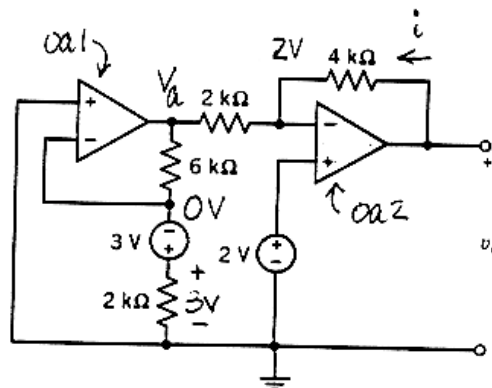

Finally, apply KCL at the inverting node of oa1 to get

$$-\frac{9}{6000} + \frac{3}{2000} = 0$$

Since KCL is satisfied, this analysis appears to be correct.

VP 6-4

First notice that $v_e = v_f = v_e$ is required by the ideal op amp. (There is zero current into the input lead of an ideal op amp so there is zero current in the 10 k Ω connected between nodes e and f, hence zero volts across this resistor. Also, the node voltages at the input nodes of an ideal op amp are equal.)

The node equations at nodes b, c and d are all satisfied by the given voltages:

$$\text{node b: } \frac{0-(-5)}{10000} + \frac{0}{40000} + \frac{0-2}{4000} = 0$$

$$\text{node c: } \frac{0-2}{4000} = \frac{2-5}{6000} + 0$$

$$\text{node d: } \frac{2-5}{6000} = \frac{5}{5000} + \frac{5-11}{4000}$$

Therefore, the analysis is correct.

VP 6-5

The node equations at nodes b and e are satisfied by the given voltages:

$$\text{node b: } \frac{-0.25-2}{20000} + \frac{-0.25}{40000} + \frac{-0.25-(-5)}{40000} = 0$$

$$\text{node e: } \frac{-2.5-(-0.25)}{9000} = \frac{-0.25}{1000} + 0$$

Therefore, the analysis is correct.


Also, the circuit is an noninverting summer with $R_a = 10 \text{ k}\Omega$ and $R_b = 1 \text{ k}\Omega$, $K_1 = 1/2$, $K_2 = 1/4$ and $K_4 = 9$. The given node voltages satisfy the equation

$$-2.5 = v_d = K_4 \left(K_1 v_a + K_2 v_c \right) = 10 \left(\frac{1}{2}(2) + \frac{1}{4}(-5) \right)$$

Again, we see that the analysis is correct.

Design Problems

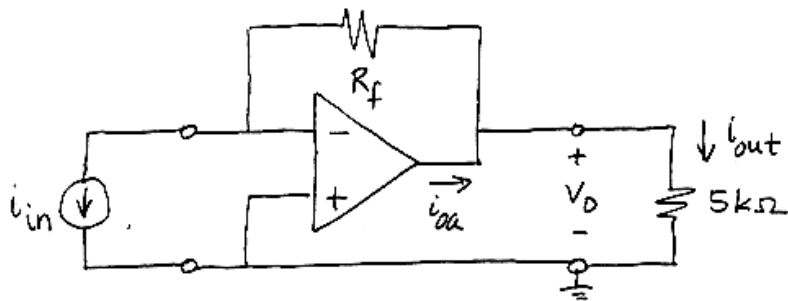DP 6-1 From Figure 6.6-1(g), this circuit



is described by $v_o = R_f i_{in}$. Since $i_{out} = \frac{v_o}{5k\Omega}$


we require $\frac{1}{4} = \frac{i_{out}}{i_{in}} = \frac{R_f}{5k\Omega}$

or $R_f = 1250 \Omega$


Notice that $i_{oa} = i_{in} + \frac{1250 \cdot i_{in}}{5000} = \frac{5}{4} i_{in}$. To avoid current saturation of the op amp $\frac{5}{4} i_{in} < i_{sat}$ or

$i_{in} < \frac{4}{5} i_{sat}$. For example, if $i_{sat} = 2\text{mA}$, then $i_{in} < 1.6\text{mA}$ to avoid current saturation.

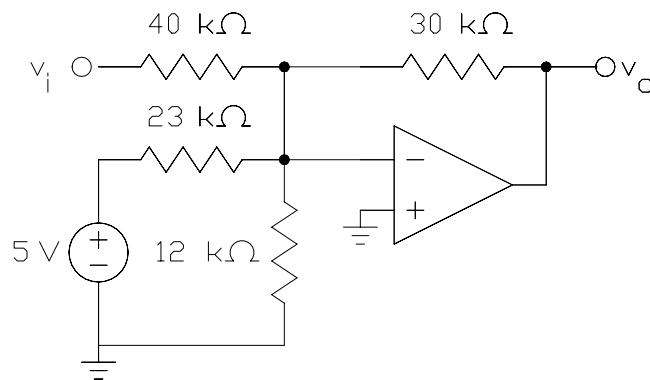
DP 6-2
$$v_o = -\frac{3}{4}v_i + 3 = -\frac{3}{4}v_i + \left(1 + \frac{3}{4}\right)\left(\frac{12}{35}\right)5$$



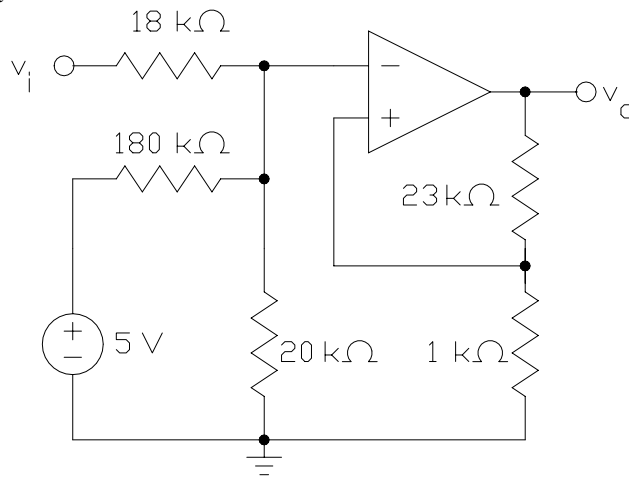
DP 6-3 (a) $12v_i + 6 = 24\left(\frac{1}{2}v_i + \frac{1}{20}(5)\right) \Rightarrow K_4 = 24, K_1 = \frac{1}{2}, \text{ and } K_2 = \frac{1}{20}$. Take $R_a = 18$ $k\Omega$ and $R_b = 1$ $k\Omega$ to get




(b)

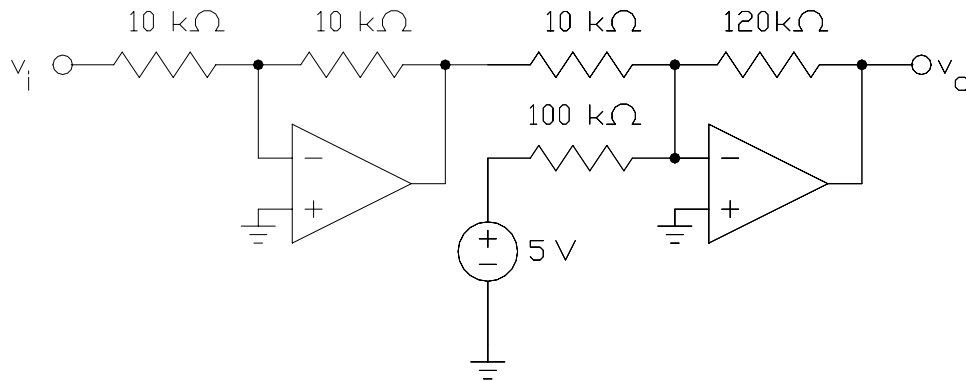


(c)

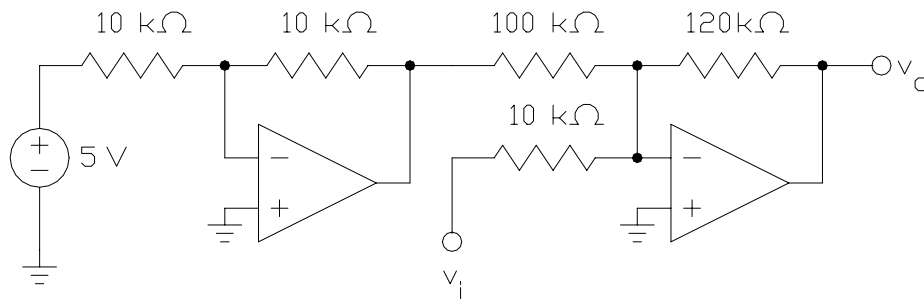

(d)

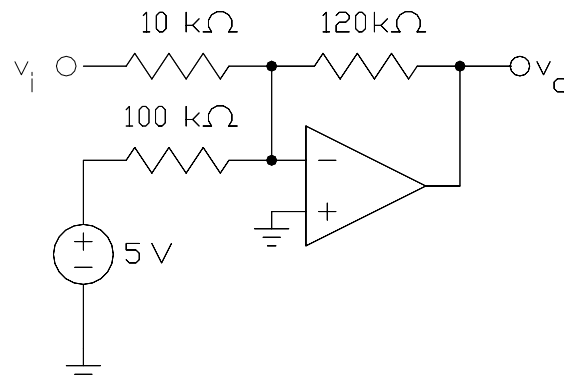


DP6-4

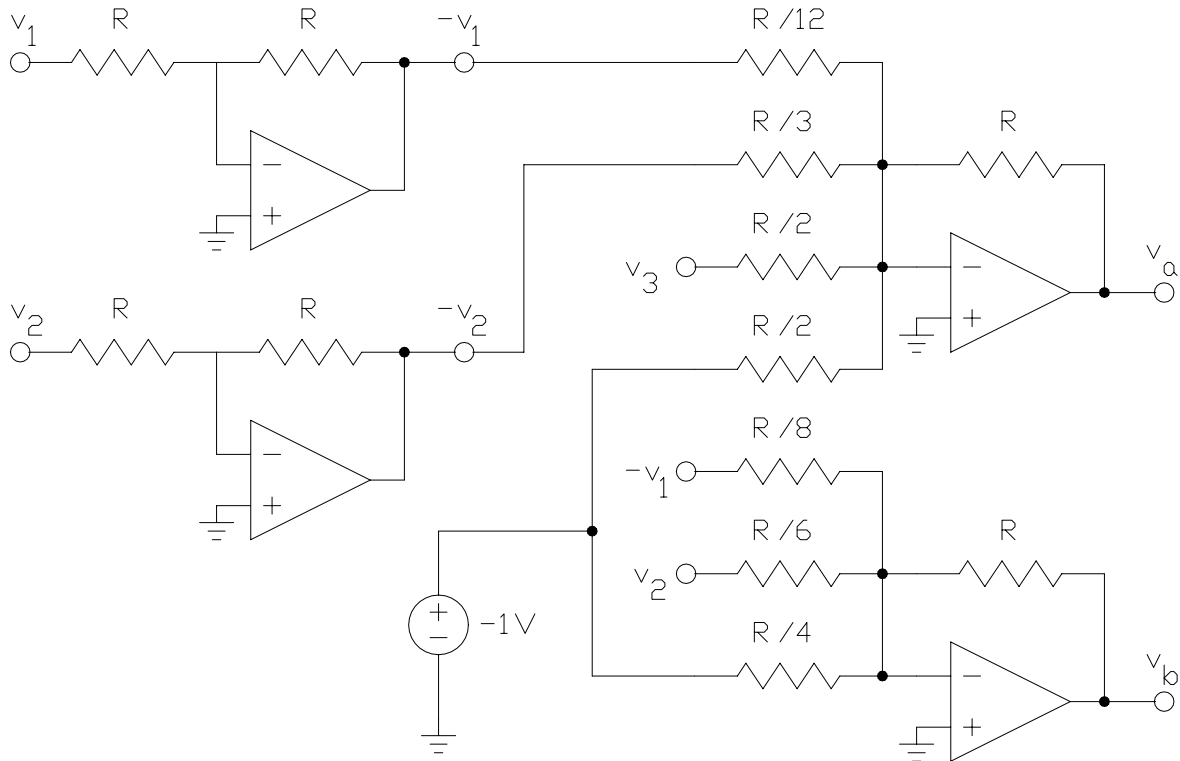

DP 6-5

Need gain $v_o/v_s = \frac{4}{20 \times 10^{-3}} = 200$


Inverting ckt

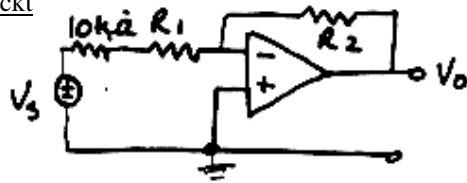

$$\frac{v_o}{v_s} = -\frac{R_2}{R_1 + R_s}$$

Use $R_2 = 2 \text{ M}\Omega$, $R_1 = 0$
 $R_s = 10 \text{ k}\Omega$

Noninverting ckt

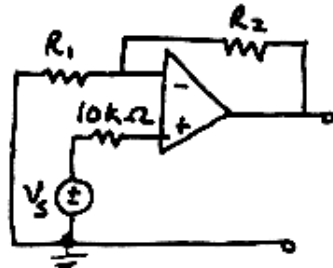

$$\frac{v_o}{v_s} = \left(1 + \frac{R_2}{R_1}\right) v_s$$

$R_{IN} =$ higher for noninverting compared to inverting

Choose $\left(1 + \frac{R_2}{R_1}\right) = 200$ use $R_1 = 1 \text{ k}\Omega$, $R_2 = 199 \text{ k}\Omega$

So use noninverting for higher R_{IN} for microphone.