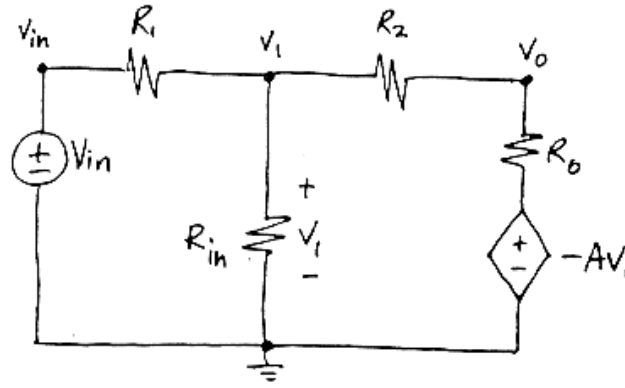


P6.7-3



$$\left. \begin{aligned} \frac{v_1 - v_{in}}{R_1} + \frac{v_1}{R_{in}} + \frac{v_1 - v_0}{R_2} &= 0 \\ \frac{v_0 + Av_1}{R_0} + \frac{v_0 - v_1}{R_2} &= 0 \end{aligned} \right\} \Rightarrow \frac{v_0}{v_{in}} = \frac{R_{in}(R_0 - AR_2)}{(R_1 + R_{in})(R_0 + R_2) + R_1 R_{in}(1 + A)}$$


P6.7-4

a) $\frac{v_0}{v_{in}} = -\frac{R_2}{R_1} = -\frac{49\text{k}\Omega}{5.1\text{k}\Omega} = -9.6078$

b) $\frac{v_0}{v_{in}} = \frac{2\text{M}\Omega(75 - (200,000)(50\text{k}\Omega))}{(5\text{k}\Omega + 2\text{M}\Omega)(75 + 50\text{k}\Omega) + (5\text{k}\Omega)(2\text{M}\Omega)(1 + 200,000)}$
 $= -9.9995$

c) $\frac{v_0}{v_{in}} = \frac{2\text{M}\Omega(75 - (200,000)(49\text{k}\Omega))}{(5.1\text{k}\Omega + 2\text{M}\Omega)(75 + 49\text{k}\Omega) + (5.1\text{k}\Omega)(2\text{M}\Omega)(1 + 200,000)}$
 $= -9.6073$

P6.7-5

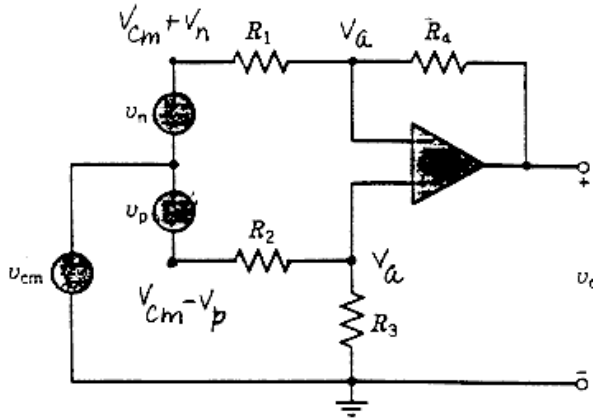

$$v_a = \frac{R_3}{R_2 + R_3}(v_{cm} - v_p)$$

$$\frac{v_a - v_0}{R_4} + \frac{v_a - (v_{cm} + v_n)}{R_1} = 0$$

$$v_0 = -\frac{R_4}{R_1}(v_{cm} + v_n) + \frac{R_4 + R_1}{R_1}v_a$$

$$= -\frac{R_4}{R_1}(v_{cm} + v_n) + \frac{(R_4 + R_1)R_3}{R_1(R_2 + R_3)}(v_{cm} - v_p)$$


when $\frac{R_4}{R_1} = \frac{R_3}{R_2}$ then $\frac{(R_4 + R_1)R_3}{R_1(R_2 + R_3)} = \frac{\frac{R_4 + 1}{R_1} \times R_3}{\frac{R_3 + 1}{R_2}} = \frac{R_4}{R_1}$

so

$$v_0 = -\frac{R_4}{R_1}(v_{cm} + v_n) + \frac{R_4}{R_1}(v_{cm} - v_p) = -\frac{R_4}{R_1}(v_n + v_p)$$


P6.7-6

(a)

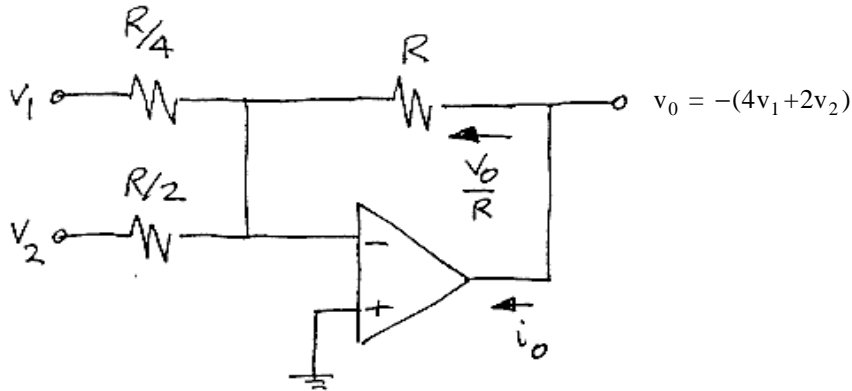

$$|i_0| \leq \frac{4|v_1| + 2|v_2|}{R} \leq \frac{6}{R} < i_{\text{sat}} \quad \text{so } R > \frac{6}{i_{\text{sat}}} = \frac{6}{2 \times 10^{-3}} = 3 \text{ k}\Omega \text{ is required}$$

(b)

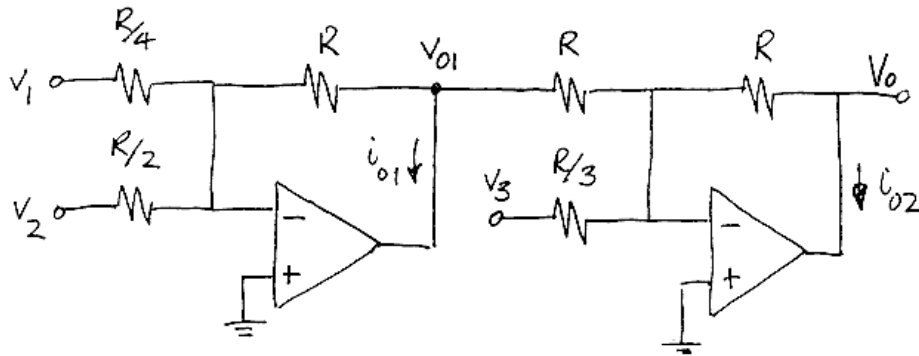

$$v_{01} = -(4v_1 + 2v_2); \quad v_0 = -(v_{01} + 3v_3) = 4v_1 + 2v_2 - 3v_3$$

$$i_{01} = -\frac{v_{01}}{R} - \frac{v_{01}}{R} = -\frac{2v_{01}}{R}$$

$$|i_{01}| \leq \frac{2}{R}(4|v_1| + 2|v_2|) \leq \frac{12}{R} \leq i_{\text{sat}}$$

$$\text{so } R \geq \frac{12}{i_{\text{sat}}} = \frac{12}{2 \cdot 10^{-3}} = 6 \text{ k}\Omega$$

Also


$$i_{02} = -\frac{v_0}{R} = -\frac{4v_1 + 2v_2 - 3v_3}{R}$$

$$|i_{02}| \leq \frac{4|v_1| + 2|v_2| + 3|v_3|}{R} \leq \frac{9}{R} < i_{\text{sat}}$$

$$\text{so } R \geq \frac{9}{i_{\text{sat}}} = \frac{9}{2 \cdot 10^{-3}} = 4.5 \text{ k}\Omega$$

$\therefore R \geq 6 \text{ k}\Omega$ satisfies both constraints.

P6.7-7

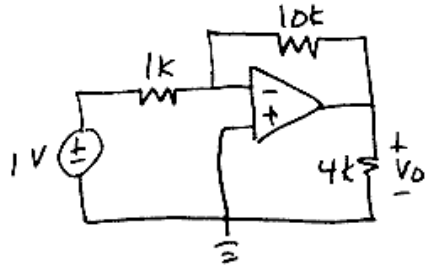


(a) Ideal op amp, KCL

$$\frac{1}{1\text{k}\Omega} + \frac{v_0}{10\text{k}\Omega} = 0$$

$$\underline{v_0 = -10\text{ V}}$$

b) Finite gain op amp

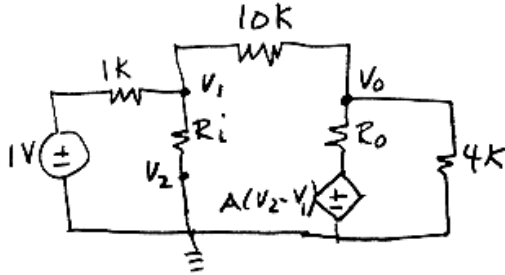

$$A = 10^4, R_i = 200\text{k}\Omega, R_o = 5\text{k}\Omega$$

$$\text{KCL @ } v_1: \frac{1-v_1}{1\text{k}} + \frac{v_0-v_1}{10\text{k}\Omega} - \frac{v_1}{R_i} = 0$$

$$\text{KCL @ } v_0: \frac{v_1-v_0}{10\text{k}\Omega} + \frac{A(v_2-v_1)-v_0}{R_o} - \frac{v_0}{4\text{k}\Omega} = 0$$

Solving yields $\underline{v_0 = -10.03\text{ V}}$



PSpice Problems

SP 6-1

From the PROBE plot shown below

$$v_0 \approx 1 \text{ V when } v_s \approx 0.1 \text{ V}$$

$$\text{Then } i_0 = \frac{v_0}{2000} \approx 0.5 \text{ mA}$$

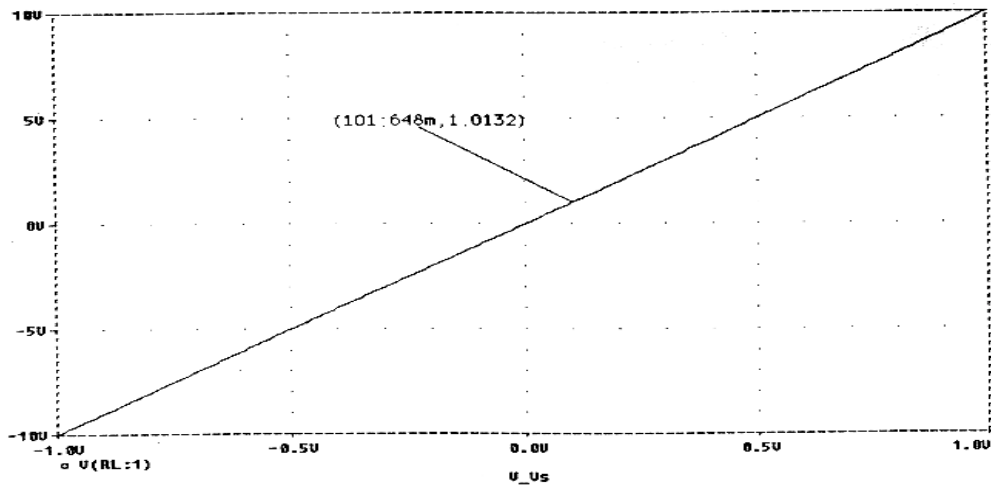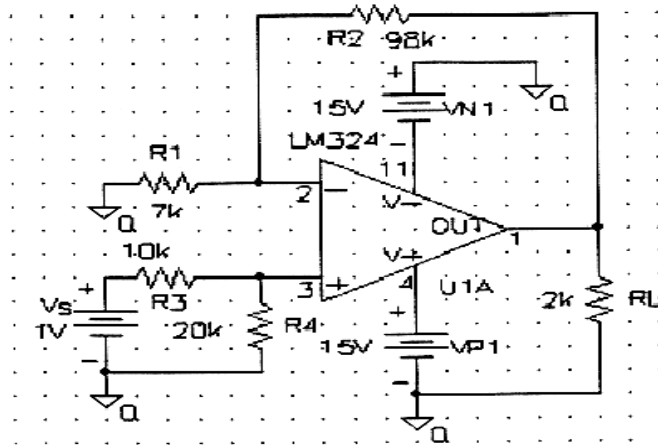


SP 6-2

These PROBE plots indicates that


$$v_0 = -8.0024 \text{ V and}$$

$$i_0 = -2.0006 \text{ mA}$$

Notice that a model of the LM324 op amp was used instead of an ideal op amp

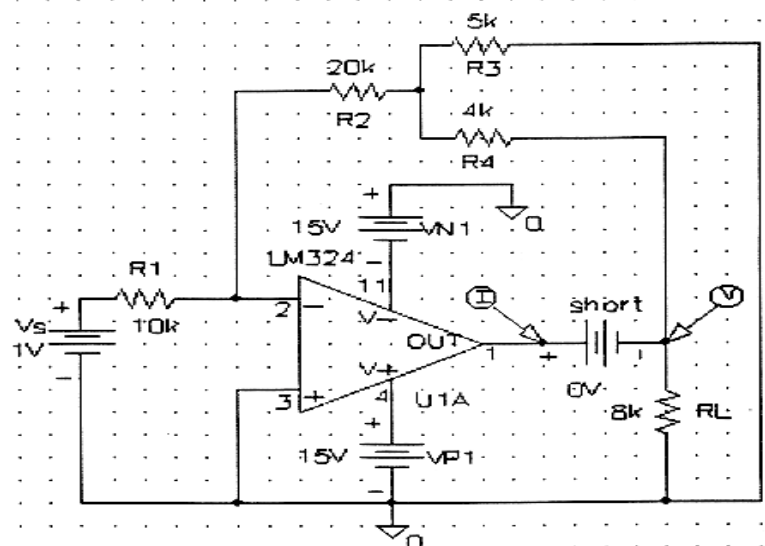


SP 6-2 (continued)

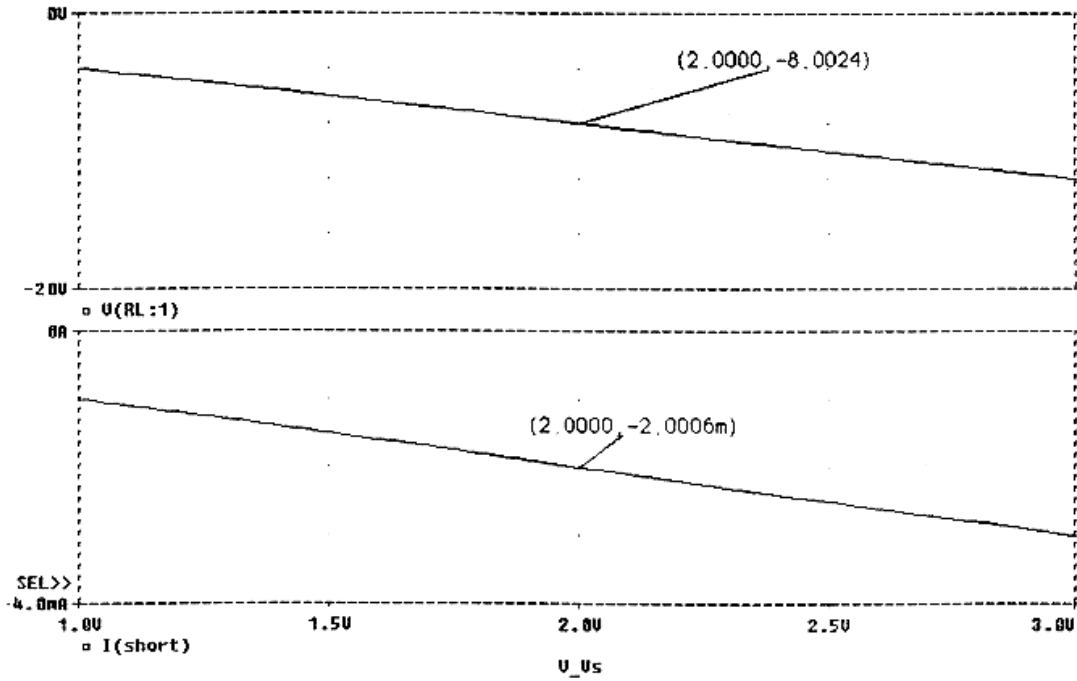

SP 6-3 Spice deck corresponding to SP 6-3

```
R1 1 0 10K
R2 1 5 30K
R3 1 2 10K
R4 1 3 30K
R5 2 4 30K
R6 3 4 10K
VS 2 3 DC 6
RI 4 0 10MEG
XOA1 4 0 5 IDEAL
R7 5 0 30K
```
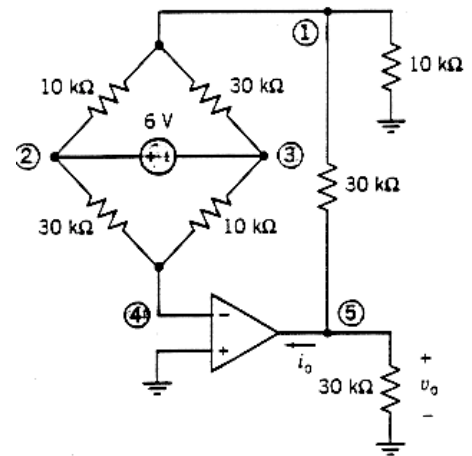
```
.SUBCKT IDEAL 1 2 3
E 3 0 1 2 -1G
.ENDS IDEAL
.END
```



NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(1)	3.0000	(2)	4.5000	(3)	-1.5000
(4)	-12.00E-09	(5)	12.0000		

```
VOLTAGE SOURCE CURRENTS
NAME          CURRENTS
VS            -3.000E-04
```


SP 6-4 Spice deck corresponding to Problem SP 6-4(a)

```
V1 1 0 DC .02
R1 1 2 2K
R2 2 0 50K
R3 2 3 10K
R4 3 4 10K
R5 4 0 2K
X0A 1 4 2 3 IDEAL
```

```
.SUBCKT IDEAL 1 2 3
E 3 0 1 2 -1G
.ENDS IDEAL
.END
```

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(1)	.0200	(2)	.5000	(3)	3.0000
(4)	.5000				

```
VOLTAGE SOURCE CURRENTS
NAME          CURRENTS
VS            2.400E-04
```

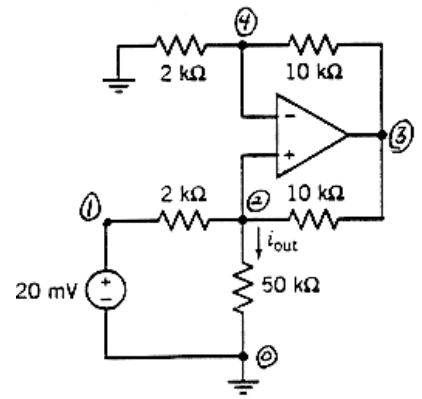

SP 6-4b Spice deck corresponding to Problem SP 6-4(b)

```
VS 1 0 DC .02
R1 1 2 2K
R2 2 0 50K
R3 2 3 10K
R4 3 4 10K
R5 4 0 2K
X0A 1 4 2 3 UA741
```

```
.SUBCKT UA741 1 2 5
IB1 1 0 70nA
IB2 2 0 90nA
VOS 3 2 1mV
RI 1 3 2MEG
E 4 0 1 3 -200000
RO 4 5 75
.ENDS UA741
.END
```


NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(1)	.0200	(2)	.5285	(3)	3.1777
(4)	.5295	(X0A1.3)	.5295	(X0A1.4)	3.2174

```
VOLTAGE SOURCE CURRENTS
NAME          CURRENT
VS            2.543E-04
X0A1.VOS     -8.044E-12
```

SP 6-5 Spice deck corresponding to Problem SP 6-5(a)

```
V1 1 0 DC .02
R1 1 2 2K
R2 2 3 5K
R3 2 0 3.33K
V2 3 0 DC .01
X0A 1 5 2 4 IDEAL
R4 4 5 9K
R5 5 0 1K
```
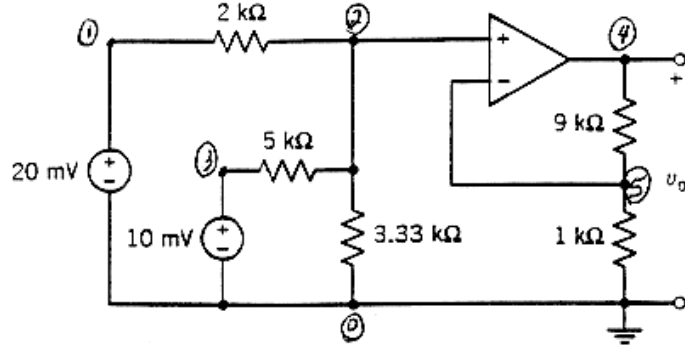
```
.SUBCKT IDEAL 1 2 3
E 3 0 1 2 -1G
.ENDS IDEAL
.END
```



NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(1)	.0200	(2)	.0120	(3)	.0100
(4)	.1200	(5)	.0120		

```
VOLTAGE SOURCE CURRENTS
NAME          CURRENTS
V1            -4.002E-06
V2            3.993E-07
```

SP 6-5 Spice deck corresponding to Problem SP 6-5(b)



```
V1 1 0 DC .02
R1 1 2 2K
R2 2 3 5K
R3 2 0 3.33K
V2 3 0 DC .01
X0A 1 5 2 4 UA741
R4 4 5 9K
R5 5 0 1K
```

```
.SUBCKT UA741 1 2 5
IB1 1 0 70nA
IB2 2 0 90nA
VOS 3 2 1mV
RI 1 3 2MEG
E 4 0 1 3 -200000
RO 4 5 75
.ENDS UA741
.END
```



NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(1)	.0200	(2)	.0119	(3)	.0100
(4)	.1297	(5)	.0129	(X0A1.3)	.0129
(X0A1.4)	.1307				

```
VOLTAGE SOURCE CURRENTS
NAME          CURRENT
V1            -4.047E-06
V2            3.813E-07
X0A1.VOS     -3.267E-13
```



SP 6-6

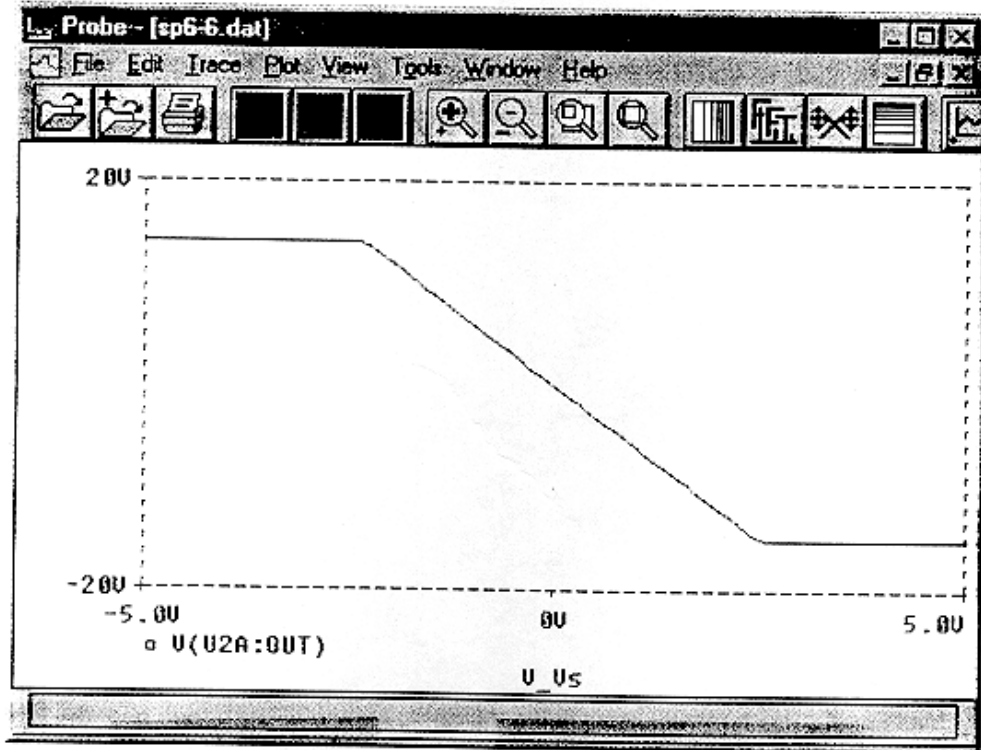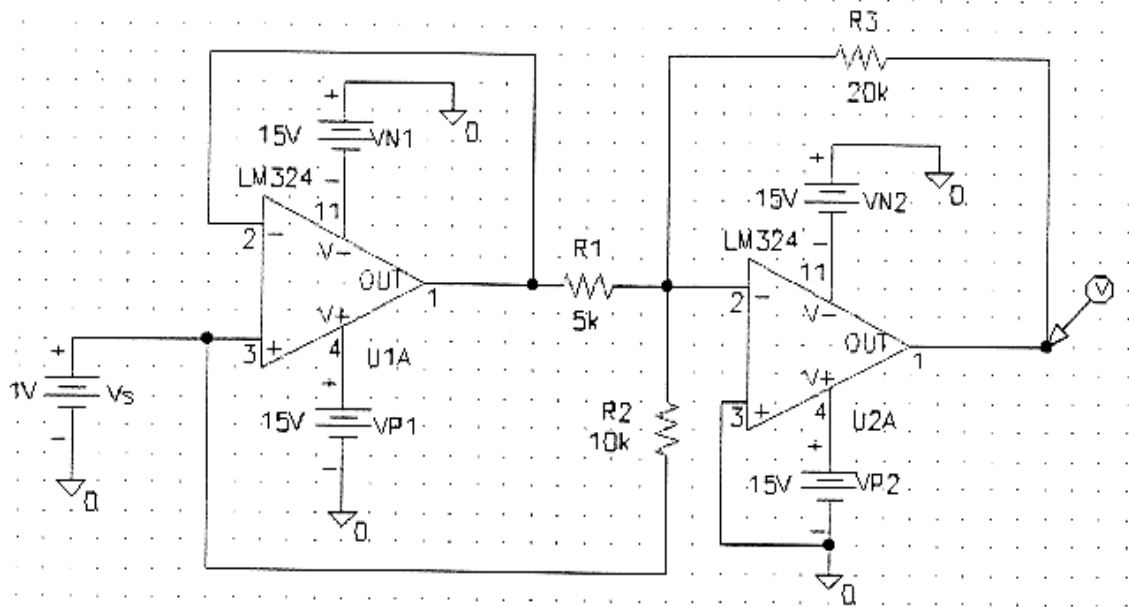

SP 6-7

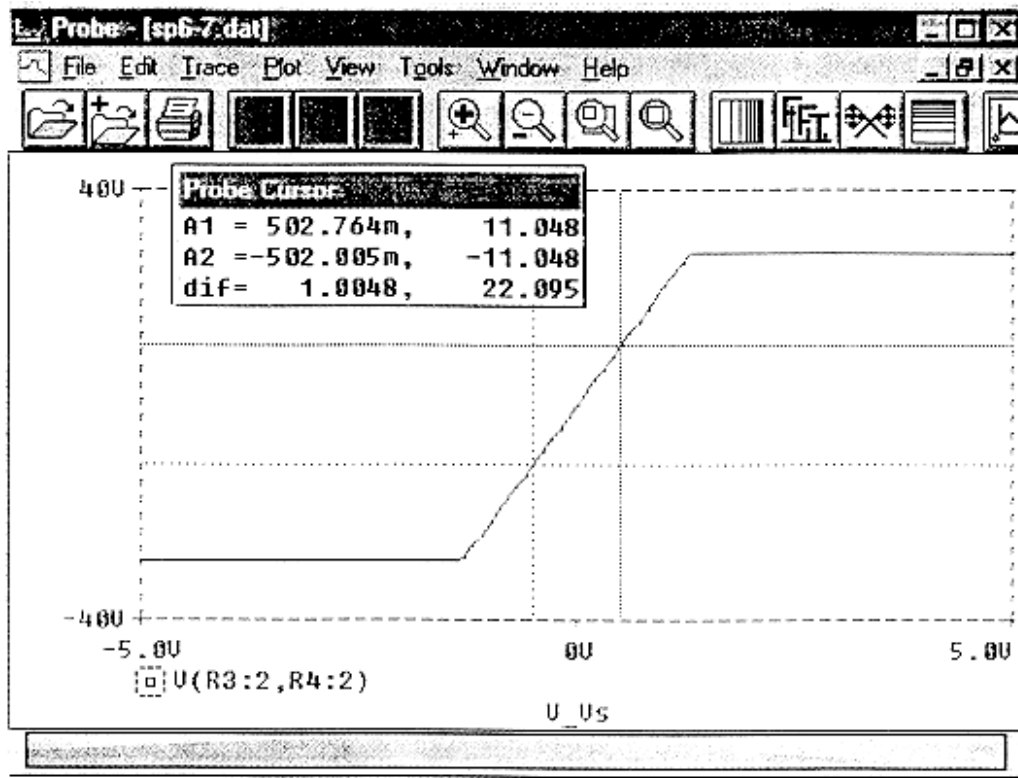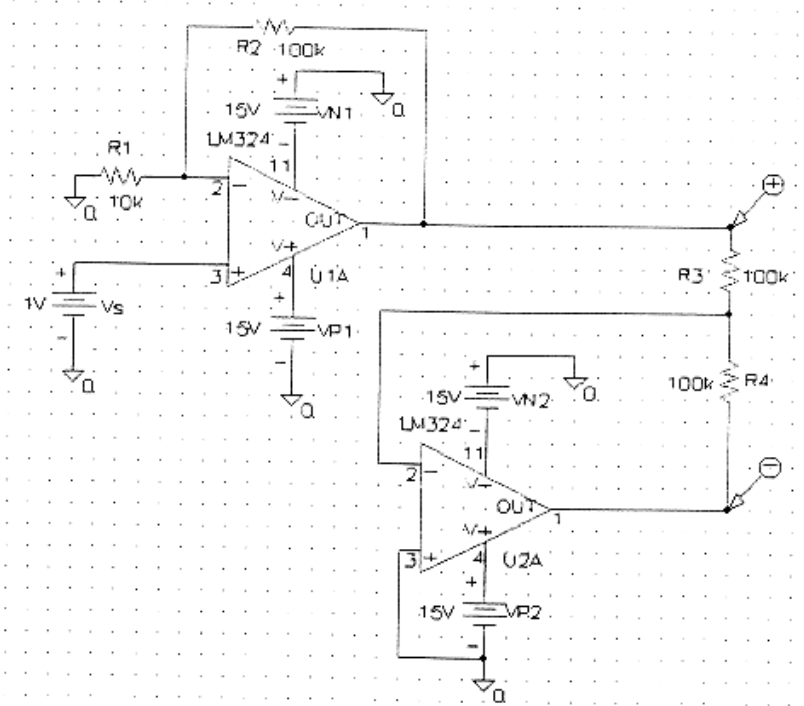


SP 6-8

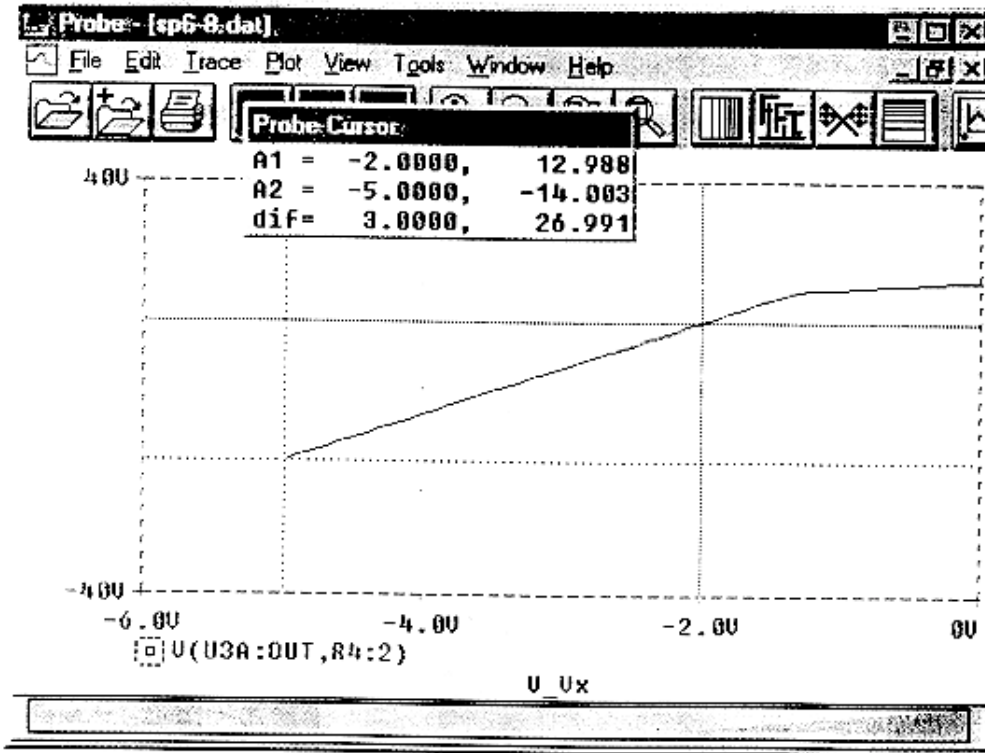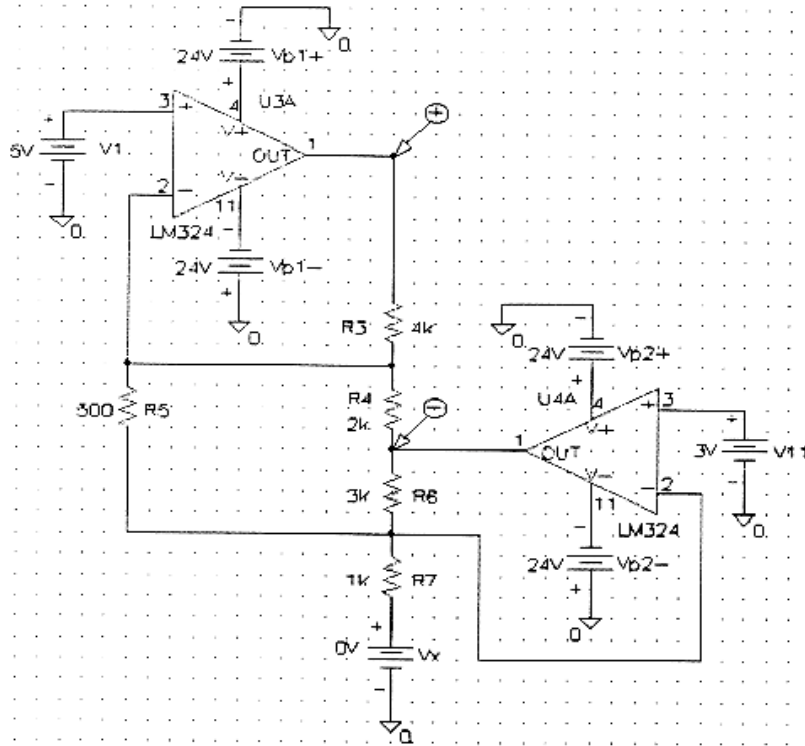

Verification Problems

VP 6-1

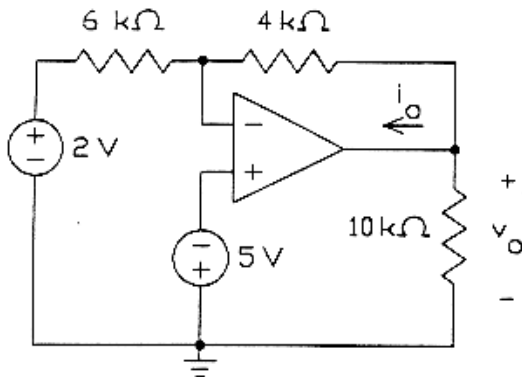

Apply KCL at the output node of the op amp to get


$$i_o + \frac{v_o}{10,000} + \frac{v_o - (-5)}{4000} = 0$$

or, when $v_o = 7$ V and $i_o = -1$ mA,

$$-10^{-3} + \frac{7}{10,000} + \frac{12}{4000} = 2.7 \times 10^{-3} \neq 0$$

KCL is not satisfied, so the analysis cannot be correct.

VP 6-2

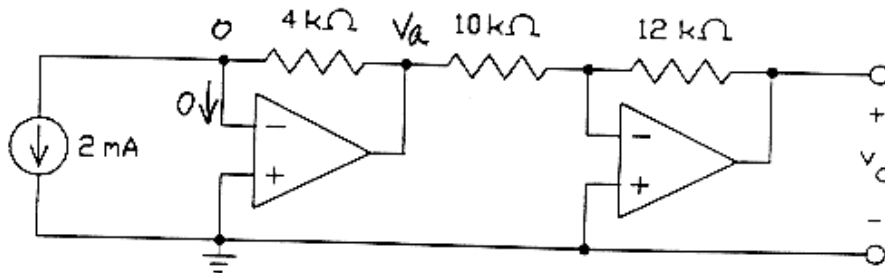

$$v_a = (4 \times 10^3)(2 \times 10^{-3}) = 8 \text{ V}$$

$$v_o = -\frac{12 \times 10^3}{10 \times 10^3} v_a = -1.2(8) = -9.6 \text{ V}$$

So $v_o = -9.6$ V instead of 9.6 V.

VP 6-3

When $v_o = -12$ V, the current in the $4 \text{ k}\Omega$ resistor is

$$i = \frac{-12 - 2}{4000} = -3.5 \text{ mA}$$


Then

$$i = \frac{2 - v_a}{2000}$$

or

$$2 - v_a = 2000(-3.5 \times 10^{-3})$$

$$v_a = 2 + 2(3.5) = 9 \text{ V}$$

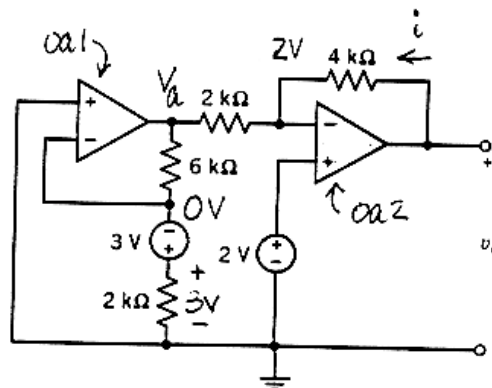

Finally, apply KCL at the inverting node of oal to get

$$-\frac{9}{6000} + \frac{3}{2000} = 0$$

Since KCL is satisfied, this analysis appears to be correct.

VP 6-4

First notice that $v_e = v_f = v_e$ is required by the ideal op amp. (There is zero current into the input lead of an ideal op amp so there is zero current in the 10 k Ω connected between nodes e and f, hence zero volts across this resistor. Also, the node voltages at the input nodes of an ideal op amp are equal.)

The node equations at nodes b, c and d are all satisfied by the given voltages:

$$\text{node b: } \frac{0-(-5)}{10000} + \frac{0}{40000} + \frac{0-2}{4000} = 0$$

$$\text{node c: } \frac{0-2}{4000} = \frac{2-5}{6000} + 0$$

$$\text{node d: } \frac{2-5}{6000} = \frac{5}{5000} + \frac{5-11}{4000}$$

Therefore, the analysis is correct.

VP 6-5

The node equations at nodes b and e are satisfied by the given voltages:

$$\text{node b: } \frac{-0.25-2}{20000} + \frac{-0.25}{40000} + \frac{-0.25-(-5)}{40000} = 0$$

$$\text{node e: } \frac{-2.5-(-0.25)}{9000} = \frac{-0.25}{1000} + 0$$

Therefore, the analysis is correct.


Also, the circuit is an noninverting summer with $R_a = 10 \text{ k}\Omega$ and $R_b = 1 \text{ k}\Omega$, $K_1 = 1/2$, $K_2 = 1/4$ and $K_4 = 9$. The given node voltages satisfy the equation

$$-2.5 = v_d = K_4 (K_1 v_a + K_2 v_c) = 10 \left(\frac{1}{2}(2) + \frac{1}{4}(-5) \right)$$

Again, we see that the analysis is correct.

Design Problems

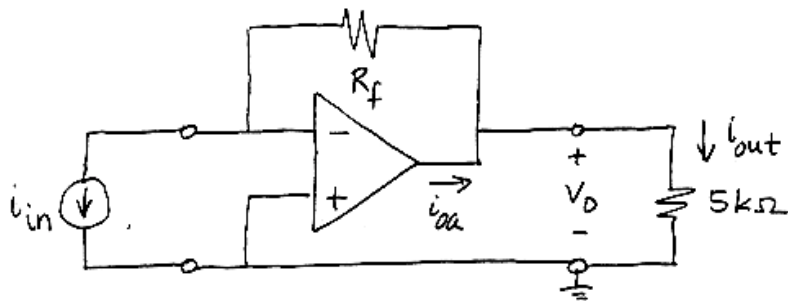DP 6-1 From Figure 6.6-1(g), this circuit



is described by $v_o = R_f i_{in}$. Since $i_{out} = \frac{v_o}{5k\Omega}$


we require $\frac{1}{4} = \frac{i_{out}}{i_{in}} = \frac{R_f}{5k\Omega}$

or $R_f = 1250 \Omega$


Notice that $i_{oa} = i_{in} + \frac{1250 \cdot i_{in}}{5000} = \frac{5}{4} i_{in}$. To avoid current saturation of the op amp $\frac{5}{4} i_{in} < i_{sat}$ or

$i_{in} < \frac{4}{5} i_{sat}$. For example, if $i_{sat} = 2\text{mA}$, then $i_{in} < 1.6\text{mA}$ to avoid current saturation.

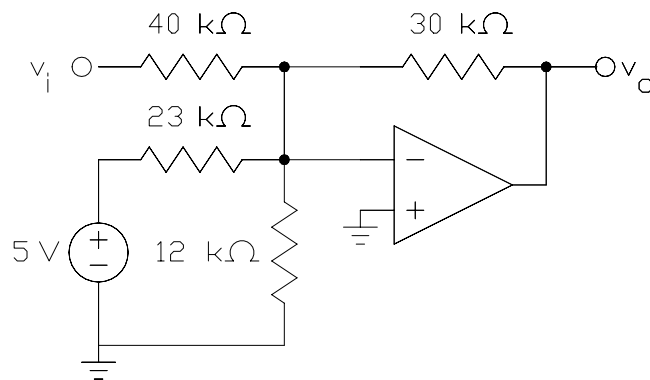
DP 6-2
$$v_o = -\frac{3}{4}v_i + 3 = -\frac{3}{4}v_i + \left(1 + \frac{3}{4}\right)\left(\frac{12}{35}\right)5$$



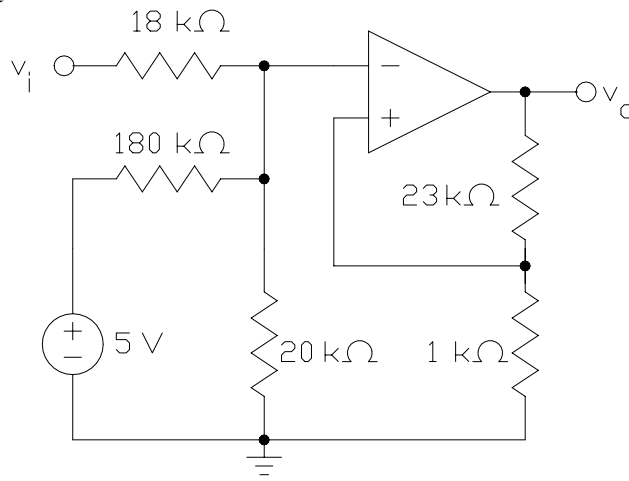
DP 6-3 (a) $12v_i + 6 = 24\left(\frac{1}{2}v_i + \frac{1}{20}(5)\right) \Rightarrow K_4 = 24, K_1 = \frac{1}{2}, \text{ and } K_2 = \frac{1}{20}$. Take $R_a = 18$ $k\Omega$ and $R_b = 1$ $k\Omega$ to get




(b)

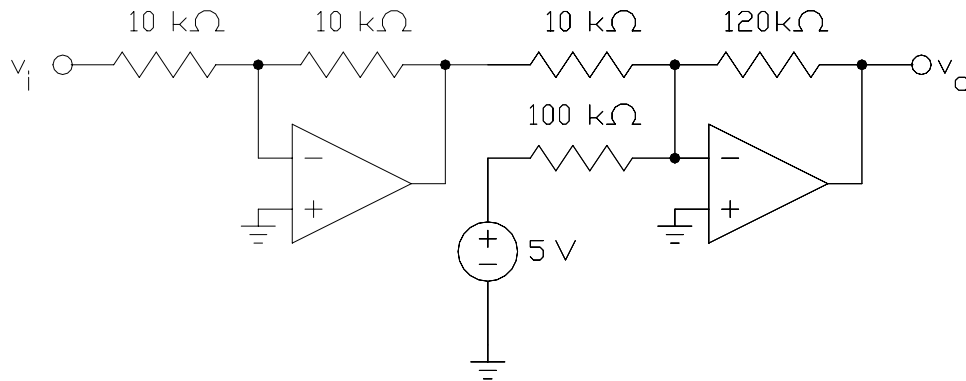


(c)

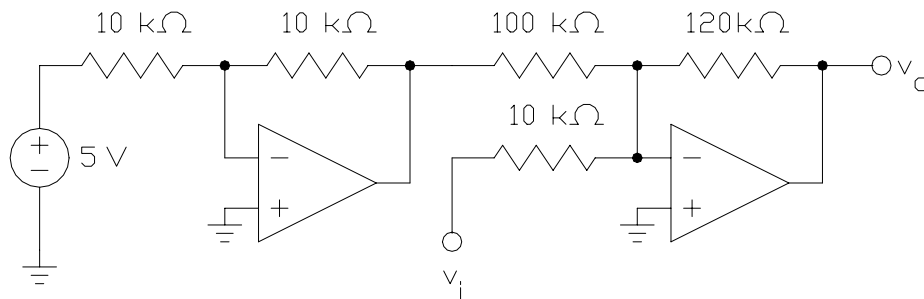

(d)

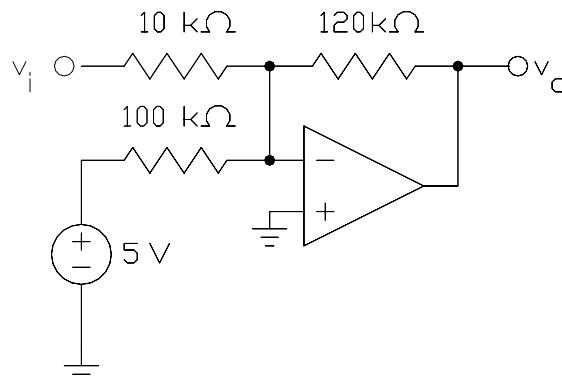


DP6-4

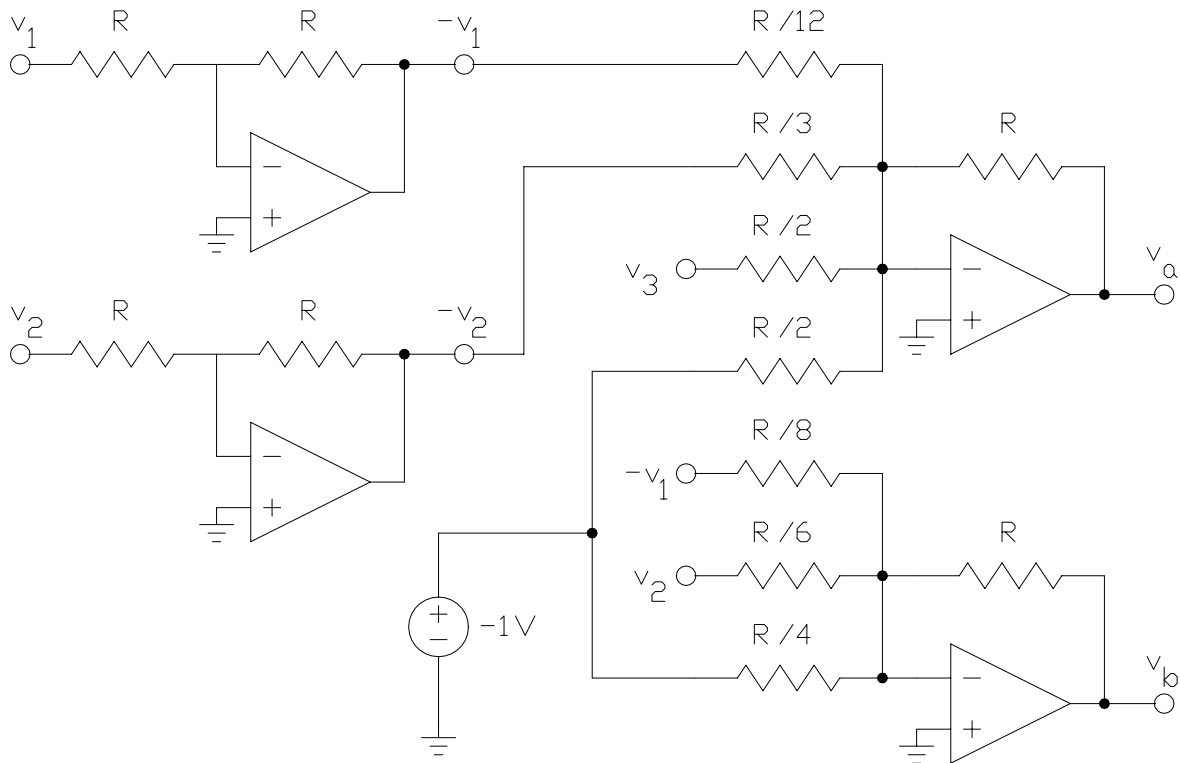

DP 6-5

Need gain $v_o/v_s = \frac{4}{20 \times 10^{-3}} = 200$


Inverting ckt

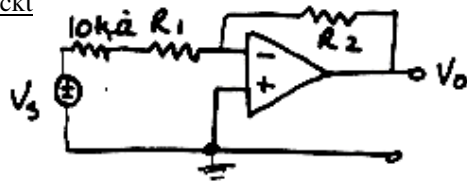

$$\frac{v_o}{v_s} = -\frac{R_2}{R_1 + R_s}$$

Use $R_2 = 2 \text{ M}\Omega$, $R_1 = 0$
 $R_s = 10 \text{ k}\Omega$

Noninverting ckt

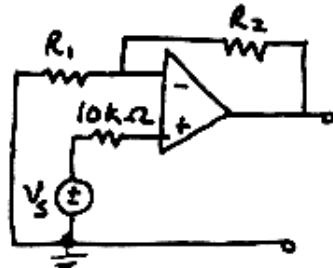

$$\frac{v_o}{v_s} = \left(1 + \frac{R_2}{R_1}\right) v_s$$

$R_{IN} =$ higher for noninverting compared to inverting

Choose $\left(1 + \frac{R_2}{R_1}\right) = 200$ use $R_1 = 1 \text{ k}\Omega$, $R_2 = 199 \text{ k}\Omega$

So use noninverting for higher R_{IN} for microphone.