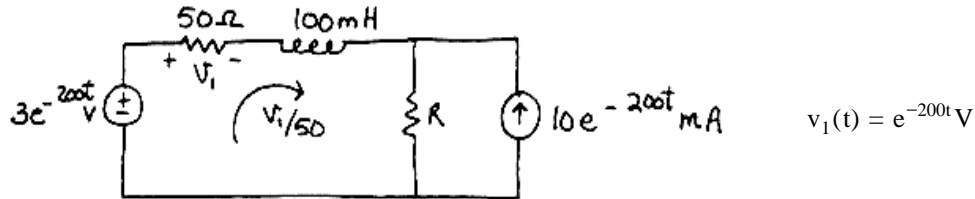


P7.6-7



$$\begin{aligned} \text{KVL a: } -3e^{-200t} + v_1 + .1 \frac{d}{dt} \left(\frac{v_1}{50} \right) + R \left[\frac{v_1}{50} + .01e^{-200t} \right] &= 0 \\ -3e^{-200t} + e^{-200t} - .4e^{-200t} + R \left[\frac{1}{50} + .01 \right] e^{-200t} &= 0 \\ -2.4 + R(.03) = 0 \Rightarrow R = \frac{2.4}{.03} = 80\Omega \end{aligned}$$

P 7.6-8

$$(a) v(t) = L \frac{d}{dt} i(t) = \begin{cases} 0 & 0 < t < 2 \\ 0.1 & 2 < t < 6 \\ 0 & 6 < t \end{cases}$$

$$(b) i(t) = \frac{1}{L} \int_0^t v(\tau) d\tau + i(0) = 2 \int_0^t v(\tau) d\tau$$

$$\text{For } 0 < t < 2, v(t) = 0 \text{ V so } i(t) = 2 \int_0^t 0 d\tau + 0 = 0 \text{ A}$$

For $2 < t < 6$, $v(t) = 0.2t - 0.4$ V so

$$i(t) = 2 \int_0^t (0.2\tau - 0.4) d\tau + 0 = (0.2\tau^2 - 0.8\tau) \Big|_0^t = 0.2t^2 - 0.8t + 0.8 \text{ A}$$

$$i(6) = 0.2(6^2) - 0.8(6) + 0.8 = 3.2 \text{ A.}$$

$$\text{For } 6 < t, v(t) = 0.8 \text{ V so } i(t) = 2 \int_0^t 0.8 d\tau + 3.2 = 1.6t - 6.4 \text{ A}$$

Section 7-7: Energy Storage in an Inductor

P7.7-1

$$v(t) = 100 \cdot 10^{-3} \frac{d}{dt} i(t) = \begin{cases} 0 & t < 0 \\ 0.4 & 0 < t < 1 \\ 0 & t > 1 \end{cases}$$

$$p(t) = v(t) i(t) = \begin{cases} 0 & t < 0 \\ 1.6t & 0 < t < 1 \\ 0 & t > 1 \end{cases}$$

$$W(t) = \int_0^t p(\tau) d\tau = \begin{cases} 0 & t < 0 \\ 0.8t^2 & 0 < t < 1 \\ 0.8 & t > 1 \end{cases}$$

P7.7-2

$$p(t) = v(t) i(t) = \left[5 \frac{d}{dt} (4 \sin 2t) \right] (4 \sin 2t) = 5 (8 \cos 2t) (4 \sin 2t)$$

$$= 80 [2 \cos 2t \sin 2t] = 80 [\sin(2t+2t) + \sin(2t-2t)] = 80 \sin 4t \text{ W}$$

$$w(t) = \int_0^t p(\tau) d\tau = 80 \int_0^t \sin 4\tau d\tau = -\frac{80}{4} [\cos 4\tau]_0^t = 20 (1 - \cos 4t)$$

P7.7-3

$$i(t) = \frac{1}{25 \cdot 10^{-3}} \int_0^t 6 \cos 100\tau d\tau + 0 = \frac{6}{(25 \cdot 10^{-3})(100)} [\sin 100\tau]_0^t = 2.4 \sin 100t$$

$$p(t) = v(t) i(t) = (6 \cos 100t)(2.4 \sin 100t) = 7.2 [2(\cos 100t)(\sin 100t)] = 7.2 [\sin 200t + \sin 0] = 7.2 \sin 200t$$

$$W(t) = \int_0^t p(\tau) d\tau = 7.2 \int_0^t \sin 200\tau d\tau = -\frac{7.2}{200} [\cos 200\tau]_0^t = 0.036 [1 - \cos 200t] \text{ J} = 36 [1 - \cos 200t] \text{ mJ}$$

Section 7-8: Series and Parallel Inductors**P7.8-1**

$$6\text{H} \parallel 3\text{H} = \frac{6\text{H} \cdot 3\text{H}}{6\text{H} + 3\text{H}} = 2\text{H}$$

$$2\text{H} + 2\text{H} = 4\text{H}$$

$$i(t) = \frac{1}{4} \int_0^t 6 \cos 100\tau d\tau = \frac{6}{4 \cdot 100} [\sin 100\tau]_0^t = 15 \sin 100t \text{ mA}$$

P7.8-2

$$4\text{mH} + 4\text{mH} = 8\text{mH}$$

$$8\text{mH} \parallel 8\text{mH} = \frac{8\text{mH} \cdot 8\text{mH}}{8\text{mH} + 8\text{mH}} = 4\text{mH}$$

$$4\text{mH} + 4\text{mH} = 8\text{mH}$$

$$v(t) = (8 \cdot 10^{-3}) \frac{d}{dt} (5 + 3e^{-250t})(10^{-3}) = (8 \cdot 10^{-6})(0 + 3(-250)e^{-250t}) = -6e^{-250t} \text{ mV}$$

P7.8-3

$$L \parallel L = \frac{L \cdot L}{L + L} = \frac{L}{2}$$



$$L + L + \frac{L}{2} = \frac{5}{2} L$$

$$25 \cos 250t = \frac{5}{2} L \frac{d}{dt} (14 \cdot 10^{-3} \sin 250t) = \left(\frac{5}{2} L \right) (14 \cdot 10^{-3})(250) \cos 250t$$



$$\text{so } L = \frac{25}{\frac{5}{2}(14 \cdot 10^{-3})(250)} = 2.86 \text{ H}$$

Section 7-9: Initial Conditions of Switched Circuits



P7.9-1

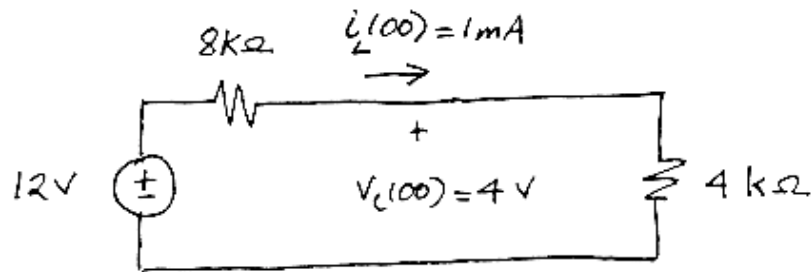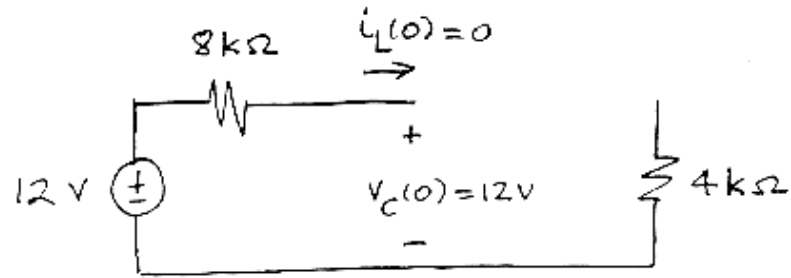


P7.9-2

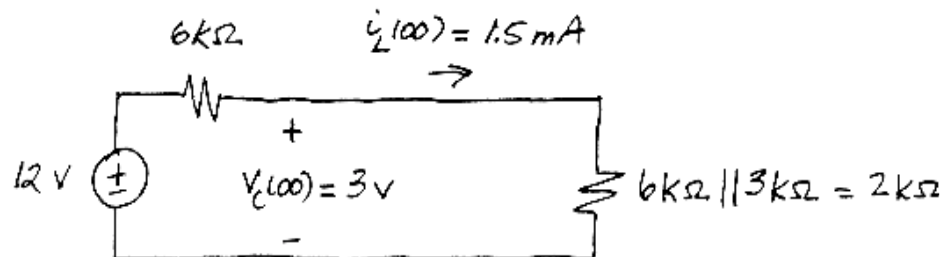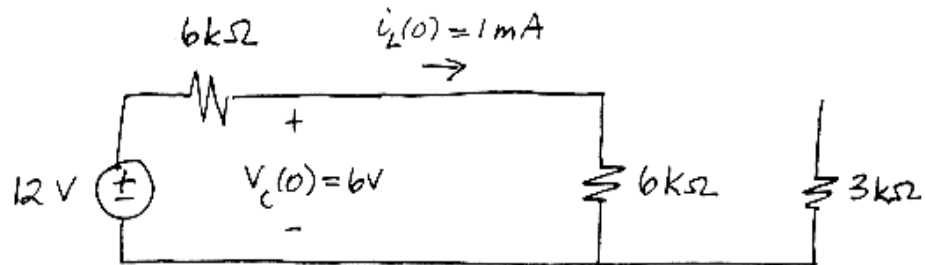

P7.9-3

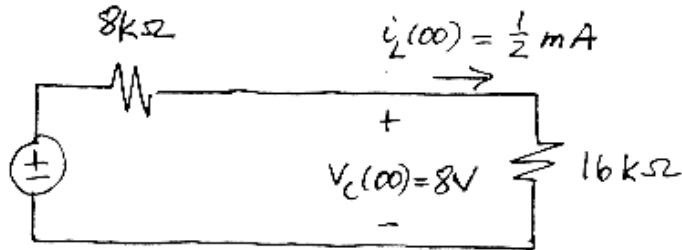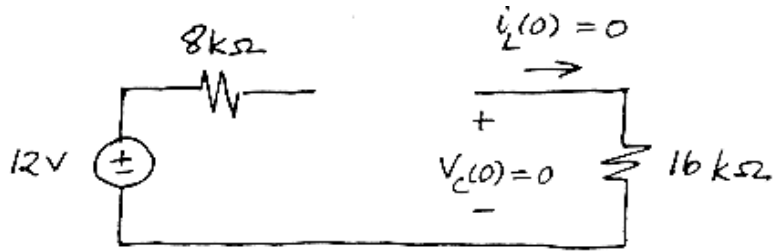


P7.9-4 at $t=0^-$

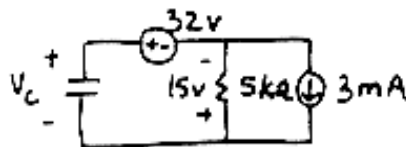

KVL: $-v_c(0^-) + 32 - 15 = 0$
 $\Rightarrow v_c(0^-) = v_c(0^+) = 17\text{V}$


at $t=0^+$

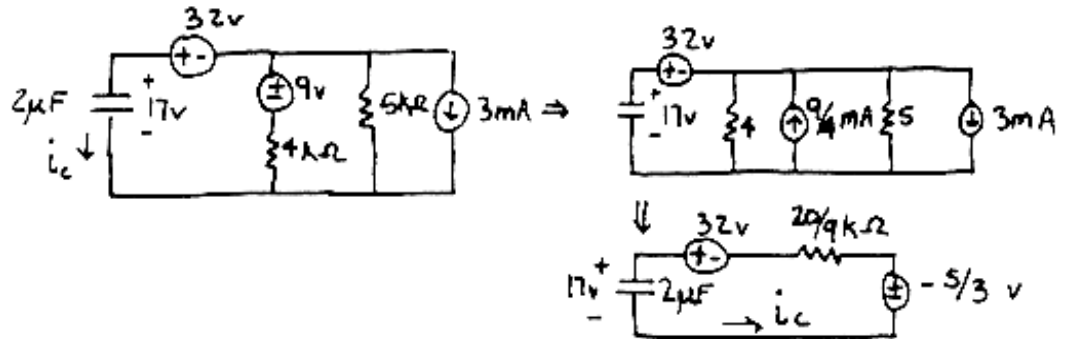

KVL: $\frac{5}{3} + \left(\frac{20}{9}\right) i_c - 32 + 17 = 0 \Rightarrow i_c(0^+) = 6\text{mA}$

Now $i_c(0^+) = C \frac{dv_c(0^+)}{dt} \Rightarrow \frac{dv_c(0^+)}{dt} = \frac{6\text{mA}}{2\mu\text{F}} = 3\text{V/ms}$

P7.9-5 at $t=0^-$

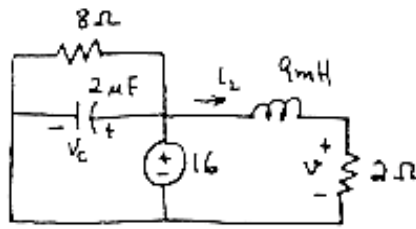


at steady - state

$$v_c(0^-) = v_c(0^+) = 16V$$

$$\text{and } i_L(0^-) = i_L(0^+) = \frac{16}{2} = 8A$$

at $t=0^+$

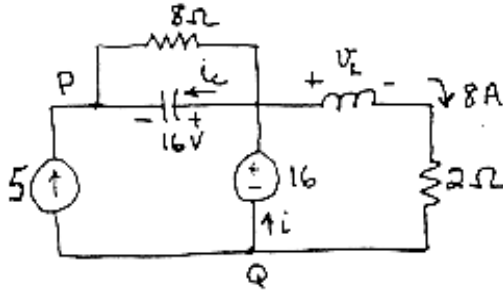


KVL: $-16 + v_L + 8(2) = 0 \Rightarrow v_L(0^+) = 0$

KCL at P: $-5 - i_c - \frac{16}{8} = 0 \Rightarrow i_c(0^+) = -7A$

KCL at Q: $5 + i - 8 = 0 \Rightarrow i(0^+) = 3A$

Then $\frac{di_L(0^+)}{dt} = \frac{v_L(0^+)}{L} = 0$ and $\frac{dv_c(0^+)}{dt} = \frac{i_c(0^+)}{C} = \frac{-7}{2\mu F} = -3.5A/\mu s$

P7.9-6 $t=0^-$

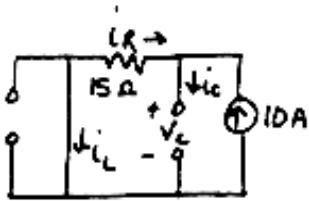

$$v_c(0^-) = (15)(10) = \underline{150V}$$

$$i_c(0^-) = \underline{0}$$


$$v_L(0^-) = \underline{0V}$$

$$i_L(0^-) = \underline{10A}$$

$$v_R(0^-) = 15(-10) = \underline{-150V}$$

$$i_R(0^-) = \underline{-10A}$$

$t=0^+$

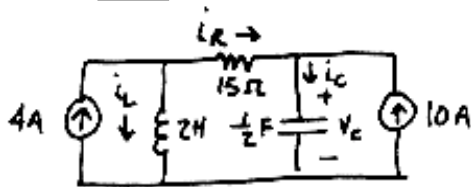

$$v_c(0^+) = v_c(0^-) = \underline{150V}$$

$$i_L(0^+) = i_L(0^-) = \underline{10A}$$

$$v_R(0^+) = -6(15) = \underline{-90V}$$

$$i_R(0^+) = 4A - 10A = \underline{-6A}$$

$$v_L(0^+) = v_R(0^+) + v_c(0^+) = \underline{60V}$$

$$i_c(0^+) = i_R(0^+) + 10A = 4A$$

Section 7-10: The Operational Amplifier and RC Circuits

P7.10-1

$$v_0(t) = -\frac{1}{RC} \int_0^t v_s(\tau) d\tau + v_0(0) = \frac{-1}{(20 \cdot 10^3)(2 \cdot 10^{-6})} \int_0^t 12 \cos 100\tau d\tau + 0$$

$$= -25 \left(\frac{12 \sin 100\tau}{100} \right)_0^t = -3 \sin 100t$$

P7.10-2

$$v_0(t) = -\frac{1}{RC} \int_0^t v_s(\tau) d\tau + v_0(0) = \frac{-1}{(2 \cdot 10^3)(10^{-6})} \int_0^t -4d\tau + 0 = 2000 t \quad 0 < t < 3\text{ms}$$

$$v_0(3\text{ms}) = (2 \cdot 10^3)(3 \cdot 10^{-3}) = 6$$

$$v_0(t) = -\frac{1}{RC} \int_3^t 0d\tau + 6 = 6 \quad t > 3\text{ms}$$

P7.10-3

$$250t = -\frac{1}{RC} \int_0^t -5 dt, \text{ when } 0 < t < 20\text{ms} = \frac{5}{RC} t$$

$$\text{so } 250 = \frac{5}{RC} \Rightarrow RC = \frac{5}{250} = \frac{1}{50}$$

$$\text{Let } C = 1\mu\text{F, then } R = \frac{1}{50(10^{-6})} = 20 \cdot 10^3 = 20\text{k}\Omega$$

Verification Problems**VP 7-1**

$$\text{at } t = 1 \quad 0.025 \stackrel{?}{=} -\frac{1}{2} + 0.065$$

$$\text{at } t = 3 \quad -\frac{3}{25} + 0.065 \stackrel{?}{=} \frac{3}{50} - 0.115$$

$$-0.55 \neq -0.485$$

The equation for the inductor current indicates that this current changes instantaneously at $t = 3\text{s}$. This equation cannot be correct.

VP 7-2

We need to check the values of the inductor current at the ends of the intervals.

$$\text{at } t = 1 \quad -\frac{1}{200} + 0.025 \stackrel{?}{=} -\frac{1}{100} + 0.03 \quad \text{Yes}$$

$$\text{at } t = 4 \quad -\frac{4}{100} + 0.03 \stackrel{?}{=} \frac{4}{100} - 0.03 \quad \text{No}$$


The equation for the inductor current indicates that this current changes instantaneously at $t = 4\text{s}$. This equation cannot be correct.

Design Problems


DP 7-1 We have $i(0) = \frac{30}{2+R} = 5$ & $v(0) = \frac{R}{2+R} 30 = 20$

Both relations above are satisfied for $R = 4\Omega$

DP 7-2 at $t = 0^-$

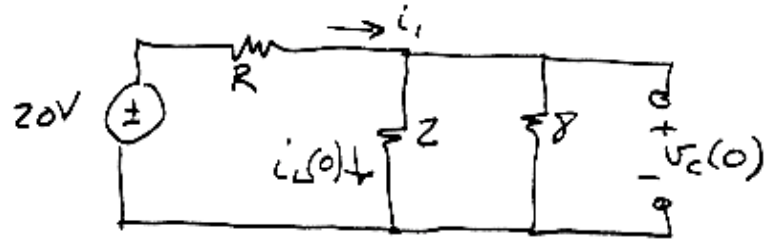

which becomes

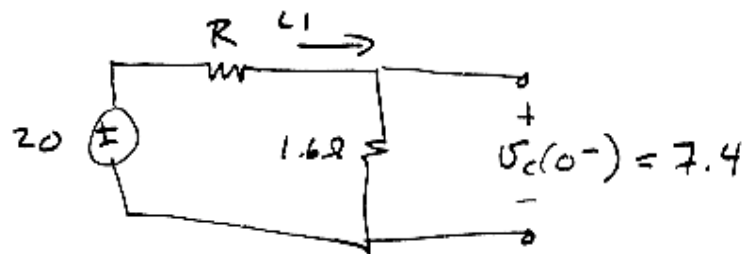

by voltage division:


$$v_c(0^-) = \left(\frac{1.6}{1.6+R} \right) 20 = 7.4 \Rightarrow R = 2.7\Omega$$

$$\text{Then } i_1 = \left(\frac{20}{2.7+1.6} \right) = 4.6 \text{ A}$$

Check with current division


$$i_L(0^-) = \left(\frac{8}{2+8} \right) i_1 = 3.7 \text{ A} \Rightarrow i_1 = 4.6 \text{ A} \quad \underline{\text{OK}}$$

DP 7-3 at $t = 0^-$

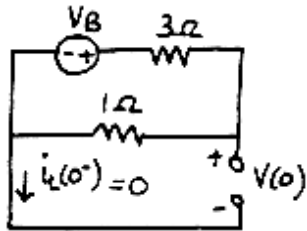

$$v(0) = \frac{1}{4}v_B$$

at $t = 0^+$

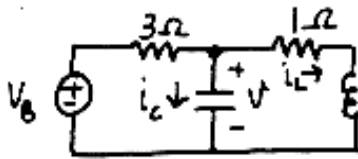

Now $\frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C}$ and $i_L(0^-) = i_L(0^+) = 0$

at top node: $\frac{v-v_B}{3} + i_L + i_c = 0$

$$i_c(0^+) = \frac{v_B - v(0^+)}{3} = \frac{v_B - 3}{3}$$

$$\frac{dv_c}{dt} = 24 = \frac{1}{\left(\frac{1}{8}\right)} \frac{(v_B - 3)}{3} \Rightarrow \underline{v_B = 12V}$$

DP 7-4

$$\frac{1}{2}Li_L^2 = \frac{1}{2}Cv_c^2 \quad (1) \quad \Leftrightarrow \text{in steady-state}$$

now in dc $i_L = v_c/R$ so (1) becomes $L\left(\frac{v_c}{R}\right)^2 = Cv_c^2 \Rightarrow C = \frac{L}{R^2}$

then $R = \sqrt{L/C} = \sqrt{\frac{10^{-2}}{10^{-6}}} = \sqrt{10^4} = 10^2$

So $R = 100 \Omega$