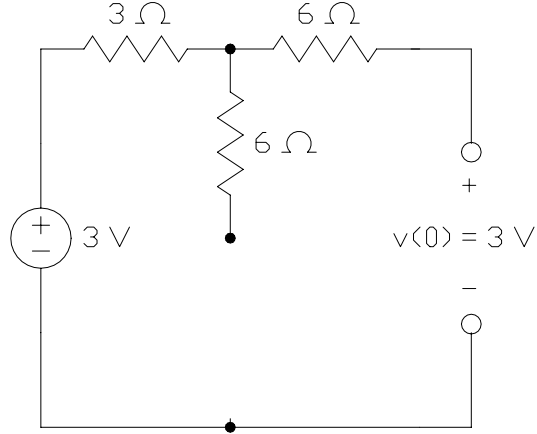



Chapter 8 – The Complete Response of RL and RC Circuits

Exercises

Ex 8.3-1 Before the switch closes:




After the switch closes:

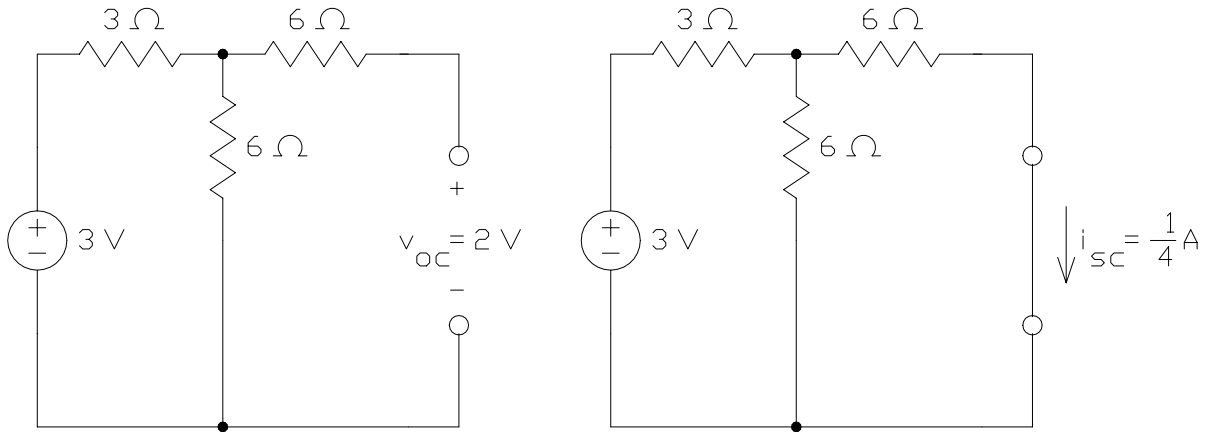


Therefore $R_t = \frac{2}{0.25} = 8\ \Omega$ so $\tau = 8(0.05) = 0.4\ \text{s}$.

Finally, $v(t) = v_{oc} + (v(0) - v_{oc}) e^{-\frac{t}{\tau}} = 2 + e^{-2.5t}\ \text{V}$ for $t > 0$

Ex 8.3-2 Before the switch closes:

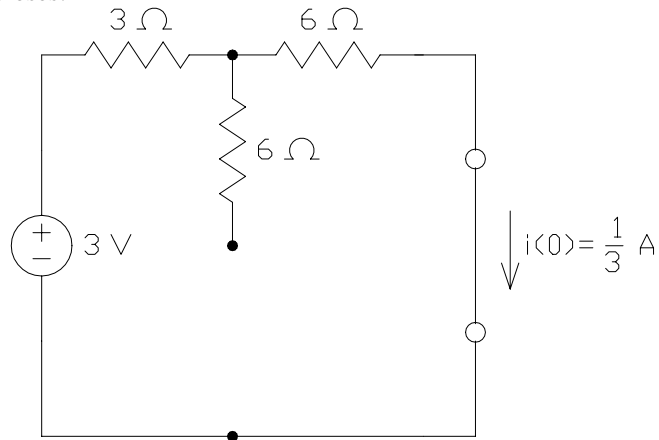


After the switch closes:

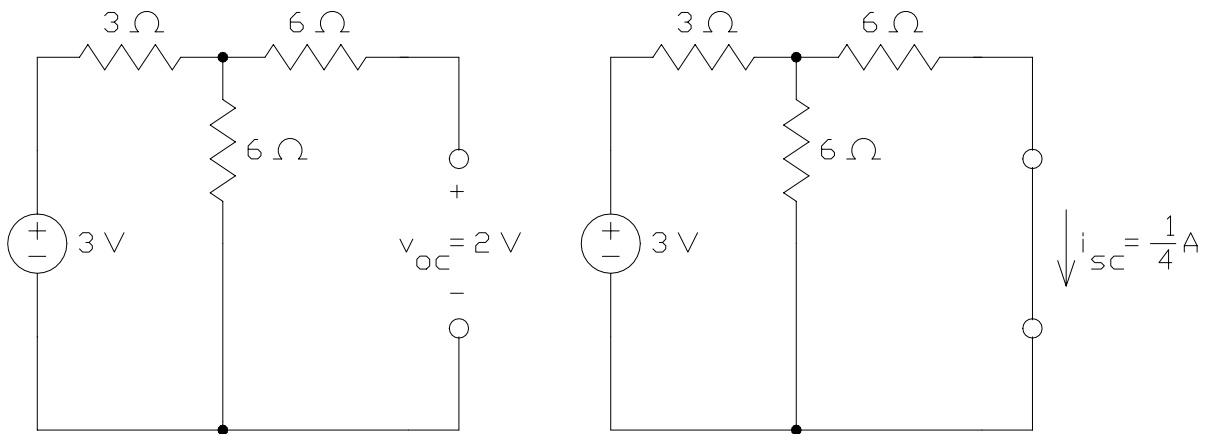


Therefore $R_t = \frac{2}{0.25} = 8 \Omega$ so $\tau = \frac{6}{8} = 0.75 \text{ s}$.

Finally, $i(t) = i_{sc} + (i(0) - i_{sc}) e^{-\frac{t}{\tau}} = \frac{1}{4} + \frac{1}{12} e^{-1.33t} \text{ A}$ for $t > 0$

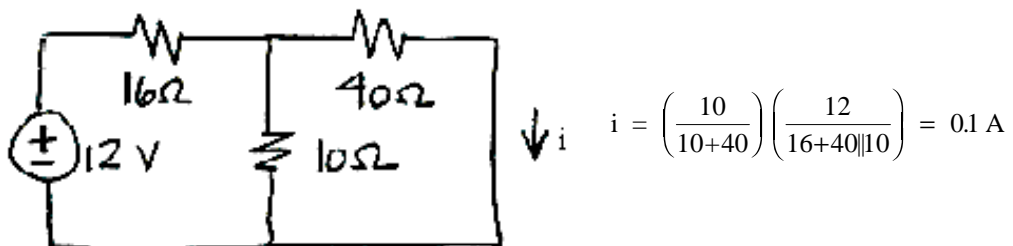
Ex. 8.3-3 At steady-state before $t = 0$:



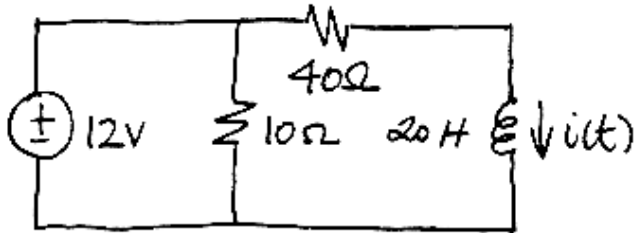After $t = 0$, the Norton equivalent of the circuit connected to the inductor is found to be




↓ becomes

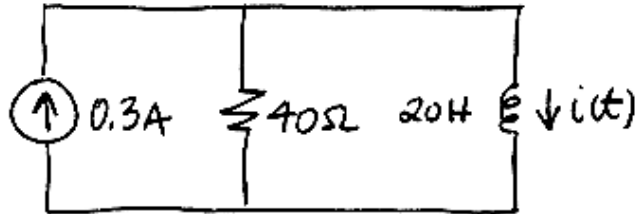


$$\text{so } I_{sc} = 0.3 \text{ A}, R_{th} = 40\Omega, \tau = \frac{L}{R_{th}} = \frac{20}{40} = \frac{1}{2}$$

$$\text{Finally: } i(t) = (0.1 - 0.3)e^{-2t} + 0.3 = 0.3 - 0.2e^{-2t} \text{ A}$$

Ex. 8.3-4 At steady-state for $t < 0$

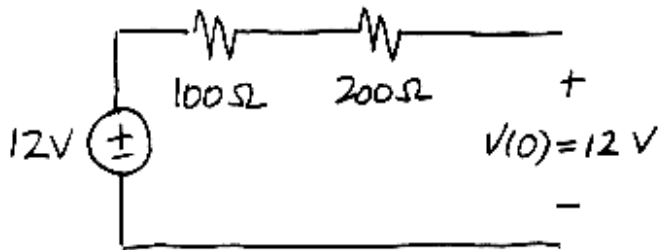

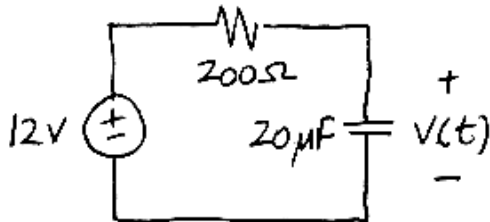After $t = 0$, replace the circuit connected to the capacitor by its Thévenin equivalent




$$\text{so } V_{oc} = 12\text{V}, R_{th} = 200\Omega, \tau = R_{th} C = (200)(20 \cdot 10^{-6}) = 4 \text{ ms}$$

$$\text{Finally: } v(t) = (12 - 12)e^{\frac{t}{4}} + 12 = 12 \text{ V}$$


Ex. 8.3-5 Before $t = 0$, $i(t) = 0$ so $I_o = 0$

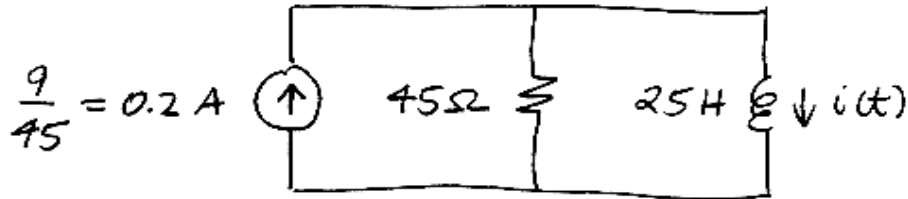After $t = 0$, replace the circuit connected to the inductor by its Norton equivalent



$$I_{sc} = 0.2 \text{ A}, R_{th} = 45\Omega, \tau = \frac{L}{R_{th}} = \frac{25}{45} = \frac{5}{9}$$


So

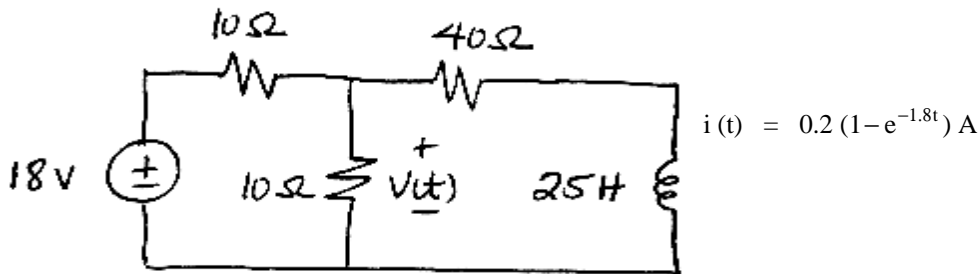

$$i(t) = 0.2(1 - e^{-1.8t}) \text{ A}$$


$$\text{Finally: } v(t) = 40 i(t) + 25 \frac{d}{dt} i(t) = 8(1 - e^{-1.8t}) + 5(1.8)e^{-1.8t} = 8 + e^{-1.8t} \text{ V}$$

Ex. 8.3-6 $t < 0$:

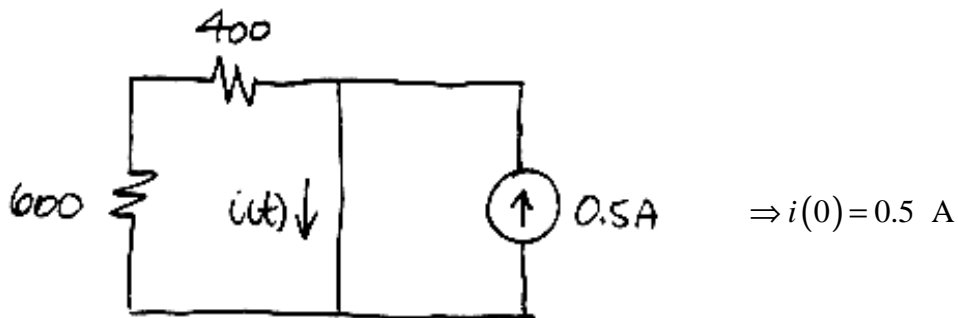

$$\Rightarrow i(0) = 0.5 \text{ A}$$

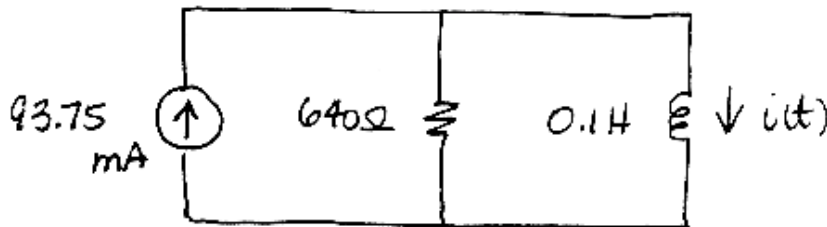
$t > 0$: Replace the circuit connected to the inductor by its Norton equivalent to get



$$I_{sc} = 93.75 \text{ mA}, R_{th} = 640\Omega, \tau = \frac{L}{R_{th}} = \frac{.1}{640} = \frac{1}{6400}$$

Continued

So

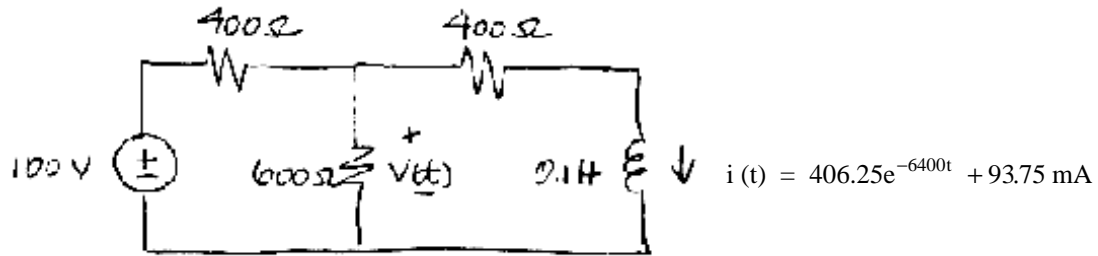


$$i(t) = 406.25e^{-6400t} + 93.75 \text{ mA}$$

Finally

$$v(t) = 400 i(t) + 0.1 \frac{d}{dt} i(t) = 400 (.40625e^{-6400t} + .09375) + 0.1(-6400)(.40625e^{-6400t}) = 37.5 - 97.5e^{-6400t} \text{ V}$$

Ex. 8.4-1

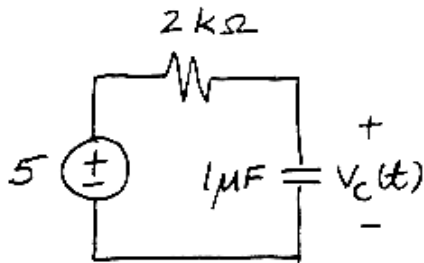


$$\tau = (2 \cdot 10^{-3})(1 \cdot 10^{-6}) = 2 \cdot 10^{-3}$$

$$v_c(t) = 5 + (1.5 - 5)e^{-\frac{t}{2}} \quad \text{where } t \text{ is in ms}$$

$$v_c(1) = 5 - 3.5e^{-\frac{1}{2}} = 2.88 \text{ V}$$

So $v_c(t)$ will be equal to v_T at $t=1 \text{ ms}$ if $v_T = 2.88 \text{ V}$

Ex. 8.4-2

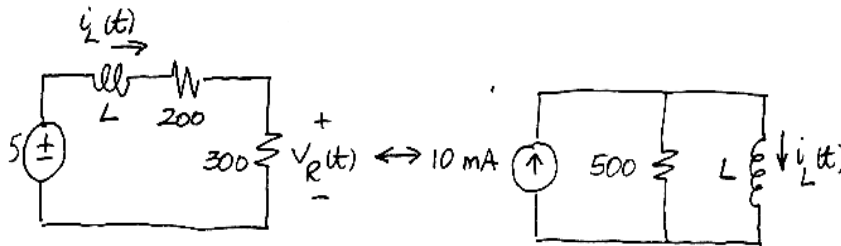

$$\left. \begin{aligned} i_L(0) = 1 \text{ mA}, I_{sc} = 10 \text{ mA} \\ R_{th} = 500 \Omega, \tau = \frac{L}{500} \end{aligned} \right\} \Rightarrow i_L(t) = 10 - 9e^{-\frac{500}{L}t} \text{ mA}$$

$$v_R(t) = 300 i_L(t) = 3 - 2.7e^{-\frac{500}{L}t} \text{ V}$$

We require that $v_R = 1.5 \text{ V}$ at $t = 10 \text{ ms} = 0.01 \text{ s}$

That is


$$1.5 = 3 - 2.7e^{-\frac{500}{L}(0.01)}$$

$$e^{-\frac{5}{L}} = \frac{1.5 - 3}{-2.7} = 0.555$$

$$-\frac{5}{L} = \ln(0.555) = -0.588$$

$$L = \frac{5}{0.588} = 8.5 \text{ H}$$

Ex. 8.6-1 $0 < t < t_1$

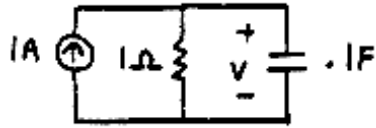

$$v(t) = v(\infty) + Ae^{-t/RC} \text{ where } v(\infty) = (1A)(1\Omega) = 1V$$

$$v(t) = 1 + Ae^{-t(1)(.1)} = 1 + Ae^{-10t}$$

Now $v(0^-) = v(0^+) = 0 = 1 + A \Rightarrow A = -1 \therefore v(t) = 1 - e^{-10t} \text{ V}$


$t > t_1$



$$t_1 = .5s \quad v(t) = v(t_1)e^{-\frac{t-t_1}{(1)(.1)}} = v(.5)e^{-10(t-.5)}$$

Now $v(.5) = 1 - e^{-10(.5)} = .993V$


$\therefore v(t) = .993e^{-10(t-.5)} \text{ V}$

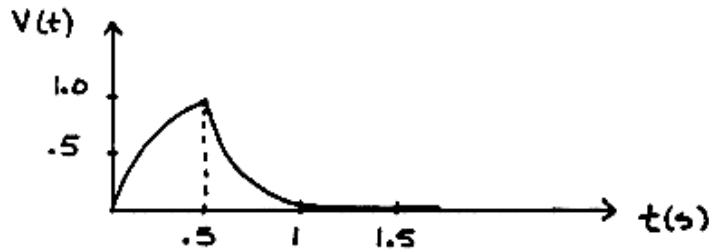

Ex. 8.6-2

$t < 0$ no sources $\therefore v(0^-) = v(0^+) = 0$

$0 < t < t_1$

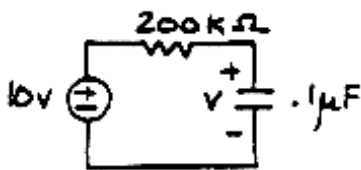

$$v(t) = v(\infty) + Ae^{-t/RC} = v(\infty) + Ae^{-\frac{t}{2 \times 10^5 (10^{-7})}}$$

where for $t = \infty$ (steady-state)
 \therefore capacitor becomes an open $\Rightarrow v(\infty) = 10V$

$$v(t) = 10 + Ae^{-50t}$$

Now $v(0) = 0 = 10 + A \Rightarrow A = -10 \therefore v(t) = 10(1 - e^{-50t}) \text{ V}$

$t > t_1, t_1 = .1s$




$$v(t) = v(.1)e^{-50(t-.1)}$$

where $v(.1) = 10(1 - e^{-50(.1)}) = 9.93 \text{ V}$

$\therefore v(t) = 9.93e^{-50(t-.1)} \text{ V}$

Ex. 8.6-3 for $t < 0$ $i = 0$

$0 < t < .2$

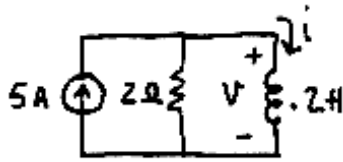

$$\left. \begin{array}{l} \text{KCL: } -5 + v/2 + i = 0 \\ \text{also: } v = 0.2 \frac{di}{dt} \end{array} \right\} \frac{di}{dt} + 10i = 50$$

$$\therefore i(t) = 5 + Ae^{-10t}$$


$$i(0) = 0 = 5 + A \Rightarrow A = -5$$

$$\text{so have } \underline{i(t) = 5(1 - e^{-10t}) \text{ A}}$$

$t > .2$

$$i(.2) = 4.32 \text{ A} \quad \therefore \underline{i(t) = 4.32e^{-10(t-.2)} \text{ A}}$$

Ex. 8.7-1

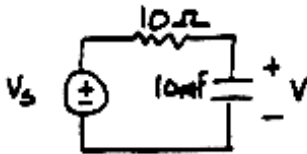

$$v_s = 10 \sin 20t \text{ V}$$

$$\text{KVL a: } -10 \sin 20t + 10 \left(.01 \frac{dv}{dt} \right) + v = 0 \Rightarrow \frac{dv}{dt} + 10v = 100 \sin 20t$$

Natural response: $s + 10 = 0 \Rightarrow s = -10 \therefore v_n(t) = Ae^{-10t}$

Forced response: try $v_f(t) = B_1 \cos 20t + B_2 \sin 20t$

plugging $v_f(t)$ into the differential equation and equating like terms

yields: $B_1 = -40$ & $B_2 = 20$


Complete response: $v(t) = v_n(t) + v_f(t)$

$$v(t) = Ae^{-10t} - 40 \cos 20t + 20 \sin 20t$$

Now $v(0^-) = v(0^+) = 0 = A - 40 \therefore A = 40$

$$\therefore \underline{v(t) = 40e^{-10t} - 40 \cos 20t + 20 \sin 20t \text{ V}}$$

Ex. 8.7-2

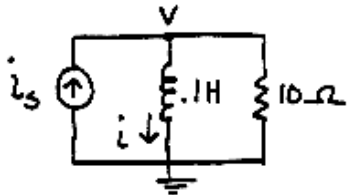

$$i_s = 10e^{-5t}$$

$$\text{KCL at top node: } -10e^{-5t} + i + v/10 = 0$$

$$\text{Now } v = .1 \frac{di}{dt} \Rightarrow \underline{\frac{di}{dt} + 100i = 1000e^{-5t}}$$

Natural response: $s + 100 = 0 \Rightarrow s = -100 \therefore i_n(t) = Ae^{-100t}$

Forced response: try $i_f(t) = Be^{-5t}$ & plug into D.E.

$$\Rightarrow -5Be^{-5t} + 100Be^{-5t} = 1000e^{-5t}$$

$$\Rightarrow B = 10.53$$

Complete response: $i(t) = Ae^{-100t} + 10.53e^{-5t}$

Now $i(0^-) = i(0^+) = 0 = A + 10.53 \Rightarrow A = -10.53$

$$\therefore \underline{i(t) = 10.53(e^{-5t} - e^{-100t}) \text{ A}}$$


Ex. 8.7-3

A current $i_L = v_s / 1$ flows in the inductor with the switch closed. When the switch opens, i_L cannot change instantaneously. Thus, the energy stored in the inductor dissipated in the spark. Add a resistor (say $1 \text{ k}\Omega$ across the switch terminals.)

Problems

Section 8.3: The Response of a First Order Circuit to a Constant Input


P8.3-1 We know that

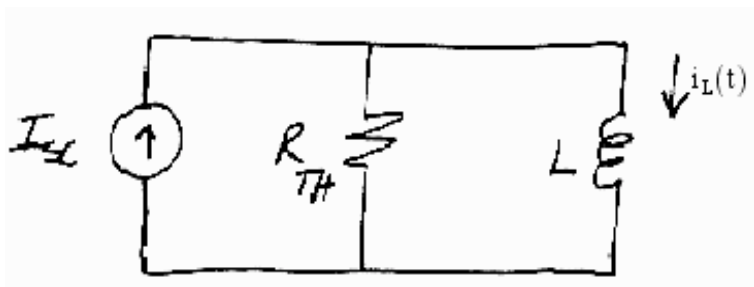


$$i_L(t) = (I_0 - I_{SC})e^{-\frac{(t-t_0)}{\tau}} + I_{SC}$$

where $I_0 = i_L(t_0)$ and $\tau = \frac{L}{R_{TH}}$. In this problem $t_0 = 0$ and $I_0 = i_L(0) = 3 \text{ mA}$.

The Norton equivalent of

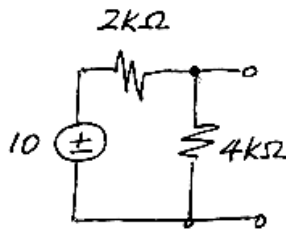

is

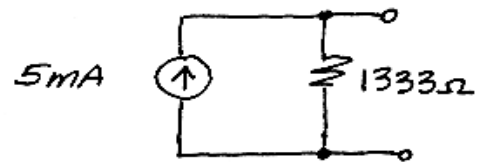


So $R_{th} = 1333\Omega$ and $I_{sc} = 5 \text{ mA}$.

$$L = 5 \text{ H so } \tau = \frac{L}{R_{th}} = \frac{5}{1333} = 3.75 \text{ ms}$$

Finally $i_L(t) = -2e^{-\frac{t}{3.75}} + 5 \text{ mA}$ $t > 0$ where t has units of ms.

P8.3-2 We know that

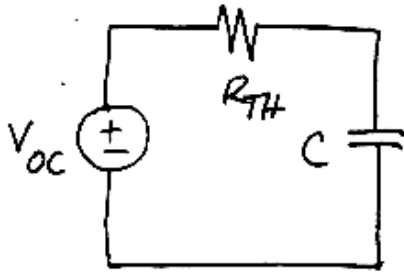


$$v_c(t) = (V_0 - V_{oc})e^{-\left(\frac{t-t_0}{\tau}\right)} + V_{oc}$$

where $v_0 = v_c(t_0)$ and $\tau = R_{th}C$,

In this problem, $t_0 = 0$ and $v_0 = v_c(0) = 8V$.

The Thèvenin equivalent of

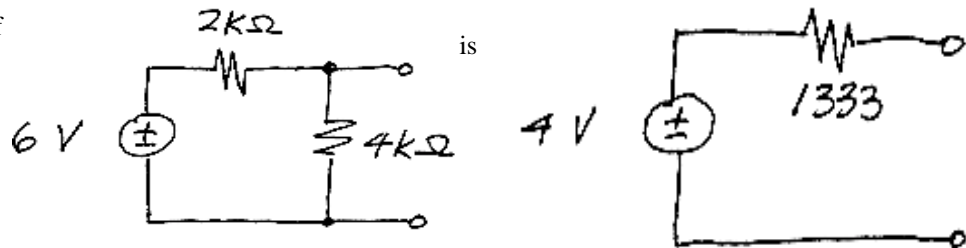


so $R_{th} = 1333$ and $V_{oc} = 4V$.


Next, $C = 0.5\mu F$ so $\tau = (0.5 \cdot 10^{-6}) 1333 = 0.67ms$

Finally $v_c(t) = 4e^{-\frac{t}{.67}} + 4V$ where t has units of ms .

P 8.3-3 Before the switch closes:

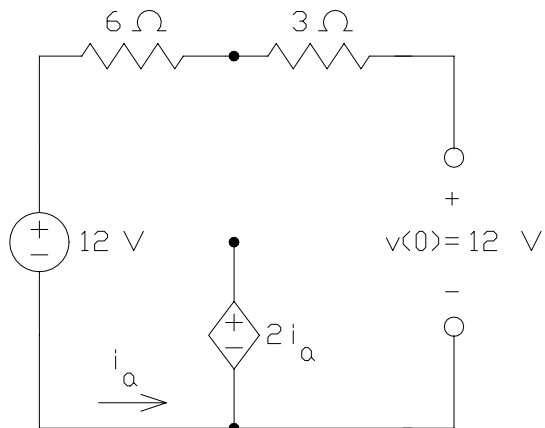


After the switch closes:

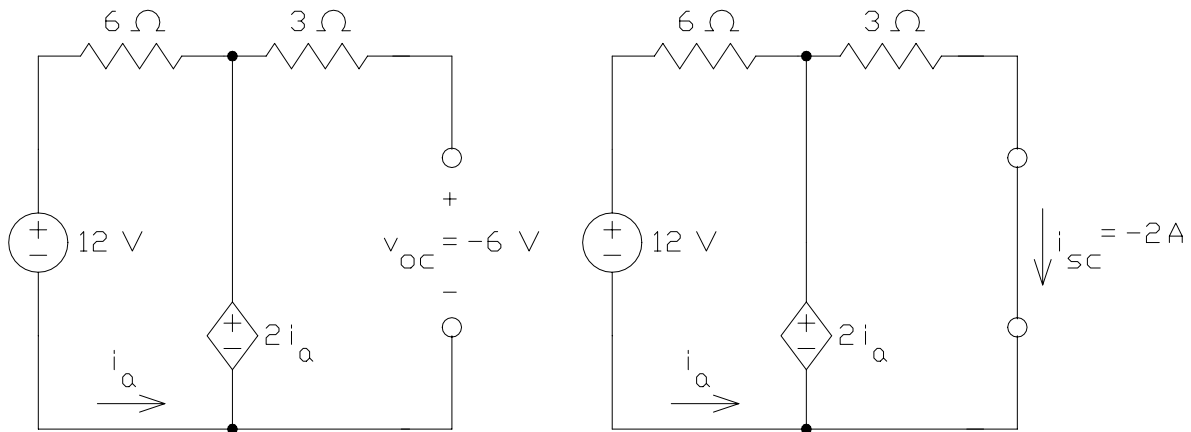


Therefore $R_t = \frac{-6}{-2} = 3 \Omega$ so $\tau = 3(0.05) = 0.15 \text{ s}$.

Finally, $v(t) = v_{oc} + (v(0) - v_{oc}) e^{-\frac{t}{\tau}} = -6 + 18 e^{-6.67t} \text{ V}$ for $t > 0$

P 8.3-4 Before the switch closes:

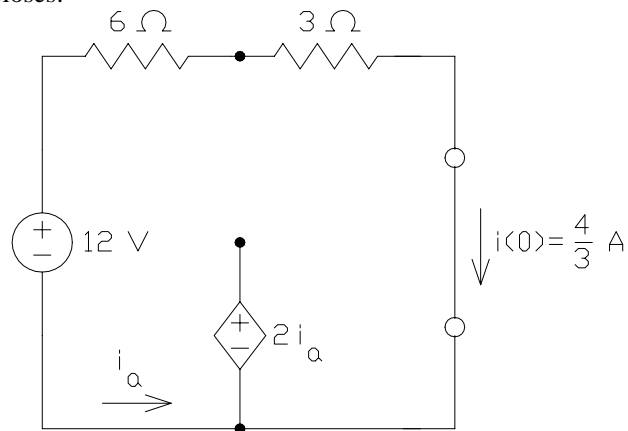

After the switch closes:

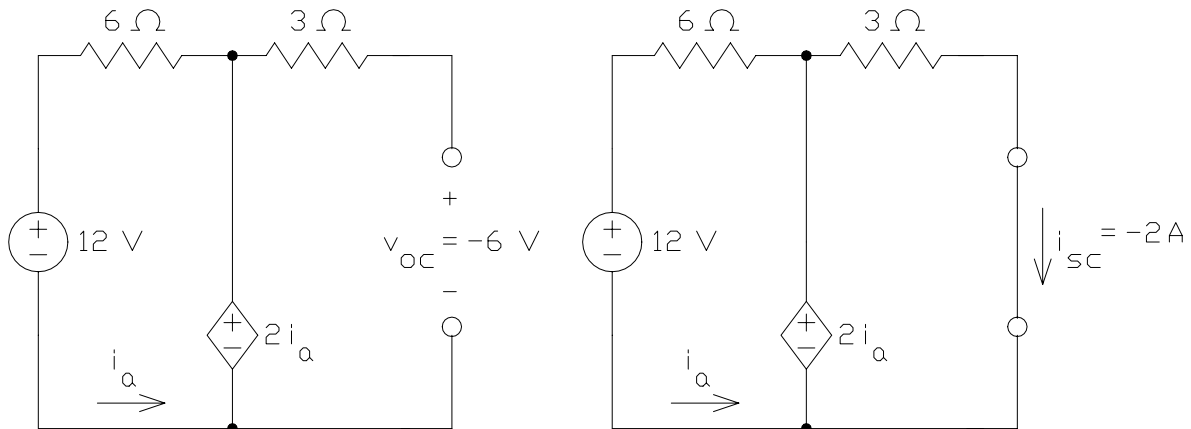


Therefore $R_t = \frac{-6}{-2} = 3 \Omega$ so $\tau = \frac{6}{3} = 2 \text{ s}$.

Finally, $i(t) = i_{sc} + (i(0) - i_{sc}) e^{-\frac{t}{\tau}} = -2 + \frac{10}{3} e^{-0.5t} \text{ A}$ for $t > 0$

P8.3-5

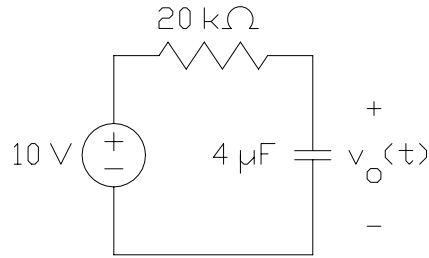Before the switch opens, $v_o(t) = 0 \text{ V} \Rightarrow v_o(0) = 0 \text{ V}$. After the switch opens the part of the circuit connected to the capacitor can be replaced by its Thevenin equivalent circuit to get:




Therefore $\tau = (20 \times 10^3)(4 \times 10^{-6}) = 0.08 \text{ s}$.

Next, $v_C(t) = v_{oc} + (v(0) - v_{oc}) e^{-\frac{t}{\tau}} = 10 - 10 e^{-12.5t} \text{ V}$ for $t > 0$

Finally, $v_o(t) = v_C(t) = 10 - 10 e^{-12.5t} \text{ V}$ for $t > 0$

P8.3-6

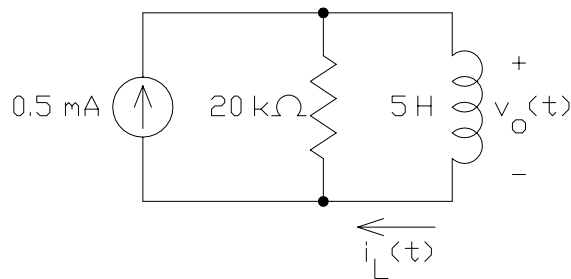Before the switch opens, $v_o(t) = 0 \text{ V} \Rightarrow v_o(0) = 0 \text{ V}$. After the switch opens the part of the circuit connected to the capacitor can be replaced by its Norton equivalent circuit to get:




Therefore $\tau = \frac{5}{20 \times 10^3} = 0.25 \text{ ms}$.

Next, $i(t) = i_{sc} + (i(0) - i_{sc}) e^{-\frac{t}{\tau}} = 0.5 \times 10^{-3} (1 - e^{-4000t}) \text{ A}$ for $t > 0$


Finally, $v_o(t) = 5 \frac{d}{dt} i_L(t) = 10 e^{-4000t} \text{ V}$ for $t > 0$

P8.3-7 Since the input to this circuit is constant, the capacitor will act like an open circuit when the circuit is at steady-state:

$t < 0$

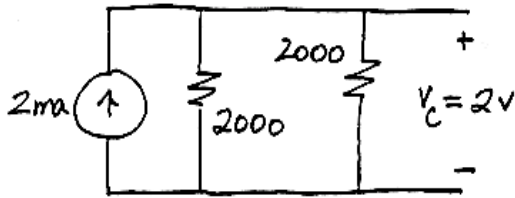


$t > 0$

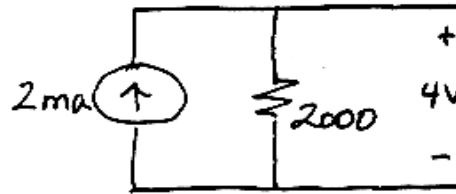


P8.3-8 Since the input to this circuit is constant, the inductor will act like a short circuit when the circuit is at steady-state:

$t < 0$

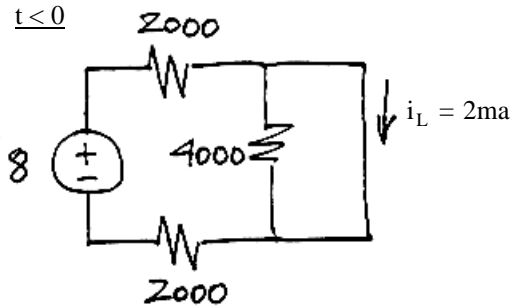

$t > 0$

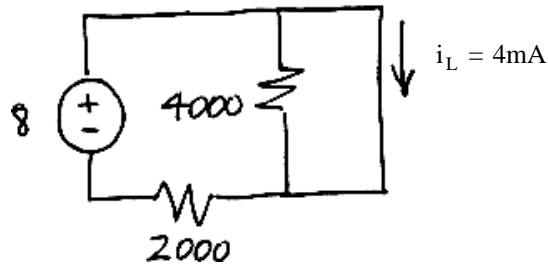


P8.3-9 Since the input to this circuit is constant, the inductor will act like a short circuit when the circuit is at steady-state:

$t < 0$




$t > 0$

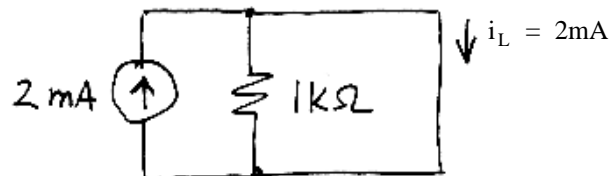


P8.3-10 Since the input to this circuit is constant, the capacitor will act like an open circuit when the circuit is at steady-state:

$t < 0$

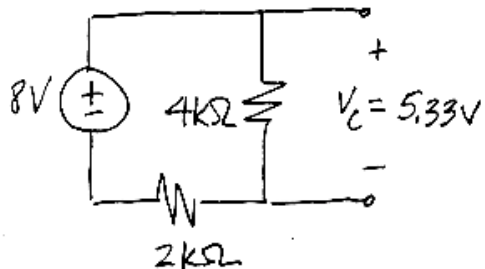


$t > 0$

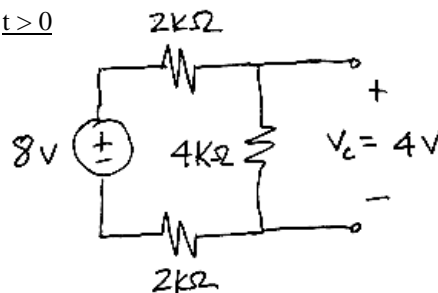


P8.3-11

at $t = 0^-$ (steady-state)

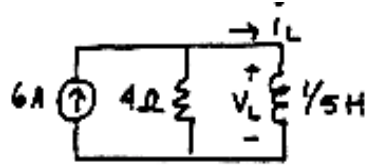


$$v_L(0^-) = 0 \quad \therefore i_L(0^-) = 6A = i_L(0^+)$$

for $t > 0$

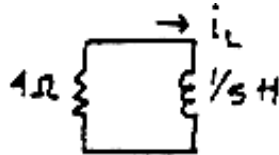

$$i_L(t) = i_L(0)e^{-(R/L)t} = 6e^{-20t} A$$

P8.3-12

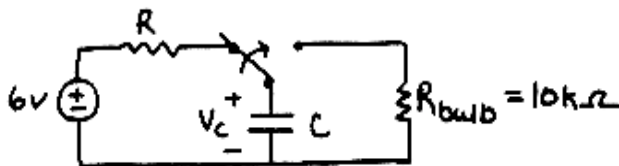

Assume the capacitor is charged at $t = 5\tau$, i.e., $\frac{V_c}{V_{c_{\max}}} = 1 - e^{-5} = .993$

Similarly, assume the capacitor is discharged when $\frac{V_c}{V_{c_{\max}}} = e^{-5} = 6.74 \times 10^{-3}$.

Now determine C from discharging condition

$$v_c(t) = v_c(t_0)e^{-\frac{(t-t_0)}{CR_{\text{bulb}}}} \Rightarrow 6.74 \times 10^{-3} = e^{-\frac{0.5}{CR_{\text{bulb}}}} \Rightarrow C = 10^{-5} F = 10 \mu F$$

Now determine a condition for R from charging circuit at the instant

$$v_c = 0 \Rightarrow \frac{6V}{R} < 100 \times 10^{-6} A \Rightarrow R > 60 k\Omega$$


then for the charging ckt.

$$.993 = 1 - e^{-5/RC}$$


$$-4.96 = -\frac{5}{RC} \Rightarrow R = \frac{5}{(4.96)(10^{-5})} = 100.8 k\Omega$$

and see that $R \approx 100k\Omega > 60k\Omega$.

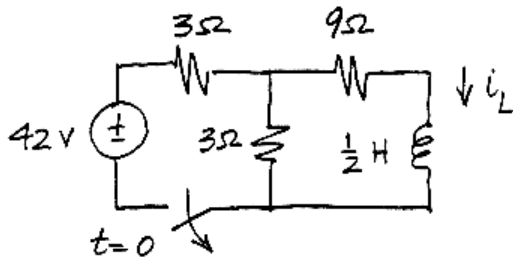
P8.3-13 First, use source transformations to obtain the equivalent circuit



for $t < 0$:

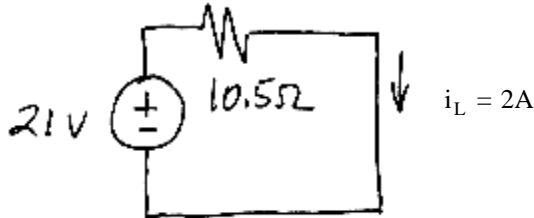

for $t > 0$:

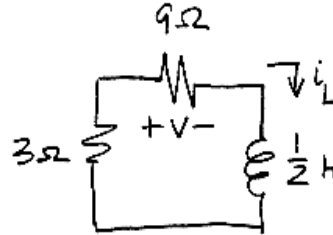


So $I_0 = 2\text{A}$, $I_{sc} = 0$, $R_{th} = 3\Omega + 9\Omega = 12\Omega$, $\tau = \frac{L}{R_{th}} = \frac{\frac{1}{2}}{12} = \frac{1}{24}$

and $i_L(t) = 2e^{-24t}$ $t > 0$

Finally $v(t) = 9i_L(t) = 18e^{-24t}$ $t > 0$

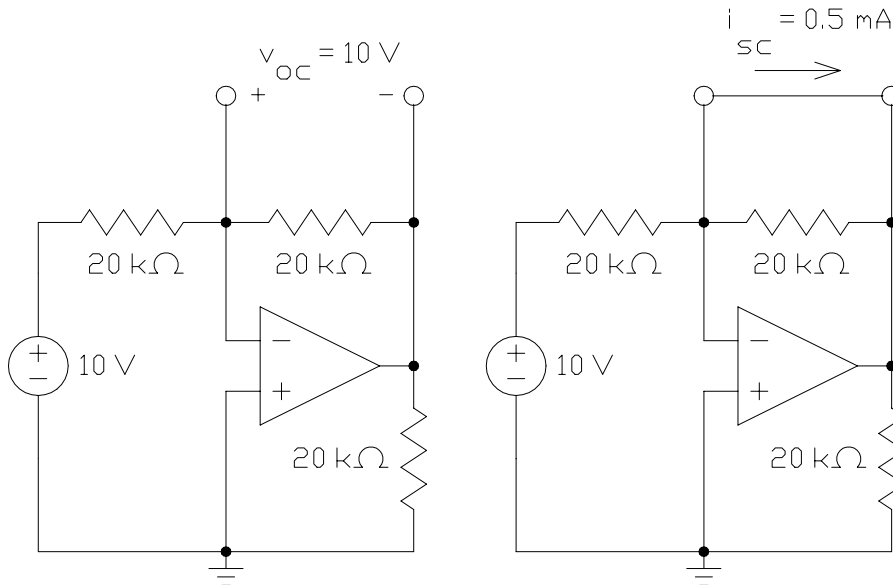P 8.3-14 Before the switch opens, $v_C(t) = 0\text{ V} \Rightarrow v_C(0) = 0\text{ V}$. After the switch opens:




Therefore $R_t = \frac{10}{0.5 \times 10^{-3}} = 20\text{ k}\Omega$ so $\tau = (20 \times 10^3)(4 \times 10^{-6}) = 0.08\text{ s}$.

Next, $v_C(t) = v_{oc} + (v(0) - v_{oc})e^{-\frac{t}{\tau}} = 10 - 10e^{-12.5t}\text{ V}$ for $t > 0$

Finally, $v_0(t) = -v_C = -10 + 10e^{-12.5t}\text{ V}$ for $t > 0$

Section 8-4: Sequential Switching

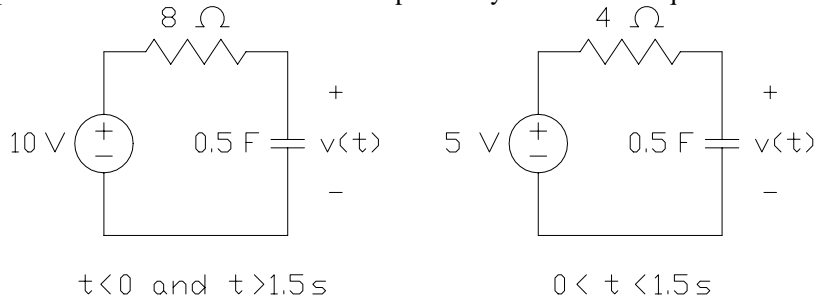P 8.4-1 Replace the part of the circuit connected to the capacitor by its Thevenin equivalent circuit to get:



Before the switch closes at $t = 0$ the circuit is at steady state so $v(0) = 10$ V. For $0 < t < 1.5$ s, $v_{oc} = 5$ V and $R_t = 4$ Ω so $\tau = 4 \times 0.5 = 2$ s. Therefore

$$v(t) = v_{oc} + (v(0) - v_{oc}) e^{-\frac{t}{\tau}} = 5 + 5e^{-0.5t} \text{ V for } 0 < t < 1.5 \text{ s}$$


At $t = 1.5$ s, $v(1.5) = 5 + 5e^{-0.5(1.5)} = 7.36$ V. For $1.5 \text{ s} < t$, $v_{oc} = 10$ V and $R_t = 8$ Ω so $\tau = 8 \times 0.5 = 4$ s. Therefore

$$v(t) = v_{oc} + (v(1.5) - v_{oc}) e^{-\frac{t-1.5}{\tau}} = 10 - 2.34 e^{-0.25(t-1.5)} \text{ V for } 1.5 \text{ s} < t$$

Finally

$$v(t) = \begin{cases} 5 + 5e^{-0.5t} \text{ V} & \text{for } 0 < t < 1.5 \text{ s} \\ 10 - 2.34 e^{-0.25(t-1.5)} \text{ V} & \text{for } 1.5 \text{ s} < t \end{cases}$$

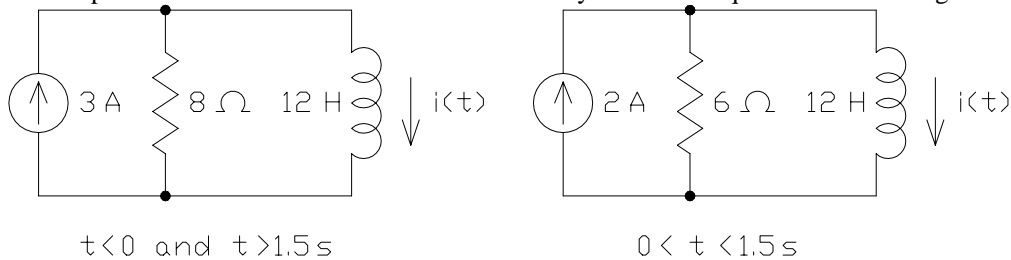P 8.4-2 Replace the part of the circuit connected to the inductor by its Norton equivalent circuit to get:



Before the switch closes at $t = 0$ the circuit is at steady state so $i(0) = 3$ A. For $0 < t < 1.5$ s, $i_{sc} = 2$ A and $R_t = 6$ Ω so $\tau = \frac{12}{6} = 2$ s. Therefore

$$i(t) = i_{sc} + (i(0) - i_{sc}) e^{-\frac{t}{\tau}} = 2 + e^{-0.5t} \text{ A for } 0 < t < 1.5 \text{ s}$$

At $t = 1.5$ s, $i(1.5) = 2 + e^{-0.5(1.5)} = 2.47$ A. For $1.5 \text{ s} < t$, $i_{sc} = 3$ A and $R_t = 8$ Ω so $\tau = \frac{12}{8} = 1.5$ s. Therefore

$$i(t) = i_{sc} + (i(1.5) - i_{sc}) e^{-\frac{t-1.5}{\tau}} = 3 - 0.64 e^{-0.667(t-1.5)} \text{ V for } 1.5 \text{ s} < t$$


$$i(t) = i_{sc} + (i(1.5) - i_{sc}) e^{-\frac{t-1.5}{\tau}} = 3 - 0.64 e^{-0.667(t-1.5)} \text{ V for } 1.5 \text{ s} < t$$

Finally

$$i(t) = \begin{cases} 2 + e^{-0.5t} \text{ A} & \text{for } 0 < t < 1.5 \text{ s} \\ 3 - 0.64 e^{-0.667(t-1.5)} \text{ A} & \text{for } 1.5 \text{ s} < t \end{cases}$$

P8.4-3


$t = 0^-$ (steady-state)

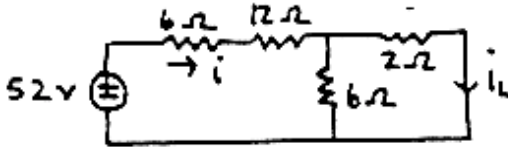

KVL: $-52 + 18i + (12/8)i = 0 \Rightarrow i(0^-) = 104/39 \text{ A}$

$\therefore i_L = i \left(\frac{6}{6+2} \right) = 2\text{A} = i_L(0^+)$

$0 < t < 51\text{ms}$

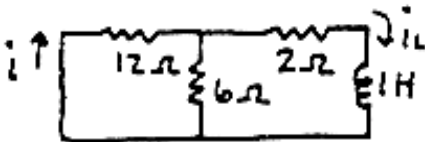


$i_L(t) = i_L(0) e^{-(R/L)t} \quad R = 6 \parallel 12 + 2 = 6\Omega$

$i_L(t) = 2e^{-6t} \text{ A}$

$\therefore i(t) = i_L(t) \left(\frac{6}{6+12} \right) = 2/3 e^{-6t} \text{ A}$

$t > 51\text{ms}$

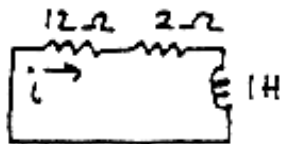

$i_L(t) = i_L(51\text{ms}) e^{-(R/L)(t-.051)}$

$i_L(51\text{ms}) = 2e^{-6(.051)} = 1.473$

$i_L(t) = 1.473 e^{-14(t-.051)} \text{ A}$

P8.4-4 $t = 0^-$

Assume $V_1 =$ voltage across $10\mu\text{F}$ capacitor $= 3\text{V}$


$0 < t < 10\text{ms}$

With R negligibly small, we may assume a static steady-state situation is obtained in the circuit nearly instantaneously ($t = 0^+$). Thus with both capacitors in parallel, the common voltage is obtained by considering charge conservation.

at $t = 0^-$, $q_{100\mu\text{F}} = CV = (100\mu\text{F})(3\text{V}) = 300\mu\text{C}$

$q_{400\mu\text{F}} = CV = (400\mu\text{F})(0) = 0$

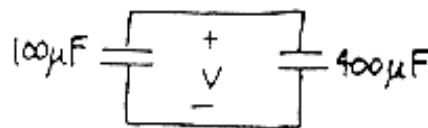$q_{\text{TOT}} = q_{100} + q_{400} = 300\mu\text{C}$




at $t = 0^+$, $q_{100} + q_{400} = 300\mu\text{C}$

Now using $q = CV \Rightarrow (100\mu\text{F})(V) + (400\mu\text{F})(V) = 300\mu\text{C} \Rightarrow V = 0.6 \text{ V}$

$10\text{ms} < t < 1\text{s}$

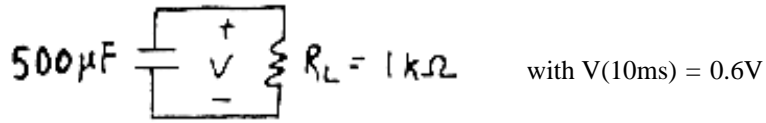Combine $100\mu\text{F}$ & $400\mu\text{F}$ in parallel to obtain




$$v(t) = V(10\text{ms}) e^{-(t-0.01)/RC} = 0.6e^{-(t-0.01)/(10^3)(5 \times 10^{-4})}$$

$$\underline{v(t) = 0.6 e^{-2(t-0.01)} \text{ V}}$$

P8.4-5

$$V_{oc} = V_T = \left(40 \times \frac{20}{20+20}\right) - 5i_1 = 20 - 5 = \left(\frac{40}{40}\right) = \underline{15 \text{ V}}$$

for R_T , kill source with $V = 0$

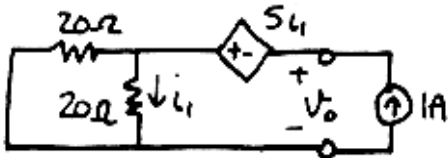


Note $i_1 = \frac{1}{2} \text{ A}$

$$R_T = \frac{V_0}{1} = 1(10\Omega) - 5\left(\frac{1}{2}\text{A}\right) = \underline{7.5\Omega}$$

$$\underline{R_{eq} = 7.5\Omega}$$

Forced response

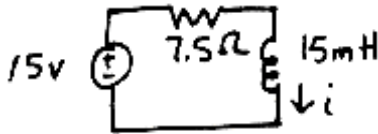

$$i = 2\text{A}$$

$$\tau = L/R = \frac{15 \times 10^{-3}}{7.5} = 2\text{ms}$$

natural: $i = Be^{-t/\tau} = Be^{-500t}$

total: $i = Be^{-500t} + 2$ now $i(0) = 0 \Rightarrow B = -2$

$$\underline{i(t) = 2(1 - e^{-500t})\text{A}}$$

time to 99%:

for $e^{-500t} = .01$ or $500t = 4.605 \Rightarrow \underline{t = 9.2\text{ms}}$

P8.4-6 $\left. \begin{array}{l} \tau = RC = 10^5 \times 10^{-6} = .1\text{s} \\ v_c(0) = 5 \text{ V} \end{array} \right\} \Rightarrow v_c(t) = 5e^{-t/\tau}$

Now $5/2 = v_c(t_1) = 5e^{-t_1/\tau}$

$$e^{-t_1/\tau} = .5 \Rightarrow \underline{t_1 = .0693\text{s}}$$


$$i(t_1) = \frac{v(t_1)}{100 \text{ k}\Omega} = \frac{5/2}{10^5} = \underline{25\mu \text{ A}}$$

P8.4-7



$$v(0^-) = v(0^+) = (2A)(5\Omega) = 10V$$


$0 < t < 100ms$

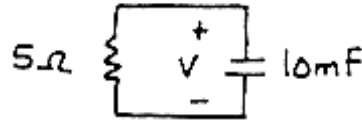

$$v(t) = v(0)e^{-t/RC}$$

$$v(t) = 10e^{-t/(5)(.01)} = 10e^{-20t} \text{ V}$$

$t > 100ms$

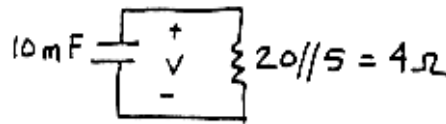

$$v(t) = v(100ms) e^{-\frac{(t-100ms)}{(4)(.01)}}$$

$$v(100ms) = 10e^{-20(.1)} = 1.35 \text{ V}$$


$$\therefore v(t) = 1.35e^{-25(t-.1)} \text{ V}$$

P8.4-8

$t = 0^-$ (steady-state)

$$i_2 = \frac{1}{1+4+2+1} 7 = \frac{7}{8} \text{ A}$$
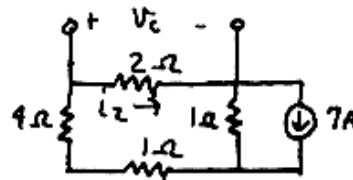
$$v_c(0^-) = v_c(0^+) = 2i_2 = 7/4 \text{ V}$$




$0 < t < .35$ Closing the rightmost switch shorts out 1Ω in parallel with $7A$ source leaving

$$\text{KCL at a: } \frac{-v_x}{4} + 5i_c + i_c + \frac{v_c}{2} = 0 \quad (1)$$

$$\text{KCL at b: } \frac{v_x}{4} - 5i_c + \frac{v_c + v_x}{1} = 0 \quad (2)$$
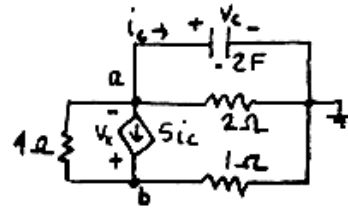
$$\text{also: } i_c = .2 \frac{dv_c}{dt} \quad (3)$$




$$\text{Plugging (3) into (1) \& (2) \& then eliminating } v_c \text{ yields } \Rightarrow \frac{dv_c}{dt} + \frac{7}{10} v_c = 0$$

$$\text{So } v_c(t) = v_c(0) e^{-0.7t} = \frac{7}{4} e^{-0.7t}, \quad i_c = .2 \frac{dv_c}{dt} = -.245e^{-.7t}$$

$$\text{So from (1) we have } v_x(t) = 24i_c + 2v_c = \underline{-2.38 e^{-.7t}}$$

$t > .35$

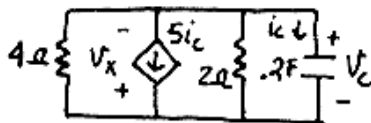

$$v_c(.35) = 7/4 e^{-(.7)(.35)} = 1.37V$$

$$\text{now } = v_x = -v_c$$


$$\text{KCL: } \frac{v_c}{4} + 5i_c + \frac{v_c}{2} + i_c = 0 \quad (1)$$

$$\text{also: } i_c = 0.2 \frac{dv_c}{dt} \quad (2)$$

$$\text{From (1) \& (2) } \Rightarrow dv_c/dt + 5/8 v_c = 0 \Rightarrow v_c(t) = v_c(.35) e^{-(t-.35)5/8} = \underline{-1.37 e^{-.625(t-.35)}}$$

Section 8-5: Stability of First Order Circuits

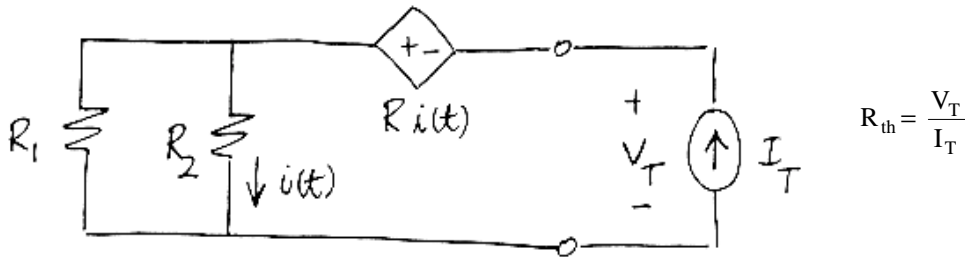
P8.5-1 This circuit will be stable if the Thévenin equivalent resistance of the circuit connected to the inductor is positive.



$$\left. \begin{aligned} i(t) &= \frac{R_1}{R_1 + R_2} I_T \\ V_T &= R_2 i(t) - R i(t) \end{aligned} \right\} \Rightarrow R_{th} = \frac{(R_2 - R)R_1}{R_1 + R_2}$$

Then $R_{th} > 0$ requires $R_2 > R$. In this case $R_2 = 400\Omega$ so $400 > R$ is required to guarantee stability.

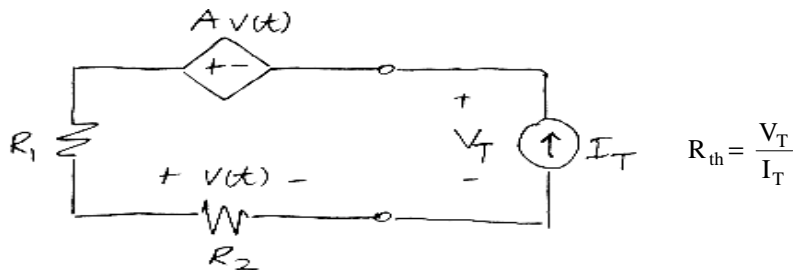P8.5-2 The Thévenin equivalent resistance of the circuit connected to the inductor is calculated as




$$\left. \begin{aligned} v(t) &= R I_T \\ V_T &= I_T (R_1 + R_2) - A R I_T \end{aligned} \right\} \Rightarrow R_{th} = R_1 + R_2 - A R_2$$

The circuit will be stable when $R_{th} > 0$, that is,

$$R_{th} > 0 \Rightarrow \frac{R_1 + R_2}{R_2} > A$$

When $R_1 = 4k\Omega$ and $R_2 = 1k\Omega$, then $A < 5$ is required to guarantee stability.

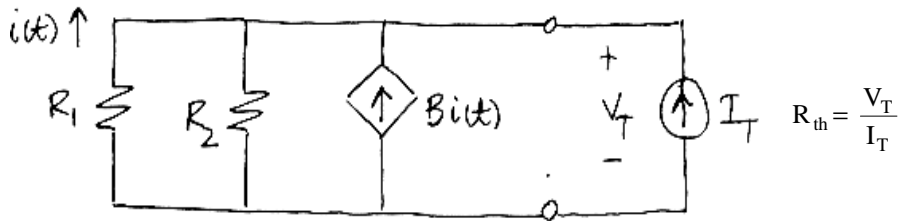P8.5-3 The Thévenin equivalent resistance of the circuit connected to the inductor is calculated as



$$V_T = -R_1 i(t) = R_2 (i(t) + Bi(t) + I_T)$$

$$i(t) = \frac{-R_2}{R_1 + R_2 + R_2 B} I_T$$

$$V_T = -R_1 \frac{-R_2}{R_1 + R_2 + R_2 B} I_T$$


$$R_{th} = \frac{R_1 R_2}{R_1 + R_2 + R_2 B}$$

The circuit is stable when $R_{th} > 0$, that is

$$R_1 + R_2 + R_2 B > 0 \Rightarrow B > -\frac{R_1 + R_2}{R_2}$$

when $R_1 = 6\text{k}\Omega$ and $R_2 = 3\text{k}\Omega$, $B > -3$ is required to guarantee stability.

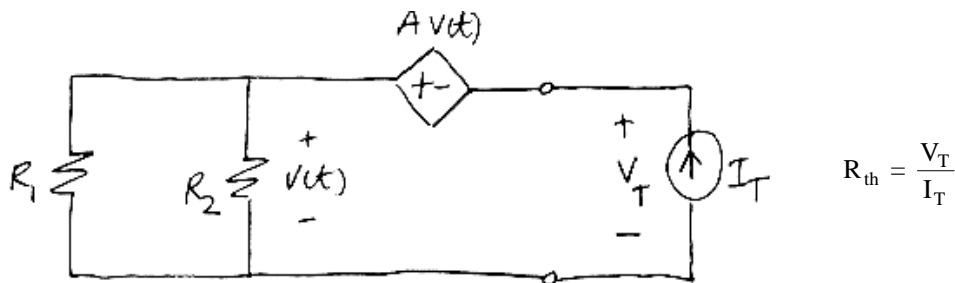P8.5-4 The Thévenin equivalent resistance of the circuit connected to the inductor is calculated as



$$\left. \begin{aligned} v(t) &= \frac{R_1 R_2}{R_1 + R_2} I_T \\ V_T &= v(t) - Av(t) \end{aligned} \right\} R_{th} = \frac{R_1 R_2}{R_1 + R_2} (1 - A)$$


The circuit will be stable when $R_{th} > 0$, that is, when $A < 1$.

Section 8-6: The Unit Step Response


P8.6-1

$$10u(t) - 4 = \begin{cases} 10(0) - 4 = -4 & t < 0 \\ 10(1) - 4 = 6 & t > 0 \end{cases}$$

t < 0:

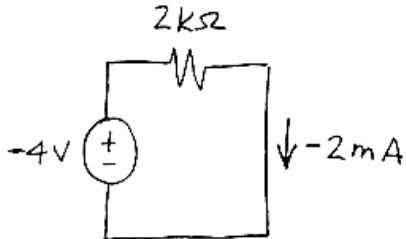


t > 0:

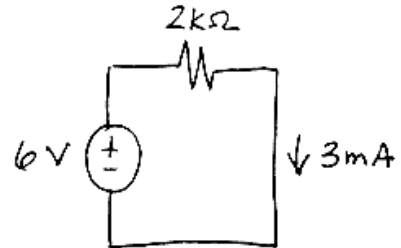

P8.6-2

$$6u(-t) + 4u(t) = \begin{cases} 6(1) + 4(0) = 6 & t < 0 \\ 6(0) + 4(1) = 4 & t > 0 \end{cases}$$

t < 0:

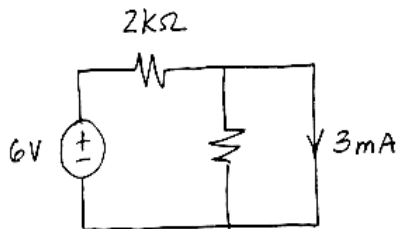

t > 0:

