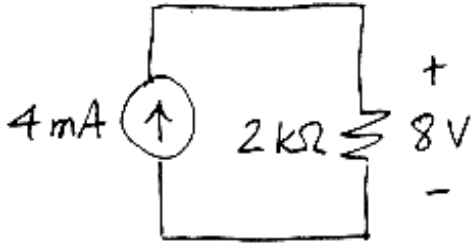



P8.6-3

$$4 + 2u(t) = \begin{cases} 4 + 2(0) = 4 & t < 0 \\ 4 + 2(1) = 6 & t > 0 \end{cases}$$

$t < 0$:




$t > 0$:

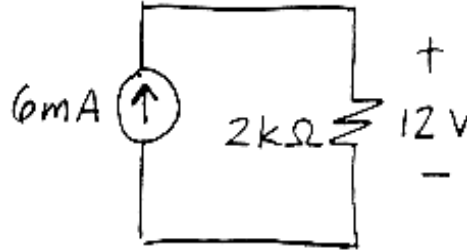


P8.6-4

$$6u(-t) + 6 = \begin{cases} 6(1) + 6 = 12 & t < 0 \\ 6(0) + 6 = 6 & t > 0 \end{cases}$$

$t < 0$:

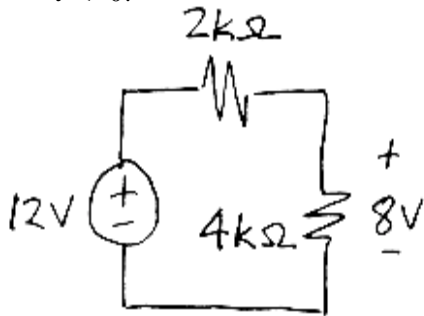


$t > 0$:

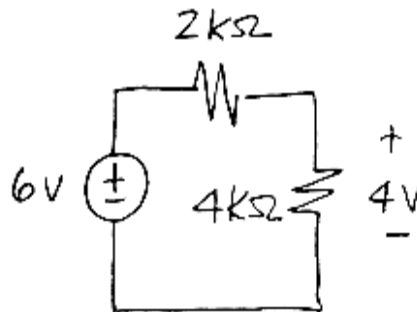

P8.6-5

$t < 0$ (steady-state)

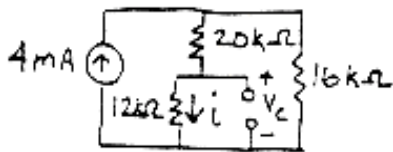


Current divider $i(0^-) = 4 \left(\frac{16}{16 + 32} \right) = 4/3 \text{ mA}$

$\therefore v_c(0^-) = 12i(0^-) = 16 \text{ V} = v_c(0^+) = 12i(0^+)$

$\therefore i(0^+) = 4/3 \text{ mA}$

$t > 0$

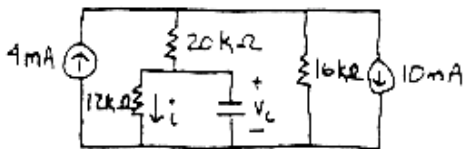


$$i(t) = i(\infty) + Ae^{-t/R_c} = i(\infty) + Ae^{-2000t}$$

$R = 12 || 32 = 9 \text{ k}\Omega$

$C = 1/18 \mu\text{F}$

$t = \infty$ (steady-state)

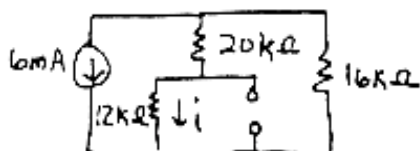

$i(\infty) = -6 \left[\frac{16}{16 + 32} \right] = -2 \text{ mA}$


$\therefore i(t) = -2 + Ae^{-2000t}$

Now $i(0) = 4/3 = -2 + A \Rightarrow A = 10/3$

$\therefore i(t) = (10/3)e^{-2000t} - 2 \text{ mA} \quad t > 0$

P8.6-6

$t > 0$

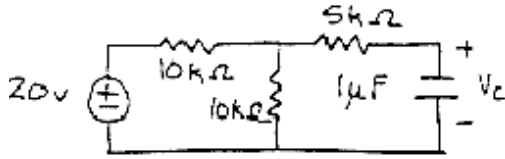

$$v_c(t) = v_c(\infty) + Ae^{-t/RC}$$

where $R = 5\text{ k}\Omega + 10\text{ k}\Omega \parallel 10\text{ k}\Omega = 10\text{ k}\Omega$

from voltage divider $v(\infty) = 20 \left(\frac{10}{10+10} \right) = 10\text{ V}$


$$\therefore v_c(t) = 10 + Ae^{-100t}$$

$$\text{now } v_c(0) = 0 = 10 + A \Rightarrow A = -10$$

$$\underline{v_c(t) = 10(1 - e^{-100t})\text{ V}}$$

P8.6-7 Use superposition, first look at $15e^{-t} u(t)$ source

$t > 0$

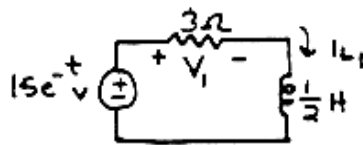

$$\text{KVL a: } -15e^{-t} + 3i_{L_1} + 1/2 \frac{di_{L_1}}{dt} = 0 \Rightarrow \underline{\frac{di_{L_1}}{dt} + 6i_{L_1} = 30e^{-t}}$$

$$\therefore i_{L_1}(t) = Ae^{-6t} + i_{L_p}(t) \Rightarrow \text{try } i_{L_p}(t) = Be^{-t} \text{ \& plug into D.E. } \Rightarrow B=6$$

$$i_{L_1}(t) = Ae^{-6t} + 6e^{-t}$$

$t = 0^-$ (steady - state)



$$i_{L_1}(0^-) = 0 = i_{L_1}(0^+)$$

$$\therefore i_{L_1}(t) = -6e^{-6t} + 6e^{-t}$$

$$\text{Now } \underline{v_1(t) = 3i_{L_1}(t) = -18e^{-6t} + 18e^{-t}\text{ V}} \quad u(t)$$

Now consider $-15e^{-t} u(t-1)$ source


Just take previous result and change $t \rightarrow t-1$ and flip signs

$$\therefore v_2(t) = 18e^{-6(t-1)} - 18e^{-(t-1)} u(t-1)$$

$$\underline{\therefore v(t) = [-18e^{-6t} + 18e^{-t}] u(t) + [18e^{-6(t-1)} - 18e^{-(t-1)}] u(t-1)}$$

P8.6-8 $v(t) = 4u(t) - u(t-1) - u(t-2) + u(t-4) - u(t-6)$

P8.6-9
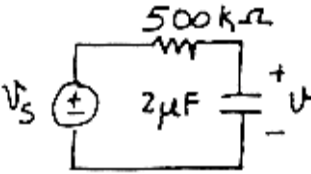
$$v_s = \begin{cases} 0 & t < 1 \\ 4 & 1 < t < 2 \\ 0 & t > 2 \end{cases}$$


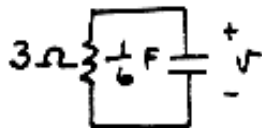
$$RC = (5 \times 10^5)(2 \times 10^{-6}) = 1$$

Now $v(2) = 4 - 4e^{-1}$ so $v(t) = (4 - 4e^{-1})e^{-(t-2)}$ $t > 2$

$$\therefore v(t) = \begin{cases} 0 & t < 1 \\ 4 - 4e^{-(t-1)} & 1 < t < 2 \\ (4 - 4e^{-1})e^{-(t-2)} & t > 2 \end{cases}$$


P8.6-10 $v(0) = 10V$, need solve for $v(t)$ for $0 < t < 2$

$0 < t < .5$



KCL: $v/3 + \frac{1}{6} \frac{dv}{dt} = 0$ or $(s+2)v = 0$
 so $v(t) = 10e^{-2t}$

$t \geq .5$

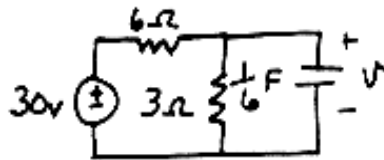

$v(.5) = 10e^{-1} = 3.68$
 KCL: $\frac{1}{6}(v-30) + \frac{v}{3} + \frac{1}{6} \frac{dv}{dt} = 0$
 or $(s+3)v = 30$

$v_n = Be^{-3t}$ & $v_f = 10 \Rightarrow v(t) = 10 + Be^{-3(t-.5)} \Rightarrow v(.5) = 3.68 = 10 + B \Rightarrow B = -6.32$

$$\text{so } v(t) = \begin{cases} 10 \text{ V} & t = 0 \\ 10e^{-2t} & 0 < t < .5 \\ 10[1 - .632e^{-3(t-.5)}] & t > .5 \end{cases}$$

P8.6-11

$i_s = 40 [u(t) - u(t - t_0)]$ A $t_0 = 1\text{ms}$

for $t < 0$ $i_s = 0$

so for $t > 0$ $v = v_n + v_f$ where $v_n = Ae^{-t/\tau}$ and $\tau = L/R = \frac{50 \times 10^{-3}}{50\Omega} = 1 \times 10^{-3} \text{ s} = 1\text{ms}$

and where $v_f = 20 \left(\frac{30}{30+20} \right) 40 = 480 \text{ V}$


$\therefore v(t) = Ae^{-1000t} + 480$

now $i_L(0) = 0$ so $v(0) = 0 \Rightarrow A = -480$ so $v = \begin{cases} 0 & t < 0 \\ 480(1 - e^{-1000t}) & 0 < t < 1\text{ms} \end{cases}$

for $t > 1\text{ms}$ $v = Be^{-1000(t-t_0)}$


$v(1\text{ms}) = B = 480(1 - e^{-1})$

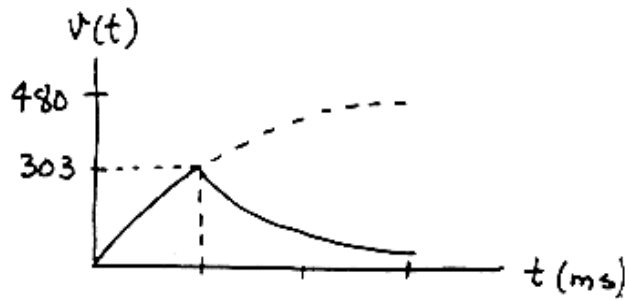$\Rightarrow v(t) = 480(1 - e^{-1}) e^{-1000(t-t_0)}$




P8.6-12

$t < 0$

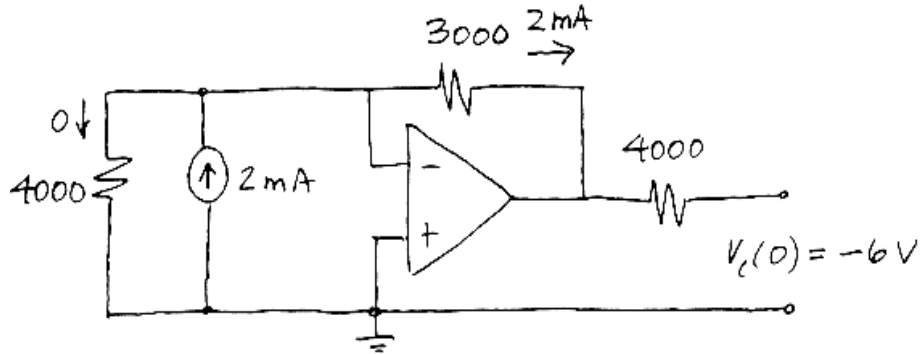

$t \geq 0$:

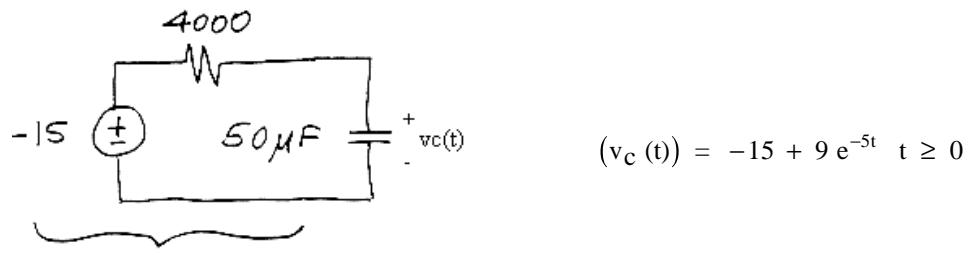


Thevenin equivalent of the circuit connected to the capacitor

Section 8-7 The Response of an RL or RC Circuit to a Nonconstant Source

P8.7-1

$t = 0^-$ (steady-state)

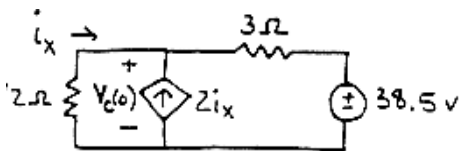


$$\text{KVL a: } 12i_x + 3(3i_x) + 38.5 = 0$$

$$\Rightarrow i_x = 01.83 \text{ A}$$

$$\text{also } \underline{v_c(0^-) - 12i_x = 22 \text{ V} = v_c(0^+)}$$

$t > 0$

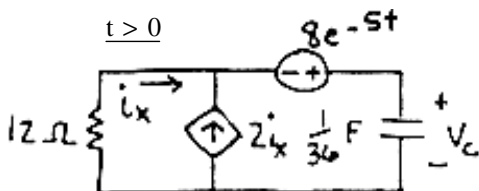

$$\text{KVL a: } \underline{12i_x - 8e^{-5t} + v_c = 0} \quad (1)$$

$$\text{KCL: } -i_x - 2i_x + (1/36) \frac{dv_c}{dt} = 0 \Rightarrow i_x = \underline{\frac{1}{108} \frac{dv_c}{dt}} \quad (2)$$

(2) into (1) yields $\frac{dv_c}{dt} + 9v_c = 72e^{-5t} \Rightarrow v_{Cn}(t) = Ae^{-9t}$


Try $v_{Cf}(t) = Be^{-5t}$ & plug into D.E. $\Rightarrow B = 18$

$\therefore v_c(t) = Ae^{-9t} + 18e^{-5t}$

$v_c(0) = 22 = A + 18 \Rightarrow A = 4 \quad \therefore v_c(t) = 4e^{-9t} + 18e^{-5t} \text{ V}$


P8.7-2

$t = 0^-$ (steady-state)

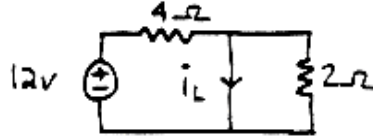

$i_L(0^-) = \frac{12 \text{ V}}{4\Omega} = 3 \text{ A} = i_L(0^+)$

$t > 0$

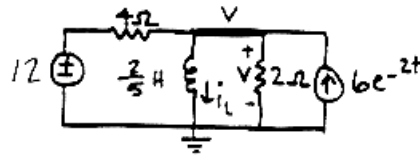

KCL at v: $\frac{(v-12)}{4} + i_L + \frac{v}{2} = 6e^{-2t}$ (1)

also: $v = (2/5) di_L / dt$ (2)

Plugging (2) into (1) $\Rightarrow di_L / dt + (10/3) i_L = 10 + 20e^{-2t}$

$\therefore i_{L_n}(t) = Ae^{-10/3t}$, try $i_{L_f}(t) = B + Ce^{-2t}$ & plugging into D.E.

& equating like terms $\Rightarrow B=3, C=15$


$\therefore i_L(t) = Ae^{-10/3t} + 3 + 15e^{-2t}, i_L(0) = 3 = A + 3 + 15 \Rightarrow A = -15$

$\therefore i_L(t) = -15e^{-(10/3)t} + 3 + 15e^{-2t}$

Now $v(t) = 2/5 \frac{di_L}{dt} = 20e^{-(10/3)t} - 12e^{-2t} \text{ V}$


P8.7-3

$t = 0^-$

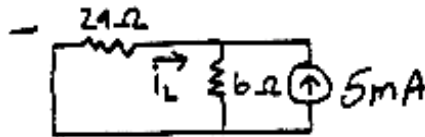

Current divider $\Rightarrow i_L(0^-) = -5 \left(\frac{6}{6+24} \right) = -1 \text{ mA}$

$t > 0$

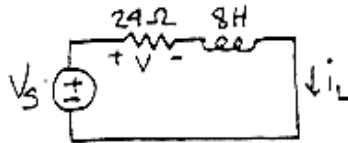

$v_s = 25 \sin 4000t$

KVL a: $-25 \sin 4000t + 24i_L + .008 \frac{di_L}{dt} = 0$

$\frac{di_L}{dt} + 3000i_L = \frac{25}{.008} \sin 4000t$

$i_{L_n}(t) = Ae^{-3000t}$, try $i_{L_f}(t) = B \cos 4000t + C \sin 4000t$ & plug into D.E. and equate like terms $\Rightarrow B = -1/2, C = 3/8$

$\therefore i_L(t) = Ae^{-3000t} - (1/2) \cos 4000t + (3/8) \sin 4000t$

$i_L(0^+) = i_L(0^-) = -1 = A - 1/2 \Rightarrow A = -1/2$

$\therefore i_L(t) = -(1/2)e^{-3000t} - (1/2) \cos 4000t + (3/8) \sin 4000t \text{ mA}$

but $v(t) = 24i_L(t) = 12 e^{-3000t} - 12 \cos 4000t + 9 \sin 4000t \text{ V}$


P8.7-4

$t = 0^-$ Steady-state



$$v_c(0^-) = 0 = v_c(0^+)$$

$t > 0$

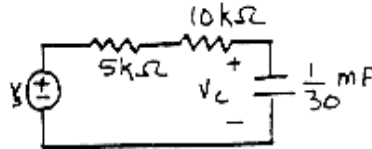

$$v_s = 10\cos 2t$$

$$\text{KVL a: } -10\cos 2t + 15 \left(\frac{1}{30} \frac{dv_c}{dt} \right) + v_c = 0$$

$$\frac{dv_c}{dt} + 2v_c = 20 \cos 2t$$

$v_{c_n}(t) = Ae^{-2t}$, try $v_{c_f}(t) = B\cos 2t + C\sin 2t$ & plug into D.E. $\Rightarrow B = C = 5$

$$\therefore v_c(t) = Ae^{-2t} + 5\cos 2t + 5\sin 2t$$


$$\text{Now } v_c(0) = 0 = A + 5 \Rightarrow A = -5$$

$$\therefore \underline{v_c(t) = -5e^{-2t} + 5\cos 2t + 5\sin 2t \text{ V}}$$

P8.7-5

$t < 0$ no sources present $\therefore i(0) = 0$

$t < 0$

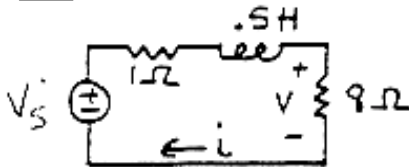

$$v_s = 10\sin 100t$$

$$\text{KVL a: } -10\sin 100t + i + 5\frac{di}{dt} + v = 0 \quad (1)$$

$$\text{also: } i = v/8 \quad (2)$$

$$(2) \text{ into } (1) \text{ yields } \underline{\frac{dv}{dt} + 18v = 160\sin 100t}$$

$\therefore v_n(t) = Ae^{-18t}$, try $v(t) = B\cos 100t + C\sin 100t$ & plug into the D.E. & equate like terms
 $\Rightarrow B = -1.55$ & $C = 0.279$


$$\therefore v(t) = Ae^{-18t} - 1.55\cos 100t + 0.279\sin 100t$$

$$\text{Now from } (2) : v(0) = 8i(0) = 0$$

$$\therefore v(0) = 0 = A - 1.55 \Rightarrow A = 1.55$$

$$\text{so } \underline{v(t) = 1.55e^{-18t} - 1.55\cos 100t + 0.279 \sin 100t \text{ V}}$$

P8.7-6

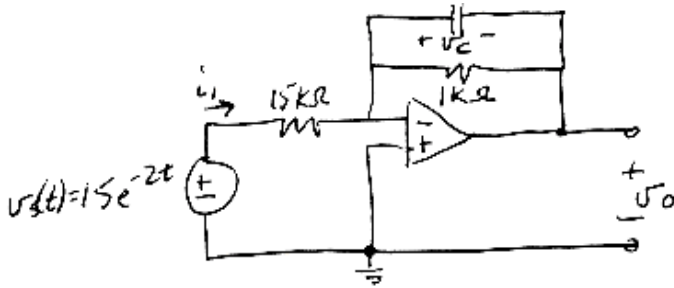

$$v_o = -v_c$$

$$\text{so } v_c(0^-) = v_c(0^+) = -10V$$

$$\left. \begin{aligned} \text{also } i &= \frac{v_s}{15k\Omega} = 0.001e^{-2t} \text{ A} \\ i &= C \frac{dv_c}{dt} + \frac{v_c}{1k\Omega} \end{aligned} \right\} \text{yields } \frac{dv_c}{dt} + 4000v_c = 4000e^{-2t}$$

$$\text{so } v_m = Ae^{-4000t} \quad \text{try } v_f = Be^{-2t} \text{ into D.E. } \Rightarrow B = 1.0005$$

$$\text{then } v_c(t) = v_f + v_m = 1.0005 e^{-2t} + Ae^{-4000t}$$

$$\text{but } v_c(0) = -10 = 1.5000 + A \Rightarrow A = -11.0005$$

$$\text{so } v_L(t) = 1.0005 e^{-2t} - 11.0005 e^{-4000t} \text{ V}$$

$$\text{but } \underline{v_o(t) = -v_c(t) = 11.0005 e^{-4000t} - 1.0005 e^{-2t} \text{ V}, t \geq 0}$$

P8.7-7

From graph $i_L(t) = -\frac{1}{4}t$ mA


$$\text{KVL in circuit yields } 1i_L + 0.4 \frac{di_L}{dt} = v_1 \Rightarrow \frac{di_L}{dt} + 2.5i_L = 2.5v_1$$

$$\text{but } i_L(t) = -\frac{1}{4}t \text{ mA}$$

$$\text{Solving gives } \underline{v_1 = -0.1 - 0.25t \text{ V}}$$

P8.7-8


$t = 0^-$ (steady-state)

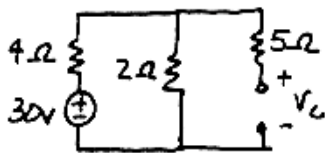

$$v_c(0^-) = \frac{2}{4+2} 30 = 10V$$

$$\therefore v_c(0^+) = 10V$$

$t > 0$

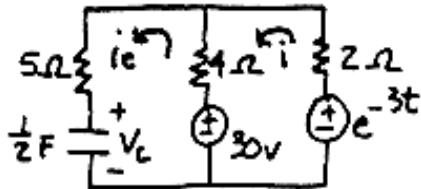

$$\text{KVL : } 5/2 \frac{dv_c}{dt} + v_c + 4 \left(\frac{1}{2} \frac{dv_c}{dt} - i \right) = 30 \quad (1)$$

$$2i + 4 \left(i - \frac{1}{2} \frac{dv_c}{dt} \right) + 30 = e^{-3t} \quad (2)$$

Solving for i in (2) and plugging into (1) yields

$$dv_c/dt + (6/19)v_c = (6/19)(10 + (2/3)e^{-3t})$$

$$v_{c_n} = Ae^{-(6/19)t}$$


$$\text{try } v_{c_f} = B + Ce^{-3t} \text{ \& plug into D.E.} \Rightarrow -3Ce^{-3t} + \frac{6}{19}(B + Ce^{-3t}) = \frac{60}{19} + \frac{4}{19}e^{-3t}$$

$$\text{Equating coefficients and like terms yields } B=10, C=-4/51 \Rightarrow v_c = 10 - \frac{4}{51}e^{-3t} + Ae^{-(6/19)t}$$

$$\text{When } t=0, v_c(0^+) = 10V$$

$$\therefore 10 = 10 - 4/51 + A \quad \therefore v_c(t) = 10 + \frac{4}{51}(e^{-(6/19)t} - e^{-3t})V \Rightarrow A = 4/51$$

P8.7-9 a)

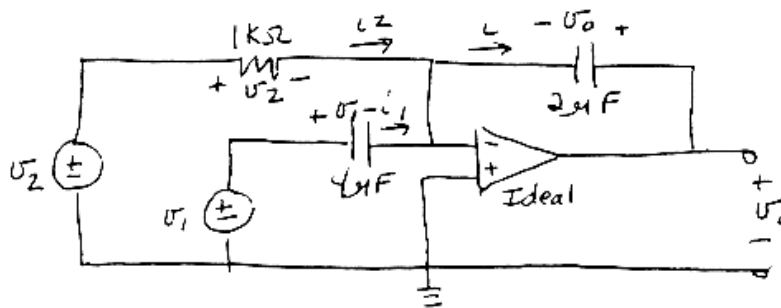

Equations :

$$\left. \begin{array}{l} v_o = -v_{c2} \\ i = C_2 \frac{dv_{c2}}{dt} \\ i = i_1 + i_2 \\ i = C_1 \frac{dv_{c1}}{dt} \\ i_2 = \frac{v_2}{R} \\ v_{c1} = v_1 \end{array} \right\} \Rightarrow v_o(t) = -2v_1(t) - 500 \int_0^t v_2(t) dt$$

b)

Plugging in the sources gives

$$v_o(t) = -20e^{-2000t} + 2.5e^{-1000t} - 2.5V$$

P8.7-10


$$v_c(0^-) = v_c(0^+) = 3V$$

$$\left. \begin{array}{l} v_c(\infty) = 12 + 4000i \\ i = 2mA \end{array} \right\} \Rightarrow v_L(\infty) = 12 - 8 = 4V$$

$$\tau = C R_{eq} = (1 \times 10^{-6})(4 \times 10^3) = 0.004 \text{ sec}, \quad 1/\tau = 250 \text{ sec}^{-1}$$


$$v(t) = 4 + (3-4)e^{-250t} = 4 - e^{-250t} \text{ v, } t \geq 0$$

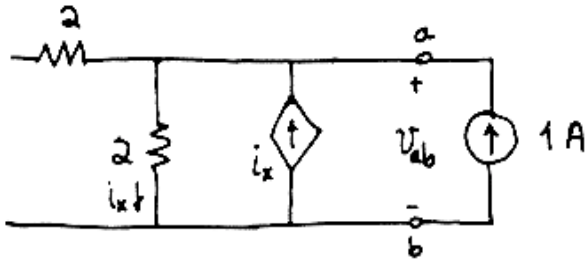P8.7-11 Find the Norton equivalent; First $I_n = I_{sc} = \frac{V_s}{2}$. Next to find R_T remove C & short v_s



$$R_T = \frac{V_{ab}}{1} \quad (\text{note } i_x = 0) \text{ so } R_T = 2$$

Norton:

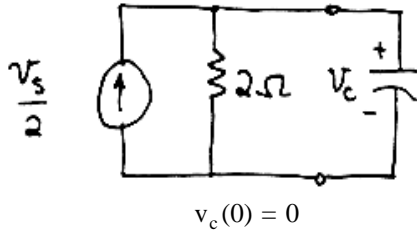

$$\frac{dv}{dt} + \frac{v}{2} = \frac{v_s}{2}$$

$$v_s = \begin{cases} 5t & 0 \leq t \leq 2 \\ 10 & t > 2 \end{cases}$$


$$v = 5t + 10(e^{-t/2} - 1) \quad 0 < t < 2$$

at $t=2$ $v = 10e^{-1} = 3.68$

$t > 2$ $v = Ae^{-t/2} + 10$


at $t=2$ $3.68 = Ae^{-1} + 10$ or $A = 10 - 10e$
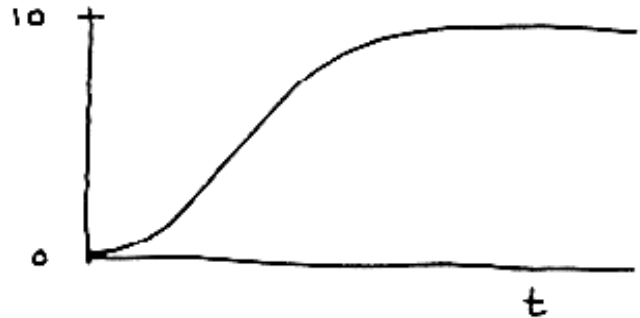
$$v = 10e^{-t/2} - 10e^{-\frac{(t-2)}{2}} + 10 \quad t \geq 2$$



P8.7-12

a)

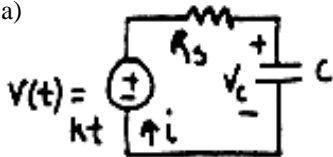

KVL a: $-kt + R_s i + v_s = 0$ and $i = C \frac{dv_c}{dt}$

$$\Rightarrow \frac{dv_c}{dt} + \frac{1}{R_s C} v_c = \frac{k}{R_s C} t$$


$v_c = v_{c_n} + v_{c_f}$, now $v_{c_n} = Ae^{-t/R_s C}$, try $v_{c_f} = B_0 + B_1 t$ & plug into D.E. $\Rightarrow B_1 + \frac{1}{R_s C} [B_0 + B_1 t] = \frac{k}{R_s C} t$

thus $B_0 = -kR_s C$, $B_1 = k$

so have $v_c(t) = Ae^{-t/R_s C} + k(t - R_s C)$, $v_c(0) = 0 = A - kR_s C \Rightarrow A = kR_s C$

$\therefore v_c(t) = k[t - R_s C(1 - e^{-t/R_s C})]$ plugging in $k=1000$, $R_s = 625k\Omega$ & $C=2000pF$ get
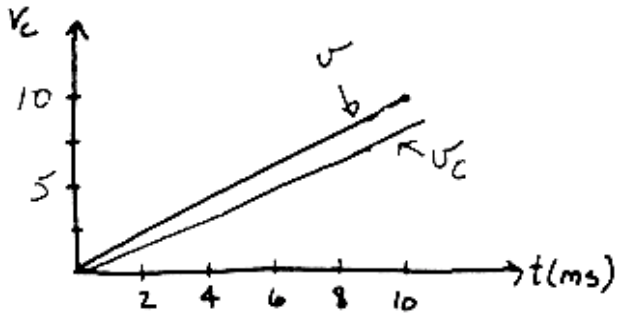
$$v_c(t) = 1000[t - 1.25 \times 10^{-5}(1 - e^{-800t})]$$



v & v_c track well on millisecond time scale

b) $F=qE$, $E=\frac{v_c}{s}$, $q=Cv_c \Rightarrow \therefore F=\frac{C}{s}v_c^2$

Now $F=m\ddot{y}$ where y = transverse deflection of beam and $y(t)$ is described by the differential equation



$$\frac{d^2y}{dt^2} = \frac{C}{ms}v_c^2(t)$$

where $v_c(t)$ is given in part a)

PSpice Problems

SP 8-1 Spice deck corresponding to Problem SP 8-1

```
L1 1 0 1m IC=.789
R1 1 2 6
R2 2 0 12
.TRAN .0001 1.5mS UIC
.PRINT TRAN I(L1)
.PROBE I(L1)
.END
```

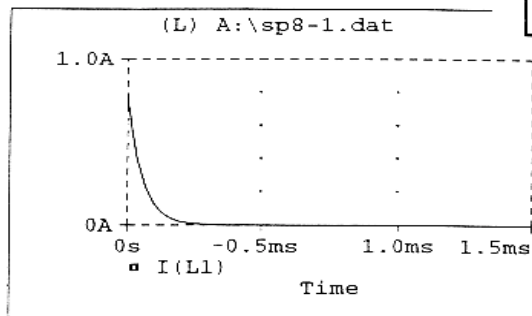
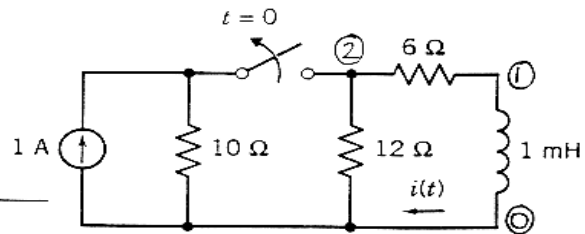


SP 8-2 Spice deck corresponding to Problem SP 8-2

```

C1 1 0 20u IC=12
R1 1 0 1k
.TRAN 5mS 100mS UIC
.PRINT TRAN V(1)
.PROBE V(1)
.END

```

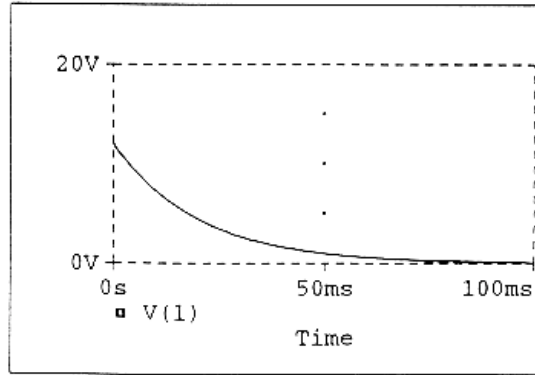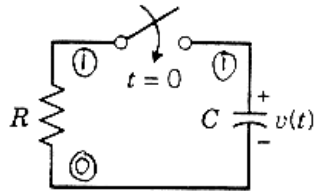

SP 8-3 Spice deck corresponding to Problem SP 8-3

```



V1 1 0 dc 10
R2 2 1 3K
R3 2 3 500
I4 3 0 dc 3m
R5 2 4 1000
C6 4 0 1000n IC=5v

```

```

.tran 1ms 20ms UIC
.PROBE V(4)
.END

```

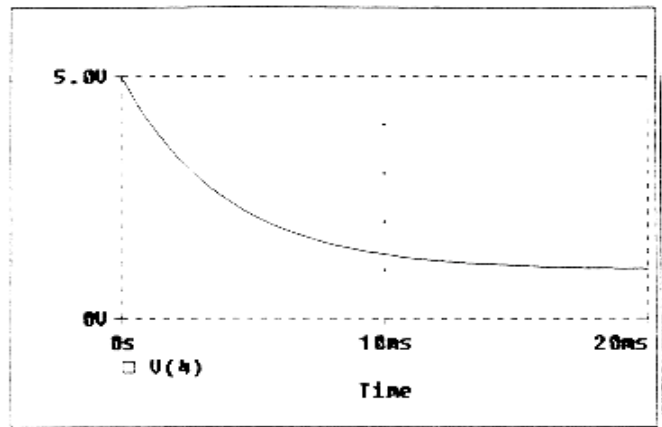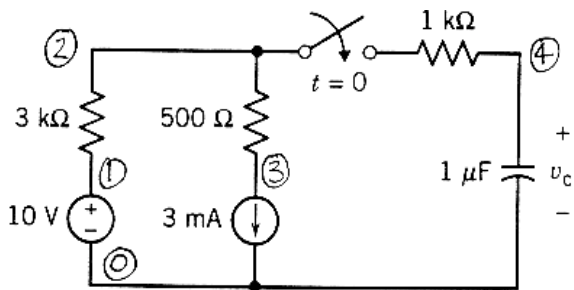


```

SP 8-4      Spice deck corresponding to Problem SP 8-4
V1  1      0      dc      4
R1  1      2      2K
C1  2      0      1000n IC=0
R2  1      3      4K
C2  3      0      1000n IC=0
R3  1      4      8K
C3  4      0      1000n IC=0
R4  1      5      16K
C4  5      0      1000n IC=0

.tran 2ms 80ms UIC
.PROBE
.END

```

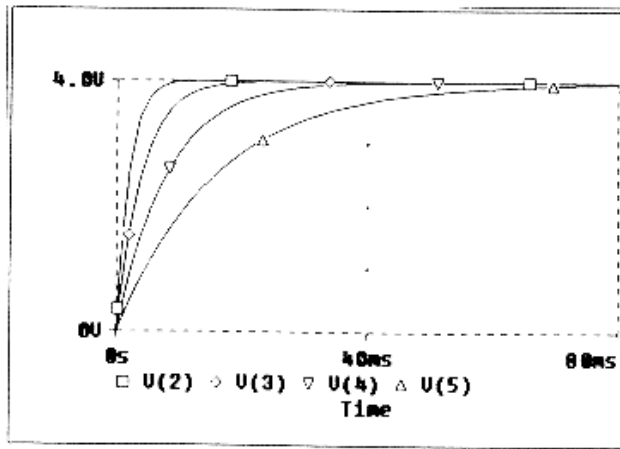

Verification Problems

VP 8-1 First look at the circuit. The initial capacitor voltage is $v_c(0) = 8$. The steady-state capacitor voltage is $v_c = 4$. We expect an exponential transition from 8 volts to 4 volts. That's consistent with the plot. Next, let's check the shape of the exponential transition. From the solution to Problem 1b

$$v_c(t) = 4e^{-\frac{t}{.67}} + 4$$

where t has units of ms. To check the point labeled on the plot, let $t_1 = 133\text{ms}$. Then

$$v_c(t_1) = 4e^{-\left(\frac{1.33}{.67}\right)} + 4 = 4.541 \approx 4.5398$$

So the plot is correct.

VP 8-2

The initial and steady-state inductor currents shown on the plot agree with the values obtained from the circuit.

The solution to Problem 1b gives

$$i_L(t) = -2e^{-\frac{t}{3.75}} + 5 \text{ mA}$$

where t has units of ms. Let $t_1 = 3.75$ ms; then


$$i_L(t_1) = -2e^{-\left(\frac{3.75}{3.75}\right)} + 5 = 4.264 \neq 4.7294$$

so the plot does not correspond to this circuit.

VP 8-3

Notice that the steady-state inductor current does not depend on the inductance, L. The initial and steady-state inductor currents shown on the plot agree with the values obtained from the circuit.

After $t = 0$

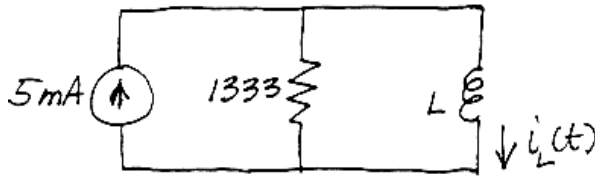

So $I_{sc} = 5\text{mA}$

$$\tau = \frac{L}{1333}$$

The inductor current is given by

$$i_L(t) = -2e^{-\frac{1333t}{L}} + 5 \text{ mA}$$

where t has units of seconds and L has units of henries.

Let $t_1 = 3.75$ ms; then


$$4.836 = i_L(t_1) = -2e^{-\frac{(1333)(.00375)}{L}} + 5 = -2e^{-\frac{5}{L}} + 5$$

$$\text{so } \frac{4.836-5}{-2} = e^{-\frac{5}{L}} \text{ and } L = \frac{-5}{\ln\left(\frac{4.836-5}{-2}\right)} = 2$$


is the required inductance.

First consider the circuit. When $t < 0$ and the circuit is at steady-state


VP 8-4

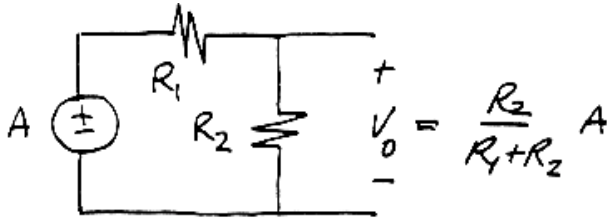

For $t > 0$

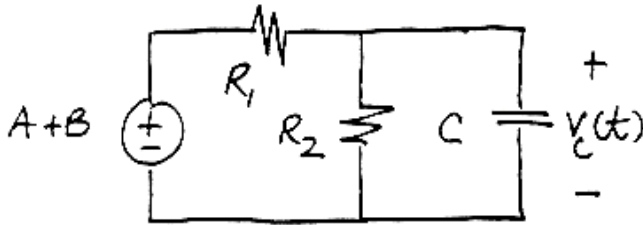
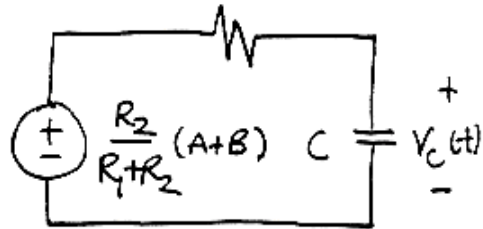
$$R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$



So

$$V_{oc} = \frac{R_2}{R_1 + R_2} (A + B), \quad R_{th} = \frac{R_1 R_2}{R_1 + R_2} \quad \text{and} \quad \tau = \frac{R_1 R_2 C}{R_1 + R_2}$$

Next, consider the plot. The initial capacitor voltage is ($V_o =$) -2 and the steady-state capacitor voltage is ($V_{oc} =$) 4

So
$$v_C(t) = -6e^{-\frac{t}{\tau}} + 4$$

At $t_1 = 1.333$ ms

$$3.1874 = v_C(t_1) = -6e^{-\frac{1.333 \text{ ms}}{\tau}} + 4$$

So
$$\tau = \frac{-1.333 \text{ ms}}{\ln\left(\frac{-4 + 3.1874}{-6}\right)} = 0.67 \text{ ms}$$

Combining the information obtained from the circuit with the information obtained from the plot gives

$$\frac{R_2}{R_1 + R_2} A = -2$$

$$\frac{R_2}{R_1 + R_2} (A + B) = 4$$

$$\frac{R_1 R_2 C}{R_1 + R_2} = 0.67 \text{ ms}$$

There are many ways that A , B , R_1 , R_2 , and C can be chosen to satisfy these equations. Here is one convenient way. Pick $R_1 = 3000$ and $R_2 = 6000$. Then

$$\frac{2A}{3} = -2 \Rightarrow A = -3$$

$$\frac{2(A+B)}{3} = 4 \Rightarrow B - 3 = 6 \Rightarrow B = 9$$

$$2000 \cdot C = \frac{2}{3} \text{ ms} \Rightarrow \frac{1}{3} \mu\text{F} = C$$

Design Problems

DP 8-1

$$6 \text{ V} = \text{the steady state response when the switch is open} = \frac{R_3}{R_1+R_2+R_3} 12 \text{ V} \Rightarrow R_1+R_2=R_3.$$

$$8 \text{ V} = \text{the steady state response when the switch is open} = \frac{R_3}{R_1+R_3} 12 \text{ V} \Rightarrow R_1 = \frac{R_3}{2}.$$

$$10 \text{ ms} = 5 \tau = \frac{R_3}{2} C$$

Let $C = 1 \mu\text{F}$. Then $R_3 = 20 \text{ k}\Omega$, $R_1 = 10 \text{ k}\Omega$ and $R_2 = 10 \text{ k}\Omega$.

DP 8-2

$$1 \text{ mA} = \text{the steady state response when the switch is open} = \frac{12 \text{ V}}{R_1+R_2} \Rightarrow R_1+R_2=12 \text{ k}\Omega.$$

$$4 \text{ mA} = \text{the steady state response when the switch is open} = \frac{12 \text{ V}}{R_1} \Rightarrow R_1=3 \text{ k}\Omega.$$

Therefore, $R_2 = 9 \text{ k}\Omega$.

$$10 \text{ ms} = 5 \tau = 5 \frac{L}{R_1+R_2} = \frac{L}{2400} \Rightarrow L=240 \text{ H}$$

DP 8-3

$R_i = 50 \text{ k}\Omega$ when the switch is open and $R_i = 49 \text{ k}\Omega \approx 50 \text{ k}\Omega$ when the switch is closed so use $R_i = 50 \text{ k}\Omega$.

$$(a) C = \frac{10^{-6}}{5(5 \times 10^3)} = 4 \text{ pF}$$

$$(b) \Delta t = 5(5 \times 10^3)(2 \times 10^{-6}) = 0.5 \text{ s}$$

DP 8-4

$R_i = 50 \text{ k}\Omega$ when the switch is open and $R_i = 49 \text{ k}\Omega \approx 50 \text{ k}\Omega$ when the switch is closed so use $R_i = 50 \text{ k}\Omega$.

$$\text{When the switch is open: } 5e^{-\frac{\Delta t}{\tau}} = (1-k)5 \Rightarrow \ln(1-k) = -\frac{\Delta t}{\tau} \Rightarrow \Delta t = -\tau \ln(1-k)$$


$$\text{When the switch is open: } 5 - 5e^{-\frac{\Delta t}{\tau}} = k5 \Rightarrow \Delta t = -\tau \ln(1-k)$$

$$(a) C = \frac{10^{-6}}{-\ln(1-.95)(5 \times 10^3)} = 6.67 \text{ pF}$$

$$(b) \Delta t = -\ln(1-.95)(5 \times 10^3)(2 \times 10^{-6}) = 0.3 \text{ s}$$


DP 8-5

$t = 0^-$

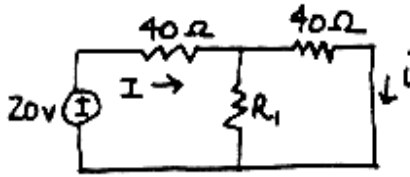

$$\text{Current divisions } i(0^-) = \frac{20V}{40 + \frac{40R_1}{40+R_1}} \cdot \frac{R_1}{R_1+40}$$

$t > 0$

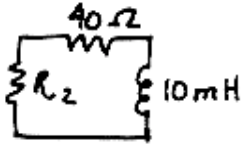

$$i(t) = i(0)e^{-t/\tau} \quad \text{where } \tau = \frac{L}{R} = \frac{10^{-2}}{40+R_2}$$

at $t < 200\mu s$ need $i > 60\text{mA}$ and $i < 180\text{mA}$

Find R_1 to set $i(0) < 180\text{ mA}$


Try a solution: if $R_1 = 40\Omega$, then $i(0) = \frac{1}{6}\text{A} = 166.6\text{mA}$

Then $i(t) = 166.6\text{ mA } e^{-t/\tau}$ at $t_1 = 200\mu s = .2\text{ms} \rightarrow i(t_1) > 60\text{mA}$ required

Try $R_2 = 10\Omega$, then $\tau = \frac{10^{-2}}{50} = .2\text{ms} = \frac{1}{5000}\text{s}$

$$i(t_1) = 166.6 \times 10^{-3} e^{-5000t_1} = 166.6 \times 10^{-3} e^{-1} = 61.2\text{mA}$$

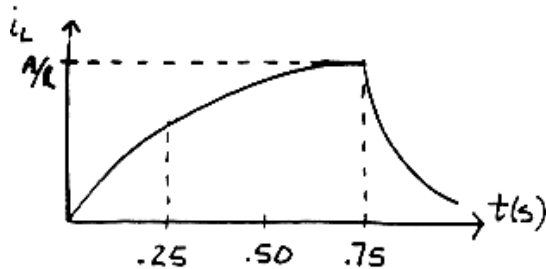DP 8-6 The current wave form will look like:



We need only consider the rise time

$$\begin{aligned} \text{where } i_L(t) &= \frac{V_s}{R}(1-e^{-t/\tau}) \\ &= \frac{A}{R}(1-e^{-t/\tau}) \end{aligned}$$

$$\text{where } \tau = \frac{L}{R_T} = \frac{.2}{3} = \frac{1}{15}$$

$$\therefore i_L(t) = \frac{A}{3}(1-e^{-15t})$$

Now find A so that $i_L^2 R_{\text{fuse}} \geq 10\text{W}$ during $.25 \leq t \leq .75$

$$\therefore \text{want } [i_L^2(.25)]R_{\text{fuse}} = 10\text{W}$$

$$\frac{A^2}{9}(1-e^{-15(.25)})^2(1) = 10 \Rightarrow \underline{A = 9.715\text{ V}}$$