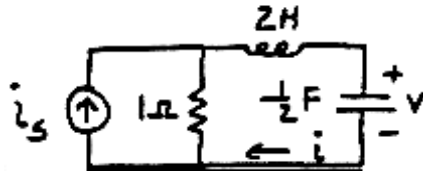


Chapter 9 - Complete Response of Circuits with Two Energy Storage Elements

Exercises

Ex. 9.3-1




$$\begin{aligned} \text{KVL a: } 2 \frac{di}{dt} + v + 1(i - i_s) &= 0 \\ \Rightarrow v &= -2 \frac{di}{dt} - i + i_s \end{aligned}$$

$$i = \frac{1}{2} \frac{dv}{dt} = \frac{1}{2} \frac{d}{dt} (-2 \frac{di}{dt} - i + i_s) = \frac{1}{2} \frac{di_s}{dt} - \frac{1}{2} \frac{di}{dt} - \frac{d^2 i}{dt^2}$$

$$\therefore \frac{d^2 i}{dt^2} + \frac{1}{2} \frac{di}{dt} + i = \frac{1}{2} \frac{di_s}{dt}$$

Ex. 9.3-2

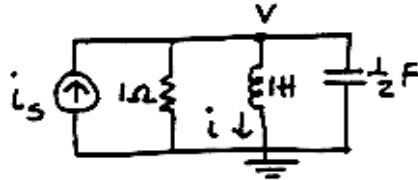


$$\begin{aligned} \text{KCL at } v: \text{ using } s = \frac{d}{dt} \\ \frac{v}{1} + i + \frac{1}{2} s v = i_s \end{aligned} \quad (1)$$

$$\text{also } v = si \quad (2) \text{ Solving for } i \text{ in (1) \& plugging into} \quad (2)$$

$$\text{yields } s^2 v + 2sv + 2v = 2si_s \quad \text{or} \quad \frac{d^2 v}{dt^2} + 2 \frac{dv}{dt} + 2v = 2 \frac{di_s}{dt}$$

Ex. 9.3-3

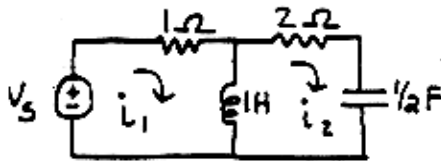

$$\text{KVL ai}_1: i_1 + s(i_1 - i_2) = v_s \quad (1)$$

$$\text{where } s = \frac{d}{dt}$$


$$\text{KVL ai}_2: 2i_2 + 2\left(\frac{1}{s}\right)i + s(i_2 - i_1) = 0$$

$$\Rightarrow i_1 = 2\left(\frac{1}{s}\right)i_2 + \left(\frac{1}{s^2}\right)i_2 + i_2 \quad (2)$$

Plugging (2) into (1) yields

$$3s^2 i_2 + 4s i_2 + 2i_2 = s^2 v_s \quad \text{or} \quad 3 \frac{d^2 i_2}{dt^2} + 4 \frac{di_2}{dt} + 2i_2 = \frac{d^2 v_s}{dt^2}$$

Ex. 9.4-1

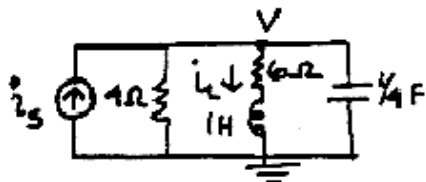

$$\text{KVL at } v: \frac{v}{4} + i_L + \frac{1}{4} \frac{dv}{dt} = i_s \quad (1)$$


$$\text{KVL right mesh a: } v = 6i_L + \frac{di_L}{dt} \quad (2)$$

$$\text{Plugging (2) into (1) yields } \frac{d^2 i_L}{dt^2} + 7 \frac{di_L}{dt} + 10i_L = 4i_s$$

$$\therefore \text{characteristic equation } \Rightarrow s^2 + 7s + 10 = 0$$

Ex. 9.4-2 natural frequencies $\Rightarrow s = -2, -5$

Assume zero initial conditions

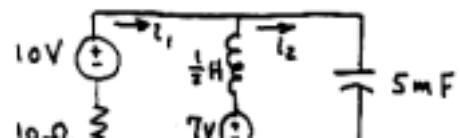

$$\text{loop 1 : } 10i_1 + \frac{1}{2} \frac{di_1}{dt} - \frac{1}{2} \frac{di_2}{dt} = 10 - 7$$

$$\text{loop 2 : } -\frac{1}{2} \frac{di_1}{dt} + \frac{1}{2} \frac{di_2}{dt} + 200 \int i_2 dt = 7$$

$$\text{determinant : } \begin{bmatrix} \left(10 + \frac{1}{2}s\right) & -\frac{1}{2}s \\ -\frac{1}{2}s & \left(\frac{1}{2}s + \frac{200}{s}\right) \end{bmatrix}$$

$$s^2 + 20s + 400 = 0, \quad \therefore s = -10 \pm j 17.3$$

Ex. 9.5-1

Let $i_s = 0$, have parallel RLC circuit

$$\alpha = \frac{1}{2RC} = \frac{1}{2(6)(1/42)} = 7/2$$


$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(7)(1/42)} = 6$$

$$\therefore s = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2} = -7/2 \pm \sqrt{(7/2)^2 - 6} = -1, -6$$

$$\therefore v_n(t) = A_1 e^{-t} + A_2 e^{-6t}$$

Need $v_n(0)$ and $\left. \frac{dv_n}{dt} \right|_{t=0}$ to evaluate A_1 & A_2

$t = 0^+$

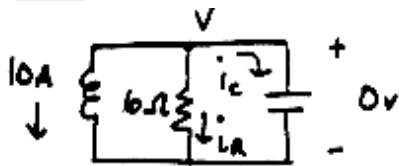


$$i_R = 0 \quad \therefore i_c = -10 \text{ A}$$

$$\Rightarrow \left. \frac{dv}{dt} \right|_{t=0} = \frac{i_c(0)}{C} = \frac{-10}{1/42} = -420 \frac{\text{V}}{\text{s}}$$

$$\text{So } \left. \begin{array}{l} v_n(0) = 0 = A_1 + A_2 \\ \left. \frac{dv_n}{dt} \right|_{t=0} = -420 = -A_1 - 6A_2 \end{array} \right\} A_1 = -84, A_2 = 84$$

$$\therefore v_n(t) = -84e^{-t} + 84e^{-6t} \text{ V}$$

Ex. 9.5-2

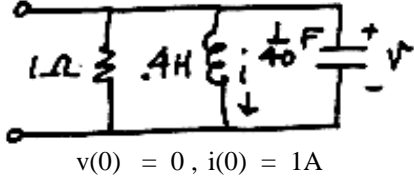

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0 \Rightarrow s^2 + 40s + 100 = 0$$

$$s = -2.7, -37.3$$

$$v_n = A_1 e^{-2.7t} + A_2 e^{-37.3t}, v(0) = 0 = A_1 + A_2 \quad (1)$$

KCL at $t = 0^+$ yields: $\frac{v(0^+)}{1} + i(0^+) + \frac{1}{40} \frac{dv(0^+)}{dt} = 0$

$$\therefore \frac{dv(0^+)}{dt} = -40v(0^+) - 40i(0^+) = -40(1) = -2.7A_1 - 37.3A_2 \quad (2)$$

from (1) and (2) $\Rightarrow A_1 = -1.16, A_2 = 1.16$

So $v(t) = v_n(t) = -1.16e^{-2.7t} + 1.16e^{-37.3t}$


Ex. 9.6-1

For parallel RLC

$$\alpha = \frac{1}{2RC} = \frac{1}{2(10)(10^{-3})} = 50, \omega_o^2 = \frac{1}{LC} = \frac{1}{(0.4)(10^{-3})} = 2500$$

$$\therefore s = -50 \pm \sqrt{(50)^2 - 2500} = -50, -50$$
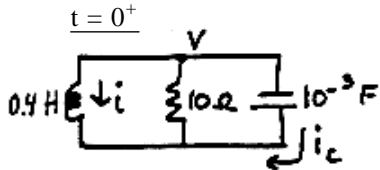
$$\therefore v_n(t) = A_1 e^{-50t} + A_2 t e^{-50t}$$



with $i(0^+) = 0$ & $v(0^+) = 8V \Rightarrow i_c = \frac{-v(0^+)}{10\Omega} = -.8V$


$$\therefore \left. \frac{dv}{dt} \right|_{t=0^+} = \frac{i_c(0^+)}{c} = -800 \text{ V/s}$$

So $v_n(0) = 8 = A_1 \Rightarrow v_n(t) = 8e^{-50t} + A_2 t e^{-50t}$

$$\frac{dv(0)}{dt} = -800 = -400 + A_2 \Rightarrow A_2 = -400$$

$$\therefore \underline{v_n(t) = 8e^{-50t} - 400t e^{-50t} \text{ V}}$$

Ex. 9.7-1

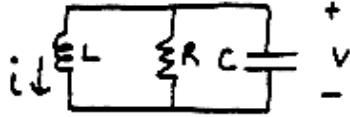


$$\alpha = \frac{1}{2RC} = \frac{1}{2(62.5)(10^{-6})} = 8000$$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(.01)(10^{-6})} = 10^8$$

$$\therefore s = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2} = -8000 \pm \sqrt{(8000)^2 - 10^8} = -8000 \pm j 6000$$

$$\therefore v_n(t) = e^{-8000t} [A_1 \cos 6000 t + A_2 \sin 6000t]$$

$t=0^+$

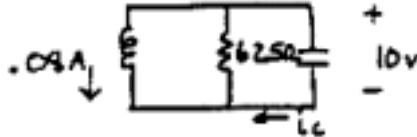

$$\text{KCL at top: } .08 + \frac{10}{62.5} + i_c = 0$$

$$\Rightarrow i_c(0^+) = -24 \text{ A}$$

$$\therefore \frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C} = -2.4 \times 10^5 \text{ V/s}$$

$$\text{So } v_n(0) = 10 = A_1$$

$$\frac{dv_n(0)}{dt} = -2.4 \times 10^5 = 6000A_2 - 8000(10) \Rightarrow A_2 = -26.7$$

$$\therefore v_n(t) = e^{-8000t} [10 \cos 6000 t - 26.7 \sin 6000t] \text{ V}$$

Ex. 9.8-1

(a) $v'' + 5v' + 6v = 8$

Try $v_f = B$ & plug into above $\Rightarrow 6B = 8 \therefore v_f = 8/6 \text{ V}$

(b) $v'' + 5v' + 6v = 3e^{-4t}$

Try $v_f = Be^{-4t}$ & plug into above

$$\Rightarrow (-4)^2 B + 5(-4)B + 6B = 3 \Rightarrow B = 3/2$$

$$\therefore v_f = 3/2 e^{-4t}$$

(c) $v'' + 5v' + 6v = 2e^{-2t}$

Try $v_f = Bte^{-2t}$ (since -2 is a natural frequency)

$$\Rightarrow (4t-4)B + 5B(1-2t) + 6Bt = 2 \Rightarrow B = 2$$

$$\therefore v_f = 2te^{-2t}$$

Ex. 9.8-2

$$i'' + 9i' + 20i = 36 + 12t$$

Try $i_f = A + Bt$ & plug into above


$$0 + 9B + 20(A + Bt) = 36 + 12t$$

$$\Rightarrow 20Bt = 12t, \Rightarrow B = .6$$

$$\Rightarrow 9B + 20A = 36, \Rightarrow A = 1.53$$

$$\therefore i_f = 1.53 + 0.6t \text{ A}$$

Ex 9.9-1

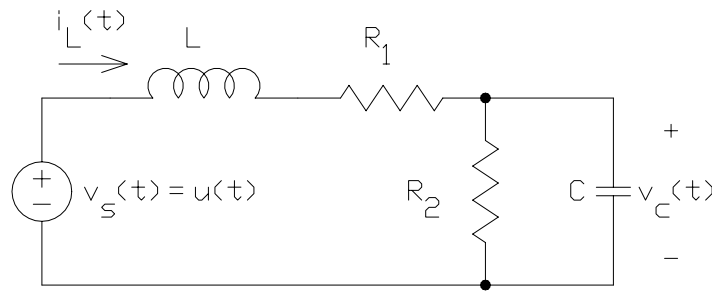

When the circuit reaches steady state after $t = 0$, the capacitor acts like an open circuit and the inductor acts like a short circuit. Under these conditions

$$v_C(\infty) = \frac{R_2}{R_1 + R_2} 1$$

Next, represent the circuit by a 2nd order differential equation:

KCL at the top node of R_2 gives:

$$\frac{v_C(t)}{R_2} + C \frac{d}{dt} v_C(t) = i_L(t)$$

KVL around the outside loop gives:

$$v_s(t) = L \frac{d}{dt} i_L(t) + R_1 i_L(t) + v_C(t)$$

Use the substitution method to get

$$\begin{aligned} v_s(t) &= L \frac{d}{dt} \left(\frac{v_C(t)}{R_2} + C \frac{d}{dt} v_C(t) \right) + R_1 \left(\frac{v_C(t)}{R_2} + C \frac{d}{dt} v_C(t) \right) + v_C(t) \\ &= LC \frac{d^2}{dt^2} v_C(t) + \left(\frac{L}{R_2} + R_1 C \right) \frac{d}{dt} v_C(t) + \left(1 + \frac{R_1}{R_2} \right) v_C(t) \end{aligned}$$

(a) $C = 1 \text{ F}$, $L = 0.25 \text{ H}$, $R_1 = R_2 = 1.309 \text{ } \Omega$

Use the steady state response as the forced response:

$$v_f = v_C(\infty) = \frac{R_2}{R_1 + R_2} 1 = \frac{1}{2}$$

The characteristic equation is

$$s^2 + \left(\frac{1}{R_2 C} + \frac{R_1}{L} \right) s + \left(\frac{1 + \frac{R_1}{R_2}}{LC} \right) = s^2 + 6s + 8 = (s + 2)(s + 4)$$

so the natural response is

$$v_n = A_1 e^{-2t} + A_2 e^{-4t} \text{ V}$$

The complete response is

$$v_c(t) = \frac{1}{2} + A_1 e^{-2t} + A_2 e^{-4t} \text{ V}$$

$$i_L(t) = \frac{v_c(t)}{1.309} + \frac{d}{dt} v_c(t) = -1.236 A_1 e^{-2t} - 3.236 A_2 e^{-4t} + 0.3819$$

At $t = 0+$

$$0 = v_c(0+) = A_1 + A_2 + 0.5$$

$$0 = i_L(0+) = -1.236 A_1 - 3.236 A_2 + 0.3819$$

Solving these equations gives $A_1 = -1$ and $A_2 = 0.5$, so

$$v_c(t) = \frac{1}{2} - e^{-2t} + \frac{1}{2} e^{-4t} \text{ V}$$

(b) $C = 1 \text{ F}$, $L = 1 \text{ H}$, $R_1 = 3 \text{ } \Omega$, $R_2 = 1 \text{ } \Omega$

Use the steady state response as the forced response:

$$v_f = v_c(\infty) = \frac{R_2}{R_1 + R_2} 1 = \frac{1}{4}$$

The characteristic equation is

$$s^2 + \left(\frac{1}{R_2 C} + \frac{R_1}{L} \right) s + \left(\frac{1 + \frac{R_1}{R_2}}{LC} \right) = s^2 + 4s + 4 = (s + 2)^2$$

so the natural response is

$$v_f = (A_1 + A_2 t) e^{-2t} \text{ V}$$

The complete response is

$$v_c(t) = \frac{1}{4} + (A_1 + A_2 t) e^{-2t} \text{ V}$$

$$i_L(t) = v_c(t) + \frac{d}{dt} v_c(t) = \frac{1}{4} + ((A_2 - A_1) - A_2 t) e^{-2t}$$

At $t = 0+$

$$0 = v_c(0+) = A_1 + \frac{1}{4}$$

$$0 = i_L(0+) = \frac{1}{4} + A_2 - A_1$$

Solving these equations gives $A_1 = -0.25$ and $A_2 = -0.5$, so

$$v_c(t) = \frac{1}{4} - \left(\frac{1}{4} + \frac{1}{2} t \right) e^{-2t} \text{ V}$$

(c) $C = 0.125 \text{ F}$, $L = 0.5 \text{ H}$, $R_1 = 1 \text{ } \Omega$, $R_2 = 4 \text{ } \Omega$

Use the steady state response as the forced response:

$$v_f = v_c(\infty) = \frac{R_2}{R_1 + R_2} 1 = \frac{4}{5}$$

The characteristic equation is

$$s^2 + \left(\frac{1}{R_2 C} + \frac{R_1}{L} \right) s + \left(\frac{1 + \frac{R_1}{R_2}}{LC} \right) = s^2 + 4s + 20 = (s + 2 - j4)(s + 2 + j4)$$

so the natural response is

$$v_f = e^{-2t} (A_1 \cos 4t + A_2 \sin 4t) \text{ V}$$

The complete response is

$$v_c(t) = 0.8 + e^{-2t} (A_1 \cos 4t + A_2 \sin 4t) \text{ V}$$

$$i_L(t) = \frac{v_c(t)}{4} + \frac{1}{8} \frac{d}{dt} v_c(t) = 0.2 + \frac{A_2}{2} e^{-2t} \cos 4t - \frac{A_1}{2} e^{-2t} \sin 4t$$

At $t = 0+$


$$0 = v_c(0+) = 0.8 + A_1$$

$$0 = i_L(0+) = 0.2 + \frac{A_2}{2}$$

Solving these equations gives $A_1 = -0.8$ and $A_2 = -0.4$, so

$$v_c(t) = 0.8 - e^{-2t} (0.8 \cos 4t + 0.4 \sin 4t) \text{ V}$$

Ex 9.9-2

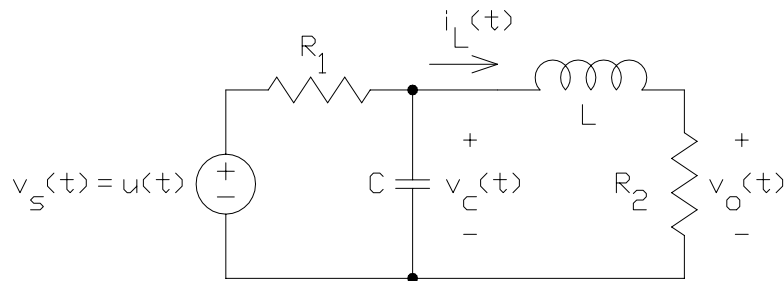

When the circuit reaches steady state after $t = 0$, the capacitor acts like an open circuit and the inductor acts like a short circuit. Under these conditions

$$v_c(\infty) = \frac{R_2}{R_1 + R_2} 1, \quad i_L(\infty) = \frac{1}{R_1 + R_2} \quad \text{and} \quad v_o(\infty) = \frac{R_2}{R_1 + R_2} 1$$

Next, represent the circuit by a 2nd order differential equation:

KVL around the right-hand mesh gives:

$$v_C(t) = L \frac{d}{dt} i_L(t) + R_2 i_L(t)$$

KCL at the top node of the capacitor gives:

$$\frac{v_s(t) - v_C(t)}{R_1} - C \frac{d}{dt} v_C(t) = i_L(t)$$

Use the substitution method to get

$$\begin{aligned} v_s(t) &= R_1 C \frac{d}{dt} \left(L \frac{d}{dt} i_L(t) + R_2 i_L(t) \right) + \left(L \frac{d}{dt} i_L(t) + R_2 i_L(t) \right) + R_1 i_L(t) \\ &= R_1 L C \frac{d^2}{dt^2} i_L(t) + (L + R_1 R_2 C) \frac{d}{dt} i_L(t) + (R_1 + R_2) i_L(t) \end{aligned}$$

Using $v_o(t) = \frac{i_L(t)}{R_2}$ gives

$$v_o(t) = \frac{R_1}{R_2} L C \frac{d^2}{dt^2} i_L(t) + \left(\frac{L}{R_2} + R_1 C \right) \frac{d}{dt} i_L(t) + \left(\frac{R_1 + R_2}{R_2} \right) i_L(t)$$

(a) $C = 1 \text{ F}$, $L = 0.25 \text{ H}$, $R_1 = R_2 = 1.309 \text{ } \Omega$

Use the steady state response as the forced response:

$$v_f = v_o(\infty) = \frac{R_2}{R_1 + R_2} 1 = \frac{1}{2}$$

The characteristic equation is

$$s^2 + \left(\frac{1}{R_1 C} + \frac{R_2}{L} \right) s + \left(\frac{1 + \frac{R_2}{R_1}}{LC} \right) = s^2 + 6s + 8 = (s + 2)(s + 4)$$

so the natural response is

$$v_n = A_1 e^{-2t} + A_2 e^{-4t} \text{ V}$$

The complete response is

$$\begin{aligned} v_o(t) &= \frac{1}{2} + A_1 e^{-2t} + A_2 e^{-4t} \text{ V} \\ i_L(t) &= \frac{v_o(t)}{1.309} = \frac{1}{2.618} + \frac{A_1}{1.309} e^{-2t} + \frac{A_2}{1.309} e^{-4t} \text{ V} \end{aligned}$$

$$v_C(t) = 1.309 i_L(t) + \frac{1}{4} \frac{d}{dt} i_L(t) = \frac{1}{2} + 0.6167 A_1 e^{-2t} + 0.2361 A_2 e^{-4t}$$

At $t = 0+$

$$0 = i_L(0+) = \frac{1}{2.618} + \frac{A_1}{1.309} + \frac{A_2}{1.309}$$

$$0 = v_C(0+) = \frac{1}{2} + 0.6167 A_1 + 0.2361 A_2$$

Solving these equations gives $A_1 = -1$ and $A_2 = 0.5$, so

$$v_o(t) = \frac{1}{2} - e^{-2t} + \frac{1}{2}e^{-4t} \text{ V}$$

(b) $C = 1 \text{ F}$, $L = 1 \text{ H}$, $R_1 = 1 \text{ } \Omega$, $R_2 = 3 \text{ } \Omega$

Use the steady state response as the forced response:

$$v_f = v_o(\infty) = \frac{R_2}{R_1 + R_2} 1 = \frac{3}{4}$$

The characteristic equation is

$$s^2 + \left(\frac{1}{R_1 C} + \frac{R_2}{L} \right) s + \left(\frac{1 + \frac{R_2}{R_1}}{LC} \right) = s^2 + 4s + 4 = (s + 2)^2$$

so the natural response is

$$v_f = (A_1 + A_2 t) e^{-2t} \text{ V}$$

The complete response is

$$v_o(t) = \frac{3}{4} + (A_1 + A_2 t) e^{-2t} \text{ V}$$

$$i_L(t) = \frac{v_o(t)}{3} = \frac{1}{4} + \left(\frac{A_1}{3} + \frac{A_2}{3} t \right) e^{-2t} \text{ V}$$

$$v_C(t) = 3i_L(t) + \frac{d}{dt} i_L(t) = \frac{3}{4} + \left(\left(\frac{A_1}{3} + \frac{A_2}{3} \right) + \frac{A_2}{3} t \right) e^{-2t}$$

At $t = 0+$

$$0 = i_L(0+) = \frac{A_1}{3} + \frac{1}{4}$$

$$0 = v_C(0+) = \frac{3}{4} + \frac{A_1}{3} + \frac{A_2}{3}$$

Solving these equations gives $A_1 = -0.75$ and $A_2 = -1.5$, so

$$v_o(t) = \frac{3}{4} - \left(\frac{3}{4} + \frac{3}{2} t \right) e^{-2t} \text{ V}$$

(c) $C = 0.125 \text{ F}$, $L = 0.5 \text{ H}$, $R_1 = 4 \text{ } \Omega$, $R_2 = 1 \text{ } \Omega$

Use the steady state response as the forced response:

$$v_f = v_o(\infty) = \frac{R_2}{R_1 + R_2} 1 = \frac{1}{5}$$

The characteristic equation is

$$s^2 + \left(\frac{1}{R_1 C} + \frac{R_2}{L} \right) s + \left(\frac{1 + \frac{R_2}{R_1}}{LC} \right) = s^2 + 4s + 20 = (s + 2 - j4)(s + 2 + j4)$$

so the natural response is

$$v_f = e^{-2t} (A_1 \cos 4t + A_2 \sin 4t) \text{ V}$$

The complete response is

$$v_o(t) = 0.2 + e^{-2t} (A_1 \cos 4t + A_2 \sin 4t) \text{ V}$$

$$i_L(t) = \frac{v_o(t)}{1} = 0.2 + e^{-2t} (A_1 \cos 4t + A_2 \sin 4t) \text{ V}$$

$$v_C(t) = i_L(t) + \frac{1}{2} \frac{d}{dt} i_L(t) = 0.2 + 2A_2 e^{-2t} \cos 4t - 2A_1 e^{-2t} \sin 4t$$

At $t = 0^+$

$$0 = i_L(0^+) = 0.2 + A_1$$

$$0 = v_C(0^+) = 0.2 + 2A_2$$


Solving these equations gives $A_1 = -0.8$ and $A_2 = -0.4$, so

$$v_c(t) = 0.2 - e^{-2t} (0.2 \cos 4t + 0.1 \sin 4t) \text{ V}$$

Ex. 9.10-1

no initial stored energy $\Rightarrow v_1(0^+) = v_2(0^+) = i(0^+) = 0$

$t = 0^+$

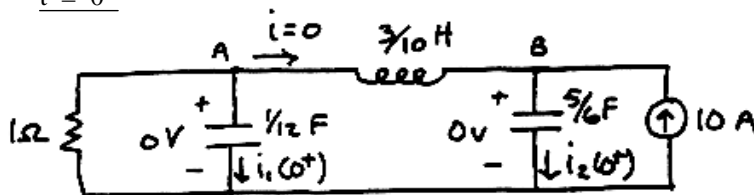


$$\text{KVL} : -0 + \frac{3}{10} \frac{di(0^+)}{dt} + 0 = 0 \Rightarrow \frac{di(0^+)}{dt} = 0$$

$$\text{KCL at A} : \frac{0V}{1\Omega} + i_1(0^+) + 0 = 0 \Rightarrow \frac{dv_1(0^+)}{dt} = 0$$

$$\text{KCL at B} : -0 + i_2(0^+) - 10 = 0 \Rightarrow i_2(0^+) = 5/6 \frac{dv_2(0^+)}{dt} = 10 \Rightarrow \frac{dv_2(0^+)}{dt} = 12 \text{ V/s}$$

$t > 0$

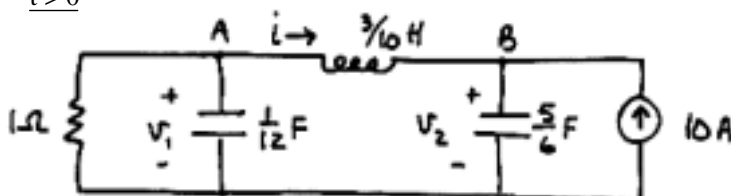

Continued

$$\text{KCL at A: } \frac{v_1}{1} + \frac{1}{12}v_1' + i = 0 \quad (1)$$

$$\text{KCL at B: } -i + (5/6)v_2' = 10 \quad (2)$$

$$\text{KCL } \downarrow \text{ :-}v_1 + (3/10)i' + v_2 = 0 \quad (3)$$

Eliminating i from (1) & (3) yields

$$v_1 + \frac{1}{12}v_1' + (5/6)v_2' - 10 = 0 \quad (4)$$

$$-v_1 + \frac{3}{10}\left(\frac{5}{6}v_2''\right) + v_2 = 0 \quad (5)$$

$$\text{from (5) } v_1 = v_2 + \frac{1}{4}v_2'' \quad \therefore v_1' = v_2' + (1/4)v_2'''$$

Now plugging into (4) yields

$$v_2' + \frac{1}{4}v_2'' + \frac{1}{12}\left(v_2' + \frac{1}{4}v_2'''\right) + \frac{5}{6}v_2' = 10$$

$$\underline{v_2'' + 12v_2'' + 44v_2' + 48v_2 = 480}$$

$$v_{2n}: s^3 + 12s^2 + 44s + 48 = 0 \Rightarrow s = -2, -4, -6$$

$$\therefore v_{2n} = A_1e^{-2t} + A_2e^{-4t} + A_3e^{-6t}$$

$$v_{2f}: \text{try } v_{2f} = B \text{ and plug into Diff. Eq. } \Rightarrow B = 10$$

$$\therefore v_2(t) = A_1e^{-2t} + A_2e^{-4t} + A_3e^{-6t} + 10$$

$$\text{Recall } v_2(0^+) = 0, \frac{dv_2(0^+)}{dt} = 12 \text{ V/s}$$

$$\text{from (5) } \frac{d^2v_2(0^+)}{dt^2} = 4[v_1(0^+) - v_2(0^+)] = 0$$

$$v_2(0^+) = 0 = A_1 + A_2 + A_3 + 10 \quad (6)$$

$$\frac{dv_2(0^+)}{dt} = 12 = -2A_1 - 4A_2 - 6A_3 \quad (7)$$

$$\frac{d^2v_2(0^+)}{dt^2} = 0 = 4A_1 + 16A_2 + 36A_3 \quad (8)$$

Solving (6)–(8) simultaneously yields

$$A_1 = -15, \quad A_2 = 6, \quad A_3 = -1$$


$$\therefore \underline{v_2(t) = -15e^{-2t} + 6e^{-4t} - e^{-6t} + 10 \text{ V}}$$

Ex. 9.11-1

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0 \quad L = 0.1, C = 0.1$$

$$\text{so have } s^2 + \frac{10}{R}s + 100 = 0$$

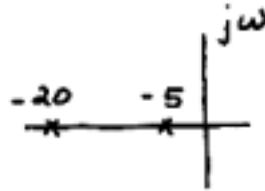a) $R = 0.4\Omega \Rightarrow s^2 + 25s + 100 = 0$
 $s = -5, -20$



b) $R = 1\Omega \Rightarrow s^2 + 10s + 100 = 0$
 $s = -5 \pm j5\sqrt{3}$

