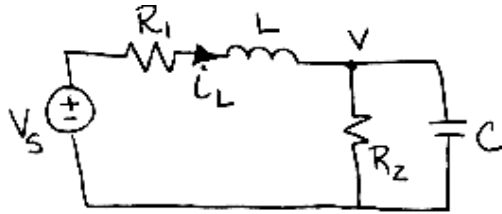


## Problems

### Section 9-3: Differential Equations for Circuits with Two Energy Storage Elements

#### P9.3-1



$$\text{KCL: } i_L = \frac{v}{R_2} + C \frac{dv}{dt}$$

$$\text{KVL: } V_s = R_1 i_L + L \frac{di_L}{dt} + v$$

$$v_s = R_1 \left[ \frac{v}{R_2} + C \frac{dv}{dt} \right] + \frac{L}{R_2} \frac{dv}{dt} + LC \frac{d^2v}{dt^2} + v$$


$$v_s = \left[ \frac{R_1}{R_2} + 1 \right] v + \left[ R_1 C + \frac{L}{R_2} \right] \frac{dv}{dt} + [LC] \frac{d^2v}{dt^2}$$

$$R_1 = 2\Omega, R_2 = 100\Omega, L = 1\text{mH}, C = 10\mu\text{F}$$

$$v_s = 1.02v + 0.00003 \frac{dv}{dt} + 1 \times 10^{-8} \frac{d^2v}{dt^2}$$

$$1 \times 10^8 v_s = 1.02 \times 10^8 v + 3000 \frac{dv}{dt} + \frac{d^2v}{dt^2}$$

#### P9.3-2

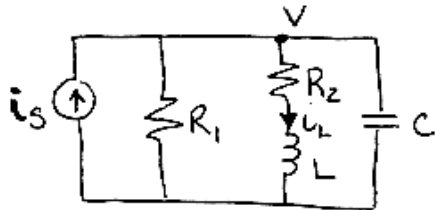

$$\text{KCL: } i_s = \frac{v}{R_1} + i_L + C s v$$

$$\text{KVL: } v = R_2 i_L + L s i_L$$

Solving Cramer's rule for  $i_L$ :

$$i_L = \frac{i_s}{\frac{R_2}{R_1} + \frac{Ls}{R_1} + R_2 Cs + LCs^2 + 1}$$

$$\left[ 1 + \frac{R_2}{R_1} \right] i_L + \left[ \frac{L}{R_1} + R_2 C \right] s i_L + [LC] s^2 i_L = i_s$$


$$R_1 = 100\Omega, R_2 = 10\Omega, L = 1\text{mH}, C = 10\mu\text{F}$$

$$1.1 i_L + 0.00011 s i_L + 1 \times 10^{-8} s^2 i_L = i_s$$

$$1.1 \times 10^8 i_L + 11000 s i_L + s^2 i_L = 1 \times 10^8 i_s$$

**P9.3-3**

$t > 0$

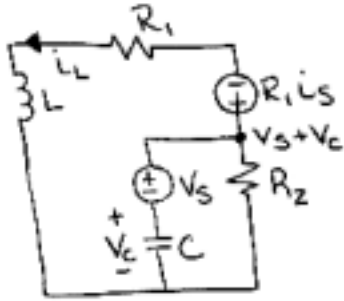

$$\text{KCL: } i_L + C \frac{dv_c}{dt} + \frac{v_s + v_c}{R_2} = 0$$

$$\text{KVL: } R_1 i_s + R_1 i_L + L \frac{di_L}{dt} - v_c - v_s = 0$$

Solving for  $i_L$ :

$$\frac{d^2 i_L}{dt^2} + \left[ \frac{R_1}{L} + \frac{1}{R_2 C} \right] \frac{di_L}{dt} + \left[ \frac{R_1}{L R_2 C} + \frac{1}{L C} \right] i_L = \frac{-R_1}{L C R_2} i_s - \frac{R_1}{L} \frac{di_s}{dt} + \frac{1}{L} \frac{dv_s}{dt}$$


**Section 9-4: Solution of the Second Order Differential Equation - The Natural Response**

**P9.4-1** From Problem P 9.3-2 the characteristic equation is

$$1.1 \times 10^8 + 11000s + s^2 = 0 \Rightarrow$$

$$s_1, s_2 = \frac{-11000 \pm \sqrt{(11000)^2 - 4(1.1 \times 10^8)}}{2} = \underline{\underline{-5500 \pm j8930}}$$

**P9.4-2**

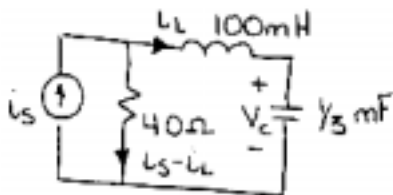

$$\text{KVL: } 40(i_s - i_L) = 100m \frac{di_L}{dt} + v_c$$

where  $m = 10^{-3}$


$$i_L = i_c = \frac{1}{3} m \frac{dv_c}{dt}$$

$$i_L = \frac{40}{3} m \frac{di_s}{dt} - \frac{40}{3} m \frac{di_L}{dt} - \frac{100}{3} m^2 \frac{d^2 i_L}{dt^2}$$

$$\frac{d^2 i_L}{dt^2} + 400 \frac{di_L}{dt} + 30000 i_L = 400 \frac{di_s}{dt}$$

$$s^2 + 400s + 30000 = 0 \Rightarrow (s+100)(s+300) = 0 \Rightarrow \underline{\underline{s_1 = -100, s_2 = -300}}$$

**P9.4-3**

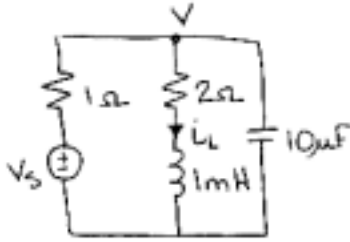

$$\text{KCL: } \frac{v-v_s}{1} + i_L + 10\mu \frac{dv}{dt} = 0 \quad \text{where } \mu = 10^{-6}$$

KVL:

$$v = 2i_L + 1m \frac{di_L}{dt} \quad \text{where } m = 10^{-3}$$

$$0 = 2i_L + 1m \frac{di_L}{dt} - v_s + i_L + 10\mu \cdot 2 \frac{di_L}{dt} + 10\mu \cdot 1m \frac{d^2i_L}{dt^2}$$

$$v_s = 3i_L + 0.00102 \frac{di_L}{dt} + 1 \times 10^{-8} \frac{d^2i_L}{dt^2}$$

$$\frac{d^2i_L}{dt^2} + 102000 \frac{di_L}{dt} + 3 \times 10^{-8} i_L = 1 \times 10^8 v_s$$

$$\underline{s^2 + 102000s + 3 \times 10^{-8} = 0, \quad \therefore s_1 = 3031, s_2 = -98969}$$

**Section 9.5: Natural Response of the Unforced Parallel RLC Circuit**

**P9.5-1**  $v(0) = 6, \frac{dv(0)}{dt} = -3000$

Using operators, the node equation is:  $Csv + \frac{v}{R} + \frac{(v-v_s)}{sL} = 0$  or  $\left( LCs^2 + \frac{L}{R}s + 1 \right) v = v_s$

So the characteristic equation is:  $s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$

$$\Rightarrow s_{1,2} = -250 \pm \sqrt{250^2 - 40,000} = -100, -400$$

So  $v(t) = Ae^{-100t} + Be^{-400t}$

$$v(0) = 6 = A + B$$

$$\left. \begin{aligned} \frac{dv(0)}{dt} = -3000 &= -100A - 400B \\ A &= -2 \\ B &= 8 \end{aligned} \right\}$$

$$\therefore \underline{v(t) = -2e^{-100t} + 8e^{-400t}} \quad t > 0$$

**P9.5-2**

$$v(0) = 2, i(0) = 0$$

Characteristic equation  $s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0 \Rightarrow s^2 + 4s + 3 = 0 \Rightarrow s = -1, -3$

$$v(t) = Ae^{-t} + Be^{-3t}$$


Use eq. 9.5-12  $\Rightarrow s_1A + s_2B = -\frac{v(0)}{RC} - \frac{i(0)}{C}$

$$-1A - 3B = -\frac{2}{\frac{1}{4}} - 0 = -8 \quad (1)$$

$$\text{also have } v(0) = 2 = A + B \quad (2)$$

From (1) & (2) get  $A = -1, B = 3$
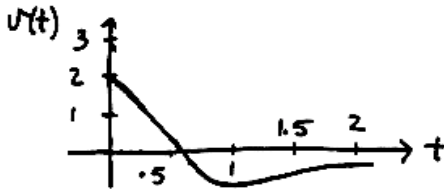
$$\therefore \underline{v(t) = -1e^{-t} + 3e^{-3t} \text{ V}}$$



**P9.5-3**

$$\text{KVL : } i_1 + 5 \frac{di_1}{dt} - 3 \frac{di_2}{dt} = 0 \quad (1)$$

$$\text{KVL : } -3 \frac{di_1}{dt} + 3 \frac{di_2}{dt} + 2i_2 = 0 \quad (2)$$

in operator form

$$\left. \begin{aligned} (1+5s)i_1 + (-3s)i_2 &= 0 \\ (-3s)i_1 + (3s+2)i_2 &= 0 \end{aligned} \right\} \text{ thus } \Delta = (1+5s)(3s+2) - 9s^2 = 6s^2 + 13s + 2 = 0 \Rightarrow s = -\frac{1}{6}, -2$$

$$\text{Thus } i_1(t) = Ae^{-t/6} + Be^{-2t}$$

$$i_2(t) = Ce^{-t/6} + De^{-2t}$$

$$\text{Now } i_1(0) = 11 = A+B; i_2(0) = 11 = C+D$$

from (1) & (2) get


$$\frac{di_1(0)}{dt} = -\frac{33}{2} = -\frac{A}{6} - 2B; \quad \frac{di_2(0)}{dt} = -\frac{143}{6} = -\frac{C}{6} - 20$$

which yields  $A = 3, B = 8, C = -1, D = 12$

$$\underline{i_1(t) = 3e^{-t/6} + 8e^{-2t} \text{ A} \quad \& \quad \underline{i_2(t) = -e^{-t/6} + 12e^{-2t} \text{ A}}$$

**Section 9.6: Natural Response of the Critically Damped Unforced Parallel RLC Circuit**

**P9.6-1**

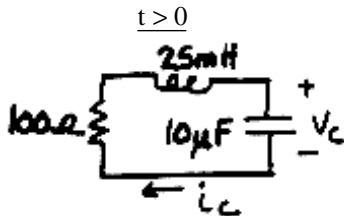


$$\text{KVL a: } 100i_c + .025 \frac{di_c}{dt} + v_c = 0, \quad i_c = 10^{-5} \frac{dv_c}{dt}$$

$$\therefore \frac{d^2 v_c}{dt^2} + 4000 \frac{dv_c}{dt} + 4 \times 10^6 v_c = 0$$

$$s^2 + 4000s + 4 \times 10^6 = 0 \Rightarrow s = -2000, -2000 \quad \therefore v_c(t) = A_1 e^{-2000t} + A_2 t e^{-2000t}$$

$t = 0^-$  (Steady-State)

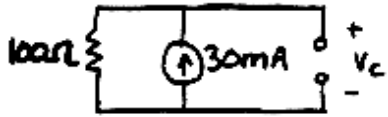

$$i_L = i_c(0^-) = 0 = i_c(0^+) \Rightarrow \frac{dv_c(0^+)}{dt} = 0$$


$$v_c(0^-) = 3 \text{ V} = v_c(0^+)$$

$$\text{so } v_c(0^+) = 3 = A_1$$

$$\frac{dv_c(0^+)}{dt} = 0 = -2000A_1 + A_2 \Rightarrow A_2 = 6000$$

$$\therefore \underline{v_c(t) = (3 + 6000t)e^{-2000t} \text{ V}}$$

**P9.6-2**

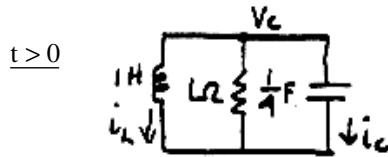


$$\text{KCL at } v_c: \int_{-\infty}^t v_c dt + v_c + \frac{1}{4} \frac{dv_c}{dt} = 0$$

$$\Rightarrow \frac{d}{dt} \frac{d^2 v_c}{dt^2} + 4 \frac{dv_c}{dt} + 4v_c = 0$$

$$s^2 + 4s + 4 = 0, s = -2, -2 \quad \therefore v_c(t) = A_1 e^{-2t} + A_2 t e^{-2t}$$

$t = 0^-$  (Steady-State)

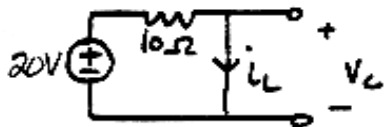

$$v_c(0^-) = 0 = v_c(0^+) \quad \& \quad i_L(0^-) = \frac{20 \text{ V}}{10 \Omega} = 2 \text{ A} = i_L(0^+)$$

$$\text{Since } v_c(0^+) = 0 \text{ then } i_c(0^+) = -i_L(0^+) = -2 \text{ A}$$

$$\therefore \frac{dv_c(0^+)}{dt} = \frac{i_c(0^+)}{1/4} = -8 \text{ V/S}$$

$$\text{So } v_c(0^+) = 0 = A_1$$


$$\frac{dv_c(0^+)}{dt} = -8 = A_2$$

$$\therefore \underline{v_c(t) = -8te^{-2t} \text{ V}}$$

**P9.6-3**

Assume steady-state at  $t = 0^-$   $\therefore v_c(0^-) = 10^4 \text{ V}$  &  $i_L(0^-) = 0$

$t > 0$

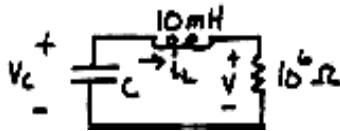

$$\text{KVL a: } -v_c + 0.01 \frac{di_L}{dt} + 10^6 i_L = 0 \quad (1)$$

$$\text{Also: } i_L = -C \frac{dv_c}{dt} = -C \left[ .01 \frac{d^2 i_L}{dt^2} + 10^6 \frac{di_L}{dt} \right] \quad (2)$$

$$\therefore .01C \frac{d^2 i_L}{dt^2} + 10^6 C \frac{di_L}{dt} + i_L = 0$$

$$\text{Characteristic eq. } \Rightarrow .01C s^2 + 10^6 s + 1 = 0 \Rightarrow s = \frac{-10^6 C \pm \sqrt{(10^6 C)^2 - 4(.01C)}}{2(.01C)}$$

for critically damped:  $10^{12} C^2 - .04C = 0$

$$\Rightarrow C = 0.04 \text{ pF} \therefore s = -5 \times 10^7, -5 \times 10^7$$

$$\text{So } i_L(t) = A_1 e^{-5 \times 10^7 t} + A_2 t e^{-5 \times 10^7 t}$$

$$\text{Now from (1)} \Rightarrow \frac{di_L}{dt}(0^+) = 100 \left[ v_c(0^+) - 10^6 i_L(0^+) \right] = 10^6 \text{ A/s}$$

$$\text{So } i_L(0) = 0 = A_1 \text{ and } \frac{di_L(0)}{dt} = 10^6 = A_2 \therefore i_L(t) = 10^6 t e^{-5 \times 10^7 t} \text{ A}$$

$$\text{Now } \underline{v(t) = 10^6 i_L(t) = 10^{12} t e^{-5 \times 10^7 t} \text{ V}}$$

**P9.6-4**

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0 \quad \text{with } \frac{1}{RC} = 500 \text{ \& } \frac{1}{LC} = 62.5 \times 10^3 \text{ yields } s = -250, -250$$

$$v(t) = A e^{-250t} + B t e^{-250t}$$

$$v(0) = 6 = A$$

$$\frac{dv(0)}{dt} = -3000 = -250A + B \Rightarrow B = -1500$$

$$\therefore \underline{v(t) = 6e^{-250t} - 1500te^{-250t}}$$

**P9.6-5**

$$\text{KVL: } \frac{di}{dt} + Ri + 2 + 4 \int_0^t i dt = 6 \quad (1)$$

taking the derivative wrt t:  $\frac{d^2i}{dt^2} + R \frac{di}{dt} + 4i = 0$

Char. eq.:  $s^2 + Rs + 4 = 0$


Let  $R=4$  for critical damping  $\Rightarrow (s+2)^2 = 0$

So  $i(t) = Ate^{-2t} + Be^{-2t}$

$i(0) = 0 \Rightarrow B = 0$

from (1)  $\frac{di(0)}{dt} = 4 - R(i(0)) = 4 - R(0) = 4 = A$


$\therefore i(t) = 4te^{-2t} \text{ A}$

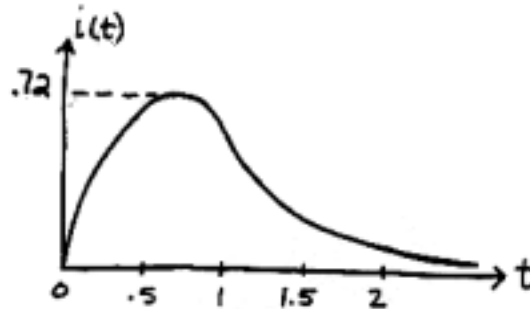

**Section 9-7: Natural Response of an Underdamped Unforced Parallel RLC Circuit**

**P9.7-1**

$t > 0$

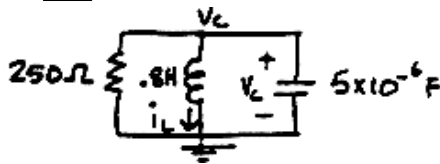

KCL at  $v_c$ :  $\frac{v_c}{250} + i_L + 5 \times 10^{-6} \frac{dv_c}{dt} = 0 \quad (1)$

also:  $v_c = .8 \frac{di_L}{dt} \quad (2)$

Solving for  $i_L$  in (1) & plugging into (2)

$$\frac{d^2v_c}{dt^2} + 800 \frac{dv_c}{dt} + 2.5 \times 10^5 v_c = 0 \Rightarrow s^2 + 800s + 250,000 = 0, s = -400 \pm j 300$$

$$\therefore v_c(t) = e^{-400t} [A_1 \cos 300t + A_2 \sin 300t]$$

$t = 0^-$  (Steady - State)

$$i_L(0^-) = \frac{-6V}{500\Omega} = -\frac{6}{500} \text{ A} = i_L(0^+)$$


$$v_c(0^-) = 250\left(-\frac{6}{500}\right) + 6 = 3V = v_c(0^+)$$

Now from (1):  $\frac{dv_c(0^+)}{dt} = -2 \times 10^5 i_L(0^+) - 800v_c(0^+) = 0$

So  $v_c(0^+) = 3 = A_1$


$$\frac{dv_c(0^+)}{dt} = 0 = -400A_1 + 300A_2 \Rightarrow A_2 = 4$$
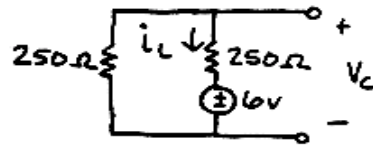
$$\therefore v_c(t) = e^{-400t} [3 \cos 300t + 4 \sin 300t] \text{ V}$$



P9.7-2


$t = 0^-$

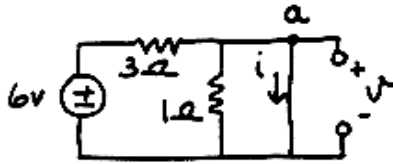

$$i(0) = 2A$$

$$v(0) = 0$$

$t = 0^+$

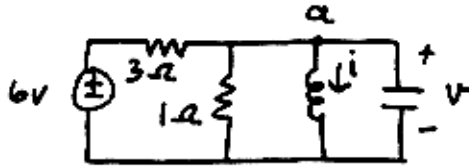

KCL at node a:

$$\frac{v}{1} + C \frac{dv}{dt} + \frac{1}{L} \int_0^t v dt + i(0) = 0 \quad (1)$$

in operator form have  $v + Csv + \frac{1}{Ls}v + i(0) = 0$  or  $\left(s^2 + \frac{1}{C}s + \frac{1}{LC}\right)v = 0$

with  $s^2 + 4s + 8 = 0 \Rightarrow s = -2 \pm j2$

$$v(t) = e^{-2t} [B_1 \cos 2t + B_2 \sin 2t]$$


$$v(0) = 0 = B_1$$

From (1),  $\frac{dv(0)}{dt} = \frac{1}{C} [-i(0) - v(0)] = -4[2] = -8 = 2B_2$  or  $B_2 = -4$

So  $v(t) = -4e^{-2t} \sin 2tV$

P9.7-3

$t > 0$

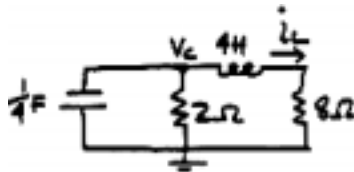


KCL at  $v_c$ :  $\frac{1}{4} \frac{dv_c}{dt} + \frac{v_c}{2} + i_L = 0 \quad (1)$

KVL:  $v_c = \frac{4di_L}{dt} + 8i_L \quad (2)$

(2) into (1) yields  $\frac{d^2i_L}{dt^2} + 4 \frac{di_L}{dt} + 5i_L = 0 \Rightarrow s^2 + 4s + 5 = 0 \Rightarrow s = -2 \pm j$

$$\therefore i_L(t) = e^{-2t} [A_1 \cos t + A_2 \sin t]$$

$t = 0^-$  (Steady-State)

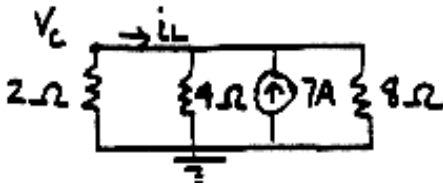

$$\frac{v_c(0^-)}{2} = 7 \left( \frac{4 \parallel 8}{4 \parallel 8 + 2} \right)$$

$$\Rightarrow v_c(0^-) = 8V = v_c(0^+)$$

$$i_L(0^-) = \frac{-8V}{\Omega} = -4A = i_L(0^+)$$

$$\therefore \text{from (2)} \frac{di_L(0^+)}{dt} = \frac{v_c(0^+)}{4} - 2i_L(0^+) = \frac{8V}{4} - 2(-4) = 10 \frac{A}{s}$$

$$\text{So } i_L(0^+) = -4 = A_1$$

$$\frac{di_L(0^+)}{dt} = 10 = -2A_1 + A_2 \Rightarrow A_2 = 2$$

$$\therefore i_L(t) = e^{-2t} [-4 \cos t + 2 \sin t] A$$



**P9.7-4** Have underdamped response

$$\begin{aligned} \therefore v(t) &= e^{-\alpha t} [k_1 \cos \omega t + k_2 \sin \omega t] + k_3 \\ v(\infty) &= 0 \Rightarrow k_3 = 0, \quad v(0) = 0 \Rightarrow k_1 = 0 \\ \therefore v(t) &= k_2 e^{-\alpha t} \sin \omega t \end{aligned}$$

from Fig. P 9.7-6

$$t \approx 5\text{ms} \leftrightarrow v \approx 260\text{mV (max)}$$

$$t \approx 7.5\text{ms} \leftrightarrow v \approx -200\text{ mV (min)}$$

$$\therefore \text{distance between adjacent maxima is } \approx 2(7.5\text{ms}) = T \Rightarrow \omega = \frac{2\pi}{T} = 1257 \text{ rad/s}$$

$$\text{So } .26 = k_2 e^{-\alpha (.005)} \sin 1257 (.005) \quad (1)$$

$$-.2 = k_2 e^{-\alpha (.0075)} \sin 1257 (.0075) \quad (2)$$


dividing (1) by (2)

$$-1.3 = e^{\alpha (.0025)} \frac{\sin (6.29 \text{ rad})}{\sin (9.43 \text{ rad})} \Rightarrow e^{.0025 \alpha} = 1.95 \Rightarrow \alpha = 267$$

From (1) get  $k_2 = 544$

$$\therefore \underline{v(t) = 544 e^{-267t} \sin 1257t} \quad (\text{approx. answer})$$

**P9.7-7**

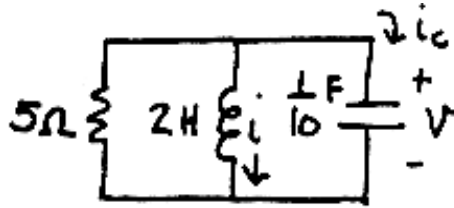

$$v(0) = 2\text{V}$$

$$i(0) = \frac{1}{10}\text{A}$$

$$\text{Char. eq.} \Rightarrow s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0 \text{ or } s^2 + 2s + 5 = 0 \text{ thus roots are } s = -1 \pm j2$$


$$\text{So have } v(t) = e^{-t} [B_1 \cos 2t + B_2 \sin 2t]$$

$$\text{now } v(0^+) = 2 = B_1$$

$$\text{Need } \frac{dv(0^+)}{dt} = \frac{1}{C} i_c(0^+) \quad \text{KCL yields } i_c(0^+) = -\frac{v(0^+)}{5} - i(0^+) = -\frac{1}{2} \frac{\text{V}}{\text{s}}$$


$$\text{So } \frac{dv(0^+)}{dt} = 10 \left( -\frac{1}{2} \right) = -B_1 + 2B_2 \Rightarrow \underline{B_2 = -\frac{3}{2}}$$

$$\text{Finally, have } \underline{v(t) = 2e^{-t} \cos 2t - \frac{3}{2} e^{-t} \sin 2t \text{ V} \quad t > 0}$$

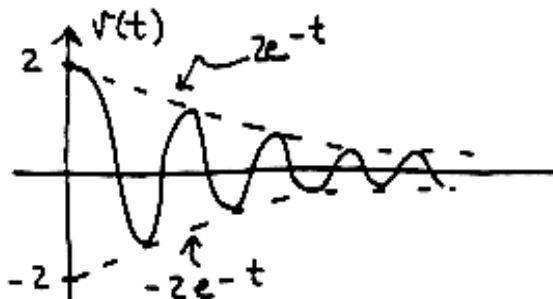

**Section 9-8:**

P9.8-1

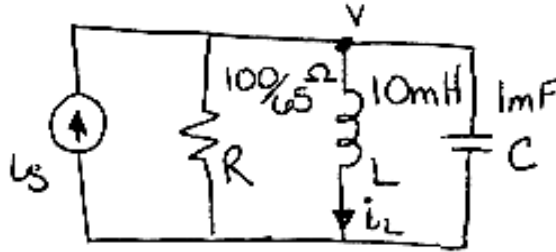

$$\text{KCL: } i_s = \frac{v}{R} + i_L + C \frac{dv}{dt}$$

$$\text{KVL: } v = L \frac{di_L}{dt}$$

$$i_s = \frac{L}{R} \frac{di_L}{dt} + i_L + LC \frac{d^2 i_L}{dt^2}$$

(a)  $i_s = 1 u(t) \therefore$  assume  $i_f = A$

$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{1}{LC} i_L = i_s$$

$$0 + 0 + A \frac{1}{(.01)(1 \times 10^{-3})} = 1$$

$$A = \underline{1 \times 10^{-5} = i_f}$$

(b)  $i_s = .5t u(t) \therefore$  assume  $i_f = At + B$

$$0 + A \frac{65}{(100)(.001)} + (At + B) \frac{1}{(.01)(.001)} = .5t$$

$$650A + 100000B = 0$$

$$100000At = .5t$$

$$A = 5 \times 10^{-6}$$

$$B = 3.25 \times 10^{-8}$$

$$\underline{i_f = 5 \times 10^{-6} t - 3.25 \times 10^{-8} \text{ A}}$$

(c)  $i_s = 2e^{-250t} \therefore$  assume  $i_f = Ae^{-250t}$

This does not work  $\therefore i_f = Bte^{-250t}$


$$\frac{Be^{-250t}}{RC} + \frac{-250Bte^{-250t}}{RC} + \frac{Bte^{-250t}}{LC} = 2e^{-250t}$$

$$150B = 2$$

$$B = .0133$$

$$\underline{i_f = .0133 te^{-250t} \text{ A}}$$

P9.8-2

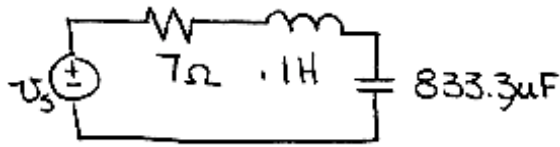


$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = v_s$$

- (a)  $v_s = 2 \therefore$  assume  $v_f = A$   
 $0 + 0 + 12000A = 2$   
 $A = \frac{1}{6000} = v_f$
- (b)  $v_s = .2t \therefore$  assume  $v_f = At + B$   
 $70A + 12000At + 12000B = .2t$   
 $70A + 12000B = 0$   
 $12000At = .2t$   
 $A = \frac{1}{60000}, B = \frac{70A}{12000}, B = 350$   
 $\therefore v_f = \frac{t}{60000} + 350 \text{ V}$
- (c)  $v_s = e^{-30t} \therefore$  assume  $Ae^{-30t}$   
 $900A - 2100Ae^{-30t} + 12000Ae^{-30t} = e^{-30t}$   
 $10800Ae^{-30t} = e^{-30t}$   
 $A = \frac{1}{10800}$   
 $v_f = \frac{e^{-30t}}{10800} \text{ V}$

**Section 9-9: Complete Response of an RLC Circuit**

P9.9-1

$t > 0$

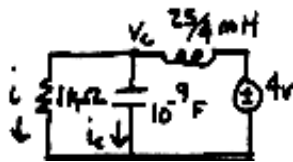

KCL at  $v_c$  :  $\frac{v_c}{1000} + 10^{-9} \frac{dv_c}{dt} + \frac{1}{25/4 \times 10^{-3}} \int_{-\infty}^t (v_c - 4) dt = 0$

$$\frac{d}{dt} 10^{-3} \frac{dv_c}{dt} + 10^{-9} \frac{d^2v_c}{dt^2} + 160(v_c - 4) = 0$$


$$\Rightarrow \frac{d^2v_c}{dt^2} + 10^6 \frac{dv_c}{dt} + 1.6 \times 10^{11} v_c = 6.4 \times 10^{11}$$

$$\therefore s^2 + 10^6 s + 1.6 \times 10^{11} = 0 \Rightarrow s = -2 \times 10^5, -8 \times 10^5 \Rightarrow v_{cn}(t) = A_1 e^{-2 \times 10^5 t} + A_2 e^{-8 \times 10^5 t}$$

Try  $v_{cf} = B$  & plug into D.E.  $\Rightarrow B = 4$

$$\therefore v_c(t) = A_1 e^{-2 \times 10^5 t} + A_2 e^{-8 \times 10^5 t} + 4$$

$t = 0^-$  (steady - state)

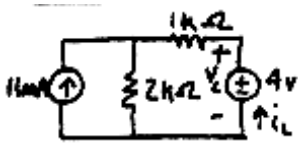

$$v_c(0^-) = 4V = v_c(0^+) \text{ \& from KVL: } -4 + i_L + 2(1 + i_L) = 0$$

$$\Rightarrow i_L(0^-) = i_L(0^+) = -6 \text{ mA}$$


$t = 0^+$

$$i_c(0^+) = i_L(0^+) - \frac{v_c(0^+)}{1} = -6 - 4 = -10 \text{ mA} \quad \therefore \frac{dv_c(0^+)}{dt} = -\frac{.01}{10^{-9}} = -10^7 \text{ V/s}$$

$$\left. \begin{aligned} \text{So } v_c(0) = 4 = A_1 + A_2 + 4 &\Rightarrow A_1 + A_2 = 0 \\ \frac{dv_c(0)}{dt} = -10^7 = -2 \times 10^5 A_1 - 8 \times 10^5 A_2 &\end{aligned} \right\} \begin{aligned} A_1 &= \frac{50}{3} \\ A_2 &= -\frac{50}{3} \end{aligned}$$


$$\text{So } i(t) = \frac{v_c(t)}{1} = \underline{\underline{-\frac{50}{3} e^{-2 \times 10^5 t} + \frac{50}{3} e^{-8 \times 10^5 t} + 4 \text{ mA}}}$$

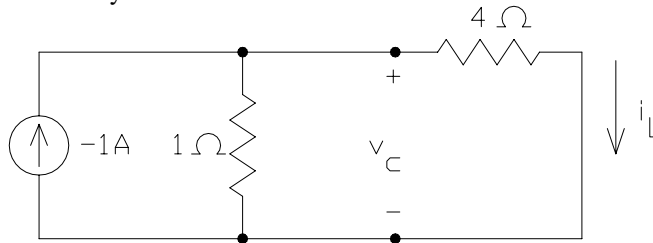**9.9-2** The circuit will be at steady state for  $t < 0$ :



so  $i_L(0^+) = i_L(0^-) = -0.2 \text{ A}$  and  $v_C(0^+) = v_C(0^-) = -0.8 \text{ V}$ .

For  $t > 0$ :

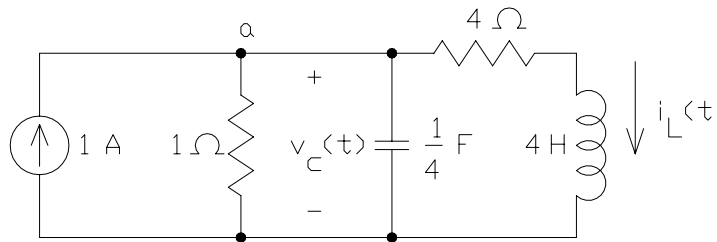

Apply KCL at node a to get:

$$1 = \frac{v_C(t)}{1} + \frac{1}{4} \frac{d}{dt} v_C(t) + i_L(t)$$

Apply KVL to the right-most mesh to get:

$$v_C(t) = 4 i_L(t) + 4 \frac{d}{dt} i_L(t)$$

Use the substitution method to get

$$1 = \left( 4 i_L(t) + 4 \frac{d}{dt} i_L(t) \right) + \frac{1}{4} \frac{d}{dt} \left( 4 i_L(t) + 4 \frac{d}{dt} i_L(t) \right) + i_L(t)$$

or

$$1 = \frac{d^2}{dt^2} i_L(t) + 5 \frac{d}{dt} i_L(t) + 5 i_L(t)$$

The forced response will be a constant,  $i_L = B$  so  $1 = \frac{d^2}{dt^2} B + 5 \frac{d}{dt} B + 5B \Rightarrow B = 0.2 \text{ A}$ .

To find the natural response, consider the characteristic equation:

$$0 = s^2 + 5s + 5 = (s + 3.62)(s + 1.38)$$

The natural response is

$$i_n = A_1 e^{-3.62t} + A_2 e^{-1.38t}$$

so

$$i_L(t) = A_1 e^{-3.62t} + A_2 e^{-1.38t} + 0.2$$

Then

$$v_C(t) = \left( 4 i_L(t) + 4 \frac{d}{dt} i_L(t) \right) = -10.48 A_1 e^{-3.62t} - 1.52 A_2 e^{-1.38t} + 0.8$$

At  $t=0+$

$$\begin{aligned} -0.2 &= i_L(0+) = A_1 + A_2 + 0.2 \\ -0.8 &= v_C(0+) = -10.48 A_1 - 1.52 A_2 + 0.8 \end{aligned}$$

so  $A_1 = 0.246$  and  $A_2 = -0.646$ . Finally

$$i_L(t) = 0.246 e^{-3.62t} - 0.646 e^{-1.38t} \text{ A}$$

### P9.9-3 $t \geq 0$

$$\text{KCL at } v_1: \frac{v_1 - 20}{1000} + \frac{1}{6} \times 10^{-6} \frac{dv_1}{dt} + \frac{v_1 - v_2}{1000} = 0$$

$$\text{yields } 2v_1 + \frac{1}{6} \times 10^{-3} \frac{dv_1}{dt} - 20 = v_2$$

$$\text{also: } \frac{v_1 - v_2}{1000} = \frac{1}{16} \times 10^{-6} \frac{dv_2}{dt}$$

$$\text{yields } v_1 - v_2 - \frac{1}{16} \times 10^{-3} \frac{dv_2}{dt} = 0$$

$$(1) \text{ into } (2) \text{ Yields: } \frac{d^2 v_1}{dt^2} + 2.8 \times 10^4 \frac{dv_1}{dt} + 9.6 \times 10^7 v_1 = 1.92 \times 10^9$$



$$\Rightarrow s^2 + 2.8 \times 10^4 s + 9.6 \times 10^7 = 0 \Rightarrow s = -4 \times 10^3, -2.4 \times 10^4$$

$$\therefore v_{1n}(t) = A_1 e^{-4 \times 10^3 t} + A_2 e^{-2.4 \times 10^4 t}$$

$$\text{Try } v_{1f} = B \text{ \& \text{ plug into D.E. } \Rightarrow B = 20}$$

$$\text{So } v_1(t) = A_1 e^{-4 \times 10^3 t} + A_2 e^{-2.4 \times 10^4 t} + 20$$

$t = 0^-$  (steady-state)

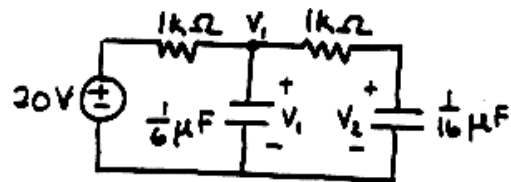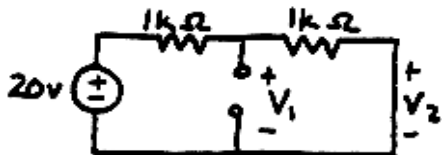

$$v_2(0^-) = 0 = v_2(0^+) \quad \& \quad v_1(0^-) = 10V = v_1(0^+)$$

$$\therefore \text{from (1)} \quad \frac{dv_1(0^+)}{dt} = -1.2 \times 10^4 v_1(0^+) + 1.2 \times 10^5$$

$$= -1.2 \times 10^4(10) + 1.2 \times 10^5 = 0$$

$$\text{So } v_1(0^+) = 10 = A_1 + A_2 + 20$$


$$\frac{dv_1(0^+)}{dt} = 0 = -4 \times 10^3 A_1 + 2.4 \times 10^4 A_2$$

$$\left. \begin{array}{l} A_1 = -12 \\ A_2 = 2 \end{array} \right\}$$

$$\therefore \underline{v_1(t) = -12e^{-4 \times 10^3 t} + 2e^{-2.4 \times 10^4 t} + 20 \text{ V}}$$

**P9.9-4**

$t > 0$

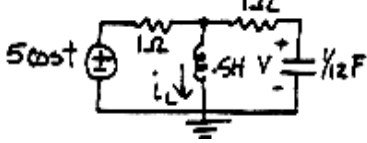

KCL at top node :  $\left( 5 \frac{di_L}{dt} - 5 \cos t \right) + i_L + \frac{1}{12} \frac{dv}{dt} = 0$  (1)

KVL at right loop :  $.5 \frac{di_L}{dt} = \frac{1}{12} \frac{dv}{dt} + v$  (2)

$$\frac{d}{dt} \text{ of (1)} \Rightarrow .5 \frac{d^2 i_L}{dt^2} + \frac{di_L}{dt} + \frac{1}{12} \frac{d^2 v}{dt^2} = -5 \sin t$$
 (3)

$$\frac{d}{dt} \text{ of (2)} \Rightarrow .5 \frac{d^2 i_L}{dt^2} = \frac{1}{12} \frac{d^2 v}{dt^2} + \frac{dv}{dt}$$
 (4)

Solving for  $\frac{d^2 i_L}{dt^2}$  in (4) and  $\frac{di_L}{dt}$  in (2) & plugging into (3)


$$\frac{d^2 v}{dt^2} + 7 \frac{dv}{dt} + 12v = -30 \sin t \quad \Rightarrow \quad s^2 + 7s + 12 = 0 \Rightarrow s = -3, -4$$

$$\text{so } v(t) = A_1 e^{-3t} + A_2 e^{-4t} + v_f$$

Try  $v_f = B_1 \cos t + B_2 \sin t$  & plug into D.E., equating like terms

yields  $B_1 = 21/17, B_2 = -33/17$

$t = 0^+$

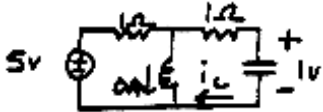

$$i_c(0^+) = \frac{5V - 1V}{1\Omega + 1\Omega} = 2A \quad \therefore \quad \frac{dv(0^+)}{dt} = \frac{2}{1/12} = 24 \text{ V/s}$$


$$\text{So } v(0^+) = 1 = A_1 + A_2 + 21/17$$

$$\frac{dv(0^+)}{dt} = 24 = -3A_1 - 4A_2 - 33/17$$

$$\left. \begin{array}{l} A_1 = 25 \\ A_2 = -429/17 \end{array} \right\}$$

$$\therefore \underline{v(t) = 25e^{-3t} - \frac{1}{17}(429e^{-4t} - 21 \cos t + 33 \sin t) \text{ V}}$$

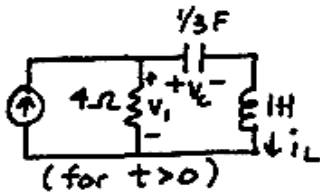**P9.9-5** Use superposition – first consider  $2u(t)$  source



$$\text{KVL at right mesh : } v_c + s i_L + 4(i_L - 2) = 0 \quad (1)$$

$$\text{also : } i_L = (1/3) s v_c \Rightarrow v_c = (3/s) i_L \quad (2)$$

Plugging (2) into (1) yields  $(s^2 + 4s + 3) i_L = 0$ , roots :  $s = -1, -3$

$$\text{So } i_L(t) = A_1 e^{-t} + A_2 e^{-3t}$$

$$\underline{t = 0^-} \Rightarrow \text{circuit is dead} \quad \therefore v_c(0) = i_L(0) = 0$$

$$\text{Now from (1) } \frac{di_L(0^+)}{dt} = 8 - 4i_L(0^+) - v_c(0^+) = 8 \text{ A/s}$$

$$\left. \begin{aligned} \text{So } i_L(0) = 0 &= A_1 + A_2 \\ \frac{di_L(0)}{dt} = 8 &= -A_1 - 3A_2 \end{aligned} \right\} A_1 = 4, A_2 = -4$$

$$\therefore i_L(t) = 4e^{-t} - 4e^{-3t}$$

$$\therefore v_1(t) = 8 - 4i_L(t) = 8 - 16e^{-t} + 16e^{-3t} \text{ V}$$

Now for  $2u(t-2)$  source, just take above expression and replace  $t \rightarrow t-2$  and flip signs

$$\therefore v_2(t) = -8 + 16e^{-(t-2)} - 16e^{-3(t-2)} \text{ V}$$

$$\therefore v(t) = v_1(t) + v_2(t)$$

$$\underline{v(t) = [8 - 16e^{-t} + 16e^{-3t}]u(t) + [-8 + 16e^{-(t-2)} - 16e^{-3(t-2)}]u(t-2) \text{ V}}$$

**P9.9-6**  $t > 0$

$$\text{KVL: } -10 \cos t + 4 \frac{di_L}{dt} + v_c + 4i_L = 0 \quad (1)$$

$$\text{KCL at P : } i_L = (1/8) \frac{dv_c}{dt} + v_c / 2 \quad (2)$$

$$(2) \text{ into (1) yields } \frac{d^2 v_c}{dt^2} + 5 \frac{dv_c}{dt} + 6v_c = 20 \cos t$$

$$\Rightarrow s^2 + 5s + 6 = 0, s = -2, -3 \text{ so } v_{c_n}(t) = A_1 e^{-2t} + A_2 e^{-3t}$$

Try  $v_{cf}(t) = B_1 \cos t + B_2 \sin t$  & plug into D.E.  $\Rightarrow B_1 = B_2 = 2$

$$\therefore v_c(t) = A_1 e^{-2t} + A_2 e^{-3t} + 2 \cos t + \sin t$$


$\underline{t = 0^-}$  (steady-state)

$$v_c(0^-) = v_c(0^+) = 5\text{V} \text{ \& } i_L(0^-) = \frac{-5\text{V}}{4\Omega} = \frac{-5}{4} = i_L(0^+)$$

$$\text{Now from (2) } \frac{dv_c(0^+)}{dt} = 8i_L(0^+) - 4v_c(0^+) = -30 \frac{\text{V}}{\text{s}}$$

$$\left. \begin{aligned} \text{So } v_c(0^+) = 5 &= A_1 + A_2 + 2 \Rightarrow A_1 + A_2 = 3 \\ \frac{dv_c(0^+)}{dt} = -30 &= -2A_1 - 3A_2 + 2 \Rightarrow 2A_1 + 3A_2 = 32 \end{aligned} \right\} \begin{aligned} A_1 &= -23 \\ A_2 &= 26 \end{aligned}$$
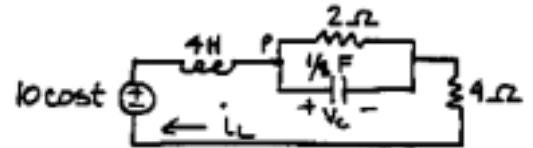
$$\therefore \underline{v_c(t) = -23e^{-2t} + 26e^{-3t} + 2 \cos t + \sin t \text{ V}}$$



**P9.9-7**


$t = 0^-$  (steady-state)



$$v_c(0) = 0$$

$$i_L(0) = 0$$

$t = 0^+$

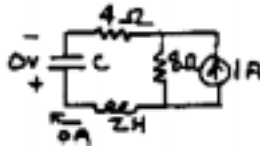

Since  $i_c(0^+) = 0 \Rightarrow \frac{dv_c(0^+)}{dt} = 0$

also at  $t = \infty \Rightarrow$  steady-state  $\therefore v_c(\infty) = -8\Omega (1 \text{ A}) = -8 \text{ V}$

(a)  $C = 1/18\text{F}$  series RLC  $\Rightarrow s = -R/2L \pm \sqrt{(R/2L)^2 - 1/LC} = -3, -3$

$$\therefore v_c(t) = A_1 e^{-3t} + A_2 t e^{-3t} + v_c(\infty) = A_1 e^{-3t} + A_2 t e^{-3t} - 8$$

Now  $v_c(0) = 0 = A_1 - 8 \Rightarrow A_1 = 8$  &  $\frac{dv_c(0)}{dt} = 0 = -3A_1 + A_2 \Rightarrow A_2 = 24$

So  $v_c(t) = 8e^{-3t} + 24te^{-3t} - 8 \text{ V}$

(b)  $C = 1/10\text{F} \Rightarrow s = -12/4 \pm \sqrt{9 - 10/2} = -5, -1 \therefore v_c(t) = A_1 e^{-t} + A_2 e^{-5t} - 8$

$$\text{Now } \left. \begin{aligned} v_c(0) = 0 = A_1 + A_2 - 8 \\ \frac{dv_c(0)}{dt} = 0 = -A_1 - 5A_2 \end{aligned} \right\} \begin{aligned} A_1 = 10 \text{ \& } A_2 = -2 \end{aligned}$$


$\therefore v_c(t) = 10e^{-t} - 2e^{-5t} - 8 \text{ V}$

(c)  $C = 1/20\text{F} \Rightarrow s = -3 \pm \sqrt{9 - 20/2} = -3 \pm j \therefore v_c(t) = e^{-3t} [A_1 \cos t + A_2 \sin t] - 8$

Now  $v_c(0) = 0 = A_1 - 8$  &  $\frac{dv_c(0)}{dt} = 0 = -3A_1 + A_2 \Rightarrow A_2 = 24$

$\therefore v_c(t) = e^{-3t} [8 \cos t + 24 \sin t] - 8 \text{ V}$

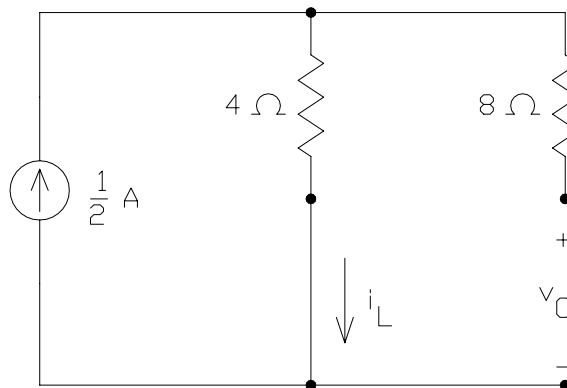
**9.9-8** The circuit will be at steady state for  $t < 0$ :



so  $i_L(0^+) = i_L(0^-) = 0.5 \text{ A}$  and  $v_c(0^+) = v_c(0^-) = 2 \text{ V}$ .



For  $t > 0$ :

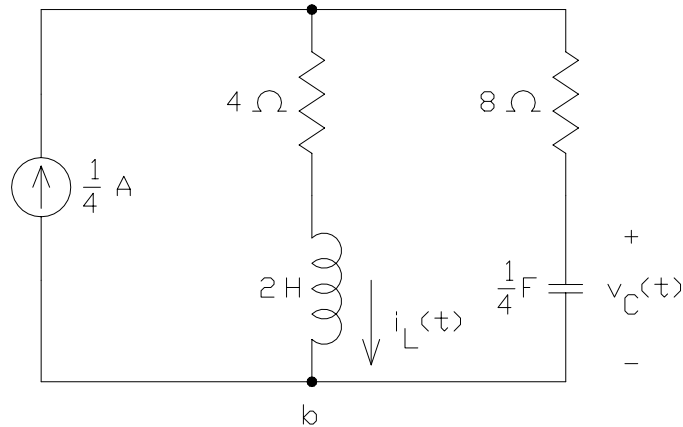

Apply KCL at node b to get: 
$$\frac{1}{4} = i_L(t) + \frac{1}{4} \frac{d}{dt} v_C(t) \Rightarrow i_L(t) = \frac{1}{4} - \frac{1}{4} \frac{d}{dt} v_C(t)$$

Apply KVL to the right-most mesh to get: 
$$4 i_L(t) + 2 \frac{d}{dt} i_L(t) = 8 \left( \frac{1}{4} \frac{d}{dt} v_C(t) \right) + v_C(t)$$

Use the substitution method to get

$$4 \left( \frac{1}{4} - \frac{1}{4} \frac{d}{dt} v_C(t) \right) + 2 \frac{d}{dt} \left( \frac{1}{4} - \frac{1}{4} \frac{d}{dt} v_C(t) \right) = 8 \left( \frac{1}{4} \frac{d}{dt} v_C(t) \right) + v_C(t)$$

or

$$2 = \frac{d^2}{dt^2} v_C(t) + 6 \frac{d}{dt} v_C(t) + 2 v_C(t)$$

The forced response will be a constant,  $v_C = B$  so  $2 = \frac{d^2}{dt^2} B + 6 \frac{d}{dt} B + 2B \Rightarrow B = 1 \text{ V}$ .

To find the natural response, consider the characteristic equation:

$$0 = s^2 + 6s + 2 = (s + 5.65)(s + 0.35)$$

The natural response is

$$v_n = A_1 e^{-5.65t} + A_2 e^{-0.35t}$$

so

$$v_C(t) = A_1 e^{-5.65t} + A_2 e^{-0.35t} + 1$$

Then

$$i_L(t) = \frac{1}{4} + \frac{1}{4} \frac{d}{dt} v_C(t) = \frac{1}{4} + 1.41 A_1 e^{-5.65t} + 0.0875 A_2 e^{-0.35t}$$

At  $t = 0^+$

$$2 = v_C(0^+) = A_1 + A_2 + 1$$

$$\frac{1}{2} = i_L(0^+) = \frac{1}{4} + 1.41 A_1 + 0.0875 A_2$$

so  $A_1 = 0.123$  and  $A_2 = 0.877$ . Finally

$$v_C(t) = 0.123 e^{-5.65t} + 0.877 e^{-0.35t} + 1 \text{ V}$$