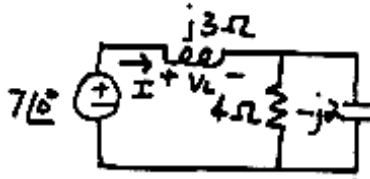


## Chapter 11: AC Steady State Power

### Exercises:

#### Ex. 11.3-1

First calculate  $i(t)$   
Phasor circuit.  $\rightarrow$



$$Z = j3 + \frac{4(-j2)}{4-j2} = 0.8 + j1.4$$

$$= 1.6 \angle 60.3^\circ \Omega$$

$$\therefore I = \frac{V}{Z} = \frac{7 \angle 0^\circ}{1.6 \angle 60.3^\circ} = 4.38 \angle -60.3^\circ \text{ A}$$

So  $i(t) = 4.38 \cos(10t - 60.3^\circ) \text{ A}$

Now  $p(t) = v(t) \cdot i(t) = (7 \cos 10t)(4.38 \cos(10t - 60.3^\circ)) = \frac{(7)(4.38)}{2} [\cos(60.3^\circ) + \cos(20t - 60.3^\circ)] = \underline{7.6 + 15.3 \cos(20t - 60.3^\circ) \text{ W}}$

Now  $V_L = I \cdot Z_L = (4.38 \angle -60.3^\circ)(j3) = 13.12 \angle 29.69^\circ \text{ V}$

$\therefore v_L(t) = 13.12 \cos(10t + 29.69^\circ) \text{ V}$

So  $P_c(t) = v_L(t) \cdot i(t) = [(13.12 \cos(10t + 29.69^\circ))(4.38 \cos(10t - 60.3^\circ))] = \frac{57.47}{2} [\cos(29.69^\circ + 60.3^\circ) + \cos(20t + 29.69^\circ - 60.3^\circ)]$

$\underline{p_c(t) = 28.7 \cos(20t - 30.6^\circ) \text{ W}}$

#### Ex. 11.3-2

a)

So  $i_R(t) = \frac{v(t)}{R} = \frac{V_m}{R} \cos(\omega t + \theta) \text{ A}$


The power into the resistor is  $P_R(t) = v(t) \cdot i(t) = V_m \cos(\omega t + \theta) \cdot \frac{V_m}{R} \cos(\omega t + \theta)$

$$= \frac{V_m^2}{R} \cos^2(\omega t + \theta) = \frac{V_m^2}{2R} + \frac{V_m^2}{2R} \cos(2\omega t + \theta)$$


(b) When the element is an inductor, the current will lag the voltage by  $90^\circ$

$Z_L = j\omega L = \omega L \angle 90^\circ$  so  $I = \frac{V}{Z} = \frac{V_m \angle \theta}{\omega L \angle 90^\circ} = \frac{V_m}{\omega L} \angle \theta - 90^\circ$

So  $P_L(t) = i(t) \cdot v(t) = \frac{V_m}{\omega L} \cos(\omega t + \theta - 90^\circ) \cdot V_m \cos(\omega t + \theta) = \frac{V_m^2}{2\omega L} \cos[2\omega t + 2\theta - 90^\circ] \text{ W}$

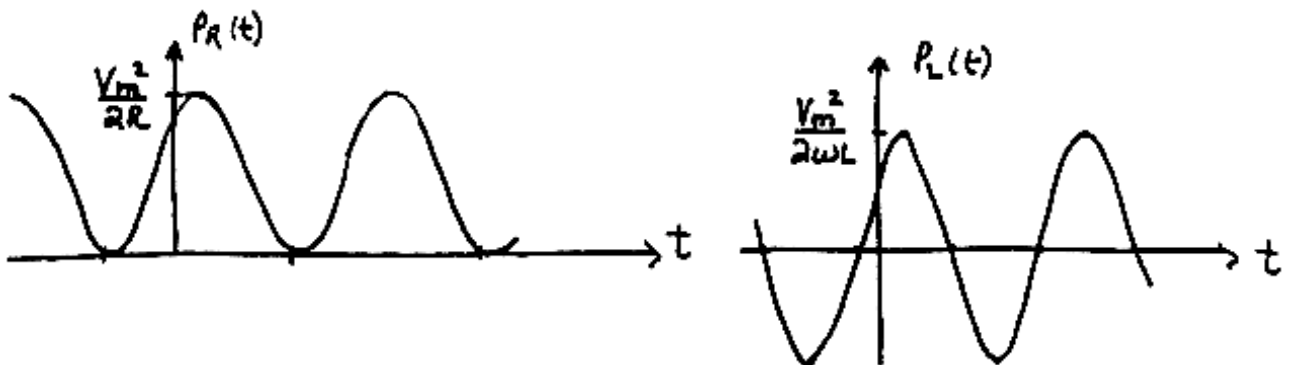

Ex. 11.3-3

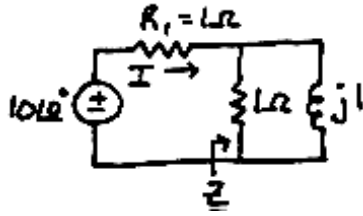


$$Z = \frac{j}{1+j} = \frac{1}{2}(1+j)$$

$$\therefore I = \frac{10\angle 0^\circ}{1 + \frac{1}{2}(1+j)} = \frac{20}{\sqrt{10}} \angle -18.4^\circ$$

(a)  $P_{\text{source}} = \frac{1}{2} |I| |V| \cos \theta = \frac{1}{2} (10) \left( \frac{20}{\sqrt{10}} \right) \cos(-18.4^\circ) = \underline{30.0 \text{ W}}$

(b)  $P_{R_1} = \frac{1}{2} I_{\text{max}}^2 R_1 = \frac{1}{2} \left( \frac{20}{\sqrt{10}} \right)^2 (1) = \underline{20 \text{ W}}$

Ex. 11.3-4

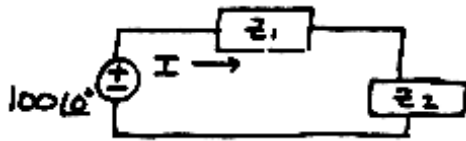

$$I = \frac{100\angle 0^\circ}{Z_1 + Z_2} = \frac{100\angle 0^\circ}{6 - j8 + 2 + j16} = \frac{100\angle 0^\circ}{8\sqrt{2} \angle 45^\circ} = 8.84 \angle -45^\circ$$

Now if  $Z_1 = R_1 + jX_1$ ,  $Z_2 = R_2 + jX_2$

then  $P_{Z_1} = P_{R_1} = \frac{1}{2} I_{\text{max}}^2 R_1 = \frac{1}{2} (8.84)^2 (6) = \underline{234 \text{ W}}$

$P_{Z_2} = P_{R_2} = \frac{1}{2} I_{\text{max}}^2 R_2 = \frac{1}{2} (8.84)^2 (2) = \underline{78.1 \text{ W}}$

Ex. 11.3-5


$0 < t < 1$   $P(t) = v(t) \cdot i(t) = 2t (2) = 4t \text{ W}$

$0 < t < 1.5$   $P(t) = (2) (2) = 4 \text{ W}$

$1.5 < t < 2$   $P(t) = (1) (2) = 2 \text{ W}$


$$P_{\text{ave}} = \frac{1}{T} \int_0^T P(t) dt = \frac{1}{2} \left[ \int_0^1 4t dt + \int_1^{1.5} 4 dt + \int_{1.5}^2 2 dt \right]$$

$$= \frac{1}{2} [2 + 2 + 1] = \underline{2.5 \text{ W}}$$

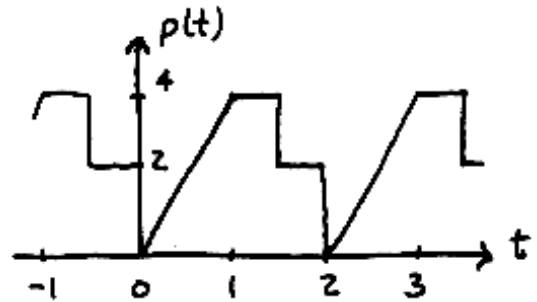

**Ex. 11.3-6**

Phasor circuit

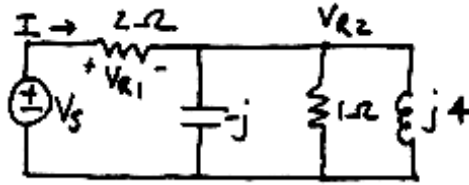

$$V_S = 5 \angle 0^\circ$$

$$Z = 2 + \left( \frac{1}{-j} + 1 + \frac{1}{j4} \right) = 2.64 - j0.48 \, \Omega$$

$$= 2.68 \angle -10.3^\circ \, \Omega$$

$$I = \frac{V}{Z} = \frac{5 \angle 0^\circ}{2.68 \angle -10.3^\circ} = 1.87 \angle 10.3^\circ \, \text{A}$$

$$\therefore P_{\text{ave source}} = \frac{V_m I_m}{2} \cos \theta = \frac{(5)(1.87)}{2} \cos(-10.3^\circ) = 4.6 \, \text{W}$$

Now  $P_R = P_{R1} = P_{R2}$  where  $P_{R1} = 1/2 I_m^2 R_1 = 1/2 (1.87)^2 (2) = 3.5 \, \text{W}$

$$P_{R2} = 1/2 V_{mR2}^2 / R \text{ where } V_{R2} = V_S - V_{R1} = 1.48 \angle -26.9^\circ$$

$$\text{so } P_{R2} = \frac{1}{2} (1.48)^2 = 1.1 \, \text{W}$$

Now with  $P_C = P_L = 0$

$$\text{so } P_R = 1.1 + 3.5 = 4.6 \, \text{W}$$

**Ex. 11.4-1**

$$I_{\text{eff}} = \sqrt{1/T \int_0^T i^2(t) dt} = \sqrt{\frac{1}{3} \left[ \int_0^2 (10)^2 dt + \int_2^3 (5)^2 dt \right]} = 8.66$$

**Ex. 11.4-2**

(a)  $i(t) = 2 \cos 3t \Rightarrow I_{\text{eff}} = \frac{I_{\text{max}}}{\sqrt{2}} = 2/\sqrt{2} = \sqrt{2}$

(b)  $i(t) = \cos(3t - 90^\circ) + \cos(3t + 60^\circ)$


$$\therefore I = 1 \angle -90^\circ + 1 \angle 60^\circ = -j + 1/2 + j\sqrt{3}/2 = .518 \angle -15^\circ$$

$$\text{So } i(t) = .518 \cos(3t - 15^\circ) \Rightarrow I_{\text{eff}} = \frac{.518}{\sqrt{2}} = .366$$

(c)  $I_{\text{eff}}^2 = \left( \frac{2}{\sqrt{2}} \right)^2 + \left( \frac{3}{\sqrt{2}} \right)^2 \Rightarrow I_{\text{eff}} = 2.55$

Use superposition

Ex. 11.4-3

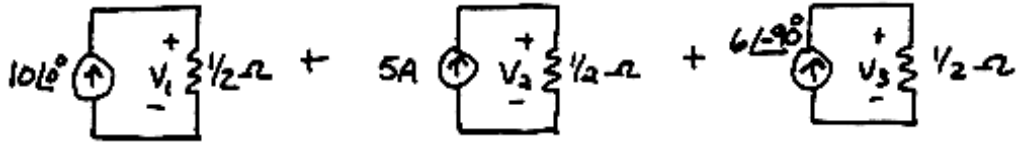

$$\left. \begin{aligned} V_1 &= 5\angle 0^\circ \text{ V} \\ V_2 &= 2.5 \text{ V (DC)} \\ V_3 &= 3\angle -90^\circ \text{ V} \end{aligned} \right\}$$

now since  $V_1$  &  $V_3$  have the same frequencies, can add them


$$V_1 + V_3 = 5\angle 0^\circ + 3\angle -90^\circ = 5 - j3 = 5.83\angle -31.0^\circ$$

$$\text{So } v_R(t) = v_1 + v_2 + v_3 = 2.5 + 5.83 \cos(100t - 31.0^\circ) \text{ V}$$

$$V_{R,\text{eff}}^2 = (2.5)^2 + \left(\frac{5.83}{\sqrt{2}}\right)^2 = 23.24$$

$$\therefore \underline{V_{R,\text{eff}} = 4.82 \text{ V}}$$

Ex. 11.5-1

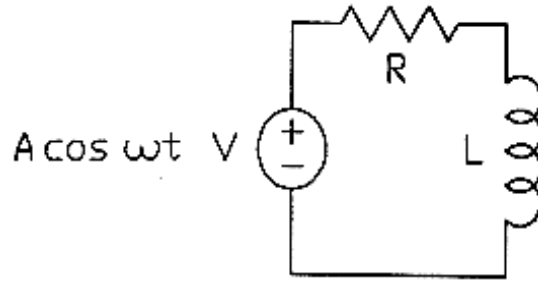

**Mathcad analysis**

Enter the parameters of the voltage source:

$$A := 12 \quad \omega := 2$$

Enter the values of R, L, and C:  $R := 10$

$$L := 4 \quad C := 0.1$$

The impedance seen by the voltage source is:

$$Z := R + j \cdot \omega \cdot L$$

The mesh current is:  $I := \frac{A}{Z}$

The complex power delivered by the source is:

$$S_v := \frac{\bar{I} \cdot (I \cdot Z)}{2} \quad S_v = 4.39 + 3.512i$$

The complex power delivered to the resistor is:

$$S_r := \frac{\bar{I} \cdot (I \cdot R)}{2} \quad S_r = 4.39$$

The complex power delivered to the inductor is:


$$S_l := \frac{\bar{I} \cdot (I \cdot j \cdot \omega \cdot L)}{2} \quad S_l = 3.512i$$

Verify  $S_v = S_r + S_l$ :

$$S_r + S_l = 4.39 + 3.512i$$

$$S_v = 4.39 + 3.512i$$

Ex. 11.5-2

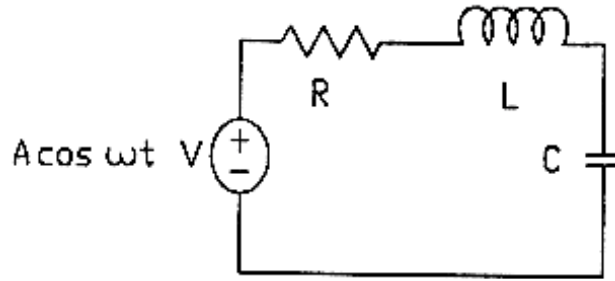

**Mathcad analysis**

Enter the parameters of the voltage source:       $A := 12$        $\omega := 2$

Enter the values of R, L, and C:       $R := 10$        $L := 4$        $C := 0.1$

The impedance seen by the voltage source is:       $Z := R + j \cdot \omega \cdot L + \frac{1}{j \cdot \omega \cdot C}$

The mesh current is :       $I := \frac{A}{Z}$

The complex power delivered by the source is :       $S_v := \frac{\bar{I} \cdot (I \cdot Z)}{2}$        $S_v = 6.606 + 1.982i$


The complex power delivered to the resistor is :       $S_r := \frac{\bar{I} \cdot (I \cdot R)}{2}$        $S_r = 6.606$

The complex power delivered to the inductor is :       $S_l := \frac{\bar{I} \cdot (I \cdot j \cdot \omega \cdot L)}{2}$        $S_l = 5.284i$

The complex power delivered to the capacitor is :       $S_c := \frac{\bar{I} \cdot \left( I \cdot \frac{1}{j \cdot \omega \cdot C} \right)}{2}$        $S_c = -3.303i$

Verify  $S_v = S_r + S_l + S_c$  :       $S_r + S_l + S_c = 6.606 + 1.982i$        $S_v = 6.606 + 1.982i$

Ex. 11.5-3

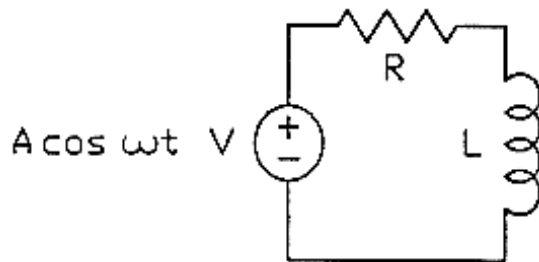

**Mathcad analysis**

Enter the parameters of the voltage source:       $A := 12$        $\omega := 2$

Enter the average and reactive power delivered to the RL circuit:       $P := 8$        $Q := 6$

The complex power delivered to the RL circuit is:       $S := P + j \cdot Q$

The impedance seen by the voltage source is:       $Z := \frac{A^2}{2 \cdot S}$

Calculate the required values of R and L       $R := \text{Re}(Z)$        $L := \frac{\text{Im}(Z)}{\omega}$        $R = 5.76$        $L = 2.16$

The mesh current is :  $I = \frac{A}{Z}$

The complex power delivered by the source is :  $S_v = \frac{\bar{I} \cdot (I \cdot Z)}{2}$   $S_v = 8 + 6i$

The complex power delivered to the resistor is :  $S_r = \frac{\bar{I} \cdot (I \cdot R)}{2}$   $S_r = 8$

The complex power delivered to the inductor is :  $S_l = \frac{\bar{I} \cdot (I \cdot j \cdot \omega \cdot L)}{2}$   $S_l = 6i$

Verify  $S_v = S_r + S_l$  :  $S_r + S_l = 8 + 6i$   $S_v = 8 + 6i$

**Ex. 11.6-1**  $PF = \cos(\angle Z) = \cos \left[ \tan^{-1} \left( \frac{\omega L}{R} \right) \right] = \cos \left[ \tan^{-1} \left( \frac{377(5)}{100} \right) \right] = 0.053$

**Ex. 11.6-2**  $PF = \cos(\angle Z) = \cos \left[ \tan^{-1} \left( \frac{Z_I}{Z_R} \right) \right] = \cos \left[ \tan^{-1} \left( \frac{80}{50} \right) \right] = 0.53$

Assume lagging

$$\Rightarrow X_I = \frac{(50)^2 + (80)^2}{50 \tan(\cos^{-1} 0.53)} = -111.25 \Omega$$

$$\therefore Z_I = -j 111.25 \Omega$$

**Ex. 11.6-3**  $P_T = 30 + 86 = 116$

$$\therefore S_T = P_T + j Q_T = 116 + j51 = 126.7 \angle 23.7^\circ$$

$$\Rightarrow \underline{PF_{\text{plant}} = \cos 23.7^\circ = 0.915}$$

**Ex. 11.6-4**  $P = VI \cos \theta$

$$I = \frac{P}{V \cos \theta} = \frac{4000}{(110)(.82)} = 44.3 \text{ A}$$

$$Z = \frac{V}{I} \angle \cos^{-1}(.82) = 2.48 \angle 34.9^\circ = 2.03 + j 1.42 = R + jX$$


To correct power factor to 0.95 have

$$X_I = \frac{R^2 + X^2}{R \tan(\cos^{-1} \text{ pfc}) - X} = \frac{(2.03)^2 + (1.42)^2}{(2.03) \tan(18.19^\circ) - 1.42} = -8.16 \Omega$$

$$C = \frac{-1}{\omega X_I} = \underline{325 \mu\text{F}}$$

Ex. 11.7-1

a)

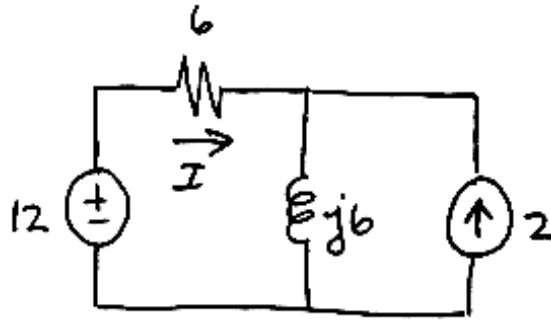


$$I = \frac{12}{6+j6} - \frac{j6}{6+j6} 2 = 2e^{-j90^\circ}$$

$$i(t) = 2 \cos(3t - 90^\circ) \text{ A}$$


$$P = \left(\frac{2}{\sqrt{2}}\right)^2 6 = \underline{12 \text{ W}}$$

b)

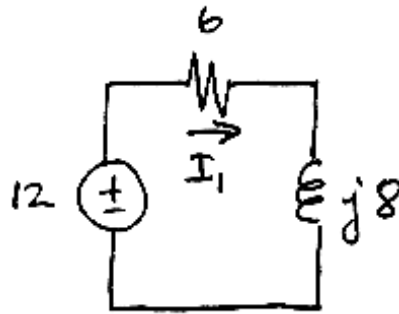

$$I_1 = \frac{12}{6+j8} = 1.2e^{-j53.13^\circ}$$

$$i_1(t) = 1.2 \cos(4t - 53.13^\circ)$$

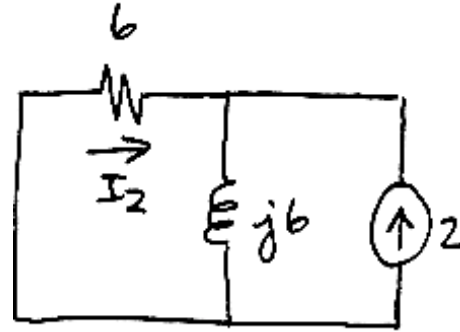


$$I_2 = -\frac{j6}{6+j6} 2 = 1.414e^{-j135^\circ}$$

$$i_2(t) = 1.4 \cos(3t - 135^\circ)$$

$$i(t) = i_1(t) + i_2(t) = 1.2 \cos(4t - 53^\circ) + 1.4 \cos(3t - 135^\circ)$$

$$P = P_1 + P_2 = \left(\frac{1.2}{\sqrt{2}}\right)^2 6 + \left(\frac{1.414}{\sqrt{2}}\right)^2 6 = \underline{10.32 \text{ W}}$$

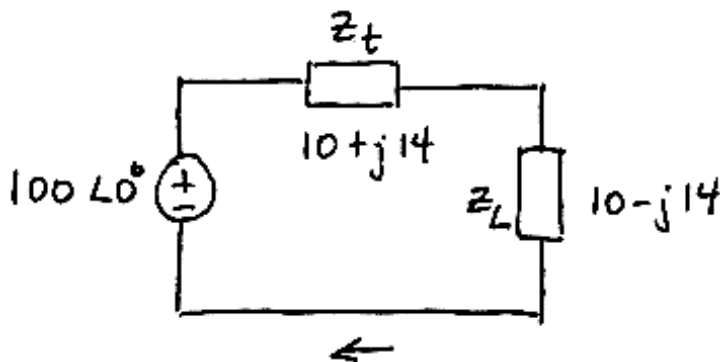
Ex. 11.8-1 For maximum power, transfer  $Z_L = Z_t^* = \underline{10-j14}$



$$I = \frac{100}{(10+j14)(10-j14)} = 5$$

$$P_L = \left(\frac{5}{\sqrt{2}}\right)^2 \text{Re}(10-j14) = \underline{125 \text{ W}}$$

Ex. 11.8-2

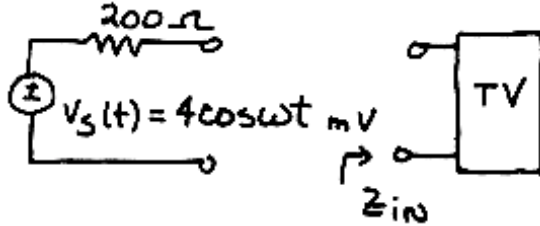

If the station transmits a signal in

52 MHz, then  $\omega = 2\pi f = 104\pi \times 10^6$  rad/sec

So the received signal is

$$v_s(t) = 4 \cos(104\pi \times 10^6 t) \text{ mV}$$

- a) If receiver has input impedance  $Z_{in} = 300 \Omega$

$$V_{in} = \frac{Z_{in}}{R + Z_{in}} \cdot V_s = \frac{300}{200 + 300} \times 4 \times 10^{-3} = 2.4 \text{ mV}$$

$$P = \frac{1}{2} V_m^2 \left( \frac{1}{R_L} \right) = \left( \frac{2.4 \times 10^{-3}}{2(300)} \right)^2 = \underline{9.6 \text{ nW}}$$

- b) If two receivers are in parallel

$$Z_{in} = \frac{(300)(300)}{300 + 300} = 150 \Omega$$

$$V_{in} = \frac{Z_{in}}{R + Z_{in}} V_s = \frac{150}{200 + 150} (4 \times 10^{-3}) = 1.71 \times 10^{-3} \text{ V}$$


$$\text{total } P = \frac{V_{in}^2}{2} \left( \frac{1}{Z_{in}} \right) = \frac{(1.71 \times 10^{-3})^2}{2(150)} = \underline{9.7 \text{ nW}} \quad \text{or} \quad 4.85 \text{ nW to each set}$$

- c) Need  $Z_{in} = R$  for max. power  $\therefore$  need another  $R_a$  in || with  $Z_{in}$

$$\Rightarrow \frac{R_a(300)}{R_a + 300} = 200 \Rightarrow R_a = 600 \Omega$$

$$\text{So } P_{\max} = \frac{V_m^2}{2Z_{in}} = \frac{(2 \times 10^{-3})^2}{2(200)} = \underline{10 \text{ nW}} \quad \text{or} \quad 5 \text{ nW to each set}$$

Ex 11.9-1

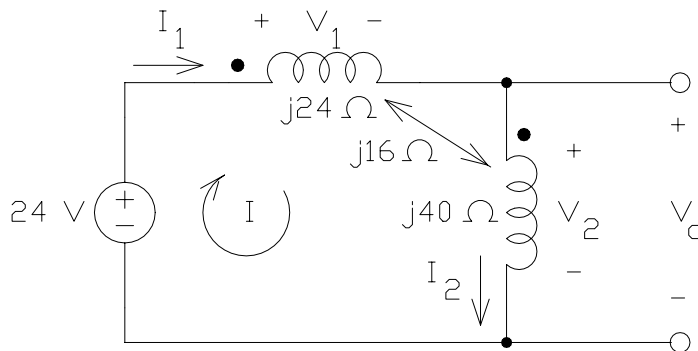

Coil voltages:

$$\mathbf{V}_1 = j24 \mathbf{I}_1 + j16 \mathbf{I}_2 = j40 \mathbf{I}$$

$$\mathbf{V}_2 = j16 \mathbf{I}_1 + j40 \mathbf{I}_2 = j56 \mathbf{I}$$

Mesh equation:

$$24 = \mathbf{V}_1 + \mathbf{V}_2 = j40 \mathbf{I} + j56 \mathbf{I} = j96 \mathbf{I}$$


$$\mathbf{I} = \frac{24}{j96} = -j \frac{1}{4}$$

$$\mathbf{V}_o = \mathbf{V}_2 = (j56) \left( -j \frac{1}{4} \right) = 14$$

$$v_o = 14 \cos 4t \text{ V}$$



**Ex 11.9-2**

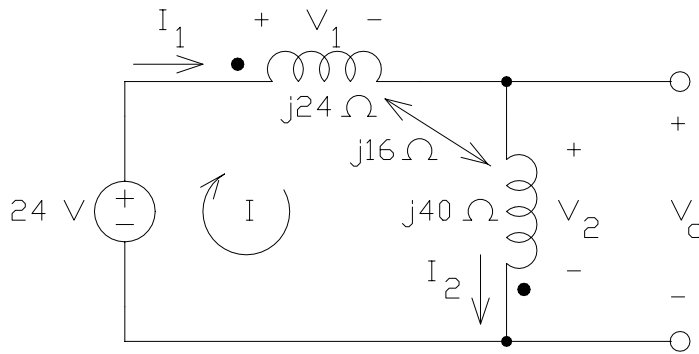

Coil voltages:

$$\mathbf{V}_1 = j24 \mathbf{I}_1 - j16 \mathbf{I}_2 = j8 \mathbf{I}$$

$$\mathbf{V}_2 = -j16 \mathbf{I}_1 + j40 \mathbf{I}_2 = j24 \mathbf{I}$$

Mesh equation:


$$24 = \mathbf{V}_1 + \mathbf{V}_2 = j8 \mathbf{I} + j24 \mathbf{I} = j32 \mathbf{I}$$

$$\mathbf{I} = \frac{24}{j32} = -j \frac{3}{4}$$

$$\mathbf{V}_o = \mathbf{V}_2 = (j24) \left( -j \frac{3}{4} \right) = 18$$

$$v_o = 18 \cos 4t \text{ V}$$

**Ex 11.9-3**

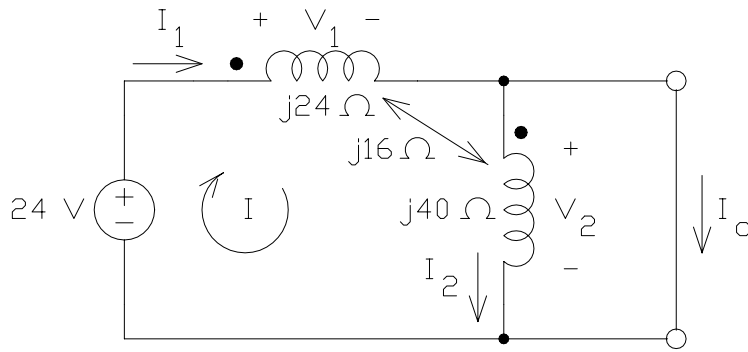

$$0 = \mathbf{V}_2 = j16 \mathbf{I}_1 + j40 \mathbf{I}_2$$

$$\Rightarrow \mathbf{I}_1 = -\frac{40}{16} \mathbf{I}_2 = -2.5 \mathbf{I}_2$$

$$\begin{aligned} \mathbf{V}_s &= \mathbf{V}_1 = j24 \mathbf{I}_1 + j16 \mathbf{I}_2 \\ &= j(24(-2.5) + 16) \mathbf{I}_2 \\ &= -j44 \mathbf{I}_2 \end{aligned}$$


$$\mathbf{I}_2 = \frac{24}{-j44} = j \frac{6}{11}$$

$$\begin{aligned} \mathbf{I}_o &= \mathbf{I}_1 - \mathbf{I}_2 = (-2.5 - 1) \mathbf{I}_2 \\ &= -3.5 \mathbf{I}_2 \end{aligned}$$

$$= -3.5 \left( j \frac{6}{11} \right) = -j1.909$$

$$i_o = 1.909 \cos (4t - 90^\circ) \text{ A}$$

Ex 11.9-4

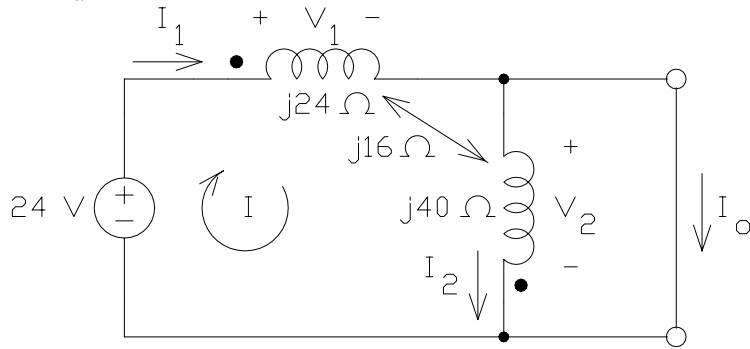

$$0 = V_2 = -j16 I_1 + j40 I_2$$

$$\Rightarrow I_1 = \frac{40}{16} I_2 = 2.5 I_2$$

$$\begin{aligned} V_s = V_1 &= j24 I_1 - j16 I_2 \\ &= j(24(2.5) - 16) I_2 \\ &= j44 I_2 \end{aligned}$$

$$I_2 = \frac{24}{j44} = -j \frac{6}{11}$$

$$\begin{aligned} I_o = I_1 - I_2 &= (2.5 - 1) I_2 \\ &= 1.5 I_2 \end{aligned}$$

$$= 1.5 \left( -j \frac{6}{11} \right) = -j 0.818$$

$$i_o = 0.818 \cos(4t - 90^\circ) \text{ A}$$

Ex. 11.10-1



(model of ideal transformer)

$$\text{KVL left ckt: } (1 + j3)I_1 + V_1 = 10 \quad (1)$$

$$\text{KVL right ckt: } I_2 = \frac{-5V_1}{100 - j75} \quad (2)$$

$$\text{also: } I_1 = -5I_2 \quad (3)$$



$$(2) \text{ into } (3) \Rightarrow I_1 = \frac{25V_1}{100 - j75} = \frac{V_1}{4 - j3}$$

$$\therefore \text{plugging into } (1) \Rightarrow (1 + j3) \left( \frac{V_1}{4 - j3} \right) + V_1 = 10$$

$$\Rightarrow \underline{V_1 = 10 \angle -36.9^\circ}$$

$$\therefore \underline{I_1 = \frac{V_1}{4 - j3} = 2 \angle 0^\circ}$$

Ex. 11.10-2

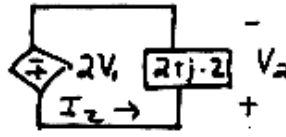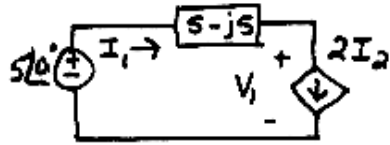

$$2V_1 = V_2 \Rightarrow V_1 = \frac{1}{2}V_2$$

$$\text{also } I_1 = 2I_2$$

$$\text{So } Z_1 = \frac{V_1}{I_1} = \frac{V_2/2}{2I_2} = \frac{1}{4}Z_2 = \frac{2.01}{4} \angle 5.7^\circ = 0.5 \angle 5.7^\circ \Omega$$

$$Z_{in} = 5 - j5 + \frac{1}{4}(2 + j0.2) = 5.5 - j4.95$$

$$I_1 = \frac{5 \angle 0^\circ}{Z_{in}} = \frac{5 \angle 0^\circ}{7.4 \angle -42^\circ} = 0.68 \angle 42^\circ \text{ A}$$


$$V_1 = I_1 \cdot Z_1 = (0.68 \angle 42^\circ)(0.5 \angle 5.7^\circ) = 0.34 \angle 47.7^\circ \text{ V}$$

$$\text{So } i_1(t) = 0.68 \cos(10t + 42^\circ) \text{ A} \quad \& \quad v_1(t) = 0.34 \cos(10t + 47.7^\circ) \text{ V}$$

$$v_2(t) = n v_1(t) = 0.68 \cos(10t + 47.7^\circ) \text{ V}$$

$$i_2(t) = \frac{i_1(t)}{n} = 0.34 \cos(10t + 42^\circ) \text{ A}$$

Ex. 11.10-3

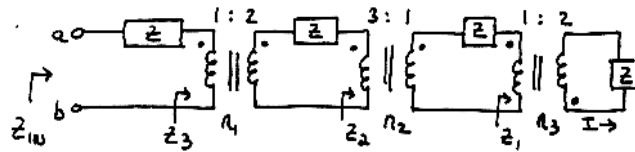

$$Z_1 = \frac{Z}{n_3^2} = \frac{Z}{4}$$

$$Z_3 = \frac{1}{n_1^2}(Z + Z_2)$$


$$Z_2 = \frac{1}{n_1^2} \left( Z + \frac{Z}{n_3^2} \right) = 9 \left( Z + \frac{Z}{4} \right)$$

$$\text{Now } Z_{ab} = Z_{IN} = Z + Z_3 = Z + \frac{1}{4} \left( Z + 9 \left( Z + \frac{Z}{4} \right) \right) = 4.0625 Z$$

Problems

Section 11-3: Instantaneous Power and Average Power

P. 11.3-1

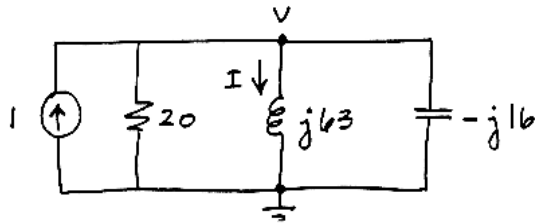


$$I = \frac{V}{20} + \frac{V}{j63} + \frac{V}{-j16} \Rightarrow V = 14.6 \angle -43^\circ$$

$$I = \frac{V}{j63} = 0.23 \angle -133^\circ$$

$$p(t) = i(t)v(t) = 0.23(\cos(2\pi \cdot 10^3 t - 133^\circ)) \times 14.6 \cos(2\pi \cdot 10^3 t - 43^\circ)$$

$$= 3.36 \cos(2\pi \cdot 10^3 t - 133^\circ) \cos(2\pi \cdot 10^3 t - 43^\circ) = 1.68 (\cos(90^\circ) + \cos(4\pi \cdot 10^3 t - 176^\circ)) = 1.68 \cos(4\pi \cdot 10^3 t - 176^\circ)$$

P. 11.3-2

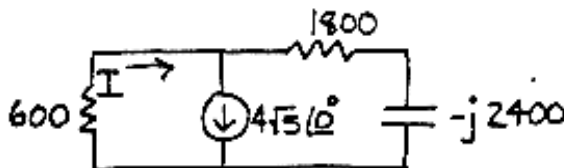


Using current divider  $I = 4\sqrt{5} \left[ \frac{1800 - j2400}{1800 - j2400 + 600} \right] = 5\sqrt{5/2} \angle -8.1^\circ$  mA

$\therefore P_{600\Omega} = 1/2 |I|^2 600 = 300(25)(5/2) = 1.875 \times 10^4 \mu W = 18.75 \text{ mW}$

$P_{source} = 1/2 |V||I| \cos \theta = 1/2 (600)(5\sqrt{5/2})(4\sqrt{5}) \cos(-8.1^\circ) = 2.1 \times 10^4 \mu W = 21 \text{ mW}$

P. 11.3-3

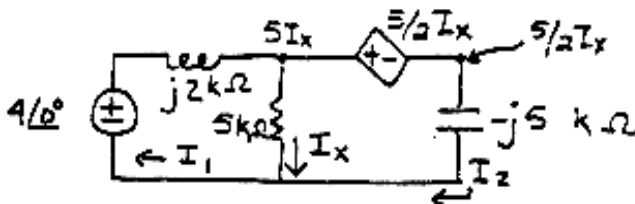

KCL at  $5I_x$ :  $\frac{5I_x - 4}{j2} + I_x + \frac{5/2 I_x}{-j5} = 0$


$$\Rightarrow I_x = \frac{2}{\sqrt{5}} \angle -26.6^\circ$$

$\therefore I_2 = \frac{5}{2} I_x / -j5 = \frac{1}{\sqrt{5}} \angle 63.4^\circ$ ,  $I_1 = I_x + I_2 = 1 \text{ mA}$

(a)  $P_{\text{indep source}} = 1/2 (4)(I_{1,\text{max}}) \cos(0^\circ) = 1/2 (4)(1) = 2 \text{ mW}$

(b)  $P_{\text{dep. source}} = 1/2 (5/2 I_{x,\text{max}})(I_{2,\text{max}}) \cos(90^\circ) = 0$

P. 11.3-4

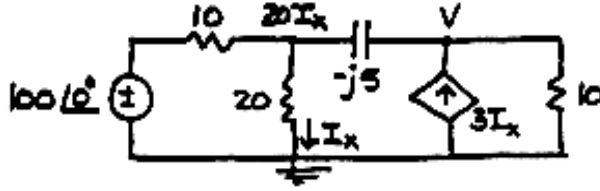

$$\text{KCL at } 20I_X: \frac{20I_X - 100}{10} + I_X + \frac{20I_X - V}{-j5} = 0 \Rightarrow I_X(20 - j15) - V = -j50 \quad (1)$$


$$\text{KCL at } V: \frac{V - 20I_X}{-j5} - 3I_X + \frac{V}{10} = 0 \Rightarrow I_X(-40 + j30) + V(-2 - j) = 0$$

Using Cramer's rule

$$I_X = \frac{j50(2 - j)}{(40 - j30) - (20 - j15)(2 - j)} = \frac{50\sqrt{5}\angle 63.4^\circ}{25\angle 53.1^\circ} = 2\sqrt{5}\angle 10.3^\circ \text{ A}$$

$$\therefore P_{\text{AVE}} = \frac{1}{2}|I_X|^2(20) = 10(2\sqrt{5})^2 = 200 \text{ W}$$

P. 11.3-5

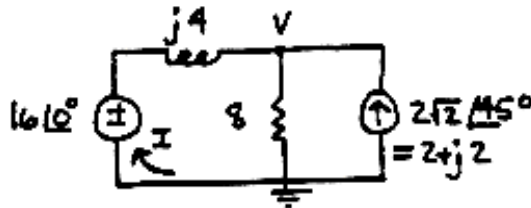

$$\text{KCL at } V: \frac{(V - 16)}{j4} + \frac{V}{8} - (2 + j2) = 0$$

$$\Rightarrow V = 16\sqrt{\frac{2}{5}} \angle 18.4^\circ$$

$$I = \frac{(16 - V)}{j4} = \sqrt{3.2} \angle -116.6^\circ$$


$$\therefore P_{\text{AVE } 8\Omega} = \frac{1}{2} \frac{|V|^2}{8} = \frac{1}{2} \frac{(16\sqrt{\frac{2}{5}})^2}{8} = 6.4 \text{ W absorbed}$$

$$P_{\text{AVE source current}} = -\frac{1}{2}|V|(2\sqrt{2})\cos\theta = -\frac{1}{2}(16\sqrt{\frac{2}{5}})(2\sqrt{2})\cos(26.6^\circ) = -12.8 \text{ W absorbed}$$

$$P_{\text{AVE inductor}} = 0$$

$$P_{\text{AVE Voltage source}} = -1/2(16)|I|\cos\theta = -1/2(16)(\sqrt{3.2})\cos(-116.6^\circ) = 6.4 \text{ W absorbed}$$

P11.3-6

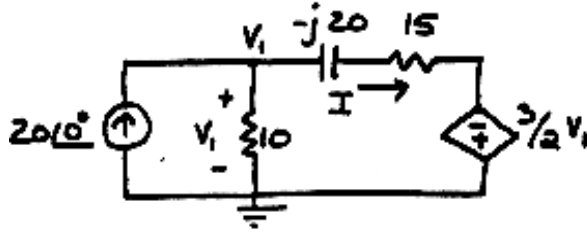

$$\begin{aligned} \text{KCL at } V_1: & -20 + \frac{V_1}{10} + \frac{V_1 + (3/2)V_1}{15 - j20} = 0 \\ \Rightarrow & V_1 = 50\sqrt{5} \angle -26.6^\circ \\ \Rightarrow & I = \frac{V_1 + 3/2 V_1}{15 - j20} = \frac{5/2 V_1}{25 \angle -53.1^\circ} = 5\sqrt{5} \angle 26.6^\circ \end{aligned}$$

$$P_{\text{AVE } 10\Omega} = \frac{1}{2} \frac{|V_1|^2}{10} = \frac{1}{2} \frac{(50\sqrt{5})^2}{10} = \underline{625 \text{ W absorbed}}$$


$$\begin{aligned} P_{\text{AVE current source}} &= -\frac{1}{2} |V|(20) \cos \theta = -\frac{1}{2} (50\sqrt{5})(20) \cos(-26.6^\circ) \\ &= \underline{-1000 \text{ W absorbed}} \end{aligned}$$

$$P_{\text{AVE } 15\Omega} = \frac{1}{2} |I|^2 (15) = -\frac{1}{2} (5\sqrt{5})^2 (15) = \underline{937.5 \text{ W absorbed}}$$

$$\begin{aligned} P_{\text{AVE voltage source}} &= -\frac{1}{2} |I| \left| \frac{3}{2} V_1 \right| \cos \theta = -\frac{1}{2} (5\sqrt{5}) (75\sqrt{5}) \cos(-53.1^\circ) \\ &= \underline{-562.5 \text{ W absorbed}} \end{aligned}$$

$$P_{\text{AVE capacitor}} = \underline{0 \text{ W}}$$

P11.3-7

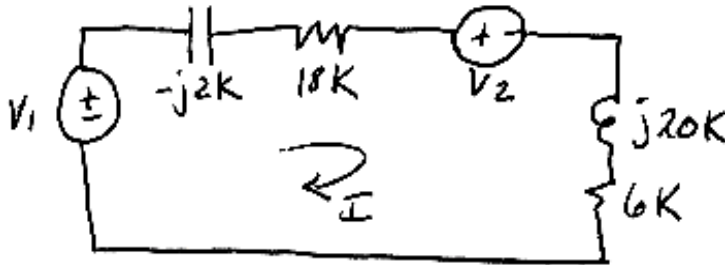

$$\begin{aligned} V_1 &= 4 \angle 60^\circ \text{ V} \\ V_2 &= 8 \angle 0^\circ \text{ V} \\ \omega &= 5 \times 10^6 \text{ rad/sec} \end{aligned}$$

$$\text{KVL: } -4 \angle 60^\circ - j2I + 18I + 8 \angle 0^\circ + j20I + 6I = 0 \quad \text{Note: } I \text{ in mA}$$

$$\text{Solving yields } I = 0.231 \angle -67^\circ \text{ mA}$$

$$\text{Then } P_{\text{ave } 6k\Omega} = \frac{1}{2} |I|^2 R = \left( \frac{0.231 \times 10^{-3}}{2} \right)^2 (6 \times 10^3) = \underline{160 \mu\text{W absorbed}}$$

$$P_{\text{ave } V_1} = \frac{1}{2} |V| |I| \cos \theta = \frac{1}{2} (4) (0.231 \times 10^{-3}) \cos(-67 - 60^\circ) = \underline{\frac{277 \mu\text{W}}{\text{delivered}}}$$

**P11.3-8**

$$Z = \frac{200 (j200)}{200 (1+j)} = \frac{200 \angle 90^\circ}{\sqrt{2} \angle 45^\circ} = \frac{200}{\sqrt{2}} \angle 45^\circ$$

$$I = \frac{120 \angle 0^\circ}{\frac{200}{\sqrt{2}} \angle 45^\circ} = 0.85 \angle -45^\circ, \quad I_R = \left( \frac{200}{200 + j200} \right) I = 0.6 \angle 0^\circ \text{ A}$$

$$P = I^2 R = (0.6)^2 (200) = 72 \text{ W} \quad \underline{w = (72) (1) = 72 \text{ J}}$$

### Section 11-4: Effective Value of a Periodic Waveform

**P11.4-1**

a)  $i = 2 - 4 \cos 2t$

(Treat as two sources of differing frequency)

$$2A \text{ source: } I_{\text{eff}} = \lim_{T \rightarrow \infty} \sqrt{\frac{1}{T} \int_0^T (2)^2 dt} = 2$$

$$4 \cos 2t \text{ source: } I_{\text{eff}} = \frac{4}{\sqrt{2}}$$

$$\therefore I_{\text{eff}}^2_{\text{Total}} = (2)^2 + \left( \frac{4}{\sqrt{2}} \right)^2 = 12$$

$$\Rightarrow \underline{I_{\text{rms}} = I_{\text{eff}} = \sqrt{12} = 2\sqrt{3} \text{ A}}$$

(b)  $i = 3 \cos(\pi t - 90^\circ) + \sqrt{2} \cos \pi t$

$$I = 3 \angle -90^\circ + \sqrt{2} \angle 0^\circ = \sqrt{2} - j3 = 3.32 \angle -64.8^\circ$$

$$\Rightarrow \underline{I_{\text{rms}} = \frac{3.32}{\sqrt{2}} = 2.35 \text{ A}}$$

(c)  $i = 2 \cos 2t + 4\sqrt{2} \cos(2t + 45^\circ) + 12 \cos(2t - 90^\circ)$

$$I = 2 \angle 0^\circ + 4\sqrt{2} \angle 45^\circ + 12 \angle -90^\circ = 2 + 4 + j4 - j12 = 10 \angle -53.1^\circ$$

$$\Rightarrow \underline{I_{\text{rms}} = \frac{10}{\sqrt{2}} = 5\sqrt{2} \text{ A}}$$

**P11.4-2**

$$(a) \quad f(t) = \begin{cases} \sqrt{3/5} & 0 < t < 4 \\ -\sqrt{3/5}(t-5) & 4 < t < 5 \\ 0 & 5 < t < 9 \\ \sqrt{3/5}(t-9) & 9 < t < 10 \end{cases}$$

$$f_{\text{rms}}^2 = \frac{1}{T} \int_0^T f^2(t) dt = \frac{1}{10} \left[ \int_0^4 \left(\frac{3}{5}\right) dt + \int_4^5 \frac{3}{5}(t-5)^2 dt + \int_9^{10} \frac{3}{5}(t-9)^2 dt \right] = \frac{1}{10} \left( \frac{14}{5} \right) \Rightarrow \underline{f_{\text{rms}} = \frac{\sqrt{7}}{5}}$$

$$(b) \quad r(t) = \begin{cases} \sqrt{3/2} - \sqrt{3/6}t & 0 < t < 6 \\ -3\sqrt{3/2} + \sqrt{3/6}t & 6 < t < 12 \end{cases}$$

$$f_{\text{rms}} = \sqrt{\frac{1}{12} \left[ \int_0^6 \left(\sqrt{3/2} - \sqrt{3/6}t\right)^2 dt + \int_6^{12} \left(-3\sqrt{3/6} + \sqrt{3/6}t\right)^2 dt \right]} = \underline{1/2}$$

$$(c) \quad f(t) = \begin{cases} \sin t & 0 < t < \pi \\ 0 & \pi < t < 2\pi \end{cases}$$

$$f_{\text{rms}} = \sqrt{\frac{1}{2\pi} \left[ \int_0^\pi \sin^2 t dt + 0 \right]} = \sqrt{\frac{1}{4}} = \underline{1/2}$$

**P11.4-3** period =  $T = 4$

$$\therefore V_{\text{ave}} = \frac{(1)(1) + (3)(2) + (0)(1)}{4} = \underline{1.75V}$$

$$V_{\text{rms}} = \left[ \frac{(1)^2(1) + (3)^2(2) + (0)^2(1)}{4} \right]^{1/2} = \underline{2.18V}$$

**P11.4-4**

$$a) \quad v(t) = 1 + \cos\left(\frac{2\pi}{T}t\right)$$

$$V_{\text{eff}}^2 = V_{\text{DC}}^2 + V_{\text{AC}}^2$$

$$V_{\text{DC}}^2 = \left(\frac{1}{T} \int_0^T 1 dt\right) = \frac{t}{T} \Big|_0^T = \left(\frac{T}{T} - 0\right) = 1$$

$$V_{\text{AC}} = \frac{1}{\sqrt{2}} \quad \therefore V_{\text{eff}} = \sqrt{1^2 + \left(\frac{1}{\sqrt{2}}\right)^2} = \underline{1.225V}$$



$$\begin{aligned}
 \text{b) } \quad \omega &= \frac{2\pi}{T}, \quad I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} \\
 I_{\text{rms}}^2 &= \frac{1}{T} \int_0^{T/2} (A \sin \omega t)^2 dt = \frac{A^2}{T} \int_0^{T/2} \frac{1}{2} (1 - \cos 2\omega t) dt \\
 &= \frac{A^2}{2T} \left[ \int_0^{T/2} dt - \int_0^{T/2} \cos 2\omega t dt \right] = \frac{A^2}{4} \\
 \text{So } I_{\text{rms}} &= \sqrt{\frac{A^2}{4}} = \frac{A}{2}, \quad \text{where } A = 10 \text{ mA} \\
 \text{So } \underline{I_{\text{rms}}} &= 5 \text{ mA}
 \end{aligned}$$


**P11.4-5**

$$\begin{aligned}
 V_t &= \begin{cases} 90t & 0 \leq t \leq .1 \\ 90(0.2-t) & .1 \leq t \leq .2 \\ 0 & .2 \leq t \leq .3 \end{cases} \\
 V_{\text{rms}}^2 &= \frac{1}{.3} \left[ \int_0^{.1} (90t)^2 dt + \int_{.1}^{.2} [90(0.2-t)]^2 dt \right] \\
 &= \frac{90^2}{.3} \left[ \int_0^{.1} t^2 dt + \int_{.1}^{.2} (0.2-t)^2 dt \right] \\
 &= \frac{90^2}{.3} \left[ \frac{.001}{3} + \frac{.001}{3} \right] = 18 \\
 \therefore V_{\text{rms}} &= \sqrt{18} = \underline{4.24 \text{ V}}
 \end{aligned}$$

Section 11-5: Complex Power

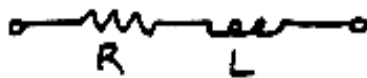**P11.5-1**

$$\Rightarrow X = -\frac{1}{\omega C} = -11588 \Rightarrow C = \frac{1}{(11.588)(2\pi)(60)} = 229 \mu\text{F}$$



$$R = \frac{P}{I^2} = \frac{20}{(2)^2} = \underline{5\Omega}$$

$$\cos \theta = \frac{P}{VI} = \frac{20}{(2)(26)} = .3846 \Rightarrow \theta = 67.4^\circ$$

$$\text{reactive power : } Q = VI \sin \theta = (2)(26) \sin 67.4^\circ = 48 \text{ VAR}$$

$$\text{but } Q = I^2 X_L$$

$$\therefore X_L = \frac{Q}{I^2} = \frac{48}{(2)^2} = 12\Omega \Rightarrow L = \frac{X_L}{\omega} = \frac{12}{377} = \underline{31.8 \text{ mH}}$$

**P11.5-2** From Problem P11.5-1:

$$S_{\text{resistor}} = 20 + j0 \text{ VA}$$

$$S_{\text{coil}} = 0 + j48 \text{ VA}$$

$$Z = R + j\omega L = 5 + j12 = 13\angle 67.4^\circ$$


For 26V source :  $I = \frac{V}{Z} = \frac{26\angle 0^\circ}{13\angle 67.4^\circ} = 2\angle -67.4^\circ$

$\therefore S_{26V} = VI^* = (26)(2\angle 67.4^\circ) = 52\angle 67.4^\circ = 20 + j48 \text{ VA}$   
(delivered by)

So  $S_{26V} = -20 - j48 \text{ VA}$  delivered

$S_{\text{Total}} = S_{\text{resistor}} + S_{\text{coil}} + S_{26V} = 20 + j48 - 20 - j48 = \underline{0}$

**P11.5-3**

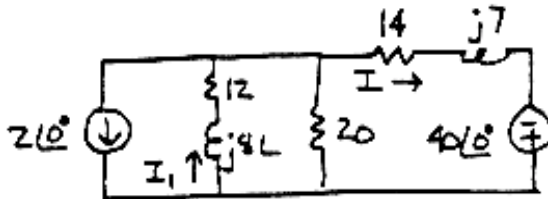

If  $P_{\text{complex}} = \frac{50}{3}\angle 53.1^\circ = \frac{1}{2}I^*(40\angle 0^\circ)$   
 $\Rightarrow I^* = \frac{5}{6}\angle 53.1^\circ$   
 $\Rightarrow I = \frac{5}{6}\angle -53.1^\circ = \frac{1}{2} - j\frac{2}{3} \text{ A}$


From current divider:  $I_1 = (2+I)\left(\frac{20}{32+j8L}\right) = \frac{75-j20}{48+j12L} \quad (1)$

Also from KVL:  $I_1(12+j8L) + I(14+j7) - 40 = 0$

$\Rightarrow I_1 = \frac{170+j35}{72+j48L} \quad (2)$

Equating (1) & (2) (both real & imaginary parts)  $\Rightarrow \underline{L = 2H}$

**P11.5-4**

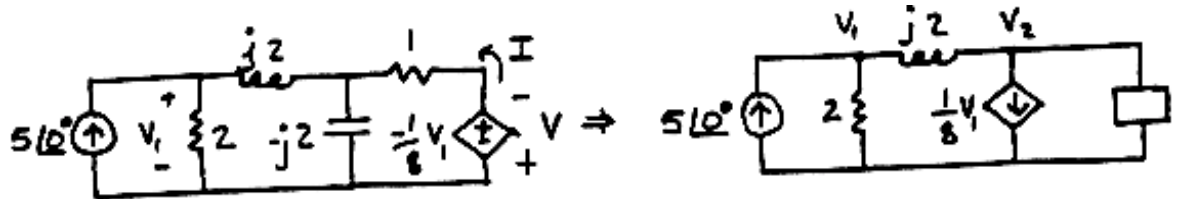

KCL at  $V_1$  :  $-5 + \frac{V_1}{2} + \frac{(V_1 - V_2)}{j2} = 0 \Rightarrow V_1(1+j) - V_2 = 10 \quad (1)$

KCL at  $V_2$  :  $\frac{(V_2 - V_1)}{j2} + \frac{1}{8}V_1 + \frac{V_2}{(.8+j.4)} = 0 \Rightarrow V_1(-4+j) + V_2(j8) = 0 \quad (2)$

Using Cramer's rule


$V_1 = \frac{80}{(4-j) - j8(1+j)} = (16/3)\angle 126.9^\circ$

$\therefore I = -\frac{1}{8}V_1 - V_2 = -\frac{1}{8}V_1 - V_1(1+j) + j10 = 2.66\angle 126.9^\circ$

$\therefore \text{Complex power} = S = \frac{1}{2}I^*(-(1/8)V_1) = \frac{1}{2}(2.66\angle -126.9^\circ)\left(-\frac{2}{3}\angle 36.9^\circ\right) = -j8/9 \text{ VA}$

Now  $S = P + jQ = j\frac{8}{9} \Rightarrow \underline{P=0, Q=\frac{8}{9} \text{ VAR}}$

P11.5-5

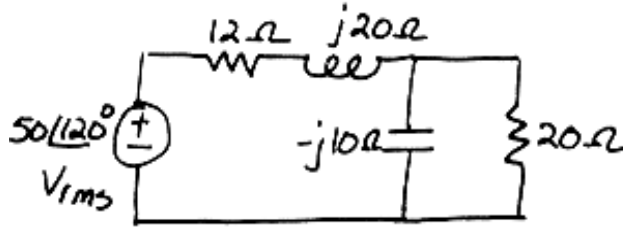


$$Z_{eq} = 16 + j12 = 20\angle 36.87^\circ$$

$$I = \frac{50\angle 120^\circ}{20\angle 36.87^\circ} = 2.5\angle 83.13^\circ \text{ A}$$

$$S = VI^* = (50\angle 120^\circ)(2.5\angle -83.13^\circ) \\ = 125\angle 36.87^\circ = \underline{100 + j75 \text{ VA}}$$

P 11.5-6

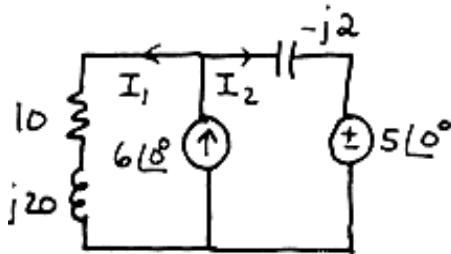

$$\text{KVL: } (10 + j20)I_1 = 5\angle 0^\circ - j2I_2 \quad (1)$$

$$\text{or } (10 + j20)I_1 + j2I_2 = 5\angle 0^\circ$$

$$\text{KCL: } I_1 + I_2 = 6\angle 0^\circ \quad (2)$$

Powers delivered by sources  $\rightarrow S = \frac{1}{2} VI^*$

$$S_{5\angle 0^\circ} = \frac{1}{2}(5\angle 0^\circ)(-I_2^*) = 2.5(6.41\angle(180-4.47)) = -16.0 + j1.1$$

$$S_{6\angle 0^\circ} = \frac{1}{2}[5 - j2I_2](6\angle 0^\circ) = [5 - j2(6.39 + j.5)]3 = 18.0 - j38.3$$

$$S_{\text{Total delivered}} = S_{5\angle 0^\circ} + S_{6\angle 0^\circ} = \underline{2.0 - j37.2 \text{ VA}}$$

$$\text{From (1) \& (2) } \Delta = \begin{vmatrix} 10 + j20 & j2 \\ 1 & 1 \end{vmatrix} = 10 + j18$$

$$I_1 = \frac{1}{\Delta} \begin{vmatrix} 5 & j2 \\ 6 & 1 \end{vmatrix} = \frac{5 - j12}{10 + j18} = 0.63\angle 232^\circ \text{ A} = -0.39 - j.5$$

$$I_2 = 6 - I_1 = 6 + 0.39 + j.5 = 6.39 + j.5 = 6.41\angle 4.47^\circ$$

Powers absorbed


$$S_{10\Omega} = \frac{1}{2}10|I_1|^2 = \frac{10}{2}(.63)^2 = 2.0$$

$$S_{j20\Omega} = \frac{j20}{2}|I_1|^2 = j4.0$$

$$S_{-j2\Omega} = \frac{1}{2}(-j2)|I_2|^2 = -j(6.41)^2 = -j41.1$$

$$S_{\text{Total absorbed}} = \underline{2.0 - j37.1 \text{ VA}} \quad \text{to numerical accuracy } S_{\text{del}} = S_{\text{abs}}$$

P11.5-7

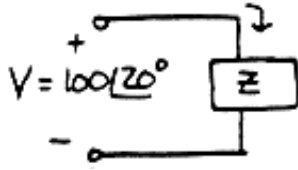

(a)

$$Z = \frac{V}{I} = \frac{100\angle 20^\circ}{25\angle -10^\circ} = 4\angle 30^\circ \Omega$$

(b)  $P = \frac{1}{2} |I| |V| \cos \theta = \frac{1}{2} (100)(25) \cos 30^\circ = 1082.5 \text{ W}$

(c)  $Y = \frac{1}{Z} = .25\angle -30^\circ = .2165 - j.125$


So to cancel phase, need to add  $Y_c = j.125$

= admittance of a capacitor

$$\therefore \omega C = .125$$

$$\Rightarrow C = 1.25 \text{ mF}$$

P 11.5-8

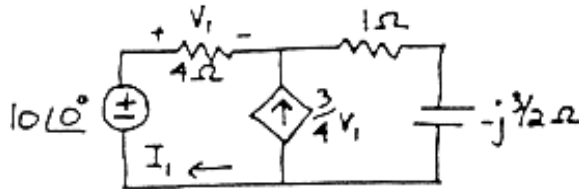

KCL at top node:  $-\frac{V_1}{4} - \frac{3}{4} V_1 + (10 - V_1) / (1 - j \frac{3}{2}) = 0 \Rightarrow V_1 = 4\angle 36.9^\circ$

$$\therefore I_1 = \frac{V_1}{4} = 1\angle 36.9^\circ \Rightarrow I_{1\text{rms}} = \frac{1}{\sqrt{2}} \angle 36.9^\circ$$


$$\therefore \text{complex power phasor for source} = S = I_{1\text{rms}}^* V_{\text{rms}} = \left( \frac{1}{\sqrt{2}} \angle -36.9^\circ \right) \left( \frac{10}{\sqrt{2}} \angle 0^\circ \right) = 5\angle -36.9^\circ \text{ VA}$$

power factor = pf =  $\cos(-36.9^\circ) = .8$  leading

P11.5-9

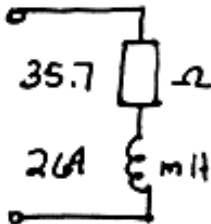1) Inrush conditions  $Z_{\text{coil}} = \frac{\text{VA}(\text{inrush})}{I^2(\text{inrush})} = \frac{136.2}{(1.135)^2} = 105.73 \Omega$

$$R_{\text{coil}} = \frac{\text{Watts}(\text{inrush})}{I^2(\text{inrush})} = \frac{46.0}{(1.135)^2} = 35.7 \Omega$$




$$X_L = \sqrt{Z^2 - R^2} = \sqrt{(105.73)^2 - (35.7)^2} = 99.51 \Omega$$

$$L = \frac{X_L}{2\pi f} = \frac{99.51}{2\pi(60)} = 0.264 \text{ H}$$

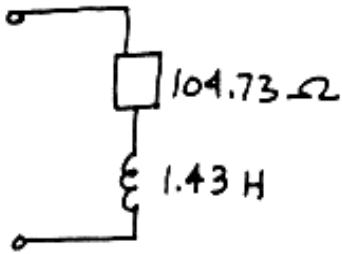2) Seal conditions :  $Z_{\text{coil}} = \frac{\text{Seal VA}}{(\text{Seal I})^2} = \frac{26.22}{(0.2185)^2} = 549.2 \Omega$

$$R_{\text{coil}} = \frac{\text{Seal watts}}{(\text{Seal I})^2} = \frac{5.0}{(0.2185)^2} = 104.73 \Omega$$



$$X_L = \sqrt{(549.2)^2 - (104.73)^2} = 539.12\Omega$$

$$L = \frac{539.12}{2\pi 60} = 1.43\text{H}$$

**P 11.5-10**

$R_s$  = Source resistance =  $3\Omega$

$P_L$  = Lamp power consumption

$R_L$  = Lamp equivalent resistance

$\zeta$  = Power transfer efficiency

$P_T$  = Total power consumption

$$P_T = \left( \frac{V_s}{R_L + R_s} \right)^2 (R_L + R_s) = \frac{v_s^2}{R_L + R_s}, \quad P_L = \left( \frac{v_s}{R_L + R_s} \right)^2 \cdot R_L$$

$$\zeta = \frac{P_L}{P_T} = \frac{R_L}{R_L + R_s}$$

$$\text{For incandescent : } P_T = \frac{120^2}{192 + 3} = 73.85 \text{ W ; } P_L = \left( \frac{120}{195} \right)^2 (192) = 72.71 \text{ W}$$

$$\zeta = \frac{72.71}{73.85} = 0.98$$

$$\text{For compact fluorescent: } P_T = \frac{(120)^2}{800 + 3} = 17.93 \text{ W ; } P_L = \frac{(120)^2}{(803)^2} \cdot 800 = 17.87 \text{ W}$$

$$\zeta = \frac{17.87}{17.97} = 0.99$$

Although less power is delivered to the fluorescent lamp, it has higher illumination and power transfer efficiency.

**Section 11.6: Power Factor**

**P11.6-1**

For heating :  $P_{AV} = 30\text{kW}$

For motor :  $\theta = \cos^{-1}(.6) = 53.1^\circ$ ,  $VI_{\text{rms}} = 150 \text{ kVA}$

$$\Rightarrow P_{AV} = 150 \cos 53.1^\circ = 90\text{kW}$$

$$Q = 150 \sin 53.1^\circ = 120\text{kVAR}$$

$$\therefore \text{ total } P_{av} = 30 + 90 = 120 \text{ kW}$$

so for the plant:  $P_{AV} = 120 \text{ kW}$

$$Q = 0 + 120 = 120 \text{ kVAR}$$

$$\Rightarrow S = 120 + j120 = 170 \angle 45^\circ$$

$$\therefore \text{ pf} = \cos 45^\circ = .707$$

$$\text{Then the current in the plant is } I = \frac{(VI)}{4\text{kV}} = \frac{170\text{kVA}}{4\text{kV}} = 42.5\text{A}$$

**P 11.6-2**

Load 1:  $P_1 = VI \cos\theta = (12\text{kVA})(.7) = 8.4\text{kW}$

$Q_1 = VI \sin(\cos^{-1}(.7)) = 12\sin(45.6^\circ) = 8.57\text{kVAR}$


Load 2:  $P_2 = (10\text{kVA})(.8) = 8\text{kW}$

$Q_2 = 10\sin(\cos^{-1}(.8)) = 10\sin(36.9^\circ) = 6.0\text{kVAR}$

$\therefore$  Total:  $S_T = P_T + jQ_T = 8.4 + 8 + j(8.57 + 6.0)$   
 $= 16.4 + j14.57 = 21.9\angle 41.6^\circ$

So  $\text{pf}_T = \cos(41.6^\circ) = .75$ ,  $P_{TAV} = 8.4\text{kW}$ , and  
 $VI_T = 21.9\text{kVA}$

**P11.6-3**

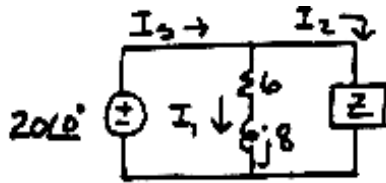

$$S = \frac{1}{2} V_s I_s^* \Rightarrow I_s^* = \frac{2S}{V_s}$$

$$= \frac{2(50\angle \cos^{-1} 0.8)}{20\angle 0^\circ}$$

$$= 5\angle 36.9^\circ$$


$$\therefore I_s = 5\angle -36.9^\circ = 4 - j3 \text{ A}$$

Now  $I_1 = \frac{V_s}{6 + j8} = \frac{20\angle 0^\circ}{10\angle 53.1^\circ} = 2\angle -53.1^\circ = 1.2 - j1.6$

$I_2 = I_s - I_1 = 4 - j3 - 1.2 + j1.6 = 2.8 - j1.4 = 3.13\angle -26.6^\circ$

$\therefore Z = \frac{V_s}{I_2} = \frac{20\angle 0^\circ}{3.13\angle -26.6^\circ} = \underline{6.39\angle 26.6^\circ \Omega}$

**P11.6-4**

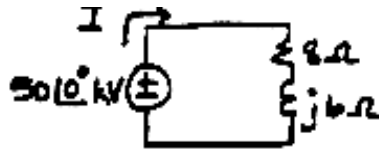

$f = 60 \text{ Hz}$

$I = \frac{50\angle 0^\circ}{8 + j6} = 5\angle -36.9^\circ \text{ kA}$

(a)  $P_{\text{complex}} = S = 2VI^* = 2(50\angle 0^\circ)(5\angle 36.9^\circ) = \underline{500\angle 36.9^\circ \text{ MVA}}$

(b) Power factor =  $\text{pf} = \cos(36.9^\circ) = \underline{.8 \text{ lagging}}$

(c) Using Equation 11-25

$$X = \frac{8^2 + 6^2}{-8 \tan(\cos^{-1}(.95)) - 6} = -11.588$$

**P 11.6-5** Using all rms values

$$(a) \quad P = |I|^2 R = \frac{|V|^2}{R} \Rightarrow |V|^2 = P \cdot R = (500)(20)$$

$$|V| = 100 \text{ V}$$


$$\therefore \underline{V_{\text{rms}} = 100 \angle 0^\circ \text{ V}}$$

$$(b) \quad I_s = I + I_L = \text{where } I = \frac{V}{20} = \frac{100 \angle 0^\circ}{20} = 5 \text{ A}$$

$$I_L = \frac{V}{j20} = \frac{100 \angle 0^\circ}{20 \angle 90^\circ} = -j 5 \text{ A}$$

$$\therefore \underline{I_s = 5 - j5 = 5\sqrt{2} \angle -45^\circ \text{ A}}$$

(c)

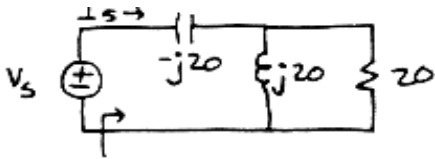

$$Z_s = -j20 + \frac{(20)(j20)}{20 + j20} = 10\sqrt{2} \angle -45^\circ \Omega$$

$$\therefore \underline{\text{circuit power factor} = \cos(-45^\circ) = \frac{1}{\sqrt{2}} \text{ leading}}$$

(d) Because no average power gets dissipated in the capacitor or inductor, then

$$P_{\text{AVE source}} = P_{\text{AVE } 20\Omega} = 500 \text{ W}$$

$$\Rightarrow |V_s| |I_s| \cos \theta = 500 \text{ W}$$

$$\Rightarrow |V_s| = \frac{500}{|I_s| \cos \theta} = \frac{500}{(5\sqrt{2}) \left(\frac{1}{\sqrt{2}}\right)} = \underline{100 \text{ V}}$$

**P11.6-6**

$$V = 100 \angle 160^\circ \text{ V}$$

$$I = 2 \angle 190^\circ \text{ A} = -1.97 - j0.348$$

$$P_1 = 23.2 \text{ W}, Q_1 = 50 \text{ VARs}$$

$$\underline{S}_1 = P_1 + jQ_1 = 23.2 + j50 = 55.12 \angle 65.1^\circ \text{ VA}$$

$$\text{pf}_1 = \cos 65.1^\circ = .422 \text{ lag}$$

$$\text{Now } \underline{I}_1^* = \frac{\underline{S}_1}{V_s} = \frac{55.12 \angle 65.1^\circ}{100 \angle 160^\circ} = 0.551 \angle -94.9^\circ, \text{ so } I_1 = 0.551 \angle 94.9^\circ$$

$$I_2 = I - I_1 = -1.97 - j0.348 + 0.047 - j0.549 = 2.12 \angle -155^\circ \text{ A}$$

$$\underline{S}_2 = VI_2^* = (100 \angle 160^\circ)(2.12 \angle 155^\circ) = 212 \angle -45^\circ = 150 - j150$$

$$\text{pf}_2 = \cos(-45^\circ) = .707 \text{ leading}$$

$$\underline{S} = \underline{S}_1 + \underline{S}_2 = (23.2 + j50) + (150 - j150) = 173.2 - j100 = 200 \angle -30^\circ$$

$$\text{So total pf} = \cos(-30^\circ) = \underline{.866 \text{ leading}}$$

**P11.6-7**


$$\underline{S} = P + jQ, I = 1, V = \sqrt{2}(120), \cos\theta = .6$$

$$(a) P = \frac{1}{2} VI \cos\theta = \frac{1}{2} (120) (1) \sqrt{2} (.6) = 50.9 \text{ W}$$

$$Q = \frac{P \sin\theta}{\cos\theta} = 67.8 \text{ VAR} \quad \sin\theta = .8$$

$$\text{so } \theta = 53.1^\circ$$

$$\underline{S} = 50.9 + j67.8$$

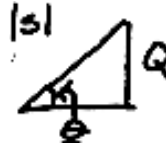


(b) With  $Z = R + j67.8$

$$P = \frac{I^2 R}{2} \text{ or } R = \frac{2P}{I^2} = \frac{2(50.9)}{1^2} = 101.8 \Omega$$

$$Q = \frac{1}{2} \omega L I^2 \text{ or } L = \frac{2Q}{\omega I^2} = \frac{2(67.8)}{377(1^2)} = 0.36 \text{ H}$$

**P11.6-8**

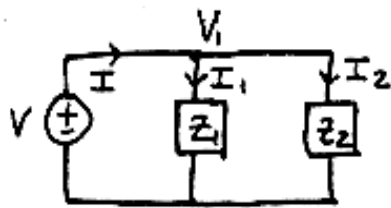

$$P_1 = V_1 I_1 \cos\theta_1 = 4800(.85) = 4080 \text{ W}$$

$$\therefore P_T = P_1 + P_2 = 4080 + 4000 = 8.08 \text{ kW}$$

$$Q_1 = V_1 I_1 \sin\theta_1 = 4800 \sin 31.8^\circ = 2529 \text{ VAR}$$

$$Q = VI \sin(\cos^{-1}.75) = 8080 \sin 41.4^\circ = 5343 \text{ VAR}$$

$$\text{So } Q_2 = Q - Q_1 = 5343 - 2529 = 2814 \text{ VAR}$$

$$\text{Now } P_2 = V_2 I_2 \cos\theta_2, Q_2 = V_2 I_2 \sin\theta_2$$


$$\therefore \frac{Q_2}{P_2} = \tan\theta_2 = \frac{2814}{4000} = 0.704 \Rightarrow \theta_2 = 35.1^\circ$$

$$\text{Apparent power load 2} = V_2 I_2 = \frac{P_2}{\cos\theta_2} = \frac{4000}{0.82} = 4878 \text{ W}$$

$$\text{Power factor} = \cos\theta_2 = 0.82$$



P 11.6-9

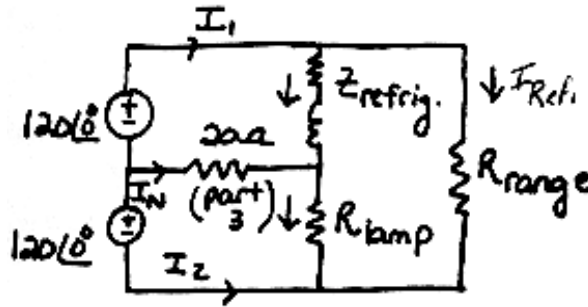

$$|Z_{\text{refrig}}| = \frac{120\text{V}}{8.5\text{A}} = 14.12\Omega$$

$$Z_{\text{refrig}} = 14.12\angle 45^\circ = 10 + j10\Omega$$

$$R_{\text{lamp}} = \frac{V^2}{P} = \frac{(120)^2}{100} = 144\Omega$$

$$R_{\text{range}} = \frac{(240)^2}{12,000} = 4.8\Omega$$

1) Now  $I_{\text{refrig}} = \frac{120\angle 0^\circ}{10 + j10} = 8.5\angle -45^\circ \text{ A}$ ,  $I_{\text{lamp}} = \frac{120\angle 0^\circ}{144} = 0.83\angle 0^\circ \text{ A}$

$$I_{\text{range}} = \frac{240\angle 0^\circ}{4.8} = 50\angle 0^\circ \text{ A}$$

From KCL:  $I_1 = I_{\text{refrig}} + I_{\text{range}} = 56 - j6 = 56.3\angle -6.1^\circ \text{ A}$

$$I_2 = -I_{\text{lamp}} - I_{\text{range}} = 50.83\angle 180^\circ \text{ A}$$

$$I_N = -I_1 - I_2 = 7.92\angle -49^\circ \text{ A}$$

2)  $P_{\text{refrig}} = I_{\text{refrig}}^2 R_{\text{refrig}} = 722.5\text{W}$

$$Q_{\text{refrig}} = I_{\text{refrig}}^2 X_{\text{refrig}} = 722.5 \text{ VAR}$$

Now  $|S| = |V||I| = (120)(8.5) = 1020 \text{ VA}$

$$S = 1020\angle 45^\circ = 722 + j722 \text{ VA}$$

$$P_{\text{lamp}} = 100\text{W}, Q_{\text{lamp}} = 0$$

$$P_{\text{TOT}} = 722 + 100 + 12,000 = 12.82\text{kW}$$

$$Q_{\text{TOT}} = 722 + 0 + 0 = 722 \text{ VAR}$$

$$\Rightarrow S = 12,822 + j722 = 12.84\text{kVAR}\angle 3.2^\circ$$

$$\text{pf} = \cos(3.2^\circ) = 0.998$$

Continued

3) Mesh equations: 
$$\begin{bmatrix} 30 + j10 & -20 & -10 - j10 \\ -20 & 164 & -144 \\ -10 - j10 & -144 & 158.8 + j10 \end{bmatrix} \begin{bmatrix} I_A \\ I_B \\ I_C \end{bmatrix} = \begin{bmatrix} 120\angle 0^\circ \\ 120\angle 0^\circ \\ 0 \end{bmatrix}$$

yields  $I_A = 54.3\angle -1.7^\circ \text{ A}$

$$I_B = 51.3\angle -0.2^\circ \text{ A}$$

$$I_C = 50.0\angle 0^\circ \text{ A}$$

Thus  $|V_{\text{lamp}}| = R_{\text{lamp}} |I_B - I_C| = 144 |1.27\angle -8.6^\circ| = 183.2\text{V}$

Lamp will not last very long!

**P 11.6-10**

a)  $VI = 220(7.6) = \underline{1672 \text{ VA}}$

$$\text{pf} = \frac{P}{VI} = \frac{1317}{1672} = .788$$

$$\theta = \cos^{-1}\text{pf} = 38.0^\circ \Rightarrow \underline{Q = VI\sin\theta = 1030\text{VAR}}$$

b) To restore the pf to 1.0, a capacitor is required to eliminate Q by introducing -Q, then

$$1030 = \frac{V^2}{X_c} = \frac{(220)^2}{X_c} \Rightarrow X_c = 47\Omega$$

$$\therefore \underline{C = \frac{1}{\omega X} = \frac{1}{(377)(47)} = 56.5\mu\text{F}}$$

c)  $P = VI \cos\theta$  where  $\theta = 0^\circ$

then  $1317 = 220I$

$\therefore \underline{I = 6.0\text{A}}$  for corrected pf


\*Note  $I = 7.6\text{A}$  for uncorrected pf

**P11.6-11**

First load:  $S_1 = P + jQ = P(1 + j \tan(\cos^{-1}(.6))) = 500(1 + j \tan 53.1^\circ) = 500 + j677\text{kVA}$

Second load:  $S_2 = 400 + j600\text{kVA}$

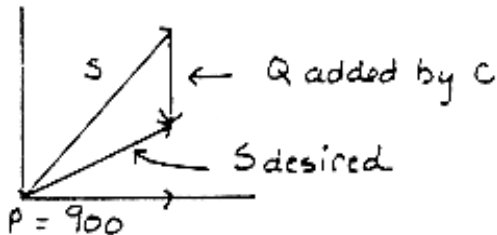$\therefore S = S_1 + S_2 = 900 + j1277\text{kVA}$



$$S_{\text{desired}} = P + jP \tan(\cos^{-1}(.90)) = 900 + j436$$

From vector diagram  $S_{\text{desired}} = S + Q$

$\therefore 900 + j436 = 900 + j1277 + Q \Rightarrow Q = -j841 \text{ VAR}$

So  $\frac{|V|^2}{Z^*} = -j841 \Rightarrow Z^* = \frac{|V|^2}{-j841} = \frac{(1000)^2}{-j841} = j1189$

$\therefore Z = -j1189 = -j/(377)\text{C}$

So  $\underline{C = 1/(1189)(377) = 2.20\mu\text{F}}$

**P11.6-12**

(a)  $S = P + jQ = P + jP \tan(\cos^{-1} \text{pf}) = 1000 + j1000 \tan(\cos^{-1} .8) = 1000 + j750$

Let  $V_L = 100 \angle 0^\circ$  rms

Then  $I^* = S/V_L = \frac{1000 + j750}{100 \angle 0^\circ} = 10 + j7.5$

so  $I = 10 - j7.5$

$\therefore Z_L = \frac{V_L}{I} = \frac{100 \angle 0^\circ}{12.5 \angle -36.9^\circ} = 8 \angle 36.9^\circ = 6.4 + j4.8$

$\Rightarrow V = [6.4 + j(200)(.024) + Z_L](I) = \underline{(12.8 + j9.6)(10 - j7.5) = 200 \angle 0^\circ \text{ V}}$

(b) Need  $Z_L^* = Z_L \parallel Z_{\text{new}} = \frac{1}{Y_L + Y_{\text{new}}}$

$\frac{1}{(6.4 - j4.8)} = Y_L + Y_{\text{new}}$

$\Rightarrow Y_{\text{new}} = \frac{1}{6.4 - j4.8} - \frac{1}{6.4 + j4.8} = j.15$

So  $Z_{\text{new}} = -j6.67 \Omega$

$\therefore$  need capacitor  $\frac{1}{\omega C} = 6.67 \Rightarrow C = \frac{1}{(6.67)(200)} = \underline{0.075 \mu\text{F}}$

**P11.6-13**

$S = P + jQ$  and  $|S| = \frac{P}{\text{pf}} = \frac{100}{.8} = 125 \text{ kVA}$

So  $Q = |S| \sin(\cos^{-1}.8) = 125 \sin(36.9^\circ) = 75 \text{ kVAR}$

(a) pf of .95 lagging

$P = 100 \text{ kW}, Q = P \tan(36.9^\circ) = 32.9 \text{ kVAR}$

$\Rightarrow |S| = (P^2 + Q^2)^{1/2} = [(100)^2 + (32.9)^2]^{1/2} = 105.3 \text{ kVA}$

$\therefore$  released capacity = 125 - 105.3 = 19.7 kVA

(b) pf of 1.0

Need  $Q = 0 \Rightarrow |S| = P = 100 \text{ kVA}$

$\therefore$  released = 125 - 100 = 25 kVA

(c) Relative capacity required

Part (a):  $75 - 32.9 = \underline{42.1 \text{ kVAR}}$


Part (b):  $75 - 0 = \underline{75 \text{ kVAR}}$

(d) Corrected pf

	.95	1.0
released capacity	19.7 kVA	25 kVA
required reactive capacity	42.1 kVAR	75 kVAR
ratio	$\sim 1/2$	1/3

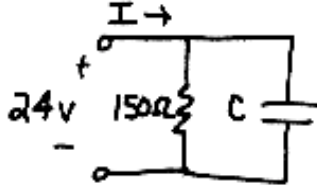**P11.6-14**

$I = 0.2 \text{ A}$   
 $f = 400 \text{ Hz}$   
 $\text{pf} = .8 \text{ leading}$



$$|Y| = \frac{I}{V} = \frac{0.2}{24} = 8.33 \text{ mS}$$

$$\angle\theta_Y = \cos^{-1}(.8) = 36.9^\circ$$

$$\therefore Y = 8.33 \angle 36.9^\circ = 6.67 + j5 \text{ mS}$$


$$\text{so } R = \frac{1}{G} = \frac{1}{6.67 \times 10^{-3}} = 150 \Omega \Rightarrow \text{checks}$$

$$B = \omega C \text{ or } C = \frac{5 \times 10^{-3}}{2\pi(400)} = 1.99 \mu\text{F}$$

**P11.6-15**

This example demonstrates that loads can be specified either by kW or kVA. The procedure is as follows:

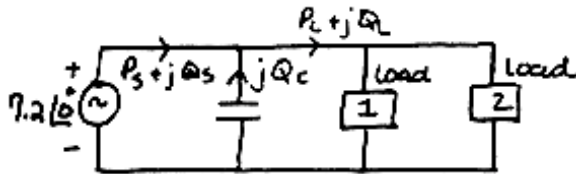- 1) Combine loads and determine the overall  $P_L + jQ_L$
- 2) Given that  $P_S = P_L$ , determine the required  $Q_S$
- 3) Determine  $Q_C = Q_L - Q_S$  (Note: assume  $f = 60 \text{ Hz}$ )
- 4) Determine  $C$  given  $Q_C$  and  $V_c$



$$P_L + jQ_L = (45 + 45) + j(21.8 + 20.5)$$

$$= 90 + j42.3 \text{ kVA}$$

$$\therefore P_S = 90 \text{ kW and } Q_S = \frac{90}{0.97} \sin(\cos^{-1} 0.97)$$

$$= 22.6 \text{ kVAR}$$

$$\text{so } Q_C = 42.3 - 22.6 = 19.7 \text{ kVAR}$$

$$X_C = \frac{|V_c|^2}{Q_C} = \frac{(7.2 \times 10^3)^2}{19.7 \times 10^3} = 2626 \Omega \Rightarrow C = \frac{1}{377(2626)} = 1.01 \mu\text{F}$$

**P11.6-16**

pf	P	Q kVAR	S  (kVA)	I	
.6 lag	48 kW	64	80	160	load 1
.96 load	24 kW	-7	25	50	load 2
	72 kW	57	91.8	184	Total

$$\text{Load 1: } |S_1| = \frac{48 \text{ kW}}{.6} = 80 \text{ kVA}, \quad Q_1 = \sqrt{(80)^2 - (48)^2} = 64 \text{ kVAR}$$

$$|I_1| = \frac{80 \text{ kVA}}{500 \text{ V}} = 160 \text{ A}$$

$$\text{Load 2: } |S_2| = \frac{24 \text{ kVA}}{.96} = 25 \text{ kVA}, \quad Q_2 = -\sqrt{(25)^2 - (24)^2} = -7 \text{ since lead pf}$$

$$|S| = \sqrt{|S_1|^2 + |S_2|^2} = \sqrt{80^2 + 25^2} = 91.8 \text{ kVA}$$

$$|I| = \frac{91.8 \text{ kVA}}{500} = 184 \quad \text{total pf} = \frac{P_{\text{TOT}}}{|S|_{\text{TOT}}} = \frac{72}{91.8} = .784$$


Need correction  $Q_c = -57 \text{ kVA}$

$$C = \frac{-Q_c}{\omega |V|^2} = \frac{57 \times 10^3}{377(500)^2} = 605 \mu\text{F}$$

## Section 11-7: The Power Superposition Principle
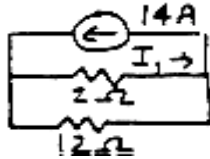
### P11.7-1


Use superposition since we have two different frequency sources.  
First consider dc sources ( $\omega = 0$ )



$$I_1 = 14 \left( \frac{12}{12+2} \right) = 12 \text{ A}$$

$$\therefore P_{1\text{AVE}} = I_1^2 R = (12)^2 (2) = \underline{288 \text{ W}}$$

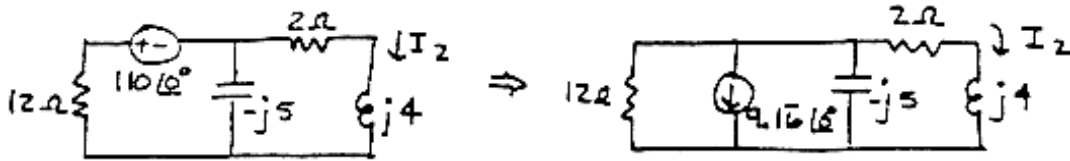Consider  $\omega = 20 \text{ rad/s}$  source




$$\text{Current divider} \Rightarrow I_2 = -9.166 \left[ \frac{\frac{-j60}{(12-j5)}}{\frac{-j60}{(12-j5)} + 2 + j4} \right] = \frac{25}{\sqrt{5}} \angle 116.6^\circ$$

$$\therefore P_{2\text{AVE}} = 1/2 |I_2|^2 (2) = 1/2 (125)(2) = \underline{125 \text{ W}}$$

$$\text{so } P_{\text{AVE}} = P_{1\text{AVE}} + P_{2\text{AVE}} = 288 + 125 = \underline{413 \text{ W}}$$
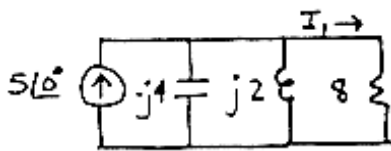
### P11.7-2

Use superposition since we have two different frequency sources  
First consider  $\omega = 2000 \text{ rad/s}$  source




$$\therefore P_{1\text{AVE}} = \frac{1}{2} |I_1|^2 8 = \underline{20 \text{ W}}$$

Using current divider

$$I_1 = 5 \left[ \frac{\frac{8}{-j2}}{\frac{8}{-j2} + 8} \right] = \frac{5}{\sqrt{5}} \angle 63.4^\circ$$

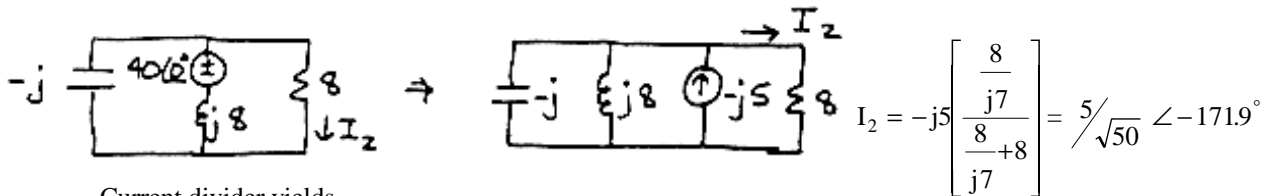Next consider  $\omega = 8000 \text{ rad/s}$  source



Current divider yields


$$\therefore P_{2\text{AVE}} = \frac{1}{2} |I_2|^2 8 = \underline{2 \text{ W}}$$

$$\text{So } P_{\text{AVE}} = P_{1\text{AV}} + P_{2\text{AV}} = \underline{22 \text{ W}}$$

**P11.7-3**

Use superposition

$\omega = 0$

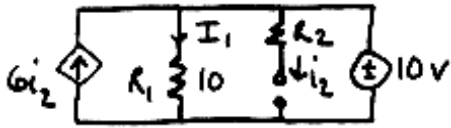


$$I_1 = 10 \left( \frac{1}{10} \right) = 1 \text{ A} \quad i_2(t) = 0$$

$$\therefore P_{R_1 \text{ AVE}} = I_1^2 R_1 = 1^2 (10) = 10 \text{ W}$$

$$P_{R_2 \text{ AV}} = 0 \text{ W}$$

$\omega = 5$

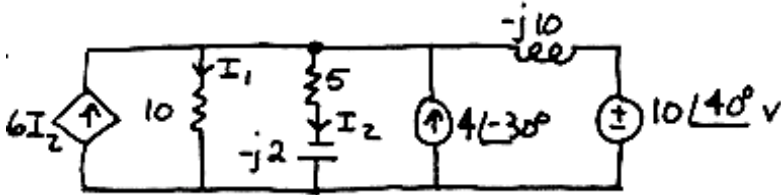

KCL at top node ( $V_a = 10 I_1$ )

$$-6I_2 + I_1 + I_2 - 4 \angle -30^\circ + \frac{(10I_1 - 10 \angle 40^\circ)}{j10} = 0 \quad (1)$$

$$\text{KVL } -10I_1 + (5 - j2)I_2 = 0 \quad (2)$$

Solving (1) and (2) yields  $I_1 = -0.56 \angle -64.3^\circ \text{ A}$

$$I_2 = -1.04 \angle -42.5^\circ \text{ A}$$

$$\text{So } P_{R_1 \text{ AV}} = \frac{1}{2} I_{1m}^2 R_1 = \frac{1}{2} (.56)^2 (10) = 1.57 \text{ W}$$

$$P_{R_2 \text{ AV}} = \frac{1}{2} I_{2m}^2 R_2 = \frac{1}{2} (1.04)^2 (5) = 2.7 \text{ W}$$


$$\therefore P_{R_1 \text{ TOT}} = 10 \text{ W} + 1.57 \text{ W} = \underline{11.57 \text{ W}}$$

$$P_{R_2 \text{ TOT}} = 0 + 2.7 \text{ W} = \underline{2.7 \text{ W}}$$

**P11.7-4**

Use superposition

$\omega = 10$

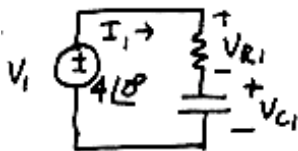


$$I_1 = \frac{V_1}{Z} = \frac{4 \angle 0^\circ}{2 - j5} = 0.28 + j0.7 \text{ A}$$

$$V_{R_1} = 2I_1 = 2(.28 + j.7) = .56 + j1.4 = 1.51 \angle 68.2^\circ$$

$$V_{C_1} = -j5I_1 = 3.77 \angle -21.8^\circ \text{ V}$$

$\omega = 5$

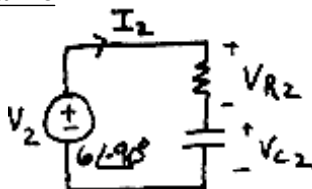

$$I_2 = \frac{V_2}{Z} = \frac{6 \angle -90^\circ}{2 - j10} = .577 - j0.12 \text{ A}$$

$$V_{R_2} = 2I_2 = 2(.577 - j0.12) = 1.15 - j0.24$$

$$= 1.17 \angle -11.8^\circ \text{ V}$$

$$V_{C_2} = -j10I_2 = 5.9 \angle 258.3^\circ \text{ V}$$

$$\text{So } V_R(t) = 1.51 \cos(10t + 68.2^\circ) + 1.17 \cos(5t - 11.8^\circ) \text{ V}$$

$$V_C(t) = 3.77 \cos(10t - 21.8^\circ) + 5.9 \cos(5t - 258.3^\circ) \text{ V}$$

$$\text{so } V_{\text{Reff}}^2 = \left(\frac{1.51}{\sqrt{2}}\right)^2 + \left(\frac{1.17}{\sqrt{2}}\right)^2 = 1.82 \Rightarrow \underline{V_{\text{Reff}} = 1.35 \text{ V}}$$

$$V_{\text{Ceff}}^2 = \left(\frac{3.77}{\sqrt{2}}\right)^2 + \left(\frac{5.9}{\sqrt{2}}\right)^2 = 24.52 \Rightarrow \underline{V_{\text{Ceff}} = 4.95 \text{ V}}$$

### Section 11-8: Maximum Power Transfer Theorem

#### P11.8-1

$$Z_t = 4000 \parallel -j2000 = 800 - j1600$$

$$Z_L = Z_t^* = 800 + j1600$$

$$R + j1000L = 800 + j1600 \Rightarrow \begin{cases} R = 800 \Omega \\ L = 1.6 \text{ H} \end{cases}$$

#### P11.8-2

$$Z_t = 25,000 \parallel -j50,000 = 20,000 - j10,000$$

$$Z_L = Z_t^* = 20,000 + j10,000$$

$$R + j\omega L = 20,000 + j10,000 \Rightarrow \begin{cases} R = 20 \text{ k}\Omega \\ 100L = 10,000 \\ L = 100 \text{ H} \end{cases}$$

The choices yield  $|I| = 1.4 \text{ mA}$  and

$$P = \left(\frac{0.14 \times 10^{-2}}{\sqrt{2}}\right)^2 (20\text{k}) = 19.5 \text{ mW}$$

Since the maximum power is  $> 12 \text{ mW}$ , then yes, we can deliver  $12 \text{ mW}$  to the load.

#### P11.8-3

$$Z_t = 800 + j1600$$

$$Z_L = \frac{R \left(\frac{-j}{\omega C}\right)}{R - \frac{j}{\omega C}} = \frac{R - j\omega R^2 C}{1 + (\omega RC)^2} = Z_t^* = 800 - j1600$$

Equating the real parts gives

$$800 = \frac{R}{1 + (\omega RC)^2} = \frac{4000}{1 + [(5000)(4000)C]^2}$$

$$\Rightarrow C = 0.1 \mu\text{F}$$

**P 11.8-4**

$$Z_t = 400 + j800$$

$$Z_L = 2000 \parallel -j1000 = 400 - j800$$

Since  $Z_L = Z_t^*$  the average power delivered to the load is maximum and cannot be increased by adjusting the value of the capacitance.

The voltage across the 2000Ω resistor is

$$V_R = 5 \frac{Z_L}{Z_t + Z_L} = 2.5 - j5 = 5.59e^{-j63.4}$$


So  $P = \left(\frac{5.59}{\sqrt{2}}\right)^2 \frac{1}{2000} = \underline{7.8 \text{ mW}}$  is the average power delivered to the 2000Ω resistor.

**P11.8-5**

Notice that  $Z_t$ , not  $Z_L$ , is being adjusted. When  $Z_t$  is fixed, then the average power delivered to the load is maximized by choosing  $Z_L = Z_t^*$ . In contrast, when  $Z_L$  is fixed, then the average power delivered to the load is maximized by minimizing the real part of  $Z_t$ . In this case, choose  $R = 0$ . Since no average power is dissipated by capacitors or inductors, all of the average power provided by source is delivered to the load.


**P 11.8-6**

Find  $Z_T$  (open current source)

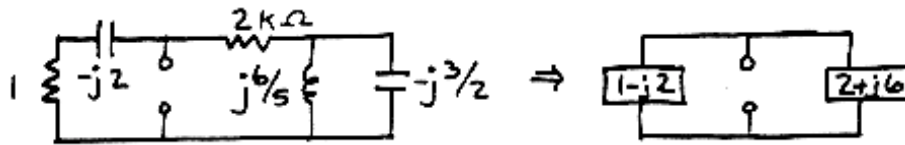

$$\therefore Z_T = \frac{(1-j2)(2+j6)}{1-j2+2+j6} = \underline{2\sqrt{2} \angle -44.9^\circ \text{ k}\Omega}$$


Find  $V_{oc}$

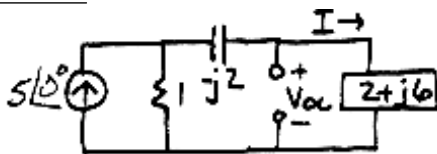

Current divider  $\Rightarrow I = 5 \left[ \frac{1}{1+2+j4} \right] = 1 \angle -53.1^\circ \text{ mA}$

$$\Rightarrow V_{oc} = (2+j6)(I) = \sqrt{40} \angle 71.6^\circ (1 \angle -53.1^\circ) = \underline{2\sqrt{10} \angle 18.5^\circ \text{ V}}$$

$\therefore$  have

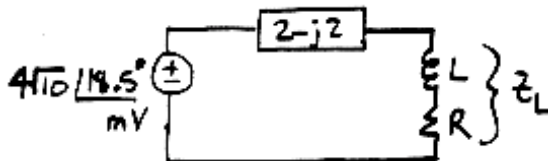

For maximum power transfer  $Z_L = Z_T^*$


$$\Rightarrow R + j2 \times 10^6 L = 2 + j2 \text{ k}\Omega$$

$$\Rightarrow R = 2 \text{ k}\Omega \text{ and } L = 1 \text{ mH}$$

$$\text{Now } P_{Lmax} = \frac{1}{2} \frac{\left| \frac{V_{oc}}{2} \right|^2}{\text{Re}(Z_L)} = \frac{1}{2} \frac{(1\sqrt{10})^2}{2 \text{ k}\Omega} = \underline{2.5 \text{ mW}}$$



P11.8-7

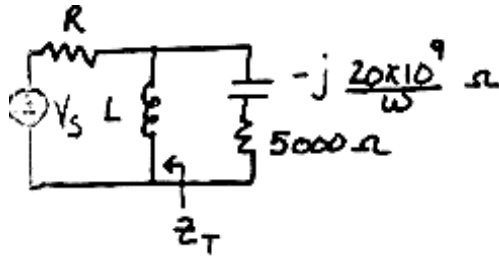

Here  $\omega = 4 \times 10^6 \text{ s}^{-1}$ ,  $V_s = 10 \angle 0^\circ$

$$Z_T = \frac{(R)(j\omega L)}{R + j\omega L} = \frac{(R - j\omega L)(R)(j\omega L)}{R^2 + (\omega L)^2}$$

$$= \frac{(\omega L)^2 R}{R^2 + (\omega L)^2} + \frac{\omega L R^2}{R^2 + (\omega L)^2}$$

$$\& Z_L = 5000 - j \frac{20 \times 10^9}{\omega}$$

So equating  $Z_L = Z_T^*$  yields:

$$5000 = \frac{(\omega L)^2 R}{R^2 + (\omega L)^2} \quad (1) \quad \& \quad \frac{20 \times 10^9}{\omega} = \frac{\omega L R^2}{R^2 + (\omega L)^2} \quad (2)$$


Dividing (2) by (1) yields:  $\frac{R}{L} = 4 \times 10^6$

$$\text{From (2) we can write } L = \frac{\left[ \left( \frac{R}{L} \right)^2 + \omega^2 \right] 20 \times 10^9}{\omega^2 \left( \frac{R}{L} \right)^2}$$


$$L = \frac{\left[ 16 \times 10^{12} + 16 \times 10^{12} \right] 20 \times 10^9}{(16 \times 10^{12})(16 \times 10^{12})} = 2.5 \times 10^{-3} \text{ H} = \underline{2.5 \text{ mH}}$$

$$\therefore R = 4 \times 10^6 L = \underline{10 \text{ k}\Omega}$$

Thévenin Equivalent

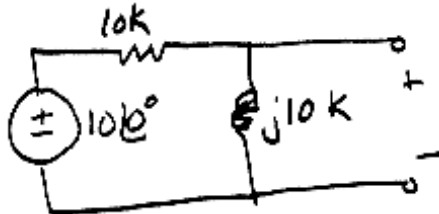

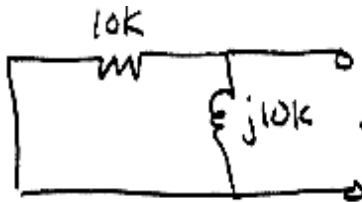
$$V_{oc} = \left( \frac{j10 \text{ k}\Omega}{10 \text{ k}\Omega + j10 \text{ k}\Omega} \right) 10 \angle 0^\circ = 7.07 \angle 45^\circ \text{ V}$$



$$Z_{TH} = \frac{(10 \text{ k}\Omega)(j10 \text{ k}\Omega)}{10 + j10 \text{ k}\Omega} = 7070 \angle 45^\circ$$

$$= 5000 + j5000 \Omega$$


So we have

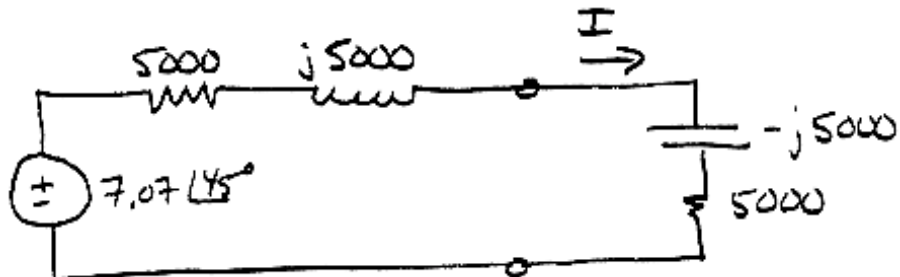

$$I = \frac{7.07 \angle 45^\circ}{(5 + j5 - j5 + 5) \text{ k}\Omega} = 0.7 \angle 45^\circ \text{ mA}$$

$$P = I^2 R = (0.7)^2 (5000) = \underline{2.5 \text{ mW}}$$

P11.8-8

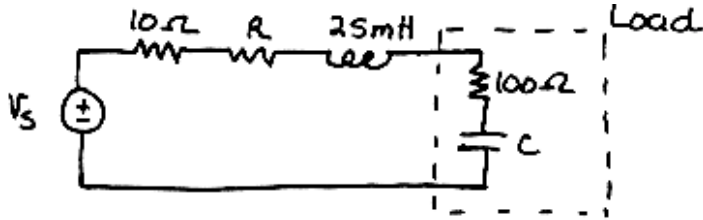


For maximum power transfer, set  $R = \text{zero}$ , then set  $X_L = X_{TH}^*$

$$\Rightarrow 1/\omega C = \omega L \text{ or } C = \frac{1}{\omega^2 L} = \frac{1}{(10^3)^2 (.025)} = 40 \mu\text{F}$$

$$P_{L\text{max}} = 1/2 I^2 (100) = 1/2 \left( \frac{100}{10+100} \right)^2 (100) = \underline{41.3 \text{ W}}$$

P11.8-9


Lefthand circuit

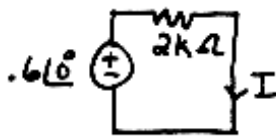

$$I = \frac{.6}{2 \text{ k}\Omega} = .3 \text{ mA}$$

$$50I = 15 \text{ mA}, V_1 = 150 \text{ V}$$

Right-side equivalent circuit

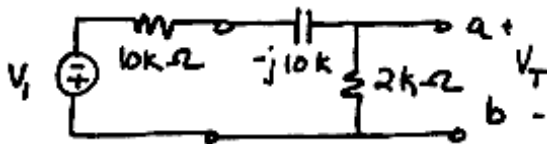

$$V_T = \frac{2000(150)}{12,000 - j10,000} = 19.2 \angle 39.8^\circ \text{ V}$$


To get  $Z_T = 0$  set  $V_s = 0$  then  $I = 0$

$$Z_T = \frac{2 \text{ k}\Omega (10 \text{ k}\Omega - j10 \text{ k}\Omega)}{2 \text{ k}\Omega + 10 \text{ k}\Omega - j10 \text{ k}\Omega} = \frac{2(10 - j10)}{(12 - j10)} \text{ k}\Omega = \underline{1.81 \angle -5.2^\circ \text{ k}\Omega}$$

$$V_{oc} = 19.21 \angle -140^\circ \text{ V} \quad \text{So}$$


$$|I| = \frac{19.21}{2(1805)} = 5.3 \text{ mA}$$

$$\text{and } P_L = \frac{|I|^2}{2} R = \frac{(5.3 \times 10^{-3})^2 (1805)}{2} = \underline{25.6 \text{ mW}}$$

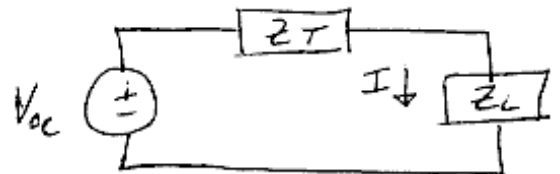

**P11.8-10**

a) Find  $V_{oc}$

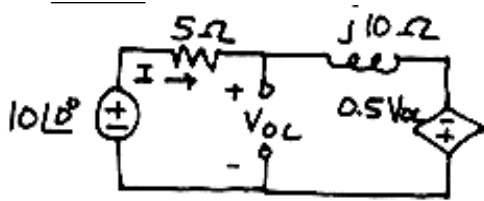


$\omega = 100 \text{ rad/sec}$

KVL:  $-10 + 5I + j10I - 0.5V_{oc} = 0$  (1)

also:  $I = \frac{10 - V_{oc}}{5}$  (2)

Solving (1) & (2) yields  $V_{oc} = 8\angle 36.9^\circ = 6.4 + j4.8 \text{ V}$


Find  $I_{sc}$

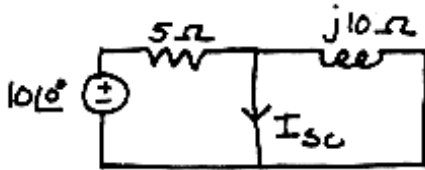

$I_{sc} = \frac{10\angle 0^\circ}{5} = 2\angle 0^\circ \text{ A}$


$\therefore Z_{TH} = \frac{V_{oc}}{I_{sc}} = \underline{3.2 + j2.4\Omega}$

So the Thévenin Equivalent circuit is

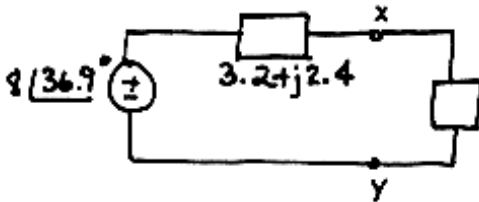

$Z_L = Z_{TH}^* = \underline{3.2 - j2.4\Omega}$  for maximum power transfer

b)

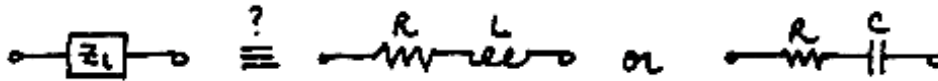


$\Rightarrow$  capacitive load with  $R = 3.2\Omega$  &  $C = \frac{1}{(100)(2.4)} = 4.17\text{mF}$

c)  $P_{L_1, \max} = \frac{|V_{TH}|^2}{8R_L} = \frac{64}{8(3.2)} = \underline{2.5 \text{ W}}$

**Section 11-9: Mutual Inductance**

**P11-9-1**

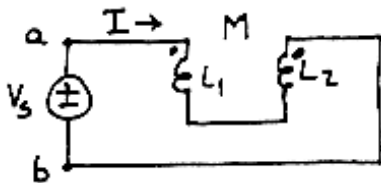


KVL :  $V_s + Ij\omega L_1 + Ij\omega M + Ij\omega L_2 - Ij\omega M = 0$

$\Rightarrow j\omega(L_1 + L_2 - 2M) = \frac{V_s}{I}$

$\therefore \underline{L_{ab} = L_1 + L_2 - 2M}$

P11.9-2

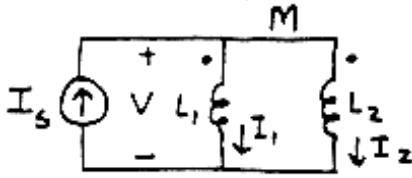

$$\begin{aligned} \text{KCL at top : } I_1 + I_2 &= I_s & (1) \\ \text{also : } V &= I_1 j\omega L_1 + I_2 j\omega M & (2) \\ V &= I_2 j\omega L_2 + I_1 j\omega M & (3) \end{aligned}$$

Solving for  $I_1$  in (1) and plugging into (2) and (3)

$$\Rightarrow I_2 = \frac{V - j\omega L_1 I_s}{j\omega(M - L_1)} \quad (4)$$

$$V = I_2 j\omega L_2 + (I_s - I_2) j\omega M \quad (5)$$


Plugging (4) into (5)

$$V = \frac{(V - j\omega L_1 I_s) [j\omega(L_2 - M)]}{j\omega(M - L_1)} + j\omega M I_s$$

Solving for the ratio  $V/I_s$

$$\begin{aligned} \Rightarrow \frac{V}{I_s} &= j\omega \left[ \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} \right] \\ \therefore L_{ab} &= \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} \end{aligned}$$

P11.9-3

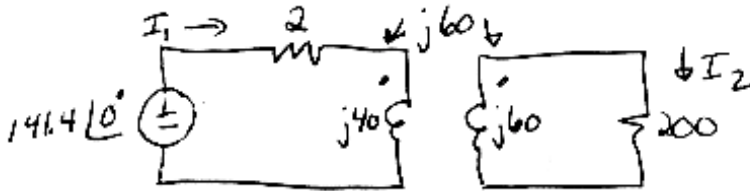

$$\omega = 100 \text{ rad/sec}$$

$$\text{loop 1 : } -141.4\angle 0^\circ + 2I_1 + j40I_1 - j60I_2 = 0 \quad (1)$$

$$\text{loop 2 : } 200 I_2 + j60I_2 - j60I_1 = 0 \Rightarrow I_2 = (0.23\angle 51^\circ) I_1 \quad (2)$$


Plugging this into (1) yields  $I_1 = 4.17\angle -68^\circ \text{ A}$

Plugging this into (2) yields  $I_2 = 0.96\angle -17^\circ \text{ A}$

So  $i_1(t) = 4.2 \cos(100t - 68^\circ) \text{ A}$

and  $i_2(t) = 1.0 \cos(100t - 17^\circ) \text{ A}$

P11.9-4

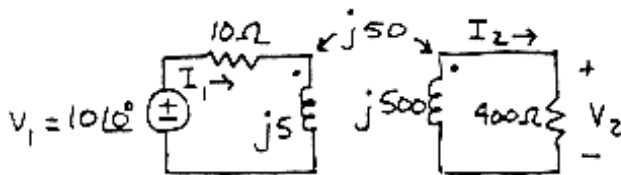

$$\text{KVL } I_1: (10 + j5)I_1 - j50I_2 = 10$$


$$\text{KVL } I_2: -j50I_1 + (400 + j500)I_2 = 1$$

$$\text{Using Cramer's rule, } I_2 = \frac{(10 + j5)(0) - (-j50)(10)}{(10 + j5)(400 + j500) - (-j50)^2} = 0.062 \angle 29.7^\circ$$

$$\therefore \frac{V_2}{V_1} = \frac{400I_2}{10\angle 0^\circ} = 40I_2 = 40(0.062 \angle 29.7^\circ) = 2.5 \angle 29.7^\circ$$

**P11.9-5**

$\omega = 30 \text{ rad/sec}$

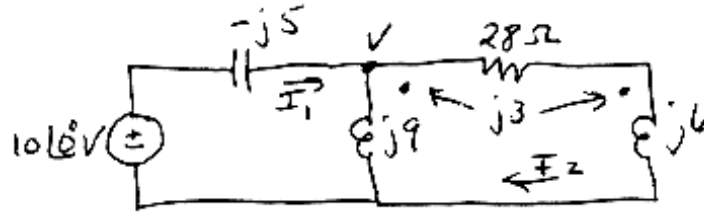

$$\text{loop1: } -10\angle 0^\circ - j5I_1 + j9I_1 + j3I_2 = 0 \quad (1)$$


$$\text{loop2: } 28I_2 + j6I_2 + j3I_1 + j9I_2 - j3I_2 = 0 \quad (2)$$

Solving (1)+(2) yields  $I_1 = 0.25\angle 161^\circ$  and  $I_2 = 2.55\angle -86^\circ$

but  $V = j9(I_1 - I_2)$  where  $I_1 - I_2 = 2.6\angle -81^\circ$ , so  $V = 23\angle 9^\circ$

or  $v(t) = 23 \cos(30t + 9^\circ) \text{ V}$

**P11.9-6**

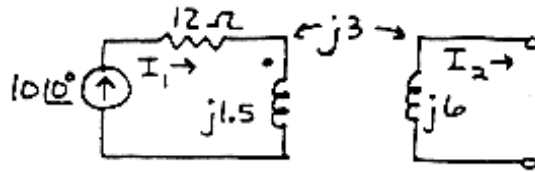

(a) Open - circuit

$$I_2 = 0 \Rightarrow I_1 = 10\angle 0^\circ \Rightarrow i_1(0) = 10 \text{ A}$$

$$\therefore W = \frac{1}{2} L_1 i_1^2(0) = \frac{1}{2} (.3) (10)^2 = 15 \text{ J}$$

(b) Short - circuit

$$\text{KVL right loop: } j6I_2 - j3I_1 = 0 \Rightarrow I_1 = 2I_2$$

$$I_1 = 10\angle 0^\circ \Rightarrow I_2 = 5\angle 0^\circ$$

$$\therefore W = \frac{1}{2} L_1 i_1^2(0) + \frac{1}{2} L_2 i_2^2(0) - M i_1(0) i_2(0)$$

$$W = \frac{1}{2} (.3)(10)^2 + \frac{1}{2} (1.2)(5)^2 - (.6)(10)(5) = 0$$

(c) Connected to  $7\Omega$


$$\text{KVL right loop: } (7 + j6)I_2 - j3I_1 = 0 \Rightarrow I_2 = 3.25\angle 49.4^\circ$$

$$\text{so } i_2(t) = 3.25 \cos(5t + 49.4)$$

$$\Rightarrow i_2(0) = 2.12 \text{ A}$$

$$\therefore W = \frac{1}{2} (.3) (10)^2 + \frac{1}{2} (1.2) (2.12)^2 - (.6) (10) (2.12) = 5.0 \text{ J}$$

P11.9-7

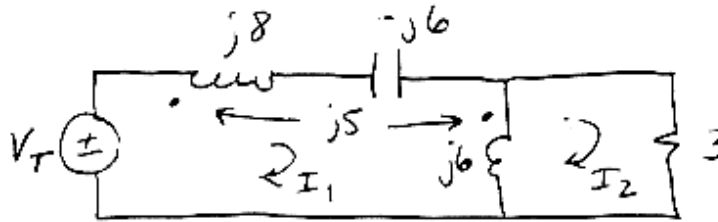

$$-V_T + j8I_1 + j5(I_1 - I_2) - j6I_1 + j6(I_1 - I_2) + j5I_1 = 0 \quad (1)$$

$$3I_2 + j6(I_2 - I_1) - j5I_1 = 0 \quad (2)$$


$$\text{From Eq. (2) : } I_2 = (1.64 \angle 27^\circ) I_1 \quad (3)$$

$$\text{From Eq. (1) : } I_1(j18) + I_2(-j11) = V_T \quad (4)$$

Plugging Eq. (3) into (4) and solving yields

$$Z = \frac{V_T}{I_1} = 8.2 + j^2 = \underline{8.4 \angle 14^\circ \Omega}$$

P11.9-8

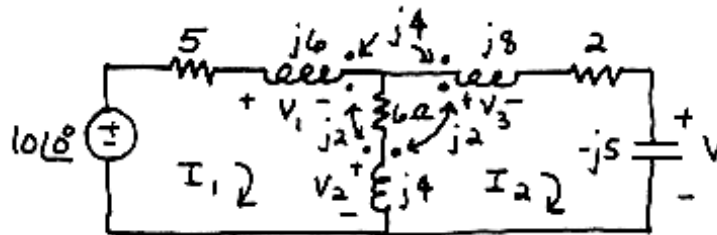

$$3 \text{ coils : } \begin{cases} V_1 = j6I_1 - j2(I_1 - I_2) - j4I_2 = j4I_1 - j2I_2 \\ V_2 = j4(I_1 - I_2) - j2I_1 + j2I_2 = j2I_1 - j2I_2 \\ V_3 = j8I_2 - j4I_1 + j2(I_1 - I_2) = -j2I_1 + j6I_2 \end{cases}$$

$$\text{mesh } I_1 : 5I_1 + V_1 + 6(I_1 - I_2) + V_2 = 10\angle 0^\circ$$

$$\text{mesh } I_2 : -V_2 + 6(I_2 - I_1) + 2I_2 + V_3 - j5I_2 = 0$$

Substituting  $V_1, V_2, V_3$  into mesh equations


$$I_2 = \frac{\begin{vmatrix} 11 + j6 & 10 \\ -6 - j4 & 0 \end{vmatrix}}{\begin{vmatrix} 11 + j6 & -6 - j4 \\ -6 - j4 & 8 + j3 \end{vmatrix}} = \frac{60 + j40}{50 + j33} = 1.2 \angle 0.28^\circ$$

$$\text{Now } V = -j5I_2 = 6.0 \angle -89.72^\circ$$

$$\therefore \underline{v(t) = 6 \sin(2t - 89.7^\circ) \text{ V}}$$

Section 11-10: The Ideal Transformer

P11.10-1

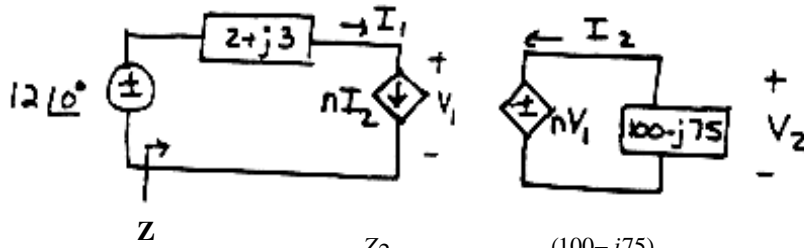

$$Z = Z_s + \frac{Z_2}{n^2} = (2 + j3) + \frac{(100 - j75)}{25} = 6\Omega$$

$$\therefore I_1 = \frac{12\angle 0^\circ}{Z} = \frac{12\angle 0^\circ}{6} = 2\text{ A}$$

$$\Rightarrow V_1 = I_1 \left( \frac{Z_2}{n^2} \right) = (2)(4 - j3) = 10\angle -36.9^\circ \text{ V}$$

$$\text{Now } V_2 = nV_1 = 5(10\angle -36.9^\circ) = \underline{50\angle -36.9^\circ \text{ V}}$$

$$\text{and } I_2 = \frac{I_1}{n} = \frac{2}{5} \text{ A}$$

P11.10-2


(a)  $V_0 = (5 \times 10^{-3} \text{ A})(10,000\Omega) = 50 \text{ V}$

$$\therefore \frac{N_1}{N_2} = \frac{V_1}{V_0} = \frac{10}{50} = \frac{1}{5} \Rightarrow \underline{n = 5}$$

(b)  $R_{ab} = \frac{1}{n^2} R_2 = \frac{1}{25} (10\text{k}\Omega) = \underline{400\Omega}$

(c)  $I_s = \frac{10}{R_{ab}} = \frac{10}{400} = \underline{0.025\text{A} = 25\text{mA}}$

P11.10-3

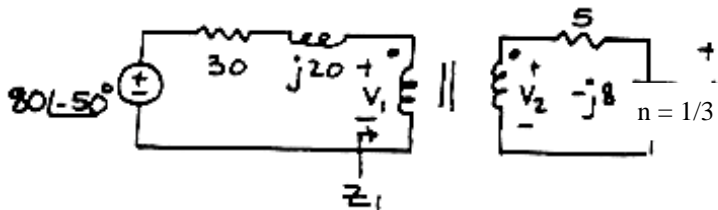

$$Z_1 = \frac{1}{n^2} Z_2 = 9Z_2 = 9(5 - j8) = 45 - j72$$

From voltage division, voltage across  $Z_1$  is:

$$V_1 = 80\angle -50^\circ \left( \frac{45 - j72}{45 - j72 + 30 + j20} \right) = 74.4\angle -73.3^\circ$$

$\therefore$  the voltage across the secondary coil is:

$$V_2 = nV_1 = \frac{74.4}{3} \angle -73.3^\circ = 24.8 \angle -73.3^\circ$$


Then from voltage division again

$$V_c = V_2 \left( \frac{-j8}{5 - j8} \right) = (24.8\angle -73.3^\circ) \left( \frac{8\angle -90^\circ}{\sqrt{89}\angle -58^\circ} \right) = \underline{21.0\angle -105.3^\circ \text{ V}}$$

**P11.10-4**  $n = 5, Z_1 = \frac{200}{(5)^2} = 8 \Rightarrow V_1 = \frac{8}{10}(50) = 40V = 40\angle 0^\circ$   
 now  $V_2 = nV_1 = 200\angle 0^\circ V$

**P11.10-5**

$\omega = 10^5$

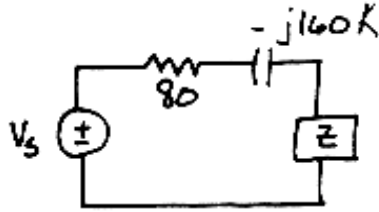

$Z = \frac{320}{n^2} + \frac{j\omega L}{n^2}$


For maximum power transfer, need  $\frac{j\omega L}{n^2} = j160k\Omega$

and  $\frac{320}{n^2} = 80 \therefore \underline{n = 2}$


If  $n = 2$ , then  $\omega L = 640k\Omega$

$L = \frac{640k\Omega}{10^5} = \underline{6.4 H}$

**P11.10-6**

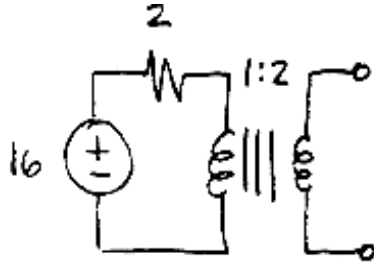

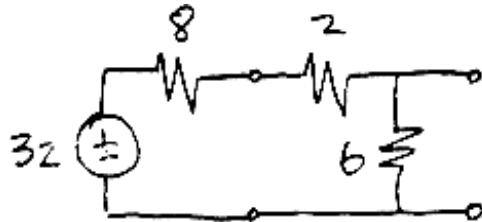$V_{oc} = 32 V$   
 $Z_{Th} = (2)^2 2 = 8\Omega$



$V_{oc} = \frac{6}{6}(32) = 12 V$   
 $Z_{Th} = \frac{16}{6 \parallel 10} = 3.75\Omega$



P11.10-7

$$V_2 = \frac{1}{2}V_1$$


$$I_3 = \frac{V_1 - V_2}{2} = \frac{V_1}{4}$$

$$I_2 = I_3 - \frac{V_2}{6} = \frac{V_1}{6}$$


$$I_1 = -\frac{1}{2}I_2 = -\frac{V_1}{12}$$

$$I_T = I_3 - I_1 = \frac{V_1}{6}$$

$$Z = \frac{V_1}{I_T} = 6$$

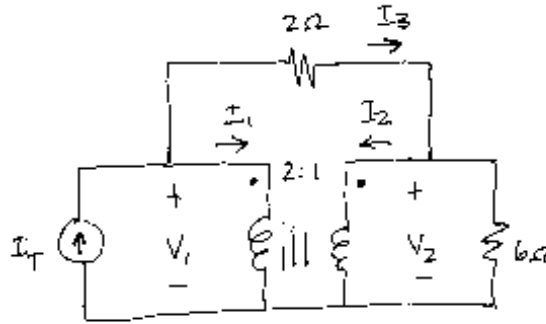

P 11.10-8

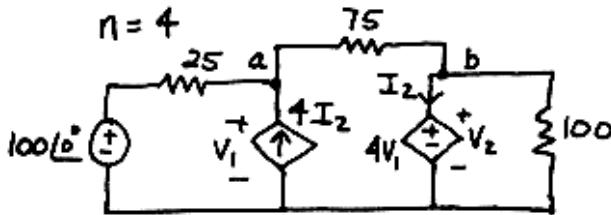

$$I_1 = -4I_2$$

$$V_2 = 4V_1$$

KCL at a:  $\frac{V_a - 200}{25} + \frac{V_a - V_b}{75} - 4I_2 = 0$  (1)

at b:  $\frac{V_b}{100} + \frac{V_b - V_a}{75} + I_2 = 0$  (2)

also  $V_b = 4V_a$  (3)

Solving (1)-(3) yields  $V_a = \frac{25}{2}V$ ,  $V_b = 4V_a = 50V$


P11.10-9

Maximum Power requires  $X_{Th} = X_L^*$

$$X_{Cl} \left( \frac{1}{n_2^2} \right) = X_{L1}, \quad \frac{1}{n_2^2} = \frac{2}{10} = \frac{1}{5} \Rightarrow n_2 = \sqrt{5}$$

$$\text{Now } \left[ R_L \left( \frac{1}{n_2^2} \right) + 1\Omega \right] \left( \frac{1}{n_1^2} \right) = 100\Omega \Rightarrow \frac{1}{n_1^2} = \frac{100}{3} \text{ or } n_1 = \frac{\sqrt{3}}{10}$$

P11.10-10

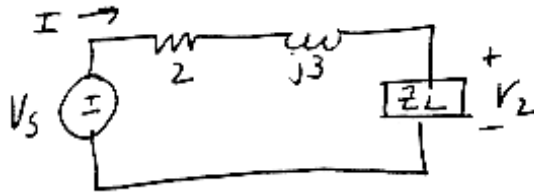


$$Z_L = \frac{20(1+j7.54)}{20+10+j7.54} = 8.1\angle 23^\circ \Omega$$

$$Z_L^{-1} = \frac{Z_L}{n^2} = \frac{8.1\angle 23^\circ}{25} = 0.3 + j0.13 \Omega$$

$$P_L = \frac{|V_L|^2}{2R_2} = \frac{|V_2|^2}{2R_L} = \frac{(230)^2}{2(0.3)} = 88 \text{ kW for 1 home} \quad \therefore \underline{529 \text{ kW for six homes}}$$

P11.10-11

Phasor circuit finding  $V_{oc}$  first

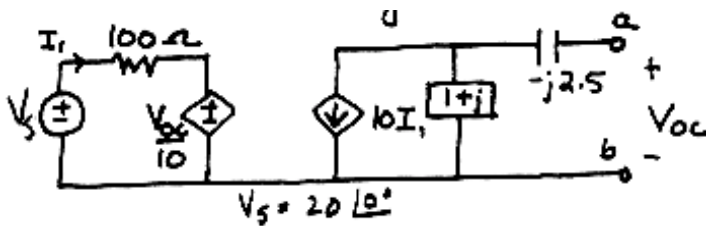


$$\text{KVL: } 100I_1 + 0.1V_{oc} = 20\angle 0^\circ \quad (1)$$

$$\text{KCL: } 10I_1 + \frac{V_{oc}}{1+j} = 0 \quad (2)$$

above yields  $\underline{V_{oc} = -2.86\angle 45.6^\circ \text{ V}}$

Now find  $I_{sc}$

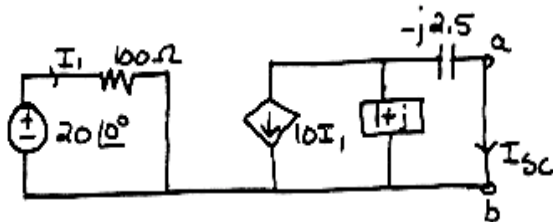


$$I_1 = \frac{20\angle 0^\circ}{100} = 0.2\angle 0^\circ \text{ A}$$

$$I_{sc} = -\frac{(1+j)}{(1+j)-j2.5}(10I_1) = -1.57\angle 101.3^\circ \text{ A}$$

$$\text{So } Z_{th} = \frac{V_{oc}}{I_{sc}} = \frac{-2.86\angle 45.6^\circ}{-1.57\angle 101.3^\circ} = \underline{1.03 - j1.5\Omega}$$

So have Thévenin Equivalent circuit

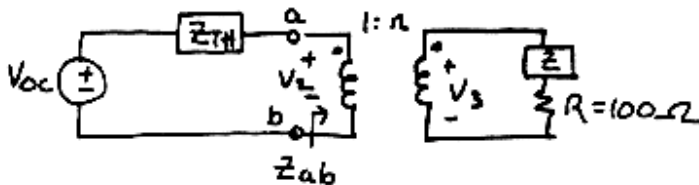

Assume  $Z = jX$

$$Z_{ab} = \frac{1}{n^2}(R+Z)$$

$$= \frac{1}{n^2}(R+jX)$$

when  $Z_{ab} = Z_{th}^* \Rightarrow$  max. power transfer

$$\text{So } \frac{1}{n^2}(R+jX) = 1.03+j1.15 \text{ So } \frac{R}{n_2} = 1.03 \text{ or } \underline{n = 9.85 \text{ turns}}$$

$$\frac{X}{n^2} = 1.5 \text{ or } X = 145.6\Omega$$

So  $Z = jX = j145.6\Omega \leftarrow$ an inductor

So have  $j\omega L = j145.6\Omega$  yields  $\underline{L = 145.6\mu\text{H}}$


$$\text{Now } V_2 = \frac{Z_{ab}}{Z_{ab}+Z_{th}} V_{oc} = \frac{1.03+j1.5}{1.03+1.03} (-2.86\angle 45.6^\circ) = -2.53\angle 101.1^\circ$$

$$V_3 = nV_2 = -24.9\angle 101.1^\circ \text{ V}$$

$$\text{So } P_{\max} = \frac{1}{2} \frac{V_m^2}{R} = \frac{1}{2} (24.9)^2 \left( \frac{1}{1.03} \right) = \underline{300 \text{ W}}$$

## PSpice Problems

### SP 11-1

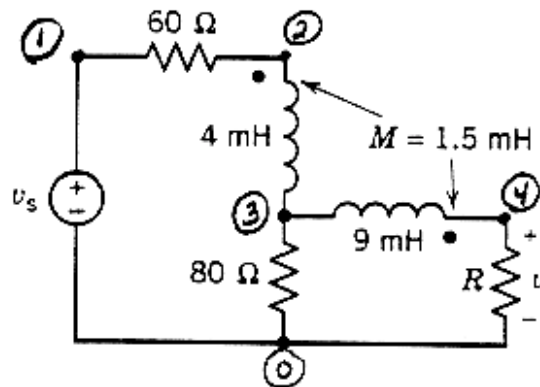

$$k = \frac{m}{\sqrt{L_1 L_2}} = 0.25$$

$$\omega = 10^4 \text{ rad/sec}$$

$$v_s = 200 \sin(\omega t + 45^\circ) \text{ V}$$

Input File:

```
Vs 1 0 ac 200 45
R1 1 2 60
R2 3 0 80
R3 4 0 100
L1 2 3 4m
L2 2 3 9m
K1 L1 L2 0.25
```


```
.ac lin 1 1591.5 1591.5
.print ac Vm(4) Vp(4)
.end
```

Output:

```
FREQ VM(4) VP(4)
1.592E+03 7.001E+01 7.177E+00
```

$$\text{So } v(t) = \underline{70 \sin(\omega t + 7.2^\circ) \text{ V}}$$

SP 11-2

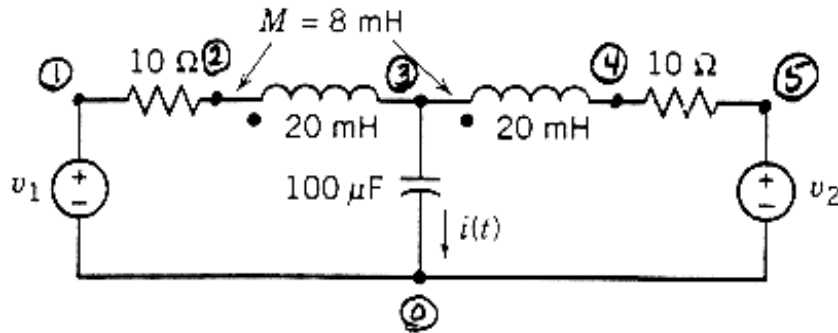

$\omega = 500 \text{ rad/sec}$   
 $V_1 = 100 \angle 0^\circ$   
 $V_2 = 100 \angle -90^\circ$   
 $k = 0.4$

Input File:

```
V1 1 0 ac 100 0
V2 5 0 ac 100 -90
R1 1 2 10
R2 4 5 10
L1 2 3 20m
L2 3 4 20m
K1 L1 L2 0.4
C1 3 0 100u
```


```
.ac lin 1 79.6 79 .6
.print ac Im(C1) Ip(C1)
.end
```

Output:

FREQ	IM(C1)	IP(C1)
7.960E+01	3.992E+00	2.860E+01

So  $i(t) = 4.0 \cos(500t + 28.6^\circ) \text{ A}$

SP 11-3

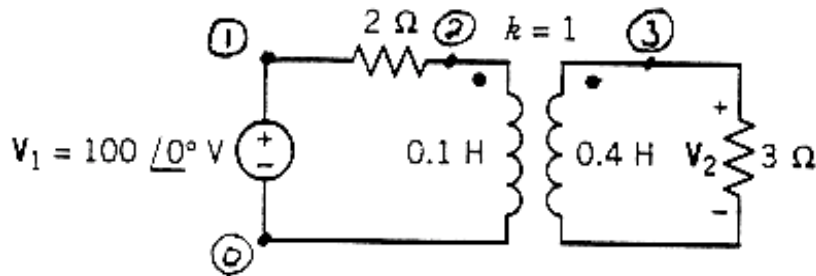

$V_1 = 100 \angle 0^\circ$   
 $\omega = 1000 \text{ rad/sec}$   
 $n^2 = \frac{L}{L} = \frac{0.4}{0.1} = 2$

```

Input File:
Vs 1 0 ac 100 0
R1 1 2 2
R2 3 0 3
L1 2 0 0.1
L2 3 0 0.4
K1 L1 L2 1

```

```

.ac lin 1 159.15 159.15
.print ac Vm(3) Vp(3)
.end

```


```

Output:
FREQ VM(3) VP(3)
1.592E+02 5.454E+01 3.125E-01

```

$$\text{So } \frac{V_2}{V_1} = \frac{54.5}{100} = \underline{0.545} \angle 0^\circ$$

### SP 11-4

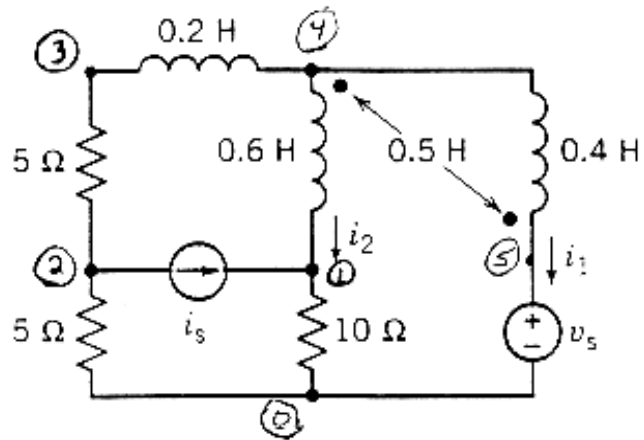

$$K = \frac{m}{\sqrt{L_1 L_2}} = \frac{-0.5}{\sqrt{(0.6)(0.4)}} = -1$$

$$f = 1.59$$

$$i_s(t) = 6 \cos(10t + 45^\circ)$$

$$v_s(t) = 12 \sin(10t) = 12 \cos(10t - 90^\circ)$$

```

Input:
R1 1 0 10
R2 2 0 5
R3 3 2 5
L1 3 4 0.2
L2 4 1 0.6
L3 4 5 0.4
K1 L2 L3 -1
Is 2 1 ac 6 45
Vs 5 0 ac 12 -90

```

```

.ac lin 1 1.59 1.59
.print ac Im(L3) Ip(L3) Im(L2) Ip(L2)
.end


```

```

Output:
FREQ IM(L3) IP(3) IM(L2) IP(L2)
1.590E+00 1.814E+00 -6.498E+01 3.729E+00 -1.677E+02

```

SP 11-5

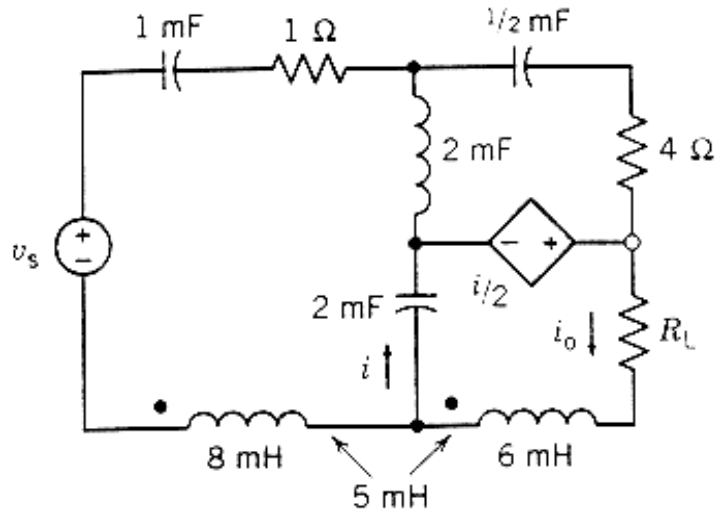

$$K = \frac{5}{\sqrt{(8)(6)}} = 0.72$$

$$v_s = 2\cos 500 t$$

$$R_L = 3\Omega$$

Input:

```
Vs      1      0      ac      2      0
R1      2      3      1
R2      4      5      4
RL      5      9      3
C1      1      2      1e-3
C2      3      4      0.5e-3
C3      7      6      2e-3
L1      3      6      2e-3
L2      0      8      8e-3
L3      8      9      6e-3
K1      L2      L3      0.72
Vdummy  8      7      0
H1      5      6      Vdummy  0.5
```

```
.ac lin 1 80 80
.print ac      Im(RL)      Ip(RL)
.end
```


Output:

```
FREQ      IM(RL)      IP(RL)
8.000E+01  5.463E-01      -1.262e+02
```


So  $i_0 = 0.546\cos(500t+126^\circ)$  A

## Verification Problems

### VP 11-1 Phasor circuit

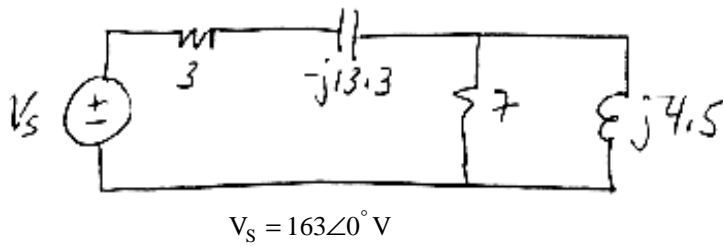

Circuit reduces to →

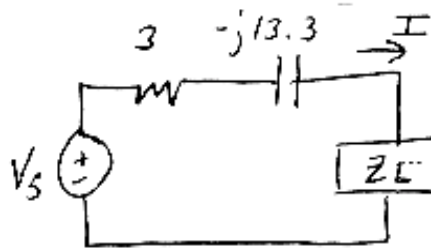

$$Z_L = \frac{(7)(j4.5)}{7 - j4.5} = \frac{31.5\angle 90^\circ}{8.32\angle 33^\circ} = 3.8\angle 57^\circ = 2.1 + j3.2$$

$$I = \frac{V}{Z_T} = \frac{163\angle 0^\circ}{3 - j13.3 + 2.1 + j3.2} = \frac{163\angle 0^\circ}{5 - j10}$$

$$= \frac{163\angle 0^\circ}{11.2\angle -63^\circ} = 14.5\angle 63^\circ \text{ A}$$


$$S = P + j\theta = VI^* = (163\angle 0^\circ)(14.5\angle -63^\circ) = 2372\angle -63^\circ \text{ VA}$$

$$S = 2372\angle -63^\circ = 1077 - j2114 = P + jQ$$

∴ P = 1077W and S = 2114 VAR Not as reported

### VP 11-2

Simplify circuit to

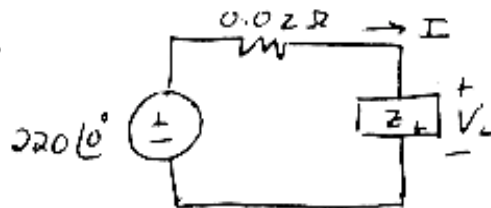

$$P_L = \frac{|V_L|^2}{2}$$

$$Z_L = \frac{(15 + j6)(20 + j4)}{15 + j6 + 20 + j4} = \frac{(16.2\angle 22^\circ)(20.4\angle 11^\circ)}{36.4\angle 16^\circ} = 9.1\angle 17^\circ = 8.65 + j2.68$$

$$V_L = \left( \frac{Z_P}{Z_P + 0.02} \right) V_s = \frac{(9.06\angle 17^\circ)(220\angle 0^\circ)}{9.08\angle 17^\circ} = 220\angle 0^\circ$$

$$P_L = \frac{|V_L|^2}{R_L} = \frac{(220)^2}{8.65} = \underline{5595\text{W}} \quad \text{Not as reported}$$


**VP 11-3**

$$v(t) = \begin{cases} 5 & 0 < t < 5 \\ -10 & 5 < t < 20 \\ 5 & 20 < t < 25 \end{cases}$$

$$V_{\text{eff}} = \sqrt{\frac{1}{25} \left[ \int_0^5 25 dt + \int_5^{20} 100 dt + \int_{20}^{25} 25 dt \right]} = \sqrt{\frac{1750}{25}} = \underline{8.37 \text{ V}} \text{ as stated}$$

**VP 11-4**

Apply test voltage

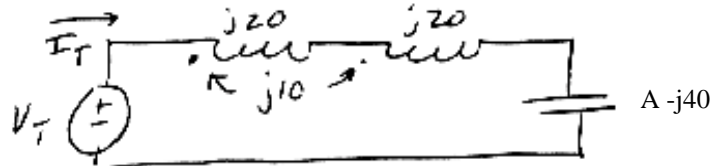


loop equation :  $j20I_T + j10I_T + j30I_T + j10I_T - j40I_T = V_T$

so  $\frac{V_T}{I_T} = Z = \underline{j30 \Omega}$  as reported

Design Problems

**DP 11-1**

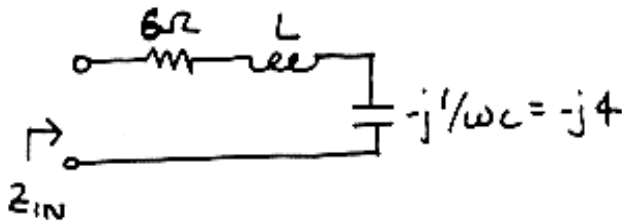

Desire  $Z_{\text{IN}} = 7.21 \angle 33.7^\circ$


Now  $Z_{\text{IN}} = 6 + jX = 7.21 \angle 33.7^\circ$

$|Z_{\text{IN}}|^2 = (7.21)^2 = 6^2 + X^2 \Rightarrow X^2 = 16.0$  or  $X = 4$

$\therefore Z_{\text{IN}} = 6 + j4 = 6 + j\omega L - j4$

Thus  $4 = \omega L - 4$  or  $\underline{L = 8/4 = 2.0 \text{ H}}$

**DP 11-2**

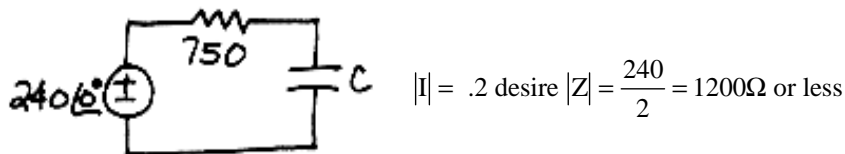

$|I| = .2$  desire  $|Z| = \frac{240}{.2} = 1200 \Omega$  or less


Now  $Z = 750 - jX$  where  $X = 1/\omega C$

$|Z|^2 = (1200)^2 = (750)^2 + X^2 \Rightarrow X = 937 \Omega$

$\therefore C = \frac{1}{\omega X} = \frac{1}{(2\pi)(400)(937)} = \underline{0.425 \mu\text{F}}$



DP 11-3

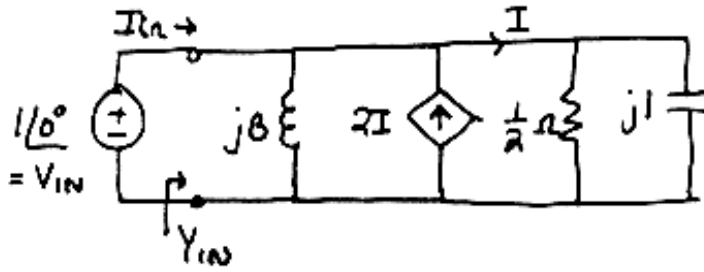

Apply test source  $V_{in} = 1\angle 0^\circ$

$$I = V_{in}(2 + j) = 1\angle 0^\circ (2 + j) = 2 + j$$

$$\text{KCL at top node: } -2I + I + V_{in}(-jB) = I_{in} \quad \text{where } B = \frac{1}{\omega L}$$

$$\Rightarrow I_{in} = -I - jB = -(2 + j) - jB = -2 - j(1 + B)$$


$$\text{Now } Y_{in} = I_{in} = Y\angle 0^\circ \text{ where } Y = \sqrt{2^2 + (1 + B)^2}$$

$$\text{Note if } B = 1, \text{ then } Y = \sqrt{8} = 2.83$$

$$\text{and } Y_{in} = 2.83\angle -135^\circ$$

$$\therefore L = \frac{1}{\omega B} = \frac{1}{5 \times 10^4} = \underline{20\mu\text{H}}$$

DP 11-4

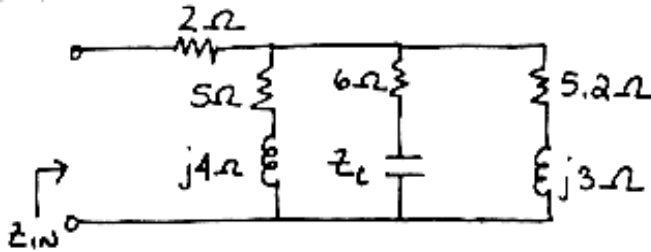

$\omega = 100 \text{ rad/sec}$   
 $Z_L = -jX \text{ where } X = \frac{1}{\omega C}$

$$Z_{in} = 2 + \frac{1}{Y}$$

$$Y = \frac{1}{5 + j4} + \frac{1}{6 - jX} + \frac{1}{5.2 + j3}$$

$$\text{Try } X = 3\Omega \Rightarrow Y = .156\angle -38.7^\circ + .149\angle 26.6^\circ + .167\angle -30^\circ = 0.416\angle -16^\circ$$


$$\therefore Z_{in} = 2 + 2.4\angle 16^\circ = 4.36\angle 8.72^\circ$$

$$\therefore |Z_{in}| = 4.36 \text{ is inside designed range}$$

$$\text{Thus } C = \frac{1}{\omega X} = \frac{1}{(100)(3)} = \underline{3.33\text{mF}}$$

DP 11-5

Equivalent circuit

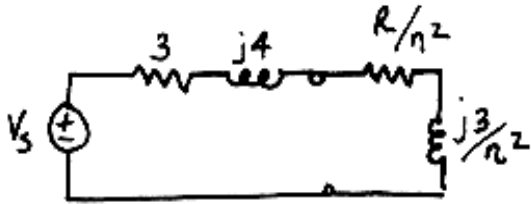

$$I = \frac{V}{\left(3 + \frac{R}{n^2}\right) + j\left(\frac{3}{n^2} + 4\right)}$$

$$P = \frac{\left(\frac{R}{n^2}\right)V^2}{\left(3 + \frac{R}{n^2}\right)^2 + \left(\frac{3}{n^2} + 4\right)^2}$$


If  $R = 4\Omega$

$$P = \frac{n^2 R V^2}{25n^4 + 48n^2 + 25} \quad \text{thus} \quad \frac{dP}{dn} = 0 = R V^2 \left[ \frac{2n(25n^4 + 48n^2 + 25) - n^2(100n^3 + 96n)}{(25n^4 + 48n^2 + 25)^2} \right]$$

$$\Rightarrow -50n^5 + 50n = 0 \Rightarrow n^4 = 1 \text{ or } \underline{n = 1}$$

If  $R = 8\Omega$  similar analysis yields  $n = 1.31$

DP 11-6

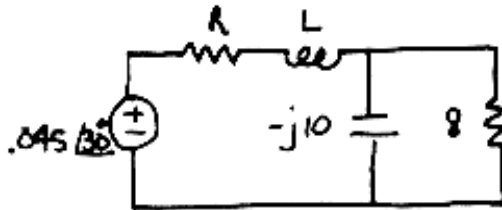

$$\omega = 10^6 \text{ rad/sec}$$

$$Z_L = \frac{8(-j10)}{8 - j10} = 4.88 - j3.9$$


So need  $j\omega L = j3.9 \Rightarrow$  then  $L = 3.9\mu\text{H}$

For maximum power to  $4.88\Omega$  of  $Z$ , we need  $\underline{R = 0}$

Then all power goes to  $4.88\Omega$ .

$$\text{So } P_{\max} = \frac{(.045/\sqrt{2})^2}{4.88} = \underline{208\mu\text{W}}$$


DP 11-7

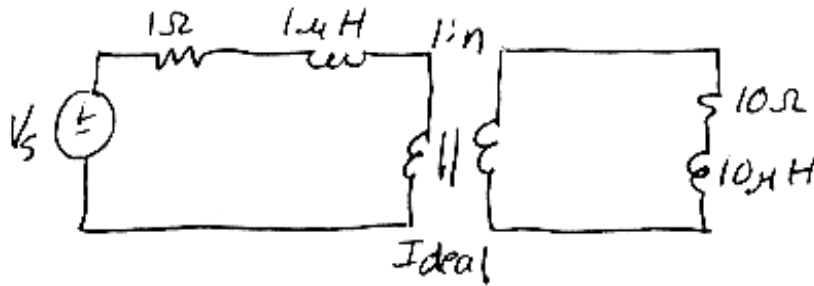

$f = 100\text{KHz}$


$Z_T = Z_L$  for maximum power transfer

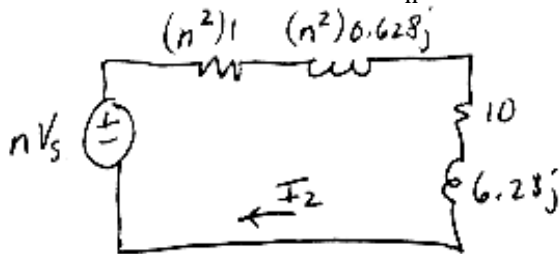$R_T = 1\Omega, R_L = 10\Omega, \text{ so } 1 = \frac{10}{n^2} \Rightarrow n^2 = 10 \Rightarrow \underline{n=3.16}$



$$I_2 = \frac{nV_s}{(10+6.28j)2} = \frac{nV_s}{17\angle 32^\circ} = \underline{(0.06\angle -32^\circ)nV_s}$$

DP 11-8

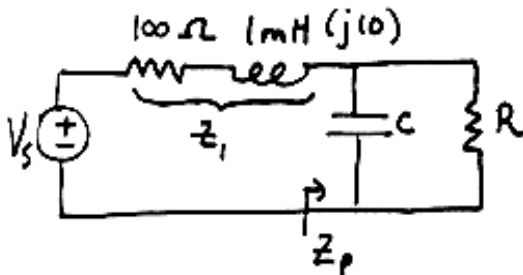

$\omega_0 = 10^7 \text{ rad/sec}$

$v_s = V_0 \sin \omega_0 t$

$Z_1 = 100 + j10$

$\therefore \text{need } Z_p = 100 - j10$

for maximum power to R

$$Y_p = j\omega C + \frac{1}{R} = G + j\omega C$$

$$Z_p = \frac{1}{G + j\omega C} = \frac{G - j\omega C}{G^2 + (\omega C)^2}$$

need  $\frac{G}{G^2 + (\omega C)^2} = 100$  (1) and  $\frac{\omega C}{G^2 + (\omega C)^2} = 10$  (2)

Taking the ratio of (1) & (2) leads to  $\frac{G}{\omega C} = 10$  or  $\underline{\underline{G^2 = 100(\omega C)}}$  (3)

Now plugging (3) into (2) yields  $\underline{C = 99\text{pf}}$

and thus  $G = 9.9 \times 10^{-3}$  or  $\underline{R = \frac{1}{G} = 101\Omega}$

