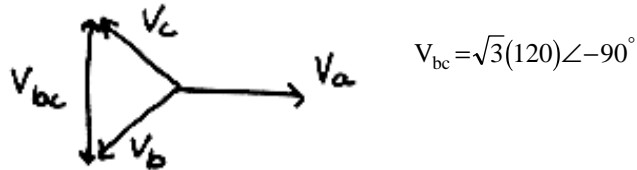


## Chapter 12: Three-Phase Circuits


### Exercises

#### Ex. 12.3-1

$$V_C = 120\angle -240^\circ \quad \text{so} \quad V_A = 120\angle 0^\circ \quad \text{and} \quad V_B = 120\angle -120^\circ$$



#### Ex. 12.4-1 Four-wire Y-to-Y Circuit

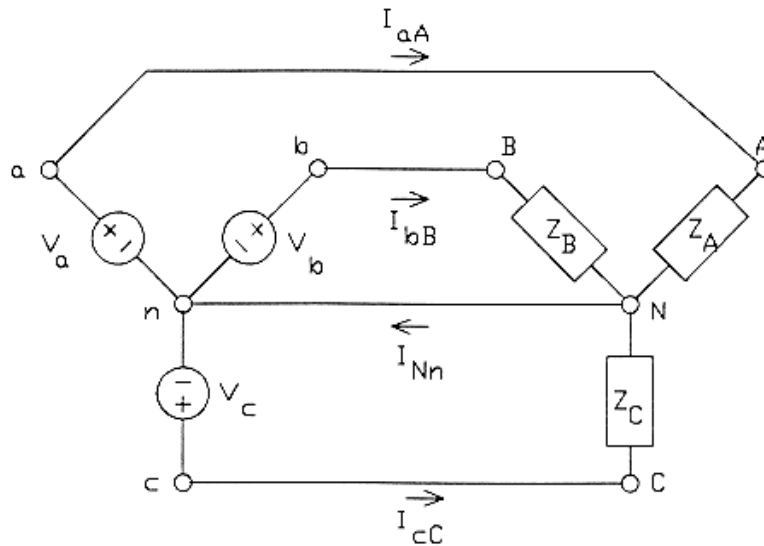

#### Mathcad analysis

Describe the three-phase source:  $V_a := 120 \cdot e^{j \cdot \frac{\pi}{180} \cdot 0}$      $V_b := V_a \cdot e^{j \cdot \frac{\pi}{180} \cdot -120}$      $V_c := V_a \cdot e^{j \cdot \frac{\pi}{180} \cdot 120}$

Describe the three-phase load:  $Z_A := 80 + j \cdot 50$      $Z_B := 80 + j \cdot 80$      $Z_C := 100 - j \cdot 25$

Calculate the line currents:  $I_{aA} := \frac{V_a}{Z_A}$      $I_{bB} := \frac{V_b}{Z_B}$      $I_{cC} := \frac{V_c}{Z_C}$

$$I_{aA} = 1.079 - 0.674i$$

$$I_{bB} = -1.025 - 0.275i$$

$$I_{cC} = -0.809 + 0.837i$$

$$|I_{aA}| = 1.272$$

$$|I_{bB}| = 1.061$$

$$|I_{cC}| = 1.164$$

$$\frac{180}{\pi} \cdot \arg(I_{aA}) = -32.005$$

$$\frac{180}{\pi} \cdot \arg(I_{bB}) = -165$$


$$\frac{180}{\pi} \cdot \arg(I_{cC}) = -134.036$$

Calculate the current in the neutral wire:  $I_{Nn} := I_{aA} + I_{bB} + I_{cC}$   $I_{Nn} = -0.755 - 0.112i$

Calculate the power delivered to the load:

$$\begin{aligned} S_A &:= \overline{I_{aA}} \cdot V_a & S_B &:= \overline{I_{bB}} \cdot V_b & S_C &:= \overline{I_{cC}} \cdot V_c \\ S_A &= 129.438 + 80.899i & S_B &= 90 + 90i & S_C &= 135.529 - 33.883i \\ S_A + S_B + S_C &= 354.968 + 137.017i \end{aligned}$$

**Ex. 12.4-2** Four-wire Y-to-Y Circuit

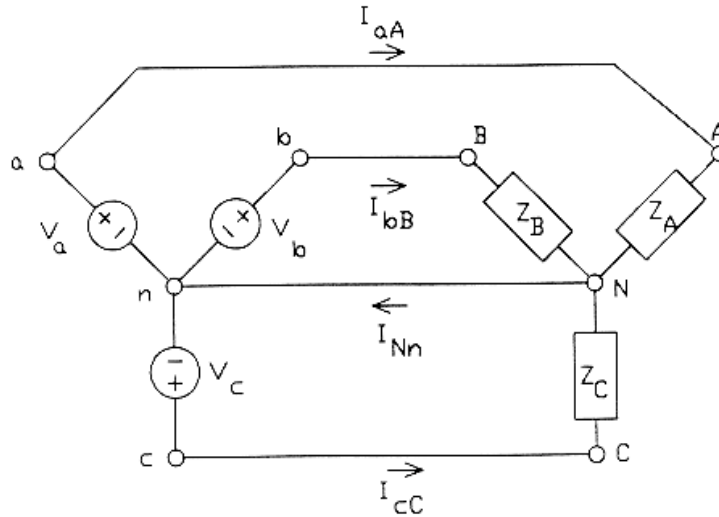

**Mathcad analysis**

Describe the three-phase source:  $V_a := 120 \cdot e^{j \frac{\pi}{180} \cdot 0}$   $V_b := V_a \cdot e^{j \frac{\pi}{180} \cdot -120}$   $V_c := V_a \cdot e^{j \frac{\pi}{180} \cdot 120}$

Describe the three-phase load:  $Z_A := 40 + j \cdot 30$   $Z_B := Z_A$   $Z_C := Z_A$

Calculate the line currents:  $I_{aA} := \frac{V_a}{Z_A}$   $I_{bB} := \frac{V_b}{Z_B}$   $I_{cC} := \frac{V_c}{Z_C}$


$$\begin{aligned} I_{aA} &= 1.92 - 1.44i & I_{bB} &= -2.207 - 0.943i & I_{cC} &= 0.287 + 2.383i \\ |I_{aA}| &= 2.4 & |I_{bB}| &= 2.4 & |I_{cC}| &= 2.4 \\ \frac{180}{\pi} \cdot \arg(I_{aA}) &= -36.87 & \frac{180}{\pi} \cdot \arg(I_{bB}) &= -156.87 & \frac{180}{\pi} \cdot \arg(I_{cC}) &= 83.13 \end{aligned}$$

Calculate the current in the neutral wire:  $I_{Nn} := I_{aA} + I_{bB} + I_{cC}$   $I_{Nn} = 0$

Calculate the power delivered to the load:

$$\begin{aligned} S_A &:= \overline{I_{aA}} \cdot V_a & S_B &:= \overline{I_{bB}} \cdot V_b & S_C &:= \overline{I_{cC}} \cdot V_c \\ S_A &= 230.4 + 172.8i & S_B &= 230.4 + 172.8i & S_C &= 230.4 + 172.8i \\ S_A + S_B + S_C &= 691.2 + 518.4i \end{aligned}$$

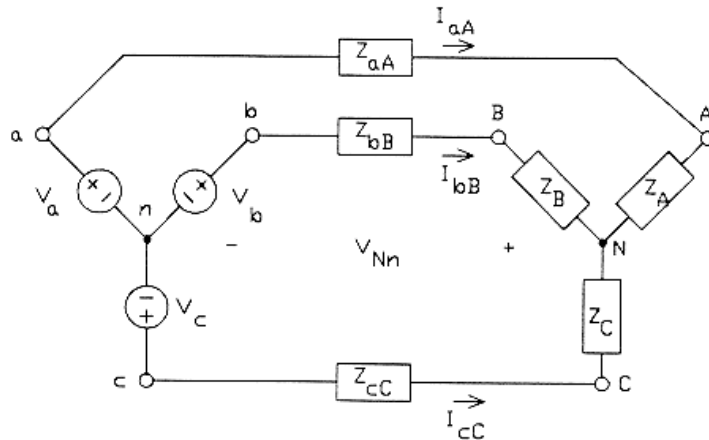**Ex. 12.4-3** Three-wire Y-to-Y Circuit with line impedances



**Mathcad analysis**

Describe the three-phase source:  $V_p := 120$

$$V_a := V_p \cdot e^{j \frac{\pi}{180} \cdot 0} \quad V_b := V_a \cdot e^{j \frac{\pi}{180} \cdot 120} \quad V_c := V_a \cdot e^{j \frac{\pi}{180} \cdot 240}$$

Describe the three-phase load:  $Z_A := 80 + j \cdot 50 \quad Z_B := 80 + j \cdot 80 \quad Z_C := 100 - j \cdot 25$

Describe the three-phase line:  $Z_{aA} := 0 \quad Z_{bB} := 0 \quad Z_{cC} := 0$

Calculate the voltage at the neutral of the load with respect to the neutral of the source:

$$V_{nN} := \frac{(Z_{aA} + Z_A) \cdot (Z_{cC} + Z_C) \cdot e^{j \frac{4}{3} \pi} + (Z_{aA} + Z_A) \cdot (Z_{bB} + Z_B) \cdot e^{j \frac{2}{3} \pi} + (Z_{bB} + Z_B) \cdot (Z_{cC} + Z_C)}{(Z_{aA} + Z_A) \cdot (Z_{cC} + Z_C) + (Z_{aA} + Z_A) \cdot (Z_{bB} + Z_B) + (Z_{bB} + Z_B) \cdot (Z_{cC} + Z_C)} \cdot V_p$$

$$V_{nN} = -25.137 - 14.236i \quad |V_{nN}| = 28.888 \quad \frac{180}{\pi} \cdot \arg(V_{nN}) = -150.475$$

Calculate the line currents:  $I_{aA} := \frac{V_a - V_{nN}}{Z_A + Z_{aA}} \quad I_{bB} := \frac{V_b - V_{nN}}{Z_B + Z_{bB}} \quad I_{cC} := \frac{V_c - V_{nN}}{Z_C + Z_{cC}}$

$$I_{aA} = 1.385 - 0.687i \quad I_{bB} = -0.778 - 0.343i \quad I_{cC} = -0.606 + 1.03i$$

$$|I_{aA}| = 1.546 \quad |I_{bB}| = 0.851 \quad |I_{cC}| = 1.195$$

$$\frac{180}{\pi} \cdot \arg(I_{aA}) = -26.403 \quad \frac{180}{\pi} \cdot \arg(I_{bB}) = -156.242 \quad \frac{180}{\pi} \cdot \arg(I_{cC}) = 120.475$$

Calculate the power delivered to the load:

$$S_A := \overline{I_{aA}} \cdot I_{aA} \cdot Z_A \quad S_B := \overline{I_{bB}} \cdot I_{bB} \cdot Z_B \quad S_C := \overline{I_{cC}} \cdot I_{cC} \cdot Z_C$$

$$S_A = 191.168 + 119.48i \quad S_B = 57.87 + 57.87i \quad S_C = 142.843 - 35.711i$$

$$S_A + S_B + S_C = 391.88 + 141.639i$$

**Ex. 12.4-4**

**Mathcad analysis**

Describe the three-phase source:  $V_p := 120$

$$V_a := V_p \cdot e^{j \frac{\pi}{180} \cdot 0} \quad V_b := V_a \cdot e^{j \frac{\pi}{180} \cdot -120} \quad V_c := V_a \cdot e^{j \frac{\pi}{180} \cdot 120}$$

Describe the three-phase load:  $Z_A := 40 + j \cdot 30$        $Z_B := Z_A$        $Z_C := Z_B$

Describe the three-phase line:  $Z_{aA} := 0$        $Z_{bB} := 0$        $Z_{cC} := 0$

Calculate the voltage at the neutral of the load with respect to the neutral of the source:

$$V_{nN} := \frac{(Z_{aA} + Z_A) \cdot (Z_{cC} + Z_C) \cdot e^{j \frac{4}{3} \pi} + (Z_{aA} + Z_A) \cdot (Z_{bB} + Z_B) \cdot e^{j \frac{2}{3} \pi} + (Z_{bB} + Z_B) \cdot (Z_{cC} + Z_C)}{(Z_{aA} + Z_A) \cdot (Z_{cC} + Z_C) + (Z_{aA} + Z_A) \cdot (Z_{bB} + Z_B) + (Z_{bB} + Z_B) \cdot (Z_{cC} + Z_C)} \cdot V_p$$

$$V_{nN} = -4.075 \cdot 10^{-15} + 1.397 \cdot 10^{-14} i \quad |V_{nN}| = 1.455 \cdot 10^{-14} \quad \frac{180}{\pi} \cdot \arg(V_{nN}) = 106.26$$

Calculate the line currents:  $I_{aA} := \frac{V_a - V_{nN}}{Z_A + Z_{aA}}$        $I_{bB} := \frac{V_b - V_{nN}}{Z_B + Z_{bB}}$        $I_{cC} := \frac{V_c - V_{nN}}{Z_C + Z_{cC}}$

$$I_{aA} = 1.92 - 1.44i \quad I_{bB} = -2.207 - 0.943i \quad I_{cC} = 0.287 + 2.383i$$

$$|I_{aA}| = 2.4 \quad |I_{bB}| = 2.4 \quad |I_{cC}| = 2.4$$

$$\frac{180}{\pi} \cdot \arg(I_{aA}) = -36.87 \quad \frac{180}{\pi} \cdot \arg(I_{bB}) = -156.87 \quad \frac{180}{\pi} \cdot \arg(I_{cC}) = 83.13$$

Calculate the power delivered to the load:


$$S_A := \overline{I_{aA}} \cdot I_{aA} \cdot Z_A \quad S_B := \overline{I_{bB}} \cdot I_{bB} \cdot Z_B \quad S_C := \overline{I_{cC}} \cdot I_{cC} \cdot Z_C$$

$$S_A = 230.4 + 172.8i \quad S_B = 230.4 + 172.8i \quad S_C = 230.4 + 172.8i$$

$$S_A + S_B + S_C = 691.2 + 518.4i$$

**Ex. 12.6-1**

balanced

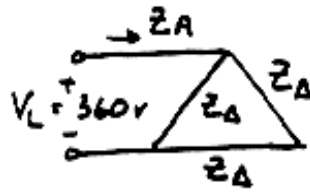

(See Table 12.5-1)

$$Z_{\Delta} = 180 \angle -45^{\circ}$$

phase currents:

$$I_{AB} = \frac{V_{AB}}{Z} = \frac{360 \angle 0^{\circ}}{180 \angle -45^{\circ}} = 2 \angle 45^{\circ} \text{ A}$$

$$I_{BC} = \frac{V_{BC}}{Z} = \frac{360 \angle -120^{\circ}}{180 \angle -45^{\circ}} = 2 \angle -75^{\circ} \text{ A}$$

$$I_{CA} = \frac{V_{CA}}{Z} = \frac{360 \angle 120^{\circ}}{180 \angle -45^{\circ}} = 2 \angle 165^{\circ} \text{ A}$$

line currents:


$$I_A = I_{AB} - I_{CA} = 2 \angle 45^{\circ} - 2 \angle 165^{\circ} = 2\sqrt{3} \angle 15^{\circ} \text{ A}$$

$$I_B = 2\sqrt{3} \angle -105^{\circ} \text{ A}$$

$$I_C = 2\sqrt{3} \angle 135^{\circ} \text{ A}$$

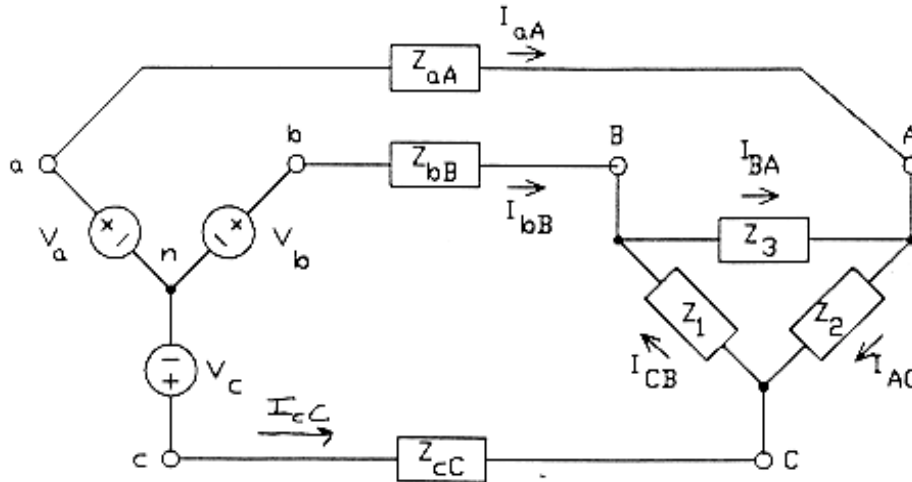**Ex. 12.7-1 and Ex. 12.8-1**

Three-wire Y-to-Delta Circuit with line impedances



**Mathcad analysis**

Describe the three-phase source:  $V_p := 110$

$$V_a := V_p \cdot e^{j \frac{\pi}{180} \cdot 0} \quad V_b := V_a \cdot e^{j \frac{\pi}{180} \cdot -120} \quad V_c := V_a \cdot e^{j \frac{\pi}{180} \cdot -240}$$


Describe the delta-connected load:  $Z_1 := 150 + j \cdot 270 \quad Z_2 := Z_1 \quad Z_3 := Z_1$

Convert the delta load to the equivalent Y load:

$$Z_A := \frac{Z_1 \cdot Z_3}{Z_1 + Z_2 + Z_3} \quad Z_B := \frac{Z_2 \cdot Z_3}{Z_1 + Z_2 + Z_3} \quad Z_C := \frac{Z_1 \cdot Z_2}{Z_1 + Z_2 + Z_3}$$

$$\cdot \quad Z_A = 50 + 90i \quad Z_B = 50 + 90i \quad Z_C = 50 + 90i$$

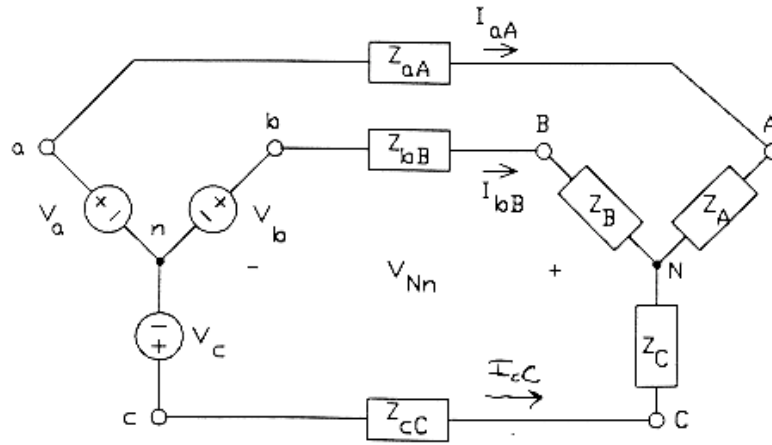Describe the three-phase line:  $Z_{aA} = 10 + j \cdot 25$   $Z_{bB} = Z_{aA}$   $Z_{cC} = Z_{aA}$



Calculate the voltage at the neutral of the load with respect to the neutral of the source:

$$V_{nN} := \frac{(Z_{aA} + Z_A) \cdot (Z_{cC} + Z_C) \cdot e^{j\frac{4}{3}\pi} + (Z_{aA} + Z_A) \cdot (Z_{bB} + Z_B) \cdot e^{j\frac{2}{3}\pi} + (Z_{bB} + Z_B) \cdot (Z_{cC} + Z_C)}{(Z_{aA} + Z_A) \cdot (Z_{cC} + Z_C) + (Z_{aA} + Z_A) \cdot (Z_{bB} + Z_B) + (Z_{bB} + Z_B) \cdot (Z_{cC} + Z_C)} \cdot V_p$$

$$V_{nN} = -4.235 \cdot 10^{-15} + 7.787j \cdot |V_{nN}| = 8.864 \cdot 10^{-15} \quad \frac{180}{\pi} \cdot \arg(V_{nN}) = 118.541$$

Calculate the line currents:  $I_{aA} = \frac{V_a - V_{nN}}{Z_A + Z_{aA}}$   $I_{bB} = \frac{V_b - V_{nN}}{Z_B + Z_{bB}}$   $I_{cC} = \frac{V_c - V_{nN}}{Z_C + Z_{cC}}$

$$I_{aA} = 0.392 - 0.752i$$

$$I_{bB} = -0.847 + 0.036i$$

$$I_{cC} = 0.455 + 0.716i$$

$$|I_{aA}| = 0.848$$

$$|I_{bB}| = 0.848$$

$$|I_{cC}| = 0.848$$

$$\frac{180}{\pi} \cdot \arg(I_{aA}) = -62.447$$

$$\frac{180}{\pi} \cdot \arg(I_{bB}) = 177.553$$

$$\frac{180}{\pi} \cdot \arg(I_{cC}) = 57.553$$

Calculate the phase voltages of the Y-connected load:

$$V_{AN} = I_{aA} \cdot Z_A$$

$$V_{BN} = I_{bB} \cdot Z_B$$

$$V_{CN} = I_{cC} \cdot Z_C$$

$$|V_{AN}| = 87.311$$

$$|V_{BN}| = 87.311$$

$$|V_{CN}| = 87.311$$

$$\frac{180}{\pi} \cdot \arg(V_{AN}) = -1.502$$

$$\frac{180}{\pi} \cdot \arg(V_{BN}) = -121.502$$

$$\frac{180}{\pi} \cdot \arg(V_{CN}) = 118.498$$

Calculate the line-to-line voltages at the load:

$$V_{AB} = V_{AN} - V_{BN}$$

$$V_{BC} = V_{BN} - V_{CN}$$

$$V_{CA} = V_{CN} - V_{AN}$$

$$|V_{AB}| = 151.227$$

$$|V_{BC}| = 151.227$$

$$|V_{CA}| = 151.227$$

$$\frac{180}{\pi} \cdot \arg(V_{AB}) = 28.498$$

$$\frac{180}{\pi} \cdot \arg(V_{BC}) = -91.502$$

$$\frac{180}{\pi} \cdot \arg(V_{CA}) = 148.49$$

Calculate the phase currents of the  $\Delta$ -connected load:

$$I_{AB} := \frac{V_{AB}}{Z_3}$$

$$I_{BC} := \frac{V_{BC}}{Z_1}$$

$$I_{CA} := \frac{V_{CA}}{Z_2}$$

$$|I_{AB}| = 0.49$$

$$|I_{BC}| = 0.49$$

$$|I_{CA}| = 0.49$$

$$\frac{180}{\pi} \cdot \arg(I_{AB}) = -32.447$$

$$\frac{180}{\pi} \cdot \arg(I_{BC}) = -152.447$$

$$\frac{180}{\pi} \cdot \arg(I_{CA}) = 87.55$$

Calculate the power delivered to the load:

$$S_A := \overline{I_{aA}} \cdot I_{aA} \cdot Z_A$$

$$S_B := \overline{I_{bB}} \cdot I_{bB} \cdot Z_B$$

$$S_C := \overline{I_{cC}} \cdot I_{cC} \cdot Z_C$$

$$S_A = 35.958 + 64.725i$$

$$S_B = 35.958 + 64.725i$$

$$S_C = 35.958 + 64.725i$$

$$S_A + S_B + S_C = 107.875 + 194.175i$$

### Ex. 12.9-1

$$P_1 = V_{AB} I_A \cos(\theta + 30^\circ) + V_{CB} I_C \cos(\theta - 30^\circ) = P_1 + P_2$$

$$\text{pf} = .4 \text{ lagging} \Rightarrow \theta = 61.97^\circ$$

$$\text{So } P_T = 450(24) [\cos 91.97^\circ + \cos 31.97^\circ] = 8791 \text{ W}$$

$$\therefore P_1 = -371 \text{ W} \quad P_2 = 9162 \text{ W}$$

### Ex. 12.9-2

See Fig. 12.9-1

$$P_1 = 60 \text{ kW} \quad P_2 = 40 \text{ kW}$$

$$\text{a) } P = P_1 + P_2 = 100 \text{ kW}$$

$$\text{b) use eqn. 12.9-7}$$

$$\tan \theta = \sqrt{3} \frac{P_2 - P_1}{P_L + P_2} = \sqrt{3} \frac{40 - 60}{100} = -0.346$$

$$\therefore \theta = -19.11^\circ$$

$$\text{so pf} = \cos(-19.11^\circ) = \underline{0.945} \text{ leading}$$

## Problems

### Section 12-3: Three Phase Voltages

#### P12.3-1

$$\text{Given } V_C = 277 \angle 45^\circ$$

$$\text{ABC reference } V_A = 277 \angle 75^\circ$$


$$V_B = 277 \angle 45^\circ + 120^\circ = 277 \angle 165^\circ$$

$$V_L = \sqrt{3} (277) = 480 \text{ V}$$

$$V_{ab} = 480 \angle -75^\circ + 30^\circ = 480 \angle -45^\circ$$

$$V_{bc} = 480 \angle -165^\circ$$

$$V_{ca} = 480 \angle 75^\circ$$

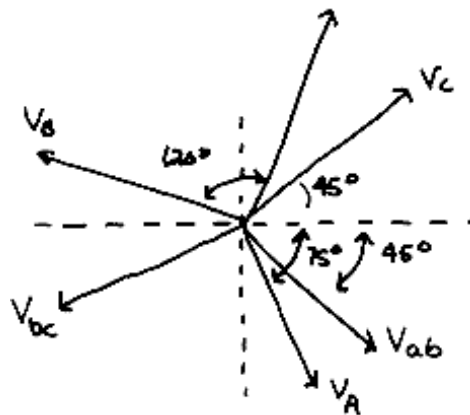

**P12.3-2**

$$V_1 = 12470\text{V} \quad V_p = \frac{12470}{\sqrt{3}} = 7200\text{V} \quad V_{BA} = 12470 \angle -35^\circ$$

$$V_b = \frac{12470}{\sqrt{3}} \angle(-35^\circ + 30^\circ) = 7200 \angle -5^\circ \text{ V}$$

$$V_a = 7200 \angle(-5^\circ + 120^\circ) = 7200 \angle -115^\circ$$

$$V_c = 7200 \angle(-5^\circ - 120^\circ) = 7200 \angle -125^\circ$$


**P12.3-3**

$$V_{ab} = 1500 \angle 30^\circ = V_L$$

$$V_p = \frac{V_L}{\sqrt{3}} \angle(\theta - 30^\circ) = \frac{1500}{\sqrt{3}} \angle(30^\circ - 30^\circ) = \underline{866 \angle 0^\circ \text{ V}}$$
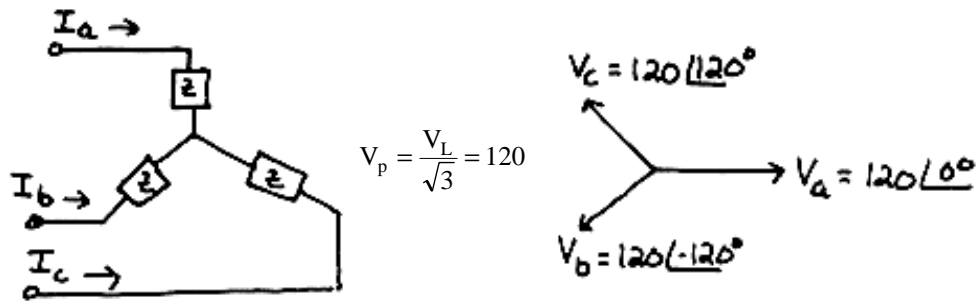
### Section 12-4: The Y-to-Y Circuit

**P12.4-1**  $V_L = 208\text{V}$  balanced Y load,  $Z = 12 \angle 30^\circ$   $12 \angle 0$




$$I_a = \frac{V_a}{Z} = \frac{120 \angle 0^\circ}{12 \angle 30^\circ} = 10 \angle -30^\circ$$

$$I_b = 10 \angle(-30^\circ - 120^\circ) = 10 \angle -150^\circ$$

$$I_c = 10 \angle 90^\circ$$
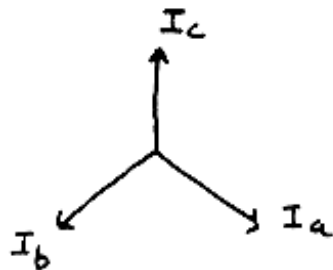
$$P = \sqrt{3} V_L I_L \cos \theta = \sqrt{3} (120)(10) \cos 30^\circ = \underline{1800 \text{ W}}$$



**P12.4-2**

$$Z_T = Z_L + Z_1 = 10 + j\omega 100 + 2 = 12 + j37.7$$

$$V_p = 120\text{V} \therefore V_L = 120\sqrt{3} \quad \text{so } V_A = 208 \angle 0^\circ$$

$$V_B = 208 \angle -120^\circ$$

$$V_C = 208 \angle +120^\circ$$

$$I_p = \frac{V_p}{Z_T} = \frac{120 \angle 0^\circ}{12 + j37.7} = \frac{120 \angle 0^\circ}{40 \angle 72^\circ} = 3 \angle -72^\circ = I_A$$


$$I_B = 3 \angle -192^\circ$$

$$I_C = 3 \angle 48^\circ$$



**P12.4-3**

a) look @ one phase

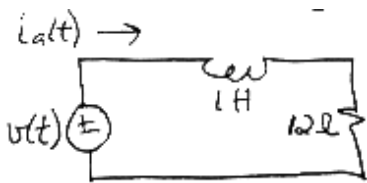

$$v(t) = 10\cos(16t - 120^\circ)$$

$$= V_p \cos(\omega t + \theta)$$

$$V_A = V_p \angle \theta_v = 10 \angle -120^\circ$$

$$Z_A = j\omega L + R = 12 + j16 = 20 \angle -53^\circ \Omega$$

$$I_A = \frac{V_A}{Z_A} = \frac{10 \angle -120^\circ}{20 \angle -53^\circ} = 0.5 \angle -173^\circ = I_p \angle \theta_I$$

$$i_a(t) = 0.5 \cos(16t - 173^\circ) \text{ A}$$


$$\text{rms} = \frac{|i_a(t)|}{\sqrt{2}} = 0.353$$

b) average power  $P = 3V_p I_p \cos \theta$

$$\theta = \theta_v - \theta_I = -120 - (-173) = 53^\circ \quad (\text{also } \theta = \theta_Z)$$

$$P = 3(10)(0.5) \cos(53^\circ) = \underline{9.0 \text{ W}}$$

**P12.4-4**

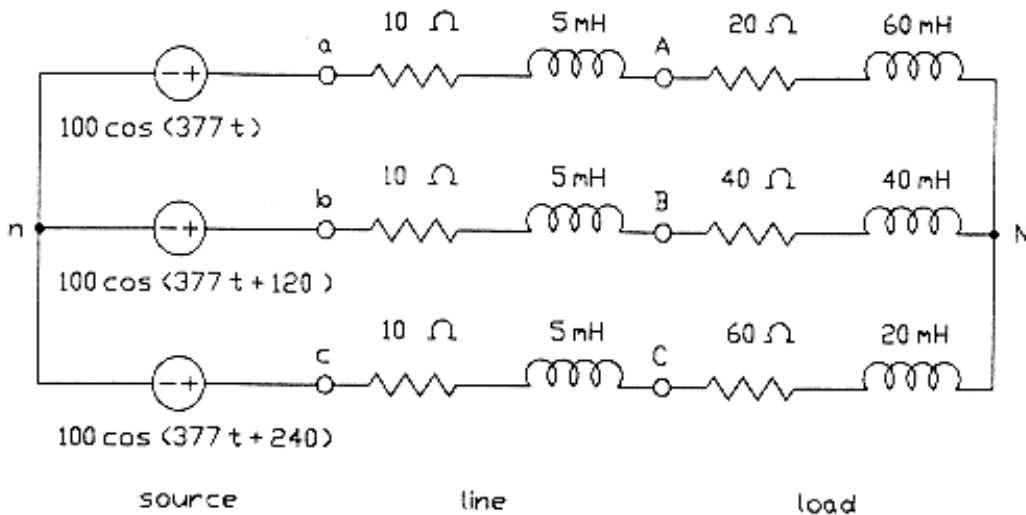

**Mathcad analysis**

Describe the three-phase source:  $V_p := 100 \quad \omega := 377$

$$V_a := V_p \cdot e^{j \frac{\pi}{180} \cdot 0} \quad V_b := V_a \cdot e^{j \frac{\pi}{180} \cdot 120} \quad V_c := V_a \cdot e^{j \frac{\pi}{180} \cdot 240}$$

Describe the three-phase load:  $Z_A := 20 + j \cdot \omega \cdot 0.06 \quad Z_B := 40 + j \cdot \omega \cdot 0.04 \quad Z_C := 60 + j \cdot \omega \cdot 0.02$

Describe the three-phase line:  $Z_{aA} := 10 + j \cdot \omega \cdot 0.005 \quad Z_{bB} := 10 + j \cdot \omega \cdot 0.005 \quad Z_{cC} := 10 + j \cdot \omega \cdot 0.005$

Calculate the voltage at the neutral of the load with respect to the neutral of the source:

$$V_{nN} := \frac{(Z_{aA}+Z_A) \cdot (Z_{cC}+Z_C) \cdot e^{j\frac{4}{3}\pi} + (Z_{aA}+Z_A) \cdot (Z_{bB}+Z_B) \cdot e^{j\frac{2}{3}\pi} + (Z_{bB}+Z_B) \cdot (Z_{cC}+Z_C)}{(Z_{aA}+Z_A) \cdot (Z_{cC}+Z_C) + (Z_{aA}+Z_A) \cdot (Z_{bB}+Z_B) + (Z_{bB}+Z_B) \cdot (Z_{cC}+Z_C)} \cdot V_p$$

$$V_{nN} = 12.209 - 24.552i \quad |V_{nN}| = 27.42 \quad \frac{180}{\pi} \cdot \arg(V_{nN}) = -63.561$$

Calculate the line currents:  $I_{aA} = \frac{V_a - V_{nN}}{Z_A + Z_{aA}} \quad I_{bB} = \frac{V_b - V_{nN}}{Z_B + Z_{bB}} \quad I_{cC} = \frac{V_c - V_{nN}}{Z_C + Z_{cC}}$

$$I_{aA} = 2.156 - 0.943i$$

$$I_{bB} = -0.439 + 2.372i$$

$$I_{cC} = -0.99 - 0.753i$$

$$|I_{aA}| = 2.353$$

$$|I_{bB}| = 2.412$$

$$|I_{cC}| = 1.244$$

$$\frac{180}{\pi} \cdot \arg(I_{aA}) = -23.619$$

$$\frac{180}{\pi} \cdot \arg(I_{bB}) = 100.492$$

$$\frac{180}{\pi} \cdot \arg(I_{cC}) = -142.741$$

Calculate the power delivered to the load:

$$S_A = \overline{I_{aA}} \cdot I_{aA} \cdot Z_A$$

$$S_B = \overline{I_{bB}} \cdot I_{bB} \cdot Z_B$$

$$S_C = \overline{I_{cC}} \cdot I_{cC} \cdot Z_C$$


$$S_A = 110.765 + 125.275i$$

$$S_B = 232.804 + 87.767i$$

$$S_C = 92.85 + 11.668i$$

$$S_A + S_B + S_C = 436.418 + 224.71i$$

#### P12.4-5

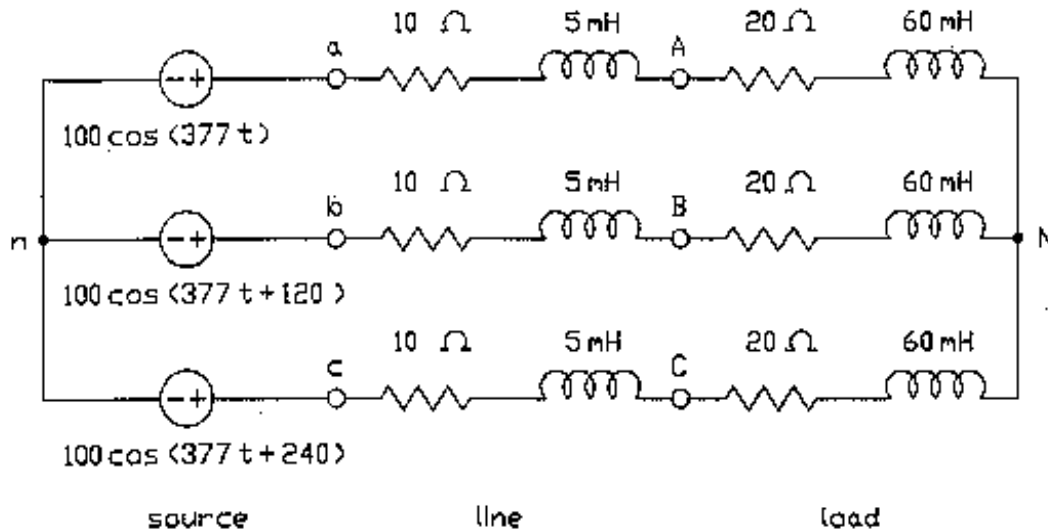

#### Mathcad analysis

Describe the three-phase source:  $V_p := 100 \quad \omega := 377$

$$V_a := V_p \cdot e^{j\frac{\pi}{180} \cdot 0} \quad V_b := V_a \cdot e^{j\frac{\pi}{180} \cdot 120} \quad V_c := V_a \cdot e^{j\frac{\pi}{180} \cdot 240}$$

Describe the three-phase load:  $Z_A := 20 + j \cdot \omega \cdot 0.06 \quad Z_B := 20 + j \cdot \omega \cdot 0.06 \quad Z_C := 20 + j \cdot \omega \cdot 0.06$

Describe the three-phase line:  $Z_{aA} := 10 + j \cdot \omega \cdot 0.005 \quad Z_{bB} := 10 + j \cdot \omega \cdot 0.005 \quad Z_{cC} := 10 + j \cdot \omega \cdot 0.005$

Calculate the voltage at the neutral of the load with respect to the neutral of the source:

$$V_{nN} := \frac{(Z_{aA}+Z_A) \cdot (Z_{cC}+Z_C) \cdot e^{j\frac{4}{3}\pi} + (Z_{aA}+Z_A) \cdot (Z_{bB}+Z_B) \cdot e^{j\frac{2}{3}\pi} + (Z_{bB}+Z_B) \cdot (Z_{cC}+Z_C)}{(Z_{aA}+Z_A) \cdot (Z_{cC}+Z_C) + (Z_{aA}+Z_A) \cdot (Z_{bB}+Z_B) + (Z_{bB}+Z_B) \cdot (Z_{cC}+Z_C)} \cdot V_p$$

$$V_{nN} = -6.966 \cdot 10^{-15} + 8.891 \cdot 10^{-15}i \quad |V_{nN}| = 1.129 \cdot 10^{-14}$$

$$\frac{180}{\pi} \cdot \arg(V_{nN}) = -128.079$$

Calculate the line currents:  $I_{aA} = \frac{V_a - V_{nN}}{Z_A + Z_{aA}}$     $I_{bB} = \frac{V_b - V_{nN}}{Z_B + Z_{bB}}$     $I_{cC} = \frac{V_c - V_{nN}}{Z_C + Z_{cC}}$

$I_{aA} = 1.999 - 1.633i$     $I_{bB} = 0.415 + 2.548i$     $I_{cC} = -2.414 - 0.915i$

$|I_{aA}| = 2.582$     $|I_{bB}| = 2.582$     $|I_{cC}| = 2.582$

$\frac{180}{\pi} \cdot \arg(I_{aA}) = -39.243$     $\frac{180}{\pi} \cdot \arg(I_{bB}) = 80.757$     $\frac{180}{\pi} \cdot \arg(I_{cC}) = -159.243$


Calculate the power delivered to the load:

$S_A = \overline{I_{aA}} \cdot I_{aA} \cdot Z_A$     $S_B = \overline{I_{bB}} \cdot I_{bB} \cdot Z_B$     $S_C = \overline{I_{cC}} \cdot I_{cC} \cdot Z_C$

$S_A = 133.289 + 150.75i$     $S_B = 133.289 + 150.75i$     $S_C = 133.289 + 150.75i$

$S_A + S_B + S_C = 399.868 + 452.251i$

**P12.4-6**

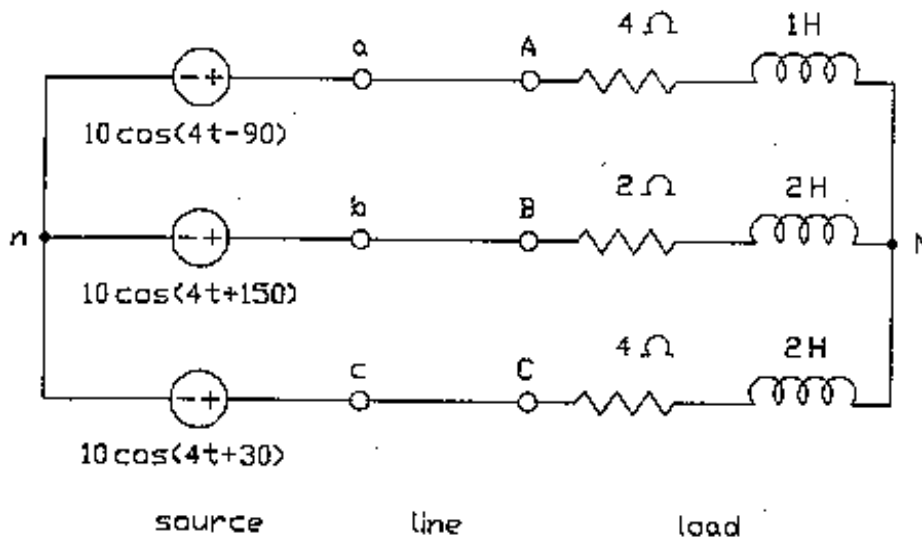

**Mathcad analysis**

Describe the three-phase source:  $V_p := 10$     $\omega := 4$

$V_a := V_p \cdot e^{j \frac{\pi}{180} \cdot 90}$     $V_b := V_p \cdot e^{j \frac{\pi}{180} \cdot 150}$     $V_c := V_p \cdot e^{j \frac{\pi}{180} \cdot 30}$

Describe the three-phase load:  $Z_A := 4 + j \cdot \omega \cdot 1$     $Z_B := 2 + j \cdot \omega \cdot 2$     $Z_C := 4 + j \cdot \omega \cdot 2$

Describe the three-phase line:  $Z_{aA} := 0$     $Z_{bB} := 0$     $Z_{cC} := 0$

Calculate the voltage at the neutral of the load with respect to the neutral of the source:

$V_{nN} := \frac{(Z_{aA} + Z_A) \cdot (Z_{cC} + Z_C) \cdot V_b + (Z_{aA} + Z_A) \cdot (Z_{bB} + Z_B) \cdot V_c + (Z_{bB} + Z_B) \cdot (Z_{cC} + Z_C) \cdot V_a}{(Z_{aA} + Z_A) \cdot (Z_{cC} + Z_C) + (Z_{aA} + Z_A) \cdot (Z_{bB} + Z_B) + (Z_{bB} + Z_B) \cdot (Z_{cC} + Z_C)}$

$V_{nN} = 1.528 - 0.863i$     $|V_{nN}| = 1.755$     $\frac{180}{\pi} \cdot \arg(V_{nN}) = -29.466$

Calculate the line currents:  $I_{aA} = \frac{V_a - V_{nN}}{Z_A + Z_{aA}}$      $I_{bB} = \frac{V_b - V_{nN}}{Z_B + Z_{bB}}$      $I_{cC} = \frac{V_c - V_{nN}}{Z_C + Z_{cC}}$

$I_{aA} = -1.333 - 0.951i$      $I_{bB} = 0.39 + 1.371i$      $I_{cC} = 0.943 - 0.42i$

$|I_{aA}| = 1.638$      $|I_{bB}| = 1.426$      $|I_{cC}| = 1.032$

$\frac{180}{\pi} \cdot \arg(I_{aA}) = -144.495$      $\frac{180}{\pi} \cdot \arg(I_{bB}) = 74.116$      $\frac{180}{\pi} \cdot \arg(I_{cC}) = -24.011$


Calculate the power delivered to the load:

$S_A = \overline{I_{aA}} \cdot I_{aA} \cdot Z_A$      $S_B = \overline{I_{bB}} \cdot I_{bB} \cdot Z_B$      $S_C = \overline{I_{cC}} \cdot I_{cC} \cdot Z_C$

$S_A = 10.727 + 10.727i$      $S_B = 4.064 + 16.257i$      $S_C = 4.262 + 8.525i$

$S_A + S_B + S_C = 19.053 + 35.508i$

**P12.4-7**

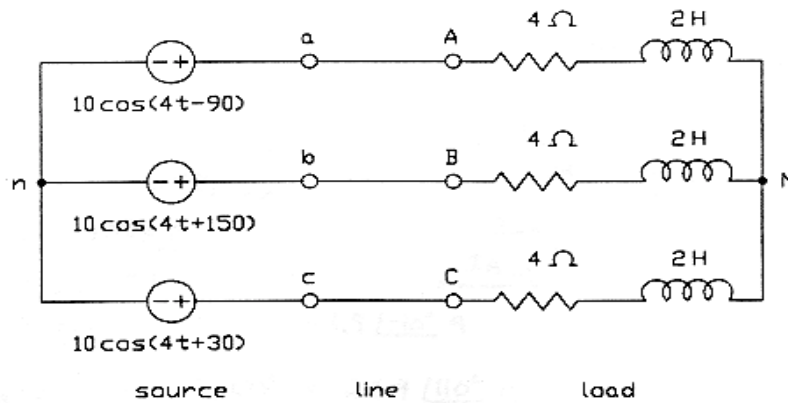

Mathcad analysis

Describe the three-phase source:  $V_p := 10$      $\omega := 4$

$V_a := V_p \cdot e^{j \frac{\pi}{180} - 90}$      $V_b := V_p \cdot e^{j \frac{\pi}{180} 150}$      $V_c := V_p \cdot e^{j \frac{\pi}{180} 30}$

Describe the three-phase load:  $Z_A := 4 + j \cdot \omega \cdot 2$      $Z_B := 4 + j \cdot \omega \cdot 2$      $Z_C := 4 + j \cdot \omega \cdot 2$

Describe the three-phase line:  $Z_{aA} := 0$      $Z_{bB} := 0$      $Z_{cC} := 0$

Calculate the voltage at the neutral of the load with respect to the neutral of the source:

$V_{nN} = \frac{(Z_{aA} + Z_A) \cdot (Z_{cC} + Z_C) \cdot V_b + (Z_{aA} + Z_A) \cdot (Z_{bB} + Z_B) \cdot V_c + (Z_{bB} + Z_B) \cdot (Z_{cC} + Z_C) \cdot V_a}{(Z_{aA} + Z_A) \cdot (Z_{cC} + Z_C) + (Z_{aA} + Z_A) \cdot (Z_{bB} + Z_B) + (Z_{bB} + Z_B) \cdot (Z_{cC} + Z_C)}$

$V_{nN} = 0$      $|V_{nN}| = 0$      $\frac{180}{\pi} \cdot \arg(V_{nN}) = -36.87$

Calculate the line currents:  $I_{aA} = \frac{V_a - V_{nN}}{Z_A + Z_{aA}}$      $I_{bB} = \frac{V_b - V_{nN}}{Z_B + Z_{bB}}$      $I_{cC} = \frac{V_c - V_{nN}}{Z_C + Z_{cC}}$

$$I_{aA} = -1 - 0.5i$$

$$I_{bB} = 0.067 + 1.116i$$

$$I_{cC} = 0.933 - 0.616i$$

$$|I_{aA}| = 1.118$$

$$|I_{bB}| = 1.118$$

$$|I_{cC}| = 1.118$$

$$\frac{180}{\pi} \cdot \arg(I_{aA}) = -153.435$$

$$\frac{180}{\pi} \cdot \arg(I_{bB}) = 86.565$$

$$\frac{180}{\pi} \cdot \arg(I_{cC}) = -33.435$$

Calculate the power delivered to the load:

$$S_A = \overline{I_{aA}} \cdot I_{aA} \cdot Z_A$$

$$S_B = \overline{I_{bB}} \cdot I_{bB} \cdot Z_B$$

$$S_C = \overline{I_{cC}} \cdot I_{cC} \cdot Z_C$$

$$S_A = 5 + 10i$$

$$S_B = 5 + 10i$$

$$S_C = 5 + 10i$$

$$S_A + S_B + S_C = 15 + 30i$$

### Section 12-6: The $\Delta$ - Connected Source and Load

#### P12.5-1

Given  $I_B = 50 \angle -40^\circ \text{ A} = I_L \angle \phi$


$$I_B = \sqrt{3} I_L \angle (\phi - 30^\circ) \text{ eqn. 19-15}$$

$$\therefore I_p = \frac{I_L}{\sqrt{3}} \angle (\phi + 30^\circ)$$

$$I_{BC} = \frac{50}{\sqrt{3}} \angle (-40^\circ + 30^\circ) = 28.9 \angle -10^\circ \text{ A}$$

$$I_{AB} = 28.9 \angle (-10^\circ + 120^\circ) = 28.9 \angle 110^\circ \text{ A}$$
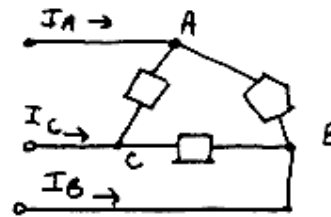
$$I_{CA} = 28.9 \angle (-10^\circ - 120^\circ) = 28.9 \angle -130^\circ \text{ A}$$




#### P12.5-2

2 delta loads in parallel so  $5 \parallel 20 = 4 \Omega$

$$V_L = V_p = 480 \text{ V}$$

$$\text{phase current } I_p = \frac{480}{4} = 120 \text{ A}$$
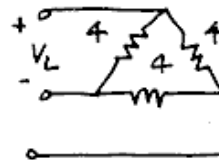
$$\text{line current } I_L = \sqrt{3} I_p = 208 \text{ A}$$



### Section 12-6: The Y- to $\Delta$ - Circuit

#### P12.6-1

$$\text{delta load } Z = 12 \angle 30^\circ = 12 \angle \theta$$

$$V_L = 208$$

$$I_p = \frac{208}{|Z|} = \frac{208}{12} = 17.32$$

$$\text{Let } V_{ab} = 208 \angle 0^\circ \rightarrow I_{ab} = 17.32 \angle -30^\circ$$


$$I_A = \sqrt{3} I_P \angle(\theta - 30^\circ) = \sqrt{3}(17.32) \angle(-30^\circ - 30^\circ) = 30 \angle -60^\circ$$

$$\text{then } I_B = 30 \angle(-60^\circ - 120^\circ) = 30 \angle -180^\circ$$

$$I_C = 30 \angle(-60^\circ + 120^\circ) = 30 \angle 60^\circ$$


$$P = \sqrt{3} V_L I_L \cos \theta = \sqrt{3} (208)(30) \cos 30^\circ = 9360W$$

P12.6-2

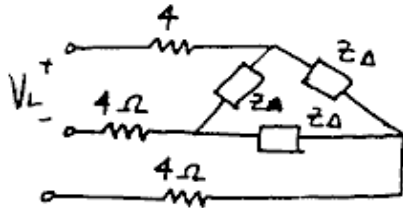

$$V_L = 480V \quad \text{Transform } Z_\Delta \Rightarrow Z_Y$$
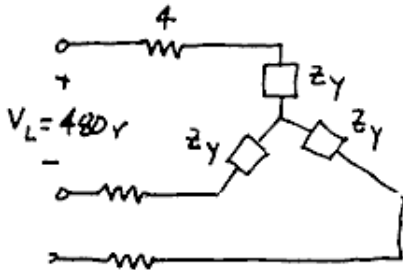
$$Z_\Delta = 39 \angle -40^\circ \Omega \quad Z_Y = \frac{Z_\Delta}{3} = 13 \angle -40^\circ = 9.96 - j8.36$$



$$Z_T = Z_Y + 4 = 13.96 - j8.36 = 16.3 \angle -30.9^\circ$$

$$\text{then } I_p = I_L = \frac{V_p}{Z_T} \quad \text{where } V_p = \frac{V_L}{\sqrt{3}}$$

$$V_a = \frac{480}{\sqrt{3}} \angle -30^\circ \quad I_A = \frac{\frac{480}{\sqrt{3}} \angle -30^\circ}{16.3 \angle -30.9^\circ} = 17 \angle 0.9^\circ$$

P12.6-3

$$Z_Y = 3 + j4 \quad V_L = 380 \Rightarrow V_p = V_L / \sqrt{3} = 220V$$

$$V_A = 220 \angle 0^\circ$$

$$V_{AB} = 380 \angle 30^\circ$$

$$V_B = 220 \angle -120^\circ$$

$$V_{BC} = 380 \angle -90^\circ$$

$$V_C = 220 \angle 120^\circ$$


$$V_{CA} = 380 \angle 150^\circ$$

$$I_A = \frac{220}{1 + j4} = 44 \angle -53.1^\circ$$

$$I_B = 44 \angle -173.1^\circ$$

$$I_C = 44 \angle 66.9^\circ$$

and  $I_A = I_a$

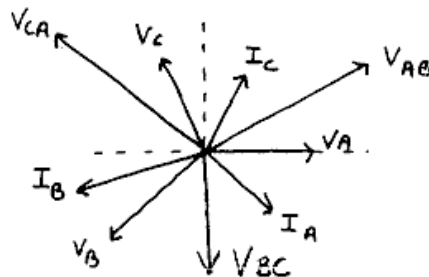

**P12.6-4** Delta load  $Z_{\Delta} = 9 + j12$       $V_L = 380V$

$V_{AB} = 380\angle 0^\circ$

$V_L = V_P$      So  $I_{AB} = \frac{380}{9 + j12} = 25.33\angle -53.1^\circ$

$I_L = \sqrt{3} I_P \angle (\phi - 30^\circ) = 43.9\angle -83^\circ$

Section 12-7: Balanced Three-Phase Circuits

**P12.7-1**      $V_\ell = 25kV$

$V_P = \frac{25}{\sqrt{3}} \times 10^3 V$      phase A:  $I_A = \frac{25/\sqrt{3} \times 10^3}{150\angle 25^\circ} \angle 0^\circ = 96\angle -25^\circ A$


$P = 3V_A I_A \cos\theta = 3\left(\frac{25}{\sqrt{3}} \times 10^3\right) 96 \cos(25^\circ) = \underline{3.77mW}$

**P12.7-2**      $V_L = 45kV$       $Z_y = 10 + j20$

$Z_L = 2\Omega$       $Z_{\Delta} = 50\Omega$       $Z_{\Delta} \Rightarrow \hat{Z}_y = \frac{50}{3}$

One per-phase circuit is:

$V_P = \frac{45}{\sqrt{3}} kV = 26kV$

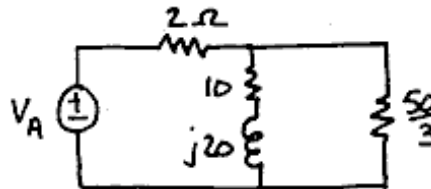

Use  $V_A = 26kV\angle 0^\circ$

$Z_{eq} = \frac{(10 + j20)(50/3)}{10 + 50/3 + j20} = 10 + j5$

$Z_T = 2 + Z_{eq} = 12 + j5 = 13\angle 22.6^\circ$


$I_L = \frac{26kV}{13} = 2kA$  and  $V_L = 45kV$

$P_{\text{loss in lines}} = |I_L|^2 (2\Omega) = 8mW$  for each line

$P_T = \sqrt{3} V_L I_L \cos\theta = \sqrt{3} (45 \times 10^3) (2 \times 10^3) \cos 22.6^\circ = 144mW = 3P_{\text{phase}}$

$\therefore \% \text{ lost} = \frac{8 \times 3 \times 100\%}{144} = \underline{16.6\%}$

**P12.7-3**

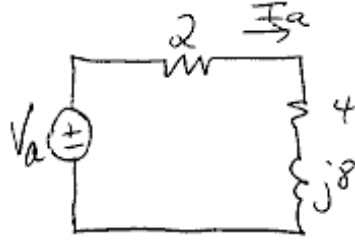

$$V_a = 5\angle 30^\circ \text{ V} \quad |V_L| = 5 \text{ V}$$

$$I_a = \frac{V_a}{Z_T} = \frac{5\angle 30^\circ}{6 + j8} = 0.5\angle -23^\circ \text{ A} \quad \therefore |I_a| = 0.5 \text{ A}$$

$$P_T = \sqrt{3} V_L I_L \cos \theta$$

$$= \sqrt{3} (5) (0.5) \cos(-30 - 23^\circ) = 2.6 \text{ W}$$

$$P_{\text{line}} = |I_L|^2 (2\Omega) = (0.5)^2 (2) = 0.5 \text{ W}$$

$$\therefore P_{\text{load}} = P_{\text{total}} - P_{\text{line}} = 2.6 - 0.5 = \underline{1.9 \text{ W}}$$

**Section 12-8: Power in a Balanced Load**

**P12.8-1**  $P = \sqrt{3} V_L I_L \cos \theta \quad V_L = 208, \quad I_L = 3$

Need power factor & need angle between  $I_B$  and  $V_B$

Assuming a Y load (or transformed to a Y load)

$$V_B \text{ leads } V_{CB} \text{ by } 120^\circ + 30^\circ = 150^\circ$$

$$\text{So } V_B = |V_B| \angle \theta = |V_B| \angle 165^\circ \text{ and } I_B = 3 \angle 110^\circ$$

$$\text{So } \theta = 165 - 110 = 55^\circ$$

$$\text{Then } P = \sqrt{3} (208) (3) \cos 55^\circ = \underline{620 \text{ W}}$$

(OR)

$$V_{CB} = 208 \angle 15^\circ = V_L$$

$$I_B = 3 \angle 110^\circ = I_L = I_P$$

$$V_B = \frac{208}{\sqrt{3}} \angle 15 - 30^\circ = 120 \angle -15^\circ = V_P$$

$$P = 3 V_P I_P \cos \theta = 3 (120) (3) \cos(125) = \underline{619 \text{ W}}$$

**P12.8-2**

$$V_L = 480 \quad \eta = .85 \quad \text{pf} = .8 = \cos \theta \quad \text{so } \theta = 36.9^\circ$$

$$P_{in} = \frac{P_{out}}{\eta} = \frac{20(745.7)}{.85} = 17.55 \text{ kW} \quad \text{where } 1 \text{ hp} = 745.7 \text{ kW} = \sqrt{3} V_L I_L \cos \theta$$

$$\text{Thus } I_L = \frac{17.55 \times 10^3}{\sqrt{3}(480)(.8)} = 26.4 \text{ A}$$

$$\text{Assume Y connected load } I_A = 26.4 \angle -36.9^\circ \text{ if } V_A = 480 \angle 0^\circ$$



**P12.8-3**

$$V_L = 220\text{V} \quad P_T = 1500\text{W} \quad \text{pf} = .8 \text{ lagging}$$

$$\text{a) } \Delta \text{ connected : } P_T = \sqrt{3} V_L I_L \text{pf} \quad \Rightarrow I_L = \frac{1500}{\sqrt{3}(220)(.8)} = 4.92$$

$$\text{so } |Z_{\text{ph}}| = \frac{220}{2.84} = 77.44 \quad I_P = \frac{I_L}{\sqrt{3}} = 2.84$$

$$\underline{Z_{\Delta} = 77.44 \angle \cos^{-1}(.8) = 77.44 \angle 36.9^\circ \Omega}$$

$$\text{b) } Y \text{ connected : } I_L = 4.92 \text{ as above } I_L = I_P$$

$$V_P = \frac{V_L}{\sqrt{3}} = 127 \text{ V}$$

$$\therefore |Z_{\text{ph}}| = \frac{127}{4.92} = 25.8$$

$$\text{So } \underline{Z_Y = 25.8 \angle 36.9^\circ \Omega}$$

**P12.8-4**

Parallel  $\Delta$  loads

$$Z_{\Delta} = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{(40 \angle 30^\circ)(50 \angle -60^\circ)}{40 \angle 30^\circ + 50 \angle -60^\circ} = 31.2 \angle -8.7^\circ \Omega$$

$$V_L = V_P, \quad I_P = \frac{V_P}{|Z_{\Delta}|} = \frac{600}{31.2} = 19.2 \text{ A}, \quad I_L = \sqrt{3} I_P = 33.3 \text{ A}$$

$$\text{So } P = \sqrt{3} V_L I_L \text{pf} = \sqrt{3} (600) (33.3) \cos(-8.7^\circ) = \underline{34.2 \text{ kW}}$$

**P12.8-5**

$$\tilde{S}_1 = 27.3 + j 27.85$$

$$\tilde{S}_2 = 15.0 - j 70.57$$

$$\tilde{S}_{3\phi} = 42.3 - j 42.72 \text{ kVA} \Rightarrow \tilde{S}_{\phi} = 14.1 - j 14.24 \text{ kVA} = \tilde{S}_{3\phi}/3$$


$$|\tilde{V}_{LP}| = \frac{208}{\sqrt{3}} = 120 \text{ V} = |V_P|$$

$$\tilde{I}_L = \frac{(14100 + j 14240)}{120} = 117.5 + j 118.7 \text{ A} = 167 \angle 45.3^\circ \text{ A}$$

$$\begin{aligned} \text{Thus } \tilde{V}_{S\phi} &= 120 \angle 0^\circ + (0.038 + j 0.072)(117.5 + j 118.7) = 115.9 + j 12.9 \\ &= 116.6 \angle 6.4^\circ \text{ V (phase-neutral)} \end{aligned}$$

$$\therefore |\tilde{V}_{SL}| = \sqrt{3} (116.6) = \underline{202.0 \text{ V}}$$

P12.8-6

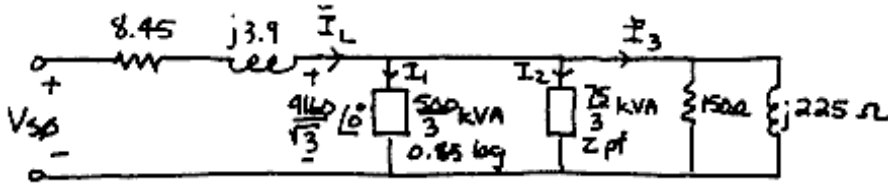

$$\tilde{I}_1 = \frac{500/\sqrt{3} \angle -\cos^{-1} 0.85}{2402} = 58.98 - j 36.56 \text{ A}, \quad \tilde{I}_2 = \frac{25 \angle 90^\circ}{2402} = j 10.4 \text{ A}$$

$$\tilde{I}_3 = \frac{2402}{150} + \frac{2402}{j 225} = 16 - j 10.7 \text{ A}$$

$$\tilde{I}_L = \tilde{I}_1 + \tilde{I}_2 + \tilde{I}_3 = 75 - j 36.8 \text{ A}$$

$$\tilde{V}_{S\phi} = 2402 \angle 0^\circ + (8.45 + j 3.9)(75 - j 36.8) = 3179 \angle -0.3^\circ$$

$$\therefore |V_{SL}| = \sqrt{3} (3179) = \underline{5506 \text{ V}}$$

P12.8-7

a)  $\tilde{S}_1 = 1.125 + j 0.9922 \quad V_L = \frac{4160}{\sqrt{3}} \quad \phi \text{ refers to per-phase}$

$$\tilde{S}_2 = 2.000 + j 1.500$$

$$\tilde{S}_L = 3.125 + j 2.4922 \Rightarrow \tilde{S}_{L\phi} = 1.042 + j 0.831 \text{ MVA/phase}$$

$$\tilde{I}_L = \frac{(1.042 - j 0.831) \times 10^6}{2402} = 4.337 - j 345.9 \text{ A} = 554.7 \angle -38.6^\circ \text{ A}$$


$$\tilde{V}_{S\phi} = 2402 \angle 0^\circ + (0.4 + j 0.8)(4.337 - j 345.9) = 2859.6 \angle 4.2^\circ \text{ V}$$

$$\therefore |V_{SL}| = \sqrt{3} (2859.6) = \underline{4953 \text{ V}}$$

b)  $P_S = \sqrt{3} (4953)(554.7) \cos(4.2^\circ + 38.6^\circ) = \underline{3.49 \text{ MW}}$

c)  $\text{efficiency} = \eta = \frac{3.125}{3.49} \times 100\% = \underline{89.5\%}$

**P12.8-8**

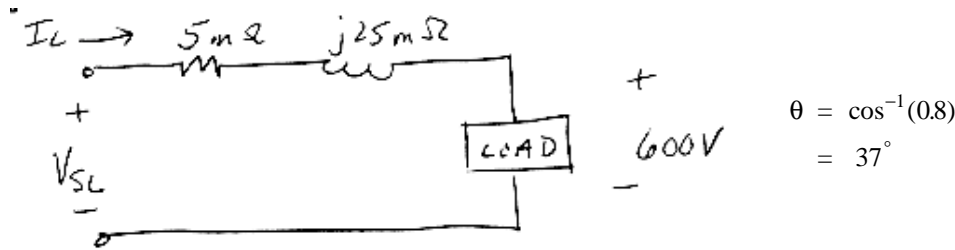

$$P_{\text{LOAD}} = \sqrt{3} V_L I_L \text{ pf}$$

$$|I_L| = \frac{P_{\text{LOAD}}}{\sqrt{3} V_L \text{ pf}} = \frac{480 \text{ k}}{\sqrt{3} (600) (0.8)} = 577 \angle -37^\circ = 461.6 - j 346.2$$

$$V_{\text{SL}} = 600 \angle 0^\circ + (5\text{m} + j 25\text{m}) (461.6 - j 346.2)$$

$$= \underline{610.1 + j 9.8 = 611 \angle 0.92^\circ \text{ V}}$$

$$\text{pf} = \cos(\theta_V - \theta_I) = \cos(0.92 - (-37)) = \underline{0.789}$$

**Section 12-9: Two-Wattmeter Power Measurement**

**P12.9-1** Assume motor is a balanced load  $V_L = 440$ ,  $I_L = 52.5$

$$P_{\text{in}} = \frac{P_{\text{out}}}{\eta} \quad \eta = .746$$

$$P_T = P_{\text{in}} = \frac{(20\text{hp})(746 \text{ W/hp})}{.746} = 20 \text{ kW}$$

$$\text{also } P_T = \sqrt{3} V_L I_L \cos \theta \quad \text{then } \cos \theta = \frac{20 \times 10^3}{\sqrt{3} (440) (52.5)} = 0.50$$

$$\text{so } \theta = + 60^\circ$$

Use eqn. 12.9-5

$$P_T = V_L I_L [\cos(\theta + 30^\circ) + \cos(\theta - 30^\circ)]$$

$$\text{Then } W_A = 0$$

$$W_C = 20 \text{ kW}$$

**P12.9-2**  $V_L = 4000$        $Z_\Delta = 40 + j 30 = 50 \angle 36.9^\circ$

$$V_P = V_L = 4000$$

$$I_P = \frac{V_P}{50} = \frac{4000}{50} = 80\text{A} \quad I_L = \sqrt{3} I_P = 138.6 \text{ A}$$

$$\text{pf} = \cos \theta = \cos(36.9^\circ) = .80$$

$$P_1 = V_L I_L \cos(\theta + 30^\circ) = 4000 (138.6) \cos 66.9^\circ = 217.5 \text{ kW}$$

$$P_2 = V_L I_L \cos(\theta - 30^\circ) = 4000 (138.6) \cos 6.9^\circ = 550.4 \text{ kW}$$


$$P_T = P_1 + P_2 = 767.9 \text{ kW}$$

$$\text{Check : } P_T = \sqrt{3} I_L V_L \cos \theta = \sqrt{3} (4000) (138.6) \cos 36.9^\circ$$

$$= 768 \text{ kW} \quad \text{which checks}$$

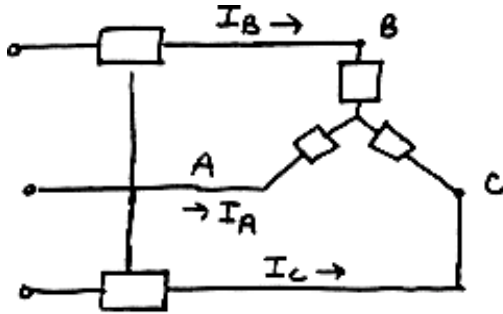**P12.9-3**

$$V_L = 200\text{V, Y load} \Rightarrow z = 70.7\angle 45^\circ$$



$$V_p = \frac{200}{\sqrt{3}} = 115.47 \text{ V}$$

$$V_A = 115.47\angle 0^\circ \quad V_B = 115.47\angle -120^\circ$$

$$I_A = \frac{V_A}{Z} = \frac{115.47\angle 0^\circ}{70.7\angle 45^\circ} = 1.633\angle -45^\circ$$

$$I_B = 1.633\angle -165^\circ \quad I_C = 1.633\angle 75^\circ$$

$$P_T = \sqrt{3} V_L I_L \cos \theta = \sqrt{3} (200) (1.633) \cos 45^\circ = 400 \text{ W}$$

$$P_B = V_{AC} I_A \cos \theta_1 = 200 (1.633) \cos (45^\circ - 30^\circ) = 315.47 \text{ W}$$

$$P_C = V_{BC} I_B \cos \theta_2 = 200 (1.633) \cos (45^\circ + 30^\circ) = 84.53 \text{ W}$$

**P12.9-4**

$$V_L = 208\text{V}$$

$$Z_Y = 10\angle -30^\circ \quad Z_\Delta = 15\angle 30^\circ$$

$$\text{Convert } Z_\Delta \text{ to } Z_{\hat{Y}} \rightarrow Z_{\hat{Y}} = \frac{Z_\Delta}{3} = 5\angle 30^\circ$$

$$\text{then } Z_{\text{eq}} = \frac{(10\angle -30^\circ)(5\angle 30^\circ)}{10\angle -30^\circ + 5\angle 30^\circ} = \frac{50\angle 0^\circ}{13.228\angle -10.9^\circ} = 3.78\angle 10.9^\circ$$

$$V_p = \frac{208}{\sqrt{3}} = 120\text{V}$$

$$V_A = 120\angle 0^\circ \Rightarrow I_A = \frac{120\angle 0^\circ}{3.78\angle 10.9^\circ} = 31.75\angle -10.9^\circ$$

$$I_B = 31.75\angle -130.9^\circ$$

$$I_C = 31.75\angle 109.1^\circ$$

$$P_T = \sqrt{3} V_L I_L \cos \theta = \sqrt{3} (208) (31.75) \cos (10.9) = 11.23 \text{ kW}$$

$$W_1 = V_L I_L \cos(\theta - 30^\circ) = 6.24 \text{ kW}$$

$$W_2 = V_L I_L \cos(\theta + 30^\circ) = 4.99 \text{ kW}$$

**P12.9-5**  $W_1 = W_A$       Let  $W_1 = 920$        $W_2 = 460$   
 $P_T = W_1 + W_2 = 920 + 460 = 1380 \text{ W}$   
 $P_T = \sqrt{3} V_L I_L \cos \theta$  and  $V_L = 120 \text{ V}$   
 $\tan \theta = \sqrt{3} \frac{P_2 - P_1}{P_2 + P_1} = \sqrt{3} \frac{(-460)}{1380} = -0.577 \Rightarrow \theta = -30^\circ$   
 $P_T = \sqrt{3} V_L I_L \cos \theta$  so  $I_L = \frac{P_T}{\sqrt{3} V_L \cos \theta} = 7.67 \text{ A}$   
 $I_P = \frac{I_L}{\sqrt{3}} = 4.43 \therefore |Z_\Delta| = \frac{120}{4.43} = 27.1 \Omega$  or  $\underline{Z_\Delta = 27.1 \angle -30^\circ}$

P12.9-6

$$Z = 0.868 + j4.924 = 5 \angle 80^\circ \quad \theta = 80^\circ \quad V_L = 380 \text{ V}, V_P = \frac{380}{\sqrt{3}} = 219.4 \text{ V}$$

$$I_L = I_P \text{ and } I_P = \frac{V_P}{Z} = 43.9 \text{ A}$$

$$W_1 = (380)(43.9) \cos(\theta - 30^\circ) = 10,723$$

$$W_2 = (380)(43.9) \cos(\theta + 30^\circ) = -5706$$

$$\therefore P_T = 5017 \text{ W}$$

### Verification Problems

**VP 12-1** Y-Y connection

$$|V_P| = \frac{416}{\sqrt{3}} = 240 \text{ V} = |V_A|$$

$$Z = 10 + j4 = 10.77 \angle 21.8^\circ \Omega$$

$$|I_A| = \frac{|V_A|}{Z} = \frac{240}{10.77} = \underline{22.28 \text{ A}}$$

$$P = \sqrt{3} V_L I_L \cos \theta = \sqrt{3} (416) (22.28) \cos(-21.8^\circ) = \underline{14.9 \text{ kW}}$$

**VP 12-2**


$$\Delta \text{ connection } V_L = V_P = 240 \text{ V}$$

$$Z = 40 + j30 = 50 \angle 36.9^\circ \Omega$$

$$I_P = \frac{V_P}{Z_\Delta} = \frac{240}{50 \angle 36.9^\circ} = \underline{4.8 \angle -36.9^\circ \text{ A}}$$

## PSpice Problems

### SP 12-1

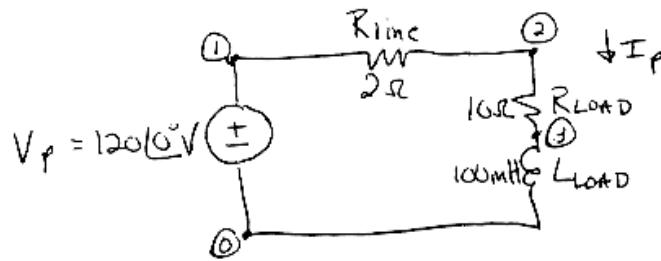


Input:

```
Vs 1 0 ac 120 0
Rline 1 2 2
Rload 2 3 10
Lload 3 0 100m
.ac lin 1 60 60
.print ac Im(Rline) Ip(Rline)
.end
```

Output:

FREQ	IM(Rline)	IP(Rline)
6.000E+01	3.033E+00	-7.234E+01

### SP 12-2

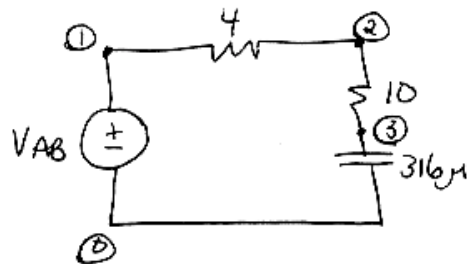

$$f = 60\text{Hz}$$

$$-j8.4 = \frac{-j}{\omega C} \Rightarrow C = 316\mu\text{F}$$


INPUT:

```
Vs 1 0 ac 277 -30
Rline 1 2 4
Rload 2 3 10
Cload 3 0 316u
.ac lin 1 60 60
.print ac Im(Rline) Ip(Rline)
.end
```

OUTPUT:

FREQ	IM(Rline)	IP(Rline)
6.000E+01	1.697E+01	9.464E-01

SP 12-3

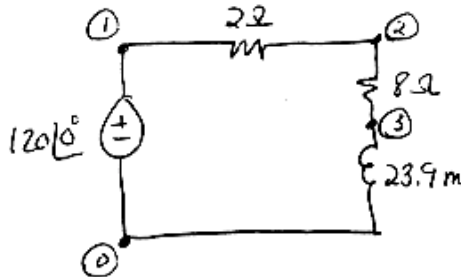

$$f = 60 \text{ Hz}, \omega = 377 \frac{\text{rad}}{\text{sec}}$$

$$j9 = j\omega L$$

$$L = 23.9 \text{ mH}$$

Input:

```
Vs 1 0 ac 120 0
Rline 1 2 2
Rload 2 3 8
Lload 3 0 24m
.ac lin 1 60 60
.print ac Im(Rline) Ip(Rline)
.end
```

Output:

```
FREQ      IM(Rline)      IP(Rline)
6.000E+01  8.898E+00      -4.214E+01
```

Design Problems

DP 12-1

$$P_{\text{per phase}} = 400, \text{ pf} = \cos \theta = \cos 20^\circ \Rightarrow \theta = 20^\circ$$

$$400 = \frac{208}{\sqrt{3}} I_L \cos 20^\circ \Rightarrow I_L = 3.5 \text{ A}$$

$$\text{each } \Delta \text{ phase: } I_{\Delta} = \frac{I_L}{\sqrt{3}} = 2.04 \text{ A}$$

$$|Z| = \frac{V_L}{I_{\Delta}} = \frac{208}{2.04} = 101.8 \Omega$$

$$\text{so } \underline{Z} = 101.8 \angle 20^\circ \Omega$$

DP 12-2

$$V_L = 240 \text{ V}$$

$$P_A = V_L I_L \cos (30^\circ + \theta) = 1440 \text{ W}$$

$$P_C = V_L I_L \cos (30^\circ - \theta) = 0 \text{ W}$$

$$\text{now } \cos \phi = 0, \text{ when } \phi = 30^\circ - \theta = 90^\circ \text{ or } \theta = -60^\circ$$

$$\text{then } 1440 = 240 (I_L) \cos (-30^\circ) \Rightarrow I_L = 6.93 \text{ A}$$

$$I_L = I_P = \frac{V_P}{Z}$$

$$\text{So } |Z| = \frac{V_P}{I_P} = \frac{240/\sqrt{3}}{6.93} = 20 \Omega$$

$$\text{Thus } \underline{Z} = 20 \angle -60^\circ \Omega$$

**DP 12-3**

$$V_L = 480\text{V}$$

$$P_{\text{in}} = \frac{P_0}{\eta} = \frac{100(746)}{.8} = 93.2 \text{ kW}$$

$$\text{correction } C = P_{\text{in}} \frac{[\tan(\cos^{-1}.75) - \tan(\cos^{-1}.9)]}{3(377)(480)^2} = \underline{160 \mu\text{F}}$$

where pfc = .9 and pf = .75

**DP 12-4**

$$V_L = 4 \text{ kV} \quad Z_L = \frac{4}{3} \Omega$$

If  $n_2 = 25 \rightarrow 25 : 1$  step down at load to 4 kV

then  $V_2 = 100 \text{ kV}$

$$\Rightarrow I_L \text{ at load} = \frac{4 \times 10^3}{Z_L} = 3 \text{ kA}$$

The line current in  $2.5 \Omega$  is  $|I| = \frac{3 \text{ kA}}{25} = 120 \text{ A}$

Thus  $V_1 = (R + jX)I + V_2$

$$= (2.5 + j40)(120) + 100 \times 10^3 = 100.4 \angle 2.7^\circ \text{ kV}$$

Step need :  $n_1 = \frac{100.4 \text{ kV}}{20 \text{ kV}} = 5.02 \cong 5$

$$P_{\text{loss}} = |I|^2 R = |120|^2 (2.5) = 36 \text{ kW}, \quad P = (4 \times 10^3)(3 \times 10^3) = 12 \text{ MW}$$

$$\eta = \frac{12 - .036}{12} \times 100\% = 99.7\% \text{ to load}$$