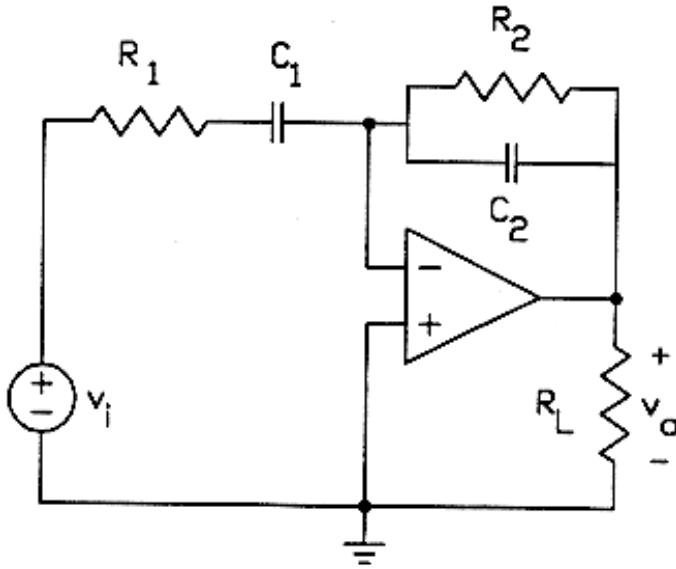


P13.4-16

Pick the appropriate circuit from Table 13.4-2.



$$H(\omega) = -\frac{k}{\left(1+j\frac{\omega}{p_1}\right)\left(1+j\frac{\omega}{p_2}\right)}$$

where

$$k = C_1 R_2$$

$$p_1 = \frac{1}{C_1 R_1}$$

$$p_2 = \frac{1}{C_2 R_2}$$

We require

$$200 = p_1 = \frac{1}{C_1 R_1}$$


$$500 = p_2 = \frac{1}{C_2 R_2}$$

$$34\text{dB} = 50 = k = C_1 R_2$$


Pick  $C_1 = 1\mu\text{F}$ . Then  $R_1 = 5\text{k}\Omega$ ,  $R_2 = 50\text{k}\Omega$  and  $C_2 = 0.04\mu\text{F}$ .

P13.4-17
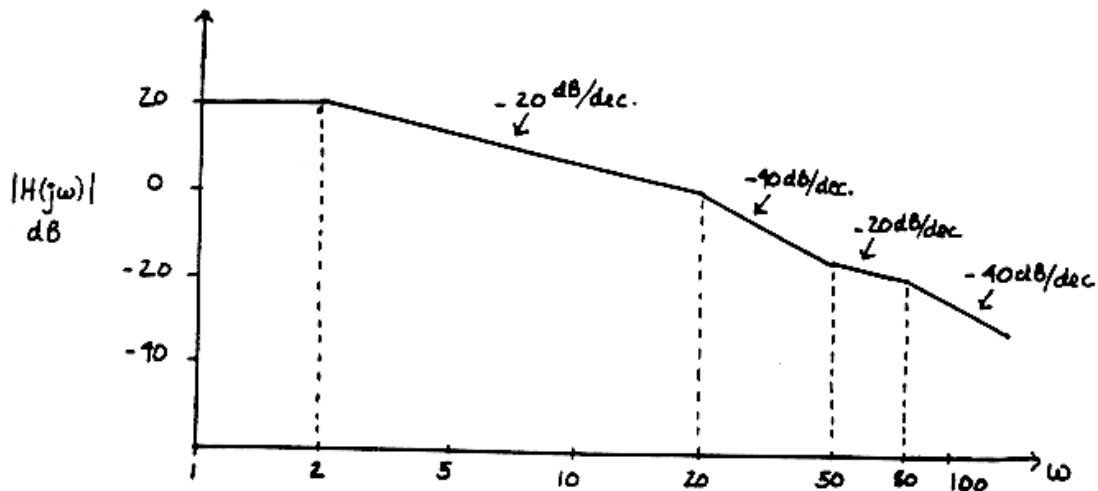
$$H(j\omega) = \frac{10(j\omega/50+1)}{(j\omega/2+1)(j\omega/50+1)(j\omega/80+1)}$$


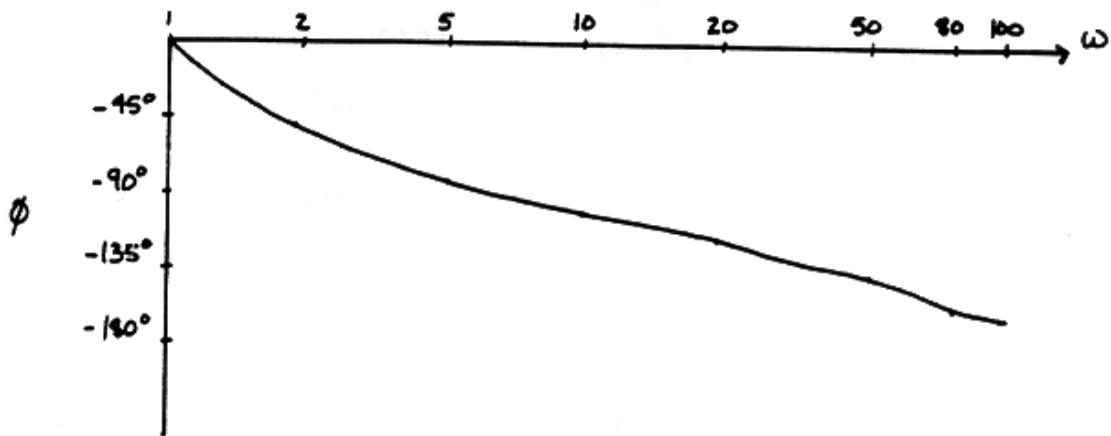
$$\phi = \tan^{-1} \omega/50 - \tan^{-1} \omega/2 - \tan^{-1} \omega/20 - \tan^{-1} \omega/80$$



**P13.4-18**

$$H_{1,2} = -\frac{R_2/R_1}{1+j\omega R_2 C} \Rightarrow H_{\text{Total}} = H_{1,2}^2 = (R_2/R_1)^2 \left( \frac{1}{1+j\omega R_2 C} \right)^2$$

(a) At low frequency,

$$H_T = (R_2/R_1)^2 \therefore \text{for } H_T = 1, \text{ need } R_1 = R_2$$

Now also  $\omega_1 = 1000 = 1/R_2 C$ , so let  $C = 1\mu\text{F}$


$$\therefore R_1 = R_2 = 1/(1000)(10^{-6}) = 1\text{k}\Omega$$

(b) At  $\omega = 10,000$

$$|H| = \frac{1}{1+(\omega R_2 C)^2} = \frac{1}{1+[(10^4)(10^3)(10^{-6})]^2} = 10^{-2}$$

$$\Rightarrow 20\log |H| = 20\log 10^{-2} = \underline{-40\text{dB}}$$

**P13.4-19**

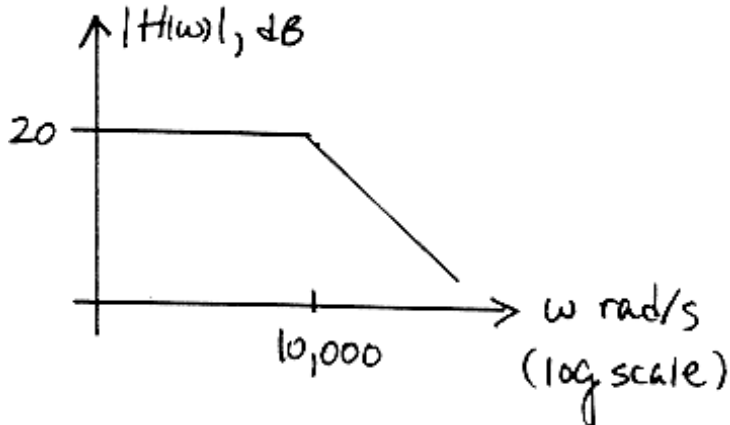


$$(a) H(\omega) = \frac{V_o(\omega)}{V_s(\omega)} = -\frac{R_2/R_1}{1+j\omega R_2 C} = -\frac{10}{1+j\frac{\omega}{10,000}}$$

(b)  $10 = 20\text{dB}$

(c)  $10,000 \text{ rad/sec}$

P13.4-20

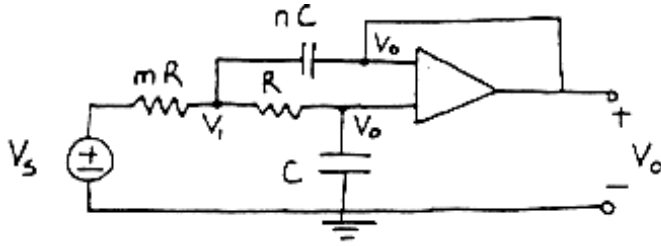

Assume  $V_i \approx 0$ , then  $V_+ = V_- = V_o$   
 Use  $s = j\omega$

Voltage divider yields :  $V_o = V_1 \frac{1/sC}{R+1/sC} \Rightarrow V_1 = (1+sRC)V_o$

KCL at  $V_1$ :  $(V_1 - V_s)/mR + (V_1 - V_o)/R + (V_1 - V_o)snC = 0$


Plugging  $V_1$  into above yields

$$V_o \left[ \frac{1}{mR} + sC + \frac{sC}{m} + s^2 nRC^2 \right] = \frac{V_s}{mR}$$


$$\therefore \frac{V_o}{V_s} = \frac{1}{1 + s(m+1)RC + nmR^2C^2s^2}$$

$$\Rightarrow H(j\omega) = \frac{V_o}{V_s} = \frac{1}{1 - (\omega/\omega_0)^2 + j(\omega/Q\omega_0)} \quad \text{where } \omega_0 = \frac{1}{\sqrt{mnRC}}$$

$$Q = \frac{\sqrt{mn}}{m+1}$$

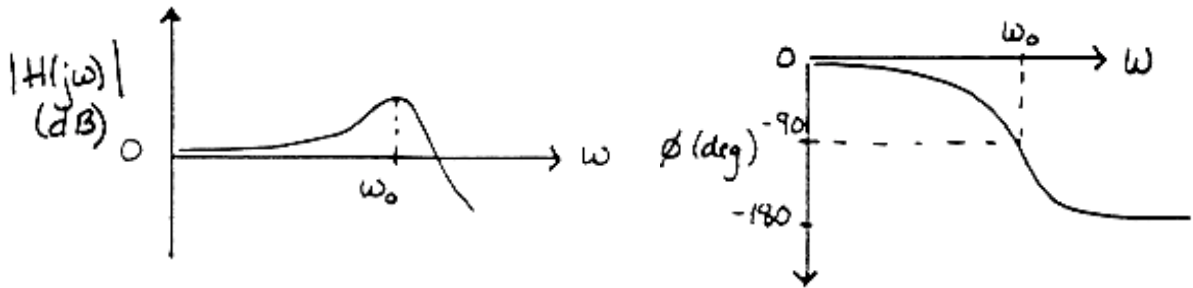


P13.4-21

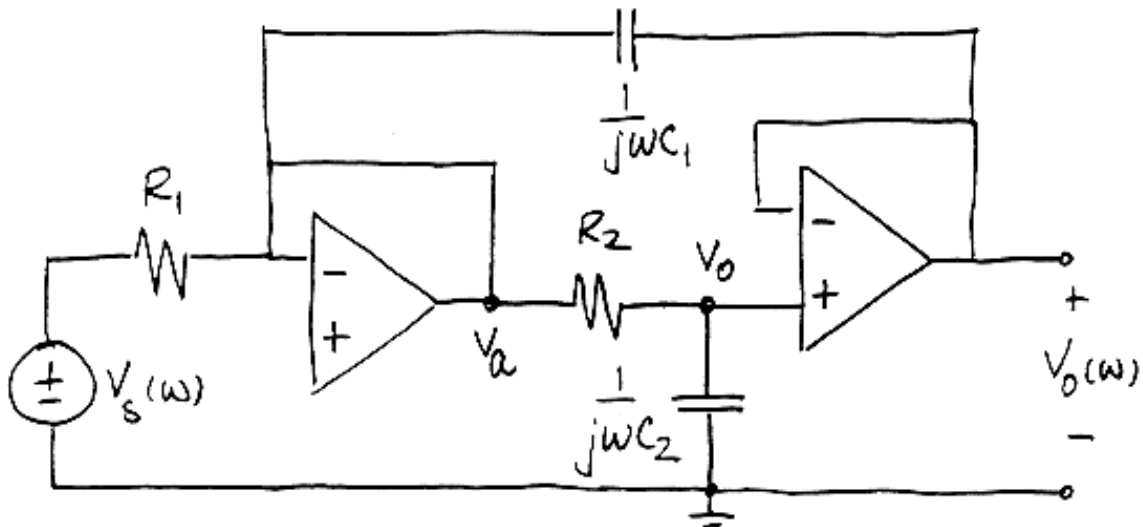

$$\left. \begin{aligned} V_o(\omega) &= \frac{\frac{1}{j\omega C_2}}{R + \frac{1}{j\omega C_2}} V_a(\omega) \\ 0 &= \frac{V_a(\omega) - V_s(\omega)}{R_1} + j\omega C_1(V_a(\omega) - V_o(\omega)) \end{aligned} \right\} \Rightarrow V_o(1 + j\omega C_1 R_1)(1 + j\omega C_2 R_2) = j\omega C_1 R_1 V_o + V_s$$

$$T(\omega) = \frac{V_o(\omega)}{V_s(\omega)} = \frac{1}{1 + C_2 R_2 j\omega - \omega^2 C_1 C_2 R_1 R_2} = \frac{1}{-\omega^2 + 8j\omega + 1}$$

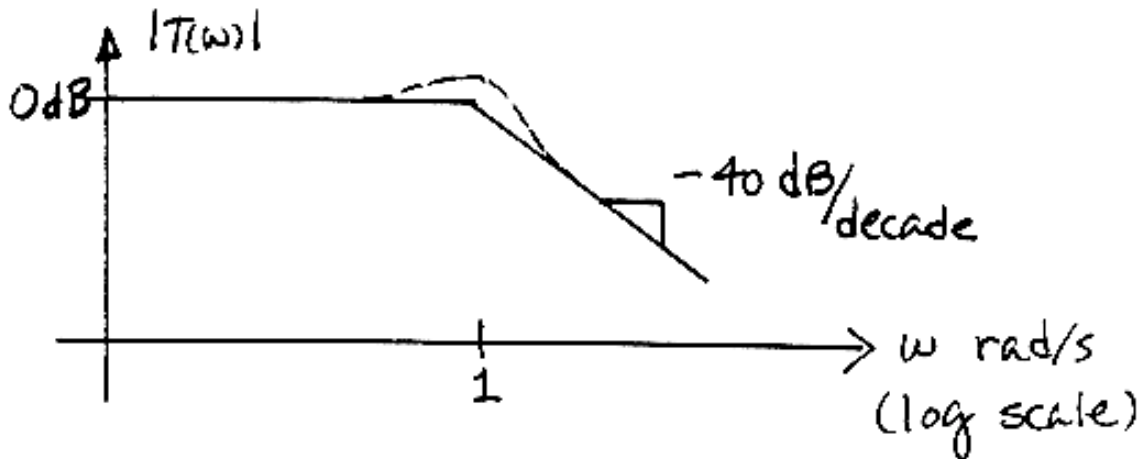Second order poles with  $\omega_o = 0$  and  $\delta = .4$



### Section 13-5: Resonant Circuits

P13.5-1

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\left(\frac{1}{120}\right)\left(\frac{1}{30} \times 10^{-6}\right)}} = 60 \text{ k rad/sec}$$

$$Q = R\sqrt{\frac{C}{L}} = 10,000 \sqrt{\frac{\frac{1}{30} \times 10^{-6}}{\frac{1}{120}}} = 20$$

$$\omega_1 = -\frac{\omega_0}{2Q} + \sqrt{\left(\frac{\omega_0}{2Q}\right)^2 + \omega_0^2} = 58.52 \text{ k rad/s}$$

$$\omega_2 = \frac{\omega_0}{2Q} + \sqrt{\left(\frac{\omega_0}{2Q}\right)^2 + \omega_0^2} = 61.52 \text{ k rad/s}$$

$$BW = \frac{1}{RC} = \frac{1}{(10000)\left(\frac{1}{30} \times 10^{-6}\right)} = 3 \text{ k rad/s}$$

$$\text{Notice that } BW = \omega_2 - \omega_1 = \frac{\omega_0}{Q}$$

**P13.5-2**

$$R = k = |H(\omega_0)| = \frac{8}{20 \cdot 10^{-3}} = 400 \Omega$$

$$\omega_0 = 1000 \text{ rad/s}$$

$$|H(\omega)| = \frac{k}{\sqrt{1+Q^2 \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2}}$$

$$\text{At } \omega = 897.6 \text{ rad/s, } |H(\omega)| = \frac{4}{20 \cdot 10^{-3}} = 200, \text{ so}$$

$$200 = \frac{400}{\sqrt{1+Q^2 \left( \frac{897.6}{1000} - \frac{1000}{897.6} \right)^2}} \Rightarrow Q = 8$$

Now

$$\left. \begin{array}{l} \frac{1}{\sqrt{LC}} = \omega_0 = 1000 \\ 400 \sqrt{\frac{C}{L}} = Q = 8 \end{array} \right\} \Rightarrow \begin{array}{l} C = 20 \mu\text{F} \\ L = 50 \text{ mH} \end{array}$$

**P13.5-3**

$$\omega_0 = \frac{1}{\sqrt{LC}} = 10^5 \text{ rad/s, } Q = \frac{1}{R} \sqrt{\frac{L}{C}} = 10, \text{ BW} = \frac{R}{L} = 10^4 \text{ rad/s}$$

**P13.5-4**

$$\omega_0 = \frac{1}{\sqrt{LC}} = 10^4 \text{ rad/s, } Q = \frac{1}{R} \sqrt{\frac{L}{C}} = 10, \text{ BW} = \frac{R}{L} = 10^3 \text{ rad/s}$$

**P13.5-5**

$$R = Z(\omega_0) = 100 \Omega$$

$$\frac{1}{100C} = \text{BW} = 500 \Rightarrow C = 20 \mu\text{F}$$

$$\frac{1}{\sqrt{(20 \cdot 10^{-6})L}} = \omega_0 = 2500 \Rightarrow L = 8 \text{ mH}$$


**P13.5-6**

$$R = \frac{1}{Y(\omega_0)} = 100 \Omega$$

$$\frac{100 \Omega}{L} = \text{BW} = 500 \Rightarrow L = 0.2 \text{ H}$$

$$\frac{1}{\sqrt{(0.2)C}} = \omega_0 = 2500 \Rightarrow C = 0.8 \mu\text{F}$$

P13.5-7

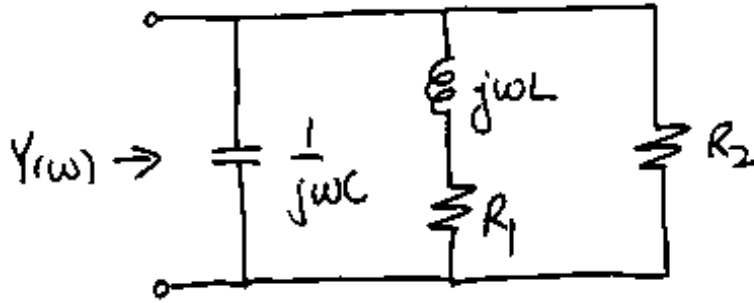


$$\begin{aligned}
 Y(\omega) &= j\omega C + \frac{1}{R_1 + j\omega L} + \frac{1}{R_2} \\
 &= \frac{(R_1 + R_2 - \omega^2 CLR_2) + j\omega(L + CR_1R_2)}{R_2(R_1 + j\omega L)} \times \frac{R_1 - j\omega L}{R_1 - j\omega L} \\
 &= \frac{R_1(R_1 + R_2 - \omega^2 CLR_2) - \omega^2 L(L + CR_1R_2) + j\omega R_1(LCR_1R_2) - j\omega L(R_1 + R_2 - \omega^2 CLR_2)}{R_2(R_1 - \omega^2 L^2)}
 \end{aligned}$$

$\omega = \omega_0$  is the frequency at which the imaginary part of  $Y(\omega)$  is zero:

$$R_1(LCR_1R_2) - L(R_1 + R_2 - \omega_0^2 CLR_2) = 0$$

$$\omega_0 = \sqrt{\frac{LR_2 - CR_1^2R_2}{CL^2R_2}} = 12.9 \text{ M rad/sec}$$

P13.5-8

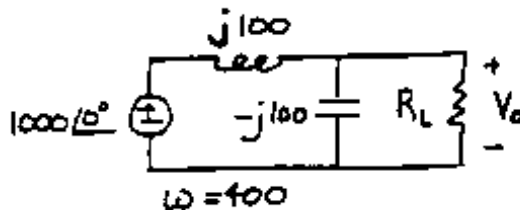


(a) Using voltage divider

$$V_o = (1000\angle 0^\circ) \frac{(100)(-j100)}{(100)(-j100) + j100} = (1000\angle 0^\circ) \frac{100/\sqrt{2}\angle -135^\circ}{100/\sqrt{2}\angle -135^\circ + j100} = \frac{10^5/\sqrt{2}\angle -135^\circ}{50\sqrt{2}\angle -135^\circ} = 1000\angle 90^\circ$$

$\therefore |V_o| = 1000V$


(b) Do a source transformation to obtain

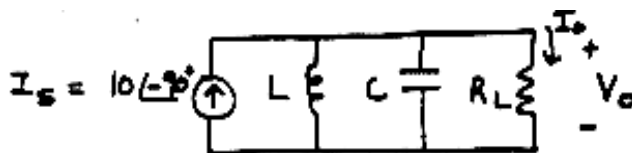

So have an RLC resonant circuit with  $\omega_0 = 1/\sqrt{LC} = 400$

Therefore the circuit is operated at resonance. This means that the L-C parallel combination has an overall  $Z = \infty$  and hence  $I_s = I_o$ . When  $R_L$  is suddenly changed from  $100\Omega$  to  $1\text{ k}\Omega$ , due to the resonance condition,  $V_o = R_L I_o$  suddenly increases by a factor of 10. This in turn causes very large (equal & opposite) currents in the L & C as the capacitor voltage is forced to abruptly change. Thus very large currents radiate electromagnetic radiation and thus see sparks. Clearly we need a variable capacitor that varies as  $R_L$  varies such that when  $R_L \neq 100\Omega$ ,  $V_o \neq V_o$  and thus have  $V_o = R_L I_o$  constant while both  $R_L$  and  $I_o$  change abruptly.

**P13.5-9**

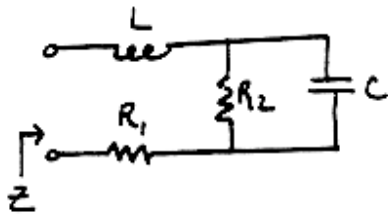

$$\begin{aligned} \tilde{Z} &= R_1 + j\omega L + \frac{1}{G_2 + j\omega C}; \quad G_2 = 1/R_2 \\ &= \frac{(R_1 G_2 + 1 - \omega^2 LC) + j(\omega L G_2 + \omega C R_1)}{G_2 + j\omega C} \end{aligned}$$

at resonance  $\tilde{Z} = Z \angle 0^\circ$

$$\text{or } \tan^{-1} \frac{\omega L G_2 + \omega C R_1}{(R_1 G_2 + 1 - \omega^2 LC)} = \tan^{-1} \frac{\omega C}{G_2}$$


$$\text{thus } \frac{\omega L G_2 + \omega C R_1}{(R_1 G_2 + 1 - \omega^2 LC)} = \frac{\omega C}{G_2} \Rightarrow \omega^2 = \frac{C - L G_2^2}{L C^2} \quad \& \quad C > G_2^2 L$$

with  $R_1 = R_2 = 1\Omega$  and  $\omega_0 = 100 \text{ rad/s}$

$$\omega_0^2 = 10^4 = \frac{C - L}{L C^2}, \text{ if } C = 10\text{mF} \Rightarrow L = 5\text{mH}$$

and  $C > G_2^2 L$  checks


**P13.5-10**

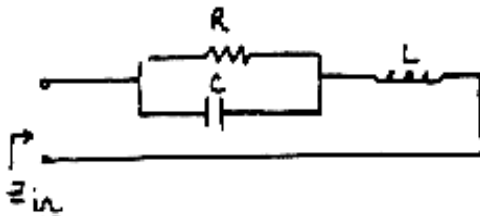

$$\begin{aligned} \text{(a) } Z_{in} &= j\omega L + \frac{R/j\omega C}{R + 1/j\omega C} \\ Z_{in} &= \frac{(R - \omega^2 RLC) + j\omega L}{1 + j\omega RC} \end{aligned}$$

$$\therefore |Z_{in}| = \sqrt{\frac{(R - \omega^2 RLC)^2 + (\omega L)^2}{1 + (\omega RC)^2}}$$

(b)

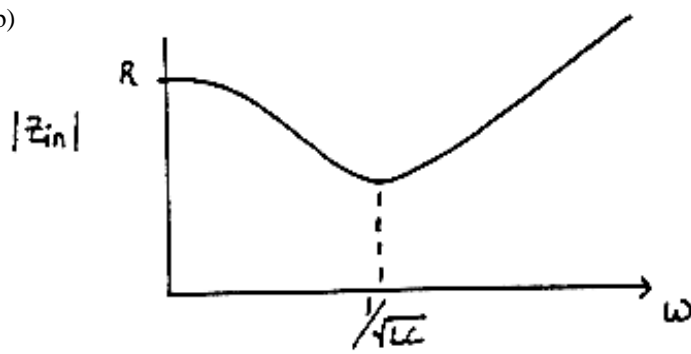

(c) at  $\omega = 1/\sqrt{LC}$ ,  $|Z_{in}| = \frac{1}{\sqrt{(C/L)(1+R^2 C/L)}}$

**P13.5-11**

Let  $V(\omega) = A\angle\theta^\circ = A$  and  $V_2(\omega) = B\angle\theta$


$$Y(\omega) = \frac{I(\omega)}{V(\omega)} = \frac{\frac{V(\omega) - V_2(\omega)}{R}}{V(\omega)} = \frac{A - B\angle\theta}{AR}$$
$$= \frac{A - B\cos\theta - j B\sin\theta}{AR}$$

$$|Y(\omega)| = \frac{\sqrt{(A - B\cos\theta)^2 + (B\sin\theta)^2}}{AR}$$



# PSpice Problems

## SP 13-1

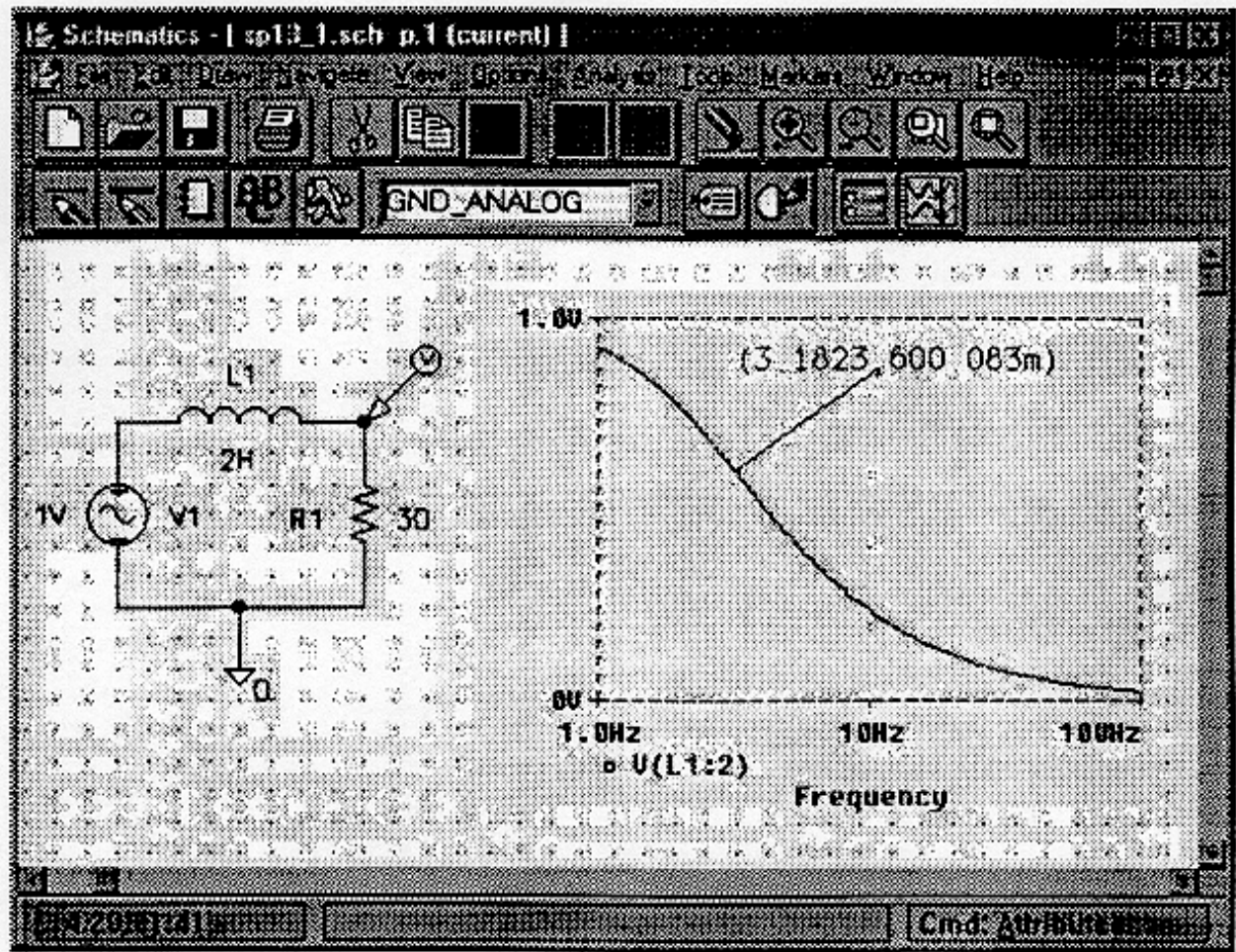

This simulation shows that the gain is


$$g = 600 \times 10^{-3} = 0.6$$

at the frequency

$$\omega = 2\pi \times 3.1823 = 20 \text{ rad/sec}$$

SP 13-2

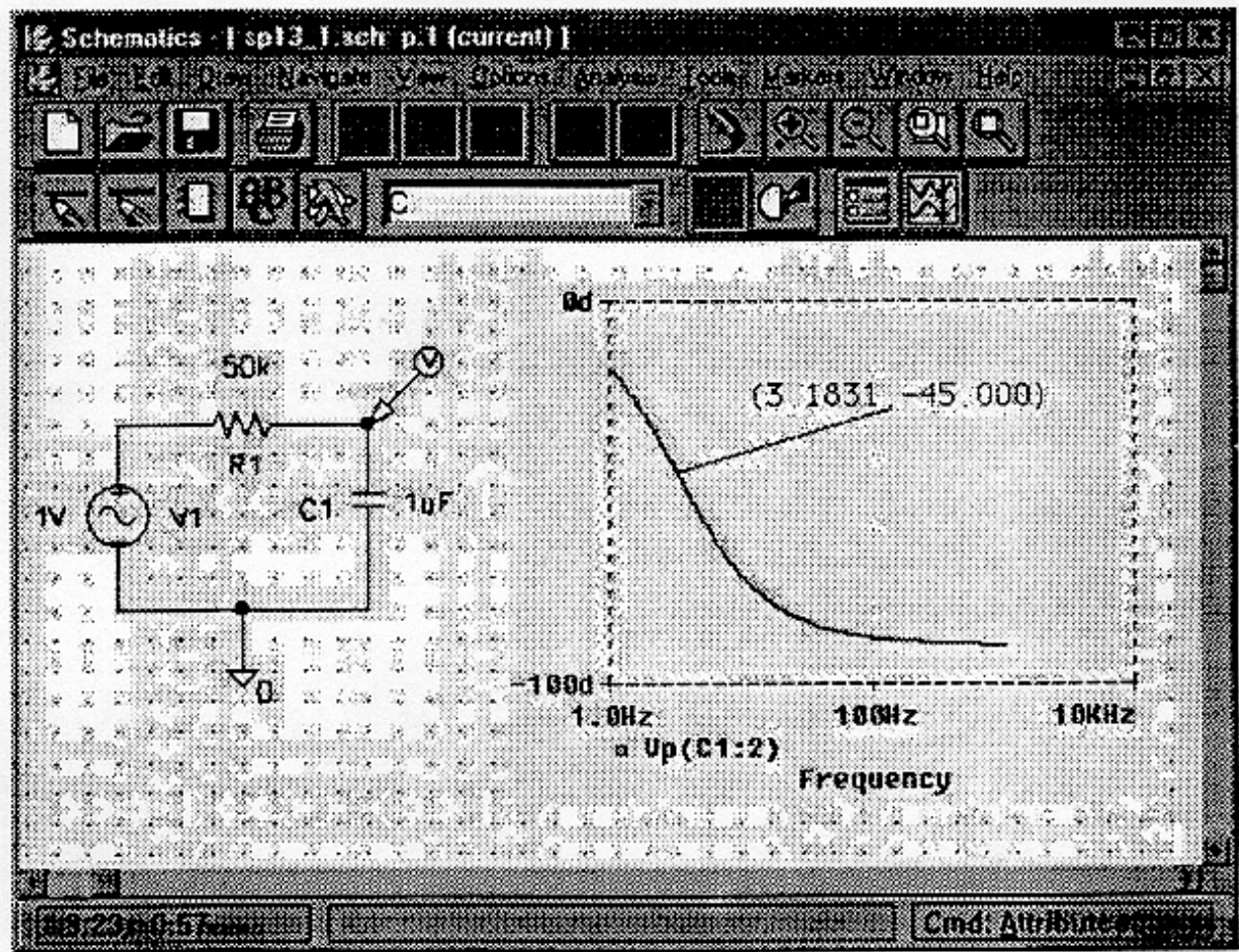Here is a simulation of the circuit when  $R = 50k\Omega$




The phase shift is  $-45^\circ$  at the frequency

$$\omega = 2\pi \times 3.1831 = 20\text{rad/sec}$$

as required.

SP 13-3

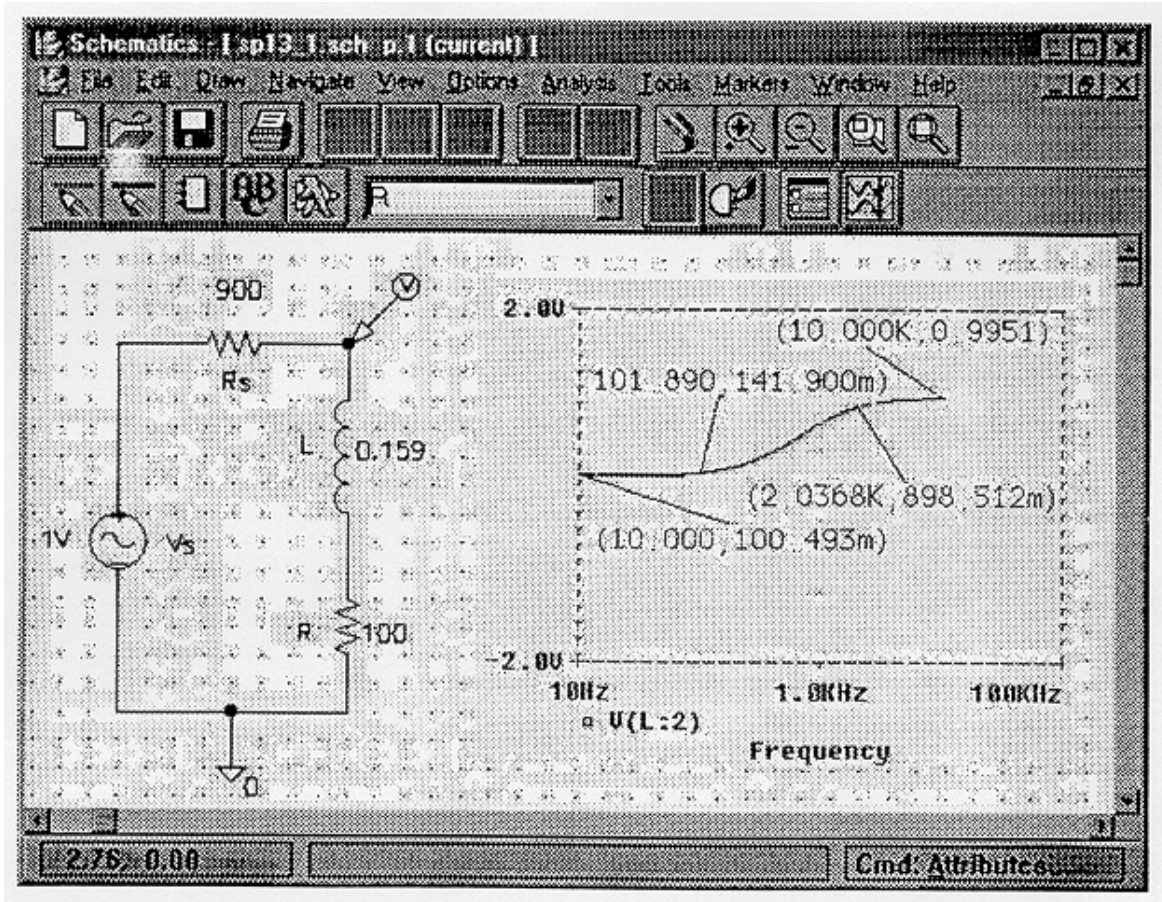


This simulation shows that the gain of the circuit is 0.1 at 10Hz and 0.995 at 10,000 Hz.

To satisfy the specifications on the corner frequencies, the gain must be  $\leq 1.414$  at 200 Hz and  $\geq 7.07$  at 2000 Hz.

Both conditions are met.

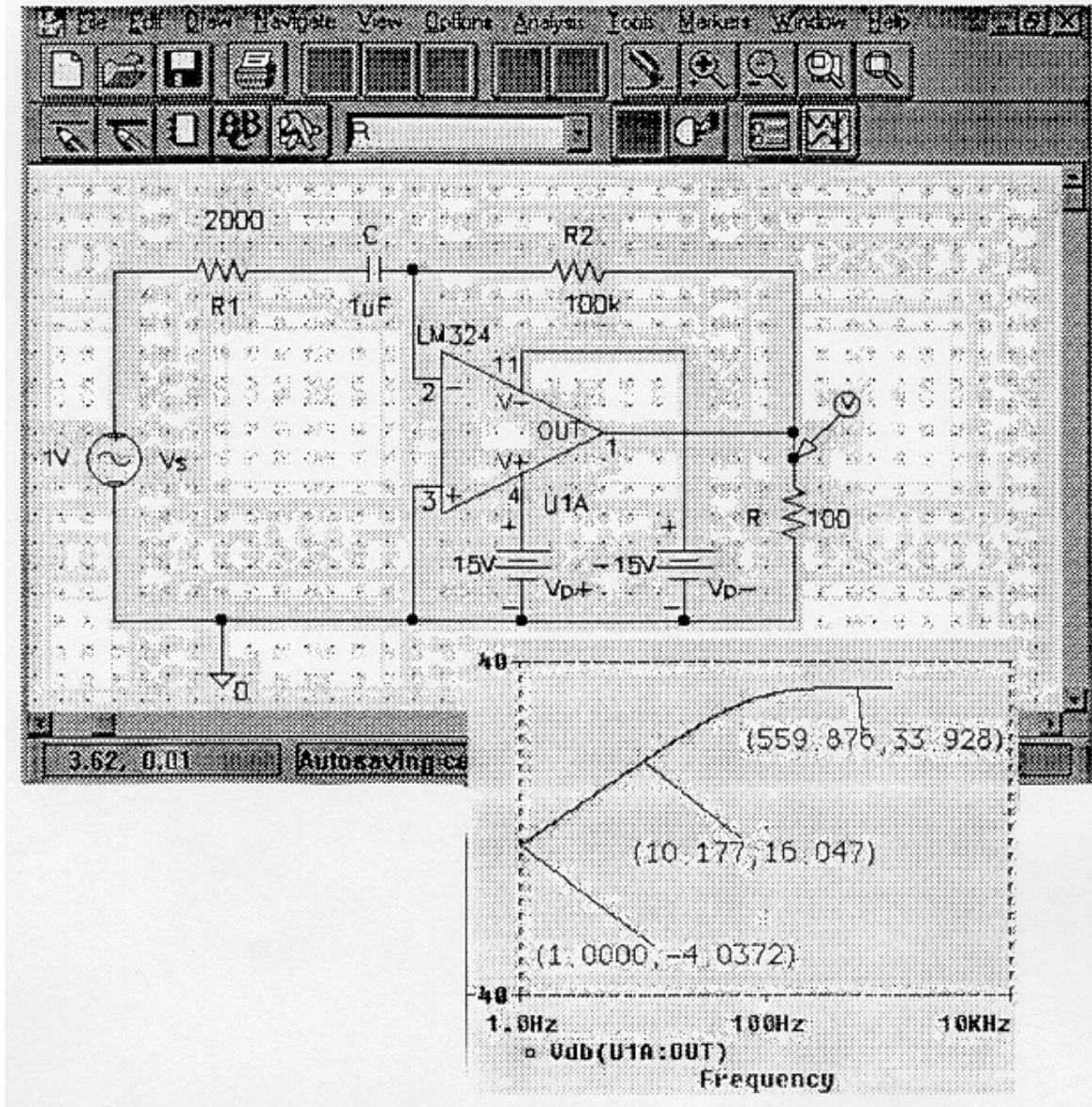
The circuit satisfies the specifications.



This simulation shows

- The high-frequency gain is  $33.928 \approx 34\text{dB}$
- The slope of the low-frequency asymptote is
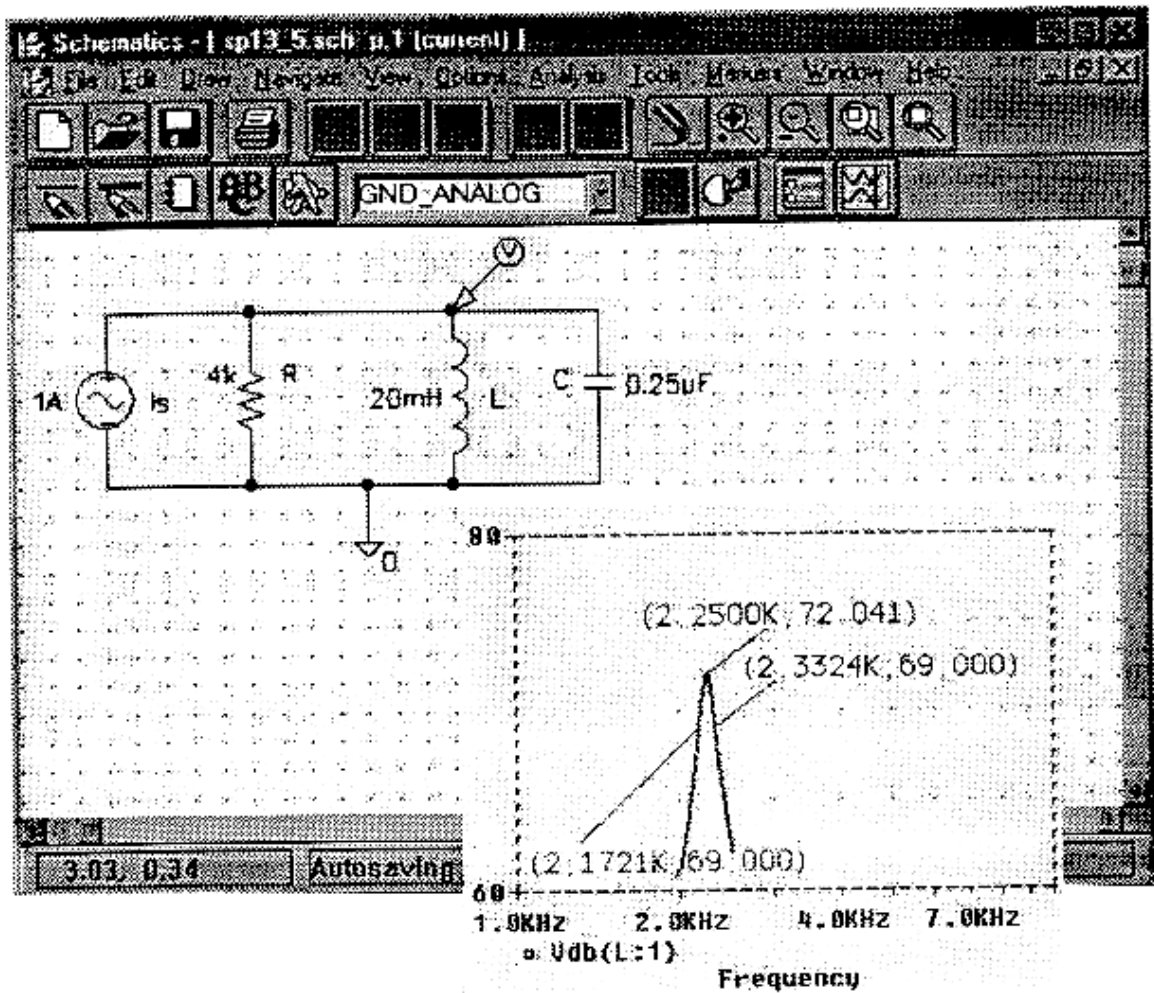
$$\frac{16\text{dB} - (-4\text{dB})}{\text{decade}} = 20\text{dB/decade}$$




The peak of the frequency response is  $72\text{dB} = 4000$  at  $2.25\text{Hz} = 14130\text{rad/sec}$ . So  $k = 4000$  and  $\omega_0 = 14130$

$\omega_1$  and  $\omega_2$  are identified as the frequencies where the gain is  $72-3 = 69\text{dB}$


$$Q = \frac{\omega_0}{\omega_2 - \omega_1} = \frac{f_0}{f_2 - f_1} = \frac{2250}{2332.4 - 2172.1} = 14$$

SP 13-6

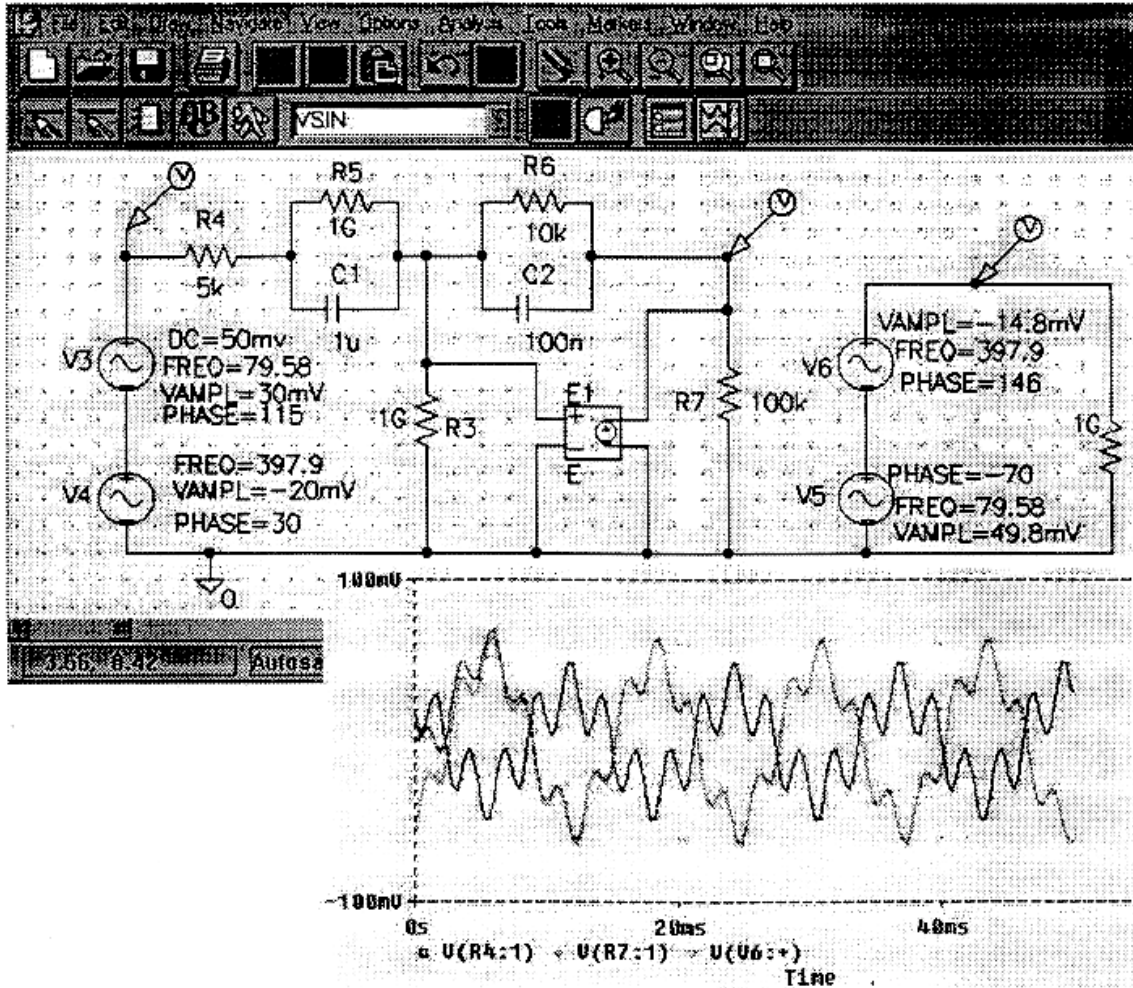

R3 and the dependent source E1 model an ideal op amp.  $V(R4:1)$  is  $v_s(t)$ .  $V(R7:1)$  is  $v_o(t)$ .  $V(U6:t)$  is the answer given in this solution manual. After the transient part dies out,  $V(R7:1)$  is identical to  $V(U6:t)$ . The answer is correct.

SP 13-7

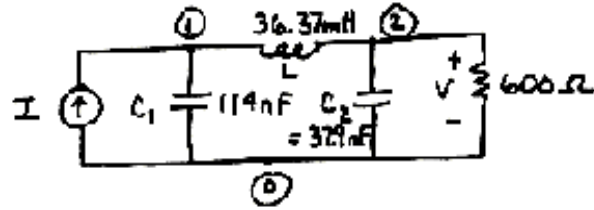


```


Is      1      0      ac      1
R1      2      0      600
C1      1      0      114n
C2      2      0      37.9n
L1      1      2      36.37m
    
```

```

.ac dec 50 100 10k
.probe
.end
    
```

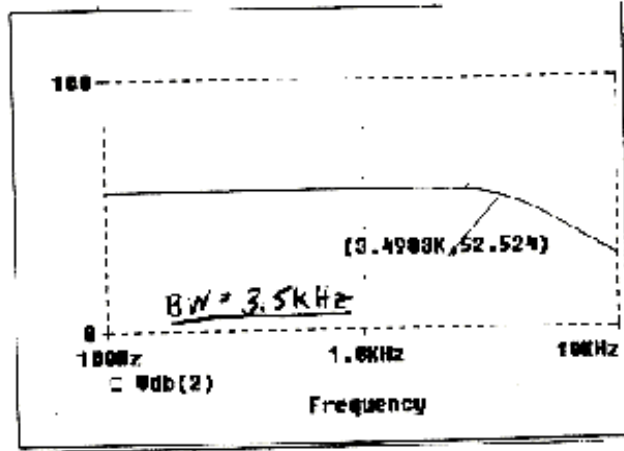

SP 13-8

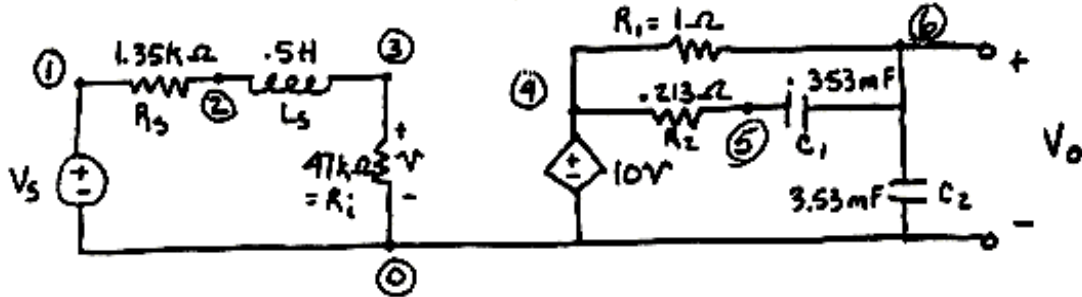


```


V1      1      0      ac      1
R2      1      2      1.35k
L3      2      3      500m
R4      3      0      47k
E5      4      0      3      0      10
R6      4      6      1
R7      4      5      213m
C8      5      6      353u
C9      6      0      3.53m
    
```

```

.ac dec 50 20 20k
.probe
.End
    
```

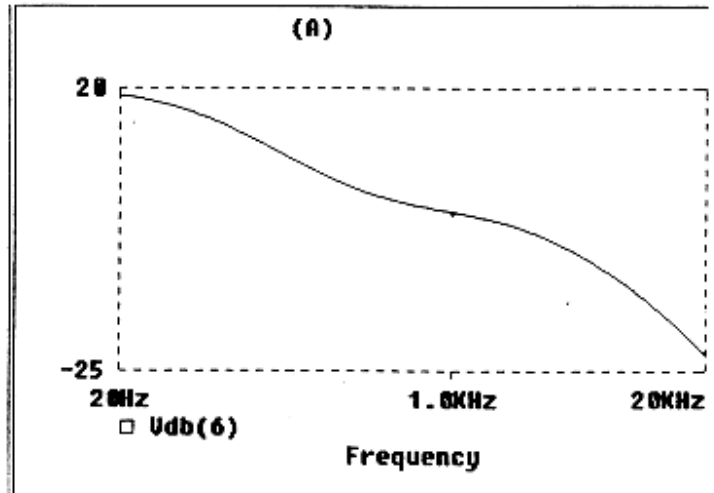

SP 13-9

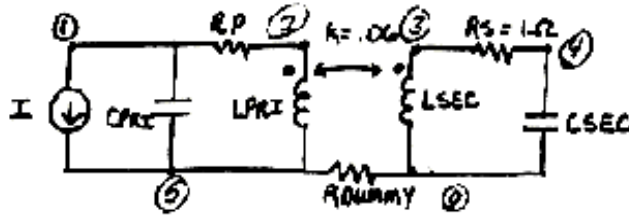


```

Is      1      5      ac      1m
C1      1      5      2.53n
R1      1      2      1
L1      2      5      10u
L2      3      0      10u
R2      3      4      1
C2      4      0      2.53n
K1      L1     L2     0.06
Rdummy  5      0      1000k
    
```

```

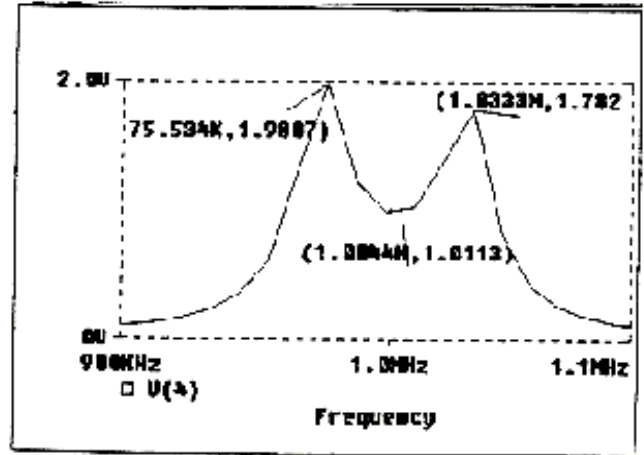.ac dec 200 900k 1100k
.probe
.end
    
```



Verification Problems

VP 13-1

When  $\omega < 630$  rad / sec,  $T(\omega) \approx \frac{1}{10}$  which agrees with the tabulated values of  $|T(\omega)|$  corresponding to  $\omega = 200$  and  $400$  rad/sec.

When  $\omega > 6300$  rad / sec,  $T(\omega) \approx 1$  which agrees with the tabulated values of  $|T(\omega)|$  corresponding to  $\omega = 12600, 25000, 50000$  and  $100000$  rad/sec.

At  $\omega = 630$  we expect  $|T(\omega)| = -3\text{dB} = 0.707$ . This agrees with the tabulated value of  $|T(\omega)|$  corresponding to  $\omega = 6310$ .

At  $\omega=630$  we expect  $|T(\omega)| = -20 + 3 = -17\text{dB} = 0.14$  which agrees with the tabulated values of  $|T(\omega)|$  corresponding to  $\omega = 400$  and  $795$  rad/s.

This data does seem reasonable.

VP 13-2  $BW = \frac{\omega_0}{Q} = \frac{10,000}{70} = 143 \neq 71.4$  rad/s This report is not correct.



**VP 13-3**

$$\omega_0 = \frac{1}{\sqrt{LC}} = 10\text{k rad/s} = 1.59\text{ kHz}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} = 20$$

$$\text{BW} = \frac{R}{L} = 500\text{ rad/s} = 79.6\text{ Hz}$$

The reported results are correct.

**VP 13-4**

The network function indicates a zero at 200 rad/s and a pole at 800 rad/s. In contrast, the Bode plot indicates a pole at 200 rad/s and a zero at 800 rad/s.

The Bode plot and network function don't correspond to each other.

p

where


$$k = \frac{R_2}{R_1}$$

$$Z = \frac{1}{C_1 R_1}$$

$$p = \frac{1}{C_2 R_2}$$

Design Problems

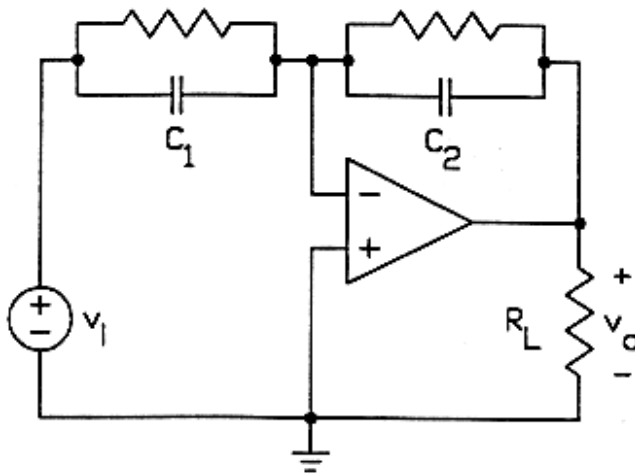**DP 13-1** Pick an appropriate circuit from Table 13.4-2.



The specifications indicate that

$$2 = k = \frac{R_2}{R_1}, \quad 5 = k \frac{p}{z} = \frac{C_1}{C_2}$$


$$2\pi \cdot 1000 < z = \frac{1}{C_1 R_1} \text{ and } 2\pi \cdot 10,000 > p = \frac{1}{C_2 R_2}$$

Try  $z = 2\pi \cdot 2000$  rad/s. Pick  $C_1 = 0.05 \mu F$ . Then

$$R_1 = \frac{1}{C_1 z} = 1.592 \text{ k}\Omega, \quad R_2 = 2R_1 = 3.183 \text{ k}\Omega, \quad C_2 = \frac{C_1}{k \frac{p}{z}} = 0.01 \mu F$$

$$\text{Check : } p = \frac{1}{C_2 R_2} = 31.42 \text{ k rad/s} < 2\pi \cdot 10,000$$

### DP 13-2

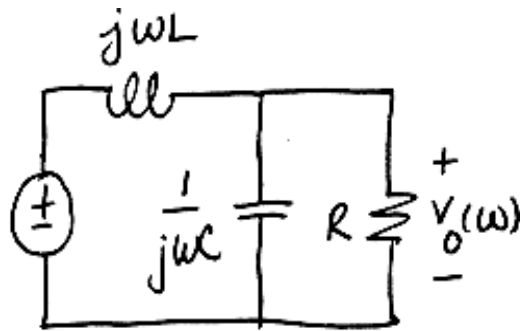

$$H(\omega) = \frac{V_o(\omega)}{V_s(\omega)} = \frac{1}{j\omega C} \parallel R$$

$$H(\omega) = \frac{V_o(\omega)}{V_s(\omega)} = \frac{\frac{1}{j\omega C} \parallel R}{j\omega L + \left( \frac{1}{j\omega C} \parallel R \right)} = \frac{\frac{R}{1+j\omega CR}}{j\omega L + \frac{R}{1+j\omega CR}} = \frac{\frac{1}{LC}}{-\omega^2 + j\omega \frac{1}{RC} + \frac{1}{LC}}$$

Pick  $\frac{1}{\sqrt{LC}} = \omega_0 = 2\pi(100 \cdot 10^3)$  rad/s. When  $\omega = \omega_0$

$$H_0(\omega) = \frac{\frac{1}{LC}}{-\frac{1}{LC} + j \frac{1}{\sqrt{LC}} \frac{1}{RC} + \frac{1}{LC}}$$

So

$$|H(\omega_0)| = R \sqrt{\frac{C}{L}}$$


We require

$$-3\text{dB} = 0.707 = |H(\omega_0)| = R \sqrt{\frac{C}{L}} = 1000 \sqrt{\frac{C}{L}}$$

Finally

$$\left. \begin{array}{l} \frac{1}{\sqrt{LC}} = 2\pi(100 \cdot 10^3) \\ 0.707 = 1000 \sqrt{\frac{C}{L}} \end{array} \right\} \Rightarrow \begin{array}{l} C = 1.13 \text{ nF} \\ L = 2.26 \text{ mH} \end{array}$$

DP 13-3

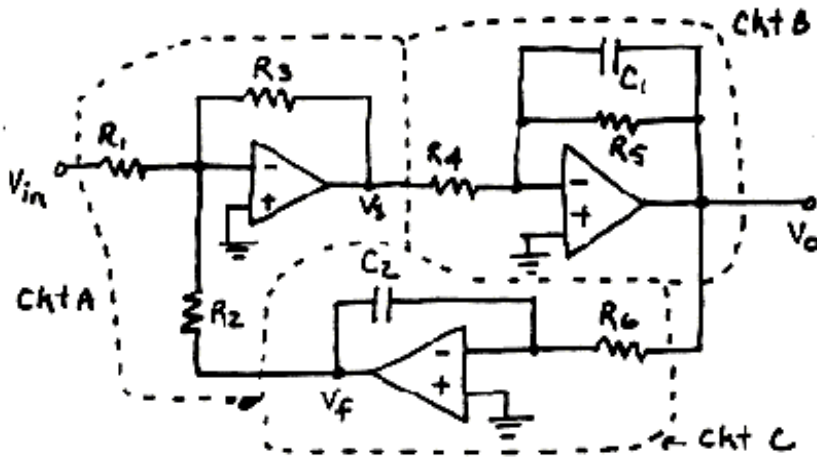

- $R_1 = 10k\Omega$
- $R_2 = 866k\Omega$
- $R_3 = 8.06k\Omega$
- $R_4 = 1M\Omega$
- $R_5 = 2.37M\Omega$
- $R_6 = 499k\Omega$
- $C_1 = 0.47\mu F$
- $C_2 = 0.1\mu F$

ckt A is inverting summer  $\Rightarrow V_s = -R_3 \left[ \frac{V_{in}}{R_1} + \frac{V_f}{R_2} \right]$  (1)

ckt B is first order LPF  $\Rightarrow V_o = -V_s \frac{Z_f}{Z_i} = -V_s \frac{R_5}{R_4} \left[ \frac{1}{C_1 R_5 s + 1} \right]$  (2)



ckt C is an integrator  $\Rightarrow V_f = -\frac{1}{C_s R_6 s} V_o$  (3)

Continued


Solving (1)  $\rightarrow$  (3) for  $V_o/V_{in}$  yields

$$\frac{V_o}{V_{in}} = \frac{\frac{R_3}{R_1 R_4 C_1} s}{s^2 + \frac{1}{R_5 C_1} s + \frac{R_3}{R_2 R_4 R_6 C_1 C_2}}$$

plugging in the values for the resistors & capacitors, can draw

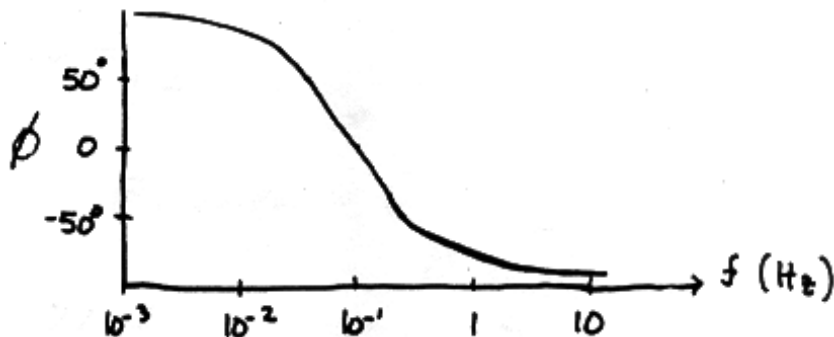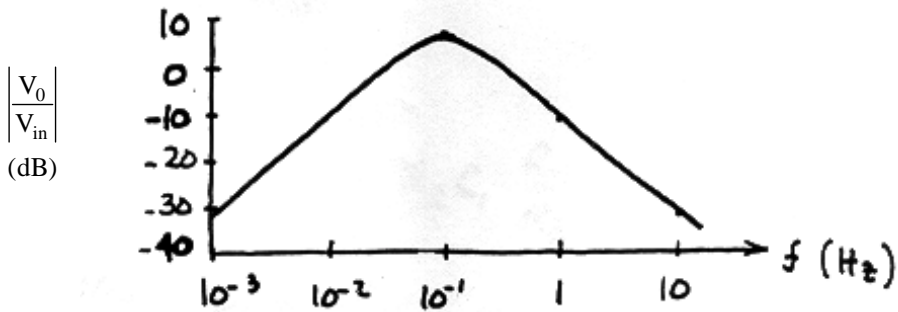

DP 13-4

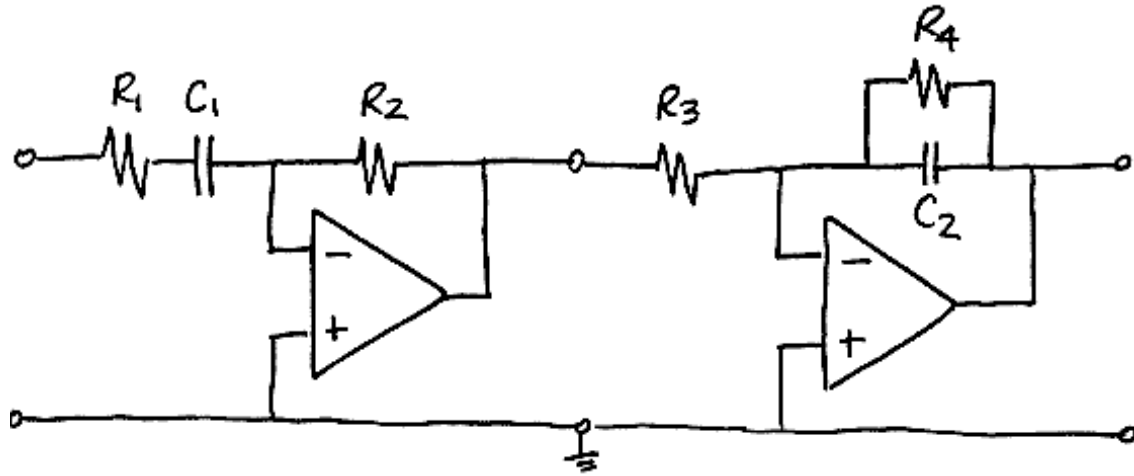

$$H_1(\omega) = -K_1 \frac{j\omega}{1 + j\frac{\omega}{p_1}}$$

where

$$K_1 = R_2 C_1, \quad p_1 = \frac{1}{C_1 R_1}$$

$$H_2(\omega) = \frac{K_2}{1 + j\frac{\omega}{p_2}}$$

where

$$K_2 = -\frac{R_4}{R_3}, \quad p_2 = \frac{1}{C_2 R_4}$$

We require

$$10 = -K_1 K_2 = R_2 C_1 \frac{R_4}{R_3}$$

$$200 = p_1 = \frac{1}{R_1 C_1}$$

$$500 = p_2 = \frac{1}{C_2 R_4}$$


Pick  $C_1 = 1\mu\text{F}$ . Then  $R_1 = \frac{1}{p_1 C_1} = 5\text{k}\Omega$

Pick  $C_2 = 0.1\mu\text{F}$ . Then  $R_4 = \frac{1}{p_2 C_2} = 20\text{k}\Omega$

Next  $10 = \frac{R_2}{R_3} (10^{-6})(20 \cdot 10^3) \Rightarrow \frac{R_2}{R_3} = 500$

Let  $R_2 = 500\text{k}\Omega$  and  $R_3 = 1\text{k}\Omega$

DP 13-5

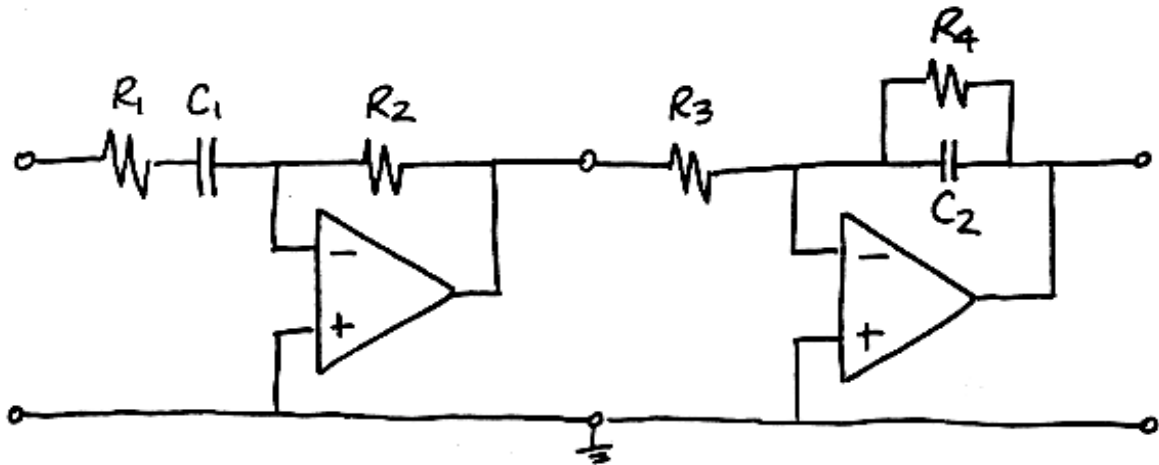

$$H_1(\omega) = -K_1 \frac{j\omega}{1 + j\frac{\omega}{p_1}}$$

where

$$K_1 = R_2 C_1, \quad p_1 = \frac{1}{C_1 R_1}$$

$$H_2(\omega) = \frac{K_2}{1 + j\frac{\omega}{p_2}}$$

where

$$K_2 = -\frac{R_4}{R_3}, \quad p_2 = \frac{1}{C_2 R_2}$$

We require

$$20\text{dB} = 10 = -K_1 K_2 = R_2 C_1 \frac{R_4}{R_3}$$

$$0.1 = p_1 = \frac{1}{R_1 C_1}$$

$$100 = p_2 = \frac{1}{R_4 C_2}$$

$$\text{Pick } C_1 = 20\mu\text{F. Then } R_1 = \frac{1}{p_1 C_1} = 500\text{k}\Omega$$

$$\text{Pick } C_2 = 1\mu\text{F. Then } R_4 = \frac{1}{p_2 C_2} = 10\text{k}\Omega$$

Next

$$10 = \frac{R_2}{R_3} (20 \cdot 10^{-6})(10 \cdot 10^3) \Rightarrow \frac{R_2}{R_3} = 50$$

Let  $R_2 = 200\text{k}\Omega$  and  $R_3 = 4\text{k}\Omega$

**DP 13-6**

The network function of this circuit is

$$T(\omega) = \frac{1 + \frac{R_2}{R_3}}{1 + j\omega R_1 C}$$

The phase shift of this network function is  $\theta = -\tan^{-1} \omega R_1 C$

The gain of this network function is  $G = \frac{1 + \frac{R_3}{R_2}}{\sqrt{1 + (\omega R_1 C)^2}} = \frac{1 + \frac{R_3}{R_2}}{\sqrt{1 + (\tan \theta)^2}}$

Design of this circuit proceeds as follows. Since the frequency and capacitance are known,  $R_1$  is calculated from

$$R_1 = \frac{\tan(-\theta)}{\omega C}$$

Next pick  $R_2 = 10\text{k}\Omega$  (a convenient value) and calculate  $R_3$  using

$$R_3 = (G \cdot \sqrt{1 + (\tan \theta)^2} - 1) \cdot R_2$$

$\theta = -45^\circ$ ,  $G = 2$ ,  $\omega = 1000 \text{ rad/s} \Rightarrow R_1 = 10\text{k}\Omega$ ,  $R_2 = 10\text{k}\Omega$ ,  $R_3 = 18.284 \text{ k}\Omega$ ,  $C = 0.1\mu\text{F}$

**DP 13-7** From Table 13.4-2 and the Bode plot:

$$800 = z = \frac{1}{R_1(0.5 \times 10^{-6})} \Rightarrow R_1 = 2.5 \text{ k}\Omega$$

$$32\text{dB} = 40 = \frac{R_2}{R_1} \Rightarrow R_2 = 100 \text{ k}\Omega$$

$$200 = p = \frac{1}{R_2 C} \Rightarrow C = \frac{1}{(200)(100\text{k}\Omega)} = 0.05\mu\text{F}$$

$$20\text{dB} = 10 = k \frac{p}{z} = \frac{0.5\mu\text{F}}{C} = \frac{0.5\mu\text{F}}{0.05\mu\text{F}}$$

**DP 13-8**

$$H(\omega) = \frac{-R_2}{1 + \frac{1}{j\omega C}} = -\frac{j\omega C R_2}{1 + j\omega C R_1}$$

$$195^\circ = 180 + 90 - \tan^{-1} \omega C R_1$$

$$\Rightarrow R_1 = \frac{\tan(270 - 195)}{(1000)(0.1 \times 10^{-6})} = 37.3 \text{ k}\Omega$$

$$10 = \lim_{\omega \rightarrow \infty} |H(\omega)| = \frac{R_2}{R_1} \Rightarrow R_2 = 10R_1 = 373 \text{ k}\Omega$$