

Chapter 14: The Laplace Transform

Exercises

Ex. 14.3-1 $\cos \omega t = \frac{1}{2}(e^{+j\omega t} + e^{-j\omega t})$ and $\mathcal{L}[e^{at}] = \frac{1}{s-a}$
 $\therefore \mathcal{L}[\cos \omega t] = \frac{1}{2} \left[\frac{1}{s-j\omega} + \frac{1}{s+j\omega} \right] = \frac{s}{s^2 + \omega^2} \Rightarrow F(s) = \frac{s}{s^2 + \omega^2}$

Ex. 14.3-2 $\mathcal{L}[e^{-2t} + \sin t] = \mathcal{L}[e^{-2t}] + \mathcal{L}[\sin t] = \frac{1}{s+2} + \frac{1}{s^2+1}$


$$F(s) = \frac{s^2 + s + 3}{(s+2)(s^2+1)}$$

Ex. 14.4-1 $P(s) = \mathcal{L}[2u(t) + 3e^{-4t}u(t)] = 2\mathcal{L}[u(t)] + 3\mathcal{L}[e^{-4t}u(t)] = \frac{2}{s} + \frac{3}{s+4}$

Ex. 14.4-2 $F(s) = \mathcal{L}[\sin(t-2)u(t-2)] = e^{-2s} \mathcal{L}[\sin t] = e^{-2s} \left(\frac{1}{s^2+1} \right)$

Ex. 14.4-3 $F(s) = \mathcal{L}[te^{-t}]$
 Now, since $\mathcal{L}[t] = \frac{1}{s^2}$, use a frequency shift $s \rightarrow s+1$
 $\therefore F(s) = \frac{1}{(s+1)^2}$

Ex. 14.4-4

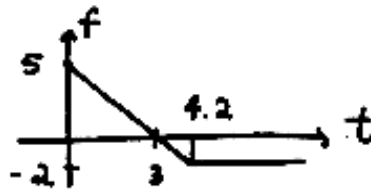

$$f(t) = f_1(t) + f_2(t)$$

$$f_1 = \left(-\frac{5}{3}t + 5 \right) u(t)$$

$$f_2 = \left(\frac{5}{3}(t-4.2) - 2 \right) u(t-4.2)$$

$$\therefore F_1(s) = -\frac{5}{3s^2} + \frac{5}{s} \quad F_2(s) = \frac{5}{3} \frac{e^{-4.2s}}{s^2} - \frac{2e^{-4.2s}}{s}$$

$$\text{so } F(s) = F_1(s) + F_2(s) = \frac{5e^{-4.2s} - 6se^{-4.2s} + 15s - 5}{3s^2}$$

Ex. 14.4-5 Using eqn. 14-1 $f(s) = \int_0^{\infty} f(t)e^{-st} dt = \int_0^2 3e^{-st} dt + 0 = \frac{3e^{-st}}{-s} \Big|_0^2 = \frac{3(1-e^{-2s})}{s}$

Ex. 14.4-6 From Fig. 1 $f(t) = \begin{cases} 5/2 t & 0 < t < 2 \\ 0 & \text{otherwise} \end{cases}$

$$\text{So } f(t) = \frac{5}{2}t[u(t)-u(t-2)] = \frac{5}{2}t u(t) - \frac{5}{2}t u(t-2) = \frac{5}{2}[tu(t) - (t-2)u(t-2) - 2u(t-2)]$$

$$\therefore F(s) = \mathcal{L}[f(t)] = \frac{5}{2} \left[\frac{1}{s^2} \frac{e^{-2s}}{s^2} - \frac{2e^{-2s}}{s} \right] = \frac{5}{2} \frac{1}{s^2} [1 - e^{-2s} - 2se^{-2s}]$$

Ex. 14.5-1 $F(s) = \frac{c+jd}{s+a-j\omega} + \frac{c-jd}{s+a+j\omega} = \frac{me^{j\theta}}{s+a-j\omega} + \frac{me^{j\theta}}{s+a+j\omega}$ where $m = \sqrt{c^2+d^2}$, $\theta = \tan^{-1} d/c$

$$\therefore f(t) = e^{-at} [c \cos \omega t - d \sin \omega t] = e^{-at} [\sqrt{c^2+d^2} \cos(\omega t + \theta)] = \underline{m e^{-at} \cos(\omega t + \theta)}$$

Ex. 14.5-2

(a) $F(s) = \frac{8s-3}{s^2+4s+13} = \frac{1}{2} \times \frac{2(8s-3)}{(s+2)^2+9}$

$$\therefore a=2, c=8, \omega=3 \text{ \& } ca-\omega d=-3 \Rightarrow d = \frac{-3(8)(2)}{-3} = 6.33$$

$$\therefore \theta = \tan^{-1} \left(\frac{6.33}{8} \right) = 38.4^\circ, m = \sqrt{(8)^2 + (6.33)^2} = 10.2$$

$$\Rightarrow \underline{f(t) = 10.2 e^{-2t} \cos(3t + 38.40)} \quad t \geq 0$$

(b) $F(s) = \frac{3e^{-s}}{s^2+2s+17}$

$$\text{First consider } F_1(s) = \frac{3}{s^2+2s+17} = \frac{1}{2} \times \frac{(2(3))}{(s+1)^2+16}$$

$$\text{So } a=1, c=0, \omega=4 \text{ and } -\omega d=3 \Rightarrow d=-3/4$$

$$\therefore m=|d|=3/4, \theta = \tan^{-1}(-3/(4/0)) = -90^\circ$$

$$\text{So } f_1(t) = (3/4)e^{-t} \sin 4t$$

$$\text{Now since } F(s) = e^{-s} F_1(s) \Rightarrow f(t) = f_1(t-1)$$

$$\therefore \underline{f(t) = (3/4)e^{-(t-1)} \sin[4(t-1)]} \quad t \geq 1$$

Ex. 14.5-3

(a) $F(s) = \frac{s^2-5}{s(s+1)^2} = \frac{A}{s} + \frac{B}{s+1} + \frac{C}{(s+1)^2}$

$$A = sF(s)|_{s=0} = \frac{-5}{1} = -5$$

$$C = (s+1)^2 F(s)|_{s=-1} = \frac{1-5}{-1} = 4$$

$$B \Rightarrow \text{multiply both sides by } s(s+1)^2$$

$$s^2 - 5 = -5(s+1) + Bs(s+1) + 4s$$

$$\text{equating coefficients } \Rightarrow B = 6$$

$$\therefore F(s) = -5/s + 6/(s+1) + 4/(s+1)^2$$

$$\Rightarrow \underline{f(t) = -5 + 6e^{-t} + 4te^{-t}} \quad t \geq 0$$

$$(b) \quad F(s) = \frac{4s^2}{(s+3)^3} = \frac{A}{(s+3)} + \frac{B}{(s+3)^2} + \frac{C}{(s+3)^3}$$

$$A = (1/2) \frac{d^2}{ds^2} \left[(s+3)^2 F(s) \right]_{s=-3} = 4$$

$$B = \frac{d}{ds} \left[(s+3)^3 F(s) \right]_{s=-3} = -24$$

$$C = (s+3)^3 F(s)_{s=-3} = 36$$

$$\therefore F(s) = 4/(s+3) - 24/(s+3)^2 + 36/(s+3)^3$$

Using Table 14-3: $f(t) = 4e^{-3t} - 24te^{-3t} + 18t^2e^{-3t} \quad t \geq 0$

Ex. 14.6-1

$$(a) \quad F(s) = \frac{6s+5}{s^2+2s+1}$$

$$f(0) = \lim_{s \rightarrow \infty} sF(s) = \lim_{s \rightarrow \infty} \left[\frac{s(6s+5)}{s^2+2s+1} \right] = \underline{6}$$


$$f(\infty) = \lim_{s \rightarrow 0} sF(s) = \lim_{s \rightarrow 0} \left[\frac{s(6s+5)}{s^2+2s+1} \right] = \underline{0}$$

$$(b) \quad F(s) = \frac{6}{s^2-2s+1}$$

$$f(0) = \lim_{s \rightarrow \infty} \left[\frac{6s}{s^2-2s+1} \right] = \underline{0}$$

$$f(\infty) = \lim_{s \rightarrow 0} \left[\frac{6s}{s^2-2s+1} \right] = \text{undefined} \quad \therefore \text{no final value}$$

Ex. 14.7-1

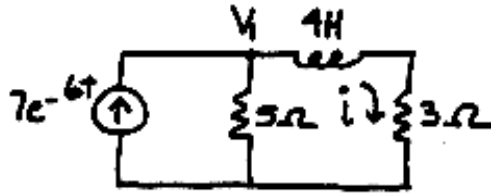

$$\text{KCL at } v_1: v_1/5 + i = 7e^{-6t} \quad (1)$$

$$\text{also: } v_1 = 3i + 4 \frac{di}{dt} \quad (2)$$

$$(2) \text{ into } (1) \text{ yields: } \frac{di}{dt} + 2i = \frac{35}{4}e^{-6t}$$

Taking the Laplace Transform of the D.E.

$$s I(s) - i(0) + 2 I(s) = \frac{35}{4} \frac{1}{s+6} \quad \text{where } i(0) = 0$$


$$\Rightarrow I(s) = \frac{35}{4} \frac{1}{(s+2)(s+6)}$$

Now $\frac{1}{(s+2)(s+6)} = \frac{A}{s+2} + \frac{B}{s+6}$ where $A = \frac{1}{s+6} \Big|_{s=-2} = \frac{1}{4}$ and $B = \frac{1}{s+2} \Big|_{s=-6} = -\frac{1}{4}$

$$\therefore I(s) = \frac{35}{16} \frac{1}{s+2} - \frac{35}{16} \frac{1}{s+6}$$

$$\Rightarrow i(t) = \frac{35}{16} e^{-2t} - \frac{35}{16} e^{-6t}$$

Ex. 14.7-2

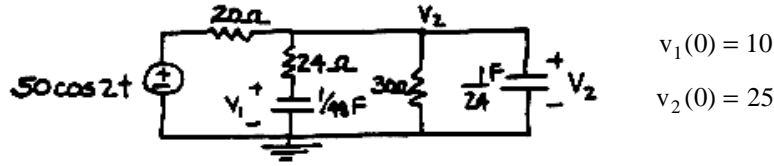

$$v_1(0) = 10$$

$$v_2(0) = 25$$

$$\text{KCL at } v_1 : (1/48) dv_1/dt + (v_1 - v_2)/24 = 0$$

$$\Rightarrow 2 v_1 + dv_1/dt - 2v_2 = 0 \tag{1}$$

$$\text{KCL at } v_2 : (v_2 - 50 \cos 2t)/20 + (v_2 - v_1)/24 + v_2/30 + (1/24) dv_2/dt = 0$$

$$\Rightarrow -v_1 + 3v_2 + dv_2/dt = 60 \cos 2t \tag{2}$$

Taking Laplace Transform of (1) & (2)

$$(2+s) V_1(s) - 2V_2(s) = 10 \tag{3}$$

$$-V_1(s) + (3+s) V_2(s) = \frac{25s^2 + 60s + 100}{s^2 + 4} \tag{4}$$

Using Cramers rule with (3) & (4)

$$V_2(s) = \frac{(2+s) \left(\frac{25s^2 + 60s + 100}{s^2 + 4} \right) + 10}{(2+s)(3+s) - 2} = \frac{(2+s)(25s^2 + 60s + 100) + 10(s^2 + 4)}{(s^2 + 4)(s+1)(s+4)} = \frac{25s^3 + 120s^2 + 220s + 240}{(s^2 + 4)(s+1)(s+4)}$$

$$\text{Let } V_2(s) = \frac{A}{s+j2} + \frac{A^*}{s-j2} + \frac{B}{s+1} + \frac{C}{s+4}$$

$$A = \left. \frac{25s^3 + 120s^2 + 220s + 240}{(s+1)(s+4)(s-j2)} \right|_{s=-j2} = \frac{-240 - j240}{-40} = 6 + j6$$

$$\therefore A^* = 6 - j6$$

$$B = \left. \frac{25s^3 + 120s^2 + 220s + 240}{(s^2 + 4)(s+4)} \right|_{s=-1} = \frac{115}{15} = \frac{23}{3}$$

$$C = \left. \frac{25s^3 + 120s^2 + 220s + 240}{(s^2 + 4)(s+1)} \right|_{s=-4} = \frac{-320}{-60} = \frac{16}{3}$$

$$\therefore V_2(s) = \frac{6+j6}{s+j2} + \frac{6-j6}{s-j2} + \frac{23/3}{s+1} + \frac{16/3}{s+4}$$

$$\Rightarrow \underline{v_2(t) = 12 \cos 2t + 12 \sin 2t + (23/3)e^{-t} + (16/3)e^{-4t} \text{ V, } t \geq 0}$$

Ex. 14.7-3 Taking Laplace Transform of the D.E.

$$s^2 F(s) = s f(0) - f'(0) + 5 [s F(s) - f(0)] + 6 F(s) = \frac{10}{s+3}$$

Plugging in initial conditions

$$(s^2 + 5s + 6) F(s) = \frac{10}{s+3} + 2s + 10 = \frac{2s^2 + 16s + 40}{s+3}$$


$$\Rightarrow F(s) = \frac{2s^2 + 16s + 40}{(s+3)(s+2)(s+3)} = \frac{A}{(s+3)^2} + \frac{B}{s+3} + \frac{C}{s+2}$$

$$\Rightarrow A = -10, B = -14, C = 16$$

$$F(s) = \frac{-10}{(s+3)^2} + \frac{-14}{s+3} + \frac{16}{s+2}$$

$$\therefore f(t) = \underline{-10te^{-3t} - 14e^{-3t} + 16e^{-2t}} \quad \text{for } t \geq 0$$

Ex. 14.8-1

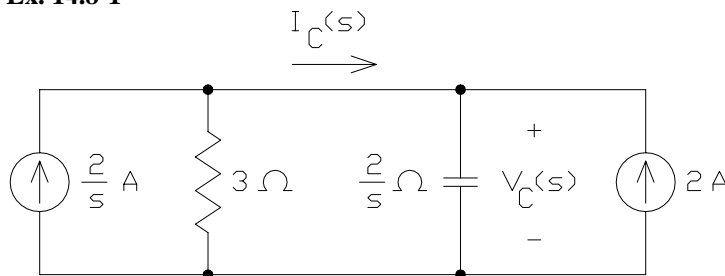

KCL at top node:

$$\frac{V_C(s)}{3} + \frac{s}{2} V_C(s) = \frac{2}{s} + 2$$


$$V_C(s) = \frac{6}{s} - \frac{2}{s + \frac{2}{3}}$$

$$v_C(t) = (6 - 2e^{-0.67t})u(t) \text{ V}$$

$$I_C(s) = \frac{V_C(s)}{\frac{2}{s}} - 2 = \frac{\frac{6}{s} - \frac{2}{s + \frac{2}{3}}}{\frac{2}{s}} - 2 = \frac{3}{s} - \frac{2}{s + \frac{2}{3}} - 2$$

$$\text{so } i_C(t) = \frac{2}{3} e^{-0.67t} u(t) \text{ A}$$

Ex. 14.8-2

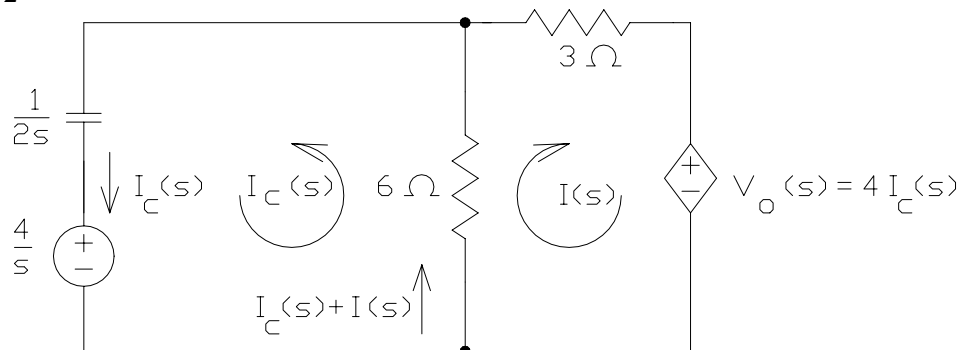

Mesh Equations:

$$-\frac{4}{s} - \frac{1}{2s} I_C(s) - 6(I(s) - I_C(s)) = 0 \Rightarrow -\frac{4}{s} = \left(6 + \frac{1}{2s}\right) I_C(s) + 6I(s)$$

$$6(I(s) - I_C(s)) + 3I(s) + 4I_C(s) = 0 \Rightarrow I(s) = -\frac{10}{9} I_C(s)$$

Solving for $I_C(s)$:

$$-\frac{4}{s} = \left(-\frac{2}{3} + \frac{1}{2s}\right) I_C(s) \Rightarrow I_C(s) = \frac{6}{s - \frac{3}{4}}$$


So $V_o(s)$ is

$$V_o(s) = 4I_C(s) = \frac{24}{s - \frac{3}{4}}$$

Back in the time domain:

$$v_o(t) = 24e^{0.75t} u(t) \text{ V}$$

Ex. 14.8-3

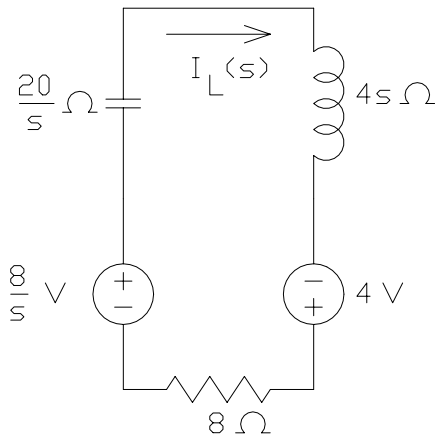

KVL:

$$\frac{8}{s} + 4 = \left(\frac{20}{s} + 8 + 4s\right) I_L(s)$$

so

$$I_L(s) = \frac{2+s}{s^2+2s+5} = \frac{(s+1)+1}{(s+1)^2+4}$$

Taking the inverse Laplace transform:

$$i(t) = \left(e^{-t} \cos 2t + \frac{1}{2} e^{-t} \sin 2t\right) u(t) \text{ A}$$

Ex 14.9-1

(a) *impulse response* = $\mathcal{L}^{-1} \left[\frac{5}{s+5} - \frac{10}{s+10} \right] = (5e^{-5t} - 10e^{-10t}) u(t)$

(b) *step response* = $\mathcal{L}^{-1} \left[\frac{1}{s+10} - \frac{1}{s+5} \right] = (e^{-10t} - e^{-5t}) u(t)$

Ex 14.9-2

$$H(s) = \mathcal{L} \left[5e^{-2t} \sin(4t) u(t) \right] = \frac{5(4)}{(s+2)^2 + 4^2} = \frac{20}{s^2 + 4s + 20}$$


$$\text{step response} = \mathcal{L}^{-1} \left[\frac{H(s)}{s} \right] = \mathcal{L}^{-1} \left[\frac{1}{s} - \frac{s+4}{s^2 + 4s + 20} \right] = (1 - e^{-2t} (\cos 4t - \frac{1}{2} \sin 4t)) u(t)$$

Ex. 14.10-1

(a) Voltage divider yields

$$H(s) = \frac{V_c(s)}{V_1(s)} = \frac{\frac{8/s/2}{8+s/2}}{2 + \frac{8/s/2}{8+s/2}} = \frac{8/(1+4s)}{2+8/(1+4s)}$$

$$= \frac{8}{10+8s} = \frac{1}{1.25+s}$$

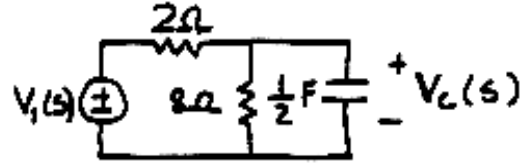

(b) $h(t) = \mathcal{L}^{-1}[H(s)] = e^{-1.25t}$

Ex. 14.10-2

$$h(t) = e^{-2t} \Rightarrow H(s) = 1/(s+2)$$

$$f(t) = u(t) \Rightarrow F(s) = 1/s$$

$$\text{so } h(t) * f(t) = \mathcal{L}^{-1}[H(s)F(s)] = \mathcal{L}^{-1}\left[\frac{1}{s(s+2)}\right] = \mathcal{L}^{-1}\left[\frac{1/2}{s} + \frac{-1/2}{s+2}\right] = 1/2u(t) - 1/2e^{-2t}$$

Ex. 14.11-1 For the poles to be in the left half of the s-plane, the s-term needs to be positive.

$$\therefore 8 - k > 0 \text{ or } k < 8 \text{ so } \underline{0 \leq k < 8}$$

Ex. 14.11-2 To get oscillation, we want the s-term to go to zero

$$\therefore \underline{k = 8} \text{ will give oscillation}$$

Ex. 14.12-1

$$V_0(s) = 0.1 \left[\frac{2}{s} - \left(2 \frac{s+5}{(s+5)^2 + 10^2} + \frac{10}{(s+5)^2 + 10^2} \right) \right]$$

$$= 0.1 \left[\frac{2}{s} - \frac{2s+20}{s^2+10s+125} \right]$$

$$= 0.1 \frac{2(s^2+10s+125) - (2s+20)s}{s^2+10s+125}$$

$$= 0.1 \frac{250}{s^2+10s+125} = \frac{25}{s^2+10s+125}$$

These specifications are consistent.

Problems

Section 14-3: Laplace Transform

P14.3-1 $\mathcal{L}[A f_1(t)] = A F_1(s)$

$$f_1(t) = \cos(\omega t) \Rightarrow F_1(s) = s / (s^2 + \omega^2)$$

$$\therefore F(s) = \frac{As}{s^2 + \omega^2}$$

P14.3-2 From Table 14.4-1: $f(t) = t^n$, $F(s) = \frac{n!}{s^{n+1}}$, but we have $n = 1$

$$\therefore F(s) = \frac{1}{s^2}$$

P14.3-3 Linearity: $\mathcal{L}[a_1 f_1(t) + a_2 f_2(t)] = a_1 F_1(s) + a_2 F_2(s)$

Here $a_1 = a_2 = 1$

$$\mathcal{L}[f_1(t)] = \mathcal{L}[e^{-3t}] = \frac{1}{s+3} = F_1(s)$$

$$\mathcal{L}[f_2(t)] = \mathcal{L}[t] = \frac{1}{s^2} = F_2(s)$$

$$\text{so } F(s) = \frac{1}{s+3} + \frac{1}{s^2}$$

P14.3-4 $f(t) = A(1 - e^{-bt})u(t) = \mathcal{L}[A f_1(t)] = A F_1(s)$

$$f_1(t) = A(1 - e^{-bt})u(t) = 1u(t) - e^{-bt}u(t) = f_2(t) + f_3(t)$$

$$F_2(s) = \frac{1}{s}, \quad F_3(s) = \frac{-1}{s+b}$$

$$\therefore F(s) = A \left[\frac{1}{s} - \frac{1}{s+b} \right] = \frac{Ab}{s(s+b)}$$

Section 14-4: Impulse Function and Time Shift Property

P14.4-1 $f(t) = A[u(t) - u(t-T)]$

$$F(s) = A\mathcal{L}[u(t)] - A\mathcal{L}[u(t-T)] = A/s - \frac{Ae^{-sT}}{s} = A \frac{(1 - e^{-sT})}{s}$$

P14.4-2 Have $f(t) = 1[u(t) - u(t-T)]e^{at}$

$$F(s) = \mathcal{L}[e^{at}[u(t) - u(t-T)]]$$

$$\text{Now } \mathcal{L}[u(t) - u(t-T)] = \frac{1 - e^{-sT}}{s} \text{ and } \mathcal{L}[e^{at}g(t)] = G(s-a)$$

$$\Rightarrow F(s) = \frac{1 - e^{(s-a)T}}{(s-a)}$$

P14.4-3

(a)
$$\underline{F(s) = 2/(s+3)^3}$$
 using Table 14-3

(b) $f(t) = \delta(t-T)u(t-T)$ & using time shift, get: $\underline{F(s) = e^{-sT} + [\delta(t)] = e^{-sT}}$

(c)
$$F(s) = \frac{5}{(s+4)^2 + (5)^2} = \frac{5}{(s+4)^2 + 25}$$
 using Table 14.4-1

P14.4-4 $g(t) = e^{-t}u(t-0.5), \tau = 0.5$

$$\mathcal{L}[f(t-\tau)u(t-\tau)] = e^{-s\tau} F(s)$$

$$f(t-\tau) = e^{-t-\tau}(e^\tau); f(t) = e^\tau e^{-t}$$

$$\mathcal{L}[e^{-at}] = \frac{1}{s+a}, \text{ here } a=1$$

$$F(s) = e^\tau \left(\frac{1}{s+1} \right) e^{-0.5s} = (e^{0.5} e^{-0.5s}) \left(\frac{1}{s+1} \right) = \frac{e^{0.5-0.5s}}{s+1}$$

P14.4-5 $\mathcal{L}[f_1(t-\tau)u(t-\tau)] = e^{-s\tau} F(s)$

$$f_1(t-\tau) = \frac{-t-T}{T}; \tau=T; f_1(t) = -t/T$$

$$\therefore F_1(s) = \frac{1}{\tau} \left(\frac{1}{s^2} \right) \text{ and } \underline{F(s) = \left[\frac{-1}{Ts^2} \right] e^{-sT}}$$

Section 14-5: Inverse Laplace Transform

P14.5-1
$$F(s) = \frac{s+3}{s^3+3s^2+6s+4} = \frac{s+3}{(s+1)[(s+1)^2+3]} = \frac{A}{s+1} + \frac{Bs+C}{s^2+2s+4}$$

$$A = \frac{s+3}{(s+1)^2+3} \Big|_{s=-1} = 2/3$$

$$\therefore \frac{(s+3)}{(s+1)(s^2+2s+4)} = \frac{2/3}{s+1} + \frac{Bs+C}{s^2+2s+4}$$

$$\Rightarrow (s+3) = (2/3 + B)s^2 + (4/3 + B + C)s + 8/3 + C$$

Equating coefficients $s^2: 0 = 2/3 + B \Rightarrow B = 2/3$

$s: 1 = 4/3 - 2/3 + C \Rightarrow C = 1/3$

$$\text{So } F(s) = \frac{2/3}{s+1} + \frac{-(2/3)s+1/3}{(s+1)^2+3} = \frac{2/3}{s+1} + \frac{-(2/3)(s+1)}{(s+1)^2+3} + \frac{(1/3)\sqrt{3}}{(s+1)^2+3}$$

$$\therefore \underline{f(t) = (2/3)e^{-t} - (2/3)e^{-t} \cos \sqrt{3}t + 1/\sqrt{3}e^{-t} \sin \sqrt{3}t}$$

P14.5-2

$$F(s) = \frac{s^2 - 2s + 1}{s^3 + 3s^2 + 4s + 2} = \frac{s^2 - 2s + 1}{(s+1)(s+1-j)(s+1+j)} = \frac{a}{s+1-j} + \frac{a^*}{s+1+j} + \frac{b}{s+1}$$

$$b = \left. \frac{s^2 - 2s + 1}{(s+1)^2 + 1} \right|_{s=-1} = 4$$

$$a = \left. \frac{s^2 - 2s + 1}{(s+1)(s+1+j)} \right|_{s=-1+j} = \frac{3-j}{-2} = -3/2 + j/2$$

$$a^* = -3/2 - j/2$$

$$\Rightarrow F(s) = \frac{-3/2 + j/2}{s+1-j} + \frac{-3/2 - j/2}{s+1+j} + \frac{4}{s+1}$$

$$\text{for first two terms : } m = \sqrt{(-3/2)^2 + (1/2)^2} = 5/2$$

$$\theta = \tan^{-1}(2/-3) = 126.9^\circ$$

$$\therefore \underline{f(t) = 5e^{-t} \cos(t + 233^\circ) + 4e^{-t}}$$

P14.5-3

$$F(s) = \frac{5s-1}{(s+1)^2(s-2)} = \frac{A}{s+1} + \frac{B}{(s+1)^2} + \frac{C}{s-2}$$

$$B = \left. \frac{5s-1}{s-2} \right|_{s=-1} = 2$$

$$C = \left. \frac{5s-1}{(s+1)^2} \right|_{s=2} = 1$$

$$A = \left. \frac{d}{ds} \left[(s+1)^2 F(s) \right] \right|_{s=-1} = -9/(s-2)^2 \Big|_{s=-1} = -1$$

$$\therefore F(s) = -1/(s+1) + 2/(s+1)^2 + 1/(s-2)$$

$$\Rightarrow \underline{f(t) = -e^{-t} + 2te^{-t} + e^{2t}}$$

P14.5-4

$$Y(s) = \frac{1}{(s+1)(s^2+2s+2)} = \frac{1}{(s+1)[(s+1)^2+1]} = \frac{A}{s+1} + \frac{Bs+C}{(s+1)^2+1}$$

$$A = \left. \frac{1}{s^2+2s+2} \right|_{s=-1} = 1$$

$$B \Rightarrow \frac{1}{(s+1)(s^2+2s+2)} = \frac{1}{s+1} + \frac{Bs+C}{s^2+2s+2}$$

$$\Rightarrow 1 = s^2 + 2s + 2 + (Bs + C)(s+1)$$

$$1 = (B+1)s^2 + (B+C+2)s + C + 2$$

$$\text{Equating coefficients : } s^2 : 0 = B+1 \Rightarrow B = -1$$

$$s : 0 = B+C+2 \Rightarrow C = -1$$

$$\therefore Y(s) = \frac{1}{s+1} - \frac{s+1}{(s+1)^2+1} \Rightarrow \underline{y(t) = e^{-t} - e^{-t} \cos t}$$

P14.5-5 $F(s) = \frac{2(s+3)}{(s+1)(s+1+2j)(s+1-2j)}$ using partial fractions yields

$$F(s) = \frac{1}{s+1} + \frac{-(s+1)}{(s+1)^2+4} + \frac{2}{(s+1)^2+4}$$

So $f(t) = e^{-t} - e^{-t} \cos(2t) + e^{-t} \sin(2t)$

P14.5-6 Use partial fractions : $\frac{2(s+3)}{s(s+1)(s+2)} = \frac{A}{s} + \frac{B}{s+1} + \frac{C}{s+2}$

$$sF(s) = \frac{2(s+3)}{(s+1)(s+2)} \Big|_{s=0} = A=3; \quad (s+1)F(s) = \frac{2(s+3)}{s(s+2)} \Big|_{s=-1} = B = -4$$

$$\text{and } (s+2)F(s) = \frac{2(s+3)}{s(s+1)} \Big|_{s=-2} = C = 1$$

So $F(s) = \frac{3}{s} + \frac{-4}{s+1} + \frac{1}{s+2}$ yields $f(t) = (3 - 4e^{-t} + e^{-2t})u(t)$

Section 14-6: Initial and Final Value Theorems

P14.6-1

(a) $f(0) = \lim_{s \rightarrow \infty} sF(s) = \lim_{s \rightarrow \infty} \frac{2s^2 - 3s + 4}{s^2 + 3s + 2} = \frac{2s^2}{s^2} = 2$

(b) $f(\infty) = \lim_{s \rightarrow 0} sF(s) = \frac{4}{2} = 2$

P14.6-2

initial value

$$\lim_{s \rightarrow \infty} sV(s) = \lim_{s \rightarrow \infty} \frac{s(s+16)}{s^2 + 4s + 12} = \lim_{s \rightarrow \infty} \frac{s^2 + 16s}{s^2 + 4s + 12} = 1 \quad \therefore \underline{v(0)=1}$$

final value

$$\lim_{s \rightarrow 0} s \left(\frac{s+16}{s^2 + 4s + 12} \right) = \lim_{s \rightarrow 0} \frac{s^2 + 16s}{s^2 + 4s + 12} = 0 \quad \therefore \underline{v(\infty)=0}$$

$$\text{Re}\{p_i\} < 0 \text{ since } p_i = -2 \pm 2.828j$$

P14.6-3

initial value : $\lim_{s \rightarrow \infty} sV(s) = \lim_{s \rightarrow \infty} \frac{s^2+10s}{3s^3+2s^2+1} = 0 \quad \therefore \underline{v(0)=0}$

final value

poles : $(3s^2+2s+1)$ yields $p_i = -0.333 \pm 0.471i \quad \therefore \text{Re}\{p_i\} < 0$

So $\lim_{s \rightarrow 0} sV(s) = \lim_{s \rightarrow 0} \frac{s(s+10)}{s(3s^2+2s+1)} = 10 \quad \therefore \underline{v(\infty)=10}$


P14.6-4

initial value: $\lim_{s \rightarrow \infty} sF(s) = \lim_{s \rightarrow \infty} \frac{-2s^2 - 14s}{s^2 - 2s + 10} = -2 \therefore \underline{f(0) = -2}$

final value: $s^2 - 2s + 10$ yields $p_i = 1 \pm 3i$ $\text{Re}\{p_1\} > 0 \therefore$ no final value exists

Section 14-7: Solution of Differential Equations Describing a Circuit

P14.7-1

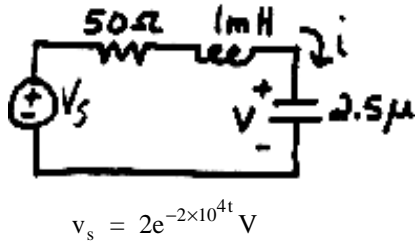

$i(0) = 1\text{A}, v(0) = 8\text{V}$

KVL: $50i + 0.001 \frac{di}{dt} + v = 2e^{-2 \times 10^4 t}$ (1)

also: $= 2.5 \times 10^{-6} \frac{dv}{dt}$ (2)

Take the transform of (1) & (2)

$50 I(s) + 0.001 [s I(s) - i(0)] + V(s) = \frac{2}{s + 2 \times 10^4}$ (3)

$I(s) = 2.5 \times 10^{-6} [s V(s) - v(0)]$ (4)

Solving for V(s) in (4) and plugging into (3) yields

$I(s) = \frac{s^2 + 1.4 \times 10^4 s - 1.6 \times 10^8}{(s+10^4)(s+2 \times 10^4)(s+4 \times 10^4)} = \frac{A}{s+10^4} + \frac{B}{s+2 \times 10^4} + \frac{C}{s+4 \times 10^4}$

$A = \frac{s^2 + 1.4 \times 10^4 s - 1.6 \times 10^8}{(s+2 \times 10^4)(s+4 \times 10^4)} \Big|_{s=-10^4} = \frac{-2 \times 10^8}{3 \times 10^8} = \frac{-2}{3}$


$B = \frac{s^2 + 1.4 \times 10^4 s - 1.6 \times 10^8}{(s+10^4)(s+4 \times 10^4)} \Big|_{s=-2 \times 10^4} = \frac{.4 \times 10^8}{2 \times 10^8} = \frac{1}{5}$

$C = \frac{s^2 + 1.4 \times 10^4 s - 1.6 \times 10^8}{(s+10^4)(s+2 \times 10^4)} \Big|_{s=-4 \times 10^4} = \frac{8.8 \times 10^8}{6 \times 10^8} = \frac{22}{15}$

$\therefore I(s) = \frac{-2/3}{s+10^4} + \frac{1/5}{s+2 \times 10^4} + \frac{22/15}{s+4 \times 10^4}$

$\Rightarrow \underline{i(t) = \frac{1}{15} [-10e^{-10^4 t} + 3e^{-2 \times 10^4 t} + 22e^{-4 \times 10^4 t}]} \text{A}$

P14.7-2

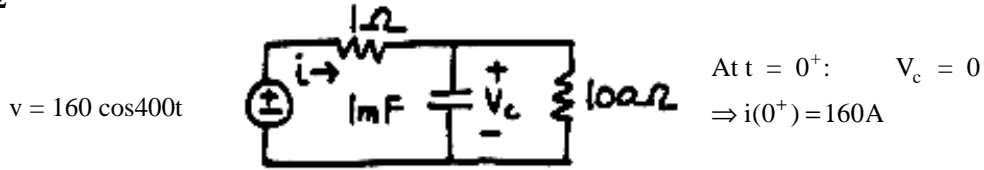

KCL at top : $10^{-3} \frac{dv_c}{dt} + v_c/100 = i$ (1)

also : $i = (v - v_c)/1 \Rightarrow v_c = v - i$ (2)

(2) into (1) yields : $\frac{di}{dt} + 1010i = 1600 \cos 400t - 6.4 \times 10^4 \sin 400t$

Taking the Laplace Transform yields:

$$sI(s) - i(0) + (1010)I(s) = \frac{1600s}{s^2 + (400)^2} - \frac{(6.4 \times 10^4)(400)}{s^2 + (400)^2}$$

$$\Rightarrow I(s) = \frac{160}{s + 1010} + \frac{1600s - 2.5 \times 10^7}{(s + 1010)[s^2 + (400)^2]}$$

$I(s) = I_1 + I_2(s)$

Now let $I_2(s) = \frac{A}{s + 1010} + \frac{B}{s + j400} + \frac{B^*}{s - j400}$

$$A = \frac{1600s - 2.5 \times 10^7}{s^2 + (400)^2} \Big|_{s = -1010} = -23.1$$

$$B = \frac{1600s - 2.5 \times 10^7}{(s + 1010)(s - j400)} \Big|_{s = -j400} = \frac{2.56 \times 10^7 \angle 14^\circ}{8.69 \times 10^5 \angle 68.4^\circ} = 11.5 - j27.2$$


$$B^* = 11.5 + j27.2$$

$$\therefore I(s) = I_1(s) + I_2(s) = \frac{136.9}{s + 1010} + \frac{11.5 - j27.2}{s + j400} + \frac{11.5 + j27.2}{s - j400}$$

$$\Rightarrow i(t) = 136.9e^{-1010t} + 2(11.5) \cos 400t - 2(27.2) \sin 400t$$

$$\underline{i(t) = 136.9e^{-1010t} + 23.0 \cos 400t - 54.4 \sin 400t}$$

P14.7-3

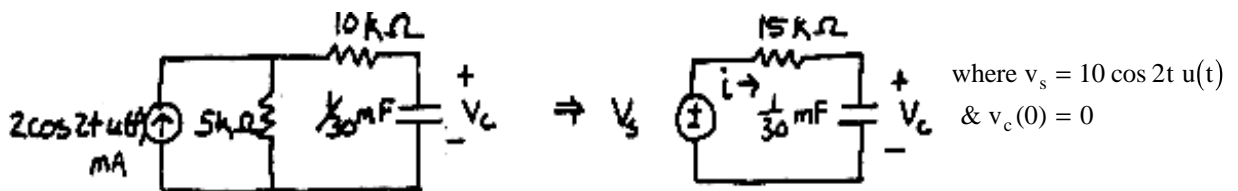

KVL : $v_c + 15i = 10 \cos 2t$ but $i = \frac{1}{30} \frac{dv_c}{dt} \Rightarrow \frac{dv_c}{dt} + 2v_c = 20 \cos 2t$

Taking the Laplace Transform yields:

$$sV_c(s) - v_c(0) + 2V_c(s) = 20s/(s^2 + 4)$$

$$\Rightarrow V_c(s) = \frac{20s}{(s+2)(s^2+4)} = \frac{A}{s+2} + \frac{B}{s+j2} + \frac{B^*}{s-j2}$$

$$A = \frac{20s}{s^2+4} \Big|_{s=-2} = \frac{-40}{8} = -5$$

$$B = \frac{20s}{(s+2)(s-j2)} \Big|_{s=-j2} = j5/(1+j) = 5/2 + j5/2$$


$$B^* = 5/2 - j5/2$$

$$\therefore V_c(s) = -5/(s+2) + (5/2 - j5/2)/(s+j2) + (5/2 + j5/2)/(s-j2)$$

$$\Rightarrow \underline{v_c(t) = -5e^{-2t} + 5(\cos 2t + \sin 2t) \text{ V}}$$

P14.7-4 From Prob. 9.9-11 : $v_c(0) = 0$, $i_L(0) = 0$

after source transformation

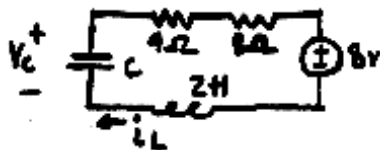

$$\text{KVL : } v_c + 12i_L + 2 di_L/dt = -8 \quad (1)$$

$$\text{also : } i_L C dv_c/dt \quad (2)$$

Laplace Transform of (1) & (2) yields:

$$V_c(s) + 12 I_L(s) + 2[sI_L(s) - i_L(0)] = -8/s \quad (3)$$

$$I_L(s) = C [sV_c(s) - v_c(0)] \quad (4)$$

$$(4) \text{ into } (3) \text{ yields : } V_c(s) = \frac{-(8/2)C}{s(s^2 + 6s + 1/2C)}$$

$$(a) \quad C = 1/18: V_c(s) = -72/s(s+3)^2 = a/s + b/(s+3) + c/(s+3)^2$$

$$\Rightarrow a = -8, b = 8, c = 24, \text{ so } V_c(s) = -8/s + 8/(s+3) + 24/(s+3)^2$$

$$\therefore \underline{v_c(t) = -8 + 8e^{-3t} + 24te^{-3t}}$$

$$(b) \quad C = 1/10: V_c(s) = -40/s(s+1)(s+5) = a/s + b/(s+1) + c/(s+5)$$


$$\Rightarrow a = -8, b = 10, c = -2, \text{ so } V_c(s) = -8/5 + b/(s+1) - 2/(s+5)$$

$$\therefore \underline{v_c(t) = -8 + 10e^{-t} - 2e^{-5t}}$$

P14.7-5

By inspection $v_c(0^-) = 10V, i_L(0^-) = 0A$

@ $t > 0$

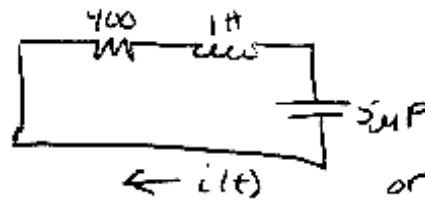

$$L \frac{d^2 i}{dt^2} + 400 \frac{di}{dt} + \frac{i_c}{C} = 0$$

$$\frac{di}{dt} = 10$$

$$L \left(s^2 I(s) - si(0) - \frac{di(0)}{dt} \right) + R (sI(s) - i(0)) + \frac{I(s)}{C} = 0$$

Solving for $I(s)$ and plugging in values yields



$$I(s) = \frac{-[Is(0) + 1(10) + 400(0)]}{s^2 + 400s + 2 \times 10^5} = \frac{-10}{s^2 + 400s + 2 \times 10^5}$$

The poles are $p_i = -200 \pm 400i$

$$\therefore i(t) = \underline{\underline{-\frac{1}{40} e^{-200t} \sin(400t) A}}$$

Section 14-8: Circuit Analysis Using Impedance and Initial Conditions



P14.8-1

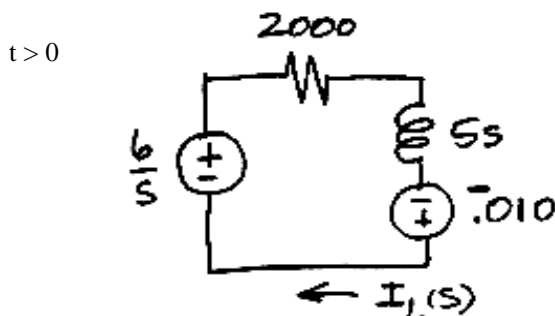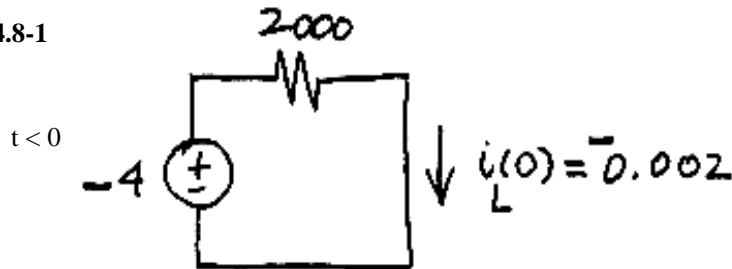

$$I_L(s) = \frac{\frac{6}{s} - 0.010}{5s + 2000} = \frac{\frac{6}{s} - 0.002s}{s(s+400)} = \frac{.003}{s} = \frac{.005}{s+400}$$

$$i_L(t) = \begin{cases} 2\text{mA} & t < 0 \\ 3 - 5e^{-400t} \text{mA} & t > 0 \end{cases}$$

P14.8-2

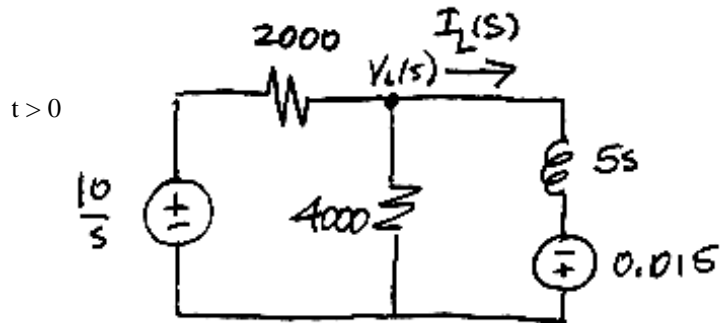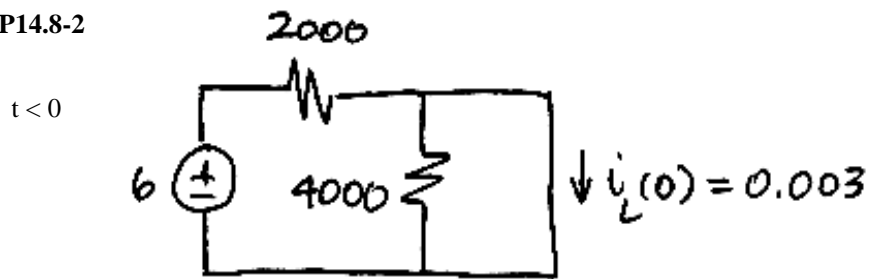

$$0 = \frac{V_L(s) - \frac{10}{s}}{2000} + \frac{V_L(s)}{4000} + \frac{V_L(s) - (-0.015)}{5s}$$

$$\Rightarrow V_L(s) = -\frac{\frac{8}{3}}{s + \frac{4000}{15}}$$


$$I_L(s) = \frac{V_L(s) + 0.015}{5s} = -\frac{\frac{8}{15}}{s \left(s + \frac{4000}{15} \right)} + 0.015$$

$$I_L(s) = \frac{0.005}{s} - \frac{0.002}{s + \frac{4000}{15}}$$


$$i_L(t) = 5 - 3e^{-\frac{4000}{15}t} \text{ mA}, t > 0$$

P14.9-3

$t < 0$

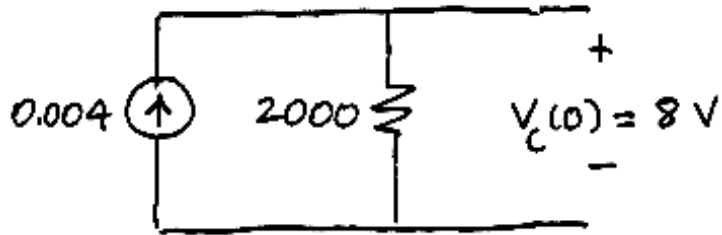

$t > 0$

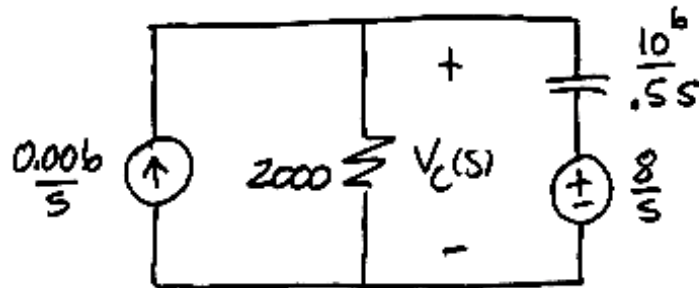



$$-\frac{0.006}{s} + \frac{V_c(s)}{2000} + \frac{V_c(s) - \frac{8}{s}}{\frac{10^6}{.5s}} = 0$$

$$-\frac{6000}{s} + 500V_c(s) + 0.5s\left(V_c(s) - \frac{8}{s}\right) = 0$$

$$V_c(s) = \frac{8s + 12000}{s(s+1000)} = \frac{12}{s} - \frac{4}{s+1000}$$

$$V_c(t) = 12 - 4e^{-1000t} \text{ V, } t > 0$$

P14.8-4

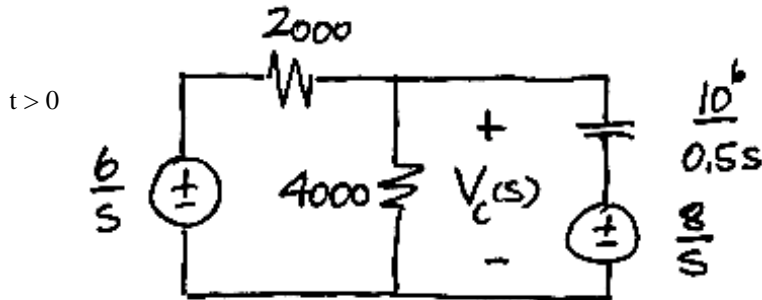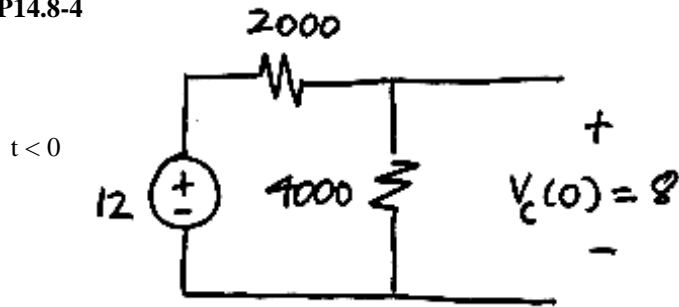


$$\frac{V_c(s) - \frac{6}{s}}{2000} + \frac{V_c(s)}{4000} + \left(\frac{0.5s}{10^6}\right) \left(V_c(s) - \frac{8}{s}\right) = 0$$

$$500 \left(V_c(s) - \frac{6}{s}\right) + 250 V_c(s) + 0.5s \left(V_c(s) - \frac{8}{s}\right) = 0$$

$$V_c(s) = \frac{6000 + 8s}{s(s+1500)} = \frac{4}{s} + \frac{4}{s+1500}$$

$$v_c(t) = 4 + 4e^{-1500t} \text{ V}, t > 0$$


P14.8-5

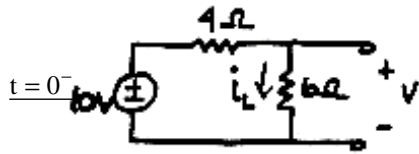

Steady - state

$$i_L(0) = \frac{10V}{10\Omega} = 1A, V(0) = 10\left(\frac{6}{6+4}\right) = 6V$$

$t > 0$

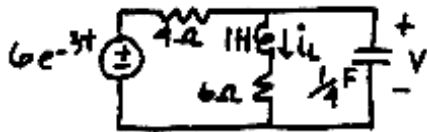

$$\text{KVL rt. mesh: } v - 6i_L - di_L/dt = 0 \quad (1)$$

$$\text{KCL top node: } v + dV/dt + 4i_L = 6e^{-3t} \quad (2)$$

Taking Laplace Transforms of (1) & (2) :

$$V(s) - (6+s)I_L(s) = -1 \quad (3)$$

$$(1+s)V(s) + 4I_L(s) = 6 + 6/(s+3) = (6s+24)/(s+3) \quad (4)$$

Using Cramer's rule on (3) & (4) yields


$$V(s) = \frac{-4 + (6+s)\left(\frac{6s+24}{s+3}\right)}{-4 + (1+s)(6+s)} = \frac{6s^2 + 56s + 132}{(s+3)(s+2)(s+5)} = \frac{A}{s+2} + \frac{B}{s+3} + \frac{C}{s+5}$$

$$A = (s+2)V(s)|_{s=-2} = 44/3, B = (s+3)V(s)|_{s=-3} = -9, C = (s+5)V(s)|_{s=-5} = 1/3$$

$$\therefore V(s) = 44/3/(s+2) - 9/(s+3) + 1/3/(s+5)$$

$$\Rightarrow \underline{v(t) = 44/3e^{-2t} - 9e^{-3t} + (1/3)e^{-5t} \text{ V}}$$

P14.8-6

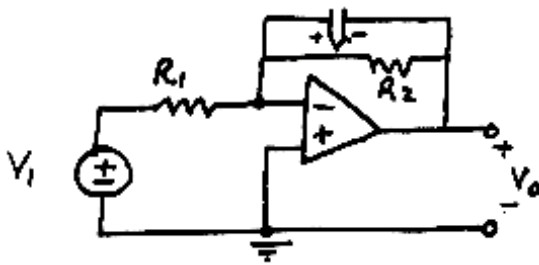

$$v_2 = 0$$

KCL node v_2

$$\frac{v_2 - v_1}{R_1} + C \frac{d}{dt} [v_2 - v_0] + \frac{v_2 - v_0}{R_2} = 0$$

$$\Rightarrow \frac{v_1}{R_1} + C \frac{dv_0}{dt} + \frac{v_0}{R_2} = 0$$

Taking Laplace Transform

$$\frac{V_1(s)}{1000} + 10^{-6} [sV_0(s) - 5] + \frac{V_0(s)}{1000} = 0$$

$$V_1(s) = \frac{10}{s} \Rightarrow V_0(s) = -\frac{10}{s} + \frac{15}{s+1000}$$

$$\therefore \underline{v_0(t) = 15e^{-1000t} - 10}, t \geq 0$$

P14.8-7

$$v_1(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \Rightarrow V_1(s) = 3sI_1 + sI_2 - 9 \quad (1)$$

$$v_2(t) = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \Rightarrow V_2(s) = sI_1 + 2sI_2 - 8 \quad (2)$$

$$\text{from KCL : } I_3 = I_1 + I_2 \quad (3)$$

$$\text{from KVL : } \frac{5}{s} = 2I_3 + V_1 \quad (4)$$

$$\& V_1 = V_2 + 1I_2 \quad (5)$$

$$\text{Plugging (1) and (3) into (4)} \Rightarrow (3s+2)I_1 + (s+2)I_2 = 9 + \frac{5}{s}$$


$$\text{Plugging (1) and (2) into (5)} \Rightarrow 2sI_1 - (s+1)I_2 = 1$$

$$\therefore \Delta = \begin{vmatrix} 3s+2 & s+2 \\ 2s & -(s+1) \end{vmatrix} = -[5s^2 + 9s + 2]$$

$$\text{So } I_2 = \frac{1}{\Delta} \begin{vmatrix} 3s+2 & \frac{5}{s} + 9 \\ 2s & 1 \end{vmatrix} = \frac{15s+8}{5s^2+9s+2} = \frac{3s+1.6}{(s+0.26)(s+1.54)} = \frac{A}{s+0.26} + \frac{B}{s+1.54}$$

$$\left. \begin{array}{l} A = \frac{3s+1.6}{s+1.54} \Big|_{s=-0.26} = 0.64 \\ B = \frac{3s+1.6}{s+0.26} \Big|_{s=-1.54} = 2.36 \end{array} \right\} I_2 = \frac{0.64}{s+0.26} + \frac{2.36}{s+1.54}$$

$$i_2(t) = 0.64e^{-0.26t} + 2.36e^{-1.54t} u(t) \text{ A}$$

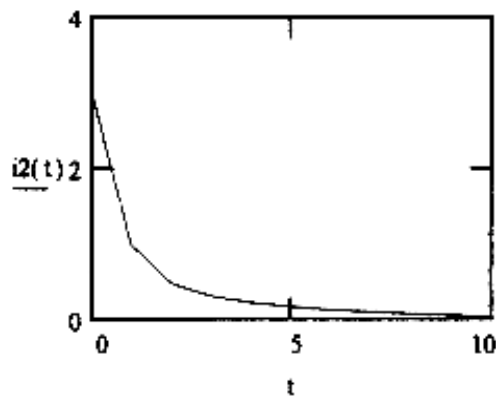

Section 14-9: Transfer Function and Impedance

P14.9-1

We want: $H(s) = a$

We have: $H(s) = \frac{Z_2}{Z_1 + Z_2}$ where $Z_1 = \frac{R_1 + 1/C_1 s}{R_1 C_1 s + 1}$ and $Z_2 = \frac{R_2}{R_2 C_2 s + 1}$


let $\tau_1 = R_1 C_1$ and $\tau_2 = R_2 C_2$

$$\therefore H(s) = \frac{R_2(\tau_1 s + 1)}{R_1(\tau_2 s + 1) + (\tau_1 s + 1) R_2}$$

When $\tau_1 = \tau_2 = \tau \Rightarrow H(s) = \frac{R_2(\tau s + 1)}{(R_1 + R_2)(\tau s + 1)} = \frac{R_2}{R_1 + R_2} = \text{constant}$

\therefore require $R_1 C_1 = R_2 C_2$

P14.9-2

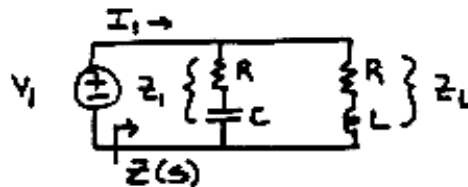


$$\begin{aligned} Z_1 &= R + 1/Cs & Z_L &= R + Ls \\ Z(s) &= \frac{Z_1 Z_L}{Z_1 + Z_L} = \frac{(R + 1/sC)(R + Ls)}{R + 1/sC + R + Ls} \\ &= R \frac{LCs^2 + (RC + L/R)s + 1}{LCs^2 + 2RCs + 1} \end{aligned}$$

Now require: $RC + L/R = 2RC$

$$\Rightarrow L = R^2 C \text{ then } Z = R$$

P14.9-3

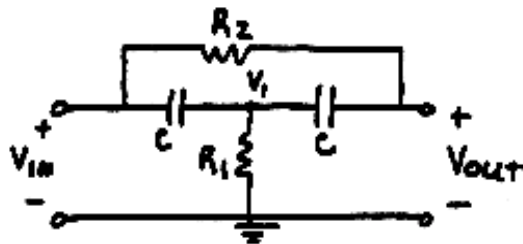

$$\text{KCL at } V_{in} : (V_{in} - V_1) sC + (V_{in} - V_{out}) / R_2 = 0$$

$$\Rightarrow V_1 = \frac{(1 + sCR_2) V_{in} - V_{out}}{sCR_2} \quad (1)$$

$$\text{KCL at } V_1 : V_1 / R_1 + (V_1 - V_{in}) sC + (V_1 - V_{out}) sC = 0 \quad (2)$$

Plugging (1) into (2) yields :

$$\frac{V_{out}}{V_{in}} = \frac{1 + (2R_1 + R_2)Cs + R_1 R_2 C^2 s^2}{1 + 2R_1 Cs + R_1 R_2 C^2 s^2}$$

P14.9-4

(a) From voltage division

$$V_0(s) = V_1(s) \left[\frac{150 + 2 \times 10^{-3}s}{150 + 2 \times 10^{-3}s + 100 + 3 \times 10^{-3}s} \right]$$

$$\Rightarrow H(s) = \frac{V_0(s)}{V_1(s)} = \frac{1.5 \times 10^5 + 2s}{2.5 \times 10^5 + 2s}$$


(b) Now $V_1(s) = 100/s$

$$\text{so } V_0(s) = (100/s) \frac{(1.5 \times 10^5 + 2s)}{2.5 \times 10^5 + 5s} = \frac{100(1.5 \times 10^5 + 2s)}{s(2.5 \times 10^5 + 5s)} = \frac{A}{s} + \frac{B}{s + 5 \times 10^4}$$

$$A = sV_0(s)|_{s=0} = 3, \quad B = (s + 5 \times 10^4)V_0(s)|_{s=-5 \times 10^4} = -20$$

$$\Rightarrow V_0(s) = 3/s + -20/(s + 5 \times 10^4) \quad \therefore v_0(t) = 3 - 20e^{-5 \times 10^4 t} \text{ V } t > 0$$

P14.9-5

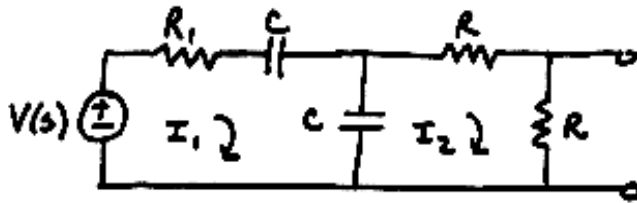


$$(a) \quad V(s) = \left(R_1 + \frac{1}{Cs} + \frac{1}{Cs} \right) I_1(s) - \frac{1}{Cs} I_2 \quad (1)$$

$$0 = \left(R + R + \frac{1}{Cs} \right) I_2 - \frac{1}{Cs} I_1 \quad (2)$$

$$\text{Solving for } I_2 \Rightarrow I_2 = \frac{V(s) \left(\frac{1}{Cs} \right)}{\left(R_1 + \frac{2}{Cs} \right) \left(2R + \frac{1}{Cs} \right) - \frac{1}{(Cs)^2}}$$

$$\therefore \frac{V_0(s)}{V(s)} = \frac{RCs}{[R_1Cs + 2][2RCs + 1] - 1} = \frac{s}{2R_1C \left[s^2 + \frac{4RC + R_1C}{2RR_1C^2} s + \frac{1}{(2RR_1C^2)^2} \right]}$$


(b)

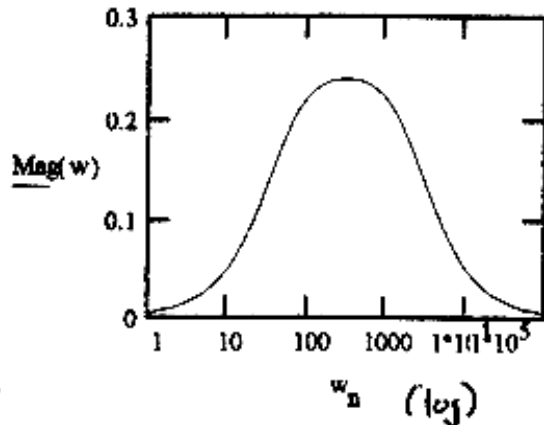

P14.9-6

$$V_s(s) = 1/s$$

Use voltage divider

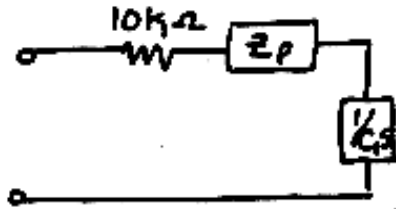

$$Z_p = \frac{(1/Cs)(Ls)}{\frac{1}{Cs} + Ls} = \frac{Ls}{1 + LCs^2}$$

$$LC = 1.67 \times 10^{-8}$$

$$H(s) = \frac{1/C_1s}{1/C_1s + \frac{Ls}{1 + LCs^2} + 10^4} = \frac{(1 + LCs^2)}{(1 + LCs^2) + LC_1s^2 + 10^4C_1s(1 + LCs^2)}$$

$$= \frac{1 + 1.67 \times 10^{-8} s^2}{1 + 5 \times 10^{-4} s + 10^{-7} s^2 + 8.33 \times 10^{-12} s^3}$$

$$\text{So } V(s) = \frac{1}{s} H(s) = \frac{1}{s} + \frac{2.65}{s + 4644} + \frac{0.826 + j.604}{s + s_1} + \frac{0.826 + j.604}{s + s_1^*}$$

$$\text{where } s_1 = -3678 + j 3509$$

$$\therefore v(t) = 1 - 2.65e^{-4644t} + e^{-3678t} [1.65 \cos 3509 - 1.209 \sin 3509t]$$

$$\underline{v(t)_0 = 1 - 2.65e^{-4644t} + 2.05e^{-3678t} \cos(3509t + 0.632)}$$

P14.9-7 $\frac{V_0(s)}{V(s)} = \frac{1/Cs}{R + Ls + 1/Cs} = \frac{1/LC}{s^2 + \frac{R}{L}s + \frac{1}{LC}} = H(s)$


Mathcad spreadsheet:

$$N : 100 \quad n := 0..N$$

$$\omega_{\min} := 100 \quad \omega_{\max} := 100000 \quad m := \ln\left(\frac{\omega_{\max}}{\omega_{\min}}\right) \quad \omega_n := \omega_{\min} e^{\frac{n}{N}m}$$

$$s_n := \omega_n \cdot j$$

$$H_n := \frac{1.136 \cdot 10^7}{(s_n)^2 + 625 \cdot s_n + 1.136 \cdot 10^7} \quad \text{Mag}(\omega) := |H_n|$$

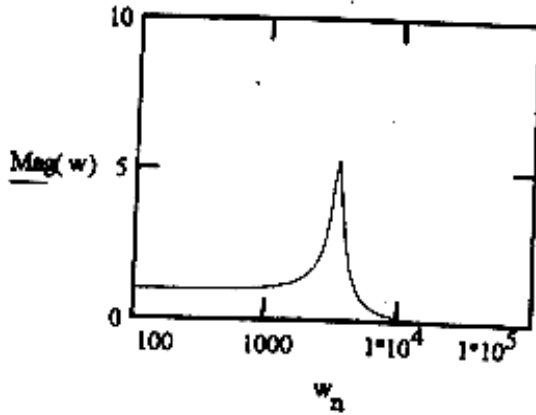


Now if $\omega = 2\pi f$, then $\omega := 9.42 \cdot 10^4 \text{ rad/sec}$

and plugging this into the transfer function: $H := \frac{1.136 \cdot 10^7}{(\omega \cdot j)^2 + 625 \cdot \omega \cdot j + 1.136 \cdot 10^7}$

yields a magnitude of $|H| = 0.001$

P14.9-8

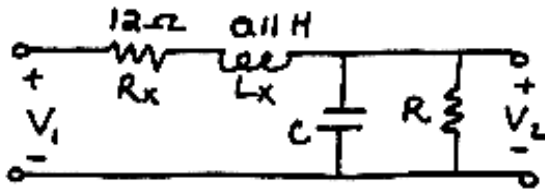


a)

$$Z_2 = \frac{R \left(\frac{1}{Cs} \right)}{R + \frac{1}{Cs}} = \frac{R}{RCs + 1}$$


$$Z_1 = R_x + L_x s$$

$$\frac{V_2}{V_1} = \frac{Z_2}{Z_1 + Z_2} = \frac{\frac{R}{RCs + 1}}{R_x + L_x s + \frac{R}{RCs + 1}} = \frac{R}{LRCs^2 + (L + R_x RC)s + R_x + R}$$
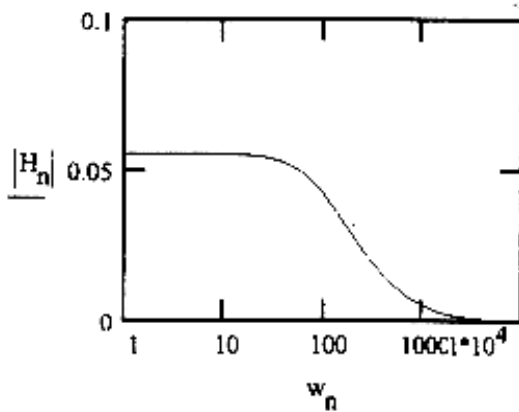
$$\frac{V_2}{V_1} = \frac{R/LRC}{s^2 + \frac{(L + R_x RC)}{LRC}s + \frac{R_x + R}{LRC}}$$



P14.9-9

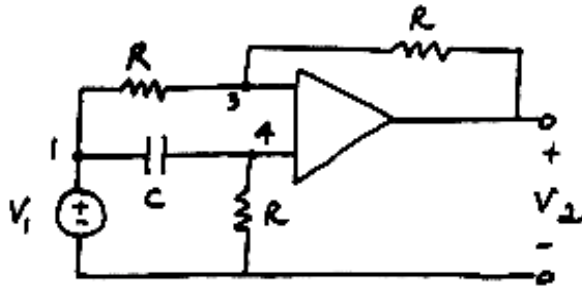

$$\text{node 3: } -GV_2 + 2GV_3 - GV_1 = 0 \quad (1)$$


$$\text{node 4: } (G+sC)V_4 - sCV_1 = 0 \quad (2)$$

$$\text{also: } V_3 = V_4 \quad (3)$$

Solving (1) \rightarrow (3) for V_2/V_1 yields

$$\underline{H(\omega) = \frac{V_2}{V_1} = \frac{(G-Cs)}{(G+Cs)}} \quad |H| = 1 \text{ for } \omega \geq 0$$

P14.9-10

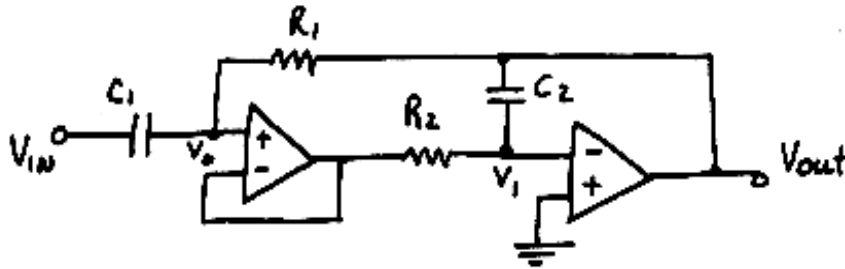

$$\text{KCL at } V_0 : (V_0 - V_{in})sC_1 + \frac{V_0 - V_{out}}{R_1} = 0 \text{ or } (R_1C_1s+1)V_0 = R_1C_1sV_{in} + V_{out}$$

$$\text{KCL at } V_1 = 0 : \frac{V_0}{R_2} + V_{out} + sC_2 = 0 \text{ or } V_0 = -R_2C_2sV_{out}$$

Solving for V_{out}/V_{in} from (1) & (2) get


$$\frac{V_{out}}{V_{in}} = \frac{-R_1C_1s}{R_1R_2C_1C_2s^2 + R_2C_2s+1}$$

$$\text{or } T(s) = \frac{-\frac{1}{R_2C_2}s}{s^2 + \frac{1}{R_1C_1}s + \frac{1}{R_1R_2C_1C_2}} = \frac{-Q\omega_0 s}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

$$\text{where } R_1C_1 = Q/\omega_0$$

$$R_2C_2 = 1/Q\omega_0$$

P14.9-11

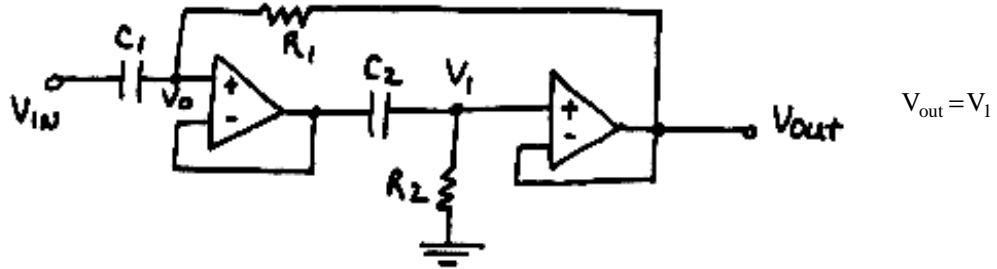

KCL at V_0 : $(V_0 - V_{in})sC_1 + \frac{V_0 - V_{out}}{R_1} = 0$ or $(R_1C_1s+1)V_0 = R_1C_1sV_{in} + V_{out}$


KCL at V_1 : $(V_1 - V_0)sC_2 + \frac{V_1}{R_2} = 0$ or $(R_2C_2s+1)V_{out} = R_2C_2sV_0$

Solving for V_{out}/V_{in} from (1) and (2) yields

$$\frac{V_{out}}{V_{in}} = \frac{R_1R_2C_1C_2s^2}{R_1R_2C_1C_2s^2 + R_1C_1s+1}$$

$$T(s) = \frac{s^2}{s^2 + \frac{1}{R_2C_2}s + \frac{1}{R_1R_2C_1C_2}} = \frac{s^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2} \quad \text{where } R_1C_1 = 1/Q\omega_0 \text{ and } R_2C_2 = Q/\omega_0$$

P14.9-12

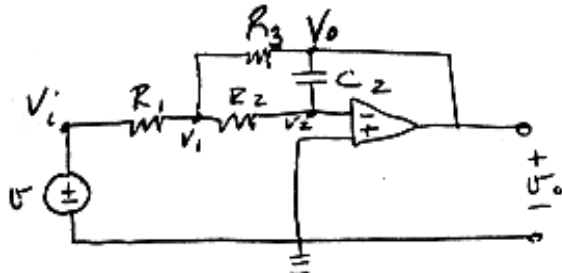

at node V_1 :

$$\frac{V_1 - V_i}{R_1} + \frac{V_1 - V_2}{R_2} + \frac{V_1 - V_0}{R_3} = 0$$

Rearranging @ node V_1 yields :

$$V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - \frac{V_0}{R_3} = \frac{V_i}{R_1} \quad (1)$$


@ node V_2 : $\frac{V_2 - V_1}{R_2} + (V_2 - V_0)sC_2 = 0$, but $V_2 = 0$

$$\therefore V_1 = -sC_2 R_2 V_0 \quad (2)$$

Plugging (2) into (1) and rearranging yields

$$\frac{V_0}{V_i} = \frac{-R_3}{sC_2R_2R_3 + sC_2R_1R_3 + sC_2R_1R_2 + R_1}$$

P14.9-13

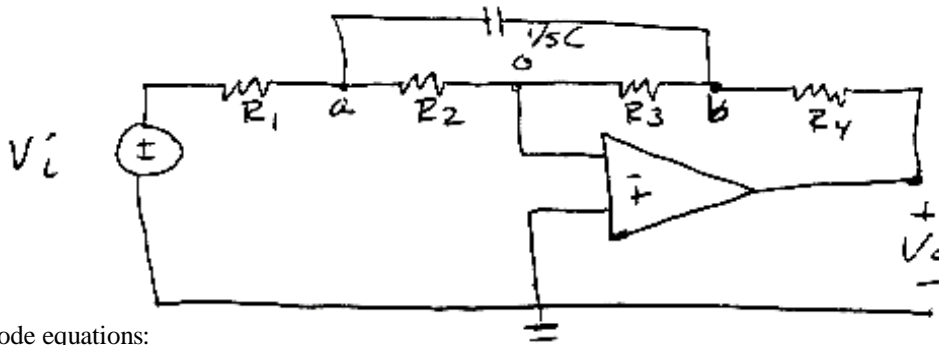

Node equations:

$$\frac{V_a - V_i}{R_1} + \frac{V_a}{R_2} + sC(V_a - V_b) = 0 \quad (1)$$

$$\frac{V_b}{R_3} + \frac{V_b - V_o}{R_4} - sC(V_a - V_b) = 0 \quad (2)$$

$$-\frac{V_b}{R_3} - \frac{V_a}{R_2} = 0 \Rightarrow V_b = -\frac{R_3}{R_2} V_a \text{ or } V_a = -\frac{R_2}{R_3} V_b \quad (3)$$

$$\Rightarrow (V_a - V_b) = \frac{R_2 + R_3}{R_2} V_a = -\frac{R_2 + R_3}{R_3} V_b$$

Solving yields

$$\frac{V_o}{V_i} = \frac{-R_3 + R_4 + sCR_4(R_2 + R_3)}{R_1 + R_2 + sCR_1(R_2 + R_3)}$$

P14.9-14 $H(s) = \frac{2}{s(s+2)(s+1)^2} = \frac{A}{s} + \frac{B}{s+2} + \frac{C}{s+1} + \frac{D}{(s+1)^2}$

$$\Rightarrow A = sH(s)|_{s=0} = 1$$

$$B = (s+2)H(s)|_{s=-2} = -2$$

$$D = (s+1)^2 H(s)|_{s=-1} = -1$$

$$C = \frac{d}{ds} \left[(s+1)^2 H(s) \right] \Big|_{s=-1} = 0$$

$$\Rightarrow h(t) = (1 - 2te^{-t} - e^{-2t})u(t)$$

$$h(0) = 0 \Rightarrow h(0) = \lim_{s \rightarrow \infty} sH(s)$$

$$h(\infty) = 1 \Rightarrow h(\infty) = \lim_{s \rightarrow 0} sH(s)$$

P14.9-15 $H(s) = 400 / (s^2 + 400s + 2 \times 10^5)$

$$F(s) = \frac{\omega}{(s+a)^2 + \omega^2} \Rightarrow f(t) = e^{-at} \sin \omega t \quad \text{Table 14.4-3}$$

gives $\omega = 400, \omega^2 = 160000$


$$\therefore H(s) = \frac{400}{(s+200)^2 + 160000} \quad \therefore \underline{h(t) = e^{-200t} \sin(400t) u(t)}$$

P14.9-16 $H(s) = \frac{4(s+3)}{s(s+2)^2} = \frac{A}{s} + \frac{B}{(s+2)} + \frac{C}{(s+2)^2}$

Solving partial fractions yields: $A=3, B=-3, C=-2$

$$\therefore H(s) = \frac{3}{s} - \frac{3}{s+2} - \frac{2}{(s+2)^2} \quad \therefore \underline{h(t) = 3 - 3e^{-1t} - 2te^{-2t}}$$

P14.9-17

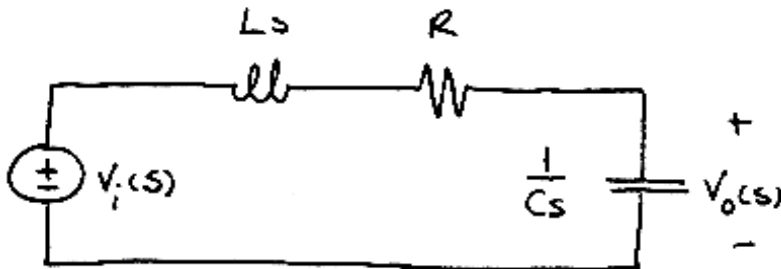

$$T(s) = \frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{Cs}}{Ls + R + \frac{1}{Cs}} = \frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

L	C	R	T(s)
2	.025	18	$\frac{20}{s^2 + 9s + 20} = \frac{20}{(s+4)(s+5)}$
2	.025	8	$\frac{20}{s^2 + 4s + 20}$
1	.391	4	$\frac{2.56}{s^2 + 4s + 2.56} = \frac{2.56}{(s + .8)(s + 3.2)}$
2	.125	8	$\frac{20}{s^2 + 4s + 4} = \frac{4}{(s+2)^2}$

$$\text{a) } T(s) = \frac{20}{(s+4)(s+5)}$$

$$\mathcal{L}\{\text{impulse response}\} = T(s) = \frac{20}{s+4} - \frac{20}{s+5}$$

$$\text{impulse response} = (20e^{-4t} - 20e^{-5t})u(t)$$

$$\mathcal{L}\{\text{step response}\} = \frac{T(s)}{s} = \frac{20}{s(s+4)(s+5)} = \frac{1}{s} + \frac{-5}{s+4} + \frac{4}{s+5}$$

$$\text{step response} = (1 + 4e^{-5t} - 5e^{-4t})u(t)$$

$$\text{b) } T(s) = \frac{20}{s^2 + 4s + 20}$$

$$\mathcal{L}\{\text{impulse response}\} = T(s) = \frac{5(4)}{(s+2)^2 + 4^2}$$

$$\text{impulse response} = 5e^{-2t} \sin 4t u(t)$$

$$\mathcal{L}\{\text{step response}\} = \frac{T(s)}{s} = \frac{20}{s(s^2 + 4s + 20)} = \frac{1}{s} + \frac{K_1s + K_2}{s^2 + 4s + 20}$$

$$20 = s^2 + 4s + 20 + s(K_1s + K_2) = s^2(1 + K_1) + s(4 + K_2) + 20 \Rightarrow K_1 = -1, K_2 = -4$$

$$\mathcal{L}\{\text{step response}\} = \frac{1}{s} + \frac{-(s+2)}{(s+2)^2 + 4^2} + \frac{-\frac{1}{2}(4)}{(s+2)^2 + 4^2}$$

$$\text{step response} = \left(1 - e^{-2t} \left(\cos 4t + \frac{1}{2} \sin 4t \right) \right) u(t)$$

$$\text{c) } T(s) = \frac{2.56}{(s + .8)(s + 3.2)}$$

$$\mathcal{L}\{\text{impulse response}\} = T(s) = \frac{1.07}{s + .8} - \frac{1.07}{s + 3.2}$$

$$\text{impulse response} = 1.07 (e^{-.8t} - e^{-3.2t})u(t)$$

$$\mathcal{L}\{\text{step response}\} = \frac{T(s)}{s} = \frac{2.56}{s(s + .8)(s + 3.2)} = \frac{1}{s} + \frac{-4}{s + .8} + \frac{\frac{1}{3}}{s + 3.2}$$

$$\text{d) } \text{step response} = \left(1 + \frac{1}{3}e^{-3.2t} - \frac{4}{3}e^{-.8t} \right) u(t)$$

$$\text{impulse response} = 4te^{-2t}u(t)$$

$$\text{step response} = (1 - (1 + 2t)e^{-2t})u(t)$$

P14.9-18

$$h(t) = \sqrt{2}e^{-t/\sqrt{2}} \sin(t/\sqrt{2})$$

(a) Using Table 14.5-1 with $\omega_{nb} = 1/\sqrt{2}$ and $\frac{\omega_n}{b} = \sqrt{2}$

$$\Rightarrow \left(\frac{\omega_n}{b}\right) (\omega_n b) = \omega_n^2 = (\sqrt{2}) (1/\sqrt{2}) = 1$$

$$\therefore b = \frac{\omega_n}{\sqrt{2}} = 1/\sqrt{2}$$

$$\therefore b = \sqrt{1-\xi^2} \Rightarrow \xi = 1/\sqrt{2}$$

$$\Rightarrow H(s) = \frac{\omega_n^2}{s^2 + 2\xi\omega_n s + \omega_n^2} = \frac{1}{s^2 + \sqrt{2}s + 1}$$

(b) $H(j\omega) = \frac{1}{(j\omega)^2 + \sqrt{2}j\omega + 1} = \frac{1}{1 - \omega^2 + j\sqrt{2}\omega}$

$$\therefore |H(j\omega)| = \frac{1}{\sqrt{(1-\omega^2)^2 + 2\omega^2}} = \frac{1}{\sqrt{1+\omega^4}}$$

P14.8-19

$$V_1(s) = 1, V_0(s) = \frac{3(s+2)}{s(s+3-j2)(s+3+j2)} = \frac{A}{s} + \frac{B}{s+3-j2} + \frac{B^*}{s+3+j2}$$

$$\Rightarrow A = sV_0(s) \Big|_{s=0} = 0.462$$

$$B = (s+3-j2)V_0(s) \Big|_{s=-3+j2} = 0.47 \angle -119.7^\circ$$

$$B^* = 0.47 \angle 119.7^\circ$$

$$\therefore V_0(s) = \frac{0.462}{s} + \frac{0.47 \angle 119.7^\circ}{s+3-j2} + \frac{0.47 \angle -119.7^\circ}{s+3+j2}$$

$$\text{So } v_0(t) = 0.462 + 2(0.47)e^{-3t} \cos(2t - 119.7^\circ) \quad t \geq 0$$

P14.9-20

(a) $H(s) = \frac{V_o}{V_1} = \frac{R/(1+RCs)}{LS + R/(1+RCs)} = \frac{R}{s^2 LCR + Ls + R}$

(b) have underdamped response $\Rightarrow s = -\frac{1}{2RC} \pm j \sqrt{1/LC - 1/(2RC)^2}$ (1)

$$T = 8 \text{ ms} \Rightarrow f = \frac{1}{8 \times 10^{-3}} = 125 \text{ Hz or } \omega = 250 \text{ } \pi \text{ rad/s}$$

Using (1): $s = \alpha + j\omega$


$$250\pi = \sqrt{1/10^{-6} - 10^{12}/4R^2} \Rightarrow R = 807.8 \Omega$$

(c) Critically damped when $\sqrt{1/LC - 1/(2RC)^2} = 0 \Rightarrow R = 1/2 \sqrt{L/C} = 1/2 \sqrt{10^6} = 500 \Omega$

Section 14-10: Convolution Theorem

P14.10-1

$$f(t) * f(t) = \mathcal{L}^{-1} [F(s) F(s)]$$

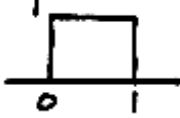pulse:  $\therefore F(s) = \frac{1-e^{-s}}{s}$

$$\therefore f * f = \mathcal{L}^{-1} \left[\frac{1-e^{-s}}{s} \right]^2 = \mathcal{L}^{-1} \left[\frac{1-2e^{-s}+e^{-2s}}{s^2} \right]$$

Now $\mathcal{L}^{-1} [1/s^2] = t u(t)$

$$\therefore \underline{f * f = t u(t) - 2(t-1) u(t-1) + (t-2)u(t-2)}$$




P14.10-2

$$f(t) = 2[u(t) - u(t-2)]$$

$$F(s) = \frac{2}{s} - \frac{2e^{-2s}}{s}$$
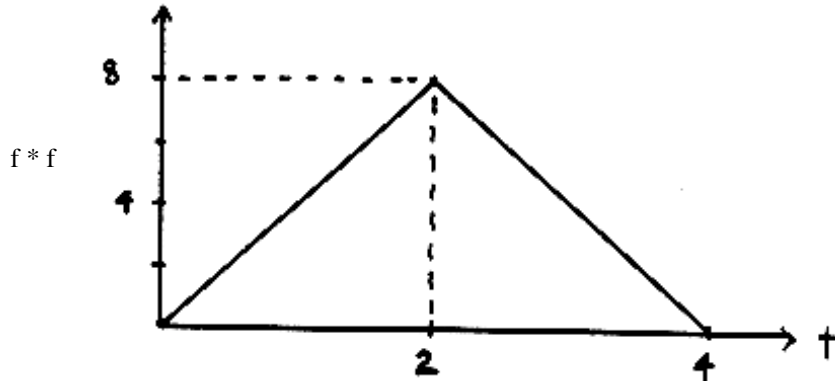
$$f * f = \mathcal{L}^{-1} [F(s)F(s)] = \mathcal{L}^{-1} \left[\frac{4}{s^2} - \frac{8e^{-2s}}{s^2} + \frac{4e^{-4s}}{s^2} \right] = 4t u(t) - 8(t-2)u(t-2) + 4(t-4)u(t-4)$$



P14.10-3

$$H(s) = \frac{V_2(s)}{V_1(s)} = \frac{1/Cs}{R+1/Cs} = \frac{1/RC}{s+1/RC}$$

$$V_2(t) = h(t) * v_1(t) = \mathcal{L}^{-1} [V_1(s) H(s)]$$

Now if $v_1(t) = tu(t)$, $V_1(s) = \frac{1}{s^2}$

$$\text{or } V_1(s) H(s) = \left(\frac{1}{s^2} \right) \left(\frac{\frac{1}{RC}}{s + \frac{1}{RC}} \right) = V_2(s)$$

and $\underline{v_2(t) = t - RC(1 - e^{-t/RC})}$, $t \geq 0$

P14.10-4 $h(t) * f(t) = \mathcal{L}^{-1} [H(s) F(s)]$ where $H(s) = \frac{1}{s^2}$ and $F(s) = \frac{1}{s+a}$

So $H(s) F(s) = \left(\frac{1}{s^2}\right) \left(\frac{1}{s+a}\right) = \frac{A}{s} + \frac{B}{s^2} + \frac{C}{s+a}$

Solving the partial fractions yields: $A = -1/a^2$, $B = 1/a$, $C = 1/a^2$

So $h(t) * f(t) = \frac{-1}{a^2} + \frac{t}{a} + \frac{e^{-at}}{a^2}$, $t \geq 0$

Section 14-11: Stability

P14.11-1 To have stable operation, the roots of the denominator must be in the left-hand s-plane


$\therefore 3 - k > 0$ or $k < 3$ so $0 \leq k < 3$ for stability

P14.11-2 We want the roots of the denominator to be in the left-hand side of the s-plane for stability,

so $6 - k < 0$ or $0 \leq k < 6$ will give this result


P14.11-3 $H(s) = \frac{s+2}{(s+1+i)(s+1-i)}$ zeros: $s = -2$

poles: $s = -1+i, -1-i$

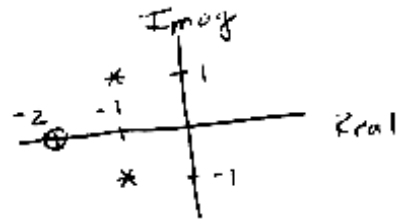

This circuit is stable since the poles are in the left-hand s-plane.

P14.11-4

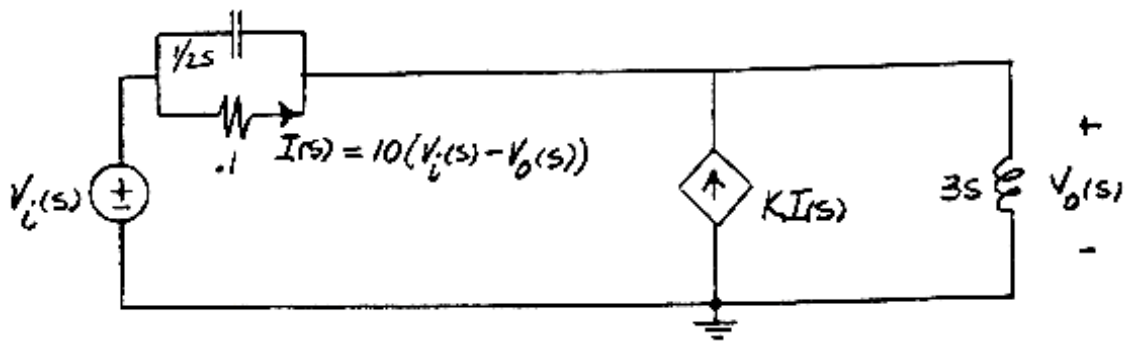

$$\frac{V_i(s) - V_0(s)}{\frac{1}{10}} + \frac{V_i(s) - V_0(s)}{\frac{1}{2s}} + K[10(V_i(s) - V_0(s))] = \frac{V_0(s)}{3s}$$

$$\Rightarrow T(s) = \frac{V_0(s)}{V_i(s)} = \frac{s^2 + 5(1+K)s}{s^2 + 5(1+K)s + \frac{1}{6}}$$

This circuit is stable for $K > -1$.

This circuit is critically damped when $(5(1+K))^2 - 4\left(\frac{1}{6}\right) = 0$

i.e., when $K = -1 + \sqrt{\frac{2}{75}}$ (but not for $K = -1 - \sqrt{\frac{2}{75}}$)


When $K=2$

$$T(s) = \frac{s^2 + 15s}{s^2 + 15s + \frac{1}{6}} \Rightarrow \omega_0 = \frac{1}{\sqrt{6}}, \quad Q = \frac{1}{15\sqrt{6}}$$

When $K = -1$, this circuit will oscillate at $\omega = \frac{1}{\sqrt{6}}$ rad/sec

Since $Q < \frac{1}{2}$, this circuit is overdamped.

P14.11-5

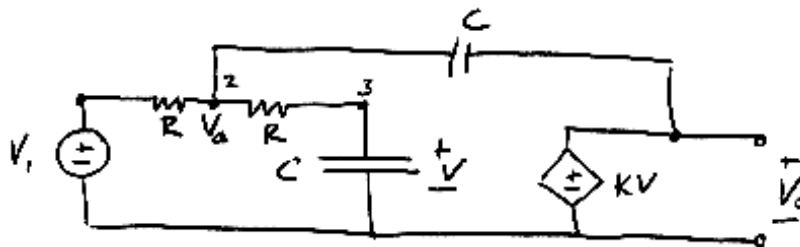

$$\text{node 2: } \frac{V_a - V_1}{R} + \frac{V_a - V}{R} + (V_a - V_0) sC = 0$$

$$\text{node 3: } \frac{V - V_a}{R} + (V - 0) sC = 0, \quad \text{also } V_0 = KV$$

$$\frac{V_0}{V_1} = \frac{K/R^2 C^2}{s^2 + \frac{(3-K)s}{RC} + \frac{1}{R^2 C^2}}$$

a) K for oscillator $\Rightarrow K = 3$


b) impulse response $K=1, R=1\text{k}\Omega, C = 0.5 \text{ mF}$

$$\frac{V_0}{V_1} = \frac{1/0.25}{s^2 + \frac{2s}{0.5} + \frac{1}{0.25}} = \frac{4}{s^2 + 4s + 4} = \frac{4}{(s+2)^2}$$

$$\therefore \underline{v_0(t) = 4te^{-2t} \text{ V}}$$

PSpice Problems

SP14-1

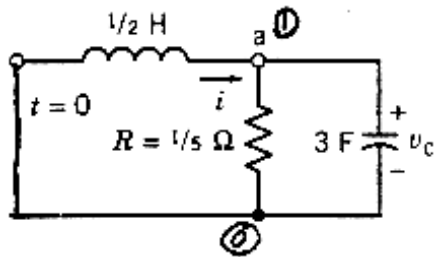


Circuit @ $t > 0$

Inut file:


```
R1 1 0 0.2
L1 1 0 0.5 IC=-60
C1 1 0 3 IC=12
```

```
.tran 0.1 10 UIC
.plot tran V(1)
.probe
.end
```

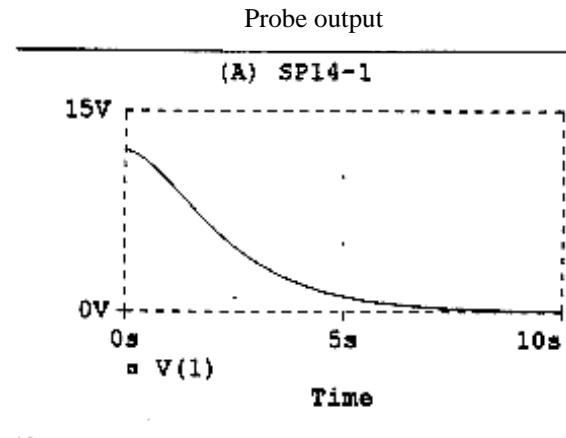

SP14-2

Circuit:

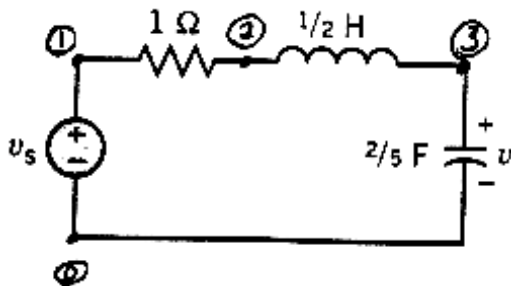


Inut file:


```
Vs 1 0 pulse(0 10 0 0 0 2
10)
R1 1 2 1
L1 2 3 0.5 IC=0
C1 3 0 0.4 IC=0
```

```
.tran 0.1 10 UIC
.plot tran V(3)
.probe
.end
```

Probe output

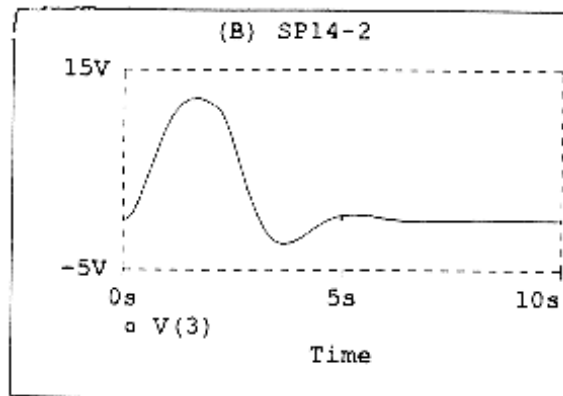

SP14-3

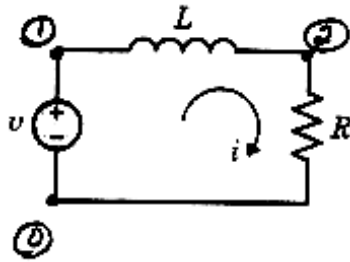


Input file:


```
Vs 1 0 pulse(0 2)
L1 1 2 0.5 IC=1
R1 2 0 1

.tran 0.1 5 UIC
.probe
.end
```

Probe output

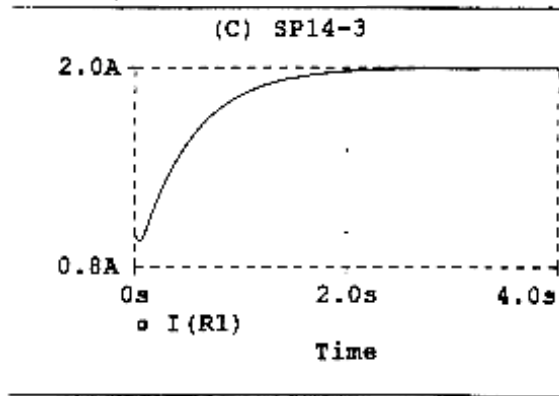

SP14-4

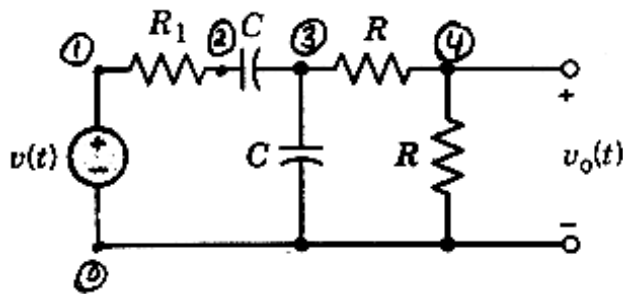


Probe output


Input file:

```
Vs 1 0 ac 1
R1 1 2 10
C1 2 3 100u
C2 3 0 100u
R2 3 4 50
R3 4 0 50

.ac dec 100 1
100k
.probe
.plot ac Vdb
(4)
.end
```

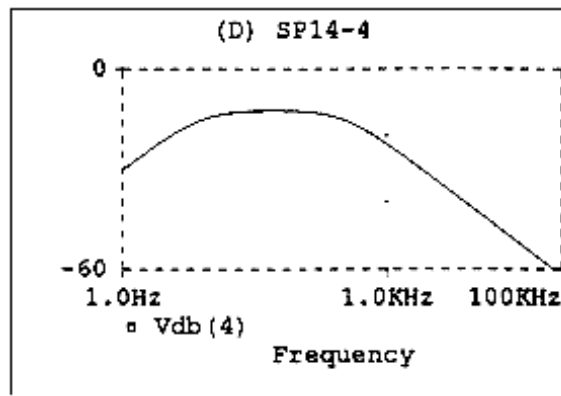


SP14-5

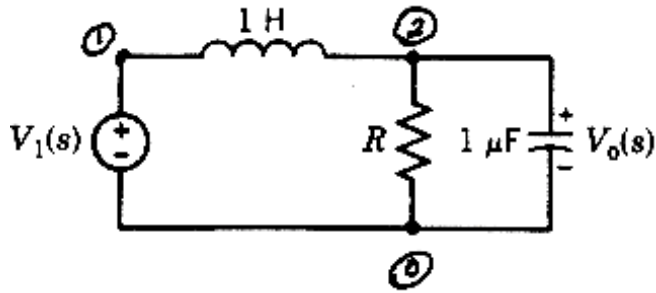

Input file:

```
Vs 1 0 pulse (0 1)
L1 1 2 1
R1 2 0 807.8
C1 2 0 1u
.tran 0.001 0.01
.probe
.end
```

Probe output

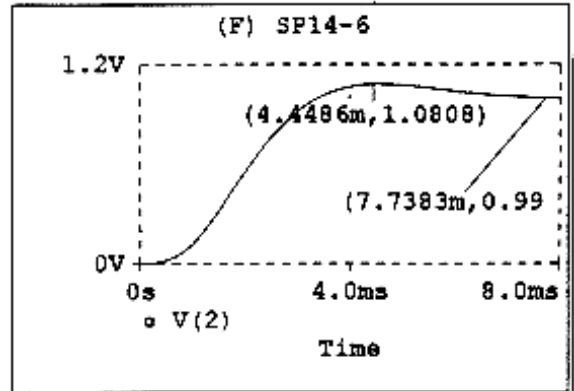

SP14-6

Input file:




```
Vs 1 0 pulse (0 1)
R1 1 2 50k
C1 2 3 2u
R2 3 4 50k
R3 4 5 262.5k *
C2 2 5 2u
XOA1 4 0 5 OA
```

* This value varies:

- 50 k Ω
- 62.5 k Ω
- 262.5 k Ω


```
.subckt OA 1 2 3
*nodes listed in order - + o
E 3 0 1 2 -1G
.ends OA

.tran 0.1 2
.probe
.end
```

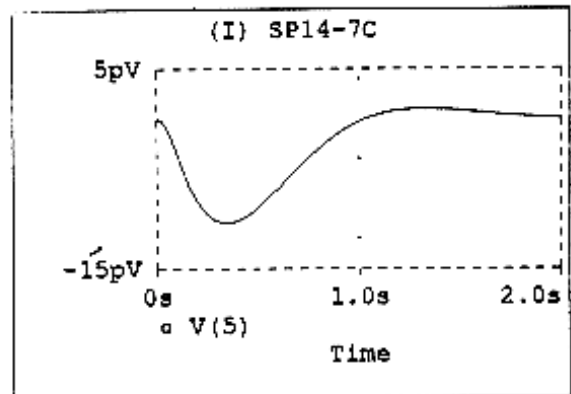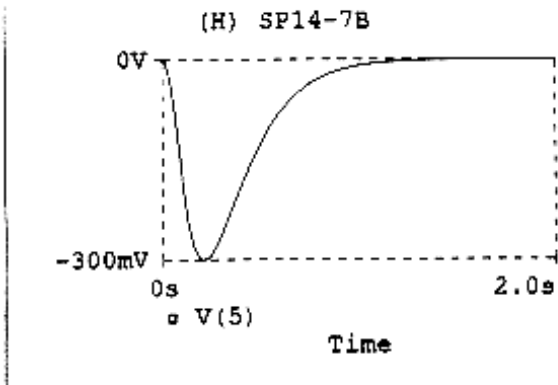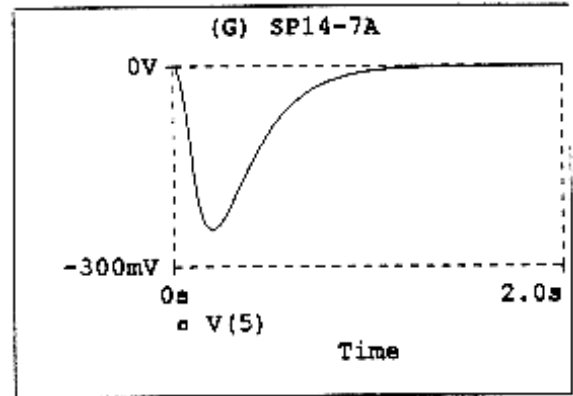

Verification Problems

VP 14-1

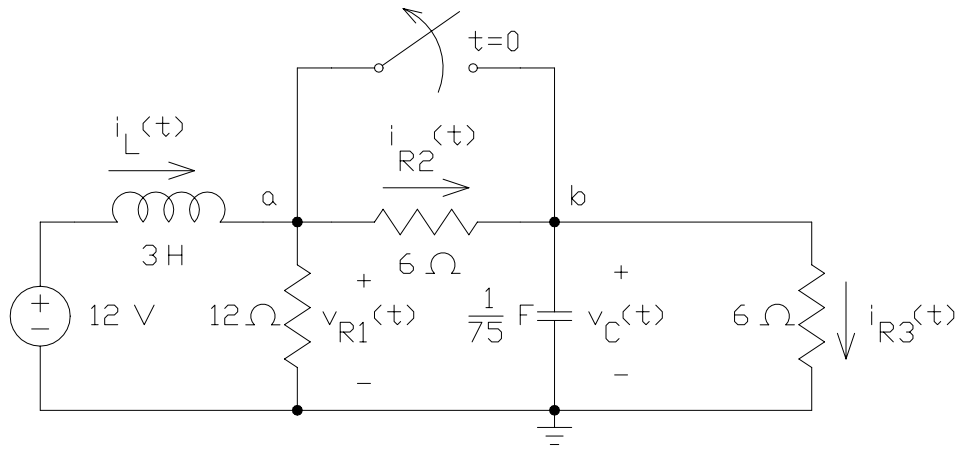

$$v_L(t) = 3 \frac{d}{dt} i_L(t) = -6e^{-2.1t} - 2e^{-15.9t}$$

$$i_C(t) = \frac{1}{75} \frac{d}{dt} v_C(t) = -0.092e^{-2.1t} - 0.575e^{-15.9t}$$

$$v_{R1}(t) = 12 - v_L(t) = 12 + 6e^{-2.1t} + 2e^{-15.9t}$$

$$i_{R2}(t) = \frac{12 - (v_L(t) + v_C(t))}{6} = 1 + 0.456e^{-2.1t} - 0.123e^{-15.9t}$$


$$i_{R3}(t) = \frac{v_C(t)}{6} = 1 + 0.548e^{-2.1t} + 0.452e^{-15.9t}$$

Thus,

$$-12 + v_L(t) + v_{R1}(t) = 0 \text{ and } i_{R2}(t) = i_C(t) + i_{R3}(t)$$

as required. The analysis is correct.

VP 14-2

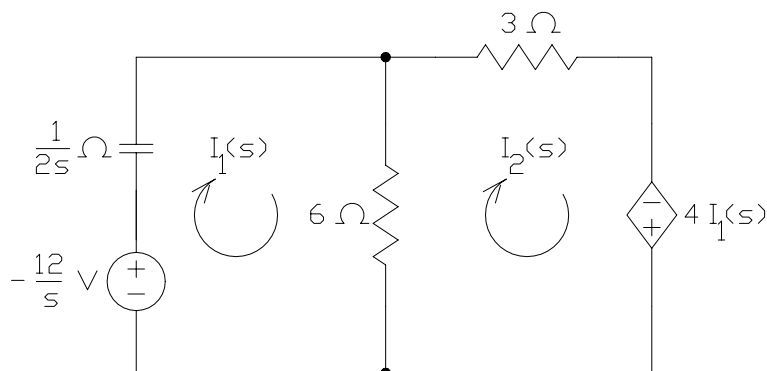

$$I_1(s) = \frac{18}{s - \frac{3}{4}} \text{ and } I_2(s) = \frac{20}{s - \frac{3}{4}}$$

KVL for left mesh: $\frac{12}{s} + \frac{1}{2s} \left(\frac{18}{s - \frac{3}{4}} \right) + 6 \left(\frac{18}{s - \frac{3}{4}} - \frac{20}{s - \frac{3}{4}} \right) = 0 \quad \checkmark$

KVL for right mesh: $-6 \left(\frac{18}{s - \frac{3}{4}} - \frac{20}{s - \frac{3}{4}} \right) + 3 \left(\frac{20}{s - \frac{3}{4}} \right) - 4 \left(\frac{18}{s - \frac{3}{4}} \right) = 0 \quad \checkmark$

The analysis is correct.

VP 14-3

Initial value of $I_L(s)$: $\lim_{s \rightarrow \infty} s \frac{s+2}{s^2+s+5} = 1 \quad \checkmark$

Final value of $I_L(s)$: $\lim_{s \rightarrow 0} s \frac{s+2}{s^2+s+5} = 0 \quad \checkmark$

Initial value of $V_C(s)$: $\lim_{s \rightarrow \infty} s \frac{-20(s+2)}{s(s^2+s+5)} = 0 \quad \times$

Final value of $V_C(s)$: $\lim_{s \rightarrow 0} s \frac{-20(s+2)}{s(s^2+s+5)} = -8 \quad \times$

Apparently the error occurred as $V_C(s)$ was calculated from $I_L(s)$. Indeed, it appears that $V_C(s)$ was

calculated as $-\frac{20}{s} I_L(s)$ instead of $-\frac{20}{s} I_L(s) + \frac{8}{s}$. After correcting this error


$$V_C(s) = -\frac{20}{s} \left(\frac{s+2}{s^2+s+5} \right) + \frac{8}{s}$$

Initial value of $V_C(s)$: $\lim_{s \rightarrow \infty} s \left(\frac{-20(s+2)}{s(s^2+s+5)} + \frac{8}{s} \right) = 8 \quad \checkmark$

Final value of $V_C(s)$: $\lim_{s \rightarrow 0} s \left(\frac{-20(s+2)}{s(s^2+s+5)} + \frac{8}{s} \right) = 0 \quad \checkmark$

Design Problems

DP 14-1

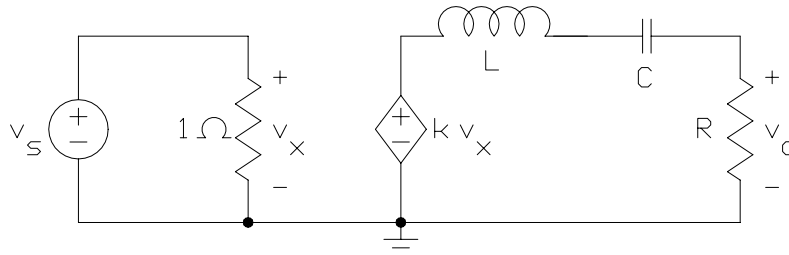

Equating the Laplace transform of the step response of the give circuit to the Laplace transform of the given step response:

$$V_o(s) = \frac{\frac{kR}{L}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} = \frac{5}{(s+4)^2}$$

Equating the poles:


$$s_{1,2} = \frac{-\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}}}{2} = -4 \pm 0$$

Summarizing the results of these comparisons:

$$\frac{R}{2L} = 4, R = \frac{2}{\sqrt{LC}} \text{ and } \frac{kR}{L} = 5$$

Pick $L = 1$ H, then $k = 0.625$ V/V, $R = 8 \Omega$ and $C = 0.0625$ F.

DP 14-2

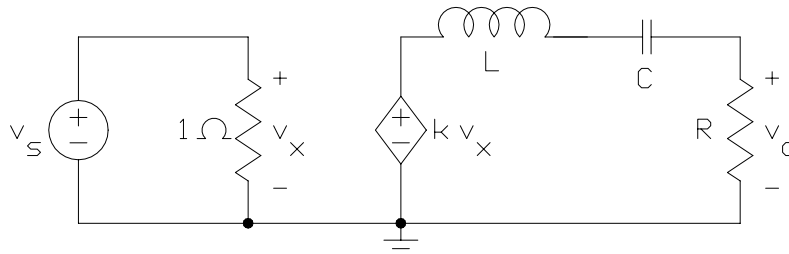

Equating the Laplace transform of the step response of the give circuit to the Laplace transform of the given step response:


$$V_o(s) = \frac{\frac{kR}{L}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} = \frac{10}{(s+4)^2 + 4} = \frac{10}{s^2 + 8s + 20}$$

Equating coefficients:

$$\frac{R}{L} = 8, \frac{1}{LC} = 20, \text{ and } \frac{kR}{L} = 10$$

Pick $L = 1$ H, then $k = 1.25$ V/V, $R = 8 \Omega$ and $C = 0.05$ F.

DP 14-3

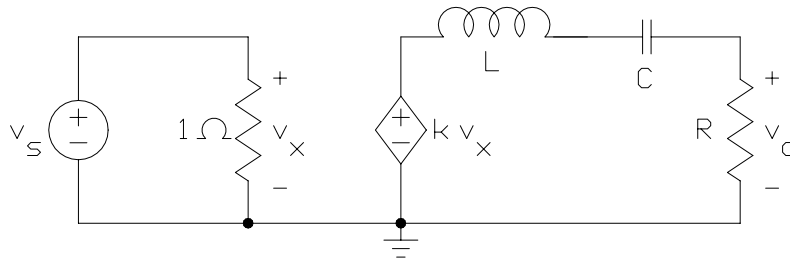

Equating the Laplace transform of the step response of the give circuit to the Laplace transform of the given step response:


$$V_o(s) = \frac{\frac{kR}{L}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} = \frac{5}{(s+2)} - \frac{5}{(s+4)} = \frac{10}{s^2 + 6s + 8}$$

Equating coefficients:

$$\frac{R}{L} = 6, \quad \frac{1}{LC} = 8, \quad \text{and} \quad \frac{kR}{L} = 10$$

Pick $L = 1$ H, then $k = 1.667$ V/V, $R = 6 \Omega$ and $C = 0.125$ F.

DP 14-4

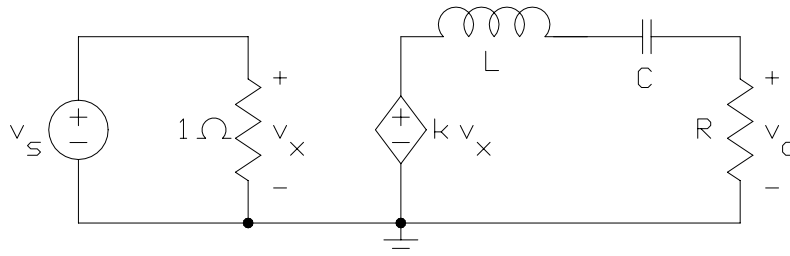

Comparing the Laplace transform of the step response of the give circuit to the Laplace transform of the given step response:

$$V_o(s) = \frac{\frac{kR}{L}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} \neq \frac{5}{(s+2)} + \frac{5}{(s+4)} = \frac{10s+30}{s^2 + 6s + 8}$$


These two functions can not be made equal by any choice of k , R , C and L because the numerators have different forms.

DP14-5

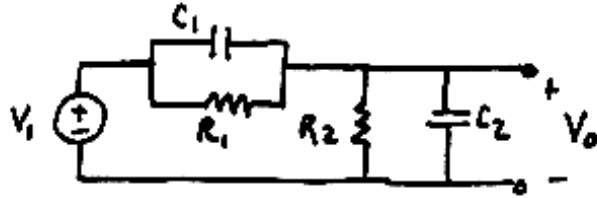a) Use voltage divider

$$\frac{V_o(s)}{V_1(s)} = \frac{\frac{R_2}{sC_2R_2+1}}{\frac{R_1}{sC_1R_1+1} + \frac{R_2}{sC_2R_2+1}}$$

$$= \frac{C_1}{C_1+C_2} \left[\frac{s+1/C_1R_1}{s + \frac{R_1+R_2}{R_1R_2(C_1+C_2)}} \right]$$



b) To make natural response zero, eliminate the pole in $\frac{V_o}{V_1}$ by causing it to cancel with the zero.

$$\Rightarrow -\frac{1}{C_1R_1} = -\frac{R_1+R_2}{R_1R_2(C_1+C_2)} \text{ leads to } \underline{\underline{\frac{C_2}{C_1} = \frac{R_1}{R_2}}}$$

c) If $v_1(t) = u(t)$, $V_1(s) = \frac{1}{s}$

$$V_o(s) = \frac{C_1}{C_1+C_2} \left[\frac{s + \frac{1}{R_1C_1}}{s + \frac{R_1+R_2}{R_1R_2(C_1+C_2)}} \right] = \frac{K_1}{s} + \frac{K_2}{s + \frac{R_1+R_2}{R_1R_2(C_1+C_2)}}$$


$$\text{where } K_1 = \frac{R_2}{R_1+R_2} \text{ and } K_2 = \frac{C_1}{C_1+C_2} - \frac{R_2}{R_1+R_2}$$

$$\text{So } v_o(t) = \frac{R_2}{R_1+R_2} + \left[\frac{C_1}{C_1+C_2} - \frac{R_2}{R_1+R_2} \right] e^{-t/\tau} \quad t > 0$$

$$\text{where } \tau = \frac{R_1R_2(C_1+C_2)}{R_1+R_2}$$

1) If $\frac{C_1}{C_1+C_2} = \frac{R_2}{R_1+R_2} \Rightarrow v_o(t) = \frac{R_2}{R_1+R_2} = \frac{C_1}{C_1+C_2}$

2) and 3) $v_o(t=0^+) = \frac{C_1}{C_1+C_2}$ and $v_o(t \rightarrow \infty) = \frac{R_2}{R_1+R_2}$

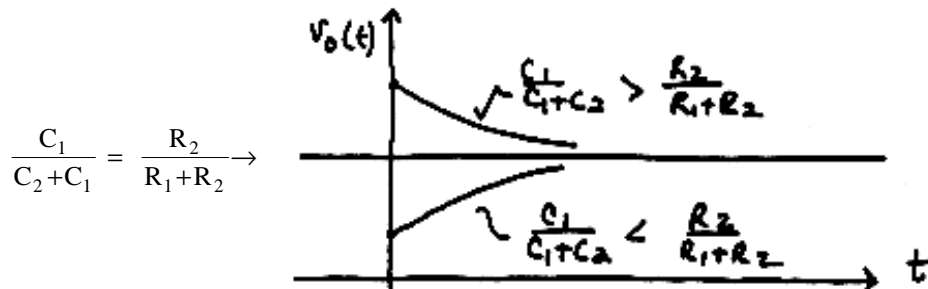

DP14-6


For $t < 0$



$$v_c(0) = -0.4V$$

$$i(0) = 0$$

For $t > 0$

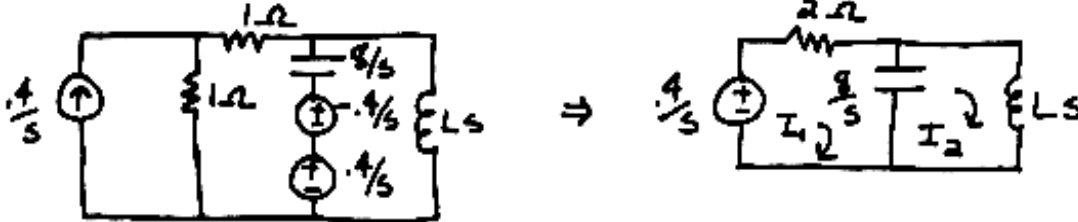

$$\text{mesh equations } \begin{cases} (2 + \frac{8}{s}) I_1 - \frac{8}{s} I_2 = 0.4/s \\ -\frac{8}{s} I_1 + (Ls + \frac{8}{s}) I_2 = 0 \end{cases}$$

$$\text{Solving for } I_2: I_2 = \frac{1.6}{s(Ls^2 + 4Ls + 8)}$$

Thus $s^2 + 4s + \frac{8}{L} = 0$ need char. eqn. with complex roots with significant damping

$$\text{If } L = 1H \Rightarrow s^2 + 4s + 8 = 0$$

$$\text{So } I(s) = \frac{1.6}{s(s^2 + 4s + 8)} = \frac{.2}{s} + \frac{-.2(s+4)}{s^2 + 4s + 8} = \frac{.2}{s} + \frac{-.2(s+2)}{(s+2)^2 + 4} - \frac{.8}{(s+2)^2 + 4}$$

$$\text{So } \underline{i(t) = .2 - .2e^{-2t} \cos 2t - .4e^{-2t} \sin 2t} \quad (A), \quad t \geq 0$$