

Chapter 16: Filter Circuits

Exercises

Ex. 16.3-1

$$T_n(s) = \frac{1}{s+1}$$

$$T(s) = T_n\left(\frac{s}{1250}\right) = \frac{1}{\frac{s}{1250}+1} = \frac{1250}{s+1250}$$

Problems

Section 16.3: Filters

P16.3-1 Equation 16-3.2 and Table 16-3.2 provide a third-order Butterworth low-pass filter having a cutoff frequency equal to 1 rad/s.

$$H_n(s) = \frac{1}{(s+1)(s^2+s+1)}$$

Frequency scaling so that $\omega_c = 2\pi 100 = 628$ rad/s:

$$\begin{aligned} H_L(s) &= \frac{1}{\left(\frac{s}{628}+1\right)\left(\left(\frac{s}{628}\right)^2+\frac{s}{628}+1\right)} \\ &= \frac{628^3}{(s+628)(s^2+628s+628^2)} \\ &= \frac{247673152}{(s+628)(s^2+628s+394384)} \end{aligned}$$

P16.3-2 Equation 16-3.2 and Table 16-3.2 provide a third-order Butterworth low-pass filter having a cutoff frequency equal to 1 rad/s and a dc gain equal to 1.

$$H_n(s) = \frac{1}{(s+1)(s^2+s+1)}$$

Multiplying by 5 to change the dc gain to 5 and frequency scaling to change the cutoff frequency to $\omega_c = 100$ rad/s:

$$\begin{aligned} H_L(s) &= \frac{5}{\left(\frac{s}{100}+1\right)\left(\left(\frac{s}{100}\right)^2+\frac{s}{100}+1\right)} = \frac{5 \cdot 100^3}{(s+100)(s^2+100s+100^2)} \\ &= \frac{5000000}{(s+100)(s^2+100s+10000)} \end{aligned}$$

- P16.3-3** Use Table 16-3.2 to obtain the transfer function of a third-order Butterworth high-pass filter having a cutoff frequency equal to 1 rad/s and a dc gain equal to 5.

$$H_n(s) = \frac{5s^3}{(s+1)(s^2+s+1)}$$

Frequency scaling to change the cutoff frequency to $\omega_c = 100$ rad / s:

$$\begin{aligned} H_H(s) &= \frac{5\left(\frac{s}{100}\right)^3}{\left(\frac{s}{100}+1\right)\left(\left(\frac{s}{100}\right)^2+\frac{s}{100}+1\right)} \\ &= \frac{5s^3}{(s+100)(s^2+100s+100^2)} \\ &= \frac{5s^3}{(s+100)(s^2+100s+10000)} \end{aligned}$$

- P16.3-4** Use Table 16-3.2 to obtain the transfer function of a fourth-order Butterworth high-pass filter having a cutoff frequency equal to 1 rad/s and a dc gain equal to 5.

$$H_n(s) = \frac{5s^4}{(s^2+0.765s+1)(s^2+1.848s+1)}$$

Frequency scaling can be used to adjust the cutoff frequency 500 hertz = 3142 rad/s:

$$\begin{aligned} H_H(s) &= \frac{5\left(\frac{s}{3142}\right)^4}{\left(\left(\frac{s}{3142}\right)^2+0.765\left(\frac{s}{3142}\right)+1\right)\left(\left(\frac{s}{3142}\right)^2+1.848\left(\frac{s}{3142}\right)+1\right)} \\ &= \frac{5s^4}{(s^2+2403.6s+3142^2)(s^2+5806.4s+3142^2)} \end{aligned}$$

- P16.3-5** First, obtain the transfer function of a second-order Butterworth low-pass filter having a dc gain equal to 2 and a cutoff frequency equal to 2000 rad/s:

$$H_L(s) = \frac{2}{\left(\frac{s}{2000}\right)^2+1.414\left(\frac{s}{2000}\right)+1} = \frac{8000000}{s^2+2828s+4000000}$$

Next, obtain the transfer function of a second-order Butterworth high-pass filter having a passband gain equal to 2 and a cutoff frequency equal to 100 rad/s:

$$H_H(s) = \frac{2 \cdot \left(\frac{s}{100}\right)^2}{\left(\frac{s}{100}\right)^2 + 1.414 \left(\frac{s}{100}\right) + 1} = \frac{2 \cdot s^2}{s^2 + 141.4s + 10000}$$

Finally, the transfer function of the bandpass filter is

$$H_B(s) = H_L(s) \cdot H_H(s) = \frac{16000000 \cdot s^2}{(s^2 + 141.4s + 10000)(s^2 + 2828s + 4000000)}$$

P16.3-6

$$H_B(s) = 4 \left(\frac{\frac{250}{1}s}{s^2 + \frac{250}{1}s + 250^2} \right)^2 = \frac{250000s^2}{(s^2 + 250s + 62500)^2}$$

P16.3-7 First, obtain the transfer function of a second-order Butterworth high-pass filter having a dc gain equal to 2 and a cutoff frequency equal to 2000 rad/s:

$$H_L(s) = \frac{2 \cdot \left(\frac{s}{2000}\right)^2}{\left(\frac{s}{2000}\right)^2 + 1.414 \left(\frac{s}{2000}\right) + 1} = \frac{2s^2}{s^2 + 2828s + 4000000}$$

Next, obtain the transfer function of a second-order Butterworth low-pass filter having a pass-band gain equal to 2 and a cutoff frequency equal to 100 rad/s:

$$H_H(s) = \frac{2}{\left(\frac{s}{100}\right)^2 + 1.414 \left(\frac{s}{100}\right) + 1} = \frac{20000}{s^2 + 141.4s + 10000}$$

Finally, the transfer function of the band-stop filter is

$$\begin{aligned} H_N(s) = H_L(s) + H_H(s) &= \frac{2s^2(s^2 + 141.4s + 10000) + 20000(s^2 + 2828s + 4000000)}{(s^2 + 141.4s + 10000)(s^2 + 2828s + 4000000)} \\ &= \frac{2s^4 + 282.8s^3 + 40000s^2 + 56560000s + 8 \cdot 10^{10}}{(s^2 + 141.4s + 10000)(s^2 + 2828s + 4000000)} \end{aligned}$$

P16.3-8

$$H_N(s) = 4 - 4 \left(\frac{\frac{250}{1}s}{s^2 + \frac{250}{1}s + 250^2} \right)^2 = \frac{4(s^2 + 62500)^2}{(s^2 + 250s + 62500)^2}$$

P16.3-9

$$H_L(s) = 4 \left(\frac{250^2}{s^2 + \frac{250}{1}s + 250^2} \right)^2 = \frac{4 \cdot 250^4}{(s^2 + 250s + 62500)^2}$$

P16.3-10

$$H_H(s) = 4 \left(\frac{s^2}{s^2 + \frac{250}{1}s + 250^2} \right)^2 = \frac{4 \cdot s^4}{(s^2 + 250s + 62500)^2}$$

Section 16.4: Second-Order Filters

P16.4-1

$$T(s) = \frac{V_o(s)}{V_s(s)} = \frac{\frac{s}{RC}}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$

So $K = 1$, $\omega_0^2 = \frac{1}{LC}$ and $\frac{1}{RC} = \frac{\omega_0}{Q} \Rightarrow Q = RC\omega_0 = R\sqrt{\frac{C}{L}}$

Pick $C = 1\mu\text{F}$. Then $L = \frac{1}{C\omega_0^2} = 1\text{H}$ and

$$R = Q\sqrt{\frac{L}{C}} = 1000\Omega$$

P 16.4-2

$$T(s) = \frac{I_o(s)}{I_s(s)} = \frac{\frac{1}{LC}}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$

So $K=1$, $\omega_0^2 = \frac{1}{LC}$ and $\frac{1}{RC} = \frac{\omega_0}{Q} \Rightarrow Q = RC\omega_0 = R\sqrt{\frac{C}{L}}$

Pick $C = 1\mu\text{F}$ then $L = \frac{1}{C\omega_0^2} = 25\text{H}$ and

$$R = Q\sqrt{\frac{L}{C}} = 3535\Omega$$

P16.4-3

$$T(s) = \frac{\frac{1}{R_1 R C^2}}{s^2 + \frac{1}{RC} \left(2 + \frac{R}{R_1} \right) s + \frac{1}{R^2 C^2}}$$

Pick $C = 0.01 \mu\text{F}$

$$\frac{1}{RC} = \omega_0 = 2000 \Rightarrow R = 50000 = 50\text{k}\Omega$$

$$\frac{\omega_0}{Q} = \frac{1}{RC} \left(2 + \frac{R}{R_1} \right) \Rightarrow R_1 = \frac{R}{Q-2} = 8333 = 8.33\text{k}\Omega$$

P16.4-4

Pick $C = 0.02 \mu\text{F}$. Then $R_1 = 40\text{k}\Omega$, $R_2 = 400\text{k}\Omega$ and $R_3 = 3.252\text{k}\Omega$.

P16.4-5


Pick $C_1 = C_2 = C = 1 \mu\text{F}$

$$\frac{10^6}{\sqrt{R_1 R_2}} = \omega_0$$

$$\frac{1}{R_1 C} = \frac{\omega_0}{Q} \Rightarrow Q = \sqrt{\frac{R_1}{R_2}} \Rightarrow R_2 = \frac{R_1}{Q^2}$$

In this case $R_2 = R_1$ and $R_1 = \frac{10^6}{1000} = 1000 = 1\text{k}\Omega$

P 16.4-6

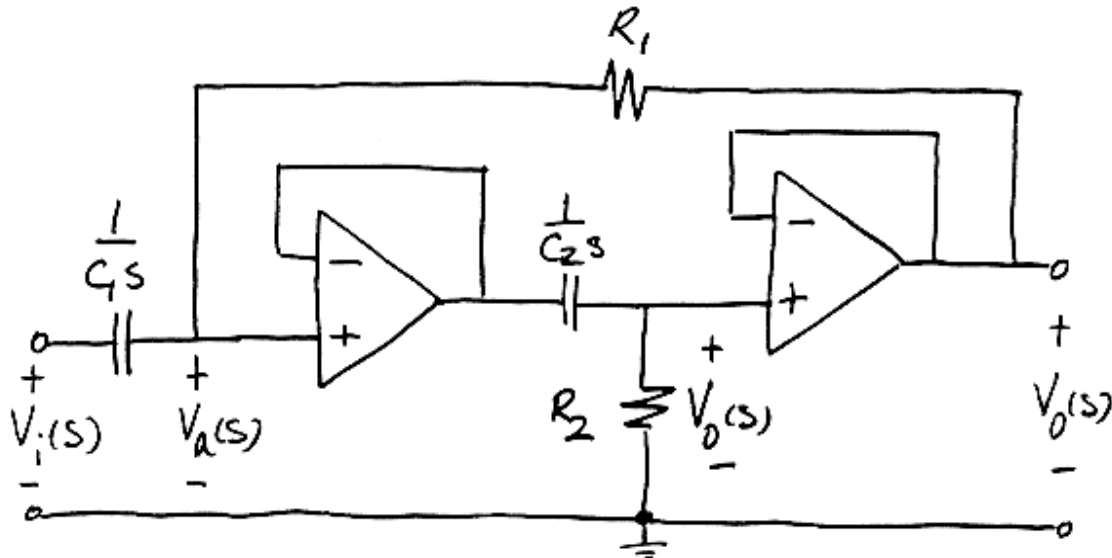

$$V_0(s) = \frac{R_2}{R_2 + \frac{1}{C_2 s}} V_a(s)$$

$$\frac{V_0(s) - V_a(s)}{R_1} - C_1 s (V_a(s) - V_i(s)) = 0$$


$$T(s) = \frac{V_0(s)}{V_i(s)} = \frac{s^2}{s^2 + \frac{s}{R_2 C_2} + \frac{1}{R_1 R_2 C_1 C_2}}$$

Pick $C_1 = C_2 = C = 1\mu\text{F}$. Then $\frac{1}{C\sqrt{R_1 R_2}} = \omega_0$

Also $\frac{1}{R_2 C} = \frac{\omega_0}{Q} \Rightarrow Q = \sqrt{\frac{R_2}{R_1}} \Rightarrow R_1 Q^2 = R_2$

In this case $R_1 = R_2 = R$ and $\frac{1}{CR} = \omega_0 \Rightarrow R = 1000\Omega$

P16.4-7

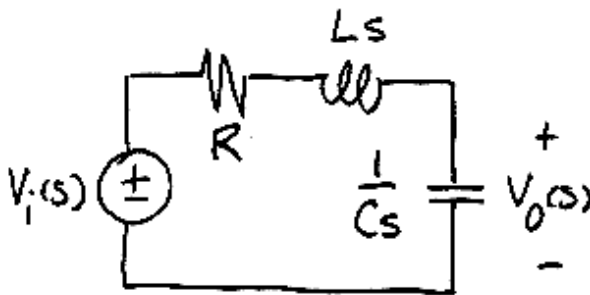

$$T(s) = \frac{V_0(s)}{V_i(s)} = \frac{\frac{1}{Cs}}{Ls + R + \frac{1}{Cs}} = \frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

When $R = 25$, $L = 10^{-2}$ and $C = 4 \times 10^{-6}$, then


$$T(s) = \frac{25 \times 10^6}{s^2 + 2500s + 25 \times 10^6}$$

So


$$\omega_{old} = \sqrt{25 \times 10^6} = 5000$$

$$K_f = \frac{\omega_{new}}{\omega_{old}} = \frac{250}{5000} = 0.05$$

The scaled circuit is

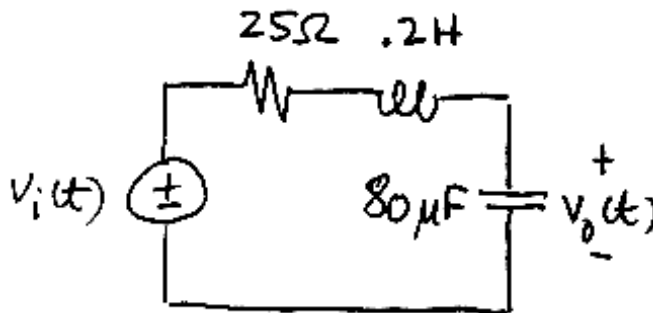

P16.4-8

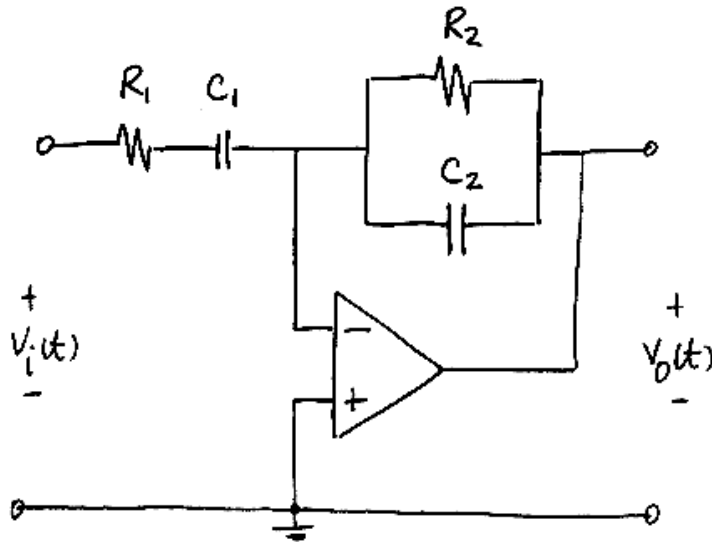

$$T(s) = \frac{V_o(s)}{V_i(s)} = -\frac{\frac{R_2}{1+R_2C_2s}}{R_1 + \frac{1}{C_1s}} = -\frac{\frac{1}{R_1C_2}s}{s^2 + \left(\frac{1}{R_1C_1} + \frac{1}{R_2C_2}\right)s + \frac{1}{R_1R_2C_1C_2}}$$

Pick $K_m = 1000$ so that the scaled capacitances will be $\frac{100\mu\text{F}}{1000} = 0.1\mu\text{F}$ and $\frac{500\mu\text{F}}{1000} = 0.5\mu\text{F}$

Before scaling ($R_1=20, C_1=100\mu\text{F}, R_2=10$ and $C_2=500\mu\text{F}$)

$$T(s) = \frac{-100s}{s^2 + 700s + 10^5}$$

After scaling ($R_1=20000, C_1=0.1\mu\text{F}, R_2=10000, C_2=0.5\mu\text{F}$)

$$T(s) = \frac{-100s}{s^2 + 700s + 10^5}$$

P16.4-9 This is the frequency response of a bandpass filter, so $T(s) = \frac{K \frac{\omega_0}{Q} s}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$

From peak of the frequency response

$$\omega_0 = 2\pi \times 10 \times 10^6 = 62.8 \times 10^6$$

$$k = 10\text{dB} = 3.16$$

next

$$\frac{\omega_0}{Q} = \text{BW} = (10.1 \times 10^6 - 9.9 \times 10^6) 2\pi = (0.2 \times 10^6) 2\pi = 1.26 \times 10^6$$

so

$$T(s) = \frac{3.16(1.26)10^6 s}{s^2 + (1.26)10^6 s + 62.8^2 \cdot 10^{12}} = \frac{(3.98)10^6 s}{s^2 + (1.26)10^6 s + 3.944 \cdot 10^{15}}$$

P16.4-10

(a) Assume ideal op amp (inverting), then $H = \frac{V_0}{V_s} = -\frac{Z_2}{Z_1}$

where $Z_1 = R_1 - j/\omega C_1$ and $Z_2 = \frac{R_2 \cdot 1/j\omega C_2}{R_2 + 1/j\omega C_2}$


$\therefore H = -\frac{j\omega R_2 C_1}{(1+j\omega/\omega_2)(1+j\omega/\omega_1)}$ where $\omega_1 = 1/R_1 C_1$, $\omega_2 = 1/R_2 C_2$

(b) $\omega_1 = 1/R_1 C_1$ and $\omega_2 = 1/R_2 C_2$

(c) at $\omega_1 \ll \omega \ll \omega_2$

$|H| \approx \frac{\omega R_2 C_1}{\omega/\omega_1} = \omega_1 R_2 C_1 = R_2/R_1$

P16.4-11

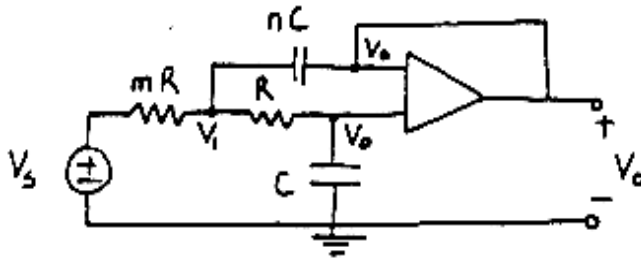

Assume $V_1 \approx 0$, then $V+ = V- = V_0$
Use $s = j\omega$

Voltage divider yields: $V_0 = V_1 \frac{1/sC}{R + 1/sC}$, $\Rightarrow V_1 = (1 + sRC)V_0$


KCL at V_1 : $(V_1 - V_s)/mR + (V_1 - V_0)/R + (V_1 - V_0)snC = 0$

Plugging V_1 into above yields


$V_0 \left[\frac{1}{mR} + sC + \frac{sC}{m} + s^2 nRC^2 \right] = \frac{V_s}{mR}$

$\therefore \frac{V_0}{V_s} = \frac{1}{1 + s(m+1)RC + nmR^2C^2s^2}$

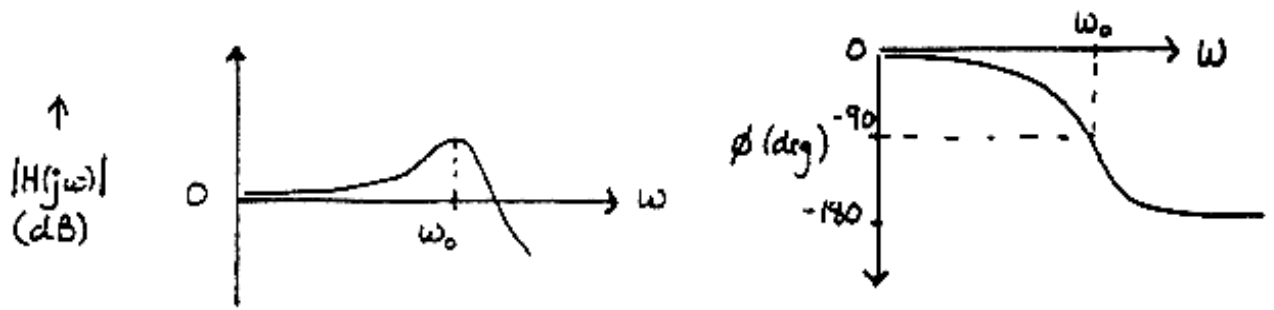$\Rightarrow H(j\omega) = \frac{V_0}{V_s} = \frac{1}{1 - (\omega/\omega_0)^2 + j(\omega/Q\omega_0)}$ where $\omega_0 = \frac{1}{\sqrt{mn}RC}$ and $Q = \frac{\sqrt{mn}}{m+1}$



P16.4-12

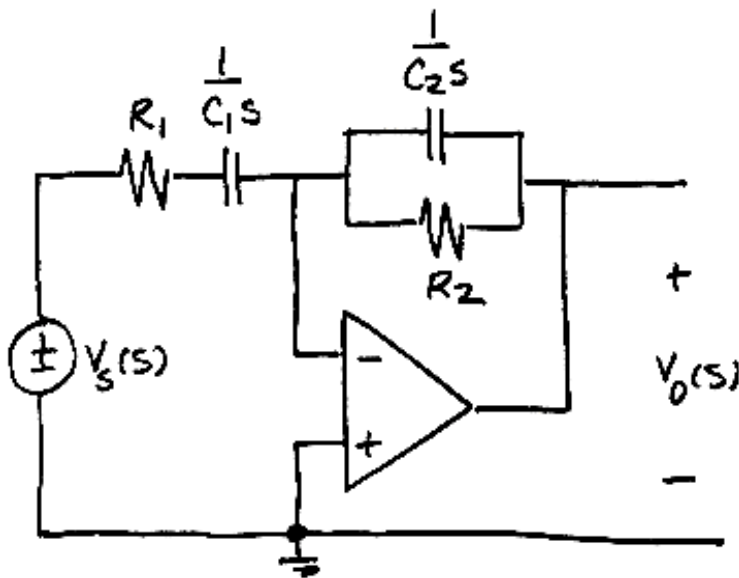


$$H(s) = \frac{V_0(s)}{V_s(s)} = -\frac{R_2 \parallel \frac{1}{C_2 s}}{R_1 + \frac{1}{C_1 s}} = \frac{R_2}{\frac{R_2 C_2 s + 1}{C_1 s}} = \frac{-\frac{1}{R_1 C_2} s}{s^2 + \left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_2} \right) s + \frac{1}{R_1 R_2 C_1 C_2}}$$

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} = 70.7 \text{ k rad/sec} = 2\pi(11.25 \text{ kHz})$$

$$BW = \frac{\omega_0}{Q} = \frac{1}{R_1 C_1} + \frac{1}{R_2 C_2} = 150 \text{ k rad/s} = 2\pi(23.9 \text{ kHz})$$

P16.4-13

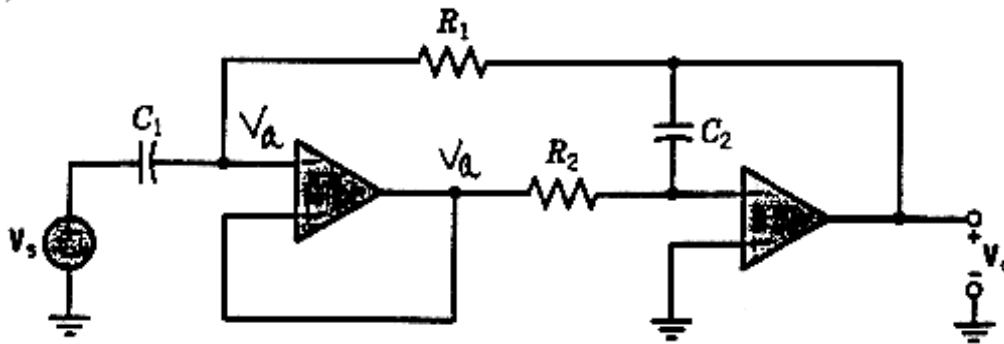


$$\left. \begin{aligned} C_1 s(V_a - V_s) + \frac{V_a - V_0}{R_1} &= 0 \\ -\frac{V_a}{R_2} - C_2 s V_0 &= 0 \end{aligned} \right\} \Rightarrow H(s) = \frac{V_0(s)}{V_s(s)} = \frac{-\frac{1}{R_2 C_2} s}{s^2 + \frac{1}{R_1 C_1} s + \frac{1}{R_1 R_2 C_1 C_2}}$$

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} = 10^4 \text{ rad/sec}$$

$$BW = \frac{1}{R_1 C_1} = 10^3 \text{ rad/sec}$$

$$Q = \frac{\omega_0}{BW} = 10$$

P16.4-14

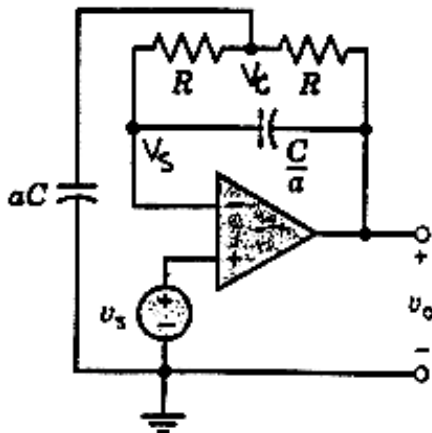

$$aCs V_c(s) + \frac{V_c(s) - V_s(s)}{R} + \frac{V_c(s) - V_0(s)}{R} = 0$$

$$\frac{C}{a} s (V_s(s) - V_0(s)) + \frac{V_s(s) - V_c(s)}{R} = 0$$

$$H(s) = \frac{V_0(s)}{V_s(s)} = \frac{s^2 + \left(\frac{2}{a} + a\right) \frac{1}{RC} s + \frac{1}{(RC)^2}}{s^2 + \left(\frac{2}{a}\right) \frac{1}{RC} s + \frac{1}{(RC)^2}}$$

We require

$$10^5 = \frac{1}{RC}$$


Pick $C = 0.01 \mu\text{F}$ then $R = 1000 \Omega$

$$\text{Next } |H(\omega_0)| = \frac{\frac{2}{a} + a}{\frac{2}{a}} = 1 + \frac{a^2}{2}$$

We require

$$201 = 1 + \frac{a^2}{2} \Rightarrow a = 20$$

P16.4-15

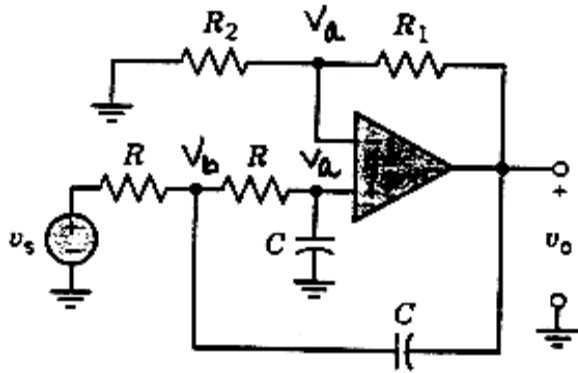

$$\frac{V_a}{R_2} + \frac{V_a - V_0}{R_1} = 0$$

$$C_s V_a + \frac{V_a - V_b}{R} = 0$$


$$C_s (V_b - V_0) + \frac{V_b - V_s}{R} = 0$$

$$\frac{V_0(s)}{V_s(s)} = \frac{\left(1 + \frac{R_1}{R_2}\right) \frac{1}{R^2 C^2}}{s^2 + \left(2 - \frac{R_1}{R_2}\right) \frac{1}{RC} s + \frac{1}{R^2 C^2}}$$


$$\omega_0 = \frac{1}{RC} = \frac{1}{(1.2 \times 10^3)(20 \times 10^{-9})} = 41.67 \text{ k rad/sec}$$

Section 16.5: High-Order Filters

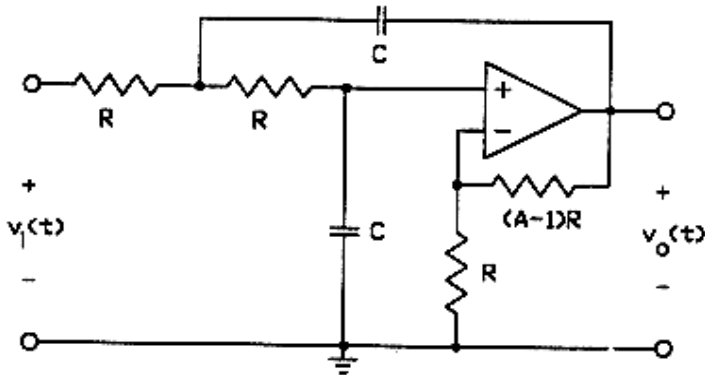P16.5-1 This filter is designed as a cascade connection of a Sallen-key low-pass filter designed as described in Table 16.4-2 and a first-order low-pass filter designed as described in Table 16.5-2.



Sallen-Key Low-Pass Filter

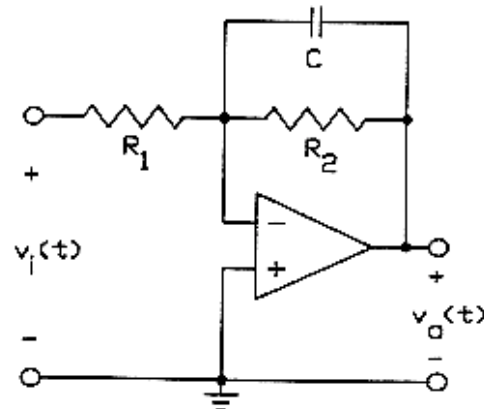

First-Order Low-Pass Filter

MathCad Spreadsheets

The transfer function is of the form $T(s) = \frac{c}{s^2 + bs + a}$

Enter the transfer function coefficients: $a := 628^2$ $b := 628$

Determine the filter specifications: $\omega_0 := \sqrt{a}$ $Q := \frac{\omega_0}{b}$ $\omega_0 = 628$ $Q = 1$

Pick a convenient value for the capacitance: $C := 0.1 \cdot 10^{-6}$

Calculate resistance values: $R := \frac{1}{C \cdot \omega_0}$ $A := 3 - \frac{1}{Q}$ $R = 1592 \cdot 10^4$ $R \cdot (A - 1) = 1592 \cdot 10^4$

Calculate the dc gain: $A=2$.

The dc gain of the Sallen-key filter is 2. Therefore, the dc gain of the first-order filter must be $\frac{1}{2}$ so that the dc gain of the whole filter is 1.

MathCad Spreadsheet

The transfer function is of the form $T(s) = \frac{-k}{s+p}$


Enter the transfer function coefficients: $p := 628$ $k := 0.5 \cdot p$

Pick a convenient value for the capacitance: $C := 0.1 \cdot 10^{-6}$


Calculate resistance values: $R2 := \frac{1}{C \cdot p}$ $R1 := \frac{1}{C \cdot k}$ $R1 = 3.185 \cdot 10^4$ $R2 = 1.592 \cdot 10^4$

P16.5-2 This filter is designed as a cascade connection of a Sallen-key high-pass filter, designed as described in Table 16.4-2, and a first-order high-pass filter, designed as described in Table 16.5-2.

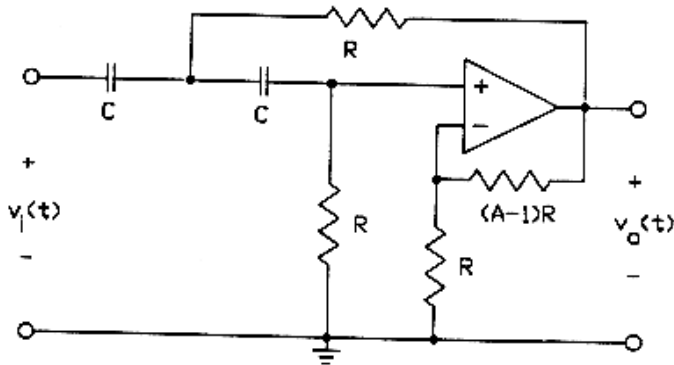The passband gain of the Sallen key stage is 2 and the passband gain of the first-order stage is 2.5 So the overall passband gain is $2 \times 2.5 = 5$



Sallen-Key High-Pass Filter

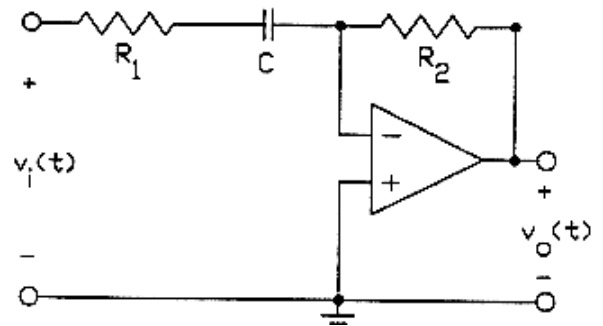

First-Order High-Pass Filter

MathCad Spreadsheet:

The transfer function is of the form $T(s) = \frac{cs^2}{s^2+bs+a}$

Enter the transfer function coefficients: $a = 10000$ $b = 100$

Determine the filter specifications: $\omega_0 := \sqrt{a}$ $Q := \frac{\omega_0}{b}$ $\omega_0 = 100$ $Q = 1$

Pick a convenient value for the capacitance: $C := 0.1 \cdot 10^{-6}$

Calculate resistance values: $R := \frac{1}{C \cdot \omega_0}$ $A := 3 - \frac{1}{Q}$ $R = 1.10^5$ $R \cdot (A-1) = 1 \cdot 10^5$

Calculate the passband gain: $A = 2$


The transfer function is of the form $T(s) = \frac{-ks}{s + p}$

Enter the transfer function coefficients: $p:=100$ $k:= 2.5$


Pick a convenient value for the capacitance: $C:= 0.1 \cdot 10^{-6}$

Calculate resistance values: $R1:= \frac{1}{C \cdot p}$ $R2:=k \cdot R1$ $R1 = 1 \cdot 10^5$ $R2 = 2.5 \cdot 10^5$

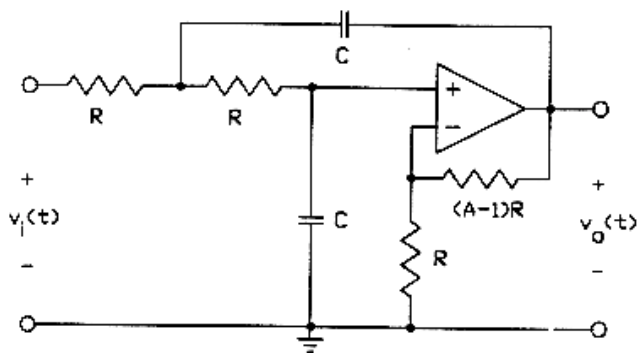P16.5-3 This filter is designed as a cascade connection of a Sallen-key low-pass filter, a Sallen-key high-pass filter and an inverting amplifier.



Sallen-key Low-Pass Filter

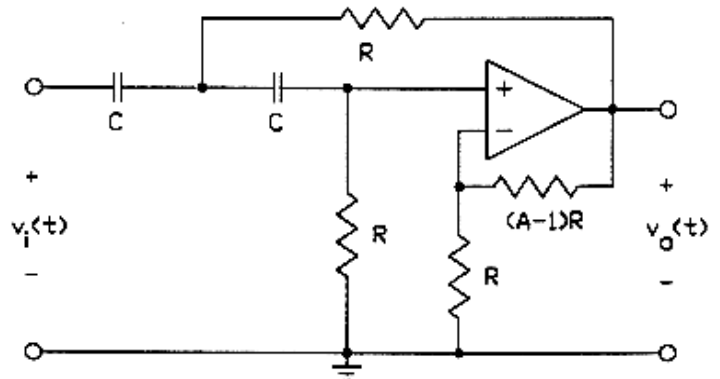

Sallen-Key High-Pass Filter

MathCad Spreadsheet:

The transfer function is of the form $T(s) = \frac{c}{s^2 + bs + a}$.

Enter the transfer function coefficients: $a = 4000000$ $b = 2828$

Determine the filter specifications: $\omega_0 = \sqrt{a}$ $Q = \frac{\omega_0}{b}$ $\omega_0 = 2 \cdot 10^3$ $Q = 0.707$

Pick a convenient value for the capacitance: $C = 0.1 \cdot 10^{-6}$

Calculate resistance values : $R := \frac{1}{C \cdot \omega_0}$ $A := 3 - \frac{1}{Q}$ $R = 5 \cdot 10^3$ $R \cdot (A-1) = 2.93 \cdot 10^3$

Calculate the dc gain: $A = 1.586$

The transfer function is of the form $T(s) = \frac{cs^2}{s^2 + bs + a}$.

Enter the transfer function coefficients: $a = 10000$ $b = 141.4$

Determine the filter specifications: $\omega_0 = \sqrt{a}$ $Q = \frac{\omega_0}{b}$ $\omega_0 = 100$ $Q = 0.707$

Pick a convenient value for the capacitance: $C = 0.1 \cdot 10^{-6}$

Calculate resistance values: $R = \frac{1}{C \cdot \omega_0}$ $A = 3 - \frac{1}{Q}$ $R = 1 \cdot 10^5$ $R \cdot (A - 1) = 5.86 \cdot 10^4$

Calculate the pass band gain: $A = 1.586$

The passband gain of these two stages is

$$1.586 \times 1.586 = 2.515$$


The required passband gain is

$$\frac{1.6 \times 10^6}{141.4 \times 2828} = 4.00$$

An amplifier with a gain equal to $\frac{4.0}{2.515} = 1.59$ is needed to achieve the specified gain.

P16.5-4

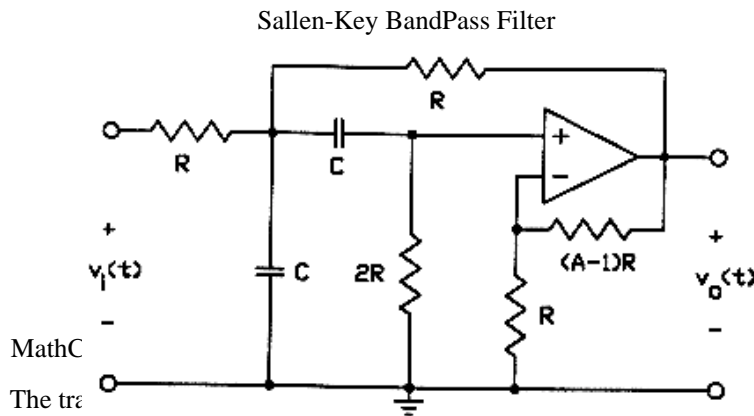This filter is designed as the cascade connection of two identical Sallen-key bandpass filters



Enter the transfer function coefficients: $a = 62500$ $b = 250$

Determine the filter specifications: $\omega_0 = \sqrt{a}$ $Q = \frac{\omega_0}{b}$ $\omega_0 = 250$ $Q = 1$

Pick a convenient value for the capacitance: $C = 0.1 \cdot 10^{-6}$


Calculate resistance values: $R = \frac{1}{C \cdot \omega_0}$ $A = 3 - \frac{1}{Q}$

$$R = 4 \cdot 10^4 \quad 2 \cdot R = 8 \cdot 10^4 \quad R \cdot (A - 1) = 4 \cdot 10^4$$


Calculate the passband gain: $A \cdot Q = 2$

This filter is designed using this structure:

P16.5-5

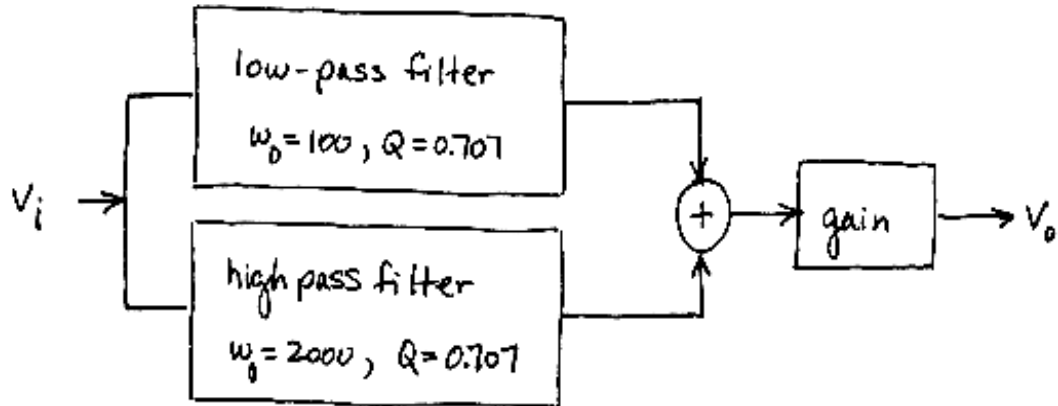

Here's the low-pass filter design:

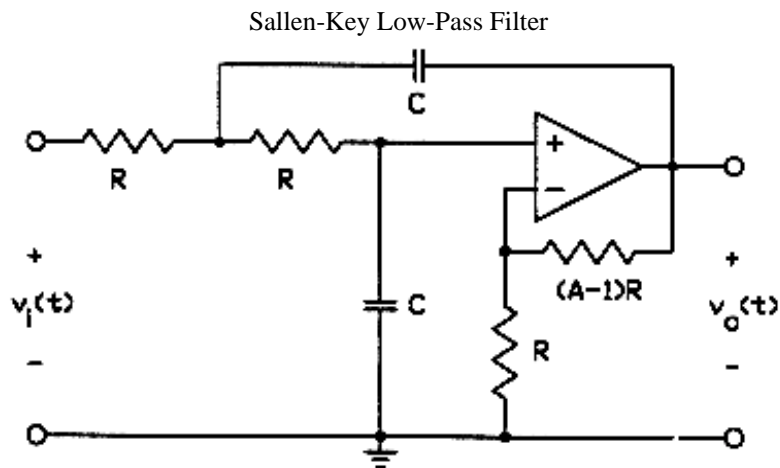

MathCad Spreadsheet

The transfer function is of the form $T(s) = \frac{c}{s^2 + bs + a}$

Enter the transfer function coefficients: $a = 10000$ $b = 141.4$


Determine the filter specifications: $\omega_0 = \sqrt{a}$ $Q = \frac{\omega_0}{b}$ $\omega_0 = 100$ $Q = 0.707$

Pick a convenient value for the capacitance: $C = 0.1 \cdot 10^{-6}$

Calculate resistance values: $R := \frac{1}{C \cdot \omega_0}$ $A := 3 - \frac{1}{Q}$ $R = 1 \cdot 10^5$ $R \cdot (A - 1) = 5.86 \cdot 10^4$

Calculate the dc gain: $A = 1.586$

Here's the high-pass filter design:

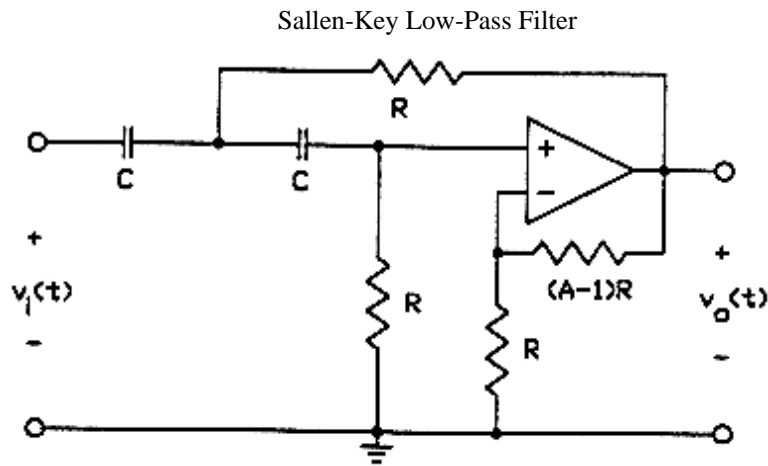

MathCad Spreadsheet

The transfer function is of the form $T(s) = \frac{cs^2}{s^2 + bs + a}$

Enter the transfer function coefficients: $a = 4000000$ $b = 2828$

Determine the filter specifications: $\omega_0 = \sqrt{a}$ $Q = \frac{\omega_0}{b}$ $\omega_0 = 2 \cdot 10^3$ $Q = 0.707$

Pick a convenient value for the capacitance: $C = 0.1 \cdot 10^{-6}$

Calculate resistance values: $R = \frac{1}{C \cdot \omega_0}$ $A = 3 - \frac{1}{Q}$ $R = 5 \cdot 10^3$ $R \cdot (A - 1) = 2.93 \cdot 10^3$


Calculate the dc gain: $A = 1.586$

The required passband gain is 2, but both Sallen - key filters have pass band gains equal to 1.586. The

amplifier has a gain of $\frac{2}{1.586} = 1.26$, to make the passband gain of the entire filter 2.

P16.5-6

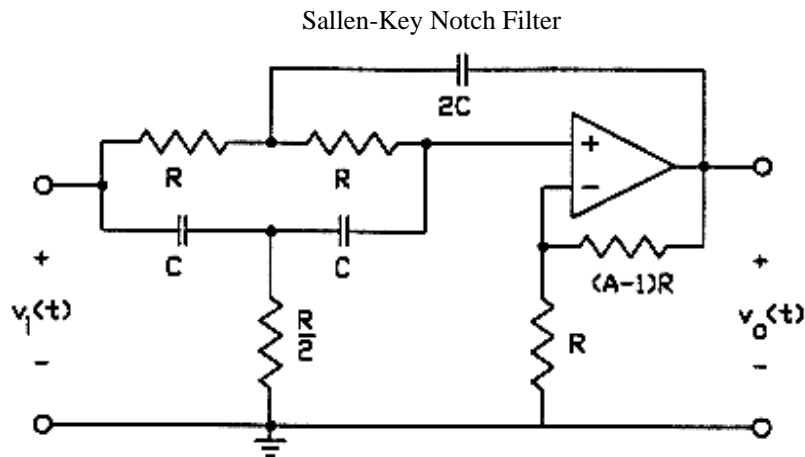This filter is designed as the cascade connection of two identical Sallen-key notch filters.



The transfer function is of the form $T(s) = \frac{c(s^2+a)}{s^2+bs+a}$.

Enter the transfer function coefficients: $a = 62500$ $b = 250$

Determine the filter specifications: $\omega_0 = \sqrt{a}$ $Q = \frac{\omega_0}{b}$ $\omega_0 = 250$ $Q = 1$

Pick a convenient value for the capacitance: $C = 0.1 \cdot 10^{-6}$ $2 \cdot C = 2 \cdot 10^{-7}$

Calculate resistance values: $R = \frac{1}{C \cdot \omega_0}$ $A = 2 - \frac{1}{2 \cdot Q}$

$R = 4 \cdot 10^4$ $\frac{R}{2} = 2 \cdot 10^4$ $R \cdot (A-1) = 2 \cdot 10^4$

Calculate the passband gain: $A = 1.5$

The required passband gain is 4. An amplifier having a gain equal to $\frac{4}{(1.5)(1.5)} = 1.78$ is needed to achieve the required gain.

P16.5-7

(a) $H_1 = V_1 / V_s = \frac{R_1}{R_1 + 1/sC} = \frac{R_1 sC}{1 + R_1 sC}$


$$\Rightarrow |H_1(j\omega)| = \frac{\omega R_1 C}{\sqrt{1 + (\omega R_1 C)^2}} = \frac{\omega / \omega_1}{\sqrt{1 + (\omega / \omega_1)^2}}, \quad \omega_1 = 1 / R_1 C$$

(b) $H_2 = V_2 / V_1 = \frac{sL}{R_2 + sL} \Rightarrow |H_2(j\omega)| = \frac{\omega / \omega_2}{\sqrt{1 + (\omega / \omega_2)^2}} \quad \omega_2 = R_2 / L$

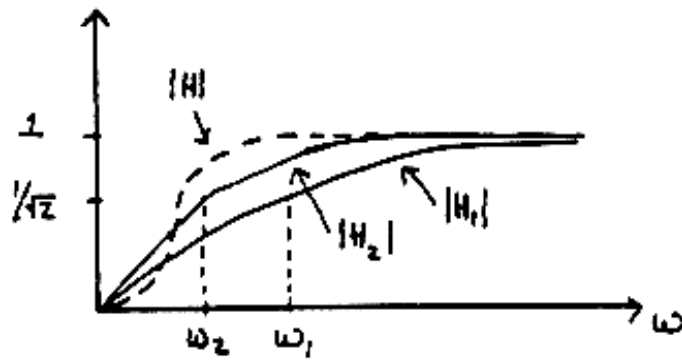(c) $H(j\omega) = H_1(j\omega) H_2(j\omega) = \frac{(sR_1C)}{(1+sR_1C)} \frac{(sL/R_2)}{(1+sL/R_2)} = \frac{s^2 R_1 LC / R_2}{1 + s(R_1 C + L/R_2) + s^2 (R_1 LC / R_2)}$


$$H(j\omega) = \frac{\left(\frac{s}{\omega_0}\right)^2}{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$

where $\omega_0^2 = \frac{R_2}{R_1} LC$, $\omega_0 Q = \frac{1}{R_1 C + L/R_2}$



(d) The circuit of Figure P13-32d is not the same as $H=H_1H_2$ since the first filter (looking from V_s) consists of C and $R_1 \parallel (R_2+sL)$. Thus effectively H_1 is altered, and we won't get the response as sketched in part (c). So we need to place a buffer to the right of R_1 to isolate each first-order filter, then $H=H_1H_2$ will be obtained.

P16.5-8

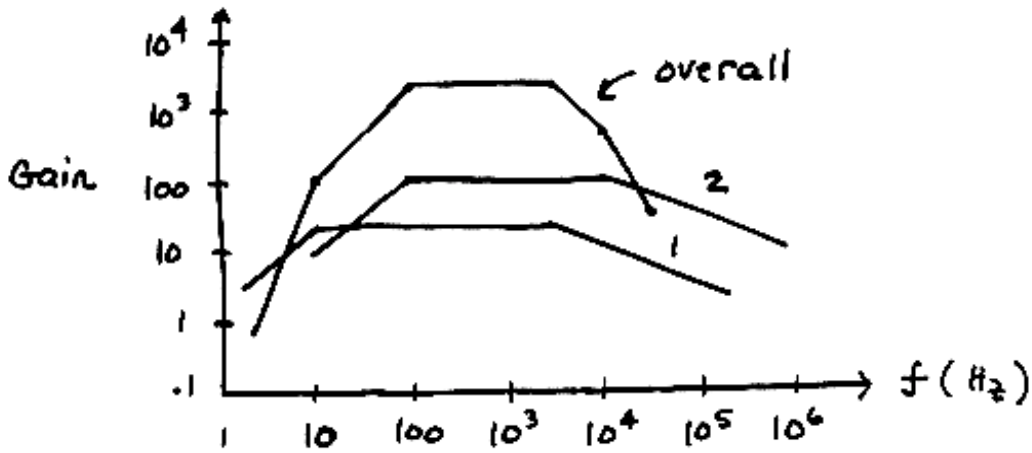

total midband gain = 2000

$f(H_z)$	$ G_1 $	$ O_2 $	$\left \frac{V_0}{V_s} \right $
1	2	1	2
10	20	10	200
100	20	100	2000
2000	20	100	2000
10,000	4	100	400
100,000	0.4	10	4

P16.5-9

$$H_{1,2} = -\frac{R_2/R_1}{1+j\omega R_2 C} \Rightarrow H_{\text{Total}} = H_{1,2}^2 = \left(\frac{R_2/R_1}{1+j\omega R_2 C} \right)^2$$

(a) At low frequency,

$$H_T = \left(\frac{R_2}{R_1}\right)^2 \quad \therefore \text{for } H_T = 1, \text{ need } R_1 = R_2$$

$$\text{Now also } \omega_1 = 1000 = \frac{1}{R_2 C}, \text{ so let } C = 1\mu\text{F}$$

$$\therefore R_1 = R_2 = \frac{1}{(1000)} (10^{-6}) = 1\text{k}\Omega$$


(b) At $\omega = 10,000$

$$|H| = \frac{1}{1 + (\omega R_2 C)^2} = \frac{1}{1 + [(10^4)(10^3)(10^{-6})]^2} = 10^{-2}$$

$$\Rightarrow 20 \log |H| = 20 \log 10^{-2} = \underline{-40\text{dB}}$$

PSpice Problems

SP 16-7

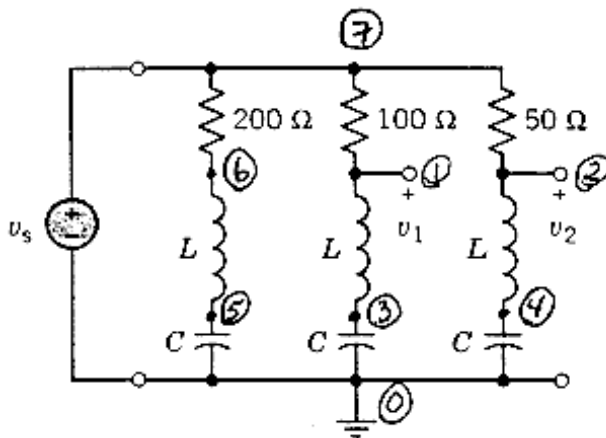

```


Vs      7      0      ac      1
R1      7      6      200
R2      7      1      100
R3      7      2      50
L1      6      5      10m
L2      1      3      10m
L3      2      4      10m
C1      5      0      1u
C2      3      0      1u
C3      4      0      1u

```


```

.ac dec 100 100 10k
.probe
.end

```

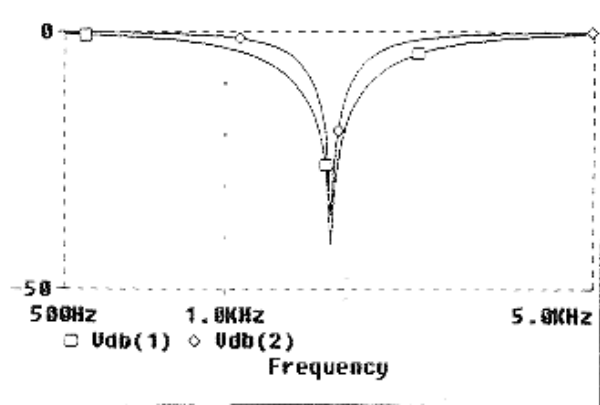

SP 16-8

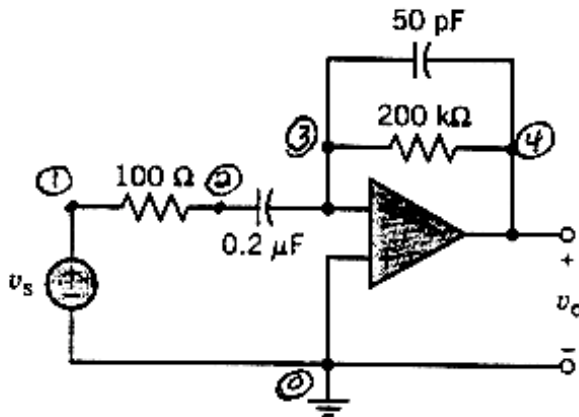


```
Vs 1 0 ac 1
R1 1 2 100
C1 2 3 0.2u
R2 3 4 200k
C2 3 4 50p
```


```
Xoa5 3 0 4 FGOA
```

```
.subckt FGOA 1 2 4
*nodes listed in order - + o
Ri 1 2 500k
E 3 0 1 2 100k
Ro 4 3 1k
.ends FGOA
```

```
.ac dec 100 1k 100k
.probe
.end
```

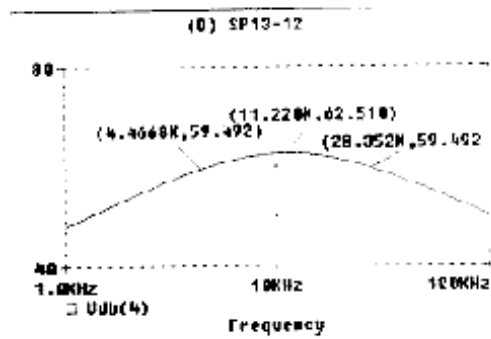


SP 16-9

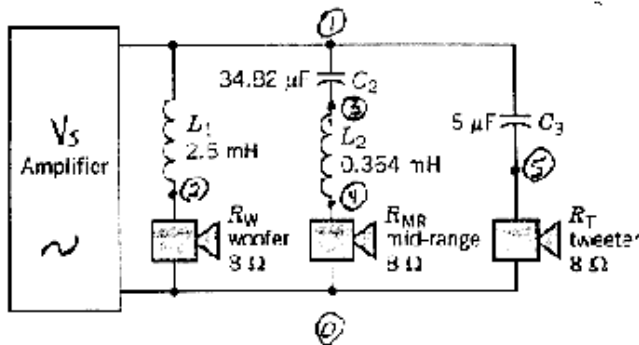

```
Vs 1 0 ac 1
L1 1 2 2.5m
Rw 2 0 8
C2 1 3 34.82u
L2 3 4 0.364m
Rmr 4 0 8
C3 1 5 5u
Rt 5 0 8
```

```
.ac dec 100 10 100k
.probe
.end
```

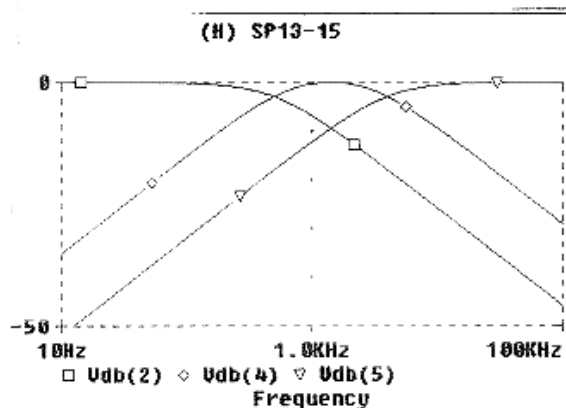

Bw=4.07k - 493 Hz \approx 3600Hz

Verification Problems

VP 16.1

$$\omega_0 = \sqrt{10000} = 100 \text{ rad/s}$$
$$\frac{\omega_0}{Q} = 25 \Rightarrow Q = \frac{100}{25} = 4 \neq 5$$

This filter does not satisfy the specifications.

VP 16.2

$$\omega_0 = \sqrt{10000} = 100 \text{ rad/s}$$
$$\frac{\omega_0}{Q} = 25 \Rightarrow Q = \frac{100}{25} = 4$$
$$K = \frac{75}{25} = 3$$

This filter does satisfy the specifications.

VP16.3

$$\omega_0 = \sqrt{400} = 20 \text{ rad/s}$$
$$\frac{\omega_0}{Q} = 25 \Rightarrow Q = \frac{20}{25} = 0.8$$
$$K = \frac{600}{400} = 1.5$$

This filter does satisfy the specifications.

VP16.4

$$\omega_0 = \sqrt{625} = 25 \text{ rad/s}$$
$$\frac{\omega_0}{Q} = 62.5 \Rightarrow Q = \frac{25}{62.5} = 0.4$$
$$K = \frac{750}{625} = 1.2$$

This filter does satisfy the specifications.

VP 16.5

$$\omega_0 = \sqrt{144} = 12 \text{ rad/s}$$
$$\frac{\omega_0}{Q} = 30 \Rightarrow Q = \frac{12}{30} = 0.4$$

This filter does not satisfy the specifications.

Design Problems

DP 16.1

$$\frac{V_0(s)}{V_1(s)} = \frac{-\frac{s}{RC}}{s + \frac{2}{R_3 C} s + \frac{2}{RR_3 C^2}}$$

$$2\pi(100 \cdot 10^3) = \omega_0 = \sqrt{\frac{2}{RR_3 C^2}}$$


$$2\pi(10 \cdot 10^3) = BW = \frac{\omega_0}{Q} = \frac{2}{R_3 C}$$

$C = 100 \text{ pF}$ is specified so

$$R_3 = \frac{2}{(100 \times 10^{-12})(2\pi \times 10 \times 10^3)} = 318 \text{ k}\Omega$$

$$R = \frac{2}{R_3 C^2 \omega_0^2} = 1.6 \text{ k}\Omega$$


DP16.2

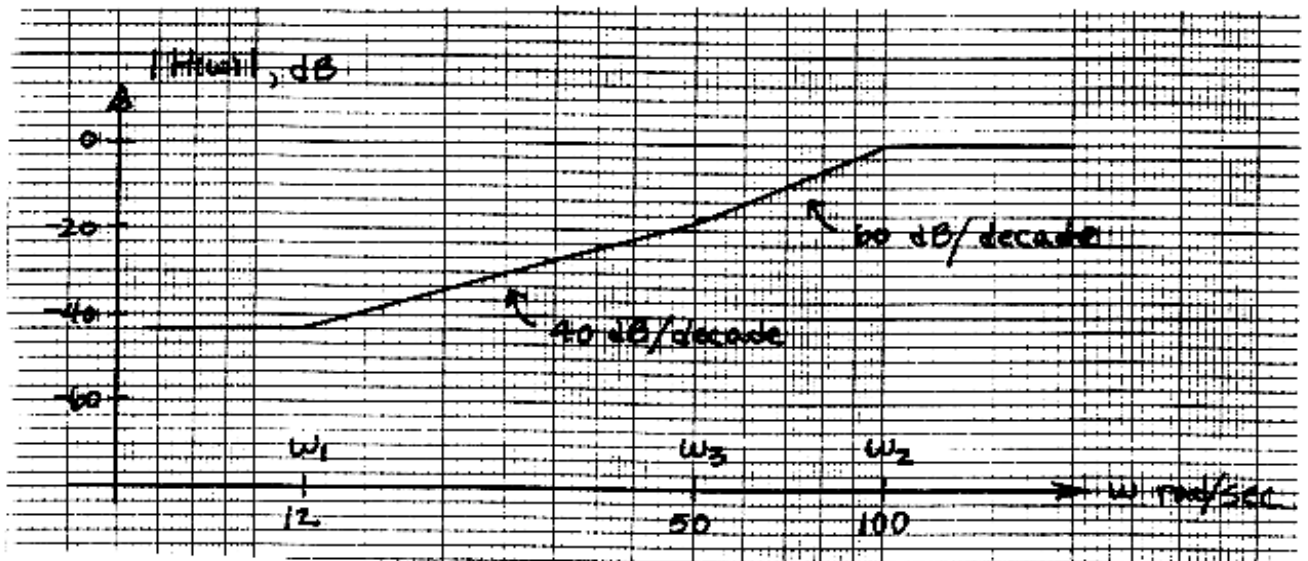

DP 16.3

Choose $\omega_1 = 0.1$, $\omega_2 = 2$, $\omega_3 = 5$, $\omega_4 = 100$ rad/s

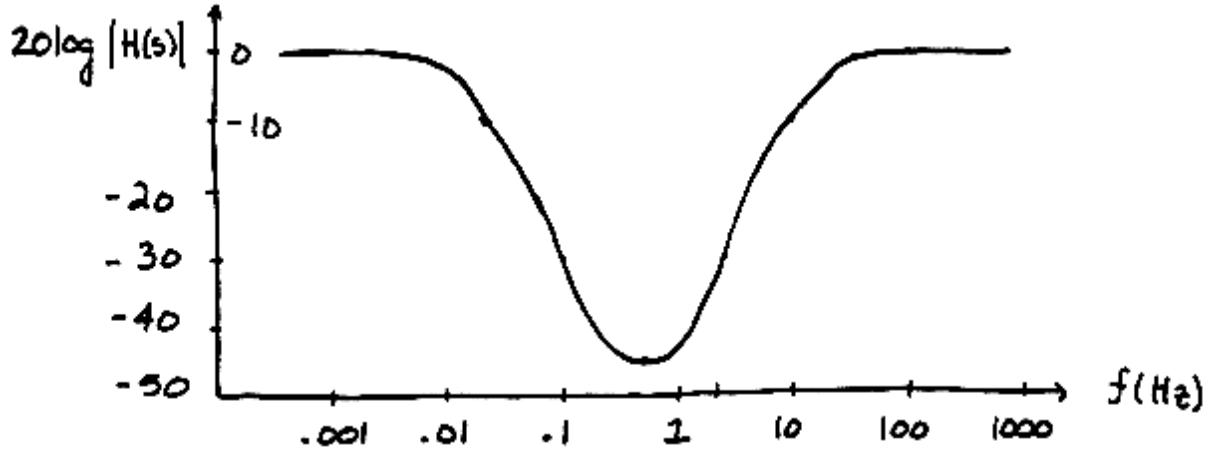The corresponding Bode magnitude plot is:



$$H(s) = \frac{\left(1 + \frac{s}{\omega_1}\right)^2 \left(1 + \frac{s}{\omega_3}\right)^2}{\left(1 + \frac{s}{\omega_2}\right)^2 \left(1 + \frac{s}{\omega_4}\right)^2}$$

Minimum is -46.2 db at $f_{\min} = 0.505$ Hz