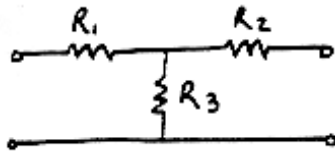


Chapter 17- Two-Port and Three Port Networks

Exercises

Ex. 17.4-1




$$R_1 = \frac{R_a R_c}{R_a + R_b + R_c} = \frac{25(100)}{250} = 10\Omega$$

$$R_2 = \frac{R_b R_c}{R_a + R_b + R_c} = \frac{(125)(125)}{250} = 12.5\Omega$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c} = \frac{100(125)}{250} = 50\Omega$$

Ex. 17.5-1

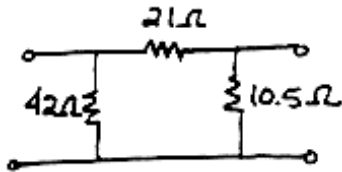

$$-Y_{12} = -Y_{21} = \frac{1}{21}$$

$$Y_{11} + Y_{12} = \frac{1}{42} \quad \text{so} \quad Y_{11} = \frac{1}{42} - \left(-\frac{1}{21}\right) = \frac{3}{42}$$

$$Y_{22} + Y_{21} = 10.5 \quad \text{so} \quad Y_{22} = \frac{1}{10.5} - \left(-\frac{1}{21}\right) = 1/7$$

$$Y = \begin{bmatrix} \frac{1}{42} & -\frac{1}{21} \\ -\frac{1}{21} & \frac{1}{7} \end{bmatrix}$$

To find the Z parameters, use the definitions


$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = \frac{42(21+10.5)}{42+31.5} = 18\Omega$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = \frac{10.5(63)}{73.5} = 9\Omega$$


$$Z_{12} = Z_{21} = \frac{V_1}{I_2} \Big|_{I_1=0} = 6\Omega$$

Since  $I = \frac{10.5}{73.5} I_2$ , then  $V_1 = \frac{42(10.5)}{73.5} I_2 = 6I_2$


$$\therefore Z = \begin{bmatrix} 18 & 6 \\ 6 & 9 \end{bmatrix}$$

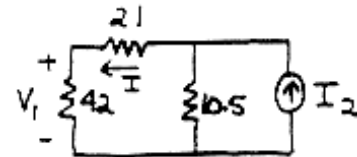

Ex. 17.6-1

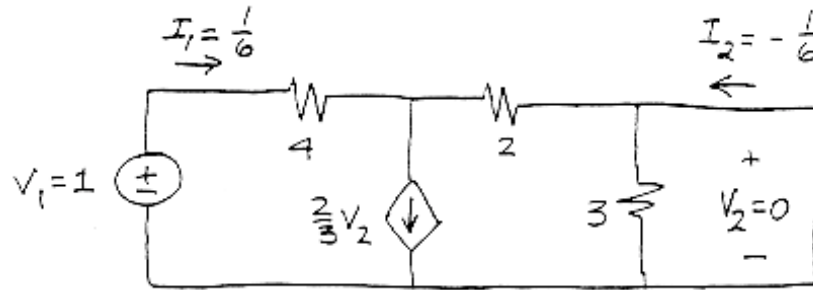

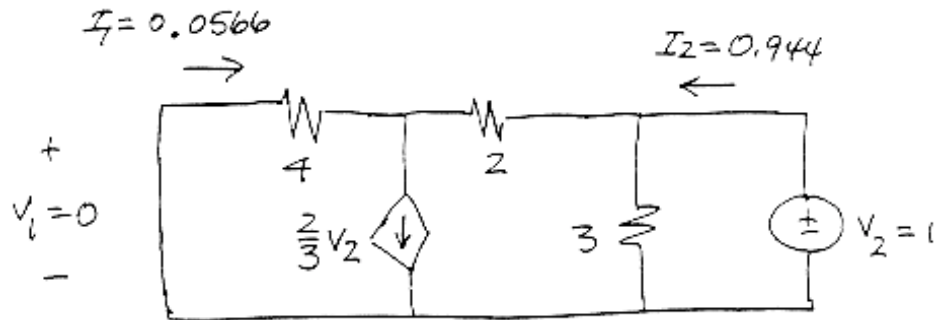
$$Y_{11} = \frac{I_1}{V_1} = \frac{1}{6} \quad Y_{21} = \frac{I_2}{V_1} = -\frac{1}{6} = -0.167$$



$$Y_{12} = \frac{I_1}{V_2} = 0.0566 \quad Y_{22} = \frac{I_2}{V_2} = 0.944$$

Ex. 17.7-1

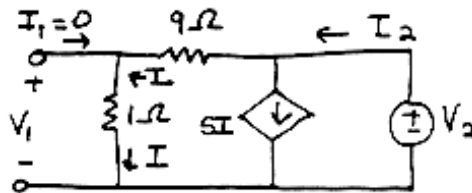Set  $I_1 = 0$   
and connect  $V_2$   
and find  $I_2$  and  $V_1$




Note :  $I_2 = 6I$ ,  $V_2 = (9+1)I = 10I$ ,  $V_1 = 1I$

Thus  $h_{22} = \frac{I_2}{V_2} = \frac{6I}{10I} = 0.6 \text{ S}$

$$h_{12} = \frac{V_1}{V_2} = \frac{I}{10I} = 0.1$$

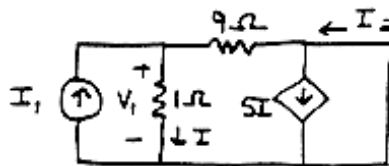Set  $V_2 = 0$   
and connect  $I_1$   
and find  $I_2$  and  $V_1$



$$V_1 = 1 I$$

$$I_1 = I + \frac{V_1}{9} = \frac{10}{9} I$$

$$I_2 = 5I - \frac{V_1}{9} = \frac{44}{9} I$$

$$h_{11} = \frac{V_1}{I_1} = \frac{I}{10/9 I} = 0.9 \Omega$$

$$h_{21} = \frac{I_2}{I_1} = \frac{44/9 I}{10/9 I} = 4.4$$

**Ex. 17.8-1**  $Y = \begin{bmatrix} 2/15 & -1/5 \\ -1/10 & 2/5 \end{bmatrix}$   $\Delta Y = \frac{4}{75} - \frac{1}{50} = \frac{1}{30}$

then  $Z = 30 \begin{bmatrix} 2/5 & 1/5 \\ 1/10 & 2/15 \end{bmatrix} = \begin{bmatrix} 12 & 6 \\ 3 & 4 \end{bmatrix}$

**Ex. 17.8-2**  $T = \begin{bmatrix} \frac{2/5}{(-1/10)} & \frac{1}{(-1/10)} \\ \frac{1/30}{(-1/10)} & \frac{2/15}{(-1/10)} \end{bmatrix} = \begin{bmatrix} 4 & 10 \\ 1/3 & 4/3 \end{bmatrix}$

**Ex. 17.9-1**  $T_a = \begin{bmatrix} 1 & 12 \\ 0 & 1 \end{bmatrix}$   $T_b = \begin{bmatrix} 1 & 0 \\ 1/6 & 1 \end{bmatrix}$   $T_c = \begin{bmatrix} 1 & 3 \\ 0 & 1 \end{bmatrix}$

$T_a T_b T_c = \begin{bmatrix} 1 & 12 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1/6 & 1 \end{bmatrix} T_c$   
 $= \begin{bmatrix} 3 & 12 \\ 1/6 & 1 \end{bmatrix} \begin{bmatrix} 1 & 3 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 3 & 21 \\ 1/6 & 3/2 \end{bmatrix}$

Problems

Section 17-4: T-to-T1 Transformations


17.4-1



(a)

Determine equivalent resistance,  $R_{ab}$  of Fig.(a)

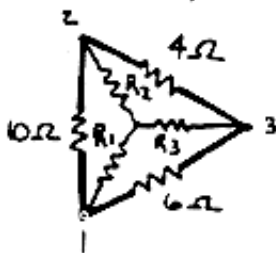Now the  $10\Omega$  resistance is part of two 3-terminals circuits that cannot be simplified by series-parallel combination. First replace circuit with thicker lines by an equivalent Y (Fig.(b)).




(b)

$$Z_1 = \frac{Z_{12}Z_{31}}{Z_{12}+Z_{23}+Z_{31}} = \frac{(10)(6)}{10+6+4} = 3\Omega$$


$$Z_2 = \frac{Z_{23}Z_{12}}{Z_{12}+Z_{23}+Z_{31}} = \frac{(4)(10)}{20} = 2\Omega$$

$$Z_3 = \frac{Z_{31}Z_{23}}{Z_{12}+Z_{23}+Z_{31}} = \frac{(6)(4)}{20} = 1.2\Omega$$

Thus have

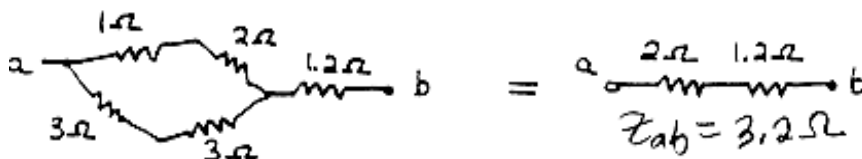

17.4-2

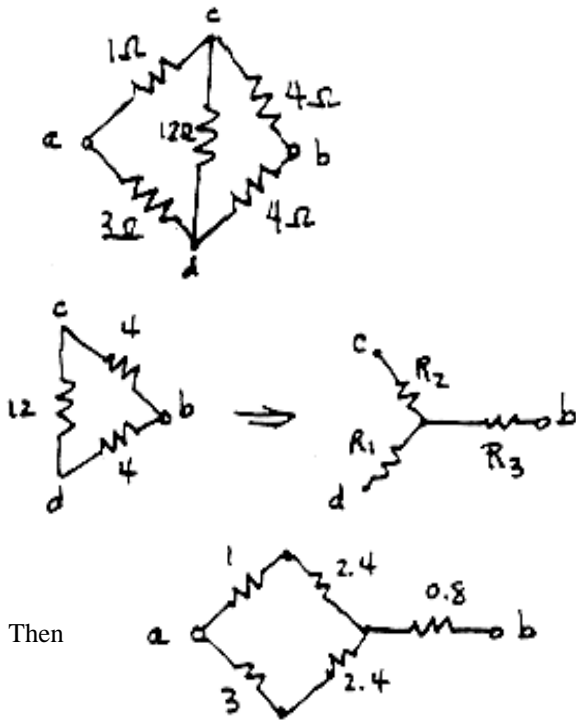

$$R_1 = \frac{12 \times 4}{12 + 4 + 4} = \frac{48}{20} = 2.4$$


$$R_2 = \frac{12 \times 4}{20} = 2.4$$

$$R_3 = \frac{4 \times 4}{20} = 0.8$$

Then

$$R_p = \frac{3.4(5.4)}{3.4 + 5.4} = 2.086 \quad \text{so } R_{ab} = 2.886\Omega$$

17.4-3

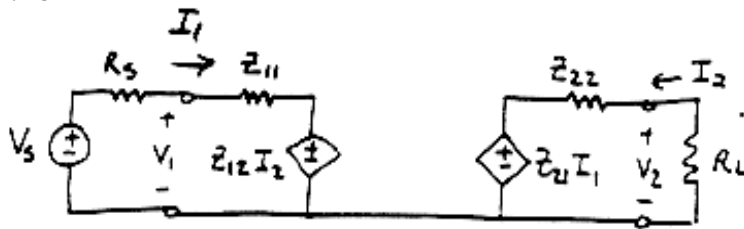

$$I_2 = \frac{-Z_{21} I_1}{Z_{22} + R_L}$$

$$A_i = \frac{-I_2}{I_1} = \frac{Z_{21}}{Z_{22} + R_L}$$

(forward current gain)

$$R_{in} = \frac{V_1}{I_1} = \frac{Z_{11} I_1 + Z_{12} I_2}{I_1}$$

$$= Z_{11} - \frac{Z_{12} A_i I_1}{I_1} \quad \text{where } I_2 = A_i I_1 = \frac{Z_{21} I_1}{Z_{22} + R_L}$$

$$= Z_{11} - \frac{Z_{12} Z_{21}}{(Z_{22} + R_L)}$$

Forward voltage gain  $A_v = \frac{V_2}{V_1}$  where  $V_2 = -I_2 R_L = A_i R_L I_1$


also note :  $V = R_{in} I_1$

$$\text{So } A_v = \frac{V_2}{V_1} = \frac{A_i R_L}{R_{in}}$$


$$\therefore A_p = A_i A_v = A_i^2 \frac{R_L}{R_{in}}$$
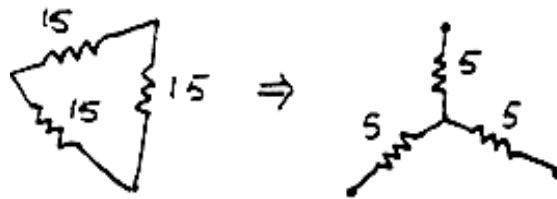
#### 17.4-4

Use  $\Delta$  to Y transformation to transform  $R_1 \Delta$  network



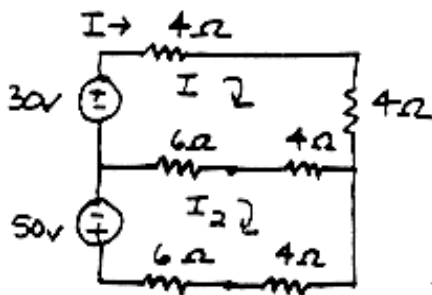
$$\text{Have } 5 \parallel R = 5 \parallel 20 = 4 \Omega$$



$$\begin{cases} 30 = 18I - 10I_2 \\ 50 = 10I - 20I_2 \end{cases}$$

$$I = \frac{\begin{vmatrix} 30 & -10 \\ 50 & -20 \end{vmatrix}}{18(-20) - (-10)10} = \frac{-100}{-260} = \underline{0.385A}$$

#### 17.4-5

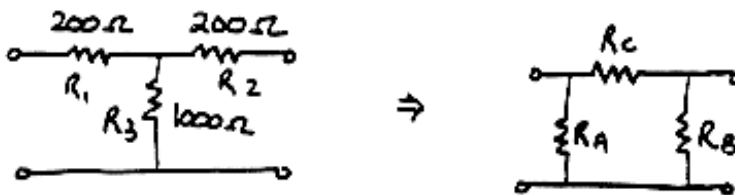


See Fig. 18-2.

$$R_A = R_B = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} \quad \text{Since } R_1 = R_2$$


$$\text{then } R_A = R_B = \frac{200(200) + 200(1000) + 1000(200)}{200} = 2200 \Omega$$

$$R_C = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = \frac{44 \times 10^4}{10^3} = 440 \Omega$$

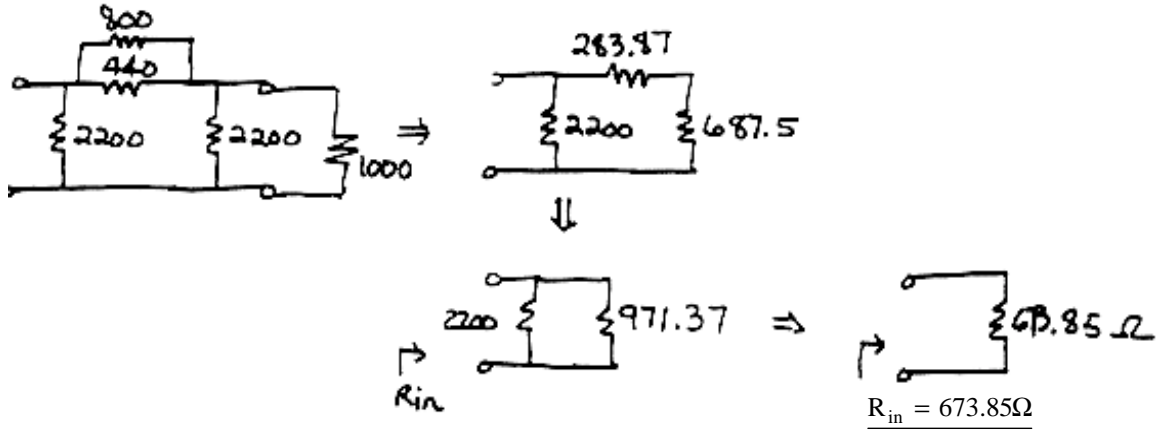

Section 17-5: Equations of Two-Port Networks

17-5-1

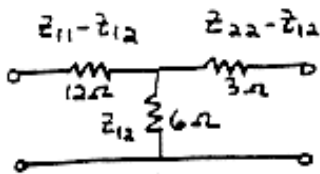

T-network  $\Rightarrow$  use Fig.17.5-1 to get parameters

Note =  $Z_{12} = 6$        $Z_{22} = 9$   
 $Z_{11} = 18$

so  $Z = \begin{bmatrix} 18 & 6 \\ 6 & 9 \end{bmatrix}$


Y parameters:

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{1}{14}$$


$$Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = \frac{-6 I_2}{(6+12)V_2} = -\frac{1}{21} = Y_{21}$$

$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = \frac{V_2/7}{V_2} = \frac{1}{7}$$

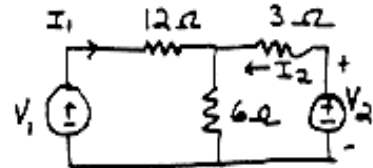So  $Y = \begin{bmatrix} 1/14 & -1/21 \\ -1/21 & 1/7 \end{bmatrix}$




17.5-2

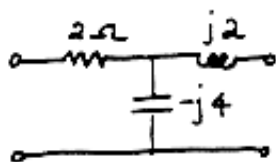

$$Z = \begin{bmatrix} 2-j4 & -j4 \\ -j4 & +j2 \end{bmatrix}$$

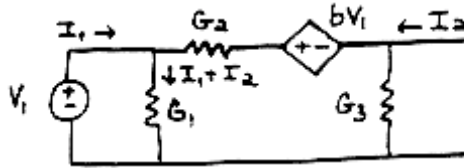17.5-3

If  $V_2 = 0 \rightarrow$  short circuit the output




$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}, \quad Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

Now  $V_1 = \frac{I_1 + I_2}{G_1}$  and  $\frac{I_1 + I_2}{G_1} + \frac{I_2}{G_2} = bV_1$

So  $I_1 = (G_1 - (b-1)G_2)V_1 = -1V_1$  &  $I_2 = (b-1)G_2V_1 = 3V_1$

Then  $Y_{11} = -1S$  and  $Y_{21} = 3S$

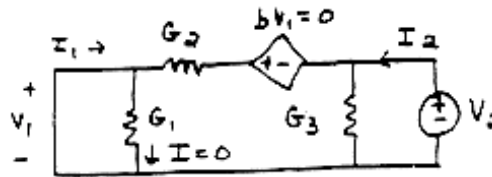If  $V_1 = 0 \rightarrow$  short circuit the input




$$V_2 = \frac{I_1 + I_2}{G_3} = V_2$$

also  $V_2 = \frac{-I_2}{G_2} \quad \therefore Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = -G_2 = -1S$

$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = G_2 + G_3 = 4S$$

17.5-4

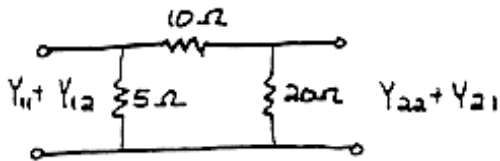

Using Fig. 17.5-2 as shown:



$$Y_{11} + Y_{12} = 0.2S$$

$$-Y_{12} = -Y_{21} = 0.1 \text{ or } Y_{12} = Y_{21} = -0.1S$$

$$Y_{11} = 0.2 - Y_{12} = 0.3S$$

$$Y_{22} = 0.05 - Y_{21} = 0.15S$$

17.5-5

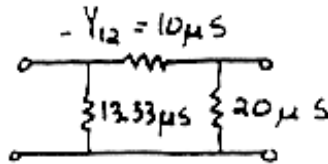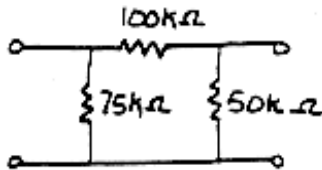


$$Y_{12} = -10\mu S = Y_{21}$$

$$Y_{11} + Y_{12} = 13.33\mu S$$

$$Y_{11} = 23.33\mu S$$

$$Y_{22} + Y_{21} = 20\mu S \quad \text{thus } Y_{22} = 30\mu S$$

17.5-6

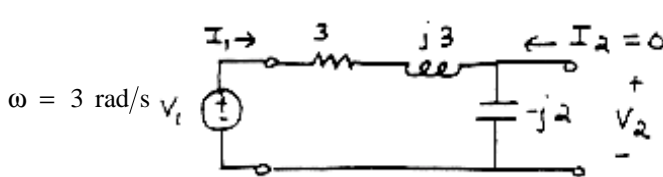


$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = 3 + j3 - j2 = (3+j)\Omega$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = \frac{-j2I_1}{I_1} = -j2\Omega$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = -j2\Omega$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = -j2\Omega$$

17.5-7

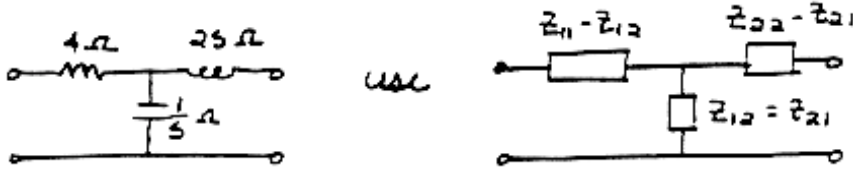


Now  $Z_{11} - Z_{21} = 4$   
 $Z_{21} - Z_{12} = 1/s$  } so  $Z_{11} = 4 + 1/s = \frac{4s+1}{s}$   
 $Z_{22} - Z_{21} = 2s$  so  $Z_{22} = 2s + 1/s = \frac{2s^2+1}{s}$

17.5-8


$Y = \begin{bmatrix} \frac{s+1}{s} & -1 \\ -1 & s+1 \end{bmatrix}$

Use  $\pi$  network

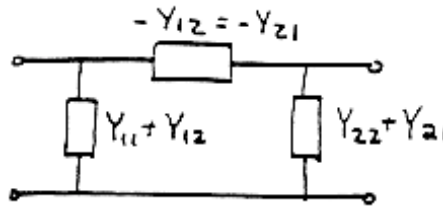


$Y_{12} = -1s$   
 $Y_{11} = \frac{s+1}{s}$  so  $Y_{11} + Y_{12} = \frac{s+1}{s} - 1 = \frac{1}{s}$   
 $Y_{22} + Y_{21} = (s+1) - 1 = s$

So have

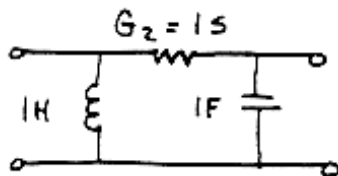

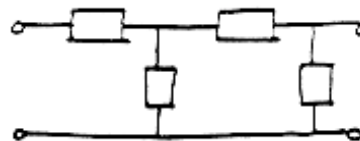17.5-9

$Z = \begin{bmatrix} \frac{s^2+2s+2}{s^2+s+1} & \frac{1}{s^2+s+1} \\ \frac{1}{s^2+s+1} & \frac{s^2+1}{s^2+s+1} \end{bmatrix}$  has 4 elements  $\Rightarrow$




$(s^2 + s + 1) = \text{char. eqn.} \Rightarrow \text{leads to } R_1 = R_2 = 1$

capacitance :  $Z = \frac{1}{Cs}$  use  $C = 1$   
 inductor :  $Z = Ls$  so use  $L = 1$  } to get  $s^2 + s + 1$

$Z_{12} = Z_{21}$  so some of symmetry required

Use a trial :

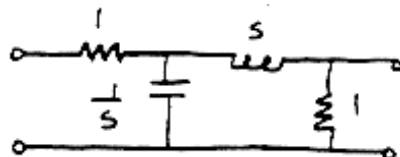




$$\text{Try } Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = \frac{1(s + \frac{1}{s})}{1 + s + \frac{1}{s}} = \frac{(s^2 + 1)}{s^2 + s + 1}$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = 1 + \frac{\frac{1}{s}(s+1)}{\frac{1}{s} + s + 1} = \frac{s^2 + 2s + 2}{s^2 + s + 1}$$

checks

### 17.5-10

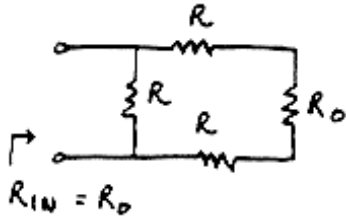


$$R_o = \frac{R(2R + R_o)}{3R + R_o}$$

$$\begin{aligned} \text{Solving for } R_o \Rightarrow R_o &= R \pm \sqrt{4R^2 + 4(2R^2)} \\ &= R \pm \sqrt{3R} = \underline{(\sqrt{3}-1)R} \end{aligned}$$

## Section 17-6: Z and Y Parameters . . .

### 17.6-1

Set  $V_2 = 0$

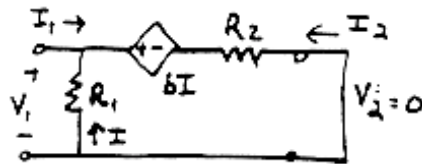


$$I = -V_1/R_1, \quad I_2 = -\frac{(b + R_1)}{R_1 R_2} V_1$$

$$I_1 = -I_2 - I = \left( \frac{b + R_1 + R_2}{R_1 R_2} \right) V_1$$

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = \frac{b + R_1 + R_2}{R_1 R_2} \quad \text{and} \quad Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} = \frac{-(b + R_1)}{R_1 R_2}$$

Set  $V_1 = 0$

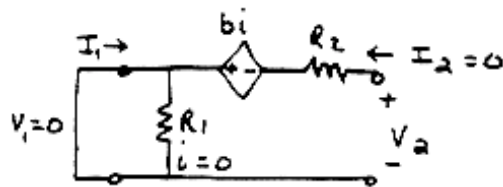


$$I_2 = -I_1$$

$$\text{KVL: } V_2 = R_2 I_2 \Rightarrow I_2 = \frac{V_2}{R_2}$$


$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = \frac{1}{R_2} \quad \text{and} \quad Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} = -\frac{1}{R_2}$$

17.6-2

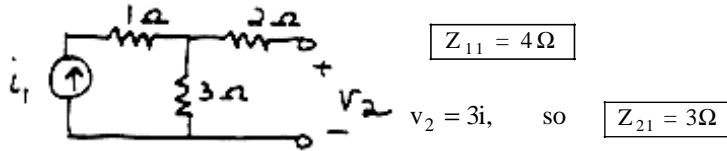(1) Place source  $i_1$  and open circuit output



(2) Set  $i_1 = 0$

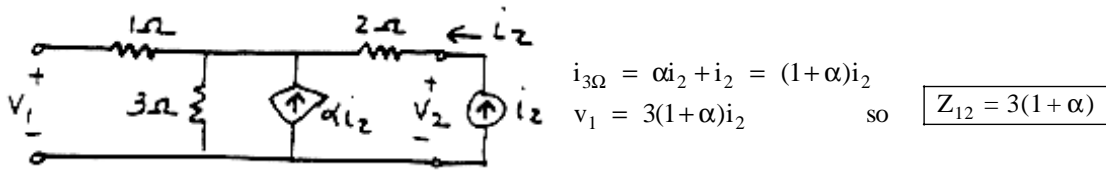

$v_2 = 2i_2 + 3(1+\alpha)i_2$  so  $Z_{22} = (5 + 3\alpha)$


So  $Z = \begin{bmatrix} 4 & 3(1+\alpha) \\ 3 & (5+3\alpha) \end{bmatrix}$

17.6-3

Use two Parallel networks

$Y_1 = \begin{bmatrix} 1 & 0 \\ 2 & 1 \end{bmatrix}$

$Y_2 = \begin{bmatrix} 2s & -s \\ -s & 2s \end{bmatrix}$

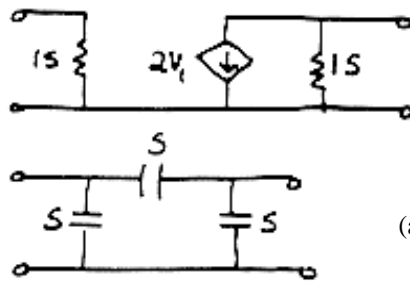

network 1

network 2  
(admittance form)

Since  $Y_{12} = Y_{21} = -s \Rightarrow Y_{11} = 2s$  and  $Y_{22} = 2s$   
 $Y_{11} = Y_{12} = s$

$Y_T = Y_1 + Y_2 = \begin{bmatrix} 1+2s & -s \\ 2-s & 1+2s \end{bmatrix}$       $Y_T \begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix} = \begin{bmatrix} 1/s \\ 0 \end{bmatrix}$


So  $\begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix} = Y_T^{-1} \begin{bmatrix} 1/s \\ 0 \end{bmatrix} = \frac{1}{q} \begin{bmatrix} 2s+1 & s \\ s-2 & 2s+1 \end{bmatrix} \begin{bmatrix} 1/s \\ 0 \end{bmatrix}$

where  $q = 3s^2 + 6s + 1$


So  $V_2(s) = \frac{(s-2)}{s(3s^2+6s+1)} = \frac{1}{3} \left[ \frac{-6}{s} + \frac{-1.25}{s+1.82} + \frac{7.25}{s+0.184} \right]$

Thus  $v_2(t) = \frac{1}{3} \left[ -6 - 1.25e^{-0.182t} + 7.25e^{-0.184t} \right] \quad t \geq 0$

17.6-4

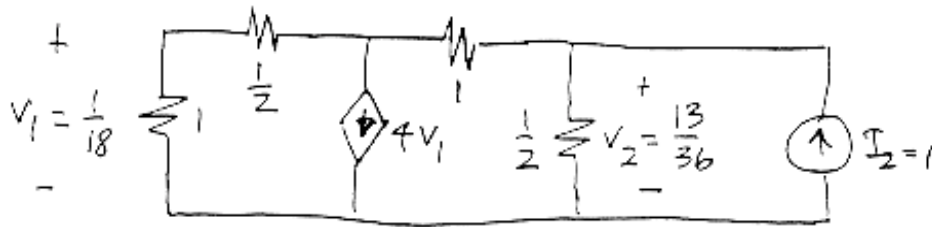

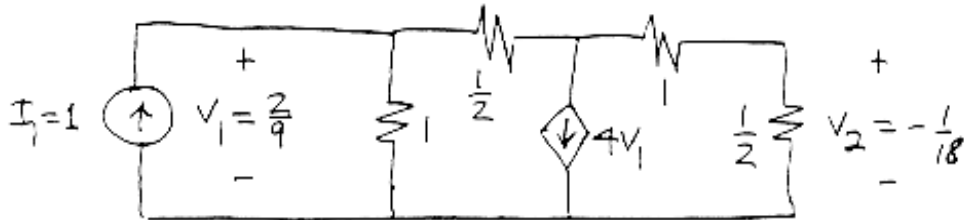
$$Z_{12} = \frac{V_1}{I_2} = \frac{1}{18} \quad Z_{22} = \frac{V_2}{I_2} = \frac{13}{36} = .361$$




$$Z_{11} = \frac{V_1}{I_1} = \frac{2}{9} \quad Z_{21} = \frac{V_2}{I_1} = -\frac{1}{8}$$

17.6-5

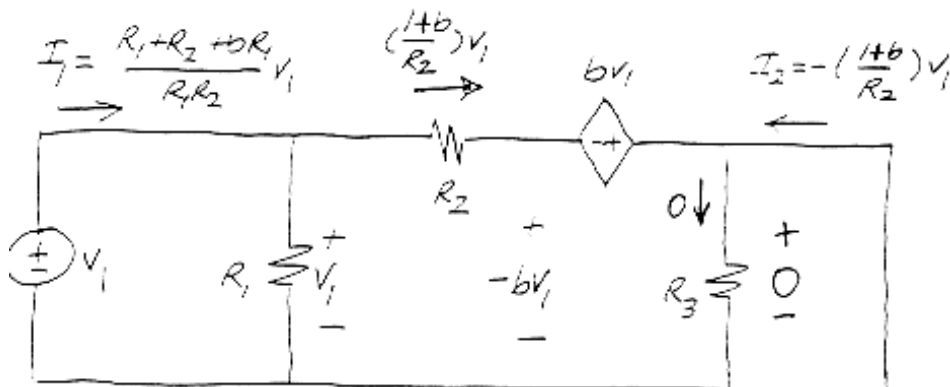

$$Y_{11} = \frac{I_1}{V_1} = \frac{R_1 + R_2 + bR_1}{R_1 R_2} \quad Y_{21} = \frac{I_2}{V_1} = -\left(\frac{1+b}{R_2}\right)$$

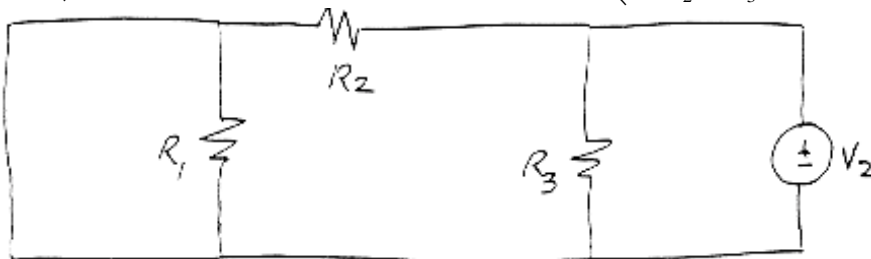
$$I_1 = -\frac{V_2}{R_2} \quad I_2 = \frac{V_2}{R_2} + \frac{V_2}{R_3}$$



$$Y_{12} = \frac{I_1}{V_1} = -\frac{1}{R_2} \quad Y_{22} = \frac{I_2}{V_2} = \frac{R_2 + R_3}{R_2 R_3}$$

Section 17-7: Hybrid Transmission Parameters

17.7-1

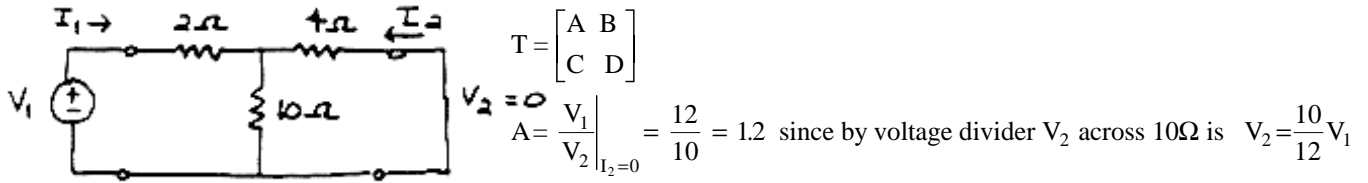

$$T = \begin{bmatrix} A & B \\ C & D \end{bmatrix}$$


$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{12}{10} = 1.2 \text{ since by voltage divider } V_2 \text{ across } 10\Omega \text{ is } V_2 = \frac{10}{12} V_1$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} = \frac{34}{5} = 6.8\Omega \text{ since } -I_2 = \frac{V_1}{2+4\parallel 10} = \frac{5}{34} V_1$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{1}{10} = 0.1S$$


$$D = \left. \frac{I_1}{-I_2} \right|_{V_2=0} = \frac{1}{10/(10+4)} = 1.4 \text{ since } I_2 = \frac{10}{10+4} I_1 \text{ (current divider)}$$

17.7-2

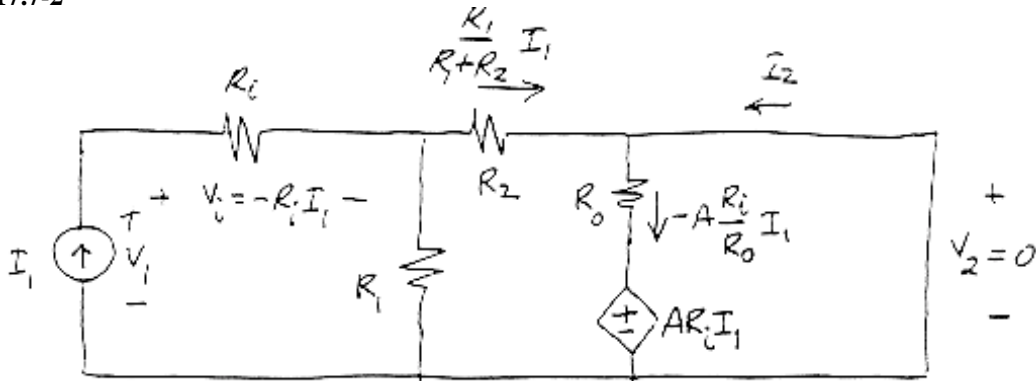

$$V_1 = (R_i + R_1 \parallel R_2) I_1 \Rightarrow h_{11} = R_i + R_1 \parallel R_2 = 600k\Omega$$

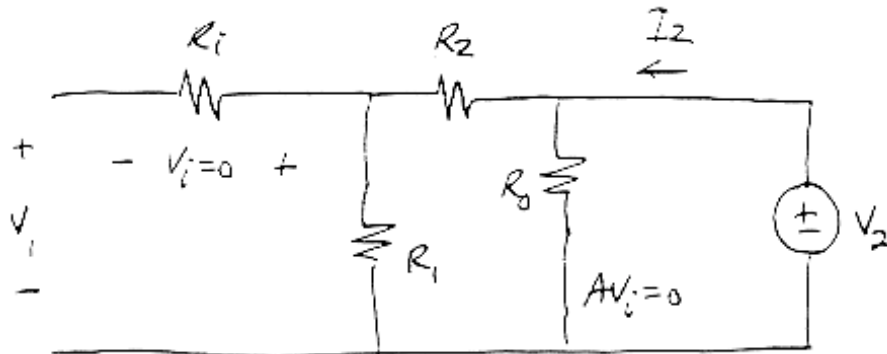
$$I_2 = -A \frac{R_i}{R_o} I_1 - \frac{R_1}{R_1 + R_2} I_1 \Rightarrow h_{21} = -\left( A \frac{R_i}{R_o} + \frac{R_1}{R_1 + R_2} \right) = -10^6$$



$$I_2 = \frac{V_2}{R_o \parallel (R_1 + R_2)} \Rightarrow h_{22} = \frac{R_o + R_1 + R_2}{R_o (R_1 + R_2)} = 10^{-3}$$

$$V_1 = \frac{R_1}{R_1 + R_2} V_2 \Rightarrow h_{12} = \frac{R_1}{R_1 + R_2} = \frac{1}{2}$$

17.7-3

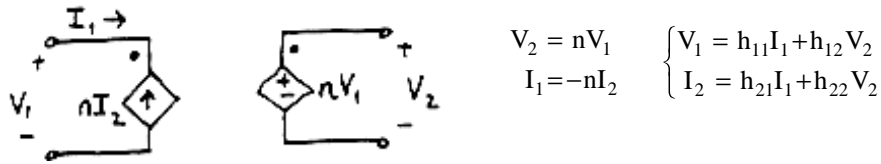


$$\begin{cases} V_2 = nV_1 \\ I_1 = -nI_2 \end{cases} \Rightarrow \begin{cases} V_1 = h_{11}I_1 + h_{12}V_2 \\ I_2 = h_{21}I_1 + h_{22}V_2 \end{cases}$$

Then  $h_{11} = 0$  and  $h_{22} = 0$


$$h_{12} = \frac{1}{n} \text{ and } h_{21} = \frac{1}{-n}$$

17.7-4

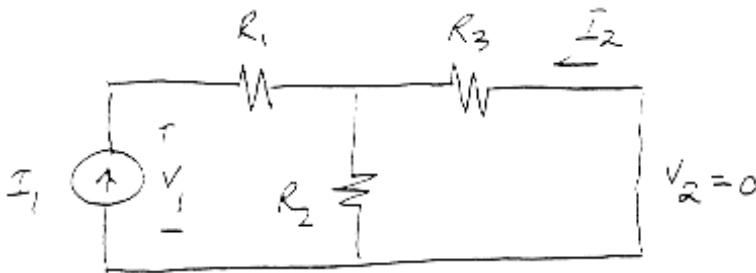

$$V_1 = (R_1 + R_2 // R_3) I_1 \Rightarrow h_{11} = R_1 + \frac{R_2 R_3}{R_2 + R_3}$$

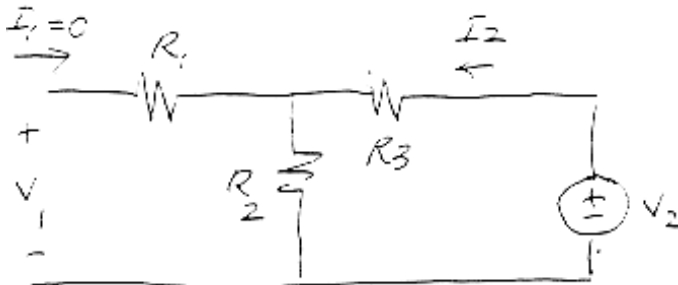
$$I_2 = -\frac{R_2}{R_2 + R_3} I_1 \Rightarrow h_{21} = -\frac{R_2}{R_2 + R_3}$$



$$I_2 = \frac{V_2}{R_2 + R_3} \Rightarrow h_{22} = \frac{1}{R_2 + R_3}$$


$$V_1 = \frac{R_2}{R_2 + R_3} V_2 \Rightarrow h_{12} = \frac{R_2}{R_2 + R_3}$$

17.7-5

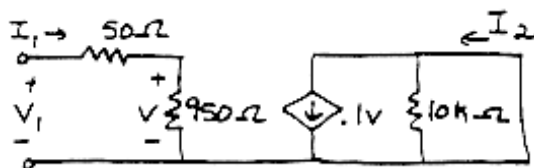

$$\begin{aligned} I_2 &= .1V, V = 950 I_1 \\ \text{so } I_2 &= .1 (950) I_1 \end{aligned}$$


$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = 50 + 950 = \underline{1000\Omega} \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} = 95$$

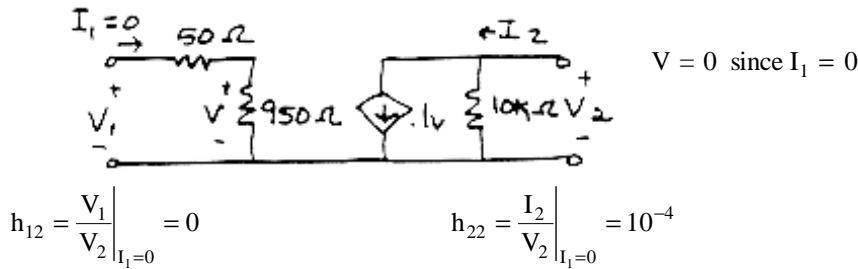

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = 0 \qquad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = 10^{-4}$$

17.7-6

$Y = G + jB$   
 $Z = R + jX$

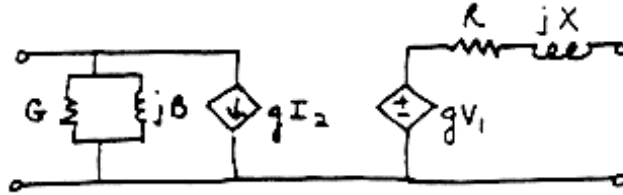

$$\left. \begin{aligned} \text{open ckt: } G &= \frac{P}{V^2} = \frac{100}{(10^3)^2} = 100\mu\text{S} \\ Y &= \frac{I}{V} = \frac{0.42}{1000} = 420\mu\text{S} \end{aligned} \right\} \begin{aligned} B &= -\sqrt{Y^2 - G^2} = -408\mu\text{S} \\ g &= \frac{V_2}{V_1} = \frac{500}{1000} = \frac{1}{2} \end{aligned}$$

$$\left. \begin{aligned} \text{shortckt: } R &= \frac{g^2 P}{I_1^2} = \frac{400}{4 \times 10^2} = 1\Omega \\ Z &= g^2 \frac{V_1}{I_1} = \frac{126}{4 \times 10} = 3.15\Omega \end{aligned} \right\} X = \sqrt{Z^2 - R^2} = 3\Omega$$

Section 17-8: Relationships between Two-Port Parameters

17.8-1  $\tilde{I} = \tilde{Y} \tilde{V}$

$$Y \text{ parameters } \begin{cases} I_1 = Y_{11}V_1 + Y_{12}V_2 \\ I_2 = Y_{21}V_1 + Y_{22}V_2 \end{cases} \quad (1) \quad h \text{ parameters } \begin{cases} V_1 = h_{11}I_1 + h_{12}V_2 \\ I_2 = h_{21}I_1 + h_{22}V_2 \end{cases} \quad (2)$$

Rewrite eqn.(1) into form of (2) to get  $I_1$  and  $V_2$  on right side of eqn.

$$-Y_{11}V_1 = I_1 + Y_{12}V_2$$

$$-Y_{21}V_1 + I_2 = Y_{22}V_2 \quad \text{or} \quad \hat{Y} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = Y^* \begin{bmatrix} -I_1 \\ V_2 \end{bmatrix}$$

where  $\hat{Y}$  and  $Y^*$  are new matrices related to  $Y$

and  $h$  requires  $\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = H \begin{bmatrix} -I_1 \\ V_2 \end{bmatrix}$

$$\therefore H = \hat{Y}^{-1} Y^* = \begin{bmatrix} -Y_{11} & 0 \\ -Y_{21} & 1 \end{bmatrix}^{-1} \begin{bmatrix} -1 & Y_{12} \\ 0 & Y_{22} \end{bmatrix} = \begin{bmatrix} -1/Y_{11} & 0 \\ -Y_{21}/Y_{11} & 1 \end{bmatrix} \begin{bmatrix} -1 & Y_{12} \\ 0 & Y_{22} \end{bmatrix} = \begin{bmatrix} 1 & -Y_{12}/Y_{11} \\ Y_{11} & Y_{22} - Y_{12}Y_{21}/Y_{11} \\ Y_{21} & Y_{22} - Y_{12}Y_{21}/Y_{11} \\ Y_{11} & Y_{11} \end{bmatrix}$$

**17.8-2**  $\Delta Z = (3)(6) - (2)(2) = 14$

$$Y = \begin{bmatrix} \frac{Z_{22}}{\Delta Z} & -\frac{Z_{12}}{\Delta Z} \\ -\frac{Z_{21}}{\Delta Z} & \frac{Z_{11}}{\Delta Z} \end{bmatrix} = \begin{bmatrix} \frac{6}{14} & -\frac{2}{14} \\ -\frac{2}{14} & \frac{3}{14} \end{bmatrix}$$

**17.8-3**  $\Delta Y = (0.1)(0.5) - (0.4)(0.1) = .01$

$$H = \begin{bmatrix} \frac{1}{Y_{11}} & -\frac{Y_{12}}{Y_{11}} \\ \frac{Y_{21}}{Y_{11}} & \frac{\Delta Y}{Y_{11}} \end{bmatrix} = \begin{bmatrix} 10 & -1 \\ 4 & 0.1 \end{bmatrix}$$

**17.8-4**  $\Delta Y = (0.5)(0.6) - (-0.4)(-0.4)$

$$H = \begin{bmatrix} \frac{1}{Y_{11}} & -\frac{Y_{12}}{Y_{11}} \\ \frac{Y_{21}}{Y_{11}} & \frac{\Delta Y}{Y_{11}} \end{bmatrix} = \begin{bmatrix} 2 & 0.8 \\ -0.8 & 0.28 \end{bmatrix}$$


**Section 17-9: Interconnection of Two-Port Networks**

**17.9-1**  $Y = Y_a + Y_b$  in parallel

$$Y_a = \begin{bmatrix} \frac{4}{3} & -\frac{1}{3} \\ -\frac{1}{3} & \frac{1}{3} \end{bmatrix}$$

$$Y_b = \begin{bmatrix} \frac{3}{2} & -1 \\ -1 & \frac{4}{3} \end{bmatrix}$$
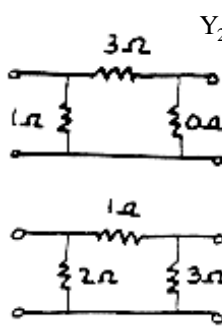
$$Y = \begin{bmatrix} (\frac{4}{3} + \frac{3}{2}) & -\frac{4}{3} \\ -\frac{4}{3} & \frac{5}{3} \end{bmatrix} = \begin{bmatrix} \frac{17}{6} & -\frac{4}{3} \\ -\frac{4}{3} & \frac{5}{3} \end{bmatrix}$$



$$Y_{22} = 0 - Y_{21} = \frac{1}{3}$$


$$Y_{11} + Y_{12} = 1 \quad \text{so } Y_{11} = 1 + \frac{1}{3} = \frac{4}{3}$$

$$Y_{11} + Y_{12} = \frac{1}{2}$$


$$Y_{11} = \frac{1}{2} - (-1) = \frac{3}{2}$$

$$Y_{21} + Y_{22} = \frac{1}{3} \quad \text{so } Y_{22} = 1 + \frac{1}{3} = \frac{4}{3}$$


17.9-2

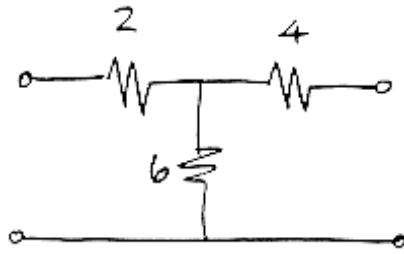
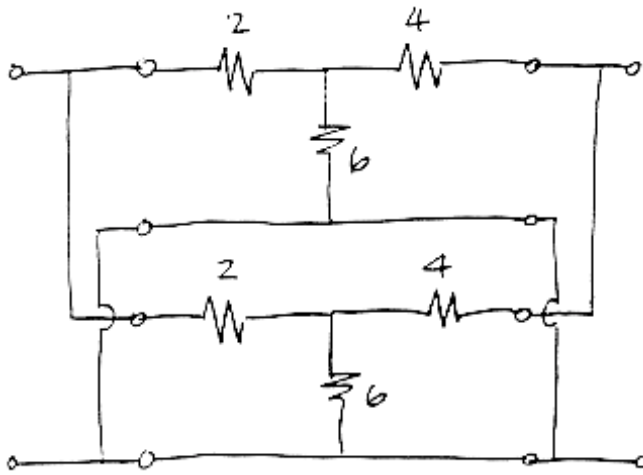
$$Y = \begin{bmatrix} 10 & -6 \\ 44 & 44 \\ -6 & 8 \\ 44 & 44 \end{bmatrix} \quad T = \begin{bmatrix} 8 & 44 \\ 6 & 6 \\ 1 & 10 \\ 6 & 6 \end{bmatrix}$$


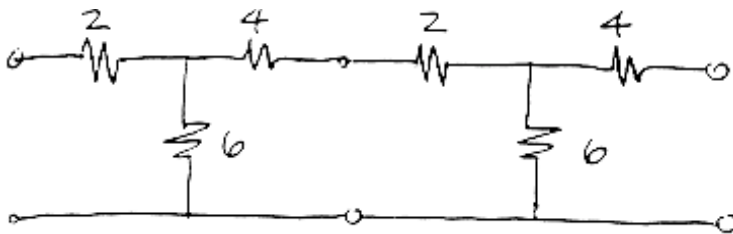
$$Y_p = Y + Y = \begin{bmatrix} 20 & -12 \\ 44 & 44 \\ -12 & 16 \\ 44 & 44 \end{bmatrix}$$



$$T_c = T \cdot T' = \begin{bmatrix} 108 & 792 \\ 36 & 36 \\ 18 & 144 \\ 36 & 36 \end{bmatrix}$$


17.9-3

$$Y = \begin{bmatrix} 1 & -s \\ -s & 1+s \end{bmatrix} + \begin{bmatrix} G_1+G_2 & -G_2 \\ -G_2 & G_2+G_3 \end{bmatrix}$$



## Verification Problems

### VP 17-1

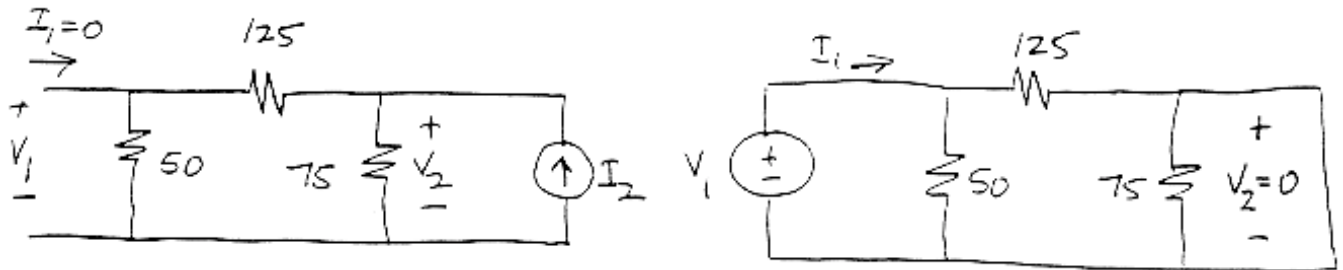


$$V_1 = 50 \left( \frac{75}{175+75} \right) I_2 = 15 I_2 \quad I_1 = \left( \frac{1}{50} + \frac{1}{125} \right) V_1 = 0.028 V_1$$


$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = 15 \quad Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = 28 \text{mS}$$

$Y_{11} \neq 24 \text{mS}$ , so the report is not correct.

### VP 17-2

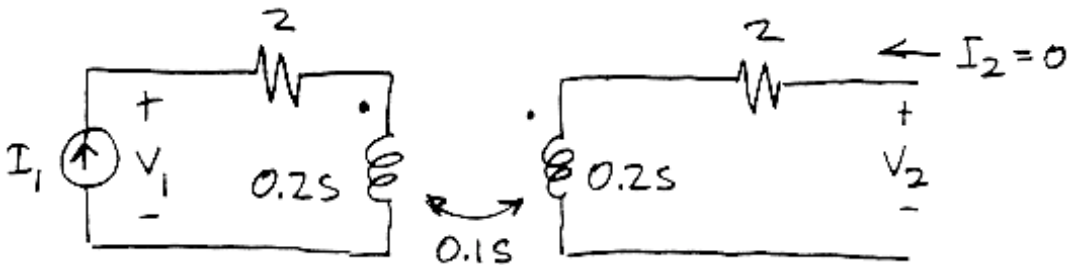
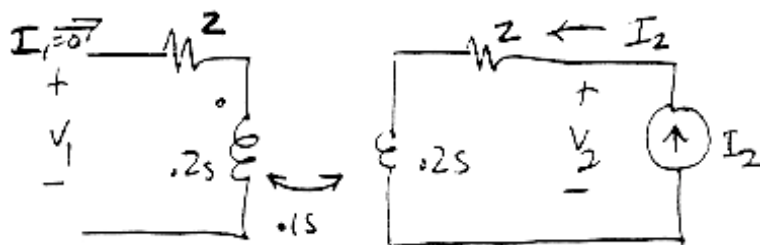
$$\left. \begin{aligned} V_1 &= (2+0.2s) I_1 \\ V_2 &= (0.1s) I_1 \end{aligned} \right\} \Rightarrow \begin{aligned} Z_{11} &= 2+0.2s = 0.2(s+10) \\ Z_{21} &= 0.1s \end{aligned}$$



$$Z_{22} = 2+2s \quad Z_{12} = 0.1s$$

$$\Delta Z = (2+2s)(2+2s) - (0.1s)(0.1s) = 0.01(3s^2 + 80s + 40)$$

$$T = \begin{bmatrix} \frac{Z_{11}}{Z_{21}} & \frac{\Delta Z}{Z_{21}} \\ \frac{1}{Z_{21}} & \frac{Z_{22}}{Z_{21}} \end{bmatrix} = \begin{bmatrix} \frac{2(s+10)}{s} & \frac{.1(3s^2+80s+40)}{s} \\ .1s & \frac{2(s+10)}{s} \end{bmatrix} \leftarrow \text{Does not agree!}$$

PSpice Problems


SP 17-1

```

I1 0 1 1
R1 1 2 12
R2 2 3 3
R3 2 0 6
I2 0 3 0

.end

```

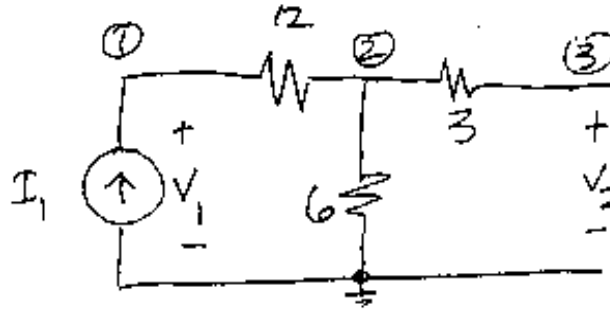

NODE	VOLTAGE :	NODE	VOLTAGE	NODE	VOLTAGE
( 1 )	18.0000	( 2 )	6.0000	( 3 )	6.0000

$$V_1 = 18 \Rightarrow Z_{11} = 18$$


$$V_2 = 6 \Rightarrow Z_{21} = 6$$

```

I1 0 1 0
R1 1 2 12
R2 2 3 3
R3 2 0 6
I2 0 3 1

.end

```

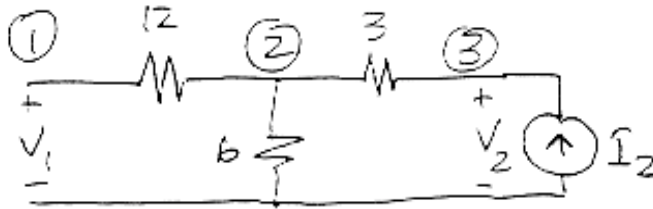

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
( 1 )	6.0000	( 2 )	6.0000	( 3 )	9.0000

$$V_1 = 6 \Rightarrow Z_{12} = 6$$

$$V_2 = 9 \Rightarrow Z_{22} = 9$$


SP 17-2

```

V1 1 0 1
R1 1 0 6
R2 1 2 3
R3 2 0 12
V2 2 0 0

.end

```

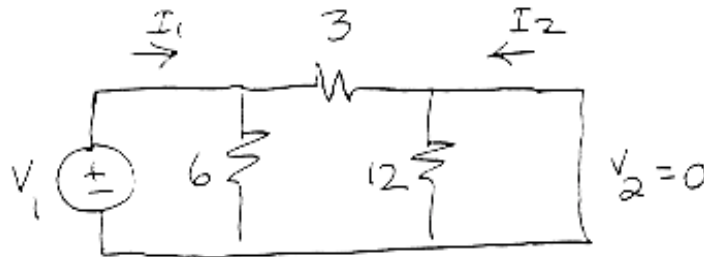


NODE	VOLTAGE	NODE	VOLTAGE
( 1 )	1.0000	( 2 )	0.0000

VOLTAGE SOURCE CURRENTS		$Y_{11} = 5$
NAME	CURRENT	
V1	$-5.000E-01 = -I_1$	
V2	$3.000E-01 = -I_2$	$Y_{21} = -.33$

```

V1  1  0  0
R1  1  0  6
R2  1  2  3
R3  2  0  12
V2  2  0  1
.end

```

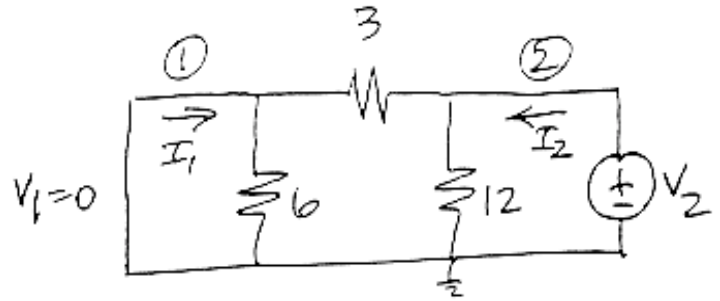

NODE	VOLTAGE	NODE	VOLTAGE
( 1 )	0.0000	( 2 )	1.0000

```

VOLTAGE SOURCE CURRENTS
NAME      CURRENT
V1        3.333E-01 = -I1
V2       -4.167E-01 = I2

```


$$Y_{12} = -.333, Y_{22} = -.4167$$

### SP 17-3

```

I1  0  1  1
R1  1  2  2
R2  2  3  3
E   3  0  2  0  6
V2  2  0  0
.end

```

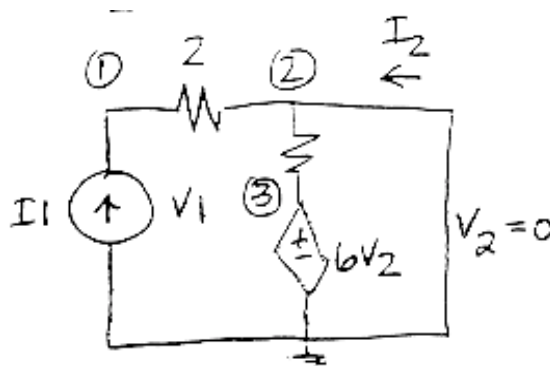

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
( 1 )	2.0000	( 2 )	0.0000	( 3 )	0.0000

$V_1 = 2 \Rightarrow h_{11} = 2$

```


VOLTAGE SOURCE CURRENTS
NAME      CURRENT
V2        1.000E+00 = -I2 ⇒ h21 = -1

```

```

I1  0  1  0
R1  1  2  2
R2  2  3  3
E   3  0  2  0  6
V2  2  0  1
.end

```

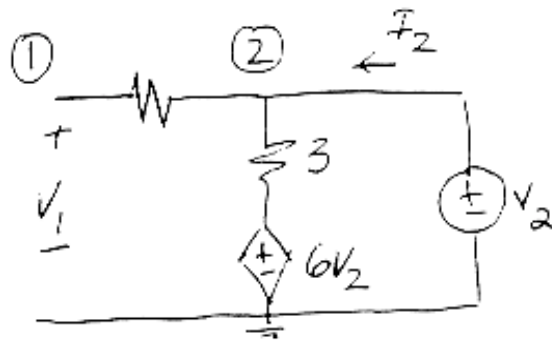

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
( 1)	1.0000	( 2)	1.0000	( 3)	6.0000


$V_1=1 \Rightarrow h_{12}=1$

VOLTAGE SOURCE CURRENTS  
NAME CURRENT  
V2 1.667E+00= $-I_2 \Rightarrow h_{22}= 1.667$

SP 17-4

I1	0	1	1
R1	1	3	1
R2	3	0	1
R3	2	3	2
R4	2	0	1
V2	2	0	0

.end

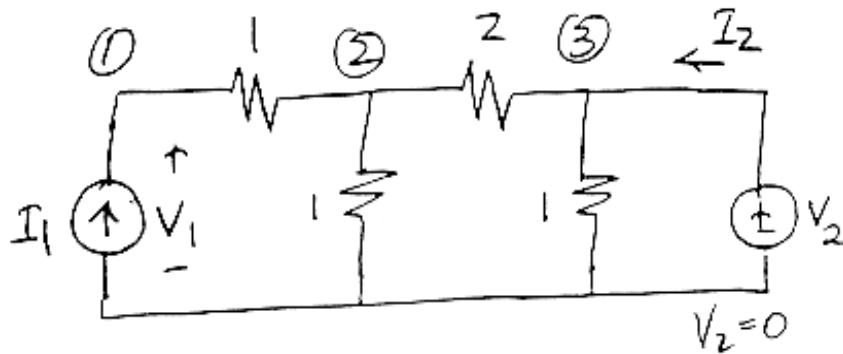


NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
( 1)	1.6667	( 2)	0.0000	( 3)	.6667

$V_1=1.667 \Rightarrow h_{11}=1.667$


VOLTAGE SOURCE CURRENTS  
NAME CURRENT  
V2 3.333E-01= $-I_2 \Rightarrow h_{21}= -.33$

## Design Problems

### DP 17-1

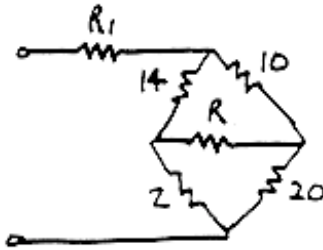

⇒

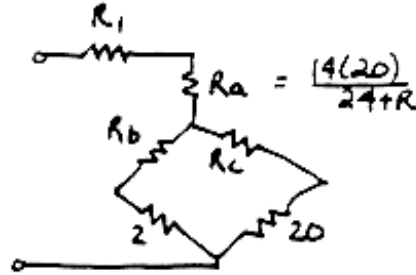

$$R_a = \frac{140}{24 + R}$$

$$R_b = \frac{14R}{24 + R}$$

$$R_c = \frac{10R}{24 + R}$$


$$R_{in} = R_1 + R_a + \frac{(2 + R_b)(20 + R_c)}{22 + R_b + R_c}$$

Need  $R_1 < 10$ ,  $R < 10 \Rightarrow$  try  $R = 6\Omega$

$$R_{in} = R_1 + \frac{140}{30} + \frac{(4.8)(22)}{26.8} = R_1 + 4.667 + 3.94$$

Now  $R_{in} = 16.6 = R_1 + 4.667 + 3.94$  thus  $R_1 = 8\Omega$

### DP 17-2

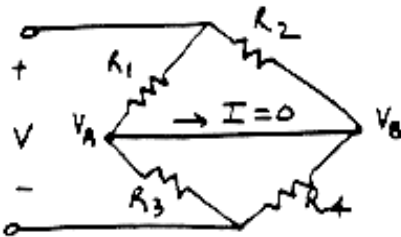

Need  $V_A + V_B$  for balance

$$\frac{R_1 V}{R_1 + R_3} = \frac{R_2 V}{R_2 + R_4} \quad (1)$$

$$\frac{R_3 V}{R_1 + R_3} = \frac{R_4 V}{R_2 + R_4} \quad (2)$$

Dividing (1) by (2) yields:  $\frac{R_1}{R_3} = \frac{R_2}{R_4}$  for balance

### DP17-3

$$\begin{cases} V_1 = h_{11}I_1 + h_{12}V_2 & (1) \\ I_2 = h_{21}I_1 + h_{22}V_2 & (2) \end{cases}$$

also  $V_2 = -I_2 R_L$  So  $I_2 = h_{21}I_1 - h_{22}R_L I_2$

$$\text{Then } \frac{I_2}{I_1} = h_{21} \left( \frac{1}{1 + h_{22}R_L} \right)$$

$$A_i = \frac{I_L}{I_1} = -\frac{I_2}{I_1} = -h_{21} \left( \frac{1}{1 + h_{22}R_L} \right)$$

$$\text{require : } 79 = 80 \left( \frac{1}{1 + h_{22}R_L} \right) \quad \text{or} \quad \frac{79}{80} \left( 1 + \frac{R_L}{80} \right) = 1 \quad R_L \text{ in k}\Omega$$

$$\Rightarrow \underline{R_L = 1\text{k}\Omega}$$

For  $R_{in}$ , need  $R_{in} = \frac{V_1}{I_1}$

$$I_2 = -\frac{V_2}{R_L} = h_{21}I_1 + h_{22}V_2 \quad \text{from (2)}$$

$$\text{or } V_2(h_{22} + 1/R_L) = -h_{21}I_1 \quad (3)$$


$$\text{Substituting (3) into (1)} \Rightarrow V_1 = h_{11}I_1 + \frac{h_{12}(-h_{21})}{(h_{22} + 1/R_L)}I_1$$

$$R_{in} \approx h_{11} - h_{12}R_L h_{21}$$

$$\text{(since } h_{22} \ll 1/R_L \text{)}$$

$$R_{in} = 45 - (5 \times 10^{-4})(10^3)(80) = \underline{5\Omega} \text{ okay since } < 10\Omega$$


#### DP 17-4

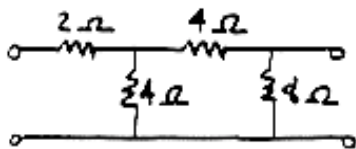

$$Z_{11} = 2 + \frac{4(12)}{4+12} = 5\Omega$$

$$Z_{22} = \frac{8(8)}{8+8} = 4\Omega$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

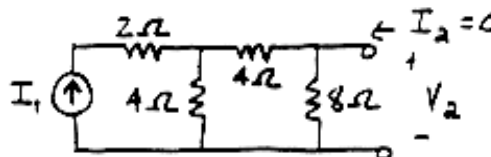

$$V_2 = 8 \left[ \frac{4}{4+12} I_1 \right] = 2I_1 \quad \text{so } Z_{21} = 2\Omega \text{ Similarly } Z_{12} = 2\Omega$$


$$\text{Connect } R_L \text{ and } V_s \Rightarrow V_2 = -I_2 R_L$$

$$V_1 = V_s$$

$$\text{Thèvenin: } Z_T = Z_{22} = 4\Omega \quad \text{so for max power transfer use } R_L = 4\Omega$$


$$P_{RL} = \frac{\left( \frac{V_s}{2} \right)^2}{4} = 89.3W \Rightarrow \underline{V_s = 37.8V}$$

DP 17-5

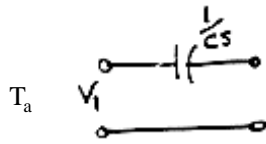


$$Z = \frac{1}{Cs}$$


$$T = T_a T_b T_c T_d$$

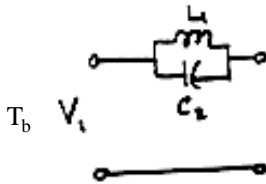

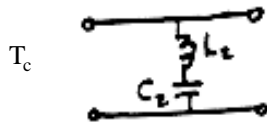
$$Z = \frac{L_1 s}{L_1 C_2 s^2 + 1} \quad \text{resonant frequency 5kHz}$$



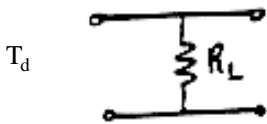
$$Y(s) = \frac{C_2 s}{L_2 C_2 s^2 + 1} \quad \text{resonant frequency 10kHz}$$




$$Y(s) = \frac{1}{R_L}$$

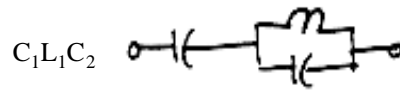

essentially a short circuit at 7.5kHz

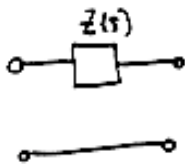
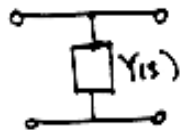
$$T = \begin{bmatrix} 1 & Z(s) \\ 0 & 1 \end{bmatrix}$$



$$T = \begin{bmatrix} 1 & 0 \\ Y(s) & 1 \end{bmatrix}$$