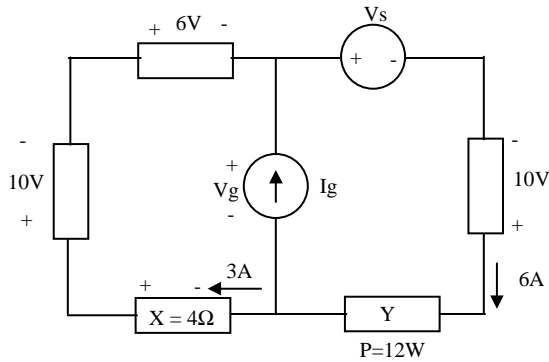


FINAL EXAM

Part I: Select the BEST answer. (4 points each). Circle only one answer. There is no partial credit.

Questions 1 to 6 refer to the following circuit:




- (a) The number of nodes in the circuit is:
 - (a) 4 nodes
 - (b) 5 nodes
 - (c) 7 nodes
 - (d) 6 nodes
 - (e) 8 nodes
 - (f) None of the above
2. The voltage in passive element X is:
 - (a) 0.75 V
 - (b) -12 V
 - (c) 7.5 V
 - (d) 12 V
 - (e) None of the above
3. The voltage V_g is:
 - (a) 28 V
 - (b) 16 V
 - (c) 4 V
 - (d) -4 V
 - (e) -28 V
 - (f) None of the above
4. The power in element X is:
 - (a) 576 W
 - (b) -36 W
 - (c) 36 W
 - (d) -576 W
 - (e) None of the above
5. The value of V_s is:
 - (a) -16 V
 - (b) -20 V
 - (c) 20 V
 - (d) 4 V
 - (e) 40 V
 - (f) None of the above

Initials _____
Last 4 digits ID _____
December 13, 2005

INEL 3105 Section 060
Electrical Systems Analysis I
Prof. Nayda G. Santiago


6. The power in element Vs is:
- (a) 24 W
 - (b) 120 W
 - (c) -120 W
 - (d) -96 W
 - (e) 240 W
 - (f) None of the above

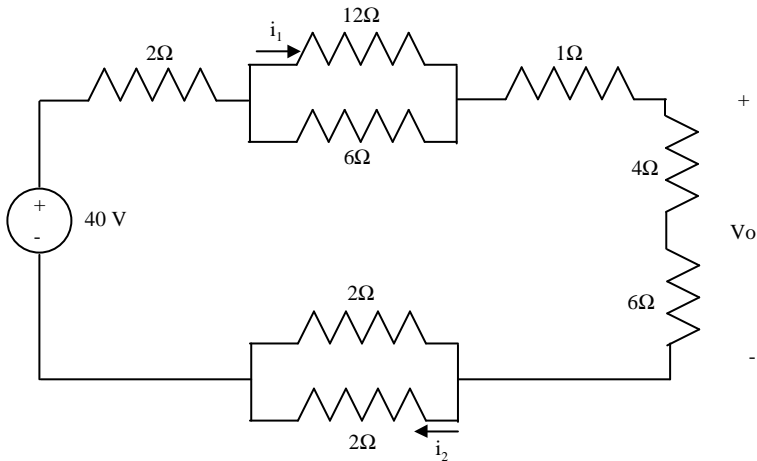Questions 7 to 9 refer to the following circuit:




7. The voltage V_o is:
- (a) 88.8 V
 - (b) 13.33 V
 - (c) 11.43 V
 - (d) 22.2 V
 - (e) 15.35 V
 - (f) None of the above
8. The current i_1 is:
- (a) 2.22 A
 - (b) 3.33 A
 - (c) 0.74 A
 - (d) 1.48 A
 - (e) 6.67 A
 - (f) None of the above
9. The current i_2 is:
- (a) 1.11 A
 - (b) 2.22 A
 - (c) 0.74 A
 - (d) 0.56 A
 - (e) 4.44 A
 - (f) None of the above

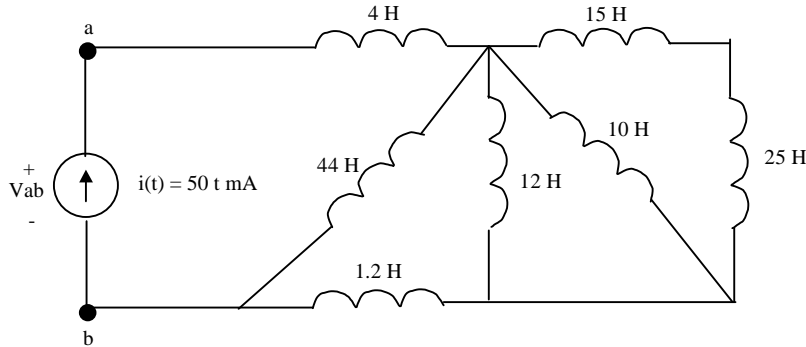Questions 10 to 12 refer to the following circuit:



10. The equivalent inductance seen from terminals a and b is:
- (a) 9.28 H
 - (b) 3.67 H
 - (c) 9.28 Ω
 - (d) 3.67 Ω
 - (e) None of the above
11. The power supplied or dissipated by the current source at $t = 2$ seconds is:
- (a) 3.75 mW
 - (b) -3.75 mW
 - (c) -1.97 mW
 - (d) 46.4 mW
 - (e) -46.4 mW
 - (f) None of the above

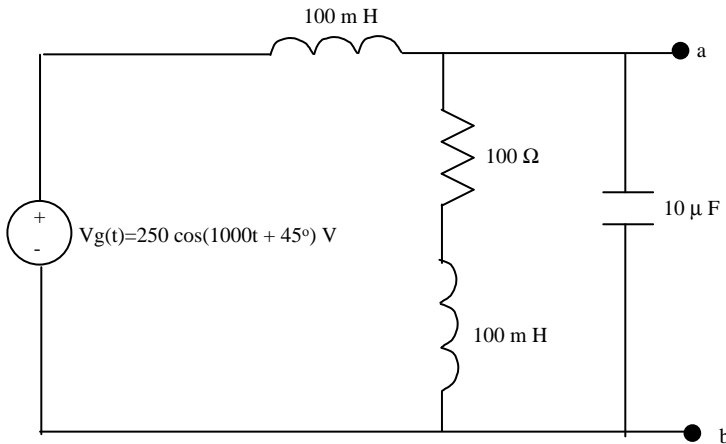Questions 13 to 17 refer to the following circuit:








12. The voltage source phasor representation is:
- (a) 250 $\angle -45^\circ$
 - (b) 250 $\angle 135^\circ$
 - (c) 250 $\angle 45^\circ$
 - (d) 250 $\angle 1000^\circ$
 - (e) None of the above
13. The impedance of the capacitor is:
- (a) $j100 \Omega$
 - (b) $-j100 \Omega$
 - (c) $j 0.01 \Omega$
 - (d) $-j 0.01 \Omega$
 - (e) None of the above

14. The impedances of the inductors are:

- (a) $j100 \Omega$
- (b) $-j100 \Omega$
- (c) $j 0.01 \Omega$
- (d) $-j 0.01 \Omega$
- (e) None of the above

15. The Thevenin equivalent circuit is:

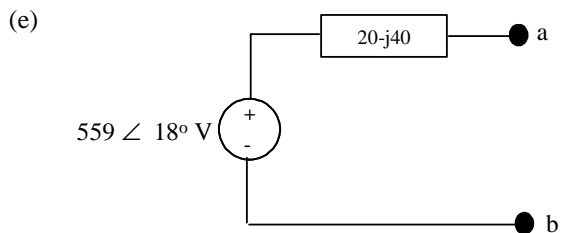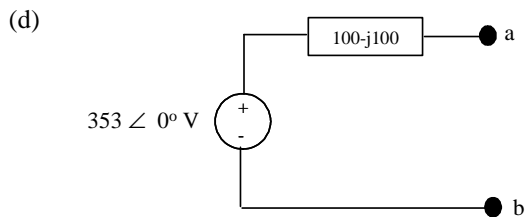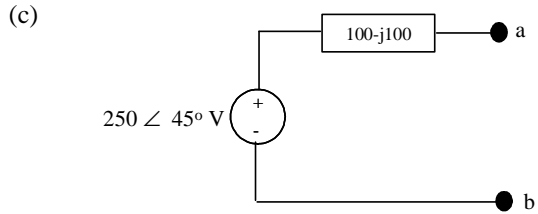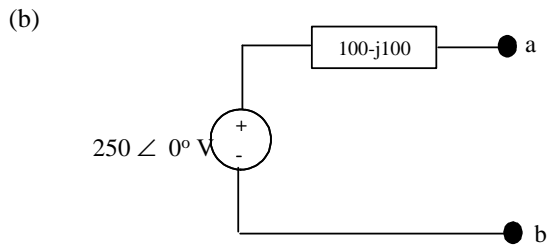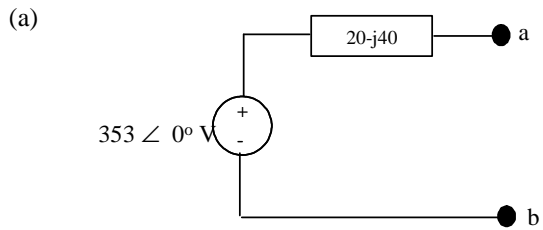

(f) None of the above


Initials _____
Last 4 digits ID _____
December 13, 2005

INEL 3105 Section 060
Electrical Systems Analysis I
Prof. Nayda G. Santiago

Part II

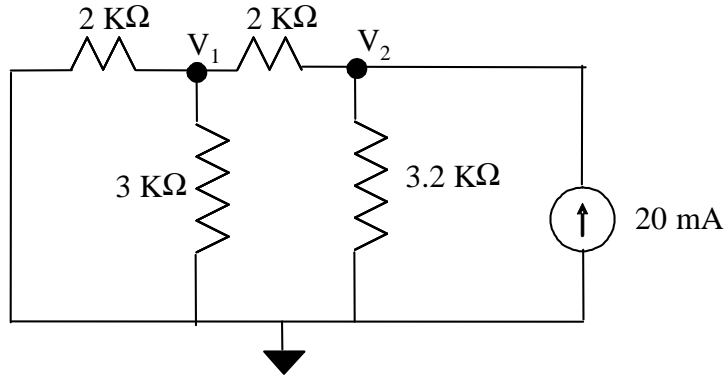Problem 1 (20 points)

Use the **node-voltage method** to find V_1 , and V_2 in the following circuit:



Problem 2 (20 points)

Use the concept of source transformation to find the phasor voltage V_0 for the following circuit.

