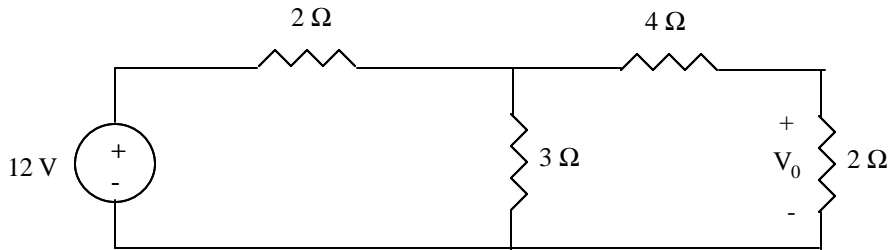



Question 1 (10 points):

Find  $V_0$  in the following circuit:




Solution:

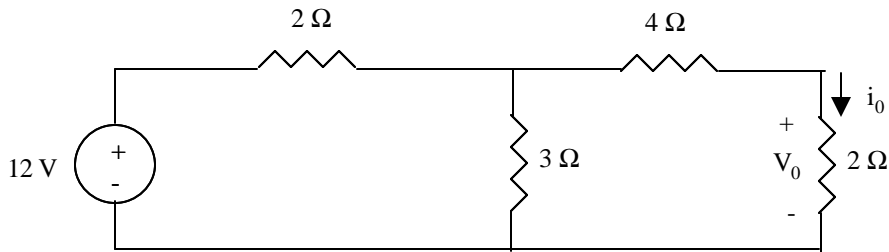
We can define  $i_0$  in the direction marked in the diagram



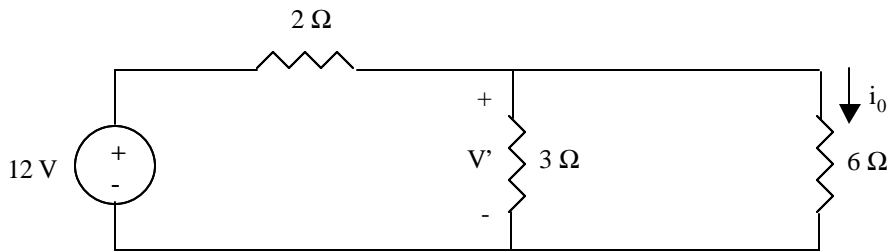By Ohm's Law:  $V_0 = i_0(2\Omega)$ . Now 4 ohms and 2 ohms are in series so its equivalent is 6 ohms. The current  $i_0$  is still there.



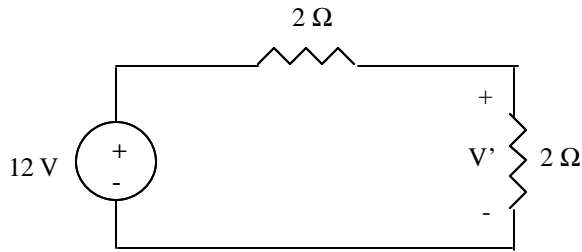Now 3 ohms are in parallel with 6 ohms. So  $R'_{eq} = \frac{(3)(6)}{3+6} = \frac{18}{9} = 2\Omega$ . So the circuit becomes:



If we define a  $V'$  at the 2 ohms resistor, notice that it is the same  $V'$  as in the previous circuit (parallel elements). Computing  $V'$ :  $V' = \frac{2}{2+2}(12) = 6V$

In the previous diagram  $i_0 = \frac{6V}{6\Omega} = 1A$ . Going back to the first diagram:  $V_0 = (1A)(2\Omega) = 2V$

RESULT:  $V_0=2V$ .