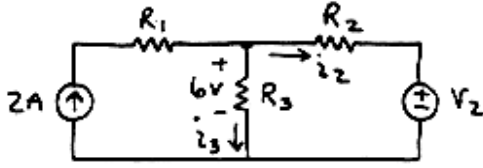


Chapter 3 – Resistive Circuits

Exercises

Ex 3.3-1



$$i_3 = \frac{6V}{R_3} = \frac{6V}{2\Omega} = 3A$$

from KCL at top node


$$i_2 = 2 - i_3 = 2 - 3 = -1A$$

KVL around 2nd loop : $-6 + R_2 i_2 + v_2 = 0 \Rightarrow v_2 = 6 - (1)(-1) = 7V$

Ex 3.3-2 $-18 + 0 - 12 - v_a = 0 \Rightarrow v_a = -30V$

Ex 3.3-3 $-v_a - 10 + 4v_a - 8 = 0 \Rightarrow v_a = \frac{18}{3} = 6V$

Ex 3.4-1

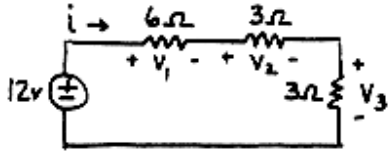


from voltage divider

$$v_3 = 12 \left(\frac{3}{3+9} \right) = 3V \therefore i = \frac{v_3}{3} = 1A$$

$$\left. \begin{aligned} \text{now } P_{6\Omega} &= i^2(6) = (1)^2(6) = 6W \\ P_{3\Omega_1} &= i^2(3) = (1)^2(3) = 3W \\ P_{3\Omega_2} &= i^2(3) = (1)^2(3) = 3W \end{aligned} \right\} P_{6\Omega} + P_{3\Omega_1} + P_{3\Omega_2} = 12W \text{ absorbed}$$

$$P_{\text{source}} = v_i = (12V)(1A) = 12W \text{ supplied}$$

Ex 3.4-2

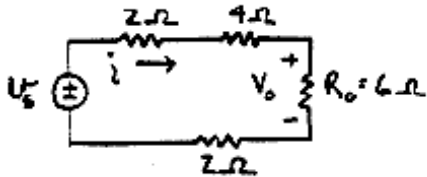

if $P_0 = 6W$ and $R_0 = 6\Omega \Rightarrow i^2 = \frac{P_0}{R_0} = \frac{6}{6} = 1$ or $i = 1A$

$\therefore v_0 = iR_0 = (1)(6) = 6V$


from KVL: $-v_s + i(2+4+6+2) = 0 \Rightarrow v_s = 14i = 14V$

Ex 3.4-3 from voltage divider $\Rightarrow v_m = \frac{25}{25+75} 8 = 2V$

Ex 3.4-4 from voltage divider $\Rightarrow v_m = \frac{25}{25+75} (-8) = -2V$

Ex. 3.5-1

Equiv. Ckt.

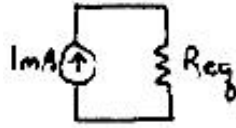

$$\frac{1}{R_{eq}} = \frac{1}{1} + \frac{1}{1} + \frac{1}{1} + \frac{1}{1}$$

$$R_{eq} = \underline{1/4 \text{ k}\Omega}$$

$$i \text{ in each } R = \frac{1}{4}(1\text{mA}) = \underline{\frac{1}{4}\text{mA}}$$

Ex 3.5-2 from current divider $\Rightarrow i_m = \frac{10}{10+40}(-5) = -2 \text{ A}$

Ex 3.6-1 $R_p = \frac{(4)(2)}{4+2} = \frac{8}{6} = \underline{\frac{4}{3}\Omega}$

$\therefore V = R_p (3\text{A}) = \frac{4}{3}(3) = \underline{4\text{V}}$

ProblemsSection 3-3 Kirchoff's Laws

P3.3-1 KVL: $v_1 + 2 - 3 - 6 - 8 + 4 = 0$ (outside loop)

$$\underline{v_1 = +11 \text{ V}}$$

KVL: $v_2 + 2 - 3 - 6 = 0$ (right mesh)

$$\underline{v_2 = 7 \text{ V}}$$

KVL: $3 + 2 - i_3 = 0$ (top node)

$$\underline{i_3 = 5 \text{ A}}$$

P3.3-2 KVL: $-v_1 + 2 + 4 + 5 = 0$ (outside loop)

$$\underline{v_1 = 11 \text{ V}}$$

KCL: $-1 + 3 + i_4 = 0$ (top, left node)

$$\underline{i_4 = -2 \text{ A}}$$

KCL: $1 + i_3 - 3 = 0$ (bottom, left node)

$$\underline{i_3 = 2 \text{ A}}$$

KCL: $-i_4 + 2 + i_2 = 0$ (top, right node)

$$-(-2) + 2 + i_2 = 0 \Rightarrow \underline{i_2 = -4 \text{ A}}$$

P3.3-3

KVL : $-12 - R_2(3) + v = 0$ (outside loop)

$$v = 12 + 3R_2 \text{ or } R_2 = \frac{v-12}{3}$$

KCL $i + \frac{12}{R_1} - 3 = 0$ (top node)

$$i = 3 - \frac{12}{R_1} \text{ or } R_1 = \frac{12}{3-i}$$

$$v = 12 + 3(3) = \underline{21 \text{ V}}$$

(a) $i = 3 - \frac{12}{6} = \underline{1 \text{ A}}$

(b) $R_2 = \frac{2-12}{3} = -\frac{10}{3} \Omega$; $R_1 = \frac{12}{3-1.5} = \underline{8 \Omega}$

(c) $24 = -12 i$, because 12 and i adhere to the passive convention.


$$\therefore \underline{i = -2 \text{ A}} \text{ and } R_1 = \frac{12}{3+2} = \underline{2.4 \Omega}$$

$9 = 3v$, because 3 and v do not adhere to the passive convention

$$\therefore \underline{v = 3} \text{ and } R_2 = \frac{3-12}{3} = \underline{-3 \Omega}$$

The situations described in (b) and (c) cannot occur if R_1 and R_2 are required to be nonnegative.

P3.3-4

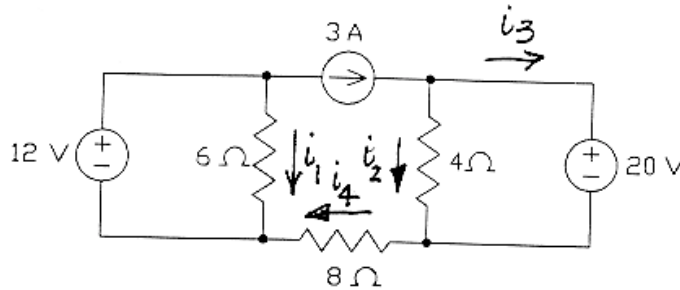

$$i_1 = \frac{12}{6} = 2 \text{ A}$$

$$i_2 = \frac{20}{4} = 5 \text{ A}$$

$$i_3 = 3 - i_2 = -2 \text{ A}$$


$$i_4 = i_2 + i_3 = 3 \text{ A}$$

Power absorbed by the 4Ω resistor = $4 \cdot i_2^2 = \underline{100 \text{ W}}$

Power absorbed by the 6Ω resistor = $6 \cdot i_1^2 = \underline{24 \text{ W}}$

Power absorbed by the 8Ω resistor = $8 \cdot i_4^2 = \underline{72 \text{ W}}$

P3.3-5

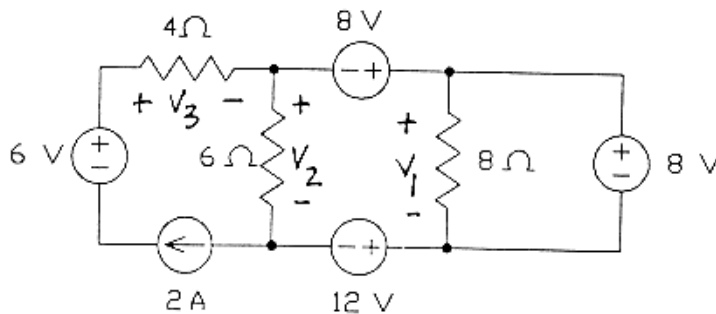

$$v_1 = 8 \text{ V}$$

$$v_2 = -8 + 8 + 12 = 12 \text{ V}$$


$$v_3 = 2 \cdot 4 = 8 \text{ V}$$

$$4 \Omega : P = \frac{v_3^2}{4} = \underline{16 \text{ W}}$$

$$6 \Omega : P = \frac{v_2^2}{6} = \underline{24 \text{ W}}$$

$$8 \Omega : P = \frac{v_1^2}{8} = \underline{8 \text{ W}}$$

P3.3-9

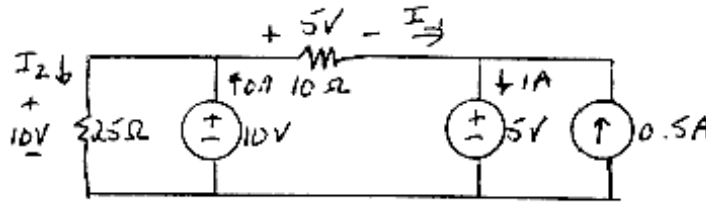

$$I_1 = \frac{5V}{10\Omega} = 0.5 \text{ A}$$

$$I_2 = \frac{10V}{25\Omega} = 0.4 \text{ A}$$

$$P_{10V} = (-10)(0.9) = -9W_{\text{absorbed}} = 9W_{\text{delivered}}$$

$$P_{5V} = (5)(1) = 5W_{\text{absorbed}}$$


$$P_{0.5A} = (-5)(0.5) = -2.5W_{\text{absorbed}} = 2.5W_{\text{delivered}}$$

$$P_{10\Omega} = (5)(0.5) = 2.5W_{\text{absorbed}}$$

$$P_{25\Omega} = (10)(0.4) = 4W_{\text{absorbed}}$$

$$\Sigma P_{\text{absorbed}} = 0W \quad \text{energy balance}$$

P3.3-10

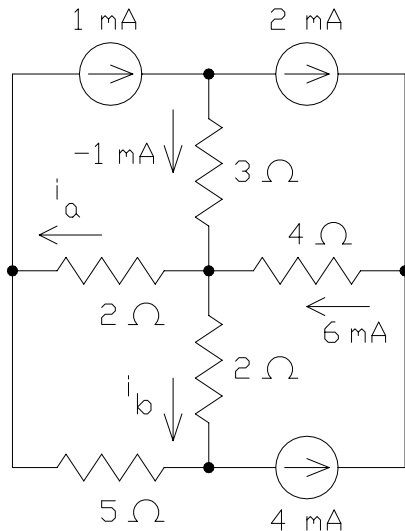

$$i_a + i_b = 6 - 1 = 5 \text{ mA} = 0.005 \text{ A}$$

$$-2i_a + 2i_b - 5(i_a - 0.001) = 0$$

Solving yields:

$$i_a = 0.00167 = 1.67 \text{ mA}$$

$$i_b = 0.005 - i_a = 0.00333 = 3.33 \text{ mA}$$

Section 3-4 A Single-Loop Circuit – The Voltage Divider

P3.4-1 $V_1 = \frac{6}{6+3+5+4} 12 = \frac{6}{18} 12 = 4 \text{ V}$

$$V_2 = \frac{3}{18} 12 = 2 \text{ V}; \quad V_3 = \frac{5}{18} 12 = \frac{10}{3} \text{ V}$$

$$V_4 = \frac{4}{18} 12 = \frac{8}{3} \text{ V}$$

P3.4-2

(a) $R = 6 + 3 + 2 + 4 = 15\Omega$

(b) $i = \frac{28}{R} = \frac{28}{15} = 1.867 \text{ A}$

(c) $P = 28 \cdot i \quad (28 \text{ and } i \text{ do not adhere to the passive convention.})$
 $= 28(1.867) = 52.27 \text{ W}$