


Capitulo 9.8 : Matching Techniques for Antenas – quarter-wave Xmer

A 0.47λ folded dipole operating at 100MHz with a $\Delta f/f_o = 0.25$ an input impedance of $306 + j75.3$ ohms is to be fed with a 75-ohm line using a 3-section $\lambda/4$ wave binomial transformer.

Find s_o , ρ_m , $VSWR_{\max}$ over the bandwidth and the Z_n 's.

Solution:

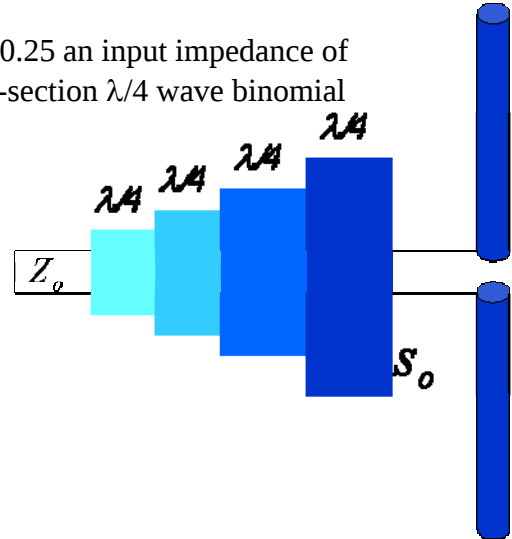Using the Smith Chart find the distance to the closest real input impedance. De-normalize it. This yields $R_L = 330 \Omega$



$$\rho_n = 2^{-N} \left(\frac{R_L - Z_o}{R_L + Z_o} \right) C_n^N$$

$$\rho_0 = 2^{-3} \left(\frac{330 - 75}{330 + 75} \right) \frac{3!}{3!0!} = 0.0787037 = \frac{Z_1 - 75}{Z_1 + 75} \quad Z_1 = 87.75 \Omega$$

$$\rho_1 = 2^{-3} \left(\frac{330 - 75}{330 + 75} \right) \frac{3!}{2!1!} = 0.234211111 = \frac{Z_2 - 87.75}{Z_2 + 87.75} \quad Z_2 = 141.42 \Omega$$

$$\rho_0 = 2^{-3} \left(\frac{330 - 75}{330 + 75} \right) \frac{3!}{2!1!} = 0.234211111 = \frac{Z_1 - 141.42}{Z_1 + 141.42} \quad Z_1 = 227.92 \Omega$$

$$\frac{\Delta f}{f_o} = \frac{2(f_o - f_m)}{f_o} = 2 - \frac{4}{\pi} \cos^{-1} \left[\frac{\rho_m (R_L + Z_o)}{(R_L - Z_o)} \right]^{1/N}$$

$$0.45 = 2 - \frac{4}{\pi} \cos^{-1} \left[\frac{\rho_m (405)}{(255)} \right]^{1/3}$$

or

$$\rho_m = \frac{255}{405} \cos^3 \left[\left(0.45 - 2 \right) \left(-\frac{\pi}{4} \right) \right] = 0.00472$$

and

$$VSWR_{\max} = \frac{1 + \rho_m}{1 - \rho_m} = 1.009$$

To plot the magnitude of the reflection coefficient versus frequency, use:

$$|\Gamma_{in}| = \rho_{in} = \left| \frac{R_L - Z_o}{R_L + Z_o} \right| \cos^N \theta = \left| \frac{R_L - Z_o}{R_L + Z_o} \right| \cos^3 \left[\frac{\pi}{2} \left(\frac{f}{f_o} \right) \right]$$