



# Transmission Lines

Dr. Sandra Cruz-Pol  
ECE Dept. UPRM



## Intro to Transmission Lines (T.L.)

- Hi-frequency or Hi-power requires T.L.
- TEM waves propagate thru T.L.
- We will develop T.L. theory to see how waves propagate thru them



Seem to be in parallel, but these V are not equal!


■ A 40-m long TL has  $V_g = 15 V_{rms}$ ,  $Z_o = 30 + j60 \Omega$ , and  $V_L = 5e^{j48^\circ} V_{rms}$ . If the input impedance is  $Z_L$  and the propagation constant is  $\gamma$ .

Don't worry about the details, I'll teach you about solving this type of problems pretty soon.

Answers:


$$Z_{in} = 30 + j60 \Omega, \quad I_{in} = 0.112 \angle -63.4^\circ A,$$

$$V_{in} = 7.5 \angle 0^\circ V_{rms}, \quad \gamma = 0.0101 + j0.02094 m^{-1}$$

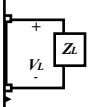
$$7.45 \angle -111^\circ e^{-\gamma 40} = 0.112 \angle -63^\circ$$


## Transmission Lines

- I. TL parameters ( $R', L', C', G'$ )
- II. TL Equations (for  $V$  and  $I$ )
- III. 3 Concepts:
  - I. Input Impedance,
  - II. Reflection Coefficient and
  - III. Characteristic Impedance
- IV. SWR, Power
- V. Smith Chart




## Transmission Lines (TL)

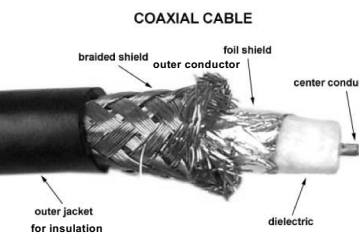

Have 2 conductors in parallel with a dielectric separating them

They transmit TEM waves inside the lines

## Common Transmission Lines

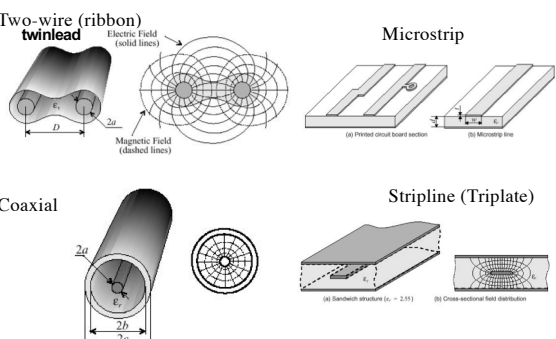

Two-wire (ribbon twinlead): Electric Field (solid lines), Magnetic Field (dashed lines)

Microstrip: (a) Printed circuit board section, (b) Microstrip line

Coaxial: (a) Sandwich structure ( $\epsilon_r = 2.5$ ), (b) Cross-sectional field distribution

Stripline (Triplate): (a) Sandwich structure ( $\epsilon_r = 2.5$ ), (b) Cross-sectional field distribution

### Other TL (higher order) [Chapter 12]

(f) Rectangular waveguide      (g) Optical fiber      (h) Coplanar waveguide

Higher Order Transmission Lines

Figure 2-4: A few examples of transverse electromagnetic (TEM) and higher-order transmission lines.

### Fields inside the TL

$$V = -\int E \cdot dl$$

- $V$  proportional to  $E$ ,
- $I$  proportional to  $H$

$$I = \oint H \cdot dl$$

Figure 2-5: In a coaxial line, the electric field lines are in the radial direction between the inner and outer conductors, and the magnetic field forms circles around the inner conductor.

### Distributed parameters

The parameters that characterize the TL are given in terms of per length.

- $R =$  ohms/meter
- $L =$  Henries/m
- $C =$  Farads/m
- $G =$  mhos/m

At high frequencies we're dealing with wavelengths comparable to the size of the circuits.

$\lambda_{60\text{Hz}} = c / 60 = 5,000\text{km}$

$\lambda_{2\text{GHz}} = c / 2,000,000,000 = 15\text{cm}$

### Common Transmission Lines

$R', L', G',$  and  $C'$  depend on the particular transmission line structure and the material properties.  $R, L, G,$  and  $C$  can be calculated using fundamental EMAG techniques.

Parameter	Two-Wire Line	Coaxial Line	Parallel-Plate Line	Unit
$R'$	$\frac{1}{\pi a \sigma_{\text{cond}} \delta}$	$\frac{1}{2\pi \sigma_{\text{cond}} \delta} \left( \frac{1}{a} + \frac{1}{b} \right)$		
$L'$	$\frac{\mu}{\pi} a \cosh\left(\frac{D}{2a}\right)$	$\frac{\mu}{2\pi} \ln\left(\frac{b}{a}\right)$		
$G'$	$\frac{\pi \sigma_{\text{insul}}}{a \cosh(D/(2a))}$	$\frac{2\pi \sigma_{\text{insul}}}{\ln(b/a)}$		
$C'$	$\frac{\pi \epsilon}{a \cosh(D/(2a))}$	$\frac{2\pi \epsilon}{\ln(b/a)}$	$\epsilon \frac{w}{d}$	$F/m$

### TL representation

(a) Parallel-wire representation

(b) Differential sections each  $\Delta z$  long

(c) Each section is represented by an equivalent circuit

Figure 2-6: Regardless of its actual shape, a TEM transmission line is represented by the parallel-wire configuration shown in (a). To analyze the voltage and current relations, the line is subdivided into small differential sections (b), each of which is then represented by an equivalent circuit (c).

### Distributed line parameters

Using KVL:

$$\frac{V(z + \Delta z, t) - V(z, t)}{\Delta z} = R I(z, t) + L \frac{\partial I(z, t)}{\partial t}$$

### Distributed parameters

- Taking the limit as  $\Delta z$  tends to 0 leads to

$$-\frac{\partial V}{\partial z} = RI + L \frac{\partial I}{\partial t}$$

- Similarly, applying KCL to the main node gives

$$-\frac{\partial I}{\partial z} = GV + C \frac{\partial V}{\partial t}$$

### Wave equation

- Using phasors
 
$$V(z,t) = \text{Re}[V_s(z)e^{j\omega t}]$$

$$I(z,t) = \text{Re}[I_s(z)e^{j\omega t}]$$
- The two expressions reduce to

$$\frac{\partial^2 V_s}{\partial z^2} - \gamma^2 V_s = 0$$


$$\frac{\partial^2 I_s}{\partial z^2} - \gamma^2 I_s = 0$$

$$\gamma^2 = (R + j\omega L)(G + j\omega C)$$

Wave Equation for voltage

### Transmission Lines

- I. TL parameters ( $R', L', C', G'$ )
- II. TL Equations (for  $V$  and  $I$ )
- III. 3 Concepts:
  - I. Input Impedance,
  - II. Reflection Coefficient and
  - III. Characteristic Impedance
- IV. SWR, Power
- V. Smith Chart



### TL Equations

- Note that these are the wave eq. for voltage and current inside the lines.

$$\frac{d^2 V_s}{dz^2} - \gamma^2 V_s = 0 \quad \frac{d^2 I_s}{dz^2} - \gamma^2 I_s = 0$$

- The propagation constant is  $\gamma$  and the wavelength and velocity are

$$\gamma = \alpha + \beta j = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\lambda = 2\pi/\beta \quad u = \omega/\beta = f\lambda$$


### Waves move through line

- The general solution is

$$V_s = V^+ e^{-\gamma z} + V^- e^{\gamma z}$$

- In time domain is

$$V(z,t) = \text{Re}[V_s(z)e^{j\omega t}]$$

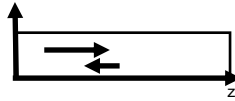
$$= V^+ e^{-\alpha z} \cos(\omega t - \beta z) + V^- e^{+\alpha z} \cos(\omega t + \beta z)$$


### Waves move through line

- For Current


$$I_s = I^+ e^{-\gamma z} + I^- e^{\gamma z}$$

- Similarly for time-domain,  $I$
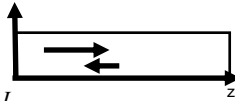
$$I(z,t) = I^+ e^{-\alpha z} \cos(\omega t - \beta z) + I^- e^{+\alpha z} \cos(\omega t + \beta z)$$


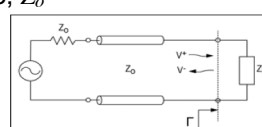
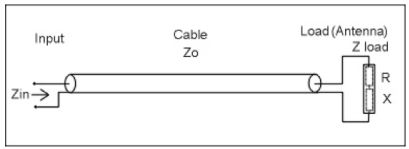
## Transmission Lines

- I. TL parameters ( $R', L', C', G'$ )
- II. TL Equations (for  $V$  and  $I$ )
- III. 3 Concepts:
  - I. Input Impedance,
  - II. Reflection Coefficient and
  - III. Characteristic Impedance
- IV. SWR, Power
- V. Smith Chart





## We will define 3 concepts:

- Characteristic impedance,  $Z_o$
- Reflection Coefficient,  $\Gamma_L$
- Input Impedance,  $Z_{in}$

## We will define 3 concepts:

- Characteristic impedance,  $Z_o$
- Reflection Coefficient,  $\Gamma_L$
- Input Impedance,  $Z_{in}$

## Characteristic Impedance of a Line, $Z_o$

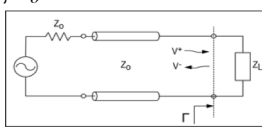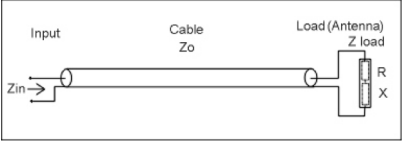- Is the ratio of positively traveling voltage wave to current wave at any point on the line



$$-\frac{dV(z)}{dz} = (R + j\omega L)I(z)$$

*substituting*

$$V(z) = V^+ e^{-\gamma z}$$

$$I(z) = I^+ e^{-\gamma z}$$

$$-(-\gamma V^+ e^{-\gamma z}) = (R + j\omega L)I^+ e^{-\gamma z}$$
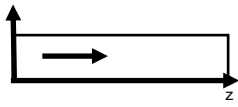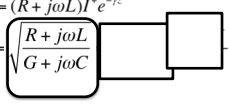
$$Z_o = \frac{V^+}{I^+} = \frac{R + j\omega L}{\gamma} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$



## Characteristic Impedance, $Z_o$




$$Z_o = \frac{V^+}{I^+} = -\frac{V^-}{I^-} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$I_s = I^+ e^{-\gamma z} + I^- e^{\gamma z}$$

$$I_s = \frac{V^+}{Z_o} e^{-\gamma z} + \frac{V^-}{-Z_o} e^{\gamma z}$$

## Different cases of TL

Find the characteristic impedance and propagation constant for each:

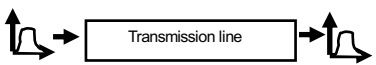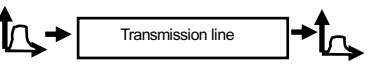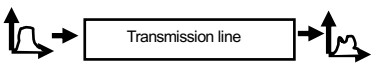- Lossless 
- Distortionless 
- Lossy 

### Lossless Lines ( $R=0=G$ )

Have perfect conductors and a perfect dielectric medium between them.

- Propagation:  $\alpha = 0, \gamma = j\beta, \beta = \omega\sqrt{LC}$
- Wavelength & Velocity:  $u = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}} = f\lambda, \lambda = \frac{2\pi}{\beta}$
- Impedance:  $Z_o = R_o = \sqrt{\frac{L}{C}}, X_o = 0$

### Distortionless line ( $R/L = G/C$ )

Is one in which the attenuation is independent on frequency.


$\gamma = \alpha + j\beta$

- Propagation:  $\alpha = \sqrt{RG}, \beta = \omega\sqrt{LC}$
- Velocity:  $u = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}} = f\lambda$
- Impedance:  $X_o = 0, Z_o = R_o = \sqrt{\frac{L}{C}} = \sqrt{\frac{R}{G}}$

### Summary

	$\gamma = \alpha + j\beta$ <i>Propagation Constant</i>	$Z_o$ <i>Characteristic Impedance</i>
<b>General (Lossy)</b>	$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$	$Z_o = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$
Lossless	$\gamma = 0 + j\omega\sqrt{LC}$	$Z_o = R_o = \sqrt{\frac{L}{C}}$
Distortionless $RC = GL$	$\gamma = \sqrt{RG} + j\omega\sqrt{LC}$	$Z_o = R_o = \sqrt{\frac{L}{C}} = \sqrt{\frac{R}{G}}$

### P.E. 11.2



A telephone line has  $R=30 \Omega/\text{km}, L=100 \text{ mH}/\text{km}, G=0,$  and  $C= 20\mu\text{F}/\text{km}.$  At 1kHz, FIND: the characteristic impedance of the line, the propagation constant, the phase velocity.

- Is it distortionless? **No**


Solution:

$$Z_o = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \boxed{\phantom{000000}} \boxed{\phantom{000000}}$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

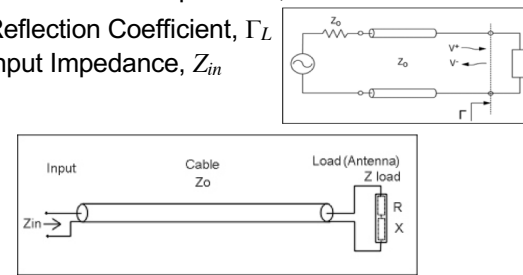
### We will define 3 concepts:

- Characteristic impedance,  $Z_o$
- Reflection Coefficient,  $\Gamma_L$
- Input Impedance,  $Z_{in}$


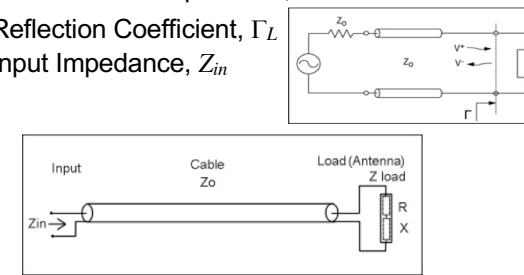
### We will define 3 concepts:

- Characteristic impedance,  $Z_o$
- Reflection Coefficient,  $\Gamma_L$
- Input Impedance,  $Z_{in}$



### Reflection coefficient at the load, $\Gamma_L$

Load is usually taken at  $z=0$  and generator at  $z=-l$

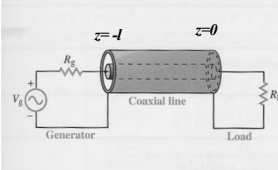


Figure 2-5: In a coaxial line, the electric field lines are in the outer conductors, and the magnetic field forms circles around

$$V_s(z) = V^+ e^{-\gamma z} + V^- e^{+\gamma z}$$

$$\Gamma_L = \frac{V^-}{V^+}$$

$$V_s(z) = V^+ (e^{-\gamma z} + \Gamma_L e^{+\gamma z})$$

### For a Lossless TL terminated with a load

Then,  $V_s(z) = V^+ (e^{-\gamma z} + \Gamma_L e^{+\gamma z})$

Similarly,  $I_s(z) = \frac{V^+}{Z_o} (e^{-\gamma z} - \Gamma_L e^{+\gamma z})$

The impedance **anywhere** along the line is given by

$$Z(z) = \frac{V_s(z)}{I_s(z)} = Z_o \frac{(e^{-\gamma z} + \Gamma_L e^{+\gamma z})}{(e^{-\gamma z} - \Gamma_L e^{+\gamma z})}$$

The impedance at the load end,  $Z_L$ , is given by

$$Z(l=0) = Z_L = Z_o \frac{(1 + \Gamma_L)}{(1 - \Gamma_L)}$$

### Terminated, Lossless TL

Solving for  $\Gamma_L$

$$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o}$$

**Conclusion:** The reflection coefficient is a function of the load impedance and the characteristic impedance.

Recall for the lossless case,  $\gamma = 0 + j\beta = j\omega\sqrt{LC}$

Then

$$V_s(z) = V^+ (e^{-j\beta z} + \Gamma_L e^{+j\beta z})$$

$$I_s(z) = \frac{V^+}{Z_o} (e^{-j\beta z} - \Gamma_L e^{+j\beta z})$$

### Definition: Matched line

- Means that  $Z_o = Z_L$
- Therefore there are no reflection!


$$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o} = 0$$

### What happens when you connect the wrong TL to a speaker?


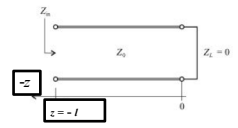
### Terminated, Lossless TL

Using convention the coordinate system,  $z = -l$ , at input.



Rewriting the expressions for voltage and current, we have

$$V(-l) = V^+ (e^{j\beta l} + \Gamma_L e^{-j\beta l})$$

$$I(-l) = \frac{V^+}{Z_o} (e^{j\beta l} - \Gamma_L e^{-j\beta l})$$

Rearranging,

$$V(-l) = V^+ e^{+j\beta l} (1 + \Gamma_L e^{-2j\beta l})$$

$$I(-l) = \frac{V^+}{Z_o} e^{+j\beta l} (1 - \Gamma_L e^{-2j\beta l})$$

### Voltage anywhere on the Line

Recall,

$$V(l) = V^+ (e^{j\beta l} + \Gamma_L e^{-j\beta l})$$

$V_m = V(-l)$       Input voltage = sending end,  
 $V_L = V(0)$       Load Voltage = receiving end  
 $V(l = \lambda/4) = V^+ (e^{j\pi/2} + (0)e^{-j\pi/2})$  Voltage quarterwave from matched load

### We will define 3 concepts:

- Characteristic impedance,  $Z_o$
- Reflection Coefficient,  $\Gamma_L$
- Input Impedance,  $Z_{in}$

### Impedance (Lossless line)

The impedance **anywhere** along the line is given by

$$Z(l) = \frac{V(l)}{I(l)} = Z_o \frac{(1 + \Gamma_L e^{-2j\beta l})}{(1 - \Gamma_L e^{-2j\beta l})}$$

The reflection coefficient at any point along the line:

$$\Gamma(l) = \Gamma_L e^{-2j\beta l} = |\Gamma_L| e^{j\theta_L} e^{-2j\beta l}$$

Then, the impedance can be written as.

$$Z(l) = Z_o \frac{(1 + \Gamma(l))}{(1 - \Gamma(l))}$$

After some algebra, an alternative expression for the impedance is given by

$$Z(l) = Z_{in} = Z_o \frac{(Z_L + jZ_o \tan \beta l)}{(Z_o + jZ_L \tan \beta l)}$$

**Conclusion:** The load impedance is “transformed” as we move away from the load.

### Impedance (Lossy line)

The impedance anywhere along the line is given by

$$Z(l) = \frac{V(l)}{I(l)} = Z_o \frac{(1 + \Gamma_L e^{-2\gamma l})}{(1 - \Gamma_L e^{-2\gamma l})}$$

The reflection coefficient can be modified as follows

$$\Gamma(l) = \Gamma_L e^{-2\gamma l} = \Gamma_L (e^{-\alpha l} e^{-2j\beta l})$$

Then, the impedance can be written as

$$Z(l) = Z_o \frac{(1 + \Gamma(l))}{(1 - \Gamma(l))}$$

After some algebra, an alternative expression for the impedance is given by

$$Z(l) = Z_{in} = Z_o \frac{(Z_L + Z_o \tanh \gamma l)}{(Z_o + Z_L \tanh \gamma l)}$$

**Conclusion:** in lossy lines, we end up with the hyperbolic tangent.

### Example: Matched Case

A TL has  $V_g = 10 \text{ V}_{\text{rms}}$ ,  $Z_o = 50 \Omega$ . If the line is matched to the load and the generator, find: the input impedance  $Z_{in}$ , the sending-end Voltage  $V_{in}$

$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o} = 0$   
 Answers:  $Z_L = Z_o \Rightarrow Z_{in} = 50 \Omega$   
 $Z_{in} = Z_o \frac{(Z_L + jZ_o \tan \beta l)}{(Z_o + jZ_L \tan \beta l)} = Z_o$   
 $\Gamma = 0$   
 Voltage Divider  $V_{in} = 5 \angle 0^\circ$

### Example: Matched Case

A  $\lambda/8$  long TL has  $V_L = 5 \angle 30^\circ$ ,  $Z_o = 50 \Omega$ . If the line is matched to the load, find: the input impedance  $Z_{in}$ , the sending-end Voltage  $V_{in}$ , the propagation constant  $\gamma$ .

Answers:  $Z_L = Z_o \Rightarrow Z_{in} = 50 \Omega$   
 $\Gamma = 0$   
 $V_L = 5 \angle 30^\circ = V|_{l=0} = V^+ (e^{j\beta 0} + (0)e^{-j\beta 0})$   
 Solve for:  $V^+ = 5 \angle 30^\circ$   
 $V(l = \lambda/8) = 5 \angle 30^\circ (e^{j\pi/4} + (0)e^{-j\pi/4})$   
 $V_m = 5 \angle 30^\circ (e^{j\pi/4}) = 5 \angle 75^\circ$

### Exercise 1: Not Matched

A 2cm lossless TL has  $V_L=10 e^{j30^\circ}$ ,  $Z_g=60 \Omega$ ,  $Z_L=50 \Omega$  and  $Z_o=100\Omega$ ,  $\lambda=10\text{cm}$ . Find: the input impedance  $Z_{in}$ , the sending-end Voltage  $V_{in}$ .

$$V(l) = V^+ (e^{j\beta l} + \Gamma_L e^{-j\beta l})$$

$$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o}$$

- Use this equation at load and at input, find  $V^+$
- Find  $V_{in}$
- Find  $Z_{in}$  (at input)

$$V^+ = 15 (e^{j30})$$

$$V_{in} = 39.9 \angle 94^\circ$$

$$Z_{in} = Z_o \frac{(Z_L + jZ_o \tan \beta l)}{(Z_o + jZ_L \tan \beta l)} = 155 + j68\Omega$$


### Exercise 2: using formulas

A 2cm lossless TL has  $V_g=10 \text{ V}_{rms}$ ,  $Z_g=60 \Omega$ ,  $Z_L=100+j80 \Omega$  and  $Z_o=40\Omega$ ,  $\lambda=10\text{cm}$ . find: the input impedance  $Z_{in}$ , the sending-end Voltage  $V_{in}$ .

$$Z_{in} = Z_o \frac{(100 + j80) + j40 \tan \frac{2\pi}{5}}{(40 + j(100 + j80) \tan \frac{2\pi}{5})}$$

$$Z_{in} = 12.2 - j21.17 \Omega$$

**Voltage Divider:**
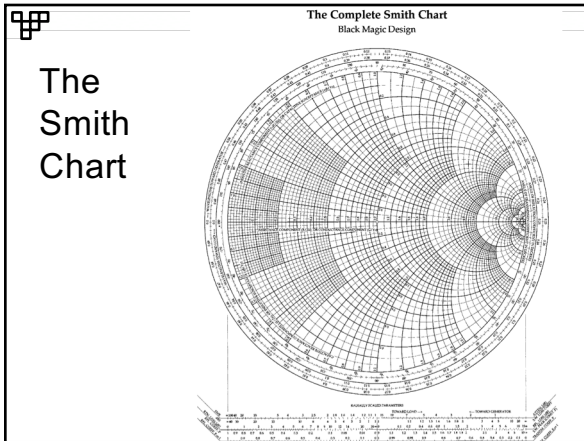
$$V_{in} = \frac{V_g Z_{in}}{Z_{in} + Z_g} = 3.30 \angle -0.766 \text{ rad}$$


### Example 3: Not matched to load

A generator with  $10V_{rms}$  and  $R_g=50$ , is connected to a  $75\Omega$  load thru a  $0.8\lambda$ ,  $50\Omega$ -lossless line.

- Find  $V_L$

$$Z_o = 50 \Omega \quad Z_L = 75, \quad l = .8\lambda$$

$$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o} = 0.2$$

$$Z_{in} = Z_o \frac{(Z_L + jZ_o \tan \beta l)}{(Z_o + jZ_L \tan \beta l)} \quad Z_{in} = 35 + j8.75 \Omega$$

$$V(l) = V^+ (e^{j\beta l} + \Gamma_L e^{-j\beta l})$$

**Power Divider**

$$V_{in} = \angle$$

$$V^+ = 5.006 \angle 1.26 \text{ rad}$$

$$V_L = V(l=0)$$

### Exercise 11.3: Matched Case

A 40-m long TL has  $V_g=15 \text{ V}_{rms}$ ,  $Z_o=30+j60 \Omega$ , and  $V_L=5e^{j48^\circ} \text{ V}_{rms}$ . If the line is matched to the load and the generator, find: the input impedance  $Z_{in}$ , the sending-end current  $I_{in}$  and Voltage  $V_{in}$ , the propagation constant  $\gamma$ .

- Answers:

$$Z_{in} = 30 + j60 \Omega, \quad I_{in} = 0.112 \angle -63.4^\circ \text{ A},$$

$$V_{in} = 7.5 \angle 0^\circ \text{ V}_{rms}, \quad \gamma = 0.0101 + j0.02094 \text{ m}^{-1}$$

$$7.45 \angle -111^\circ e^{-\gamma 40} = 0.112 \angle -63^\circ$$

### Transmission Lines

- I. TL parameters ( $R', L', C', G'$ )
- II. TL Equations (for  $V$  and  $I$ )
- III. 3 Concepts:
  - I. Input Impedance,
  - II. Reflection Coefficient and
  - III. Characteristic Impedance
- IV. SWR, Power
- V. Smith Chart



## Power

- The average input power at a distance  $l$  from the load is given by
 
$$P_{ave} = \frac{1}{2} \text{Re}[V(l)I^*(l)]$$
- which can be reduced to
 
$$P_{ave} = \frac{|V_o^+|^2}{2Z_o} (1 - |\Gamma|^2)$$
- The first term is the incident power and the second is the reflected power. Maximum power is delivered to load if  $\Gamma=0$

## SWR or VSWR or s

Whenever there is a reflected wave, a standing wave will form out of the combination of incident and reflected waves.

The (Voltage) Standing Wave Ratio - SWR (or VSWR) is defined as

$$s = SWR = \frac{|V_{max}|}{|V_{min}|} = \frac{|I_{max}|}{|I_{min}|}$$

$$s = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

The graph shows SWR on the y-axis (ranging from 0 to 20) and  $|\Gamma_L|$  on the x-axis (ranging from 0 to 1). The curve starts at (0, 1) and increases as  $|\Gamma_L|$  increases, reaching infinity as  $|\Gamma_L|$  approaches 1.

## Summary

- Input Impedance
 
$$Z_{in} = Z_o \frac{(Z_L + jZ_o \tan \beta l)}{(Z_o + jZ_L \tan \beta l)}$$
- Reflection Coef
 
$$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o}$$
- SWR
 
$$s = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

## Three (3) common Cases of line-load combinations:

- Shorted Line ( $Z_L=0$ )
 
$$Z_{in} = 0 + jZ_o \tan \beta l = jb \quad \Gamma_L = -1, \quad s = \infty$$
- Open-circuited Line ( $Z_L=\infty$ )
 
$$Z_{in} = -jZ_o \cot \beta l \quad \Gamma_L = 1, \quad s = \infty$$
- Matched Line ( $Z_L = Z_o$ )
 
$$Z_{in} = Z_o \quad \Gamma_L = 0, \quad s = 1$$

## Standing Waves –Short ( $Z_L=0$ )

$Z_{in} = jZ_o \tan \beta l, \quad \Gamma_L = -1, \quad s = \infty$

- So substituting in  $V(z)$ 

$$V(z) = V^+ [e^{j\beta l} + (-1)e^{-j\beta l}]$$

$$V(z) = V^+ (2j \sin \beta l)$$

$$|V(z)| = |V^+| |2 \sin(\beta l)|$$

$$|V(z)| = |V^+| \left| 2 \sin\left(\frac{2\pi}{\lambda} l\right) \right|$$

\*Voltage minima occurs at same place that impedance has a minimum on the line

## Standing Waves –Open ( $Z_L=\infty$ )

$Z_{in} = -jZ_o \cot \beta l, \quad \Gamma_L = +1, \quad s = \infty$

- So substituting in  $V(z)$ 

$$V(z) = V^+ [e^{j\beta l} + (+1)e^{-j\beta l}]$$

$$V(z) = V^+ (2 \cos \beta l)$$

$$|V(z)| = |V^+| |2 \cos(\beta l)|$$

$$|V(z)| = |V^+| \left| 2 \cos\left(\frac{2\pi}{\lambda} l\right) \right|$$

### Standing Waves –Matched ( $Z_L = Z_o$ )

$Z_{in} = Z_o, \Gamma_L = 0, s = 1$

- So substituting in  $V(z)$

$$V(z) = V^+ [e^{j\beta l} + (0)e^{-j\beta l}]$$

$$V(z) = V^+ e^{j\beta l}$$

$$|V(z)| = |V^+| e^{j\beta l}$$


$$|V(z)| = |V^+|$$

### Java applets

- <http://www.amanogawa.com/transmission.html>
- <http://physics.usask.ca/~hirose/ep225/>
- [http://www.educatorscorner.com/index.cgi?CONTENT\\_ID=2483](http://www.educatorscorner.com/index.cgi?CONTENT_ID=2483)

### Transmission Lines

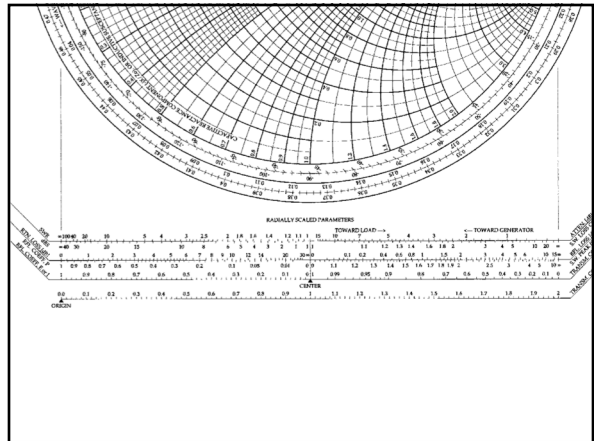- I. TL parameters ( $R', L', C', G'$ )
- II. TL Equations (for  $V$  and  $I$ )
- III. 3 Concepts:
  - I. Input Impedance,
  - II. Reflection Coefficient and
  - III. Characteristic Impedance
- IV. SWR, Power
- V. Smith Chart



### Smith Chart

- Commonly used as graphical representation of a TL.
- Used in hi-tech equipment for design and testing of microwave circuits
- 1 turn ( $360^\circ$ ) around the SC = to  $\lambda/2$

### Network Analyzer

### Smith Chart

$$z(l) = Z_o \frac{(1+\Gamma(l))}{(1-\Gamma(l))} \quad Z_L = Z_o \frac{(1+\Gamma_L)}{(1-\Gamma_L)}$$

- Use the reflection coefficient real and imaginary parts .

$$\Gamma = |\Gamma| \angle \theta_\Gamma = \Gamma_r + j\Gamma_i = \frac{(Z_L - Z_o)}{(Z_L + Z_o)}$$

and define the normalized  $Z_L$ :

$z_L = \frac{Z_L}{Z_o}$	
$\Gamma = \frac{z_L - 1}{z_L + 1}$	

### Now relating to $z = r + jx$

- After some algebra, we obtain two eqs.

$$\left(\Gamma_r - \frac{r}{1+r}\right)^2 + \Gamma_i^2 = \left[\frac{1}{1+r}\right]^2 \quad \text{Circles of } r$$

$$[\Gamma_r - 1]^2 + \left[\Gamma_i - \frac{1}{x}\right]^2 = \left[\frac{1}{x}\right]^2 \quad \text{Circles of } x$$

- Similar to general equation of a circle of radius  $a$ , center at  $(h,k)$

$$(x - h)^2 + (y - k)^2 = a^2$$


### Examples of circles of $r$ and $x$

Center =  $\left(\frac{r}{1+r}, 0\right)$  Radius =  $\left[\frac{1}{1+r}\right]$

Circles of  $r$

Center =  $\left(1, \frac{1}{x}\right)$  Radius =  $\left[\frac{1}{x}\right]$

Circles of  $x$

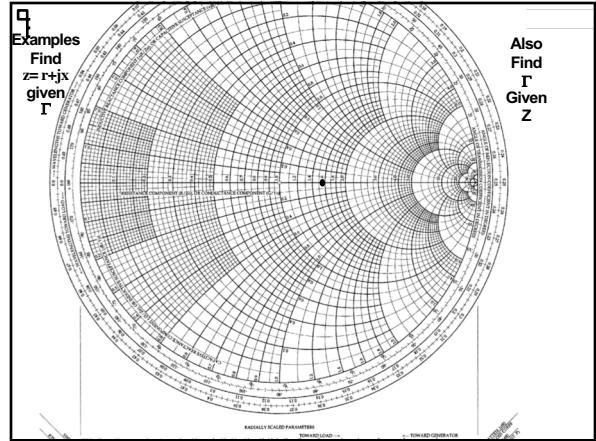

### Examples of circles of $r$ and $x$

Center =  $\left(\frac{r}{1+r}, 0\right)$  Radius =  $\frac{1}{1+r}$

Circles of  $r$

Circles of  $x$

### Find SWR on the SC

- Numerically  $s = r$  on the  $+$ axis of  $\Gamma_r$  in the SC


Proof:

$$\Gamma = \frac{z_L - 1}{z_L + 1} = (\text{when } z = r) = \frac{r - 1}{r + 1}$$

but then  $\Gamma = \Gamma_r + j0 \equiv \frac{s - 1}{s + 1}$

### Moving on the TL on the SmithC

- A lossless TL is represented as a circle of constant radius,  $|\Gamma|$ , or constant  $s$ 
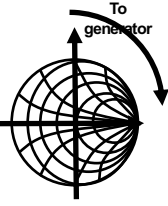
$$\Gamma(l) = \Gamma_L e^{-2j\beta l} = |\Gamma_L| e^{j\theta_L} e^{-2j\beta l}$$
- Moving along the line from the load toward the generator, the phase decrease, therefore, in the SC equals to moves clockwisely.
 

### One-turn on the Smith Chart

- One turn (360°) around the SC = to  $\lambda/2$  because in the formula below, if you substitute length for half-wavelength, the phase changes by  $2\pi$ , which is one turn.
 
$$\Gamma(l) = \Gamma_L e^{-2j\beta l}$$
- Find the point in the SC where  $\Gamma = +1, -1, j, -j, 0, 0.5$
- What is  $r$  and  $x$  for each case?

### Fun facts : Admittance in the SC

- The admittance,  $y = Y_l / Y_o$  where  $Y_o = 1/Z_o$ , can be found by moving  $1/2$  turn ( $\lambda/4$ ) on the TL circle
 
$$2\beta l = 2 \frac{2\pi}{\lambda} \left( \frac{\lambda}{4} \right) = \pi$$


$$z(l=0) = \frac{Z_L}{Z_o} = \frac{1}{Z_o} \frac{V^+}{V^-} \frac{(1 + \Gamma e^{2j\beta l})}{(1 - \Gamma e^{2j\beta l})} = \frac{1 + \Gamma e^{2j\beta l}}{1 - \Gamma e^{2j\beta l}} = \frac{1 + \Gamma e^{2j0}}{1 - \Gamma e^{2j0}} = \frac{1 + \Gamma}{1 - \Gamma}$$

$$z(l = \lambda/4) = \frac{1 + \Gamma e^{j\pi}}{1 - \Gamma e^{j\pi}} = \frac{1 + \Gamma(-1)}{1 - \Gamma(-1)} = \frac{1 - \Gamma}{1 + \Gamma}$$

$$y(l=0) = \left( \frac{1}{Y_o} \right) \frac{V^+}{V^-} \frac{(1 - \Gamma e^{2j\beta l})}{(1 + \Gamma e^{2j\beta l})} = \frac{1 - \Gamma e^{j0}}{1 + \Gamma e^{j0}} = \frac{1 - \Gamma}{1 + \Gamma}$$

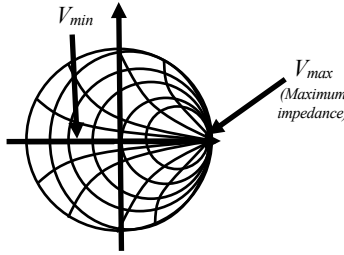
### $V_{max}$ and $V_{min}$ on the SmithC

- The  $\Gamma_r$  +axis, where  $r > 0$  corresponds to  $V_{max}$
- The  $\Gamma_r$  -axis, where  $r < 0$  corresponds to  $V_{min}$


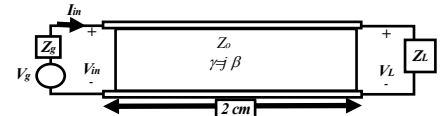
### Exercise: using S.C.

- A 2cm lossless TL has  $V_g = 10$  V<sub>rms</sub>,  $Z_g = 60 \Omega$ ,  $Z_L = 100 + j80 \Omega$  and  $Z_o = 40 \Omega$ ,  $\lambda = 10$ cm. find: the input impedance  $Z_{in}$ , the sending-end Voltage  $V_{in}$ .




$$z_L = \frac{100 + j80}{40} = 2.5 + j2$$

$$l_g = .2\lambda$$

$$\Gamma_L = 0.622 \angle 23.5^\circ$$

$$\Gamma(2cm) = 0.622 \angle -120^\circ$$

- Load is at  $.2179\lambda$  @ S.C.
- Move  $.2\lambda$  and arrive to  $.4179\lambda$ .
- Read  $z_{in} = .3 - j.55$
- $Z_{in} = 12 - j22 \Omega$
- $y_{in} = .76 - j1.4 \Omega$
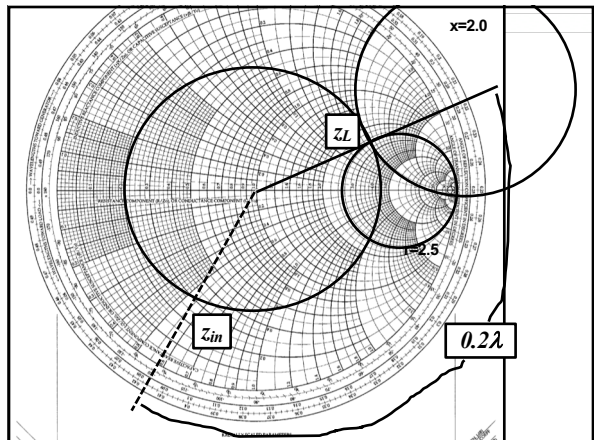
$$V_{in} = \frac{V_g Z_{in}}{Z_{in} + Z_g} = 3.32 \angle -0.775 \text{ rad}$$


### Exercise: cont....using S.C.

- A 2cm lossless TL has  $V_g=10$  V<sub>rms</sub>,  $Z_g=60 \Omega$ ,  $Z_L=100+j80 \Omega$  and  $Z_o=40 \Omega$ ,  $\lambda=10$ cm . find: the input impedance  $Z_{in}$ , the sending-end Voltage  $V_{in}$ .


$z_L = 2.5 + j2$      $l_\lambda = .2\lambda$      $\Gamma_L = 0.622 \angle 23.5^\circ$

- Distance from the load (.2179 $\lambda$ ) to the nearest minimum & max
- Move to horizontal axis toward the generator and arrive to .5 $\lambda$  ( $V_{max}$ ) and to .25 $\lambda$  for the  $V_{min}$ .
- Distance to min =  $.5 - .2179 = .282\lambda$
- Distance to 2<sup>nd</sup> voltage maximum is  $.282\lambda + .25\lambda = .532\lambda$  See drawing
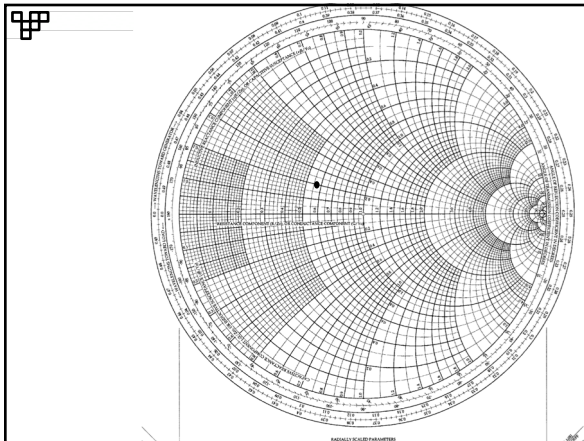
### Exercise : using formulas

- A 2cm lossless TL has  $V_g=10$  V<sub>rms</sub>,  $Z_g=60 \Omega$ ,  $Z_L=100+j80 \Omega$  and  $Z_o=40 \Omega$ ,  $\lambda=10$ cm . find: the input impedance  $Z_{in}$ , the sending-end Voltage  $V_{in}$ .

$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o} = 0.62 \angle 23.4^\circ$   
 $Z_{in} = Z(2cm) = 40 \left( \frac{100 + j80}{40} + j40 \tan \frac{2\pi}{5} \right)$   
 $Z_{in} = 12.2 - j21.17 \Omega$   
 $\Gamma(2cm) = \Gamma_L e^{-2j\beta}$   
 $\Gamma = \Gamma_L \angle -144^\circ = 0.62 \angle -120.6^\circ$   
**Voltage Divider:**  $V_{in} = \frac{V_g Z_{in}}{Z_{in} + Z_g} = 3.30 \angle -0.766 \text{ rad}$



### Another example:

- A 26cm lossless TL is connected to load  $Z_L=36-j44 \Omega$  and  $Z_o=100 \Omega$ ,  $\lambda=10$ cm . find: the input impedance  $Z_{in}$ .

$z_L = .36 - j.44$      $l_\lambda = 2.6\lambda = 5(.5\lambda) + .1\lambda$      $\Gamma_L = 0.54 \angle -127^\circ$

- Load is at  $.427\lambda$  @ S.C.
- Move  $.1\lambda$  and arrive to  $.527\lambda$  ( $=.027\lambda$ )
- Read  $z_{in} = .31 + j.16$
- $Z_{in} = 31 + j16 \Omega$
- Distance to first  $V_{max}$ :**  $l_{min} = 0.5\lambda - .427\lambda = 0.028\lambda$
- $l_{max} = 0.028\lambda + .25\lambda = .278\lambda$


### Exercise 11.4

- A 70  $\Omega$  lossless line has  $s=1.6$  and at the load  $\theta_r=300^\circ$ . If the line is  $0.6\lambda$  long, obtain  $\Gamma$ ,  $Z_L$ ,  $Z_{in}$  and the distance of the first minimum voltage from the load.

**Answer**  $\Gamma_L = 0.23 \angle 300^\circ$      $\Gamma = \frac{s-1}{s+1}$

$z_L = 1.15 - j.48$      $Z_L = Z_o z_L = 80.5 - j33.6 \Omega$      $z_{in} = 0.68 - j.25$   
 $Z_{in} = 47.6 - j17.5 \Omega$

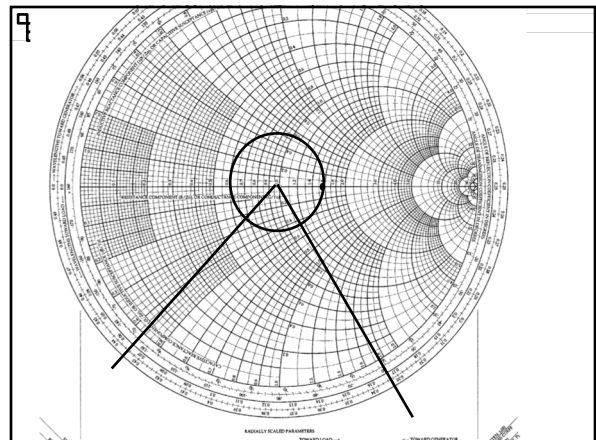- The load is located at:  $.3338\lambda$
- Move to  $.4338 \lambda$  and draw line from center to this place, then read where it crosses you TL circle.
- Distance to  $V_{min}$  in this case,  $l_{min} = .5\lambda - .3338\lambda = .1662\lambda$





## Java Applet : Smith Chart

- [http://education.tn.agilent.com/index.cgi?CONTENT\\_ID=5](http://education.tn.agilent.com/index.cgi?CONTENT_ID=5)



## The end of INEL 4151

- Material extra for (INEL 4155)