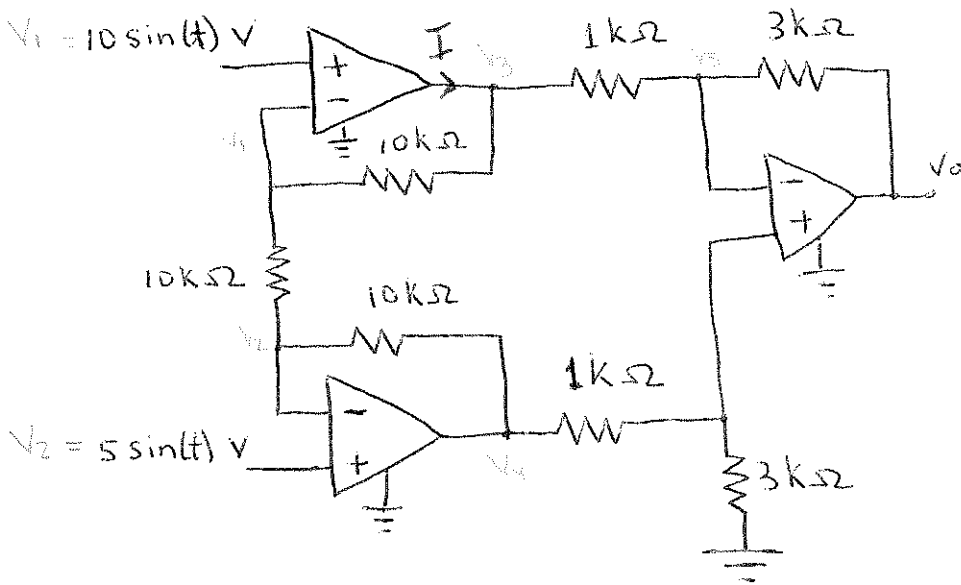


I. Halle V_o en el siguiente circuito: (30 puntos)



Si se asume $I=0$; -2

$$\frac{V_1 - V_3}{10} + \frac{V_2 - V_3}{10} = 0 \quad (6)$$

$$\frac{V_2 - V_1}{10} + \frac{V_2 - V_4}{10} = 0 \quad (6)$$

$$V_5 = \frac{3}{9} V_4 \quad (5)$$

$$\Rightarrow V_3 = 2V_1 - V_2 \quad (1)$$

$$V_4 = 2V_2 - V_1 \quad (1)$$

$$V_3 = 15 \sin(t) \text{ V}$$

$$V_4 = 0 \text{ V}$$

$$\frac{V_3 - V_5}{1} = \frac{V_5 - V_0}{3} \quad (6)$$



$$V_0 = 4V_5 - 3V_3 \quad (1)$$

$$V_0 = 4\left(\frac{3}{9} V_4\right) - 3V_3 = 3(V_4 - V_3) = 3(2V_2 - V_1 - 2V_1 + V_2) \quad (2)$$

$$V_0 = 9(V_2 - V_1) = 9(5 \sin(t) - 10 \sin(t)) \text{ V}$$

$$V_0 = -45 \sin(t) \text{ V} \quad (2)$$

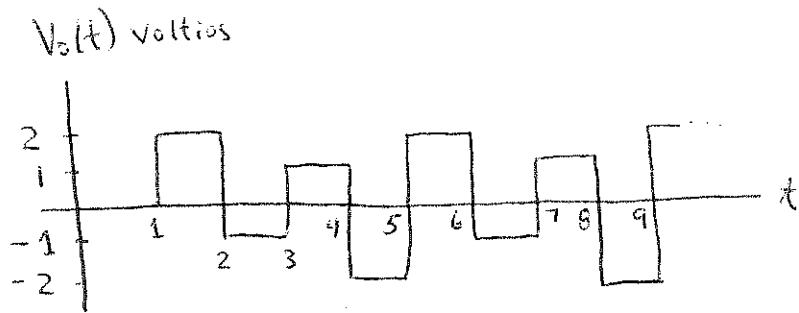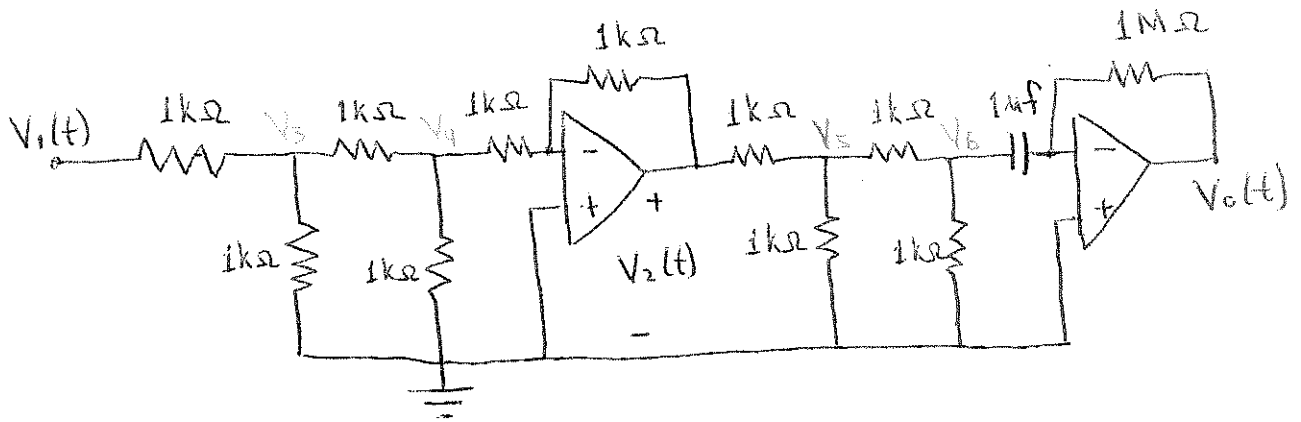II. Dado la gráfica de salida de $V_0(t)$, determine gráficamente $V_1(t)$ y $V_2(t)$. (25 puntos)



$$\begin{cases} \textcircled{3} \frac{V_3 - V_1}{1k} + \frac{V_3}{1k} + \frac{V_3 - V_4}{1k} = 0 \Rightarrow 3V_3 - V_1 - V_4 = 0 \quad \textcircled{1} \\ \textcircled{3} \frac{V_4 - V_3}{1k} + \frac{V_4}{1k} + \frac{V_4}{1k} = 0 \Rightarrow 3V_4 = V_3 \quad \textcircled{1} \end{cases} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} V_4 = \frac{V_1}{8} = -V_2$$

$$\textcircled{3} \frac{V_5 - V_2}{1k} + \frac{V_5}{1k} + \frac{V_5 - V_6}{1k} = 0 \Rightarrow 3V_5 - V_2 - V_6 = 0 \quad \textcircled{1}$$

$$\textcircled{3} \frac{V_6 - V_5}{1k} + \frac{V_6}{1k} + 1\mu f \frac{dV_6}{dt} = 0 \Rightarrow 1ms \frac{dV_6}{dt} + 2V_6 - V_5 = 0 \quad \textcircled{1}$$

$$\textcircled{3} \left[1\mu f \frac{dV_6}{dt} = \frac{-V_6}{1M\Omega} \right]^* \Rightarrow \frac{dV_6}{dt} = \frac{-V_6}{1000} \Rightarrow \left[V_6 = -\int V_0 dt \right]^* \textcircled{1}$$


$$V_5 = 1ms \dot{V}_6 + 2V_6$$

$$\Rightarrow 3(1ms \dot{V}_6 + 2V_6) - V_6 = V_2 = 3ms \dot{V}_6 + 5V_6$$

$$V_2(t) = -\frac{3V_0}{1000} - 5 \int V_0 dt \quad \textcircled{4}$$

$$V_1(t) = -8V_2(t) \quad \textcircled{1}$$


III. Halle V_o . (20 puntos)

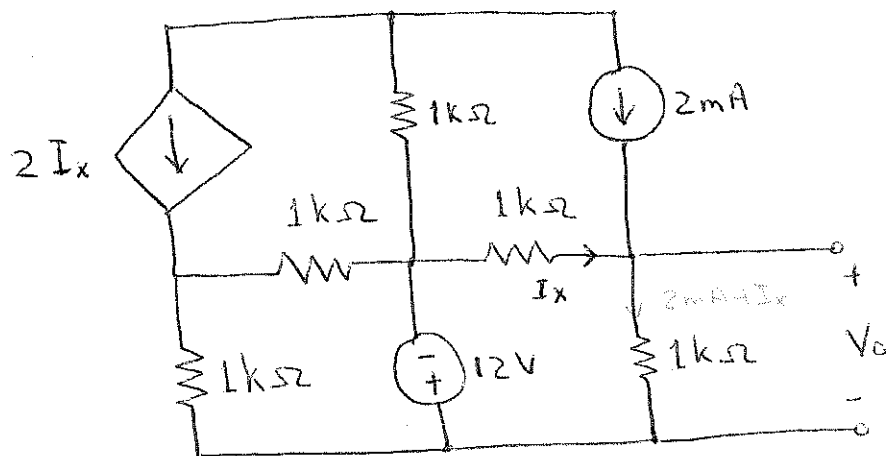

Apagar fuente dependiente: ~~-20~~
-10


Superposición:

I.

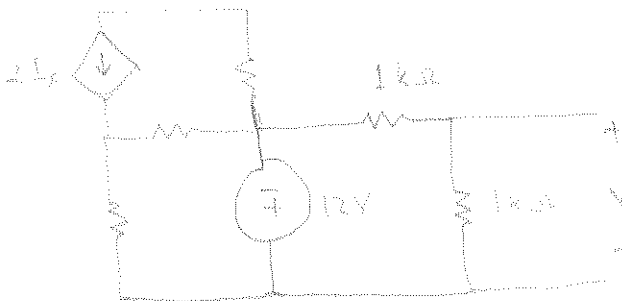

$$V_{01} = -12 \left(\frac{1}{2} \right) V = -6V \quad (8)$$

II.

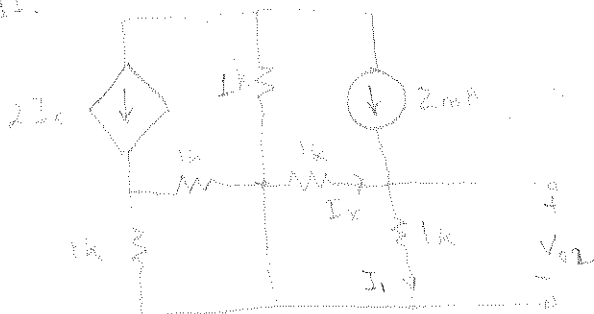

$$I_1 = 2mA + I_x$$

$$-I_x = 2mA + I_x$$

$$V_{02} = 1kI_1 = -1kI_x \Rightarrow I_x = -1mA$$

$$V_{02} = 1V \quad (10)$$



$$\Rightarrow V_o = V_{01} + V_{02} = -5V \quad (2)$$

Método 2

$$\left. \begin{aligned} \text{KVL: } 12 + (2mA + I_x)1k\Omega + I_x(1k\Omega) &= 0 \\ 14 + 2kI_x &= 0 \\ I_x &= -7mA \end{aligned} \right\} (10)$$

$$\therefore V_o = 1k\Omega (2mA + I_x) = -5V \quad (10)$$

IV. Halle V_o . (25 puntos)

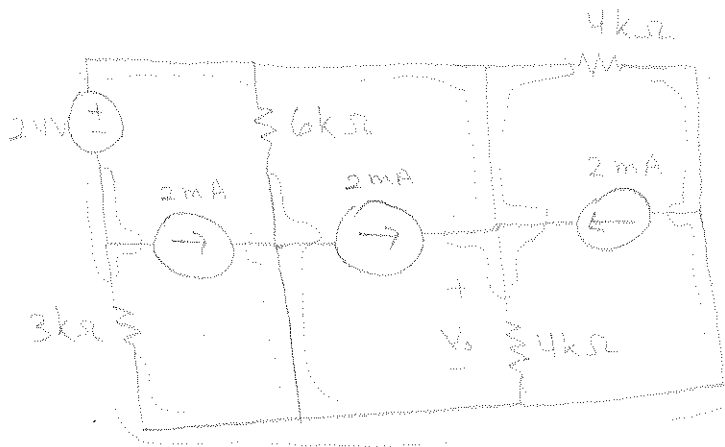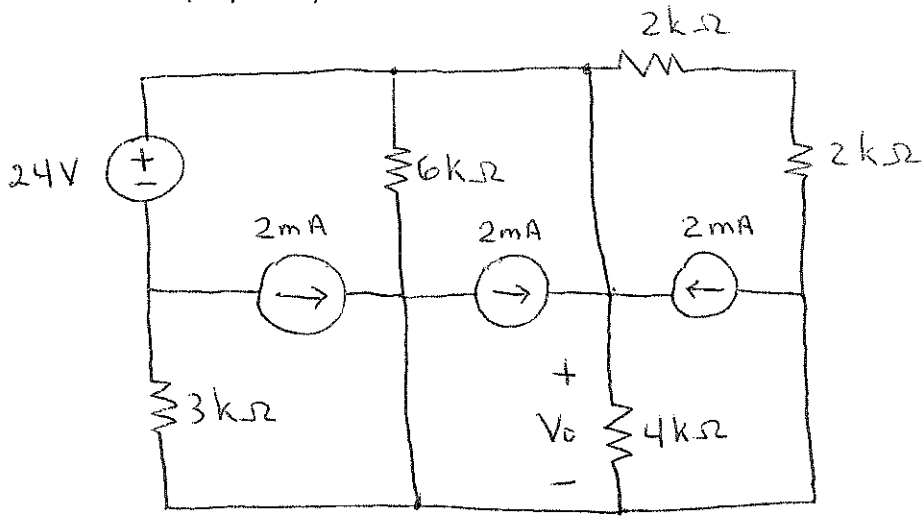


$$\frac{1}{R_p} = \frac{1}{4k} + \frac{1}{4k} + \frac{1}{2k} = \frac{1}{2k} + \frac{1}{2k}$$

$$\frac{1}{R_p} = \frac{3}{12k\Omega} = \frac{2}{6k\Omega}$$

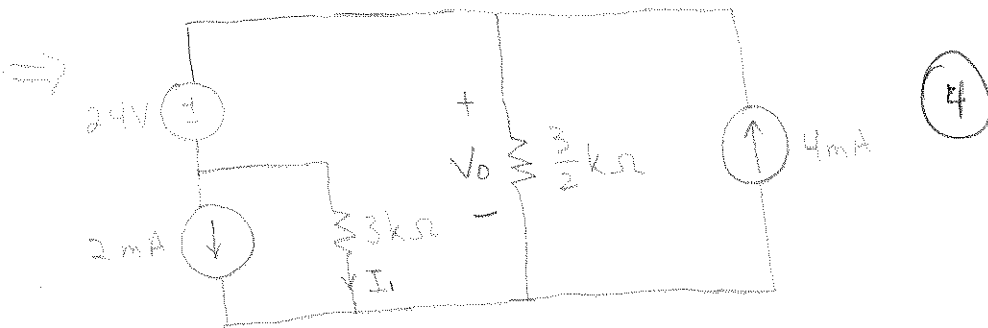(5)

$$\Rightarrow R_p = \frac{3}{2} k\Omega$$



(4)

Metodo I:

(5) KCL: $I_1 + 2mA + \frac{V_o}{\frac{3}{2}k\Omega} = 4mA \Rightarrow \frac{3}{2}kI_1 + V_o = 3V$

(6) KVL: $V_o - 24 - 3kI_1 = 0$

$$\Rightarrow \frac{3}{2}k \left(\frac{V_o - 24}{3k} \right) + V_o = 3V$$


$$V_o - 24V + 2V_o = 6V$$

$$3V_o = 30V$$

(4)

$$V_o = 10V$$

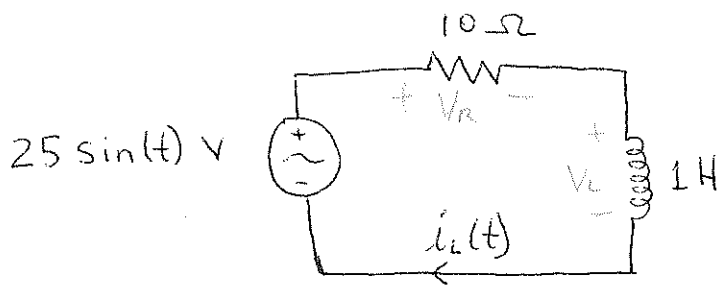- V. Dado el circuito, halle la ecuación que gobierna el comportamiento de la corriente haciendo un KVL.
(Bono de 5 puntos)



$$V_R = 10 i_L(t)$$

$$V_L = 1H \frac{di_L(t)}{dt}$$

$$\boxed{25 \sin(t) = 1H \frac{di_L(t)}{dt} + 10 i_L(t)}$$

(1) (2) (2)